

February 2010

US \$ 7.95 - Canada \$ 7.95

eLektor

www.elektor.com



PFC CRACKDOWN

Lamp power factor revealed

YOU'VE GOT THE POWER

Hands on testing, controlling, cooling, designing

6 NEW PROJECTS



Battery Capacity Checker




WinAmp Controller



No-Howl PA System



TTL Bluetooth Dongle

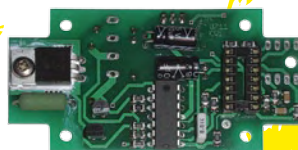

Motorbike Chain Oiler



2.4 GHz WiFi Band analyzer



0 74470 24965 8

WIRELESS MADE SIMPLE[®]

QUICKLY AND COST-EFFECTIVELY MAKE YOUR PRODUCT WIRELESS

RF MODULES

LOW COST • LONG RANGE



**TRANSMITTERS • RECEIVERS
• TRANSCEIVERS**

INTEGRATED CIRCUITS

ENCODERS • DECODERS • TRANSCODERS



**COMMAND • CONTROL
• KEYLESS ENTRY**

OEM PRODUCTS

EASILY CUSTOMIZED



ANTENNAS

FROM WHIPS TO CHIPS



Featured Products:

GPS Modules

GPS MADE SIMPLE[™]

- RXM-GPS-SR
- RXM-GPS-SG

- High Performance
- Low Cost
- Ultra Compact
- High Sensitivity
- Easy Serial Interface
- Low Power Consumption



These easily applied GPS modules blend high performance, low power and cost effectiveness into a single, compact, SMD package. The SiRFstar III low-power chipset minimizes power consumption and provides exceptional sensitivity. The receivers feature an on-board LNA and SAW filter with a choice of an integrated or external antenna. No other RF components are needed and the module's standard NMEA data output makes integration easy.

Development Systems

THE FAST TRACK TO WIRELESS SUCCESS

Linx development systems contain everything needed to evaluate the Linx product of your choice and implement it in record time.



LINX[®]
TECHNOLOGIES

WIRELESS MADE SIMPLE

800-736-6677

159 Ort Lane
Merlin, OR 97532

linxtechnologies.com

ARE YOU REALLY SURE YOU HAVE THE BEST TOOL?



“A couple of years back when I bought my EasyPIC4 and got to know it I was convinced MikroElektronika made the very best all-round development hardware. The EasyPIC6 has just strengthened that opinion.” *Roman Black*



EasyPIC6 is a development system for 8-, 14-, 18-, 20-, 28- and 40- pin PIC microcontroller applications development and testing. The **mikroICD** (Hardware In-circuit Debugger) enables very efficient step by step debugging. Examples in **C**, **BASIC** and **Pascal** are provided with the board.

When surveyed, 93.6% of customers would recommend our products to their friends



Order EasyPIC6 Development System right now and considerably reduce your prototype development time.

Power — not brawn

'Power' was set as the theme of the month and powerful it will be. For many electronics enthusiasts, designing power supplies is a necessary evil. And when the power level lies in the ampère range instead of the milliampère range, quite a few designers find themselves in unknown territory. However, this can be remedied by new highly integrated chips, ready-made driver modules, and clever reference designs. In addition, many tools are available on the Web, and most of them are free. In this the February 2010 issue of *Elektor* we provide get-you-going information on the subject (or keep-you-going?) in two articles, *Stable Starting Points* (page 20) and *Torture Rack* (page 23). To which I should hasten to add *Tailored Cooling* (page 14) because sadly some of the power you've paid for goes to waste as heat and we should find ways to deal with that!

Also on power wastage, while modern lamp technology claims to reduce electrical power consumption besides making us sleep better and feel less troubled with eco concerns, it also prompts a critical look at PFC (power factor correction). A non issue with the traditional incandescent light bulbs rapidly being phased out, PFC now looks like area where technology is not, or not yet, making a contribution to power economies — in short, a lower electricity bill. We did some research on off the shelf lamps claimed as 'all the latest' and you can read the results on page 60. *Femto OS* on page 38 proves that a lot of computing power can be packed in just a few kilobytes, just as we did in the old days when RAM was scarce & costly and programming required thinking instead of just pizzas, beer and broadband DSL. It should also stimulate many multitasking OS writers and suppliers to have a more than critical look at the size of their final product as it's often gargantuan compared to the application itself. WLAN routers and WiFi devices are now firmly established in the 2.4 GHz ISM band, all clamoring for bandwidth to operate properly. Our *2.4 GHz Bandalyzer* (page 54) will not just tell you just how busy the band is in your area, but also the where/what/who about the main interference sources your router should avoid by clever channel hopping now and then.

Jan Buiting
Editor



6 Colophon

Corporate information on Elektor magazine.

8 Mailbox

Monthly pick of letters to the Editor.

10 News & New Products

A monthly roundup of all the latest in electronics land.

14 Tailored Cooling

For heatsink dimensioning, help is just around the corner.

23 Torture Rack

PSU testing the dynamic way, but simple too.

24 Battery Checker

Handles up to ten cells at up to 10 amps.

30 Winamp Controller

With USB and a motor driven slide potentiometer.

40 Motorbike Chain Oiler with PIC

An ingenious circuit for automatic chain lubrication.

38 Femto OS

The world's tiniest multitasking operating system?

43 The Loudest!


Tweaking the Portable PA for best performance.

44 PCB design — it's not witchcraft!

Tricks and tips on board design from the Elektor lab.

46 Capacitors to the rescue

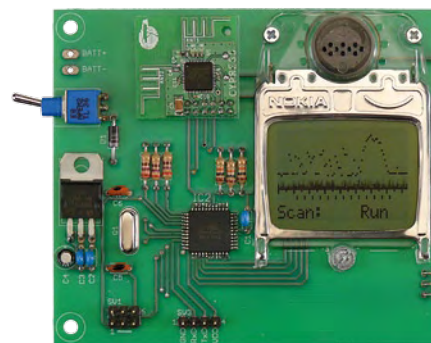The noble art of decoupling to prevent oscillation.



CONTENTS

Volume 2
February 2010
no. 14



24 Battery Checker

This intelligent battery checker will determine the state of cells so that an optimal selection can be made from them to form a pack. It is essential to measure not only the capacity of the cells, but also their internal resistance.

38 Femto OS

Here's a minuscule multitasking operating system that's currently ported to 44 of Atmel's AVR microcontrollers. It is open source and licensed under GPLv3. Femto OS is different! For one, it's extremely economical with RAM and flash memory.



54 The 2.4 GHz Bandalyzer

With this handy portable scanner, you can quickly and easily see which WiFi and WLAN frequencies are being used in your area and which channels you should avoid for your own wireless network links.



60 Blinded by the Light?

The latest lamp technologies are claimed to save huge amounts of power but has their power factor correction (PFC) been overlooked or is it a simple matter of poor standards and sluggish industry regulation again? We investigate.

48 Loud and Clear

A portable PA system with feedback suppression.

54 The 2.4 GHz Bandalyzer

Scan the WiFi band for WLAN activity and interference sources.

59 Design Tips

Computer digital audio interface

60 Blinded by the Light?

Lamp power factor correction investigated!

64 The ATM18 Radio Computer

FM, AM, RDS, all crammed into one chip!

70 TTL Bluetooth Dongle

Wireless data communications was never easier.

74 Gerard's Columns

Parts Selection

76 Hexadoku

Our monthly puzzle with an electronics touch.

77 Retronics: Elektor Teletext Decoder (1981)

Regular feature on electronics 'odd & ancient'.

84 Coming Attractions

Next month in Elektor magazine.

Elektor International Media provides a multimedia and interactive platform for everyone interested in electronics. From professionals passionate about their work to enthusiasts with professional ambitions. From beginner to diehard, from student to lecturer. Information, education, inspiration and entertainment. Analog and digital; practical and theoretical; software and hardware.



The main graphic shows a blue globe with a grid pattern. Overlaid on the globe are the flags of six countries: the United Kingdom, the Netherlands, Germany, France, the United States, and Spain. To the left of the globe is a large cover of the February 2010 issue of Elektor magazine. The cover features a hammer hitting a light bulb and the headline 'PFC CRACKDOWN Lamp power factor revealed'. Other headlines include 'YOU'VE GOT THE POWER', 'Hands on testing, controlling, cooling, designing', and '6 NEW PROJECTS'. Below the main cover are three smaller covers of the magazine, each with different headlines.

**ANALOG • DIGITAL
MICROCONTROLLERS & EMBEDDED
AUDIO • TEST & MEASUREMENT**

No. 14, FEBRUARY 2010

ISSN 1947-3753

Elektor aims at inspiring people to master electronics at any personal level by presenting construction projects and spotting developments in electronics and information technology.

Elektor (ISSN 1947-3753) is published monthly (except for one issue in July/August) at \$39.95 per year, Canada add \$11.00 per year;
by Elektor International Media LLC,
4 Park Street, Vernon, CT 06066, USA.
Phone: 860-875-2199, Fax: 860-871-0411.
www.elektor.com

Elektor is also published in French, Spanish, German and Dutch. Together with franchised editions the magazine is on circulation in more than 50 countries.

International Editor:
Wisse Hettinga (w.hettinga@elektor.com)

Editor: Jan Buiting (editor@elektor.com)

International editorial staff: Harry Baggen, Thijs Beckers, Eduardo Corral, Ernst Krempelsauer, Jens Nickel, Clemens Valens

Design staff: Antoine Authier (Head), Ton Giesberts, Luc Lemmens, Daniel Rodrigues, Jan Visser, Christian Vossen

Graphic design / DTP: Giel Dols, Mart Schroijen

Publisher: Hugo Van haecke
(h.vanhaecke@elektor.com)

Marketing: Carlo van Nistelrooy

Customer Services: sales@elektor.com

Subscriptions:
Elektor US, 4 Park Street, Vernon, CT 06066, USA.
Phone: 860-875-2199, Fax: 860-871-0411
Internet: www.elektor.com
E-mail: subscriptionsus@elektor.com

Elektor Tools for PCB Production

➔ PCB-DIY All the Way

\$150 DISCOUNT
with your combined order of the stencil machine and pick & place tool!

It's clear that a good set of tools is required for PCB production and SMD component stuffing. With the Elektor stencil machine you get the solder paste accurately positioned, and the pick & place device is ideal for manual fitting of SMT components on circuit boards.




Elektor Pick & Place Tool

For manual fitting of SMT components on circuit boards

- Adjustable anti-static arm rest for stable positioning of components
- Anti-static component storage system
- Magnetic supports for PCB
- Suction tool with different pickup needle sizes
- Maintenance-free vacuum pump
- Kit of parts for home assembly, with clear manual

450 x 350 x 100 mm | 2.5 kg | \$935.00*

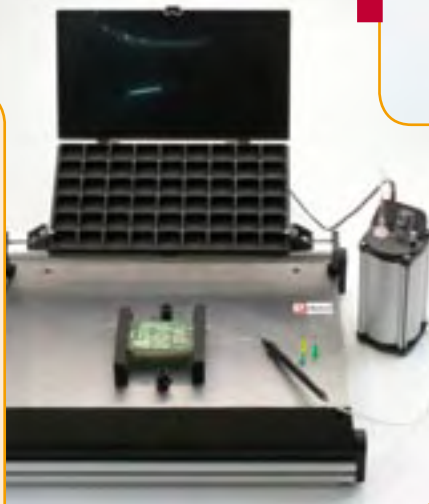*Prices including VAT (EU destinations), excluding shipping.



elektor

Elektor Stencil Machine

Use a stencil for accurate applying of solder paste on circuit boards

- Accurate X,Y alignment of PCB frame
- For single and double sided PCBs and single-sided populated PCBs
- Magnetic standoff supports for PCB
- Rapid and secure fixing of stencil
- Stencils do not need fixing holes
- Maintenance-free and robust aluminum frame
- Kit of parts for home assembly, with clear manual

450 x 300 x 60 mm | 5.5 kg | \$645.00 *



Further information and ordering at
www.elektor.com/pcbtools

Head Office:

Elektor International Media b.v.
PO Box 11 NL-6114-ZG Susteren The Netherlands
Telephone: (+31) 46 4389444. Fax: (+31) 46 4370161

US Advertising:

Strategic Media Marketing, Peter Wostrel,
1187 Washington St., Gloucester MA 01930 USA.
Phone: 978-281-7708, Fax: 978-281-7706
E-mail: peter@smmarketing.us
Advertising rates and terms available on request.

Copyright Notice


The circuits described in this magazine are for domestic use only. All drawings, photographs, printed circuit board layouts, programmed integrated circuits, disks, CD-ROMs, DVDs, software carriers and article texts published in our books and magazines (other than third-party advertisements) are copyright Elektor International Media b.v. and may not be reproduced or transmitted in any form or by any means, including photocopying, scanning and recording, in whole or in part without prior written permission from the Publisher. Such written permission must also be obtained before any part of this publication is stored in a retrieval system of any nature. Patent protection may exist in respect of circuits, devices, components etc. described in this magazine. The Publisher does

not accept responsibility for failing to identify such patent(s) or other protection. The submission of designs or articles implies permission to the Publisher to alter the text and design, and to use the contents in other Elektor International Media publications and activities. The Publisher cannot guarantee to return any material submitted.

Disclaimer

Prices and descriptions of publication-related items subject to change. Errors and omissions excluded.

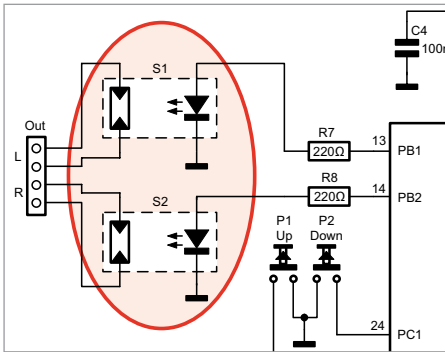© Elektor International Media b.v. 2010 Printed in the USA



AVR, dB and LDR collide at D/A Junction

Elektor November 2009, page 43, ref. 080654

Dear Sir — I hesitate to imply any sort of criticism of your excellent organ, but I must comment on the recent article “AVR, dB and LDR Collide” by Daniel Rodrigues. Daniel is very critical of a design using a light dependent resistor (LDR) in a digitally controlled volume control. The basis of his criticism is the resistive range of an LDR was only 50 to 2000 ohm. In fact there are plenty of LDRs available with dark resistance of up to 25 megohm which is altogether a different kettle of fish. In this sort of application an LDR could be used very effectively as one leg of a potential divider, to replace a conventional potentiometer in a low-level part of the circuit. In some configurations this device can be made to approximate a log-law potentiometer for audio applications. This not only provides a solid-state alternative to a potentiometer, but also makes it easy to create multi-ganged devices controlled by a single voltage source.

It is easy to make a resistive optocoupler by gluing an LED to an LDR and covering the assembly with heat shrink sleeving. Alternatively these devices are available ready made, such as the Silonex NSL32SR3.

On a note of thanks, I always enjoy reading Elektor from cover to cover, and I particularly like the Retronics column.

Paul Lister

Daniel Rodrigues replies: actually, the component Mr. Lister refers to was tested. I did not

mention the component because it's not RoHS compliant (which is not stated in the datasheet though!). It's also slow (taking 10 sec to achieve 25 MΩ), distorts the audio signal and it's not RoHS compliant, containing high amounts of cadmium. So, it's becoming increasingly difficult to find LDRs with a larger resistance range. It may also be worth noting that the circuit as discussed in the article is based on the LDR being inserted in the (low-power) loudspeaker line.

Circuit suggestions for T-Reg (2)

Mailbox, December 2009, page 8.

Dear Editor — I read the letter in December 2009 Elektor from Alexander Voigt with interest. I can add a little to your discussion on failures of valves; I worked on the rebuild of the Colossus computer at Bletchley Park for several years. That machine uses 2,500 valves and we had to replace valves now and then. There are at least two ways that valves can be damaged. The first is called cathode stripping: this is where the anode voltage is applied before the cathode is at working temperature. Because the vacuum in the tube is not perfect, ions can form and fall back onto the cathode and because they are heavy, they knock the coating off the cathode. The second is called cathode poisoning: this is where the cathode is at working temperature but there is no (or little) anode voltage to attract electrons out of the cathode. A cloud of ions forms around the cathode and this eventually leads to contamination of the material which forms the cathode. Thermionic valves in early computers suffered this fate because logic gates are either on or off. If off, then cathode poisoning is possible as no anode current is flowing, often for long periods. I hope this helps. An excellent magazine.

Charles Coultas

Thanks for that Charles and keep up the good work at Bletchley Park.

Suggestions for Retronics

Hi Jan — thanks for a great magazine. You have appealed for new subjects for your

‘Retronics’ series of articles. Here goes:

1) Magnetic Amplifiers and indeed, the whole suite of saturable reactors and oddball miscellaneous transducers. Fascinating devices.

2) The Amplidyne, Metadyne and Magnicon rotary amplifiers. OK, they may originate more from the heavy-power end of the electric-device spectrum but they are especially interesting for sheer ingenuity and the capability of controlling massive amounts of power with such a small magnitude of control current.

3) We take cheap, mass-produced consumer goods for granted but the fact that this is possible rides solely upon the back of advanced sensor/transducer technology. Could you delve into the early days of these devices. Just to kick this one off, have a look at the Petoscope. I think you will be intrigued.

4) I would particularly like to see something on the “might-have-been” devices that never quite got out of the lab. For example, ultra-miniature vacuum-tube ‘chips’ designed using silicon integrated circuit technology, cold-cathode substrate materials (no, I’m not talking about orthodox cold-cathode gas-filled tubes but the elimination of the heater entirely), revolutionary display technologies, even most recently, the abandoned new-concept electron-emission method behind Canon/Toshiba’s flat-screen alternative. I trust this keeps you busy!

Andre Rousseau

The Petoscope and the ‘might-have-beens’ in particular should make excellent reading in Retronics, which I started writing and editing in December 2004 and is currently in its 53rd instalment mostly thanks to the encouragement, hints, equipments, oddball devices and enthusiastic contributions I got from you, the Elektor readership. The same for the subjects Andre has kindly suggested — if anyone can come up with a 700-word article on the items mentioned, or simply his/her favorite vintage equipment or electronics device, do not hesitate to contact me.

Jan Buiting, Editor.

MailBox Terms



- Publication of reader's correspondence is at the discretion of the Editor.
- Viewpoints expressed by correspondents are not necessarily those of the Editor or Publisher.

- Correspondence may be translated or edited for length, clarity and style.
- When replying to Mailbox correspondence, please quote Issue number.
- Please send your MailBox correspondence to:

editor@elektor.com or

Elektor, The Editor,
4 Park Street,
Vernon CT060666, USA.

Are you up for a challenge?

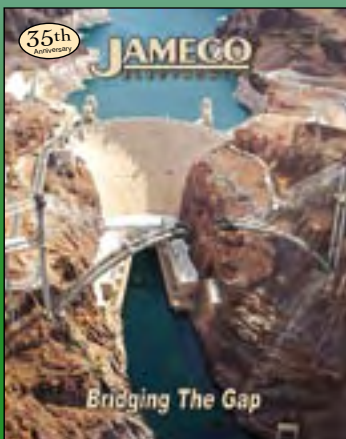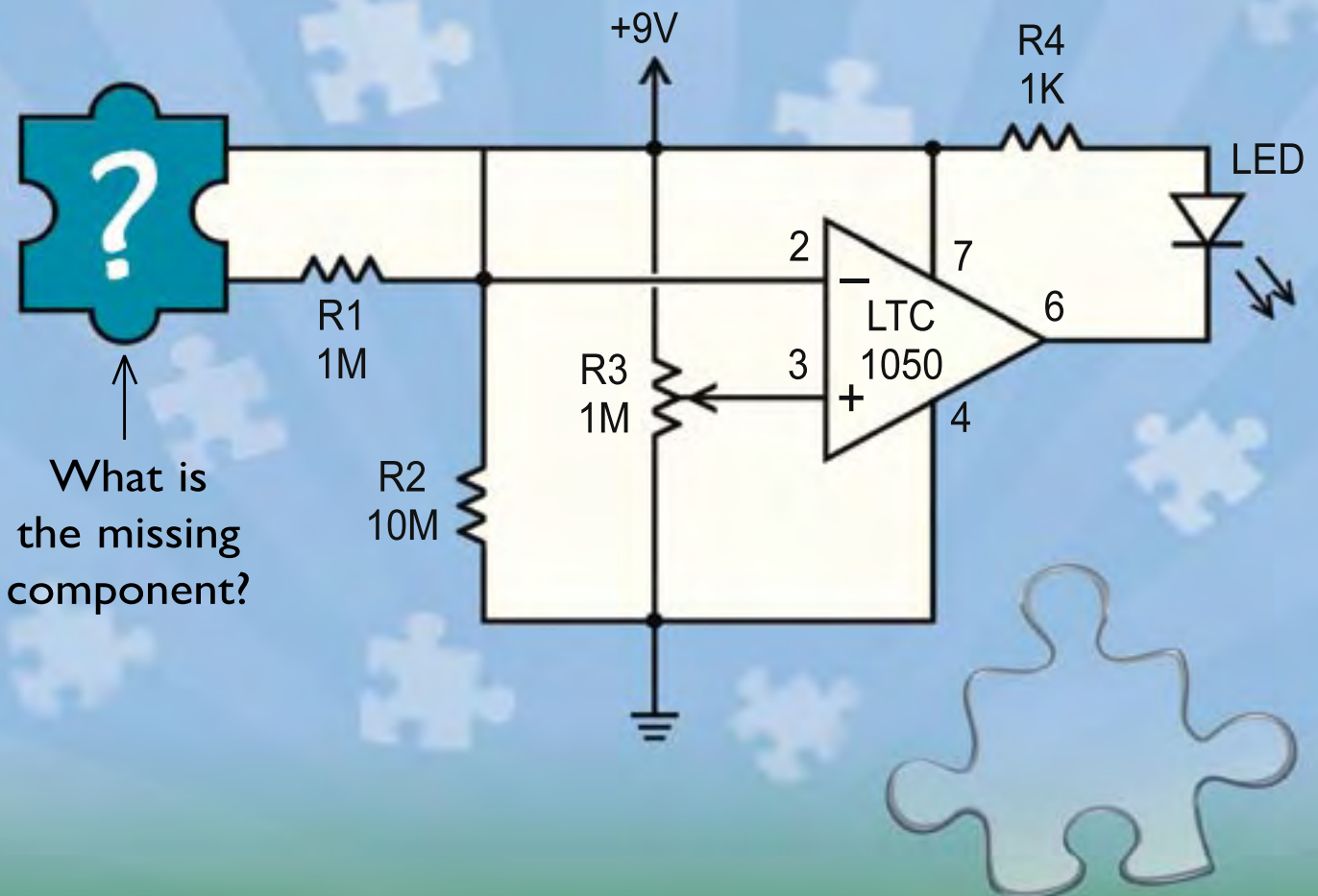

Industry guru Forrest M. Mims III has created yet another stumper. The Ultra Simple Sensors Company assigned its engineering staff to design a circuit that would trigger an LED when a few millimeters of water is present in a basement or boat. What is the water sensor behind the puzzle piece? Go to www.jameco.com/unwrap to see if you are correct and while you are there, sign-up for our free full color catalog.

JAMECO[®]
ELECTRONICS
1-800-831-4242



Osram unveils OLED lighting tiles for high-end applications

Osram Opto Semiconductors has announced the launch of its first OLED lighting tiles, dubbed Orbeos. Orbeos tiles are claimed to have higher energy efficiency than incandescent bulbs or halogen lamps and are suited to applications in the premium segment such as architecture, the hospitality industry, offices, private homes, and shops.

Orbeos OLED tiles have a circular lamp area with a diameter of 80 mm and a thickness of 2.1 mm and weigh 24 grams. With an efficiency of 25 lumens per watt, the tiles exceed the efficiency of halogen lamps. The warm white color temperature matches the warm light of an incandescent lamp.

Orbeos tiles can be switched on and off without delay and are continuously dimmable. The tiles do not emit any ultraviolet or infrared radiation. Their brightness level is typically 1,000 candelas per square meter, with a power input of less than one watt. The rated service life is around 5,000 hours.

OLED tiles open up totally new design possibilities for architects, lighting planners and designers. They can be used to create luminous surfaces, such as ceilings or partitions. Orbeos OLED tiles are the first Osram product on the market. In 2008, the first commercially available 'Early Future' table lamp by renowned lighting designer Ingo Maurer with OLED tiles from OSRAM Opto Semiconductors demonstrated how OLEDs can be used in functional lighting.

According to Osram, the rapid advances of OLEDs in general lighting applications are largely due to the Opal (organic phosphorescent lamps for applications in the lighting market) project.

www.osram-os.com/osram_os/EN/Products/Product_Promotions/OLED_Lighting/index.html (091030-II)

Microchip adds ZigBee RF4CE protocol to XLP platform


Microchip Technology Inc. announced that it has achieved certification for its ZigBee RF4CE platform, which enables the next generation of RF remote controls and consumer electronics. The platform consists of Microchip's nanoWatt XLP PIC microcontrollers, the MRF24J40 IEEE 802.15.4 transceivers and FCC-certified modules, and the ZigBee RF4CE certified protocol stack, which boasts industry's smallest memory footprint. In addition to low power consumption, the compliant PIC XLP microcontrollers offer a wide range of integrated peripherals for capacitive touch sensing, USB, and a host of analogue functions. Free software is also available to enable these peripherals, including mTouch sensing software and Microchip's USB stacks and libraries. Together with its IEEE 802.15.4 compliant 2.4 GHz MRF24J40 transceiver and FCC-certified transceiver modules, Microchip provides a highly efficient, cost-effective platform for implementing the new RF4CE protocol in RF-enabled remote controls and equipment.

Microchip offers a wide range of development tools for PIC XLP microcontrollers, including the free MPLAB IDE, the MPLAB REAL ICE emulation system, the MPLAB ICD 3 in-circuit debugger, the PICkit 3 low-cost debugger/programmer, and Microchip's free C compilers. All of these tools are available at www.microchip.com/get/V6RM.

Microchip's certified RF4CE protocol stack is currently available to Beta program participants, with general availability planned for March. The MRF24J40 transceiver and FCC certified modules are available today, as are the compliant families of PIC XLP microcontrollers.

www.microchip.com/get/JGA5

(091030-III)

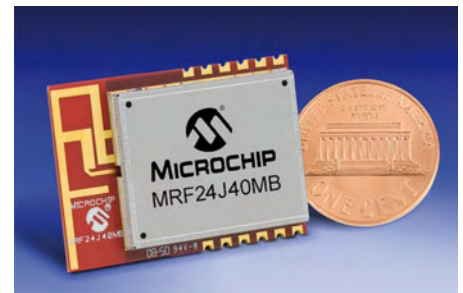

UHF Gen 2 RFID reader boasts advanced features

austriamicrosystems has enlarged their range of market-leading UHF RFID reader ICs for Gen 2 applications with the introduction of the AS3992, which includes advanced features such as programmable dense reader mode (DRM) filters, predistortion, and an increased receiver sensitivity of -86 dBm. The AS3992 UHF Gen 2 reader IC is an integrated analog front end that provides protocol handling for ISO 18000-6C/B 900-MHz RFID reader systems. A variety of built-in programming options make this device suitable for a wide range of UHF RFID applications.

Strengthening the line of Simply Gen 2 reader ICs, the AS3992 also carries on the tradition of "best in class" power consumption. The company claims that the low power consumption of the AS3992 coupled with its new advanced features makes it the most advanced Gen 2 reader IC on the market. Surf to the webpage listed below for a data sheet.

www.austriamicrosystems.com/eng/Products/RF-Products-RFID/RFID/AS3992 (091030-IV)



STMicroelectronics launches MEMS microphone array components

STMicroelectronics, a leading supplier of MEMS devices for consumer and portable applications, has expanded its portfolio with next-generation micro-machined acoustic devices. The company claims that the innovative MEMS microphones, which utilize sensor technology from Omron, will significantly enhance sound quality, reliability, and cost effectiveness in existing and emerging

audio applications such as cell phones, wireless devices, and games with voice input. MEMS microphones have recently emerged to compete with traditional electret condenser microphones (ECMs). Leveraging established high-volume silicon manufacturing processes, micro-machined acoustic devices are cost-competitive with electret microphones while boasting better reliability and robustness. MEMS microphones can also be made smaller than even the most compact ECMs and are less susceptible to mechanical vibration, temperature variations and electromagnetic interference, which is important in cell phones and other devices with audio input, such as notebook computers, video recorders, digital cameras, hearing aids and electronic stethoscopes.



Addressing widespread user demand for better audio performance in mobile devices, the new MEMS microphones enable significant improvement in sound quality and offer additional features such as noise suppression and directional voice pickup, which is useful for identifying and filtering out noise. These features, which are valuable with the increasing use of cell phones in noisy and uncontrollable environments and can perceptibly improve the quality of mobile conversations and conferencing, can be achieved by incorporating several MEMS microphones in a single device. These microphone arrays improve noise cancellation and are made possible with the unique packaging technology used for ST's digital MEMS microphones.

www.st.com/stonline/stappl/cms/press/news/year2009/t2384.htm (091030-V)

Xilinx launches new targeted development kits

Xilinx Inc has launched six new development kits for Virtex-6 and Spartan-6 FPGAs as part of the company's targeted design platforms initiative. The new kits target embedded

processing, DSP, and systems that require high-speed serial connectivity. Xilinx's targeted design platform concept aims to offer customers a validated set of components – including IP cores, reference designs, design environments and other tools – that address most of the design requirements for a particular application area, so that customers can focus their efforts on adding differentiating features.


Each of the new kits is supported by an edition of ISE Design Suite version 11.4, which according to Xilinx yields 25% runtime reduction for Spartan-6 FPGA designs and 30% runtime reduction for Virtex-6 SOC

designs relative to previous releases. The kits include scalable development boards, fully functional domain-specific IP cores, targeted reference designs, complete documentation and cables.

The connectivity development kits contain targeted reference designs that combine hard blocks in the FPGA with Xilinx connectivity IP and IP from Northwest Logic to implement a

fully scalable PCIe to XAUI or Gb Ethernet bridge. The Virtex-6 kit enables users to implement a fully compliant PCIe gen 1 or gen 2 x1, x2, or x4 interface, write and read data from external DDR3 memory, and link

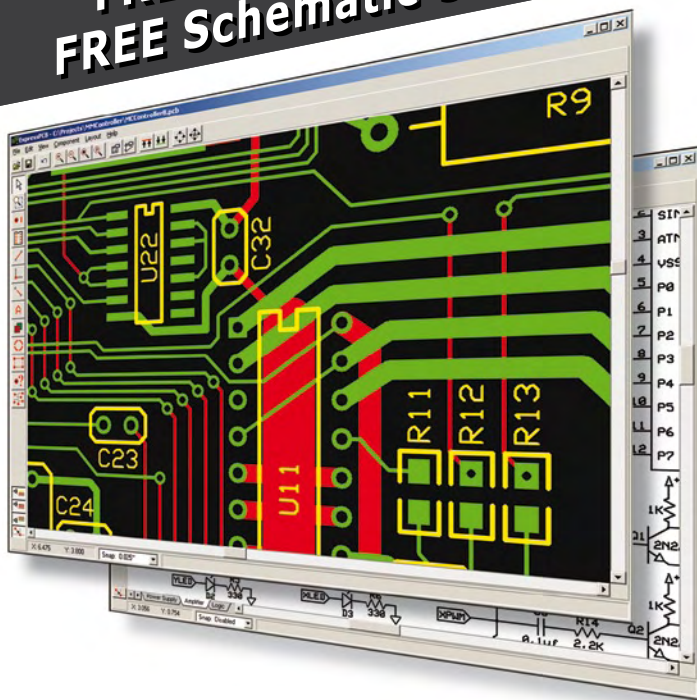For 3
\$51 PCBs
FREE Layout Software!
FREE Schematic Software!



- 01 DOWNLOAD our free CAD software
- 02 DESIGN your two or four layer PC board
- 03 SEND us your design with just a click
- 04 RECEIVE top quality boards in just days

expresspcb.com



to a full XAUI interface within a system environment. The Spartan-6 kit enables users to link fully compliant PCIe gen 1 with Gb Ethernet using a full license of Northwest Logic's DMA engine IP. Both kits enable designers to measure system bandwidth and optimize settings for power and cost savings in a host system environment.

The embedded development kits operate in the environment of ISE Design Suite 11.4 Embedded Edition and let software designers develop and run code or modify example code included with the targeted reference design, which utilizes a fully implemented MicroBlaze 32-bit RISC soft processor core and a complete set of common processor peripherals. Hardware designers can use the base system builder feature to modify the reference design to optimize performance, power or resources.

The digital signal processing development kits enable algorithm and hardware developers to evaluate performance and implementation styles of common digital signal processing elements, which can be used as building blocks in an end application. Each kit has a targeted reference design optimized for Virtex-6 or Spartan-6 FPGAs and utilizes DSP IP and ISE Design Suite System Edition.

www.xilinx.com/products/boards_kits/index.htm
(091030-VI)

New polyphase energy meter ICs boast high accuracy

Analog Devices has expanded its range of energy metering ICs with four new devices that aim to improve the accuracy and performance of commercial, industrial, and residential smart meters. A smart meter accurately measures how much electricity is consumed or generated and communicates with the local utility for power monitoring, billing, and other purposes. ADI's new energy metering ICs enable smart electricity meters to deliver improved customer billing accuracy, advanced power quality monitoring, and reduced operating costs for utility companies.

ADI's new ADE7878, ADE7868, ADE7858, and ADE7854 devices are high-accuracy energy metering ICs designed for poly-phase configurations, including three and four wire, wye and delta services. The ADE7868 and ADE7878 can measure total

Linx and Parallax co-sponsor RF design contest

Linx Technologies Inc. and Parallax Inc. have announced an RF design contest jointly sponsored by the two companies. The contest is based on the new Parallax 433 transceiver board, which incorporates the Linx LT series transceiver. This easy to use, low cost module is capable of sending and receiving serial data wirelessly between microcontrollers or to a PC, enabling the creation of applications limited only by the designer's imagination. Three thousand dollars in cash prizes as well as numerous product giveaways will go to winning designs. Contest registration is underway and open until April 30, 2010. All entries must be received by May 31, 2010.

Visit the website listed below for complete details and contest rules.

www.parallax.com/tabid/821/Default.aspx (091030-I)

active and reactive energy with an accuracy and dynamic range exceeding Class 0.2 specifications for energy meters. The four



new devices are also the first in the industry to measure both reactive energy and active energy with 0.1% accuracy. One of the device can also measure energy at the fundamental frequency only, which is critical for power quality measurements.

The ICs feature 0.1% accuracy for active and reactive energy measurements over a dynamic range of 1000:1, or 0.2% accuracy for active and reactive energy measurements over a dynamic range of 3000:1. The new products also deliver 0.1 percent accuracy over a 1000:1 dynamic range for RMS (root-mean square) current and voltage measurements.

In addition to per-phase and neutral-energy measurements, the ADE7868 and ADE7878 can monitor energy quality parameters such as sag, peak, period, phase angle, and phase sequence. The ADE7868 and ADE7878 can also detect various tamper conditions while continuing to operate properly, thereby reducing field calls and meter troubleshooting time.

www.analog.com/en/analog-to-digital-converters/energy-measurement/products/index.html


(091030-VII)

AC Current Sensors Replace Bulky Transformers

Expanding its popular ISOpro isolation product portfolio, Silicon Laboratories Inc has introduced a next-generation AC current sensor family that replaces traditional current transformers. Silicon Labs' new Si85xx AC current sensors provide up to 5 kVrms of electrical isolation to ensure safety compliance for a variety of critical power delivery systems such as AC/DC switching power supplies, isolated DC/DC supplies, motor control applications, and electronic lighting ballasts.

Si85xx AC current sensors provide a reliable, cost-effective alternative to transformers for power delivery systems. Traditional transformers are large, bulky magnetic components that contribute significant supply losses and have parasitics that complicate system design. Highly integrated ISOpro AC current sensors minimize the need for discrete components for filtering and reset circuitry..

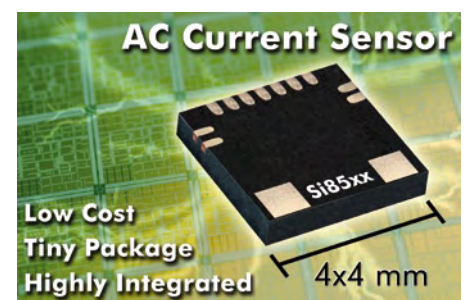With measurement accuracy better than 5%, Si85xx AC current sensors are available in 5 A, 10 A and 20 A versions. The full-scale output signal level is 2.0 V, eliminating the need for an external amplifier. A "ping-pong" output mode enables one sensor to replace two current transformers and associated compo-





nents in full-bridge applications.

Si85xx current sensors enable designers to maximize system efficiency and meet aggressive power budgets for green energy standards. The devices' low resistance (<1.3 milliohms) and small parasitic inductance (<2 nH) help increase power supply efficiency and reduce design effort.

The Si85xx AC sensor family is supported by a complete set of development tools including the Si85xx-EVB evaluation board and the OPENLPPOL-EVB open-loop point-of-load reference design.

www.silabs.com/pr/isolation

(091030-VIII)

Wireless digital monitoring patch moves to trial stage

Toumaz Technology Ltd. has begun clinical trials of its Sensium "digital patch" wireless body monitor by a specialist clinical research team at Imperial College London. The study, which is funded by global health care corporation CareFusion (a recent spin-off from Cardinal Health) and being conducted at St Mary's Hospital, is expected to demonstrate the quality of the physiological data that can be continuously acquired by unobtrusive wireless Sensium-enabled devices. Initial results are expected by the end of December this year. The trial is being conducted in three phases, consisting of an initial phase with non-patient volunteers followed by two patient study groups: patients recovering from surgery and patients with specific medical conditions in the general wards. Volunteers and patient groups participating in the trial will be provided with a wearable Sensium digital patch that can continuously monitor multiple vital signs, including temperature, heart rate and respiration. The

trial focuses on verifying that the physiological data acquired by the digital patch system within a clinical setting is equivalent to the data acquired using current gold-standard monitors used in hospitals – equipment that is often bulky, expensive and stationary and thus impairs patient mobility.

The Sensium digital patch is wireless and unobtrusive, allowing patients to remain ambulatory in hospital while being monitored. This flexibility allows continuous vital sign monitoring to be extended to patients who would not normally be monitored, thereby offering the potential to increase patient safety. The Sensium digital patch is a disposable device with a service life of several days, after which it can be discarded in a suitable waste receptacle.



The digital patch is based on the Toumaz AMx semiconductor IP platform, which enables Sensium wireless technology that is specifically designed for medical body area networks (MBANs) and non-intrusive physiological monitoring. Sensium provides a complete wireless infrastructure that allows health care providers to monitor the human body continuously, wirelessly and intelligently at low cost, with the robustness and medical compliance normally associated with considerably more expensive equipment. Sensium technology has already been validated and CE approved in the form of Toumaz Life Pebble non-disposable body-worn monitoring devices. Powered by thin batteries, body-worn Sensium-enabled monitors deliver clinical-quality data and intelligently integrate it into an electronic medical record via a network based on the Toumaz Nano Sensor Protocol (NSP), a low-power wireless operating and networking system.

www.toumaz.com

(090951-IX)



USB scopes feature 5 GS/s sampling

The PicoScope 6000 series oscilloscopes are claimed to be the first USB scopes to offer a 5 GS/s real-time sampling rate, along with a 350 MHz bandwidth on all four channels. The scopes also have a large 1 gigasample memory buffer.

Other scope functions include a built-in function generator, arbitrary waveform generator, mask limit testing, switchable bandwidth limiting on each channel, and switchable 1-megohm and 50-ohm inputs. This is in addition to the spectrum analysis, advanced triggering and serial decoding that are standard features of Pico USB oscilloscopes.

The scopes connect to any Windows XP, Windows Vista or Windows 7 computer with a USB 2.0 interface. The high sampling rate and bandwidth make these scopes well suited for analog and digital circuit designers, test engineers and installers. For users who want to write their own application to control the scope, Pico provides a software development kit, including example code, free of charge.

Like all Pico Technology PC oscilloscopes, the PicoScope 6000 series makes the most efficient possible use of your money. They are based on the principle that the specialized oscilloscope hardware handles all of the signal conditioning and acquisition tasks, while the user's PC looks after standard functions such as display, disk storage and networking. All of the scope's features are included in the initial price, so there are no expensive upgrades or optional extra modules. Purchasers only need to decide whether to buy the scope on its own or with four 500 MHz compensated x10 probes.

www.picotech.com

(090951-XII)

Tailored Cooling

Online help for heatsink dimensioning

By Harry Baggen (Elektor Netherlands Editorial)

Too many electronic circuits produce a certain amount of heat, which must be dissipated quickly and effectively to ensure proper component operation. All sorts of heatsinks are available for this purpose, but how can you calculate how much cooling you need, and how can you choose the right heatsink? Help is available on a variety of websites.

The saying ‘Where there’s smoke, there’s fire’ most likely originated before the era of electronic circuits, as otherwise we would probably say, ‘Where there’s electronics, there’s heat.’ When electrons flow through an electronic component, they generate heat. This occurs not only as a result of the circuit design, such as with a class A audio amplifier, but also because semiconductor devices never have ideal characteristics. In digital circuits, where the devices only switch between ground potential and the supply voltage, you might expect that no heat dissipation would occur. However, it does occur due to the finite switching times of digital components. If you add to this the fact that nowadays everything must operate at the highest possible clock rate, it’s easy to understand why heat dissipation is not limited to analog circuits.

In order to ensure that analog as well as digital components have a long useful life, it is essential to keep the temperature of the silicon chips within limits. This is usually achieved with the aid of heatsinks, which are available in all sorts and sizes. Unusual solutions, such as heat pipes, Peltier coolers and liquid cooling, can be used in special situations. However, they are rarely used in prototyping, where at most you might use a fan for forced-air cooling.

Heatsink calculations

Heatsink calculations are most often necessary with analog circuits, such as voltage regulators or power amplifier ICs. In such cases, you



usually know how much power must be dissipated and how the circuit will be fitted in an enclosure.

In the same way as with an electrical circuit, heat transfer can be calculated using thermal resistances, thermal differentials and heat flows. The semiconductor chip acts as a thermal source, which produces a certain amount of heat. The thermal differentials are the temperature differences across the various thermal resistances arranged in series. **Figure 1** shows an example of a thermal circuit diagram, which you have probably seen before in electronics books or application notes. The various components of this diagram are described briefly below.

The first thermal resistance ($R_{th\ j-mb}$) is located between the junction of the semiconductor device and the device package, which is called the mounting base or case (c). The next thermal resistance is located between the device case and the heatsink and is designated $R_{th\ mb-h}$. The value of this resistance depends on the material between the case and the heatsink, such as an insulating pad and/or thermal paste. Resistance $R_{th\ h-a}$ represents the interface between the heatsink and the ambient medium (usually air). The diagram also shows a thermal source that supplies a heat flow P .

The value of the first resistance $R_{th\ j-mb}$ is stated on the data sheet of the semiconductor device manufacturer. While you’re looking at the

data sheet, you should also note another value that you will need for heatsink calculations: the maximum allowable semiconductor junction temperature T_j . This value should never be exceeded, as otherwise the life of the device will be shortened dramatically. The value of the thermal resistance $R_{th\ mb-h}$ depends on how the device is mounted. It is fairly low if the semiconductor device is fitted directly to the heatsink. It can be reduced even further by using thermal paste. If insulated mounting of the semiconductor device is necessary, you can choose from a variety of insulating materials, such as silicone rubber or aluminium oxide (alumina). The manufacturers of these materials also specify their thermal resistances. Finally, you have the thermal resistance from the heatsink to the ambient ($R_{th\ h-a}$). You can obtain this value from the data provided by the heatsink manufacturer. The specified value usually applies to a black heatsink with vertical fin orientation. If the heatsink has a natural aluminium finish instead of a black finish, the thermal resistance can be assumed to be around 10% higher. If the heatsink is fitted with the fins horizontal instead of vertical, the thermal resistance can easily be 20 to 40% higher than the stated value. If it is fitted inside an enclosure, the air flow will be reduced considerably, which considerably increases the effective thermal resistance of the heatsink.

When dimensioning a heatsink, you should always base your calculations on the maximum power dissipation of the semiconductor device. For instance, if the maximum voltage over a voltage regulator is 6 V and the maximum current is 1 A, it must be able to dissipate at least 6 W. You should aim to ensure that the temperature of the semiconductor device never exceeds the maximum allowable value, and it is better to stay somewhat below this limit. With a maximum junction temperature of 175 °C and an average ambient temperature of 25 °C, the total temperature difference over all of the thermal resistances must not exceed 150 °C. Given the amount of power to be dissipated, the total thermal resistance can be calculated as

$$R_{th\ total} = \Delta T / P = 150 / 6 = 25\ ^\circ\text{C/W} = 25\ \text{K/W}.$$

If the temperature regulator IC is packaged in a case with a thermal resistance $R_{th\ j-mb}$ of 5 °C/W and the IC is fitted directly to the heatsink without an insulating tab, so that $R_{th\ mb-h}$ is very low (around 0.1–0.2 °C/W), you will need a heatsink with a thermal resistance less than 20 K/W because the thermal resistances are in series and their sum must be no higher than the calculated value. Heatsinks of this sort designed for PCB mounting are readily available.

This completes our overview of the principles of heatsink dimensioning. In practice, you need to be especially careful with the details when large amounts of power must be dissipated. A variety of insulating pads and thermal pastes are available nowadays, and you should pay attention to a variety of properties such as the mounting method, maximum insulation voltage and hold-down force when making your selection.

An excellent article on the subject of cooling electronic components [1] can be found on the Elliot Sound Products website.

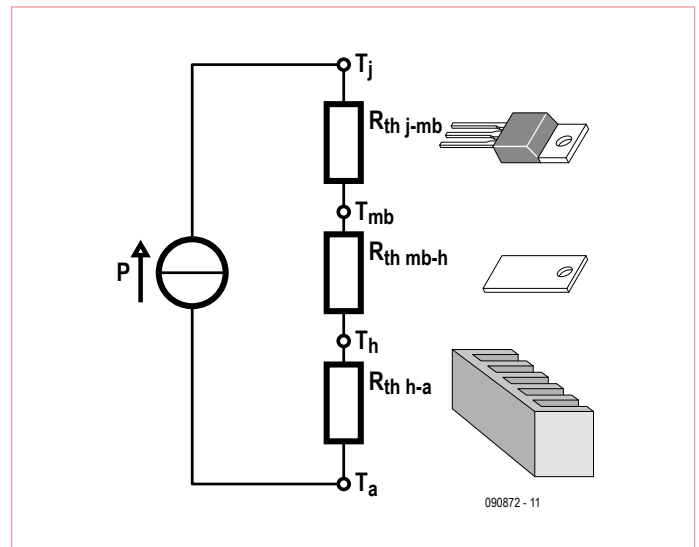


Figure 1. Thermal circuit for heatsink calculations.

Web-based help

There are a lot of websites that can help you with heatsink dimensioning and selection. Most of them have a calculation page where you only need to enter a few basic values. Here we describe a few of the more interesting sites.

Online calculations

The German heatsink manufacturer **Alutronic** provides a handy calculation program called 'Alutronic RthK Calculator', which you can download after registering on the site. There is also an online version of this program, which can be used without registration [2]. The values of the previously described thermal resistances and the amount of power to be dissipated can be set using sliders that are adjusted with the mouse, after which you can immediately see the maximum thermal resistance of the heatsink. The page also shows the maximum temperature of the heatsink, which is important information if the heatsink is mounted where it can be touched.

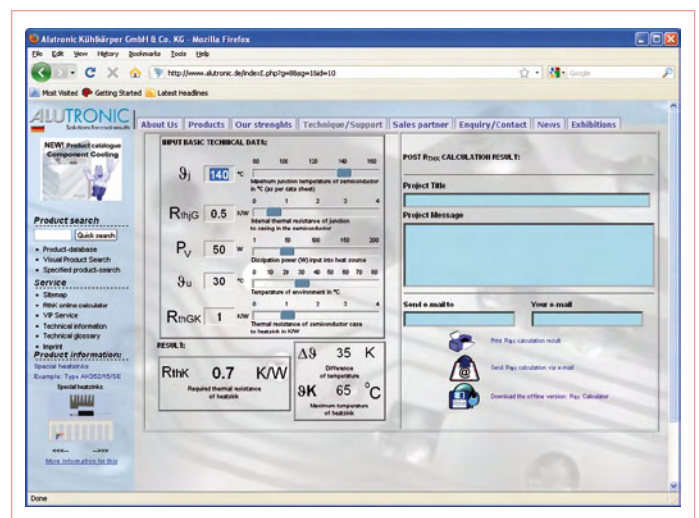


Figure 2. This online program from Alutronic lets you use sliders to set all the necessary values.

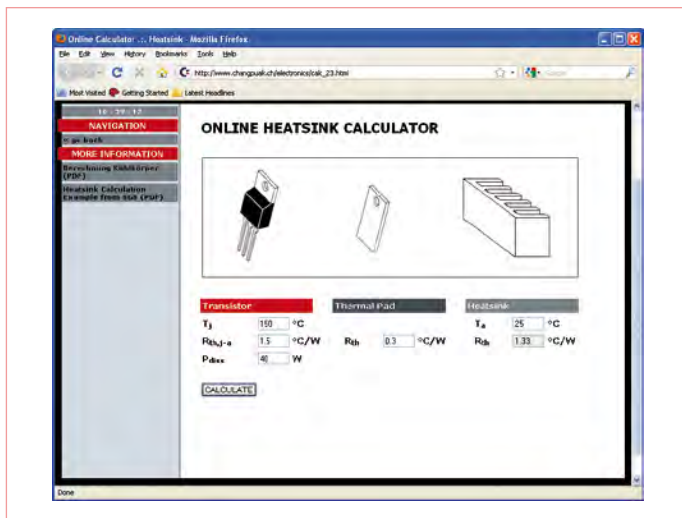


Figure 3. Clear and simple: the online heatsink calculator on the Changpuak website.

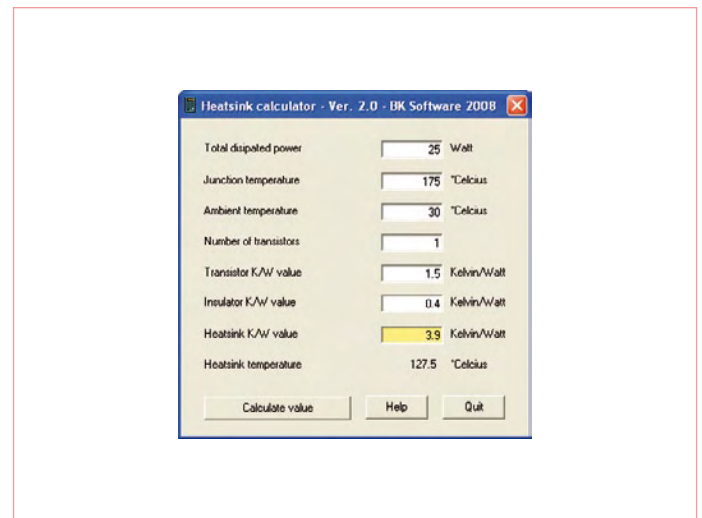


Figure 4. This free program from BK Software is small but very handy.

RS Components [3] also provides an online calculator, in this case a fairly basic version with no graphic frills. It performs the standard calculation using values that must be typed in by the user. After these values are entered, the thermal resistance of the heatsink is shown.

AAVID Thermalloy is a large manufacturer of all sorts of heatsinks and related products. Various aids for heatsink dimensioning are available on this site [4].

The **Daycounter** website offers a large number of programs (more than 50) for all sorts of electronics calculations. It's certainly worth your while to have a look around here. The heatsink calculation program [5] takes the standard approach (comparable to the RS program): you type the various values in the boxes and the program calculates the thermal resistance of the heatsink. As an extra feature, this site also provides some information on the standard values of frequently used heatsinks.

The **Changpuak** site [6], which is run by a Swiss electronics enthusiast with a penchant for Thailand (hence the unusual name), also provides an online heatsink calculation program. It takes the same approach as the previously mentioned sites: you enter several values, and then it calculates the thermal resistance of the heatsink. A few illustrations clearly indicate the components associated with the values to be entered. Like the previously mentioned site, this site also offers other items of interest to electronics enthusiasts.

Stand-alone programs

Professional heatsink calculation programs are usually rather pricey (too expensive for casual use), although they offer more features in return. However, there are also heatsink calculation programs that can be downloaded free of charge. We already mentioned the stand-alone version of the RthK Calculator program from **Alutronic**. Another handy program is Heatsink Calculator V2.0 from **BK Soft-**

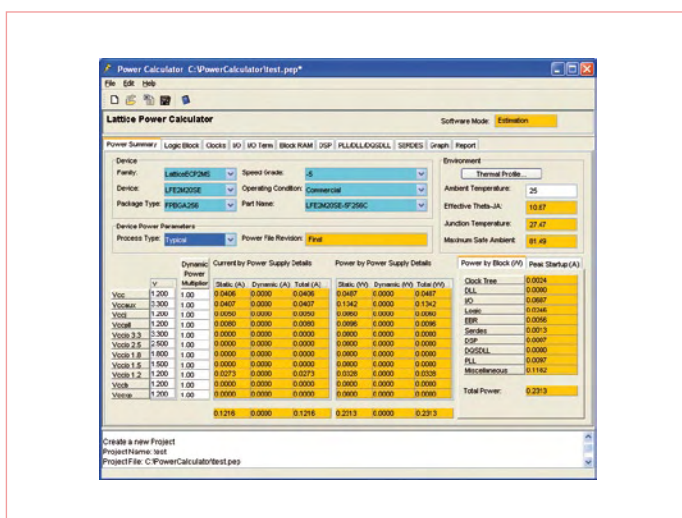


Figure 5. As you can see from the Lattice Semiconductors Power Calculator program, a lot more factors are involved in power dissipation calculations for complex digital ICs.

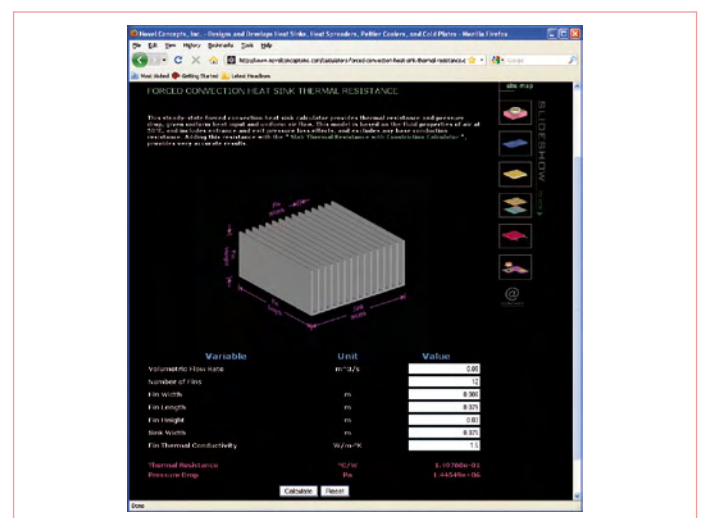


Figure 6. An online calculator for forced-air cooling is available on the Novel Concepts website.

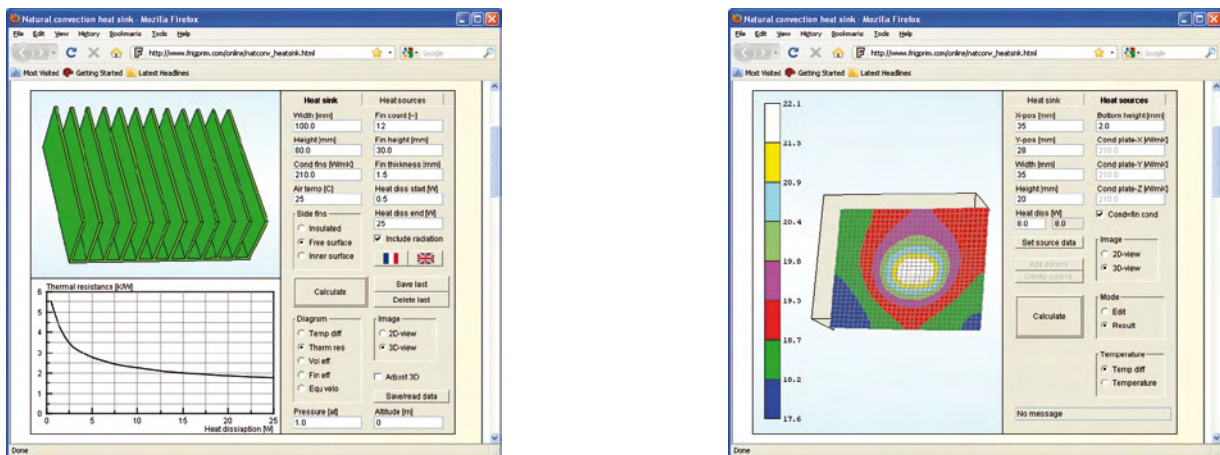


Figure 7. Frigus Primore lets you configure your own heatsink (left) and examine its characteristics, including the temperature profile over the heatsink (right).

ware, written by a Danish electronics enthusiast. This program can be downloaded from his website [7]. The nice thing about this program is that you can choose which value you want to have calculated. You enter all the known or desired resistance values and leave

the box of the value you want to know empty. This value is shown after you press the button. This means that in addition to calculating the maximum allowable thermal resistance of the heatsink as with the other programs, you can also determine the maximum allow-

Advertisement



PropScope

USB Oscilloscope

The **PropScope** is a two-channel oscilloscope that is capable of reading 25 million samples per second with ten bits of resolution over one, two, ten, or twenty volt peak-to-peak waveforms. Power is provided via USB port, requiring only a single cable to connect the PropScope to any PC. The included DAC card provides an analog trigger, a four-bit digital trigger, an eight-bit digital to analog converter, and a four-bit NTSC/PAL output. The included software provides a traditional scope interface along with auto measurements, the ability to store and export waveforms, a function generator, a logic analyzer, a spectrum analyzer, and a vectorscope.



PARALLAX

www.parallax.com

Friendly microcontrollers, legendary resources.

To order the PropScope (#32220; \$249.99)
 visit www.parallax.com or call toll-free 888-512-1024
 (Monday - Friday, 7 a.m. - 5 p.m., PST).

Prices subject to change without notice. PropScope, Propeller, Parallax and the Parallax logo are trademarks of Parallax Inc.

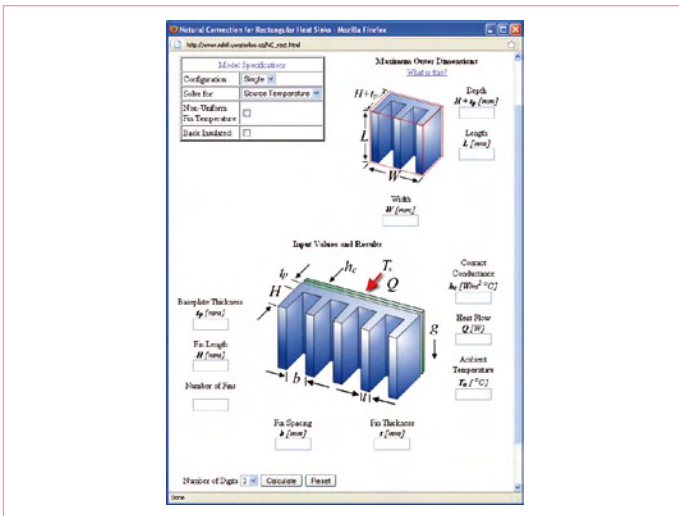


Figure 8. The Microelectronics Heat Transfer Laboratory site also enables you to configure a heatsink according to your specific wishes.

able ambient temperature for a given power dissipation when you use a particular heatsink. You can also perform calculations with more than one transistor on the same heatsink.

Of course, we shouldn't restrict our attention to analog applications. Heat dissipation is a significant factor in the digital world as well, especially with complex ICs such as the CPU in your computer. Specifically for its own ICs, **Lattice Semiconductors** offers the Power Calculator program [8], which you can use to calculate the power dissipation of Lattice FPGAs and CPLDs along with the necessary heatsink. **Altera** offers a similar program for its own ICs, which takes the form of a spreadsheet called PowerPlay [9]. These programs are a good deal more complex than standard heatsink calculation programs.

Forced-air cooling or custom dimensioning?

The **Novel Concepts** website [10] has a program for heatsinks with forced air cooling (using a fan), which provides an easy way to determine how much power a heatsink with a given set of dimensions can dissipate in combination with a particular air flow. For this purpose, you enter the dimensions of the heatsink and the

number of fins, as well as the expected speed of the air stream along the fins. This site also has several other calculators for specialised cooling calculations.

Of course, you may wish to design your own heatsink, or maybe you have a collection of several types of heatsinks for which you do not have any specific data available. In such cases, the websites mentioned below can be very helpful.

The website of **Frigus Primore**, a company that specialises in thermal calculations, offers a variety of special programs for all sorts of thermal calculations. Some of them have demo versions that can be downloaded and used for a limited period. The online heatsink dimensioning program available here [11] is especially interesting. You can use this program to configure your own heatsink (dimensions, number of fins and fin height) and then calculate its thermal resistance, temperature rise per watt and several other things, all online. In addition, a three-dimensional drawing of the heatsink is displayed, and you can rotate it in all directions using the mouse. You can then use the 'Heat Sources' tab to view the temperature profile over the heatsink, with the option of specifying exactly where the component is attached to the heatsink and the dimensions of the component. Very enlightening!

On the website of **Microelectronics Heat Transfer Laboratory** (MHTL), you can also dimension a complete heatsink yourself and calculate its characteristics using the Natural Convection for Rectangular Heatsinks program [12].

Overview

There are many manufacturers of heatsinks and related products, such as thermal pastes and insulation materials. A good starting point for looking for a suitable product or solution is the overview available on the **Heatsink Guide** site [13]. Although it's certainly not complete, it does cover a lot of suppliers and sources.

If you're looking for an extensive, practically oriented description of heatsink calculation and fitting, you should certainly read through the 'Heatsinks' article published in 1994 [14].

(090872)

Internet Links and References

[1] <http://sound.westhost.com/heatsinks.htm>

[2] www.alutronic.de/indexE.php?g=8&sg=1

[3] <http://uk.rs-online.com/web/generalDisplay.html?id=infozone/calculators&file=heatsink>

[4] www.aavidthermalloy.com/technical/thermal.shtml

[5] www.daycounter.com/Calculators/Heat-Sink-Temperature-Calculator.phtml

[6] www.changpuak.ch/electronics/calc_23.html

[7] <http://bygsselvhifi.dk/heatsinkcalc.htm>

[8] www.latticesemi.com/products/designsoftware/powercalculator.cfm

[9] www.altera.com/support/devices/estimator/pow-powerplay.jsp

[10] www.novelconceptsinc.com/calculators-forced-convection-heat-sink-thermal-resistance.cgi

[11] www.frigprim.com/online/natconv_heatsink.html

[12] www.mhtl.uwaterloo.ca/RScalculators.html

[13] www.heatsink-guide.com/content.php?content=manufacturers.shtml

[14] 'Heatsinks: how and when to use them', *Elektor Electronics*, June 1994, pp 30–33

Saelig

UNIQUE PRODUCTS + FREE SUPPORT!

www.saelig.com 888-7-SAELIG info@saelig.com

We have the testgear you need!

Call us for technical advice!


60 - 300MHz DSOs  60/100/200/300MHz 2 ch, 2GS/s DSO 2000 wfm/s refresh rate. High quality, ultra Compact Design with small footprint. Totally new price. DS1052E ~~\$595~~ \$595 •• thru •• DS1302A ~~\$4995~~ \$4995	CAN BOXes  Fanless, maintenance-free, compact Embedded CANbus PC controller series: Linux/QNX/VxWorks/Win, CF storage, touch-panels, etc. emPC series CALL	Mixed -Signal PC Oscilloscope  100 MHz Scope and Logic Analyzer lets you do complex triggering to find hard-to-get-at glitches, spikes, etc. Huge 4 or 8 MS buffer for deep data drilling and zooming. Optional built-in swept signal generator. 2 Analog channels x 10, 12, 14 bit with more than 60 dB dynamic range. 8 digital inputs for mixed signal display/trigger. CS328A-4 (4MS Buffer) \$1259 CS328A-8 (8MS Buffer) \$1474 CS700A (signal generator) \$299	LCD Scopes  Owon - 25 or 60MHz color LCD 2-ch bench scope OR 20MHz handheld scope/meter. USB interface for printouts. Includes scope probes! Battery versions available. PDS5022S / 6062T \$315 / \$499 HDS1022MN / 2062MN \$593 / \$699	
USB Bus Analyzers  Packet-Master™ - best value USB1.1/2.0 USB analyzers and generators. Identify USB problems fast, fine-tune performance, easily view Host commands, emulate host/device sequences, etc. USB12 (USB1.1) \$699 USB480+ (USB1.1/2.0) \$1199 USB500AG (USB1.1/2.0/Gen) \$1399	7 in 1 USB Scope  2-ch 10-bit 2MHz scope/spectrum-analyzer, 3MHz 8-bit wfm gen; 16 x I/O; Network Analyzer; Noise Generator; PWM. Windows/Linux/Mac compatible! USB-powered, great for toolbox, education, etc. CGR-101™ \$180	EMC Spectrum Analyzer  EMC RF & EMF Spectrum - Analyzer 1Hz to 7GHz for measuring transmissions from radar, radio/tv towers, WLAN, WiFi, WiMAX, Bluetooth, microwave ovens, etc. from \$299 / \$1990	microCAM  Compact compressed-serial output camera module for any host system. JPEG OmniVision™ CMOS VGA color camera for embedded imaging. uCAM TTL or 232 \$58	Sound Module  14-pin Tiny Audio-Sound Module plays back pre-stored audio files (voice and music) from micro-SD card - ideal for embedded audio output. SOMO-14D \$25
RF Modules  RF TX/RX Modules - simultaneously transmit composite video and stereo audio signals. 2.4 GHz ISM band. 4-ch RF, 5V operation. AWM630TX \$16 AWM634RX \$27	XP Emb Touchpanel  Touch-input 10.2" LCD 12V-powered Windows PC. LX800/512MB/4GB/Ethernet/3xUSB/SD. CUPC-80 \$849	PCB Verification  Simplify PCB rework and verification with a single easy-to-use GUI for unified view of the PCB. Automatic part location - great for ECNs GTO \$300	RF Testing/EMI Tents  Economical, portable RF test enclosures, for initial compliance testing. from \$1295 Shielding Tents with external frame, instant up/down for emissions-free room. from \$3500	 I started Saelig as an engineer - for engineers! Saelig is an old English word means 'happy, prosperous, blessed'. Check our website for lots of neat stuff! Alan Lowne • Saelig CEO

PIC Cookbook for Virtual Instrumentation

➡ Several case studies included

The software simulation of gauges, control-knobs, meters and indicators which behave just like real hardware components on a PC's screen is known as virtual instrumentation. In this book, the Delphi program is used to create these mimics and PIC based external sensors are connected via a USB/RS232 converter communication link to a PC. Several case studies of virtual instruments are detailed including a compass, an oscilloscope, a digital and analogue thermometer, a FFT-based Frequency analyser, a joystick, mouse-control panels and virtual displays for cars and aircraft. Full source code examples are provided both for several different PIC's, both in assembler and C, together with the Pascal code for the Delphi programs which use different 3rd party Delphi virtual components.

elektor

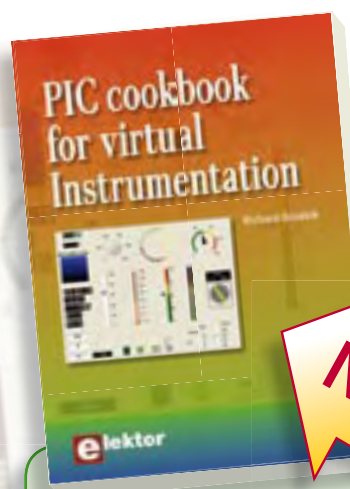

NEW!


264 pages • ISBN 978-0-905705-84-2 • \$46.00

Elektor US
 4 Park Street
 Vernon CT 06066
 USA
 Phone: 860-875-2199
 Fax: 860-871-0411
 E-mail: sales@elektor.com

Further information and ordering at www.elektor.com/shop

Stable Starting Points

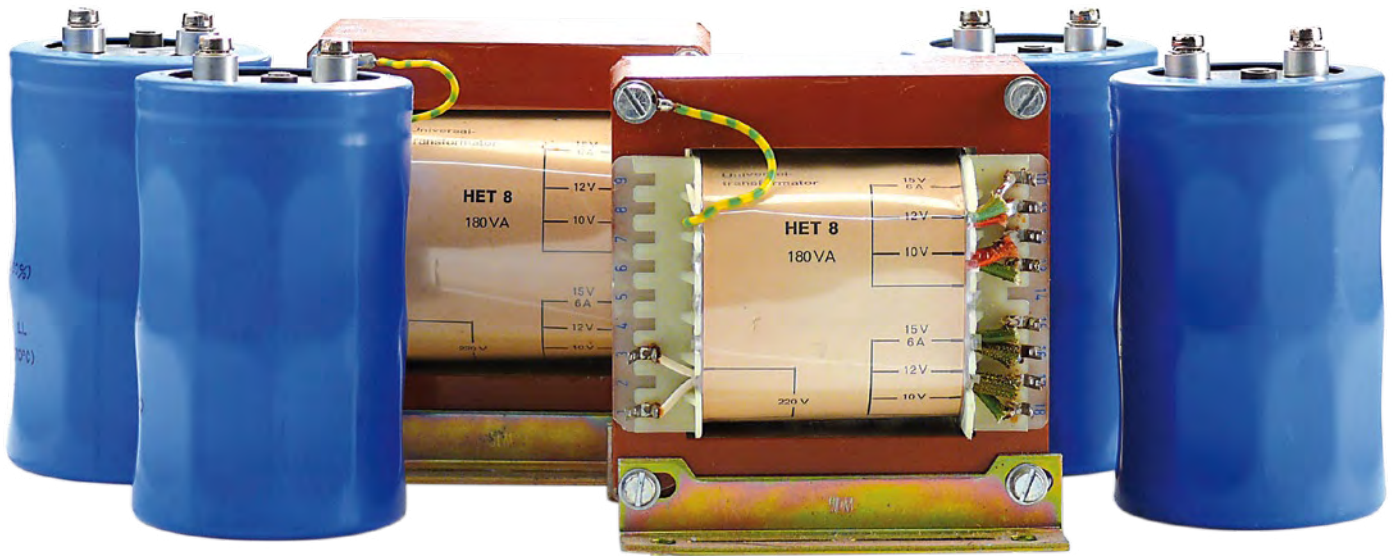An introduction to electronic power supplies



By Thijs Beckers (Elektor Netherlands Editorial)

Practically every electronic circuit needs one: a power supply. The most common source of energy for all our circuits is the AC power outlet. The function of a power supply is to turn this voltage into something more useable. What do you have to look out for when it comes to designing this elementary part of a circuit?

The simplest supply is of course a type that uses a single rectifier. This is followed by the full-wave rectifier. When an electrolytic capacitor is added to this the resulting output begins to look like a reasonable DC voltage. A choke can be added in series (see **Figure 1**) in order to reduce the inevitable ripple at the output.

When more stability of the DC voltage is required some further action is needed. The easiest is the addition of resistor and a zener diode (see **Figure 2**). This simple solution is suitable for currents up to about 50 mA (depending on the voltage). The circuit is often enhanced with the use of a transistor, where the voltage across the zener diode is used as a reference voltage. The regulated output voltage is then about 600 to 700 mV less than the zener voltage. The value for R in kilo-ohms has to be chosen such that the zener diode is properly biased and sufficient current can flow through the base of the transistor:

$$R = (V_i - V_o) / (I_L + 5)$$

where I_L is in mA. The next step (and one that is very easy to implement, see **Figure 3**) is to use one of the voltage regulators from the well-known 78xx and 79xx range, which are series regulators with three pins.

The 78xx range regulates positive voltages, whereas the 79xx range is meant for negative voltages. These devices have made life very easy when there is a need for a symmetrical, stabilized power supply. The built-in diodes at the outputs of the regulator ICs protect them from potential latch-ups when they're switched on.

Voltage regulators come in several other varieties. The LM317 (positive voltages) and the LM117 (negative voltages) have an adjustable output; if you need more current, there is the LT108x range which can supply up to 7.5 A.

Design criteria

When selecting the transformer you have to take the losses in the components and the expected ripple into account. The minimum required transformer voltage can be calculated using this formula:

$$V_{AC} = (V_o + \Delta V_{min} + V_R + 2V_D) / \sqrt{2}$$

Where V_o = output voltage, ΔV_{min} = minimum voltage drop across the regulator IC, V_R = ripple voltage at the input of the regulator, V_D = voltage across the rectifier diode.

A good approximation for the ripple voltage (V_R) can be obtained using the following rule of thumb:

$$V_R = I / 2fC$$

where I is in ampères and C is in farads. The frequency depends on the type of rectifier used (half wave or full wave).

All other values can be found in the data sheets for the components used.

A small tip: Consider using Schottky types for the rectifying diodes. These can make the required AC voltage *just* low enough so you can choose a transformer with a lower output voltage.

You have to keep the following in mind when selecting the (bridge) rectifier and the smoothing (reservoir) capacitors: the electrolytic capacitors are only charged up for a relatively short period, which is when the voltage from the rectifier is larger than that stored in the capacitor(s), see **Figure 4**. This results in large spikes in the charging current. The area underneath the current spike corresponds to the power that the circuit has drawn from the electrolytic capacitor and which therefore has to be replenished by the rectifier. In order to reduce the ripple voltage, larger electrolytics are often used. The consequence of this is that although the ripple voltage is reduced, the time available to the rectifier to recharge the electrolytic is also reduced. Assuming that the power consumption is the same, the size of the current surge will increase significantly (the area under the graph remains the same), which can have more serious consequences (such as burnt-out rectifying diodes).

In practice the transformer will be the largest limiting factor for the peak current. It will go into saturation fairly quickly and won't be able to supply the theoretical current requested of it. When it comes to selecting the diodes for the rectifier you can use the following rule of thumb: The maximum current that the diodes have to withstand is $\sqrt{2}$ times the peak current that the secondary winding of the transformer can deliver. To be on the safe side we normally specify twice this peak current. Don't forget that with the large currents involved it will often be necessary to put heatsinks on the rectifiers to keep them cool. A good approximation for the values to use for the electrolytics is that you need about 2200 μF per Amp.

Internet

For more complex designs such as switch-mode power supplies there are tools and programs available from several (semicon-

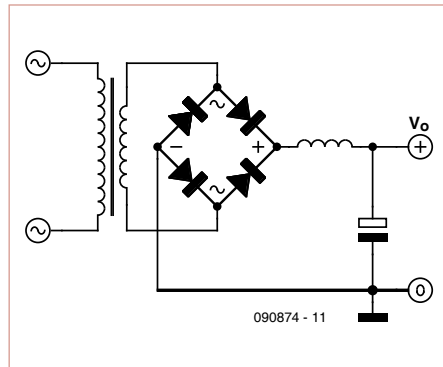


Figure 1. A bridge rectifier, a choke and an electrolytic capacitor are enough to provide a reasonably constant voltage.

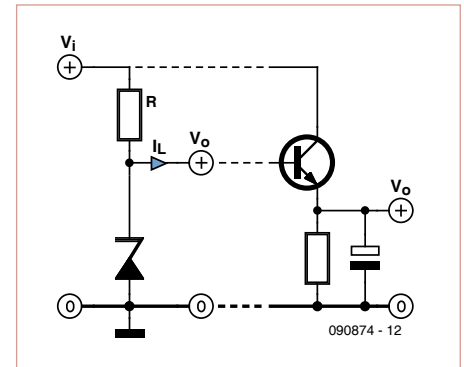


Figure 2. The addition of a zener diode as a reference increases the stability of the output voltage.

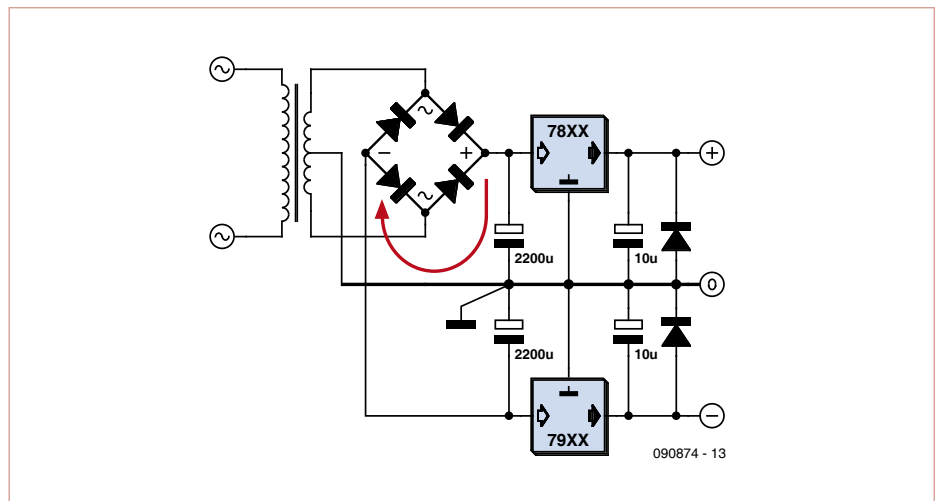


Figure 3. Thanks to integrated voltage regulators such as those from the 78xx and 79xx range the creation of stable supplies has become child's play.

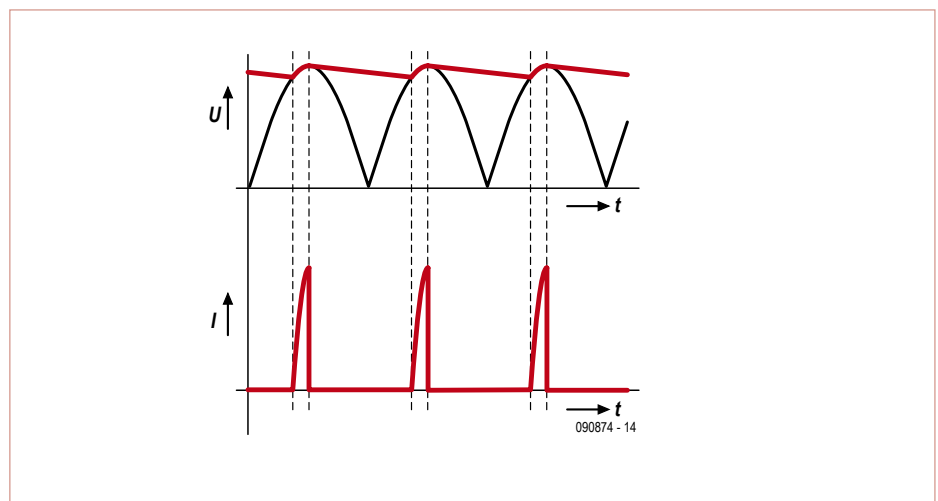


Figure 4. The peak current that occurs during the charging of the electrolytic capacitors can become quite large.

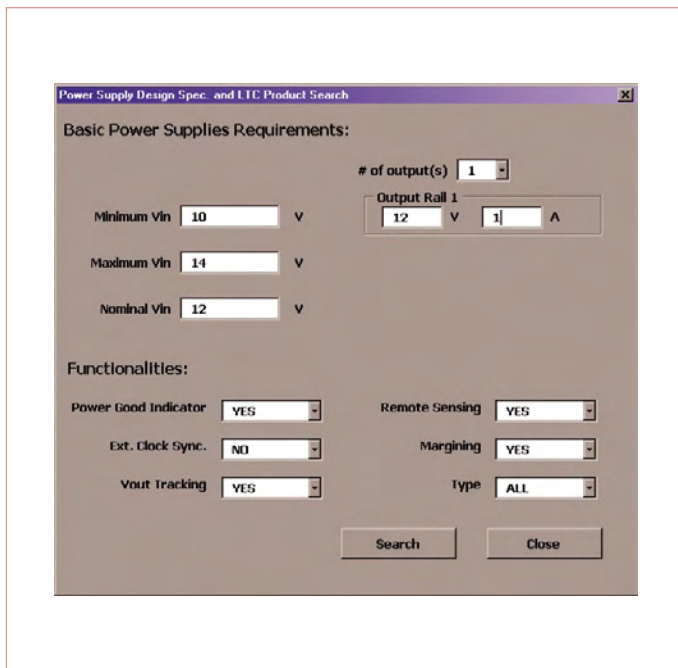


Figure 5. The program LTpowerCAD supplied by Linear Technology lets you specify a large number of parameters for your power supply.

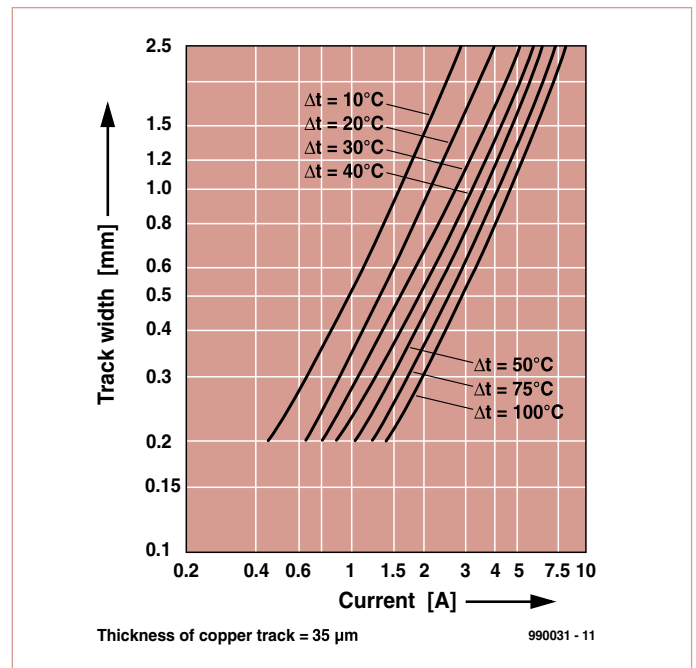


Figure 6. This graph shows just how easily PCB tracks can heat up.

ductor) manufacturers. An example of this is the 'program' *LTpowerCAD* [1] from Linear Technology. With this Microsoft Excel based tool it is very easy to design a (switch-mode) power supply that satisfies all the parameters specified on the form (see **Figure 5**). The online tool *Webench Power Designer* [2] from National Semiconductor also bursts with options and features. This list can be extended with the tools from Fairchild [3], *VIPer Design Software v.2.24* [4] from STMicroelectronics and *SwitcherPro* [5] from Texas Instruments. These are probably the most well-known. Bear in mind that most of these programs are only suitable for use with (a certain range of) special ICs made by the manufacturer in question. All of them are however free to use.

For those of you who would like to find out more about designing switch-mode power supplies, take a look at the website at www.smeps.us. This site contains a huge amount of information on the subject, including an overview of the topologies used [6]. Another interesting website is at www.poweresim.com. Here you can design circuits from 'Switched Mode Power Supplies' (SMPS), which satisfy all the criteria that you've specified.

PCB layout

When a circuit diagram on paper has to be converted into a PCB layout we obviously

come across all sorts of physical properties and obstacles. A few tips are very useful here and we wouldn't want to keep them from you. The smoothing capacitors should be positioned as close as possible to the point that needs smoothing. This means close to the components rather than the supply. Long PCB tracks introduce extra impedance (especially at higher frequencies) that reduces the effectiveness of the smoothing. In circuits that work at higher frequencies extra care has to be taken to keep these tracks as short as possible.

Remember that current always flows in a loop. As you can see from **Figure 3**, current loops also play a big role in power supplies. The red arrow indicates that the supply current flows in a loop via the Ground. When calculating the total path length of the current you therefore also have to consider the length of the Ground track (or Ground plane if it exists).

The peak current into the electrolytics that was mentioned earlier also flows via the Ground connection. To avoid unwanted interference in 'heavy' power supplies it is best to keep this current loop outside the Ground plane. This is done by wiring this separately and to choose the connection between the two large smoothing capacitors as the Ground point (where the Ground symbol is drawn in the circuit). This is sometimes called the star point.

Another area that should be given considerable thought when designing the PCB is the width (and thickness) of the tracks. Not only do they have a certain resistance, they can also heat up. The graph in **Figure 6** shows how much the temperature rises with certain widths of tracks and the size of the current through them. As can be seen, the temperature rises quickly as the current increases. It is sensible to limit the temperature increase to 30–40 degrees C because the graph shows the rise under ideal circumstances. Once the PCB has been mounted inside a case it can't lose the heat as easily and the temperature could rise much further, which could have disastrous consequences on the circuit...

(090874)

Internet Links


- [1] www.linear.com/designtools/software/ltpowercad.jsp
- [2] www.national.com/analog/webench/power
- [3] www.fairchildsemi.com/design_tools/index.html
- [4] www.st.com
- [5] <http://focus.ti.com/docs/toolsw/folders/print/switcherpro.html>
- [6] www.smeps.us/topologies.html

Torture Rack

Dynamic testing of power supplies using simple tools

By Harry Baggen (Elektor Netherlands Editorial) and Ton Giesberts (Elektor Labs)

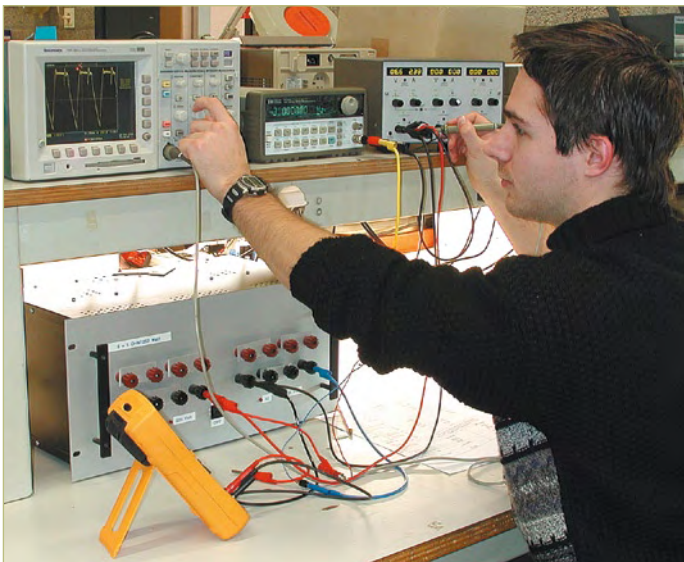How can you find out how stable a lab or benchtop supply is? You can get a good impression of the stability of a power supply under various conditions by loading the output dynamically. This can be implemented using just a handful of components.



Apart from obvious factors such as output voltage and current, noise, hum and output resistance, it is also important that a power supply has a good regulation under varying load conditions. A standard test for this uses a resistor array across the output that can be switched between two values. Manufacturers typically use resistor values that correspond to 10% and 90% of the rated power output of


the supply. The switching frequency between the values is normally several tens of hertz (e.g. 40 Hz). The behaviour of the output can then be inspected with an oscilloscope, from which you can deduce how stable the power supply is. At the rising edge of the square wave you will usually find an overshoot, which is caused by the way the regulator functions, the inductance of the internal and external wiring and any output filter.

This dynamic behaviour is normally tested at a single frequency, but the designers in the Elektor lab have tested numerous lab supplies over the years and it seemed interesting to check what happens at higher switching frequencies. The only items required for this are an ordinary signal generator with a square wave output and the circuit shown in **Figure 1**. You can then take measurements up to several megahertz, which should give you a really good insight for which applications the power supply is suitable. More often than not you will come across a resonance frequency at which the supply no longer remains stable and it's interesting to note at which frequency that occurs.

The circuit really is very simple. The power MOSFET used in the circuit is a type that is rated at 80 V/75 A and has an on-resistance of only 10 mΩ ($V_{GS} = 10$ V).

The output of the supply is continuously loaded by R2, which has a value such that 1/10th of the maximum output current flows through it ($R2 = V_{max}/0.1I_{max}$). The value of R1 is chosen such that 8/10th of the maximum current flows through it ($R1 = V_{max}/0.8I_{max}$). Together this makes 0.9 I_{max} when the MOSFET conducts. You should round the calculated values to the nearest E12 value and make sure that the resistors are able to dissipate the heat generated (using forced cooling, if required). At larger output currents the MOSFET should also be provided with a small heatsink. The gate of the FET is connected to ground via two 100 Ω resistors, providing a neat 50 Ω impedance to the output of the signal generator. The output voltage of the signal generator should be set to a level between 5 V and 10 V, and you're ready to test. Start with a low switching frequency and slowly increase it, whilst keeping an eye on the square wave on the oscilloscope. And then keep increasing the frequency... Who knows what surprises you may come across? Bear in mind though that the editorial team can't be held responsible for any damage that may occur to the tested power supply; the use of this circuit is at your own risk!

(090875)

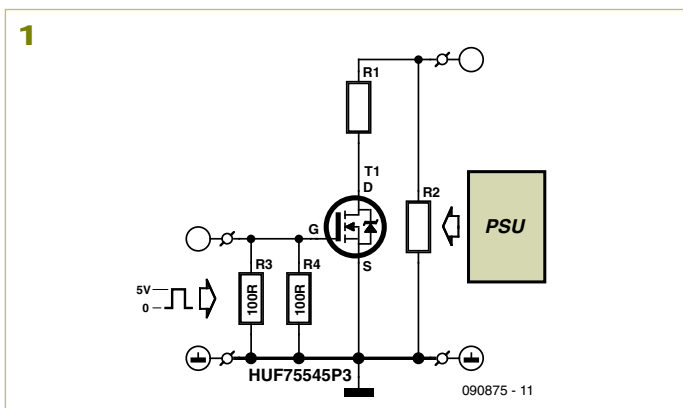

Battery Checker

One to ten cells, up to 10 A



By Rüdiger Britzen (Germany)

A battery pack is only as strong as its weakest cell. This intelligent battery checker will determine the state of cells so that an optimal selection can be made from them to form a pack. It is essential to measure not only the capacity of the cells, but also their internal resistance.

In theory it is relatively easy to determine the capacity of a battery: it is the integral of the discharge current over the time it takes a fully charged cell to reach its specified end-of-discharge voltage. This voltage is different for cells of different chemistries. In practice a single cell is discharged and the current is measured regularly.

Each measurement is made over a sufficiently short period that the current can be considered as constant over that period, at least compared to the overall accuracy of the measurement. The current measurements are summed and the result converted to a capacity in the appropriate units, usually mAh (milliampère-hour). Discharge is stopped when the end-of-discharge voltage is reached.

Criteria

When selecting cells to make up a battery pack the total capacity is not the only criterion of importance. Equally important is the internal resistance of the cells, which can be calculated by dividing the load current into the difference between the terminal voltage under load and the open-circuit terminal voltage. It is also interesting to know at what current the end-of-discharge voltage is reached and the total charge drawn from the cell to reach this point. The battery checker has a 'constant voltage' mode to make this kind of measurement, on which subject more in the section below describing the software.

In order to be able to provide adequate load for powerful cells, discharge currents as high as 10 A are needed. Commonly-available

battery packs rarely consist of more than ten NiCd or NiMH cells, and so a voltage range of 0 V to 12 V is sufficient. The user interface consists of a 2-by-16 LCD panel, a three-color (red, yellow and green) LED, four buttons, and an EIA232 interface for configuration and control. The battery voltage is measured using separate voltage sense wires to ensure that the readings taken are not affected by the voltage drop along the wires used to carry the discharge current. This voltage drop will be significant at the higher discharge currents envisaged.

The circuit

The battery checker internally uses three different supply voltages, which are generated by the circuit involving TR1, F1, B1, C1, IC1, IC2 and IC3 and associated decoupling

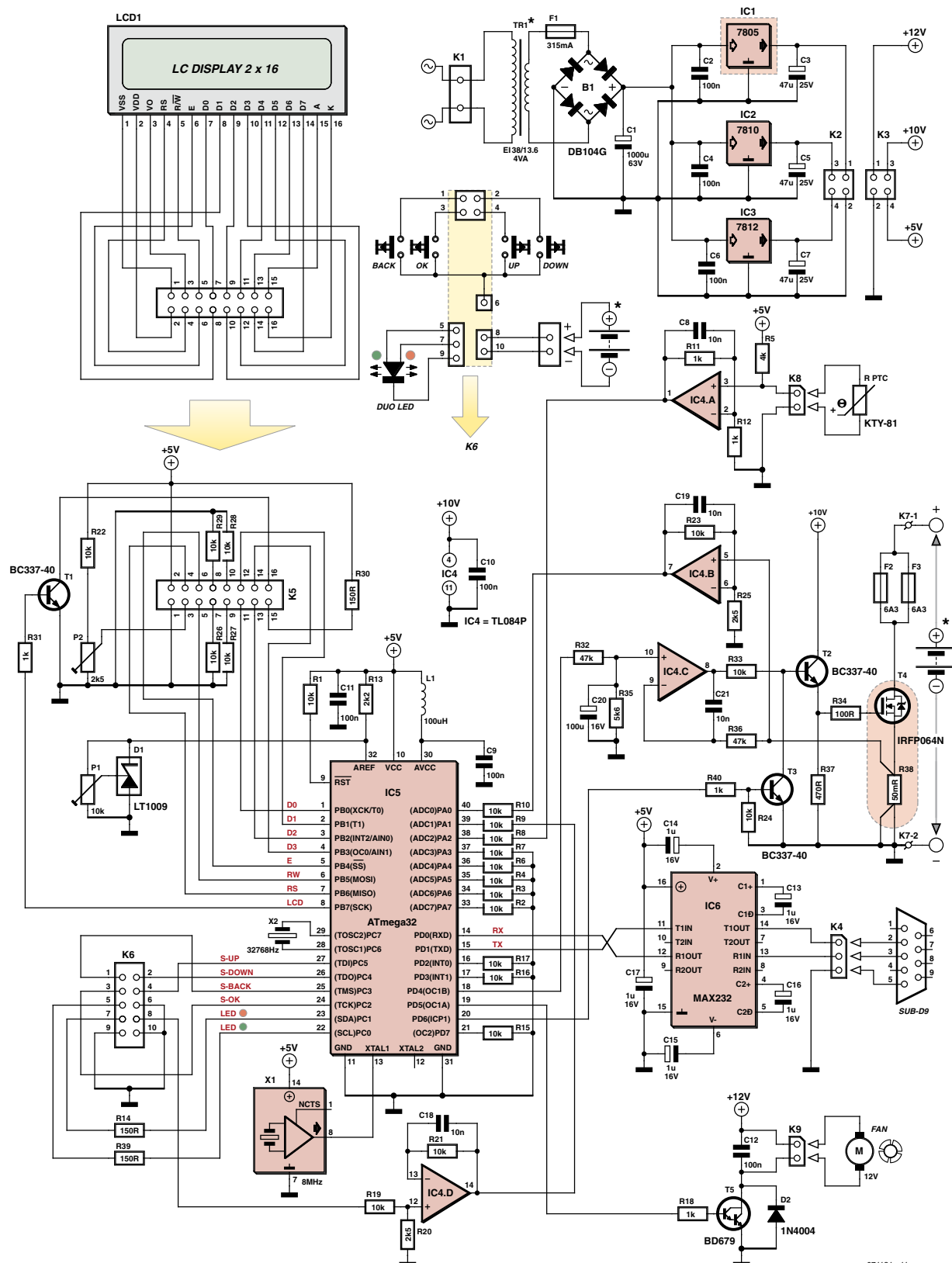


Figure 1. Circuit diagram of the battery checker. The battery under test is connected to two separate pairs of terminals, one pair to carry the discharge current and one to measure the terminal voltage.

Features

- Voltage range 0 V to 12 V (corresponding to 0 to 10 NiCd or NiMH cells)
- Discharge current up to 10 A
- Internal resistance measurement at the start of the discharge process (average of ten readings)
- Constant current discharge with switch-over to constant voltage discharge
- Display of set-point and actual values of voltage and current
- Display of discharge time, total charge, internal resistance, heatsink temperature and fan speed
- Controlled using four pushbuttons to set cell count, required discharge termination voltage and required discharge current
- Calibration facility for A/D converter and current regulator PWM
- Backlit 2-by-16 character LCD
- Status LED
- Heatsink temperature monitoring with fan control (proportional controller)
- Serial interface to output values and to receive control messages
- Maximum power dissipation 120 W (with special cooling), adjustable 40 W limit in software
- Free download of software and printed circuit board layouts at www.elektor.com/071131

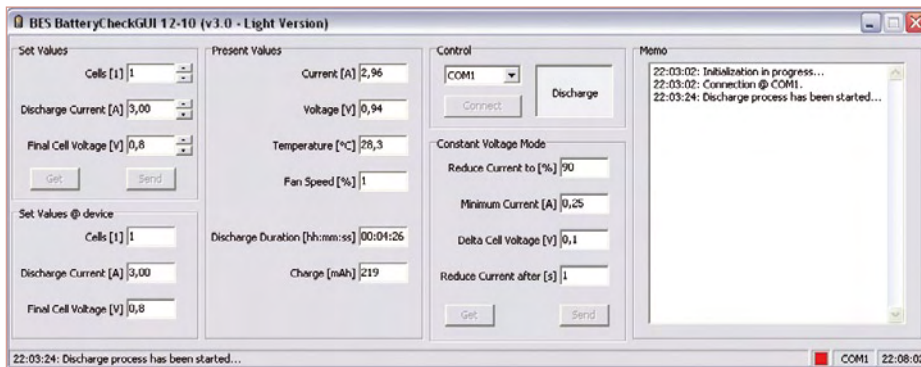


Figure 2. The Windows software displays the settings and the instantaneous measured values.

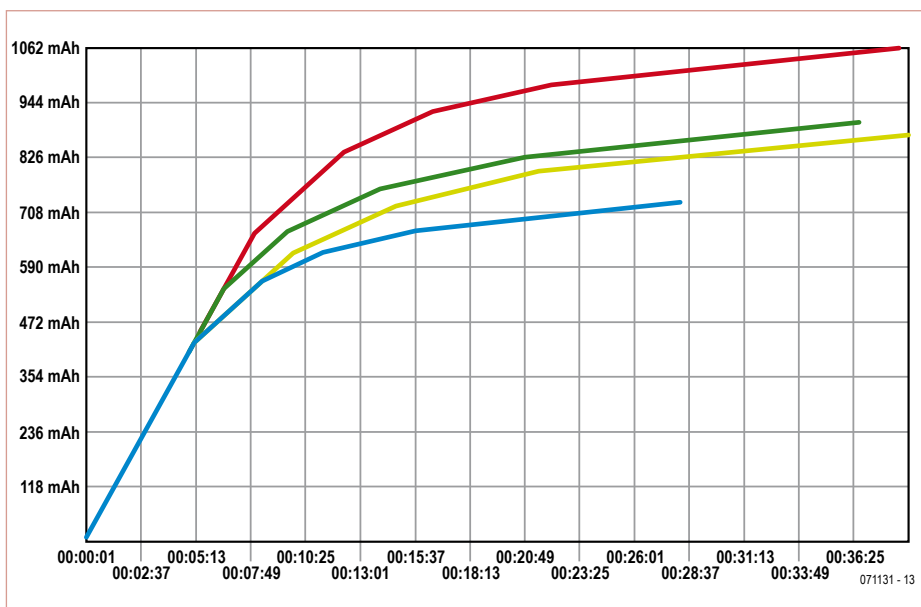


Figure 3. A planned extension to the software will feature log files and graphical output, such as this plot of charge against time.

capacitors. The voltages are: 5 V, for the microcontroller and display; 10 V, for the current regulator; and 12 V for the fan.

As is so often the case the circuit centres on a microcontroller, IC5. Around it we have an 8 MHz clock oscillator (X1), 2.56 V precision voltage source D1 used to provide a reference for the analog-to-digital converter, watch crystal X2 and quad operational amplifier IC4.

IC4.A acts as a buffer amplifier for the PTC thermistor attached at K8, used as a temperature sensor. The opamp is wired as a non-inverting amplifier and provides a gain of 2 for the voltage dropped across the thermistor.

IC4.B is also configured as a non-inverting amplifier and provides a gain of 5 for the voltage dropped across precision shunt resistor R38: this voltage is directly proportional to the discharge current.

IC4.D buffers the battery voltage, which is divided by 5 by the potential divider formed by R19 and R20. The battery under test is connected to the circuit in two places: at K7 where the discharge current is drawn, and between pins 8 and 10 of K6, where the terminal voltage is measured. Separate connections should be made to the battery terminals from these points on the circuit, as mentioned above.

IC4.C forms part of the current regulator. A DC level, smoothed by the low-pass filter formed by C20 and R35, appears at its non-inverting input. This voltage is one tenth of the average value of the PWM signal present on PD4 (pin 18) of the microcontroller, because of the potential divider comprising R32 and R35. The output of the operational amplifier is connected to the base of T2 via R33, and the emitter of this transistor is connected to the gate of power FET T4 via the current divider formed by R34 and R37. The values of R33, R34 and R37, together with the current gain of T2 and the gate capacitance of T4, determine the characteristics of the current regulation control loop. The voltage across R38 in the drain circuit of T4 is proportional to the instantaneous discharge current flowing. This voltage is taken via R36 to the inverting input of IC4.C. There are two fuseholders for F2 and F3 (each for a 6.3 A fast acting fuse) in the source circuit of T4, as the fuseholders are not rated to carry

10 A. T3 allows the current regulator to be switched off quickly by pulling the base of T2 to ground.

The circuit around IC6 is in accordance with its data sheet, converting between the TTL levels of the microcontroller and EIA232 voltage levels.

Firmware

The software running in the microcontroller is interrupt-driven. The body of the code (at main) runs after a reset and configures and initializes all the inputs, outputs and timers (Initialize, RefreshLCD). The code then enters an infinite loop, reacting to watch crystal timer overflows (every 250 ms), button presses and the reception of complete data messages, setting outputs appropriately.

Timer 0 generates interrupts at a frequency of 488.28 Hz. The service routine reads the state of the buttons and performs debouncing. Timer 1A and Timer 1B are configured as PWM generators to drive the current regulator (Timer 1B) and the fan (Timer 1A). Timer 2 is clocked by the 32.768 kHz watch crystal and overflows every 250 ms. This triggers the sending out over the EIA232 interface either of instantaneous measured values and set points (current, cell voltage, cell count, charge, discharge time and so on) or of device settings (characteristic curves, maximum values, parameters for constant voltage mode), in response to a corresponding request. Also, the interrupt flag ClockCrystalTimer is set, which causes the function CalculateValues() to be called from the main loop.

CalculateValues() first performs analog-to-digital conversions on the battery voltage, the voltage dropped across the shunt (which is proportional to the discharge current), and the voltage across the thermistor (which depends on the heatsink temperature). These values are used to calculate settings for the fan and the discharge current (if enabled), as well as to update the running total of charge. The function also implements 'constant voltage mode' and the measurement of the internal resistance of the battery. If the heatsink temperature exceeds the value 'CSMAxTemperatureInCel-

sus' discharge is stopped for the time period specified by 'CSCoolDownPeriod'.

In 'constant current mode' the battery is initially discharged at a user defined current ('SetCurrentIn10mA') down to a preset voltage ('SetVoltageIn100mV' + 'CSCurrentReductionUDeltaIn100mV'). Then, as soon as the voltage ('MeasuredVoltageIn100mV') has remained below the preset level for given time ('CSCurrentReductionTime'), the discharge current is reduced in steps ('CSCurrentReductionAmount') until a minimum value ('CSCurrentReductionMinCurrentIn10mA') is reached. The unit continues to discharge the battery at this current until the final discharge voltage ('SetVoltageIn100mV') is reached. The graph of current against time gives a clear picture of the performance of the cell, and is much more informative than a bald capacity value.

The internal resistance of the battery is measured at the start of the discharge procedure. The measurement is done by first measuring the open-circuit voltage of the battery and then measuring the terminal voltage with the specified discharge current being drawn. The measurement is repeated ten times at intervals of one second. The two smallest and the two largest calculated values for the internal resistance are discarded and the remaining six values are averaged, the result being displayed on the LCD. The code to perform this calculation is unfortunately relatively involved and not necessarily very easy to understand: this part of the CalculateValues() function may be hard to modify.

The function ProcessKey() includes the state machine behind the battery checker. Depending on the current state, a keypress recognized in the Timer 0 overflow interrupt code will cause a switch to a new state or some other response. The function RefreshLCD() writes information to the LCD panel depending on the current state of the system.

Windows software

The Windows software gives access to the basic functions of the battery checker and can also be used as a basis for expansion. The program displays the set points for cell

About the Author

Rüdiger Britzen, 32, studied Electronics and Information Technology at the German Army University in Munich, and works principally as a systems engineer in the defence industry. Alongside that he is also, as Britzen Embedded Systems, an independent hardware and software developer.

voltage, discharge current and cell count, and the measured values for current, voltage, heatsink temperature, fan speed, discharge time and total charge (see **Figure 2**). These set points and the 'constant voltage discharge' setting can be configured. If a value of less than 100 is entered in the field 'Reduce Current to %', the discharge current will be reduced by the given percentage factor at the end of any period longer than the time given at 'Reduce Current after' during which the cell voltage remains below the value 'Final Cell Voltage' plus 'Delta Cell Voltage'. This process repeats until the minimum discharge current is reached.

The unit's status is reflected in the status line of the window as a virtual LED, with colors corresponding to those of the LED on the unit.

After connecting the battery checker to the PC, choose the correct COM port setting and initialize communication by clicking on the 'Connect' button. If the connection is successfully made the input fields will become active and the unit can be configured and controlled.

The author is planning an expanded version of the software that will allow the display of log data, graphical presentation like that shown in **Figure 3**, and configuration of all the new settings.

Protocol

The author has developed a protocol for communications between the PC and the battery checker, using seven-byte messages to carry sixteen-bit values with eight-bit identifiers. The identifier is split into two bytes and the data value into four bytes, and a checksum is appended. The header file RBE_SP16.h and code RBE_SP16.c encapsulate the protocol and also implement a FIFO buffer.

Every 250 ms by default the battery checker send out either the set-points and measured values or, in response to a request, the core settings of the device (the variables whose names begin 'CS') as a single message with appended checksum (31 bytes in total).

COMPONENT LIST

Resistors

(5%, 0.25W unless otherwise indicated)

R1–R4, R6–R10, R15, R16, R17, R19, R21–R24, R26–R29, R33 = 10k Ω
 R5 = 4.02k Ω (1%)
 R11, R12, R18, R31, R40 = 1k Ω
 R13 = 2.2k Ω
 R14, R30, R39 = 150 Ω
 R20, R25 = 2.49k Ω (1%)
 R32, R36 = 47k Ω
 R34 = 100 Ω
 R35 = 5.6k Ω
 R37 = 470 Ω
 R38 = 50m Ω 0.5% precision power resistor, e.g. Isabellenhütte Heusler type PBV 0.05 (Conrad Electronics # 447382-62)
 P1 = 10k Ω preset, horizontal
 P2 = 2.5k Ω preset, vertical

Capacitors

C1 = 1000 μ F 63V radial, lead pitch 10mm
 C2, C4, C6, C9–C12 = 100nF 50V ceramic
 C3, C5, C7 = 47 μ F 25V radial, lead pitch 0.1 inch
 C13–C17 = 1 μ F 16V radial, lead pitch 0.1 inch
 C8, C18, C19, C21 = 10nF ceramic
 C20 = 100 μ F 16V, radial, lead pitch 0.2 inch

Inductors

L1 = 100 μ H miniature choke (resistor body)

Semiconductors

B1 = DB104G (Taiwan Semiconductor), 1A 400V bridge rectifier (e.g. Farnell # 706796)
 D1 = LT1009CLPG4 (TI), 2.5V voltage reference, TO-92 case (e.g. Farnell # 9589724)
 D2 = 1N4004
 IC1 = 7805 with 15 K/W heatsink
 IC2 = 7810
 IC3 = 7812
 IC4 = TLC274BCN (TI), DIP-14 with socket
 IC5 = ATmega32-16PU (ATMEL), DIL-40 with socket, programmed, order code 071131-41*
 IC6 = MAX232N (TI), DIP-16 with socket
 T1, T2, T3 = BC337-40
 T4 = IRFP064NPBF (International Rectifier, e.g. Farnell # 8649227)
 T5 = BD679

Miscellaneous

K1 = 2-way PCB screw terminal, lead pitch 7.5mm
 K2, K3, K8, K9 = 2-pin pinheader, 0.1 inch lead pitch
 K4 = 3-pin pinheader, 0.1 inch lead pitch
 K5 = 16-way (2x8) pinheader, 0.1 inch lead pitch
 K6 = 10-way (2x5) pinheader, 0.1 inch lead pitch
 K7 = 2 solder pins, 1.3mm diam.
 LCD1 = 2x16 characters, e.g. DEM16217 SYH-PY /V (Elektor-Shop # 030451-72)
 TR1 = PCB transformer, 12V 0.33A secondary, e.g. EI38/13.6 4.0 VA (Pulse), part no.: 038-5414.0 (230V primary), 038-5402.0 (115V primary) or HAHN type BV EI 382 1191 (230V primary)
 X1 = 8MHz quartz oscillator module, e.g. AEL Crystals type O8M000000L642 (Farnell # 9509712)
 X2 = 32.76 kHz watch crystal, cylindrical case
 F1 = fuse 0.315A 250V, slow blow, dim. 5x20mm, incl. fuseholder and cap
 F2, F3 = fuse 6.3A fast, dim. 5x20mm, incl. fuseholder
 9-way sub-D socket
 4 pushbuttons for front panel mounting
 Fan, 12VDC, 80mA, dim. 40x40mm
 KTY 81-122 (NXP), PTC temperature sensor, SOD-70 case
 Heatsink, Fischer Elektronik type SK 68/50 SA, dim. 50x46x33mm, rat-

ing 4.6K/W

Bicolor LED (green/red), 5mm diam.

Heat conducting glue for securing temperature sensor to heatsink

Terminal posts, 4mm diam. (1 red, 1 black)

PCB nos. 071131-1* (PSU) and 071131-2* (main board)

* Kit of parts no. 071131-71 containing PCBs, a programmed microcontroller and all parts (except case) is available from the Elektor Shop, see www.elektor.com/071131

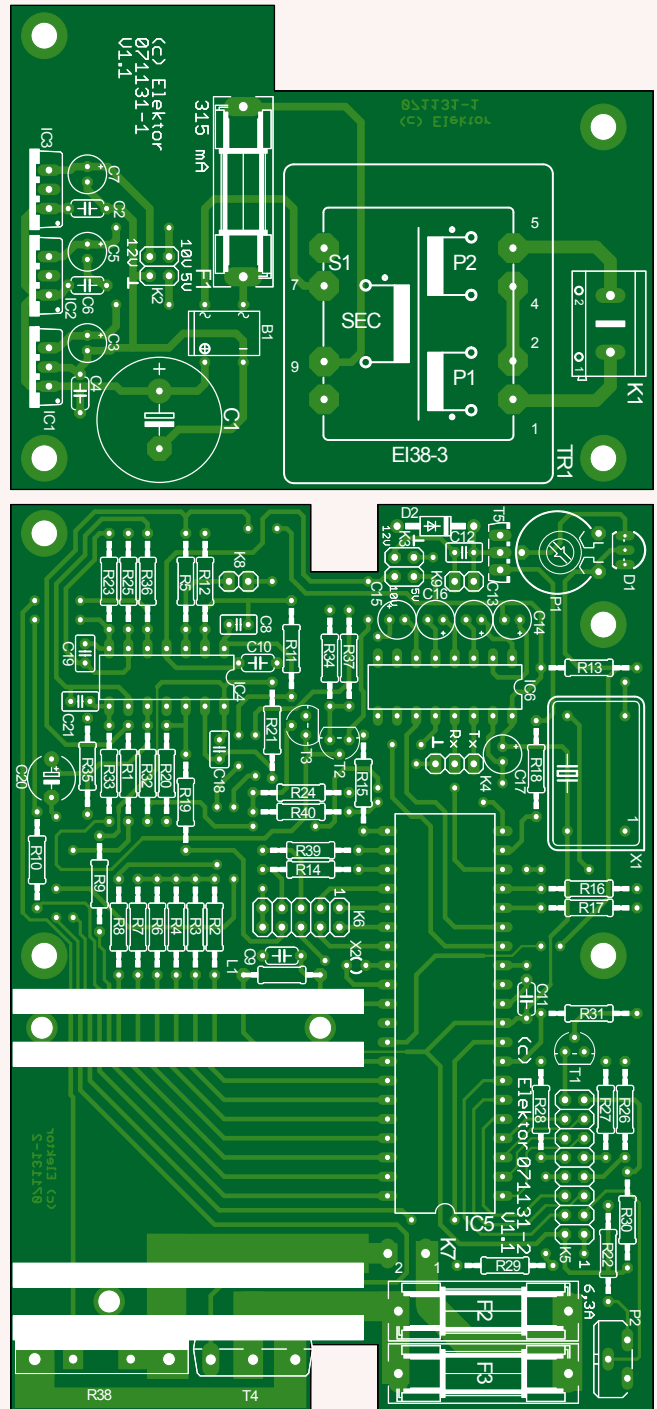


Figure 4. Component mounting plan for the power supply board and the main board.

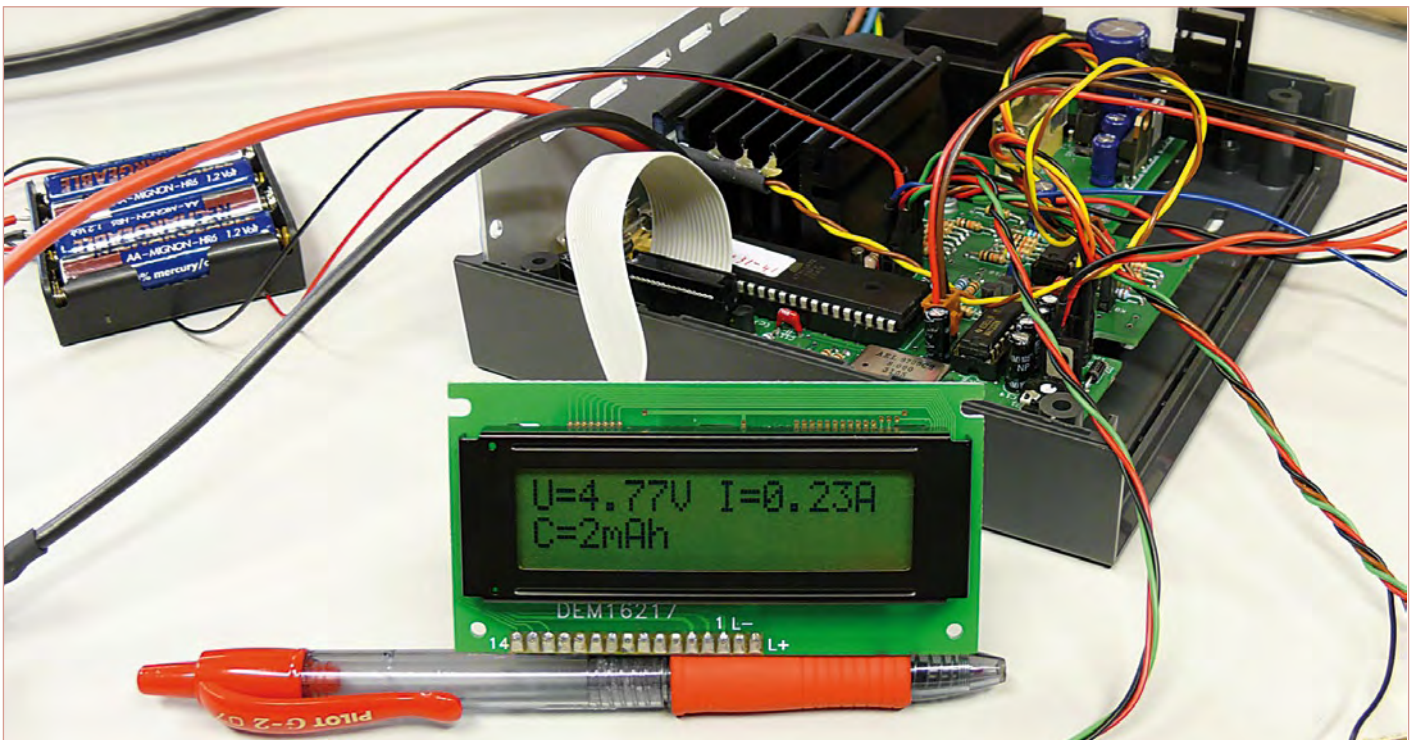


Figure 5. The Elektor laboratory prototype under test.

Construction and operation

Both the main board and the power supply board are populated exclusively using through-hole components (**Figure 4**). The tracks between the connection points for the 1.5 mm² wires (at K7), the FET and the shunt should be tinned over with extra solder (assuming the board does not have a solder mask) or reinforced using suitable soldered silver wire (if the board does have a solder mask). It is recommended to test the boards separately, starting with the power supply board. It is essential to ensure that all wires and components carrying power line voltages are adequately insulated and cannot be touched. In addition, it is advisable to use an isolation transformer. Check that the correct voltages appear on K2.

Power the main board using a laboratory supply set to a conservative current limit of say 100 mA. If nothing appears on the display, adjust P2 to set the contrast suitably. If everything appears to be working so far, you should find operating the unit self-explanatory. Two buttons ('Up' and 'Down') navigate through the menus, the third button ('OK') confirms an input, and the fourth ('Back') cancels an operation.

With the main board connected to the power supply board, adjust P1 so that the voltage on D1 (i.e., on pin 32 of IC5) is exactly 2.5 V. The next step is to calibrate the analog-to-digital converter (for the battery voltage and the shunt voltage) and the

current regulator. To do this, go to the calibration menu and select the battery voltage ADC. Short the battery voltage measurement terminals (pins 8 and 10 of K6) together and press the confirmation button to calibrate the 0 V point. Now connect the voltage measurement terminals to as precise a 6 V source as possible and press the confirmation button again.

Next, calibrate the current regulator. Connect a voltage source capable of delivering at least 2 A to the load terminals of the battery checker (on K7), with an ammeter in series with one of the connections. Then select the appropriate menu item and adjust the PWM value using the navigation buttons to make the current in the load as close to 2A as possible. Finally, calibrate the ADC for the shunt voltage. Again, a 2 A source is required connected to the load terminals. Simply select and confirm the appropriate menu option.

The calibration values can be stored in EEPROM by selecting the 'Store settings' menu option. The text is followed by a '*' if one or more of the current settings differs from that stored in EEPROM.

The parts list does not recommend a particular enclosure for this project. The author used a TEKCO CAB 022.9 enclosure for his prototype, and for the Elektor prototype we used a Retex Elbox 33030202. The parts mounted on the front panel (LCD, buttons

and sockets) are connected to the relevant points on the printed circuit board using ribbon cable or wire. For the current-carrying connections wire with a cross section of at least 1.5 mm² cross-sectional area is needed.

A DIY battery holder

Ordinary battery holders and charging cradles are only really suitable for currents of up to about 3 A. A cheap plastic battery holder may start to melt around the contacts at a discharge current of 2.5 A. The problem does not arise with cells that have solder tags.

For individual cells without solder tags the author found a solution using a ratchet clamp found in a local tool shop next to the ordinary woodworking clamps. With a bit of skill it is possible to repurpose the clamp as a 'high current discharge clamp'. The ratchet clamp has a smooth action without steps and so can easily grip cylindrical cells, allowing currents of up to 10 A to be drawn without significant temperature rise. However, it is important to be careful to avoid overloading cells: during testing the author succeeded in inadvertently destroying two brand new Panasonic AA cells through overheating in constant voltage mode ($U=0.9$ V, current reduction after 1 s) with an initial current of 10 A.

(071131)


Winamp Controller

Winamp control unit with motorized potentiometer and USB interface

By Markus Hirsch (Germany)



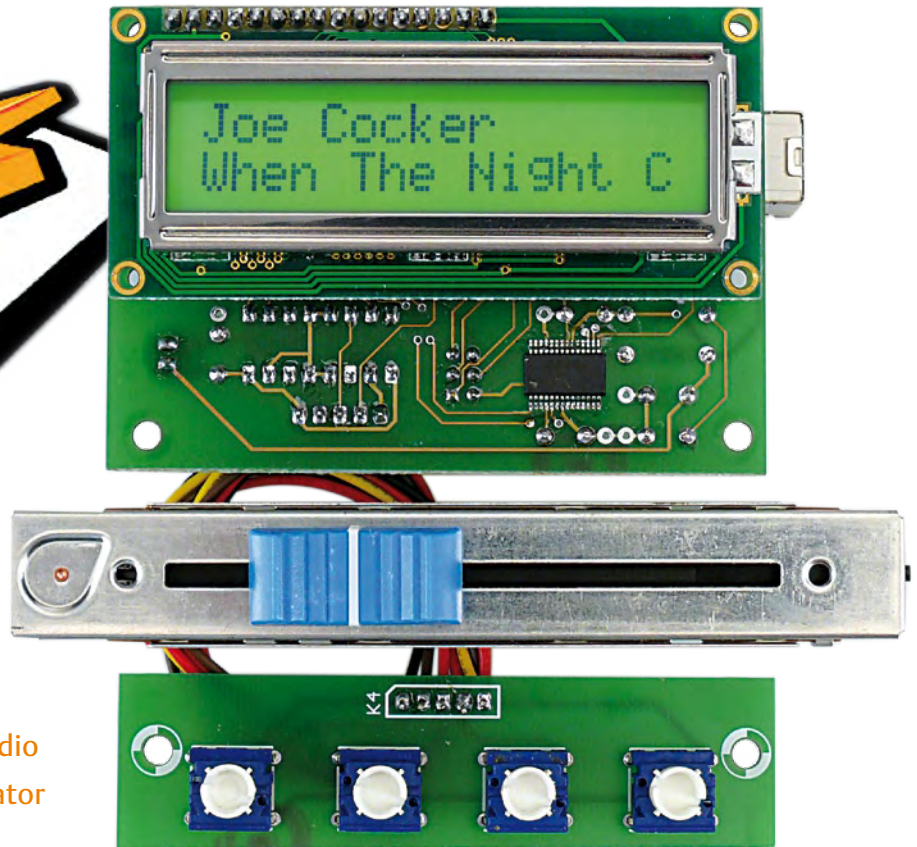This project implements a physical progress bar for Winamp. Here a small ATmega microcontroller uses the USB interface to provide a bidirectional link between the Winamp software and a hardware studio fader, which acts as a combined indicator and entry device.



A variety of remote control devices for Winamp ^[1] and other PC-based media players have been available for a good while. They include infrared interfaces (Winlirc), web browsers (Ajaxamp), and hotkeys on the keyboard. All of these systems have one

thing in common, which is that they are limited to buttons or keys or use virtual progress bars on the computer monitor. If you want to have a complete hardware interface unit with the same level of sophistication as the virtual Winamp design, you need a physical progress bar.

The difficulty with this is that it falls outside the usual scope of electronics for electro-mechanical devices. The solution must be simple and reproducible, and it should be possible to build it without having your own machine shop.

A standard studio fader unit provides a suitable solution. This is a motorized potentiometer, consisting of a linear mono slider potentiometer driven by a DC motor. The potentiometer and motor assembly forms a compact unit that is easy to use (Figure 1). The drive requirements are also relatively simple, so it can readily be integrated with

the software to serve as a physical progress bar. The software also allows its behavior to be modified and optimized relatively easily. You can also use this project as a basis for your own modifications or extensions, since the source code of the Windows program and the AVR firmware is available ^[5].

Hardware

The circuit (Figure 2) uses well known, readily obtainable components. It is built around an Atmel ATmega16 AVR microcontroller. Here the internal oscillator can be used, since the circuit does not require especially high processing power.

A standard LCD module is used to display the song titles. It can easily be driven using BAS-COM AVR code ^[2]. Four simple pushbuttons connected to four I/O pins of the microcontroller are used to control the operational functions of the media player (Play, Stop, Next

Features

- Physical progress bar for Winamp
- Fast forward and reverse using a physical slider
- Power supply via USB port
- Data transfer via USB port
- Song title display on LCD module (2 x16 characters)
- Four buttons for Play, Stop, Next, and Previous
- Runs with Winamp 5.5 (tested with Winamp 5.541)

and Previous). The internal pull-up resistors of these pins are enabled, which saves four resistors on the board. The buttons pull the I/O pins to ground when they are pressed. The connection to the PC is provided by the USB port. This has the advantage that the unit can also be used with relatively new PCs that have only USB interfaces. In addition, the USB interface provides a 5-V supply voltage with sufficient current capacity, so we can dispense with an external power supply for the Winamp controller. A USB/serial converter in the form of an FT232RL IC in the circuit provides the link to the USB port. To ensure that the Winamp controller is recognized by every PC as a USB device and avoid the need to configure the Com port in the Windows program before using the controller, it is necessary to program this FTDI IC with suitable USB descriptors. This is described in more detail later on.

An L293D (IC3) is used to drive the motor of the studio fader. Only one of the two H bridge drivers in the IC is used. As the voltage (5 V) and the current (500 mA maximum) available from the USB port are both somewhat on the low side for the fader used here (see 'Practical aspects'), PWM mode is not used for driving the motor. As a result, the motion of the slider is limited to a fixed speed. The software compensates for this by working in small steps.

The feedback signal that indicates the slider position to the microcontroller is provided directly by the potentiometer, which is wired as a voltage divider connected between the 5 V supply voltage and ground. The wiper of the potentiometer is connected to pin 4 of connector K2, which in turn is connected to I/O pin PA4 of the ATmega. This pin is configured as the input of the internal A/D converter. The voltage on the wiper of the potentiometer is thus digitized and processed in the software as the position value.

As a component designed for use in audio mixing boards, the studio fader has the advantage of a low noise level. This means that the motion of the potentiometer won't interfere with your listening pleasure.

AVR firmware

As already mentioned, the software for the AVR microcontroller has been developed

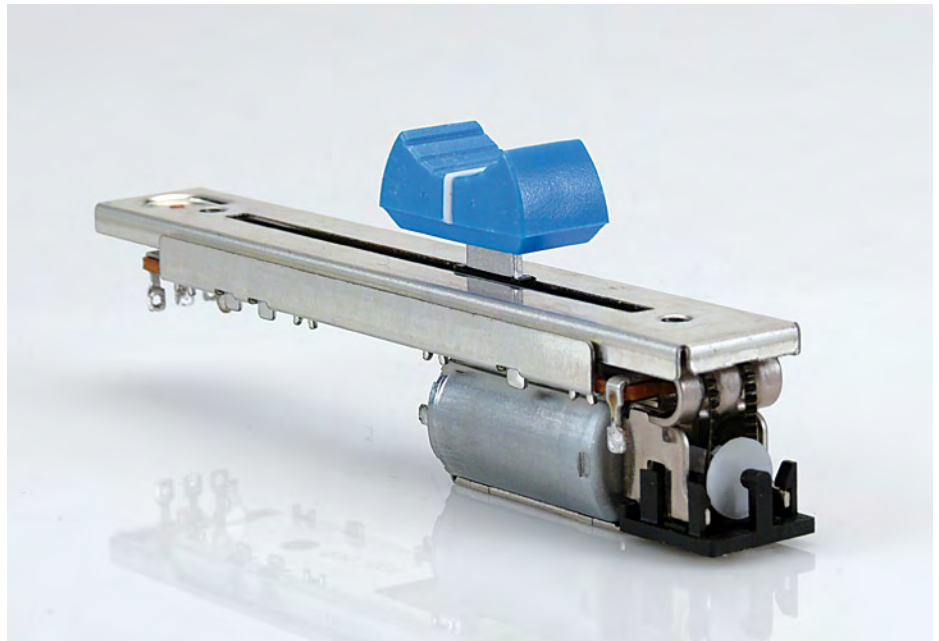


Figure 1. An Alps studio fader is used as a combined indicator and entry device.

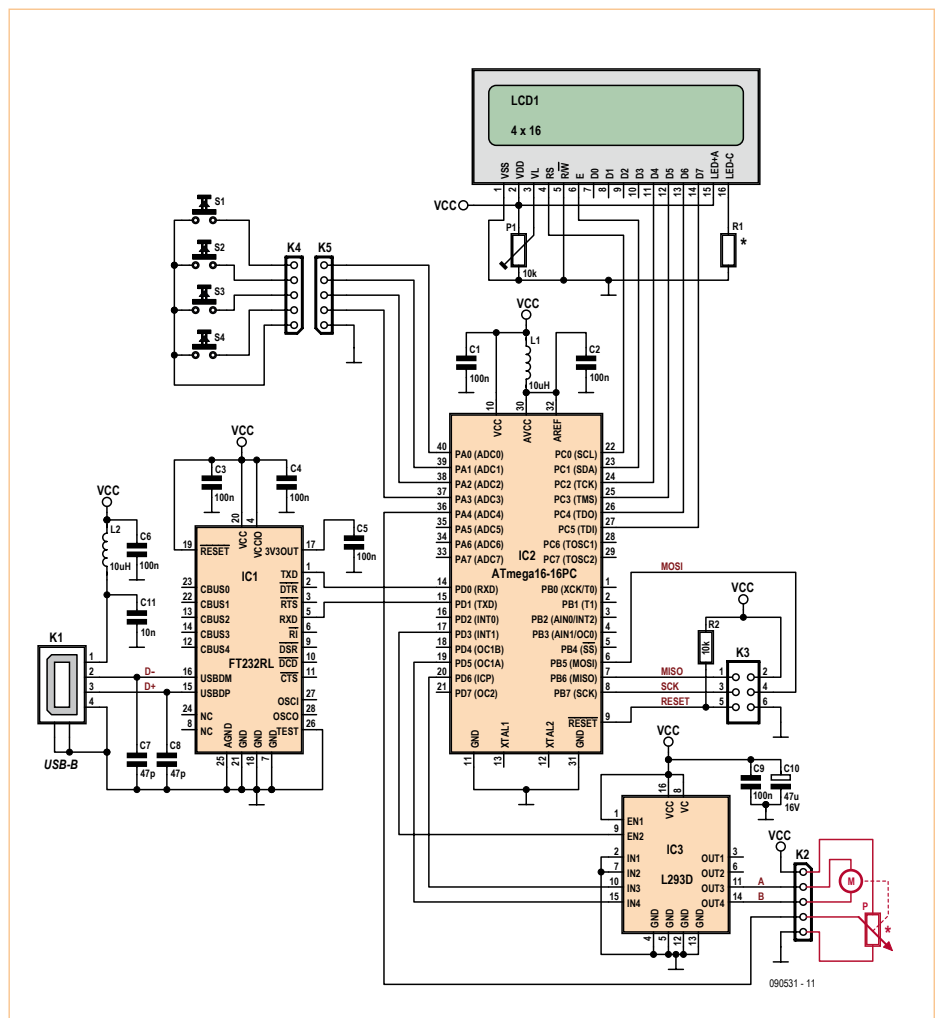


Figure 2. Schematic diagram of the Winamp controller, which the PC sees as a USB device.

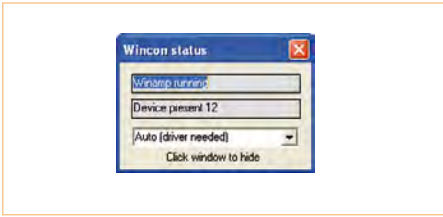


Figure 3. The Visual Basic program Wincon links the external hardware to the Winamp API via USB.

with BASCOM. In normal operation, the software compares the value received via the serial interface with the current position of the slider. If these values differ, the slider position is adjusted accordingly. If one of the buttons is pressed or manual repositioning of the slider is detected, the AVR microcontroller sends the PC a data byte with the new position.

Manual repositioning is recognized based on various trigger conditions:

- The slider value changes while the motor is not energized
- The slider value changes while the motor is energised, but in the wrong direction
- The slider value changes while the motor is energised, but at the wrong speed (the slider is blocked)

Windows software

On the PC side, a small Visual Basic program connects the external hardware to the Winamp API (with the aid of the USB

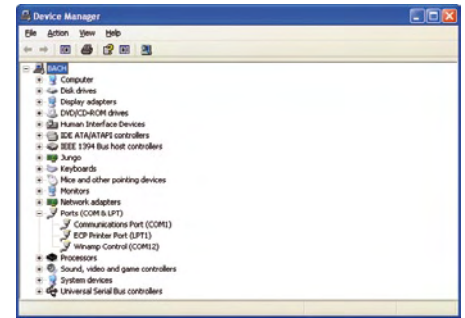


Figure 4. The Winamp controller in Windows Device Manager. The FT232RL designators are programmed to allow the Winamp controller to be recognised as a USB device.

interface). It is not necessary to configure a Com port setting, since the function *Ft_getport()* can determine which serial port is being emulated (Figure 3). If the device

COMPONENT LIST

Resistors

R1 = see text
R2 = 10kΩ
P1 = 10kΩ preset
P2 = mixing desk fader with motor, Alps type RSA0N11M9 (10kΩ) or RS60N11M9 (5kΩ); see text

Capacitors

C1,C2,C3,C4,C5,C6,C9 = 100nF
C7,C8 = 47pF
C10 = 47μF 16V radial

Inductors

L1,L2 = 10μH axial choke, e.g. Bourns JW Miller 5300-13-RC

Semiconductors

IC1 = FT232RL (FTDI)
IC2 = ATmega16-16PU (Atmel), programmed
IC3 = L293D (ST) or L293DNEE4 (TI)

Miscellaneous

K1 = USB socket, type B, PCB mount
K2,K4,K5 = 5-way SIL pinheader,

2.54mm lead pitch

K3 = 6-way DIL pinheader, 2.54mm lead pitch
S1–S4 = pushbutton, 6mm footprint; PCB mount, e.g. Multicomp MCDTS6-5N
LCD1 = LCD module, 2x16 characters, e.g. Displaytech 162C
PCB # 090531-1
Project software, file # 090531-11 from [5]
Kit of parts including PCB, item # 090531-71 from the Elektor Shop or [5]

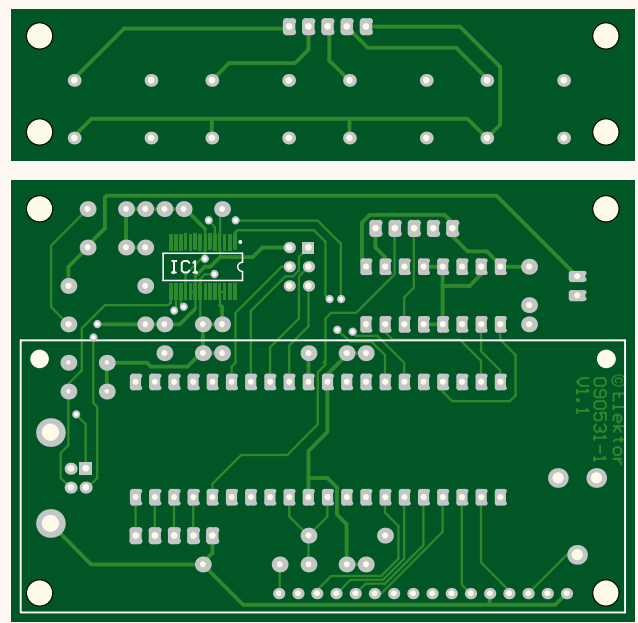
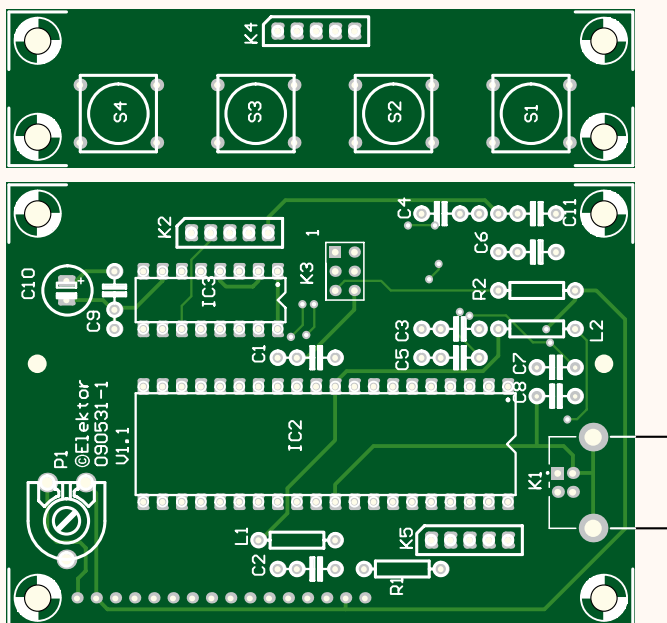


Figure 5. The Elektor lab prototype of the Winamp controller.

is not connected, no connection is found and an error message is displayed.

The program has to perform only three simple tasks, which allows it to be very compact and tidy:

1. The current position of the virtual progress bar in Winamp is sent to the hardware every second.
2. If the external hardware reports that the fader has been repositioned manually, the software executes a 'fast forward' or 'fast reverse' to the corresponding position in the song.
3. If a new song is played, its title is sent to the hardware in 32-bit format.

If Winamp is not running, an error message is displayed or the icon in the system tray turns red.

The software can be modified or extended using the free Visual Basic Express development environment [3]. For example, you could change the functions of the control buttons.

When one of the four buttons is pressed, a value in the range of 251 to 254 is sent. The value range from 0 to 200 is reserved for the slider position.

FT232RL programming

The benefits have already been mentioned briefly: if the descriptors of the FT232RL are programmed properly, Windows programs (such as programs generated in Visual Basic) can recognize the USB device and independently detect the associated Com port (Figure 4).

This requires changing the product description of the FT232RL into 'Wincon'. The drivers for the USB-to-serial converter are usually available on the Windows system, so no installation will be required. The PID and VID however have to remain at the original FTDI value. The free FTProG program from FTDI [4] is used here for programming. This program is well documented. A XML file available on the Elektor website [5] for free downloading is used for device programming. If you want to make do without this step you may select a COM port manually in the VB program. The source code of this program is also included in the downloadable Zip file.

If it is desired to retrofit the automatic COM port function to your own project, all you have to do is change the product name into 'FT232L' and convey the relevant string as a parameter to the FT-getport() function.

Practical aspects

A printed circuit board (Figure 5) has been developed for assembling this circuit. It consists of two parts: a microcontroller board and a keypad board with four buttons, which can be separated from the microcontroller board. Assembly is straightforward, with the exception of the FT232RL (IC1). It is the only SMD component in the circuit, and it is fitted on the underside of the board. With a bit of practice, the SSOP-28 package (lead pitch 0.65 mm) can be soldered reasonably well by hand.

The LCD module is also fitted on the underside of the board. It can be plugged in using pin and socket headers (see Figure 6). The value of R1 should be chosen according to the LCD module that is used. If a

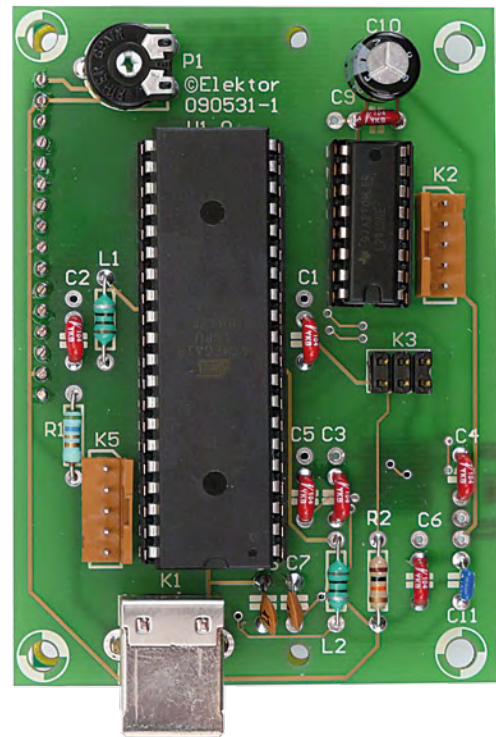


Figure 6. The fully assembled lab prototype PCB.

Advertisement

THE ORIGINAL SINCE 1994

PCB-POOL®

Beta LAYOUT

Servicing your complete PCB prototype needs :

- Low Cost - High Quality PCB Prototypes
- Easy online Ordering
- Full DRC included
- Lead-times from 24 hrs
- Optional Chemical Tin finish no extra cost

NEW! **FREE LASER STENCIL WITH ALL PROTOTYPE PCB-ORDERS**

Watch "ur" PCB®
Follow the production of your PCB in **REALTIME**

email : sales@pcb-pool.com
Toll Free USA : 1 877 390 8541
www.pcb-pool.com

Beta LAYOUT

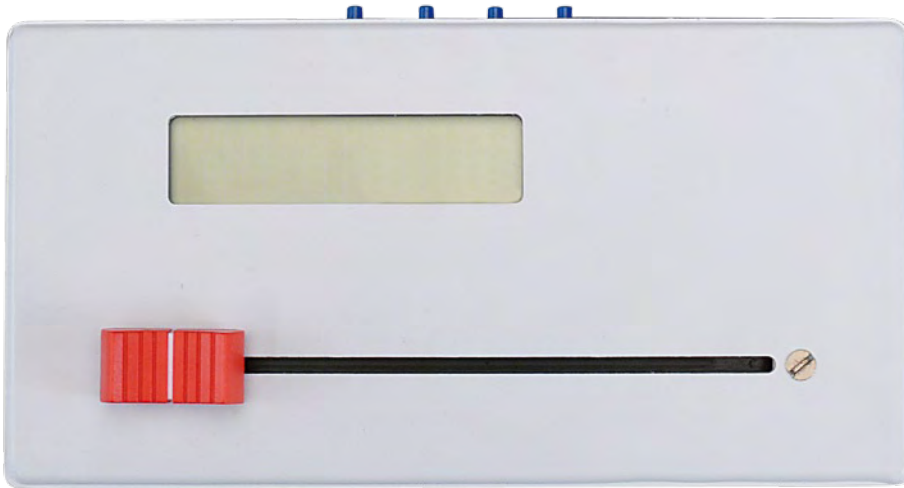


Figure 7. The author's prototype.

module without backlighting is used, pins 15 and 16 of the LCD module are not used and R1 can be omitted. The prototype was built using a module with a green backlight, with pin 15 connected to the anodes of the backlight LEDs and pin 16 connected to the cathodes. In the circuit diagram (Figure 2), pin 15 is connected to +5 V and pin 16 is connected to ground by R1. The voltage across the LEDs (U_L) is specified in the LCD data sheet as 4.2 V, with a typical LED current of 160 mA. This yields the following value for R1:

$$(5\text{ V} - 4.2\text{ V}) / 0.16\text{ A} = 5\ \Omega$$

We used a value of 5.6 Ω in our lab prototype. If you use a display module with a different type of backlight, you should adjust the value to match the LED current recommended by the manufacturer. For example, a model with a visually more attractive but more expensive blue-white backlight has a much lower LED current (around 15 to 40 mA). The microcontroller can be programmed in

circuit using a suitable programmer, such as Elektor USB AVRprog or AVRISP Mark II, via the ISP port on the PCB (connector K3). The kit of parts on sale for this project contains a ready-programmed microcontroller.

The author used a readily obtainable Alps studio fader for the motorised potentiometer. Two versions are available from catalog distributors such as Mouser, Reichelt and Conrad Electronics: one with a 5-k Ω potentiometer and 60 mm slider travel, and another (slightly more expensive) with a 10-k Ω potentiometer and 100 mm slider travel. The author used the latter version in his prototype (Figure 7), while the smaller 5-k Ω version can be seen in the photos of the Elektor lab prototype. Both versions can be used, although we recommend the 10-k Ω version due to its longer slider travel.

The only wiring that is required is to connect the studio fader and the keypad PCB to the microcontroller PCB. The slider potentiometer is shown in the schematic diagram with its leads connected to pin 1 (+5 V), pin 4

(slider) and pin 5 of K2, while the motor leads are connected to pins 2 and 3 of K2. If the slider motion matches the progress bar on the monitor after the unit is put into service, the polarity of the motor lead connections is correct. Otherwise (or if the slider does not move) the motor leads must be reversed.

The prototype can be admired in action in a video clip^[5] produced by the author.

In normal operation, with the device connected and Winamp playing an MP3 file, the PC sends the current progress bar position to the device and the slider is continuously moved to the corresponding position. When the song ends, the slider returns to its initial starting point. If you use the mouse to change the position of the virtual Winamp slider while a song is playing, the slider of the fader also moves to the corresponding position.

Thanks to the dual operating mode, the studio slider in the circuit can also be used as an input device. If the slider is moved manually, the motion is detected by the AVR microcontroller and motor-driven operation is stopped immediately. If after this the slider remains in the same position for a certain length of time, its position is sent to the PC and the Windows program moves to the corresponding position in the tune. The four buttons can be used to change to the previous or next song or to trigger the Winamp Play and Stop functions. The song title is shown on the LCD module in two lines of sixteen characters each. If you don't see anything on the display, it may be necessary adjust the display contrast with trimpot P1.

090531-I

Internet Links

- [1] www.winamp.com (Winamp)
- [2] www.mcselec.com (BASCOM AVR)
- [3] www.microsoft.com/express/vb/Default.aspx (Visual Basic Express)
- [4] www.ftdichip.com (FT232RL driver documentation and programming tool)
- [5] www.elektor.com/090531 (Elektor project web page)
- [6] www.diamantic.com/projects/electronics/021 (author's Winamp controller demo video)

About the author

Markus Hirsch was born in Hanover in 1978 and grew up in Vienna. During his course of study in precision mechanics at the University of Hanover, he discovered his passion for digital electronics — even though this had little in common with his main course of study. After working several years in a medium-sized industrial firm (ultimately in a quality assurance position), Markus completed a course of study in electrical engineering at a technical college. He now enjoys combining his two fields of knowledge.


E-mail: markus.hirsch@diamantic.com

Website: www.diamantic.com

Problem #1: rainy day, 200 miles to go, chain lube spray / forgotten / empty / under loads of baggage.
Problem #2: Touring with buddies who have shaft driven bikes. Take a break and think it's a good time to oil the chain. "What the #%^ are you doing? Got a problem with your bike?" That's enough! Something must be done. Bulky shaft driven bike? No thanks. Belt driven? Phew! How about an automatic chain oiler?

To keep things simple, let's ignore the motor's inductance. To justify this simplification, the motor is powered by a constant current source. Some analog circuitry will be needed — can't be helped.

The circuit of which the schematic is shown in **Figure 1** and the wiring diagram in **Figure 2** gets its supply voltage from the bike's

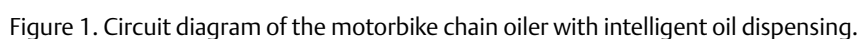

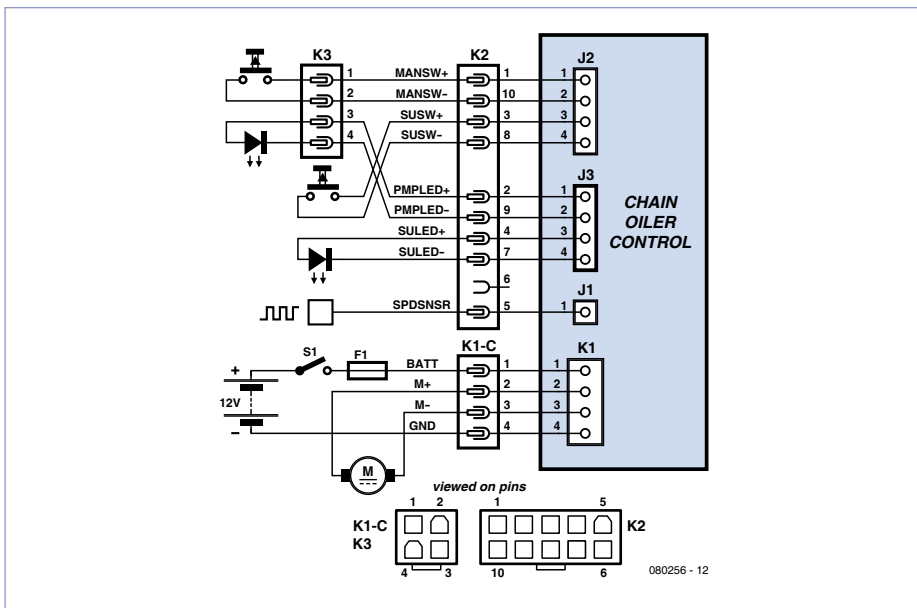


Figure 2. How to connect the unit to various signals and wires on the bike (example: Suzuki SV650S).

battery via the ignition switch and a fuse (5 A). Power for the windscreen washer pump is switched by power transistor T1 which gets its control from a PIC microcontroller via driver T2. The return current from the motor is passed through current measuring resistor R7. When the motor current reaches its high limit, transistor T3 starts to conduct and ‘steals’ base current from transistor T2. This results in T2 and consequently T1 being cut off. Negative voltage spikes due to the motor coil(s) being switched off suddenly are shunted off by flywheel diode D1. The motor voltage is measured by op amp

IC2D which is connected as a differential amplifier. The amplification factor of 0.27 scales the motor voltage (max. ~14 V) down to the PIC’s safe measuring range (max. 5 V). The motor current is sensed by R7. Differential amplifier IC2.C then amplifies the sense voltage by 2, resulting in a total amplification of 1 V/A.

The ‘simulated tachometer signal’ for the motor speed measurement is realized by subtracting the (calculated) voltage drop due to the motor’s internal resistance (R_s) from the total motor voltage. This is done by IC2.B which is connected as an asymmet-

rical differential amplifier. The amplification for the non-inverting input (i.e. motor voltage) is unity (1). The total amplification for the motor voltage is thus: $0.27 \times 1 = 0.27$. The pump motor used was found to have an R_s of 1.0Ω . So, the voltage drop due to the R_s is 1 V/A which happens to be the same ‘slope’ as that of current measuring op amp IC2.C. Because the motor voltage is scaled down by 0.27, the voltage across R_s must also be scaled by the same factor 0.27. Thus, the amplification for the inverting input is 0.27.

Referring to the labels in the circuit diagram we have:

$$\begin{aligned} \text{MEASVOLT} &= 0.27 \times \text{motor voltage} \\ \text{MEASCURR} &= 1 \text{ V/A} \times \text{motor current} \\ \text{SIMTACHO} &= 0.27 \times (\text{motor voltage} - 1 \text{ V/A} \times \text{motor current}); ([\Omega] = [\text{V/A}]) \end{aligned}$$

The measured signals are connected to the PIC’s (analog) inputs via low pass filters. Diodes D4, D5 and D6 clamp excessive input voltages to safe levels.

The type LM224 op amp is used because the common mode range of its inputs reaches GND and the output can go down to GND as well. However, the sink current of the LM224 is very small when the output is near GND, so pull-down resistors are connected to the outputs.

The digital part is quite straightforward. Pulses from the speed sensor on the bike are connected to IC2.A but noise spikes are filtered out first. IC2.A’s input impedance is high (100 k Ω) to prevent excessive loading of the speedometer electronics. The op amp is configured as a Schmitt trigger and its output is taken to a PIC digital input via resistor. Diode D3 clamps the input voltage to the safe level. The Schmitt trigger and the low pass filter are designed based on the speedometer signal present on a Suzuki DL/SV650.

Both switch inputs on J2 have pull-up resistors with small capacitors connected in parallel to eliminate noise spikes.

The PIC16F676P is configured to use its internal 4 MHz oscillator so a dedicated crystal is not needed.

There are two supply rails: +12 V and +5 V. The +12 V is taken from the bike battery through diode D2 and it powers op amp IC2 as well as voltage regulator IC4. The regula-

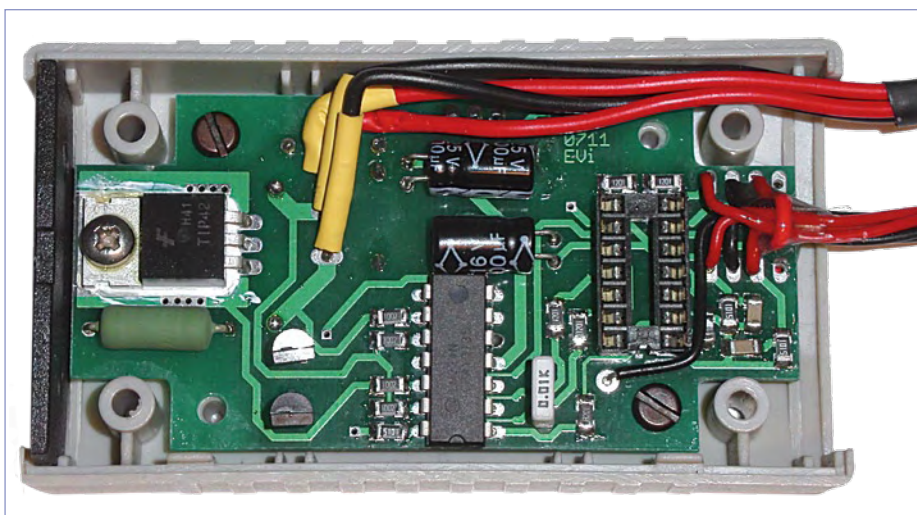


Figure 3. The board is double-sided and has a mix of SMD and through-hole components.

tor is the ubiquitous 7805 and it powers the rest of the control electronics.

Software

An assembly code program was developed under Linux using these 'gputils' (tools): gpasm, (assembler/compiler) and gplink (linker) [2]. For Windows there is a free (assembler) development environment available from Microchip called MPLAB IDE.

The final firmware is transferred to the PIC micro using the 'Tait' classic programmer and ICprog software under Windows XP. ICprog requires that the NT/2000/XPparallel port driver be installed on the system. A more contemporary alternative to use is the Microchip PICKit 2 or one of its clones.

The program has the following functions:

- Rain / Dry setting at start up.
- Manual start of oiling sequence.
- Automatic lubricating with two adjustable parameters: (1) travelled distance between oiling sequences and (2) pump 'on' time during oiling sequences.

The commented source code as well as the HEXcode files are available free from the Elektor website [3].

Construction hints and operation

Because space is at a premium in a modern motorbike, it is suggested to build the circuit on a double-sided PCB populated with SMD as well as through hole components. The author's PCB design may be downloaded from [4]; Eagle and Gerber formats are supplied. Soldering should not be a problem because no extremely small or multi-pad SMD components have been used. The PIC microcontroller should be mounted in a high quality IC socket. Diode D2 is placed between connector pads and it might be good idea to leave some clearance between it and the PCB surface. **Figure 3** gives an impression of the finished board. The PCB is designed to fit into a Kemo type G111 plastic case with dimensions 90x50x25 mm. Due to the limited space (mainly height) inside the case, the connection wires are soldered directly to the PCB. Wire-to-wire connectors are used outside the case.

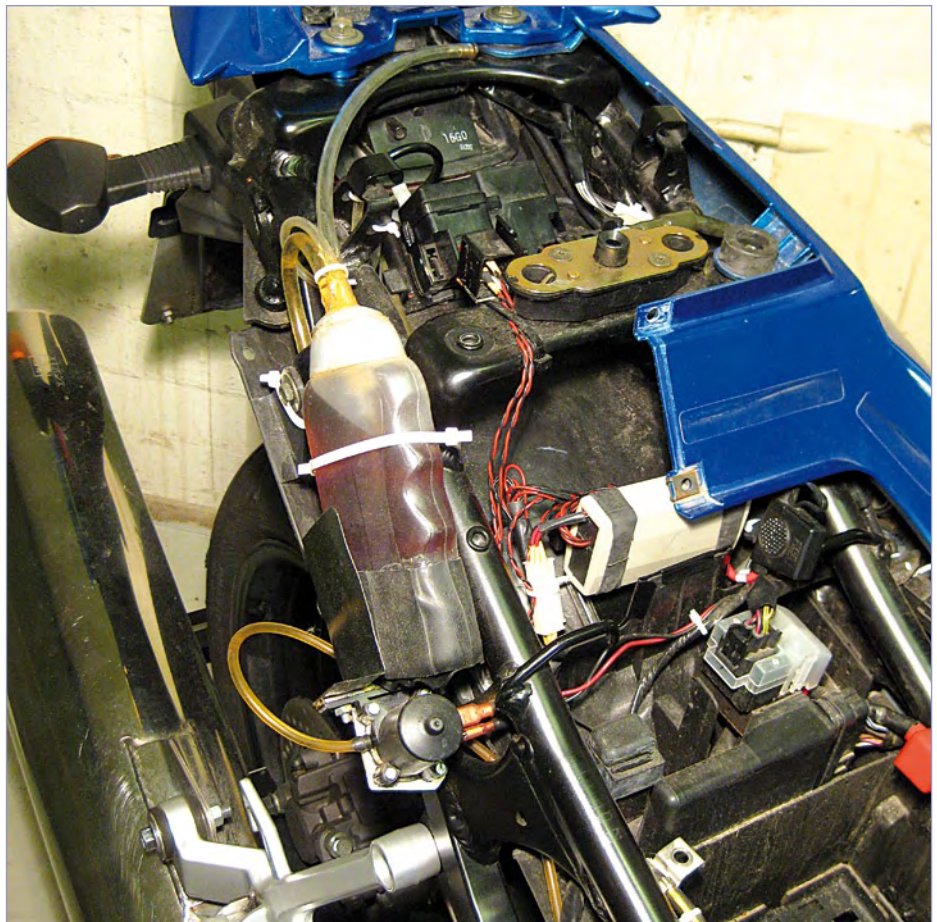


Figure 4. Suggested mounting of control circuit, pump and oil 'tank' on a Suzuki SV650S motorbike.

Finally, the operation of the unit by means of the two pushbuttons is described in a document called *080256-W.pdf* included in the project download at [4].

(080256)

Internet Links

- [1] www.24.fi/mcjaykat
- [2] <http://gputils.sourceforge.net/>
- [3] www.elektor.com/080256



Figure 4. Rather than dripping oil on the chain and spilling most of it while riding, the dispenser lubricates the rim of the chain wheel.

Femto OS

A tiny multitasking operating system for microcontrollers

By Clemens Valens (Elektor France Editorial) and Jerry Jacobs (Elektor Labs)

Do small embedded systems need a multitasking operating system? Can't you just program everything in one big loop? Sure. But have you ever noticed the wait between switching on your DVD player and the first signs of the drive responding to the Play button? We bet that there is no OS inside, just a big loop. It is easy to do better since there exists an OS for even the smallest of microcontrollers.



The next question is: do you have to write one yourself? On Wikipedia ^[1] almost one hundred are listed already, but ignoring the proprietary systems and those that are not under active development, the list is actually much shorter. Probably the only one that will fit into 8 KB of flash memory and 512 bytes of RAM and still do something useful is Femto OS ^[2]. It was written by Dr R. Vlaming MSc. to be a general-purpose OS, useful in many different applications. The word 'femto' (10^{-15}) in Femto OS indicates that the OS is very small indeed.

Goals

Femto OS is a multitasking real time operating system (RTOS) with a fairly generic design. It is portable and currently ported to 44 of Atmel's AVR microcontrollers. It is open source and licensed under GPLv3. Femto OS differs in several respects from other operating systems. First of all Femto OS is extremely economical with RAM and flash memory. Only the things you really need get compiled into the kernel. For example, you can run eight independent LED blinking tasks within 1 KB of flash and just 47 bytes of RAM. Or you can run a shell, serial communications (so you can log into the device) and eight other tasks on an ATtiny861 (8 KB flash, 512 bytes RAM). We sincerely believe that Femto OS is the smallest OS on the planet. The code is well documented too.

Why use a multitasking OS?

Often, when a microcontroller is performing a task, it waits in an infinite loop until something happens — a button press for example, before it will do something like switching on or off a light. In pseudo code:

```
forever do
{
  wait for yellow button to be pressed;
  invert yellow light state;
}
```

Now suppose you have two buttons and two lights. The following program does not work well (can you see why?):

```
forever do
{
  wait for yellow button to be pressed;
  invert yellow light state;
  wait for blue button to be pressed;
  invert blue light state;
}
```

so we have to do something like

```
forever do
{
  wait for yellow or blue button to be pressed;
  if button was yellow then invert yellow light
  state;
  if button was blue then invert blue light
  state;
}
```

But wouldn't it be much simpler if we could use two loops that

Getting started with Femto OS

There are two ways of getting started with Femto OS: the easy way and the hard way. Both ways start with downloading the Femto OS distribution from the Femto OS web site ^[2]. In the archive file for this article you will find a readme file. Read it, it's highly detailed and contains lots of useful information.

The easy way is to use Femto OS with AVR Studio ^[6] and WinAVR ^[7], but this only works with Windows. You have to download and install these two programs and then run the install_avrstudio_workspace.bat file that's included in the Femto OS distribution. That's it, you're done! Our example is presented as an AVR studio project and you could copy it into the IDE/studioprojects folder of the OS distribution.

The hard way, for those who like to know everything, is also detailed in the readme file. The hard way works on Windows, Linux and Mac.

It involves setting up your own Femto OS tool chain, building everything (yes, everything, the compiler too) from scratch. In our experience this is only for the real geeks and it never works, but we gave it a try anyway. So we did install Cygwin (this was on a Windows Vista machine), downloaded the special packages, ran the configuration scripts, built the whole kit and caboodle and what say: no errors! OK, it took five hours and 200 MB but then we were able to compile a 258 byte program! To be honest, we did run in an annoying Windows Vista security problem: we (administrators) were not allowed to access the Femto OS source files... Using the file properties the security settings were changed to get 'total control' and then it worked. To discover this it's necessary to inspect the compile_results file in the MainCode\binaries\ folder of the Femto OS distribution. Alternatively, take the easy way...

would be executed in parallel? Like this:

```

forever do
{
  wait for yellow button to be pressed;
  invert yellow light state;
}

forever do
{
  wait for blue button to be pressed;
  invert blue light state;
}

```

This is the premise of the multitasking OS—you can have one or more 'tasks' that are executed simultaneously, allowing you to reduce program complexity.

A typical multitasking OS design

Figure 1 shows the flowchart of a typical multitasking OS. After some system initialisation (the timers of the AVR for example) the scheduler takes over. The scheduler keeps a list of all tasks and selects one of the tasks to run. Which task has to be started next will depend on its priority (more important tasks go first!) and, with priorities being equal, which tasks did not yet run. This is called **round robin**. Once a task has been selected the context for that task is restored, and execution resumes at the point where the task was halted earlier on.

What does that mean 'the context is restored'? Program execution is no more than bit manipulation of the registers of the CPU and the memory. When a program resumes execution after being interrupted, at least the registers it was working with should contain the same values as before the interruption. So a 'context save' makes sure that the regular working registers of the CPU—the Status Register and Program Counter—are saved in a special area of memory

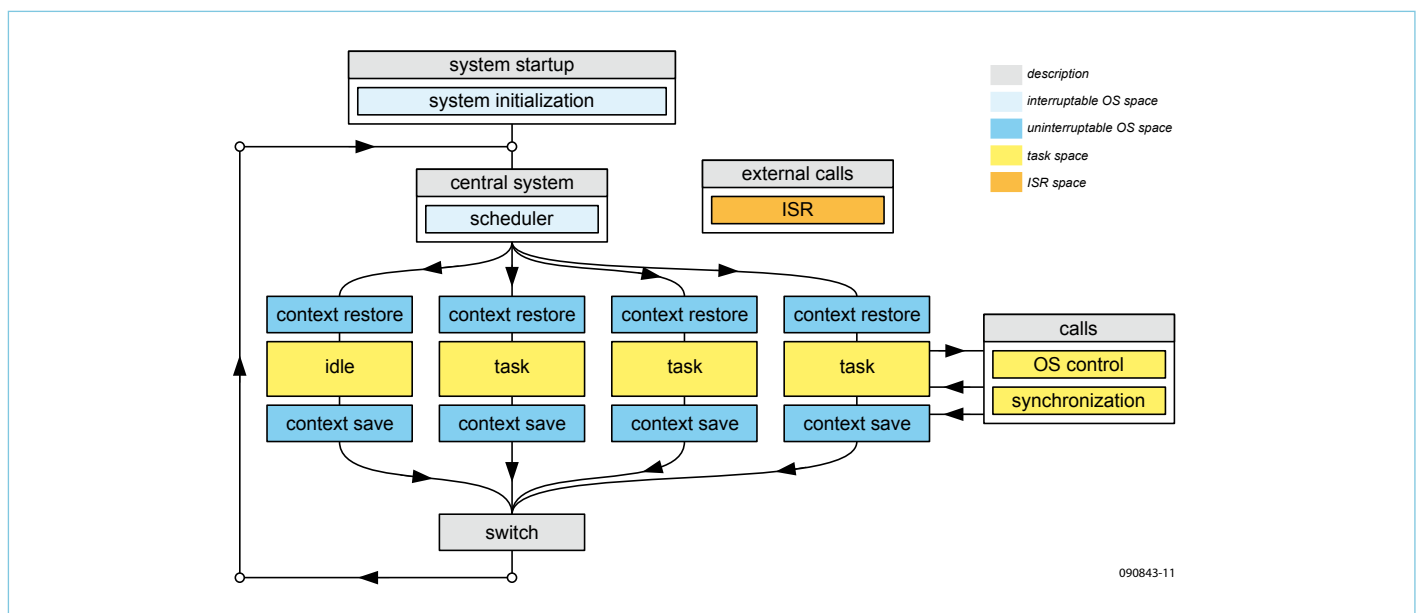


Figure 1. The flow chart of a basic operating system.

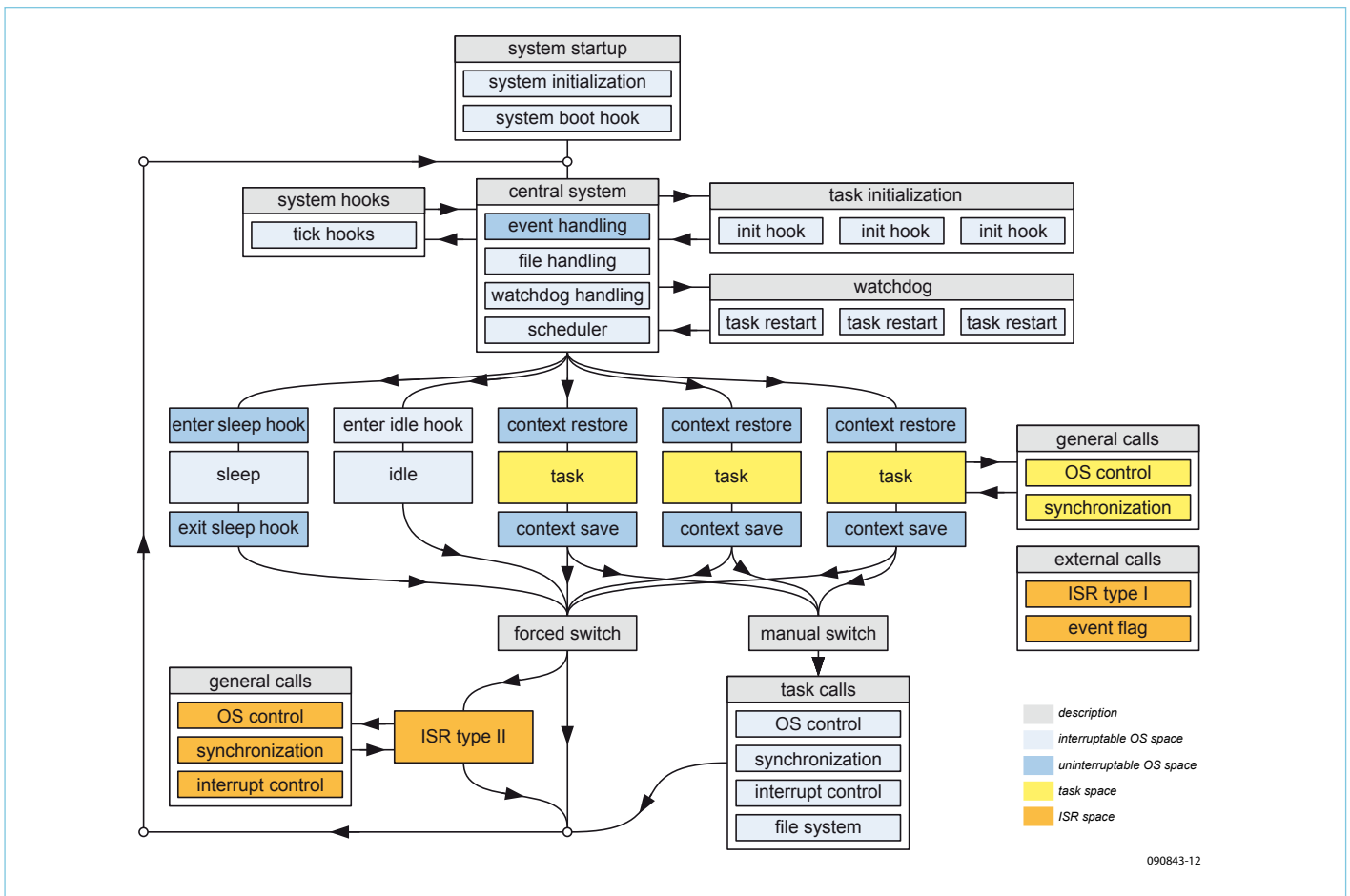


Figure 2. The flow chart of Femto OS is a bit more complicated than the one in Figure 1, but not that much.

where the program stores return addresses and temporary variables: the **stack**. The stack pointer itself must be saved at some fixed location. Just before the end of the interruption, the register values are read back from the stack and written to their original locations. This is a context restore. If the context save and restore are done properly, a program never notices that it was interrupted. When a task has run for a while, the OS takes control again by interrupting it, usually by means of a timer interrupt, the so called *tick interrupt*. Immediately after the interruption, the context of the task is saved and its state is frozen. We have now reached the block named switch in **Figure 1**. The process is called **pre-emption** because the task cannot refuse this interruption. The task control block (the memory that holds all the information about a task) is updated, and the scheduler selects a new task for execution. If there are no tasks ready to run — they may all be waiting for something — the scheduler selects the idle task, which does nothing. It can happen that a task wants to call a function that controls the OS, or a task may want to communicate with another task, so it might call some synchronisation functions. In such cases the task no longer needs to run and it may dedicate the execution time left to other tasks. The task switch is now voluntarily (so-called **cooperative** operating systems work solely on this basis). As discussed, the context save and restore ensure that the environment of the task that's allowed to run is identical to its environment when it was switched out. But what about the rest of the memory? Or indeed the registers of the peripherals? For the most part,

it doesn't really matter since the task never uses it. And for the part the task is using, it will often be the only one using it, so this part will not be touched when the task is not active. What remains are the registers in use by more than one task. How is this organised? Well, it isn't. It is your responsibility. Of course the OS offers some synchronisation tools and semaphores to make life a bit easier, but you, the application builder, have to be careful. If you aren't, tasks may deadlock forever.

This is about all there is to the design of a clock driven pre-emptive multitasking operating system. Of course, there are all kinds of other exotic designs out there, but for the discussion about Femto OS this backdrop will be sufficient.

Femto OS features

In **Figure 2** you will recognise the generic OS design from Figure 1 but also notice many new blocks. First of all, we have a system initialisation with a global boot hook and every task has an initialisation hook, which are places where you can add custom functions to initialise, for example, hardware before your tasks start. These are one-time initialisations.

The block 'central system' contains a few more gadgets. Event handling takes care of possible events that you may have initiated. These are used to quickly fire up a task from an interrupt or other task. Subsequently, file handling unblocks possible tasks that were waiting for an EEPROM write operation to end. A watchdog tests for tasks that are no longer responding and that may need to be

Timing models


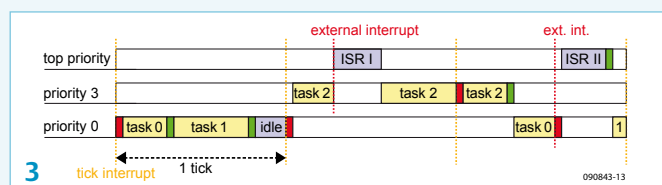


Figure 3 shows an example of how tasks execution evolves over time. The horizontal axis represents time, the vertical task priority. This snapshot of the system starts with a forced context switch (red rectangle), followed by execution of task 0. After a while this task transfers execution to the OS; a manual context switch takes place (green rectangle) followed by the execution of task 1. If it also happens that task 1 does not need the full time, it requests a manual context switch again and the rest of the tick time left is spent in the idle state. In the mean time task 2 has woken, and since this one has a higher priority, it takes precedence.

During execution of task 2 an interrupt takes place which is handled immediately. After completion of the ISR, task 2 continues until it gets interrupted by the tick interrupt. Unfortunately, task 2 hadn't finished yet, but since it has the highest priority it is rescheduled. When done it yields control to the OS who reschedules task 0.

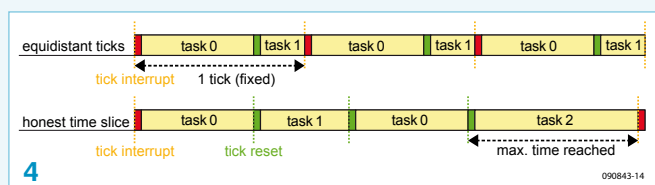Then an interrupt arrives that forces a context switch before starting the ISR. When the ISR completes no context needs to be saved, but the context of task 1 must be restored. Note that, although task 0 has not yet finished, task 1 is scheduled anyway. This is because the OS has no way of knowing if a task has finished or not, so it assumes it is.



Normally, ticks come at equidistant time intervals, which is fine for most situations, but not for all. To illustrate this, have a look at **Figure 4**. In the upper time line you see two tasks running. Since task 0 uses most of the time between the ticks (but not all of it) there is little time for task 1 left. But, because it did run, the OS will restart task 0 after the tick interrupt. This goes on and on and may lead to starvation of task 1. In extreme cases it may even execute a few instructions only. Although such situations are rare, they do occur and can be hard to track down.

Femto OS lets you use another timing model, called **honest timing**. In this case, at program start the tick interrupt timer is reset so every task gets a full tick time to run. If the task completes before the next tick arrives, the timer is reset for the next task. The tick counter keeps on counting regular ticks (for these are deducted from the sub tick counter) although it may lag a little. Observe that in this model task 1 does not starve. In fact, this allows another possibility: variable time slices per task where each task has its own maximal time slice. This can be very handy if you know beforehand that a particular task needs a little more time than one tick to complete and it may reduce context switch overload considerably.

restarted. This is a useful option for checking if a communication bus is still busy and removes the need for countless timeout checks throughout the program. And lastly the scheduler selects a task following the simple prioritised round robin scheme.

Besides starting a normal task, the system can go into idle mode, which is not a task but simply a power saved state in OS space. The system can also go to sleep (if supported by the hardware). This is a special power down mode of the chip that includes the tick interrupt.

Just as in the generic OS, tasks can be interrupted by the tick interrupt or by a manual switch. But in contrast with the generic OS, the Femto OS control calls take place in OS space for most functions, hence force a manual switch first, after which the operation is executed. This way the task stack is not used for these operations, and thus the task stack size can be smaller. In Femto OS most calls that directly force a context switch are called taskXXX and may only be used from within a task. In addition to that, there are also general calls, starting with genXXX that may be called from within tasks as well as from interrupt service routines. They do not force a context switch and are executed in the same space as the one they were called from and are usually very quick.

Femto OS provides everything you need for safe inter-task communication. This is important when two (or more) tasks need to share data or access the same register. **Mutexes**, **queues** and **rendezvous** are therefore fully supported. We do not have enough space here to dig deep into these advanced concepts, but as a potential Fem-

to OS user it is good to know that the tools to handle this properly are available.

Controlling relays...

It is all very well to know how an OS works in theory and how useful it is etc., but we are hands-on people and we want to play with it. Nothing beats a real-life example to illustrate how things work in practice. Elektor has published many AVR-based boards so we decided to reuse one of these. We went for the ATM18 board ^[3] to try Femto OS on. To make it more interesting we also added the I/O port expander (071035-5) with the relay extension card (071035-6) ^[4].

The ATM18 board sports an Atmel AVR ATmega88 microcontroller with 8 KB program flash and 1024 bytes SRAM memory. Because Femto OS has a very small memory footprint there is enough memory for a pretty big application with multiple tasks. We prepared a simple application that nicely illustrates how three tasks can make a programmer's life much easier. Of course you can download the source code from our web site ^[5].

...using multitasking

The first task is a data output task. It writes data to the shift register of the port expander board over a synchronous bus. The port expander controls eight relays. This kind of communication is a good target for a task. The application only has to send data to the task and the task will make sure that the bits and bytes are transmit-

Why would I want an OS on my microcontroller?

Most people do not understand why you would want an operating system on a microcontroller, yet everybody wants one on his PC. The first PC with its 8088 5 MIPS max processor wasn't a lot more powerful than a modern small microcontroller but yet we all wanted a DOS (disk operating system) on it. And these early operating systems weren't even multitasking.

The reason for this is probably that most people think of Windows, Linux or Mac when they hear 'OS' and how would you squeeze *that* in an 8-bit microcontroller? Within the context of Femto OS, these big operating systems look just like an Airbus A380 compared to small

remote controlled indoor helicopters. Yet they both fly.

An operating system is useful when you have many peripherals, and modern microcontrollers come loaded with these. The operating system takes care of many low-level tasks to control the peripherals and makes life of the application programmer easier. That's why you want an OS, to relieve you from the tedious tasks of handling time-outs everywhere, to do the bit-banging for you, to process interrupts properly. If you use an easily portable OS, you can run your application on many different processors without modifications. Reuse your code and save time and money, just by using an OS.

ted in the right way. While the task is doing just that, the application can do something else.

A second task reads the state of the five switches that live on the ATM18 base board. The switches connected to port lines PD0-3 control the relays and the switch connected to PD4 selects between the two rows of four relays (RE1-4 and RE5-8) on the relay card. The switches are connected to 0 V and have an internal pull-up set on the port, so they are read as 'zero' when they are pressed.

Finally a third task provides some visual feedback by controlling two LEDs to show which row of relays is selected. If LED1 lights up the relays RE1 to RE4 are selected, else LED2 lights up indicating that the relays RE5 to RE8 are selected. The LEDs are connected to PB0 and PB1.

If you look at the application file, the one with 'Elektor' in its name, you will find only a few functions and no 'main' (the main can be found in "femtoos_core.c"). So how does this work? With Femto OS you have to decide at compile time how many tasks you intend to run. That's how the OS can be so small. A special configuration file is used to tell the compiler what parts of the OS it should include and which functions are the actual tasks. If you want to understand in detail how the configuration process works, you are in for a long voyage through pre-processor land. For a quick start it is easier to just use the example configuration file "config_application.h" and change the parameters you need (only change the ones you understand).

Under the header "TASK NAMES" you define the names of your tasks (Display, Speed and Switch in our example). Then, under the header "INCLUDE TASKS" you tell the compiler which tasks should run. In the application file you should provide a function for each task with a name that starts with "appLoop_" followed by the name of the task (appLoop_Switch, appLoop_Speed & appLoop_Display in our example). If you do this correctly the Femto OS core will call your tasks at runtime. You now have sort of as many main functions as that you defined tasks (up to 16).

This example only shows a small piece of the many capabilities of Femto OS. In the OS distribution available at ^[2] you can find several other examples that you could try on the ATM18 board.

Refer to the *Getting Started* document supplied with the Femto OS frame to learn how to, well, get started! Once you are up and running, you can try our example.

Nice, but I am not convinced

After reading about our example some of you will remark that they can do the same thing using interrupts and loops etc. You are right; you do not have to use an OS. But take a good look at our example and notice how simple it really is. We only wrote the file that has 'Elektor' in its name and configured some settings. If you were to write this application using interrupts or polling you can look forward to spending a lot of time testing and figuring out how to get it working properly. You can save this time (and several headaches) by letting the OS handle it for you. Let other people do the hard work for you while you are having a beer.

(090843-I)

Links and references

- [1] http://en.wikipedia.org/wiki/List_of_real-time_operating_systems
- [2] <http://femtoos.org>,
this text is partly based on the Femto OS user's guide
- [3] ATM18 AVR Board, Elektor, April 2008
- [4] ATM18 Relay Board and Port Expander, Elektor, October 2008
- [5] www.elektor.com/090843
- [6] www.atmel.com/avrstudio
- [7] winavr.sourceforge.net

External interrupts

Femto OS can handle external interrupts in two ways: by setting an event flag or by using an interrupt service routine (ISR). The event flag can be used to wake up a high priority task which is waiting for this event. This task will then run at the next tick interrupt.

There are two ISR flavors: ISR I and ISR II. An ISR of type I can be reached after an interrupt from (almost) anywhere in the program,

whether it is in task space or OS space, but it has limited functionality. An ISR of type II can only be reached from within a task. If such interrupts happen while the OS is running, their execution will be postponed until a task is started. Such interrupts can also force the currently running task to yield just before or right after the execution of the ISR.

The loudest!

By Ton Giesberts (Elektor Labs) &
Thijs Beckers (Elektor Netherlands Editorial)

Elektor Live! 2009 was almost there. In the weeks leading up to the event, Ton Giesberts was busy in the Elektor lab with designing, measuring, testing and building of a sufficient number of 'Portable PAs' (as they are called in-house) to support the speakers at the event. Ten units had to be assembled by hand. When soldering the parts of the (mostly SMD populated) boards, our own SMD oven and a few extra hands from interns came in very handy!




To help the speakers to be more intelligible in front of their audience, it was our intention to make the box amplify the higher frequencies a little more to improve the intelligibility and make the speech sound clearer. This objective was achieved. The upper curve shows the frequency response of the circuit without the frequency shifter, so only the microphone preamplifier in combination with the output stage. The frequency response increases with a slope of about 7.5 dB across the entire bandwidth from about 200 Hz to about 5 kHz. In the middle curve the frequency shifter is inserted in the signal path and we can see the frequency response of the boxes (produced in great haste) as they were used at the Live! event.

Also because of the extensive 'practical test' at the Live event we went back into the lab and did some further tests with the frequency shifter in the circuit and with the frequency shifter bypassed using a jumper between K1 and K2 (refer to the schematic of the article on the portable PA elsewhere in this issue). Doing these comparisons we had the impression that the acoustical feedback with and without frequency shifter occurred at much the same volume, although the sound was different. This was quite a strange result of course, since the theory behind the anti-feedback circuit is quite solid. Since the feedback frequency was quite high, we changed the filter components in the microphone and output amplifiers so that we now have a flat frequency response instead of a response that increases slightly with frequency. The frequency response now looks like the curve in the bottom figure. We chose Butterworth characteristics for the filters.

When comparing the modified box with an 'original' one the result appears to be positive. That means, the modified box could be turned up much louder than the original box before acoustical feedback occurred. So the design was a success.

In addition to these filter changes we also experimented some more with the frequency shifter. A shift downwards (the signal was shifted down in frequency compared to the original) resulted in a somewhat poorer performance than a shift upwards. The latter also makes the sound a little clearer, simply because all frequencies are reproduced a little higher.

As a result of these experiments, the characteristics of the filters in the modified box are the same as those in the implementation described in the article that can be found in this issue. We had the impression that the loudspeaker volume in this implementation could be turned up a little higher before acoustical feedback occurred. As a consequence of the adapted frequency response the sound has certainly become a little fuller, but the clarity of the voice is reduced a little, but this is very subjective of course, but worth the effort in our opinion.

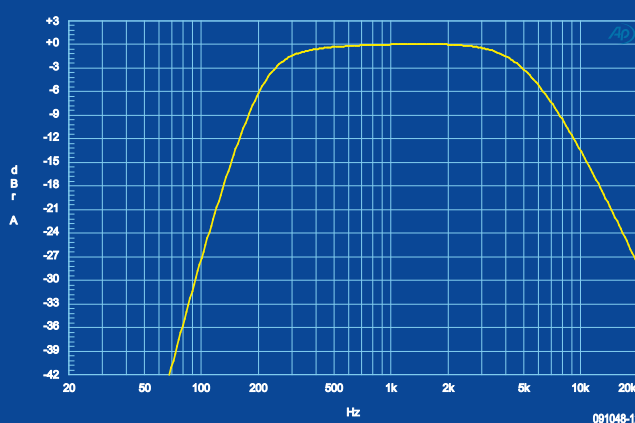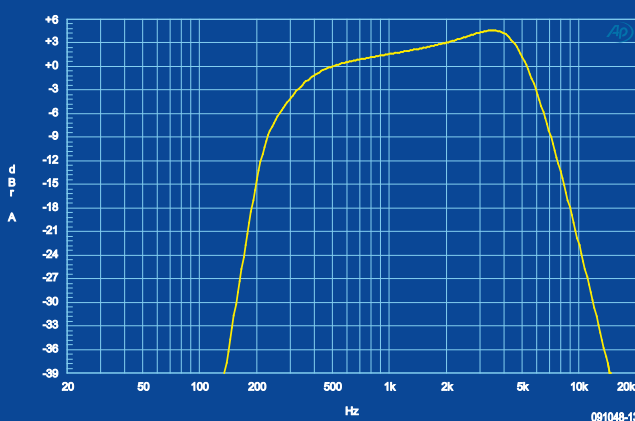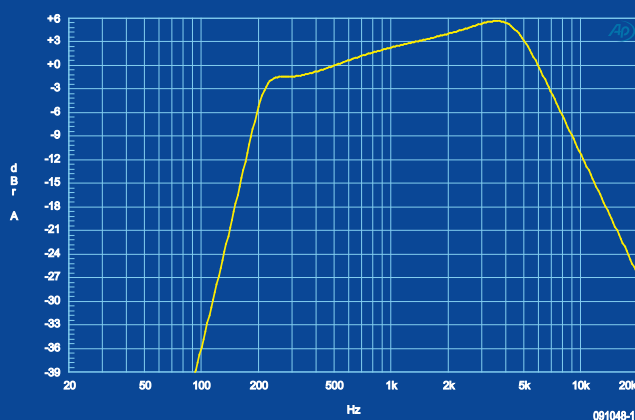

If you would like to experiment for yourself with the characteristics of the filters on the microphone/output amplifier PCB then here are the component values for the increasing frequency response characteristic that we used originally.

R5 = 2.2k	R6 = 6.8k
R7 = 12 k	C2 = 100 n
C5,C6,C7 = 100 n	C12 = 22 n
C13 = 1 n	

(091048)

PCB design – it's not witchcraft!

For many electronics enthusiasts it's no big deal selecting the right transistor for a circuit, calculating an appropriate capacitor value or choosing the right logic ICs to perform a particular function when needs must. After this it's little more effort to knock up the circuit on a breadboard or soldering it up on a scrap of breadboard. Job done!

On the other hand, designing a matching printed circuit board (PCB) is a tougher challenge for many electronics enthusiasts. In some cases a substantial number of components need to be laid out in a logical and functional manner, all the time checking minimum inter-trace clearances, smallest sizes for solder pads and all matter of other issues.

Have no fear though — designing a PCB is certainly not witchcraft. At Elektor Labs we develop several dozen boards a year, both using surface mount devices (SMDs) and also for through-hole (TH) placement. It's true that lab director Antoine Authier's team have a customized version of Altium Designer (a powerful CAD program) at their disposal, which provides elaborate simulation and auto-routing capabilities. Actually, however, these functions are used relatively infrequently, reports Chris Vossen, in charge of many microcontroller and Test & Measurement projects in the lab.

"When we line up components I try to transfer each of the circuit's functional groups onto the PCB as a complete entity," says Chris. The power supply, the microcontroller plus its support circuitry and the analog electronics are types of blocks that are seldom subdivided down to their individual components. Altium enables multiple components of the schematic to be tagged simultaneously (see illustration), so that they can then be placed on the PCB and moved around as a group. That said, Chris can manipulate individual components by hand almost as rapidly.

Another feature of the CAD package is more significant: maintaining a set minimum distance between the traces (traces), between solder pads and finally between pads and traces. In its board-view mode Altium Designer uses color codes to indicate

whether all these requirements have been observed correctly, even when routing is carried out manually. In Altium this is an interactive process, whereas many other CAD programs carry out the design-check with the press of a single key.



With SMD boards, which are sold (partially) populated in the Elektor Shop, the Elektor developer must maintain a minimum separation of 0.15 mm. This is laid down by our PCB producer, Eurocircuits, to meet the European 'Class 6' regulations [1] that Elektor aims to observe. "On boards that users themselves will fit out with components I increase the separation to 0.3 mm, to make their task simpler," adds Chris. To make the soldering task even more user-friendly the Elektor Labs staff also increase the solder pad dimensions for many commonly used components by 2 mm or more.

"On boards that don't have to be ultra-compact I also make the traces a bit wider than usual," continues Chris. For our USB-to-Magic Eye adapter [2] (see photos) the traces are almost entirely 0.7 mm wide. One exception is the traces running between two pins of the microcontroller, which were drawn manually a bit narrower for clearance. Where high currents are involved Chris prefers to use free calculation programs on the Internet, such as the one at [3]. You can set parameters such as the thickness of the copper trace layer (generally 35 µm for Eurocircuits), the current, peak voltage and so on.

It's natural that people who carry out PCB design as part of their daily work build up plenty of experience. Our Elektor designers and editors have compiled the following digest of tips for laying out components, routing and more.



(090873)

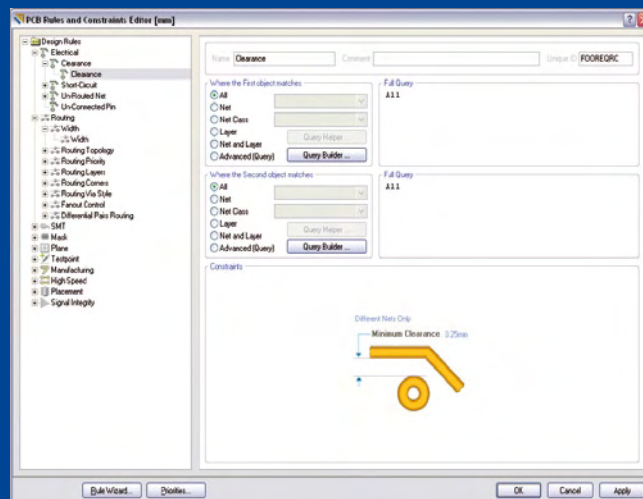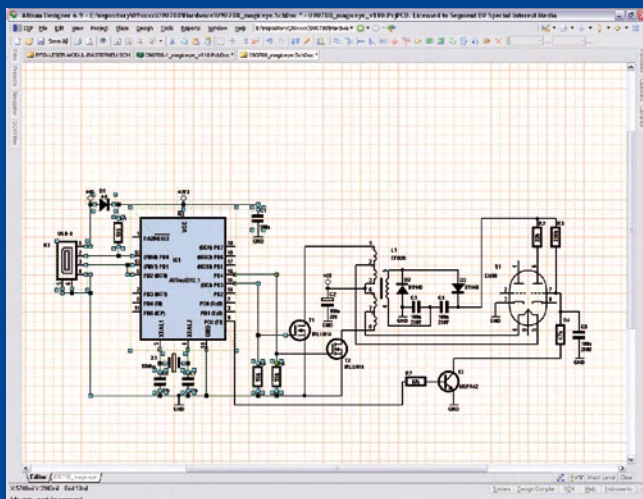- [1] www.eurocircuits.com/images/stories/classification%20january%202009.pdf
- [2] www.elektor.com/090788
- [3] <http://desmith.net/NMDS/Electronics/TraceWidth.html>
- [4] <http://www.elektor.com/magazine/construction-electrical-safety.83362.lynx>



PCB design tips

- When compactness is not a major consideration and the boards will be assembled by hand, through-hole components are the better choice. In this case you can use the pins of these components as 'vias'.
- On the other hand surface-mount components can save a whole load of drilling on self-made PCBs. They make it simpler to achieve objectives such as minimum length for traces, minimal area inside trace loops, etc.
- The orientation of components should consider not only simplicity of assembly but also the need to test the circuitry afterwards. This is the time to remember the need for test points!
- The place for switches, press buttons, plug-in connectors, LEDs and other user-interface components is outside the enclosure. Anything requiring subsequent access should be on the front panel of the case.
- Components that require assembling with the right polarity should all have the same orientation.
- Manual routing is preferable to using the autorouter. The latter has its uses nevertheless for discovering bottlenecks and other critical points.
- When routing never even think about giving up! Many PCBs appear 'unrouteable' at the outset, yet after a while it turns out you have plenty of space to spare.
- If you're not satisfied with your efforts, it's better to go back a step or two rather than just muddle onwards.
- Complete the routing for each of the functional groups of the circuit first. Link the groups together only after you have finished this stage.
- Short traces are better than long ones. High impedance connections are more sensitive to interference and for this reason require to be kept as short as possible.
- Where traces form a loop, their surface area should be kept to an absolute minimum.
- Decoupling capacitors must be located as close as possible to the switching element that needs to be decoupled.
- Traces carrying signals should be routed early on (first the short ones, then the long ones). Except, that is, when the power supply traces are particularly critical.
- Bus lines should be routed alongside one another.
- Separate analog circuitry from digital whenever possible.
- On multilayer boards arrange traces carrying signals so that one of the layers hosts the vertical traces and another one accommodates the horizontal ones.
- If possible reserve one layer or side exclusively for a continuous ground plane. Only in exceptional situations, e.g. with high speed op-amps, is this undesirable.
- Keep traces carrying heavy currents well away from sensitive pickups, sensors and suchlike.
- Beginners should take special care with mains and high voltages! The normal rule for (European) Protection Class I [4] requires a minimum separation of 3 mm between a trace carrying mains voltage and any other trace or the casing. At Protection Class II this distance rises to a minimum of 6 mm (between a trace carrying power line voltage and the case, between multiple mains traces or between AC power traces and low-voltage sections of the circuit). For the other regulations see [4].
- Ground and earth traces require exactly the same consideration as the power supply traces. Electromagnetic interference can be minimized by keeping the power and ground traces parallel (or better still arranged over each other on either side of a double-sided board).
- Bends should be no more than 45°. Sharp angles between the traces and the pads are also to be avoided.
- Observe PCB manufacturers' requirements without exception in order to avoid unpleasant surprises later.
- If you are using software for checking conformity to specifications, carry out these checks regularly at each design phase.
- A border of 0.12" (approx. 3 mm) around the edge of the PCB should be kept entirely clear of components.
- If components are to be inserted by machine you must provide at least three location marks.
- Don't forget the holes for fixing screws or pillars!
- Don't skimp on text markings on the PCB: indicate polarity, voltages, on-board functions, part designation, design date, version number...
- Check not just twice but three times that all components will actually fit the PCB!
- Leave time at the end of the process for tidying up and optimizing.

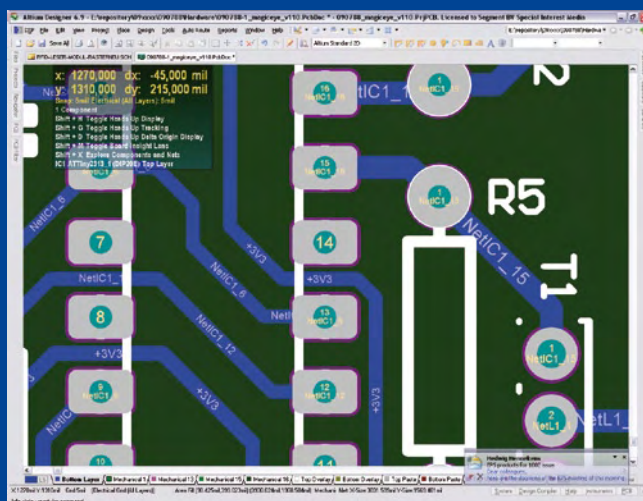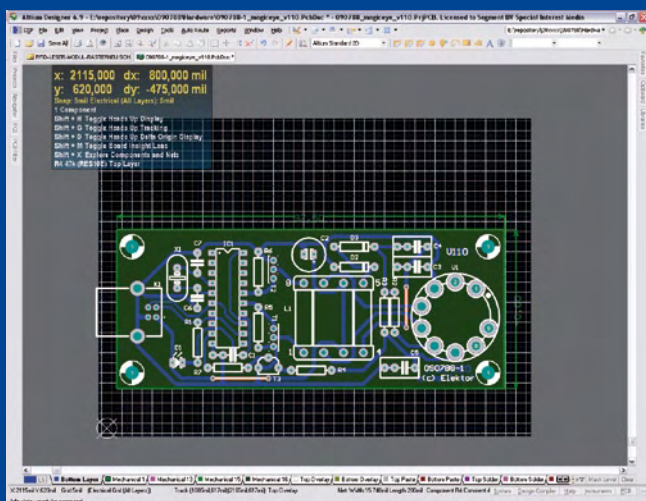

Capacitors to the rescue


Jens Nickel (Elektor Germany Editorial)

The team here in the Elektor lab are a good mix of young engineers and some more experienced 'veterans'. Ton Giesberts has been with Elektor now for over 20 years so I guess he would count himself as one of our 'vets'. Audio design is Ton's area of expertise. He has been responsible for many excellent projects and given valuable input to almost every article that concerned itself with high quality audio appearing in this publication over the last 20 years. With his experience it's no surprise that he sometimes gets a Déjà-vu moment when a new design lands on his desk. The portable 'PA amp' featured in this month's magazine [1] is a case in point. It uses the MAX9768 class D amplifier from MAXIM which according to the application note requires four capacitors for supply decoupling. Both a 33 μF and a 1 μF capacitor are connected in parallel to the two voltage supply

capacitors C18 and C19 I just used standard 10,000 μF radial electrolytics' he explained 'however during the first soak test on this design I found a major problem, after power up the thing began running so hot I could actually feel the heat from some distance away'.


A loud crack ensued and superheated capacitor internals flew around the lab. After a rethink 8,800 μF 'Sikurel' type electrolytics from Siemens, were substituted in the design and were specified in the parts list.

Capacitors came to the rescue of another large project that Ton had been working on for over a year but this time they were a much smaller variety. The beast in question was the Titan 2000 power amplifier. This fully symmetric high power mono audio amplifier is capable of delivering up to 2000 W in a bridge configuration. It was one of the most complex designs ever featured in Elektor [3] with no less than 52 transistors some of which were

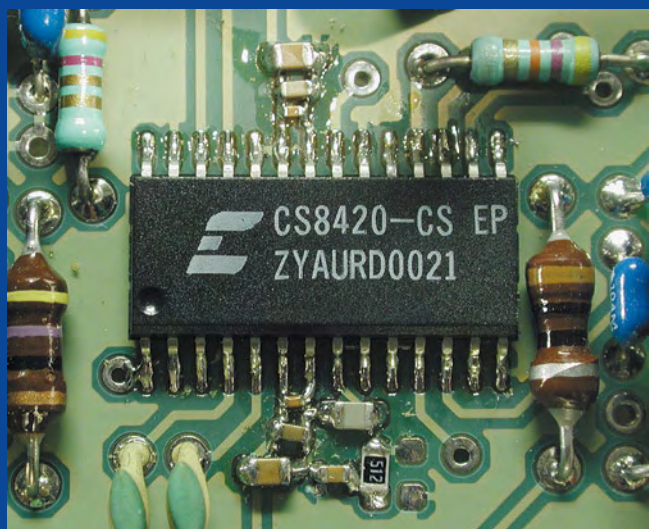

pins to ensure suppression of the widest range of frequencies. 'The chances are that internally this chip has two output stages' Ton suggested was the reason for the two supply pins. It reminded him of the 96 kHz sampling rate converter which he authored in the April 2001 edition of Elektor [2]. This used three capacitors in parallel for supply rail decoupling; one 1 μF , one 100 nF and one 1 nF. If you look closely at photos of the prototype in the article you can see three different sized SMD capacitors mounted next to each other at either side of the CS8420 chip. 'When a manufacturer indicates this kind of detail in a data sheet or application note it is wise to follow their recommendation' advised Ton. 'And another thing, when a low ESR or high ripple current type of electrolytic is specified in the parts list there's usually a good reason for it!'

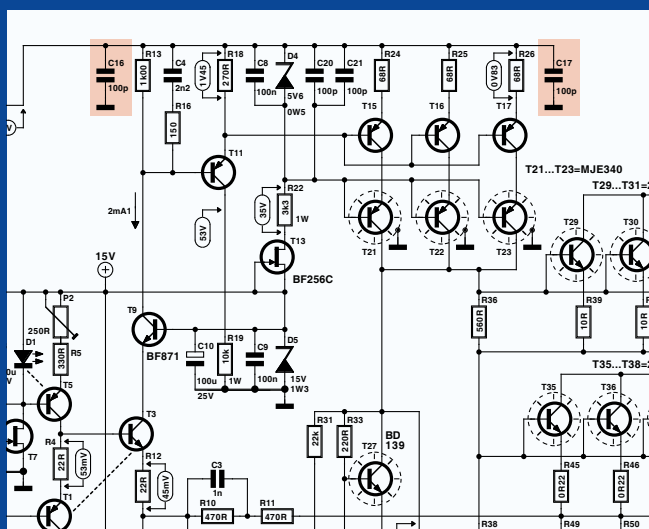It's not only important to check the voltage rating of an electrolytic but also its ripple current rating. Ton had first hand experience of this as a young engineer. One of his earlier designs was a 650 W DC inverter for an in-car audio amp or 'car booster' which featured in the October/November editions in 1994. 'For



sourced from the supplier at that time (Avera) in Japan. With all the theoretical work behind him and the first 25 x 10 cm prototype board fully stuffed with components, switch-on came as something of a shock; 'With no input signal the output would just hang, sometimes at +70 V sometimes at -70 V' It didn't take him long to find that the amplifier was oscillating but at such a high frequency the voltage amplifier couldn't keep up. To track down the source of instability Ton armed himself with a handful of 100 pF capacitors and a scope. First for some HF decoupling of the supply rails, with just one capacitor on each rail there was little improvement but after placing four at points along the length of each rail (in such cases 'cut and try' is often the only way to go to find the most effective positions) peace broke out, the oscillations ceased and the amp became stable. (090876)

[1] www.elektor.com/090675

[2] www.elektor.com/010014

[3] www.elektor.com/990001

Build Your Own:

SYNTHESIZER

FREE KIT!
www.paia.com/elektor



FatMan
 Analog MIDI Synth

PAIA paia.com Music/Tutorials/Kits
 Analog Synthesizers
 Guitar Effects
 Tube Electronics
 Studio Gear

Makers since 1959

Pololu

Robotics & Electronics

Robot Kits

Line followers
 Mini-sumos
 Robot arms

Save 10%
 With coupon code
ELEKTOR3PI9

3pi Robot

Item #975: **\$99.95**

High-performance, C-programmable, ATmega328P-based robot (with Arduino support).

Mechanical Components

Motors, servos, wheels, ball casters, chassis, & more!



Controllers and Sensors


Jrk USB motor controller with Feedback
\$49.95

Baby Orangutan robot controller
\$24.95

QTR reflectance sensors
\$3.49

Solder Paste Stencils & Laser Cutting

Both starting at \$25!

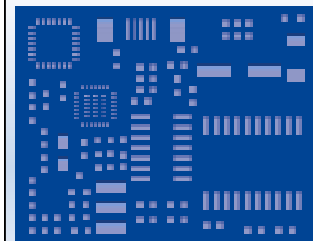

Use our low-cost plastic solder paste stencils to quickly assemble your surface-mount designs.



Laser-cut your own custom chassis, front panels, and more!

1-877-7-POLOLU
www.pololu.com

3095 E. Patrick Ln. #12, Las Vegas, NV, 89120

USB Add USB to your next project.
 It's easier than you might think!

DLP-USB1232H: USB 2.0 UART/FIFO

HIGH-SPEED
480Mb/s

- Multipurpose: 7 interfaces
- Royalty-free, robust USB drivers
- No in-depth knowledge of USB required
- Standard 18-pin DIP interface; 0.6x1.26-inch footprint



DLP-IO8-G

8-Channel Data Acquisition



Only
\$29.95!

- 8 I/Os: Digital I/O
 Analog In
 Temperature
- USB Port Powered
- Single-Byte Commands

DLP-IOR4

4-Channel Relay Cable

DLP-TH1b

Temp/Humidity Cable

DLP-RFID1

HF RFID Reader/Writer

DLP-FPGA

USB-to-Xilinx FPGA Module



www.dlpdesign.com

Loud and Clear

A portable sound system with feedback suppression

By Ton Giesberts (Elektor Labs) and Thijs Beckers (Elektor Netherlands Editorial)



Sometimes it's helpful to raise your voice just a bit. Regardless of whether the occasion is a guided tour or a presentation in a noisy room, that little bit of extra volume may be enough to ensure that everyone can understand you. However, you have to watch out for feedback with this sort of personal PA system.

For the Elektor Live! 2009 event ^[1], we wanted to make things a bit easier for the speakers in the rings of the Philips Evoluon building ^[2] by designing a portable public address system that is small and light enough to be carried on the user's belt. The problem with such a design is that due to the relatively small distance between the loudspeaker and the microphone, there's a fairly good chance of feedback howl. This occurs when the headset microphone picks up the sound from the loudspeaker, amplifies it, and emits it again via the loudspeaker, which produces an irritating howling tone. For this reason, we incorporated a

previously published anti-feedback mechanism in our design: a frequency shifter.

Frequency shifting

The most important consideration in this application is avoiding feedback. The loudspeaker is carried at waist height and is thus relatively close to the microphone. With a static configuration, an adjustable narrow-band blocking filter (a notch filter) is a good option. However, in our application the microphone and the loudspeaker move relative to each other when the speaker's head moves. This means that the filter tuning would need to be adjusted continuously.

Nowadays it's possible to implement this sort of thing with a digital signal processor (DSP), but we considered this option a bit over the top for a DIY project.

Manual adjustment of the notch filter is impractical, so we had to take a different approach to suppressing feedback. We published an article on a 'feedback killer' in the February 1990 issue of Elektor Electronics (as the magazine was called then). This circuit appeared to be a good choice for our purpose. It raises or lowers the frequency of the input signal by a few hertz so the output signal differs slightly from the input signal. This prevents the repeated amplification of

Features

- Maximum output power 10W/8 Ω (with 14 V supply)
- Feedback suppression by frequency shifting
- Suitable for electret and dynamic microphones
- Low current consumption
- Can also be used without the frequency shifter as a portable active speaker

a particular frequency (the feedback frequency). Of course, we modified the original circuit somewhat for our application. This feedback killer works as follows: all-pass filters are used to split the input signal into a pair of signals with a 90° phase difference. These two signals are mixed with two clock signals (carrier wave), which also have a phase difference of 90 degrees. The resulting signals are then summed. This produces a signal corresponding to the sum of the input signal and the carrier signal.

There are a few difficulties with this approach. For proper operation, the signals must have a phase difference of exactly 90°, but the all-pass filters cannot achieve this fully. In addition, a sinusoidal signal should actually be used as the carrier signal instead of a square-wave signal. However, the circuitry necessary for signal mixing is much simpler with a square-wave signal. As a square-wave signal can be regarded as the sum of sinusoidal signals, this can be corrected reasonably well by using a low-pass filter to eliminate everything except the desired mixer product.

In order to obtain the desired frequency shift of the input signal, the sum signal is mixed with a signal at almost the same frequency as the carrier signal. This produces all sorts of sidebands in the frequency spectrum, but we want to keep only one of them. Accordingly, we filter the other ones out. The frequency difference between the two carrier signals determines the ultimate frequency shift of the input signal. For a mathematically formulated version of this arrangement, see the original article published in 1990.

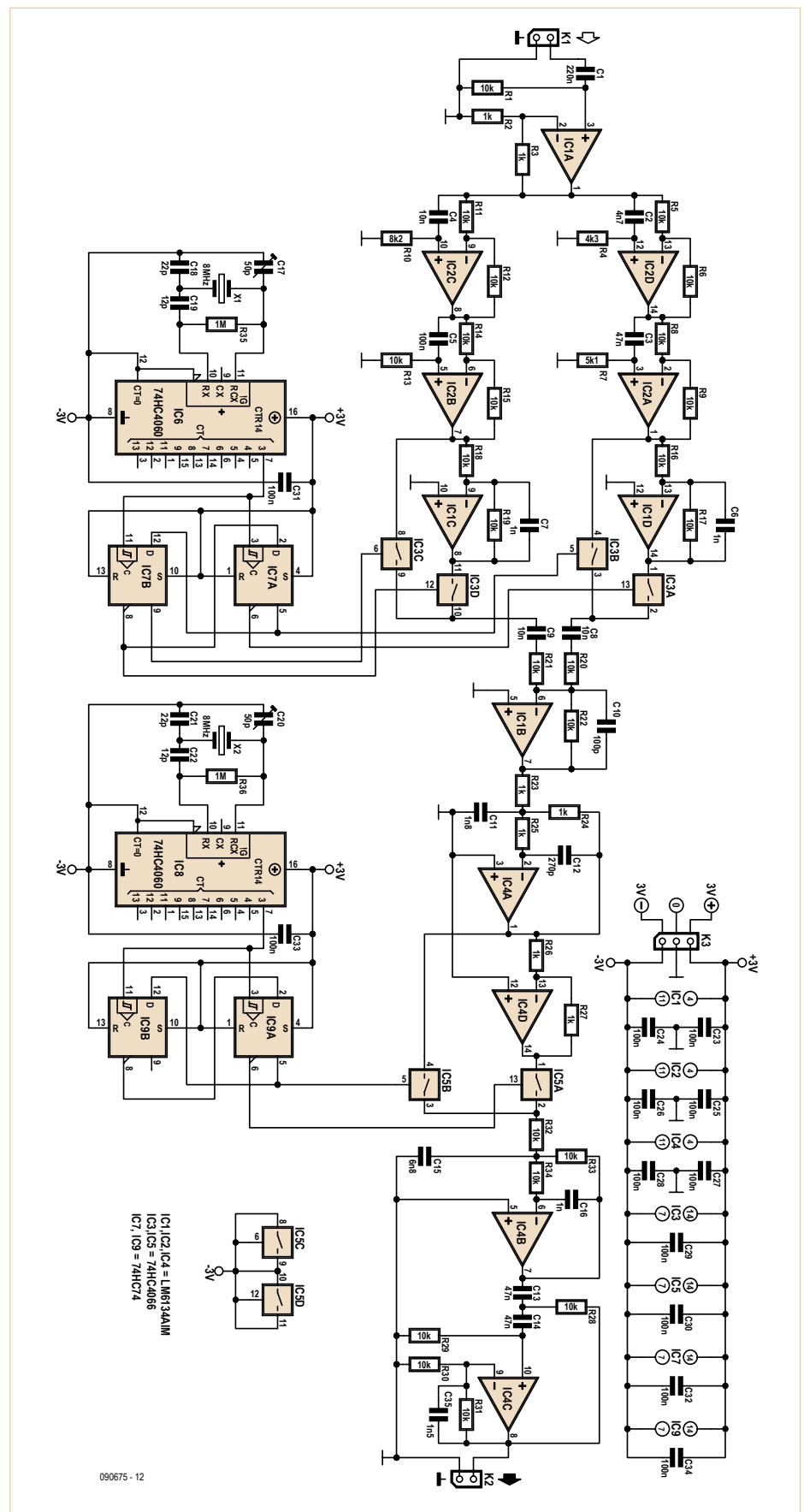


Figure 1. As you can see from the schematic diagram, the frequency shifter employs quite a few opamps.

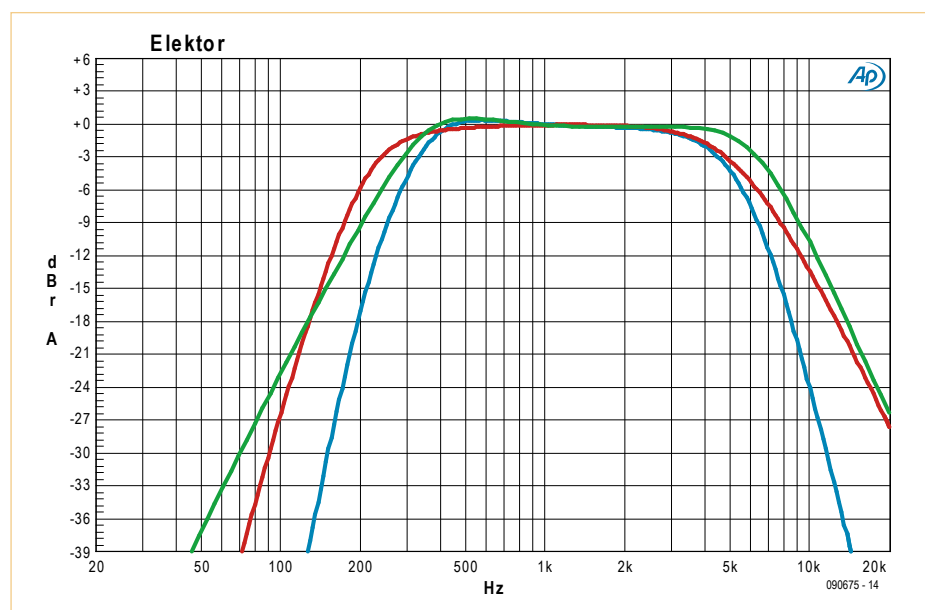


Figure 2. The frequency response curves of the frequency shifter (green), the microphone amplifier with output amplifier and filter (red) and the overall circuit (blue).

Upgraded implementation

The present circuit is battery powered, so we took several measures to reduce the current consumption, including using half as many all-pass filters. This eliminated one quad opamp. For the opamps, we selected rail-to-rail devices from National Semiconductor that combine low current consumption (360 μ A) with high bandwidth. This alone yielded a savings of 18 mA.

In addition, the supply voltage from four alkaline cells (6 V) is considerably lower than the supply voltage of the original design (around 8 V), and we used the faster HC family of logic devices. The net result is that the current consumption of the entire circuit (under quiescent conditions) is now only 15 mA instead of 45 mA as in the original design. The choice of HC logic devices prevents the use of a higher supply voltage, although the opamps can handle a higher voltage (24 V).

We also changed the component values in a few places. The input amplification is reduced by a factor of 2 because the supply voltage is a good deal lower (see **Figure 1**). The low-pass filters are built around IC2a–IC2d. The pass band of the phase shifter is approximately 300 Hz to 4 kHz ($\pm 2^\circ$ deviation), which is good enough for speech.

We selected Texas Instruments devices for the analog switches on account of their very low resistance. This allows the resistances of the summing opamp (IC1b) to be reduced

by a factor of 10, which yields less noise and better signal processing. Capacitor C10 limits the bandwidth of the mixer input signal in order to reduce the harmonics in the mixer output signal. The opamp is followed by a low-pass filter that further suppresses undesired harmonics.

In order to keep the noise level low, the resistance values of the subsequent inverter are also an order of magnitude smaller than in the original 1990 circuit. The mixer is followed by a low-pass filter and then a high-pass filter. This arrangement prevents the high-pass filter from letting through undesirable harmonics from the second mixer. The corner frequency of the low-pass filter is slightly more than 7 kHz. The corner frequency of the high-pass filter is approximately 270 Hz (see **Figure 2**). Capacitor C35 reduces the gain to 1 at high frequencies. As a result, the frequency response curve drops by 1.7 dB from 460 Hz to 4 kHz. The filter has been redesigned to have a characteristic resembling a 1-dB Chebyshev filter, which makes its cut-off a bit sharper. As a result, the gain is somewhat higher at low frequencies, but this is more than offset by the characteristics of the filters of the microphone and output amplifiers. The coupling capacitor at the input (C1) has virtually no effect on the amplitude curve (it flattens the curve by 0.1 dB).

The maximum frequency shift can be set using C17 and/or C20 and is approximately 30 Hz. The amplitude modulation (a ripple

signal at the shift frequency) is 7.5%. This is due in part to the simplification of the all-pass filters and in particular the component tolerances, which have a detrimental effect on the operation of the circuit. The end-to-end gain is approximately 2.7 with small signals. It is somewhat less with larger signals (2.55 at 100 mV).

The lowest distortion level (0.23% as measured with our prototype) occurs at an input signal level of 10 mV. The distortion increases with increasing input signal level to 1% at 30 mV and 3.2% at 100 mV, as measured with a frequency shift of +13 Hz.

Microphone amplifier and output amplifier

For obvious reasons, the enclosure that holds the circuitry, loudspeaker and batteries should not be overly large. Consequently, both PCBs are designed to use SMD components. This leaves a reasonable amount of space for the loudspeaker, which uses the enclosure as a speaker box. The amplifier board comprises a microphone amplifier, a high-pass filter and a class D amplifier with a low-pass filter (see **Figure 3**). The latter filter is combined with the driver stage of the output amplifier.

In order to provide the usual supply voltage to an electret microphone, we used a standard phantom supply circuit with a 2.2-k Ω resistor connected to the supply rail (for a total resistance of 2.42 k Ω including the decoupling resistor). The resulting open-circuit voltage is 3 V. If you use a dynamic microphone, you can omit R2 (2.2 k Ω).

Balanced supply voltages for the microphone amplifier are obtained by tapping off the ground level from the middle of the battery chain. The microphone supply voltage is adequately decoupled by R1 and C1. The DC offset voltage of the microphone is decoupled by C2.

We chose an ST dual rail-to-rail opamp for the subsequent amplifier stage: the TS922ID, which we have used previously in other projects. The amplifier stage is designed to have adjustable gain in order to compensate for large differences in the sensitivity of various types of microphones. The gain can be adjusted over a range of 1 to 21 with P1. This arrangement also allows the

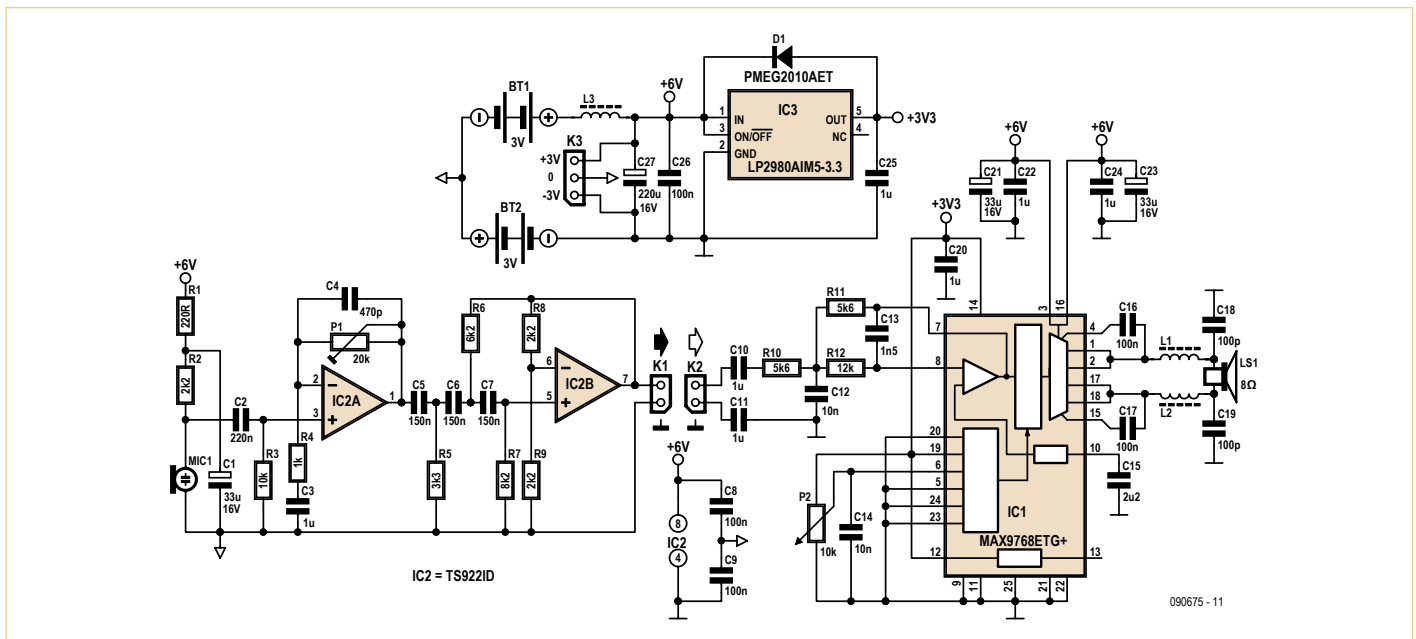


Figure 3. The microphone and output amplifier board is laid out so that it can be used without the feedback shifter board. Only one jumper between K1 and K2 is necessary for this.

circuit to be used as an active loudspeaker for an MP3 player or similar device (with R2 omitted as necessary). At maximum gain, the bandwidth is reduced somewhat by C3 and C4.

In light of the fact that the enclosure is worn on the user's body and makes use of a headset with a microphone, a third-order high-pass filter with a gain of 2 is placed after the input stage. This provides adequate suppression of low-frequency rumble and eliminates the problem of reproducing low frequencies with a small loudspeaker. The filter is a Butterworth type with a corner frequency of approximately 240 Hz.

The output of the preamplifier stage is feed to connector K1 for connection to the frequency shifter. The input of the output amplifier (K2) is located right next to K1. This way the output amplifier can be connected directly to the microphone amplifier by a simple jumper.

The ground level of the input stage is half the supply voltage, while the ground level of the output amplifier is the negative battery voltage. A capacitor (C11) is connected in series with the ground terminal of the output amplifier input to decouple this voltage difference.

With the voltage available from four pen-light cells, an output power of 2 W into 8 Ω is possible with a bridge amplifier. For the output amplifier, we looked for an IC that can also handle more than 5 V. We

chose a very nice (extremely small) IC from Maxim, the MAX9768ETG+, which comes in a 4 $\times$ 4 mm 24-lead TQFN-EP package. The power stage has an operating supply voltage range of 4.5 V to 14 V. Despite its small dimensions, this IC can deliver 10 W to an 8- Ω loudspeaker with a 14-V supply voltage. At 6 V the figure is 2 W into 8 Ω , or nearly twice as much into 4 Ω . The power dissipated in the IC is transferred to a copper plane on the PCB by an exposed pad on the bottom of the package.

Power supply

The amplifier IC has a separate driver stage that operates at a lower supply voltage (2.7 V to 3.6 V). The driver stage can be configured to provide extra gain. It needs a separate 3.3-V voltage regulator. To allow this board to be connected to a higher supply voltage if so desired, the voltage regulator must be able to handle the higher voltage. One of the few devices that meets this requirement is the National Semiconductor LP2980AIM5-3.3. This IC, which comes in an SOT23-5 package, can handle up to 16 V. Note however that the maximum rated voltage of the TS922 is 12 V, which makes this the maximum operating voltage of the microphone and output amplifier board without further adaptations. Schottky diode D1 protects the voltage regulator if the input voltage is less than the output voltage, which may for example occur if the batteries are shorted.

The voltage regulator has an extremely low dropout voltage of only 60 mV at 10 mA. This means that the entire circuit will still operate even when the batteries are close to empty. If the voltage drops below 4 V, the undervoltage lockout will disable the IC. With regard to the features of the IC, such as the patented spread-spectrum modulation, see the data sheet. There are far too many features to describe here, even in summary form.

Here we took advantage of the possibility of using a potentiometer (P2) to control the volume. We selected spread-spectrum modulation with filterless mode. We were guided primarily by the typical application circuit in the data sheet, and we used the evaluation kit as reference for the layout. The passive output filter that is usually necessary can be omitted in this application because the speaker leads are shorter than 20 cm. However, we did fit ferrite chokes (L1 and L2) in the speaker output lines. Capacitors C18 and C19 enhance the HF filtering. The selected SMD chokes (0805 package) have a DC resistance of only 50 m Ω and can handle 2 A. This corresponds to the maximum current of the MAX9768 (soft output current limit).

The supply voltage for the power stage of the IC is fed via two pins. Each pin is well decoupled with its own electrolytic capacitor (C1 & C2). Here we used a somewhat pricey type from Nichicon with a low ESR

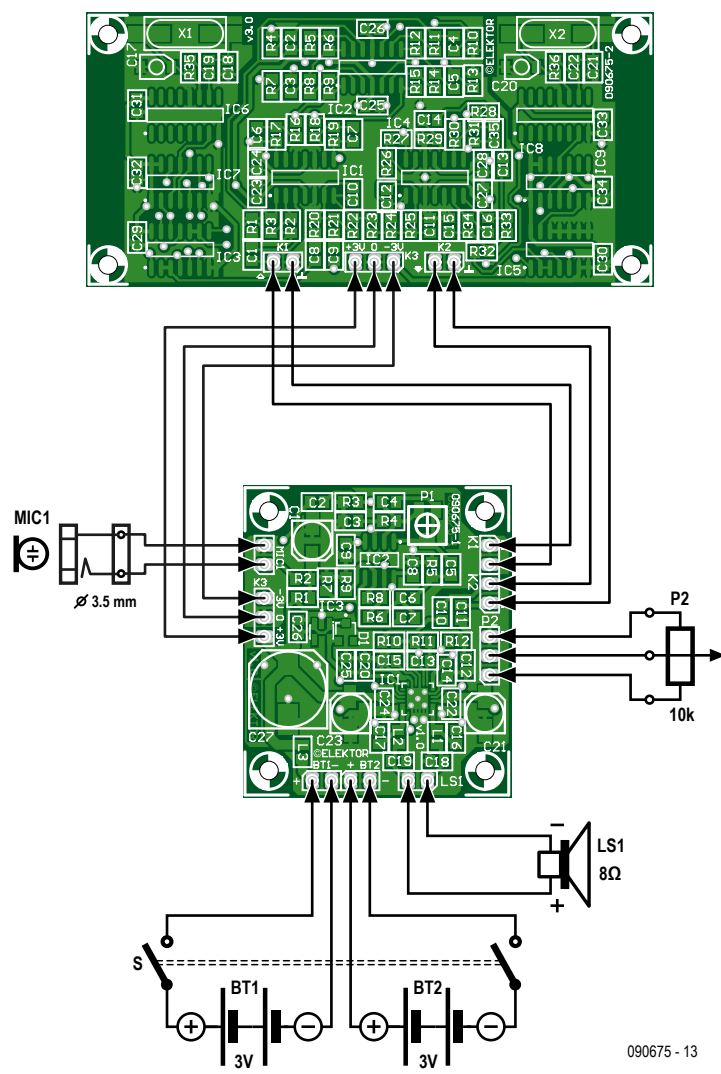


Figure 4. Follow this wiring diagram to connect everything together.

that can handle 1.9 A. The supply voltage connection on the PCB is additionally decoupled by a relatively large electrolytic capacitor with a low ESR that can handle a hefty 3.4 A. It is important to use high-quality electrolytic capacitors in order to obtain a reasonably long service life from the circuit. The circuit operates with a fairly high switching frequency ($300 \text{ kHz} \pm 7.5 \text{ kHz}$), and normal electrolytic capacitors are not suitable for this. The battery connection is additionally decoupled by a small choke (L3).

The volume control input is decoupled by C14. A connector is used for the potentiometer leads so the potentiometer can be fitted independent of the position of the board. The volume can be adjusted in 64 steps. The volume range is approximately

100 dB, which is easily more than enough. The internal gain of the IC is 9.5 dB maximum from the volume control stage (see also Table 6 in the data sheet) plus 20 dB from the output stage. The maximum total gain is thus around 30 dB.

Additional gain can be configured with the driver stage. This is done using two resistors, just like a standard inverting amplifier built around an opamp. We took advantage of this option to incorporate a second-order low-pass filter without having to use another IC. The inverting input can be used to construct a second-order multi-feedback filter. This is implemented as a second-order Butterworth filter to provide a gain characteristic that is as flat as possible over the desired bandwidth. The corner frequency is 5 kHz.

The gain of this filter is -1. Feedback via the supply voltage may occur at higher gain.

Final assembly

The enclosure we used for our prototype has dimensions of $32 \times 100 \times 162 \text{ mm}$. With the loudspeaker, the battery holders and the two PCBs installed in the enclosure, there's not much space left over. We fitted a 3.5-mm stereo headphone socket, potentiometer P2, and a dual-pole switch on one side. The loudspeaker we used is too deep to mount on the inside of the enclosure as actually intended, so we mounted it on the outside of the enclosure.

The layouts of the two PCBs for this project can be downloaded free from the associated web page [3].

The PCB for the microphone and output amplifiers is fitted on the side, which is also where the connectors are located (switch, MIC1 and P2). If everything is laid out properly, the rear of the loudspeaker just clears the frequency shifter board. We made a flat hook bracket from a piece of aluminium ($20 \times 50 \text{ mm}$) for attaching the enclosure to a belt or trouser pocket. It is fitted to the back of the enclosure (level with the loudspeaker).

All connectors are implemented as pin headers, so you can use sockets for testing. After the boards are fitted in the enclosure, you can also solder thin stranded wire directly to the header pins. Twist the wires to be joined together (with two wires) or braid them together (with three wires) to reduce the likelihood of problems. Use somewhat thicker wire for the loudspeaker. The wiring diagram in **Figure 4** clearly shows how to connect everything together.

Of course, you can also use a different enclosure and select a different loudspeaker. Pay attention to the efficiency of the loudspeaker. According to the manufacturer's specifications, the efficiency of the type we used is 88 dB/W, but many loudspeakers with these dimensions have much lower efficiency. If a low-efficiency type is used, the output amplifier will not be able to supply enough power. In other words, you will need a higher supply voltage, which means more batteries. Note that the frequency

COMPONENT LIST Frequency Shifter

Resistors (SMD 0805)

R1,R5,R6,R8,R9,R11-R22,R28-R34 = 10k Ω 1% 0.125W
 R2,R3,R23-R27 = 1k Ω 1% 0.125W
 R10 = 8.2k Ω 1% 0.125W
 R4 = 4.3k Ω 1% 0.250W
 R7 = 5.1k Ω 1% 0.250W
 R35,R36 = 1M Ω 1% 0.125W

Capacitors (SMD 0805, except C17,C20)

C1 = 220nF 10% 25V, X7R
 C2 = 4.7nF 10% 50V, X7R
 C3,C13,C14 = 47nF 10% 50V, X7R
 C4,C8,C9 = 10nF 10% 50V, X7R
 C5,C23-C34 = 100nF 10% 50V, X7R
 C6,C7,C16 = 1nF 10% 50V, X7R
 C11 = 1.8nF 10% 50V, NP0
 C12 = 270pF 5% 50V, NP0
 C15 = 6.8nF 10% 50V, X7R

C10 = 100pF 5% 50V, NP0
 C17,C20 = 50pF 25V, SMD trimmer, AVX type
 CTZ3E-50C-W1-PF
 C18,C21 = 22pF 5% 50V, NP0
 C19,C22 = 12pF 5% 50V, NP0
 C35 = 1.5nF 10% 50V, X7R


Semiconductors

IC1,IC2,IC4 = LM6134AIM SMD (SO-14)
 IC3,IC5 = 74HC4066 SMD (SO-14)
 IC6,IC8 = 74HC4060 SMD (SO-16)
 IC7,IC9 = 74HC74 SMD (SO-14)

Miscellaneous

X1,X2 = 8MHz quartz crystal, SMD, AVX type

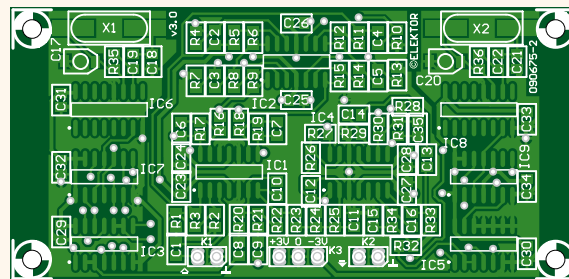CX49GFWB08000H0PESZZ
 K1,K2 = 2-pin pinheader, right angled
 K3 = 3-pin pinheader, right angled
 PCB # 090675-2 see www.elektor.com/090675



shifter is connected directly to the battery voltage, and its maximum supply voltage is 6 V. If the supply voltage is higher than this, a few more voltage regulators will be necessary.

Practical results

From practical experience, it appears that the most important factor in avoiding feedback howl is to use a good headset with a directional microphone located as close as possible to the user's mouth. The best way to avoid feedback howl is to ensure that the microphone cannot pick up the sound from the loudspeakers.

For best results, the frequency shifter should be configured for a positive frequency shift. With a bit of experimenting, you can readily find the best shift value by ear. For those of you with access to an accurate frequency meter, measure the difference between the frequencies at the outputs of D-type flip-flops IC7 and IC9. We found 13 Hz to be a good compromise between a 'robot voice' effect and feedback suppression. The tendency to feedback howl is further damped by the slight decrease in gain at higher frequencies. Although a negative shift can also be used, feedback is more likely to occur in this situation. A repetitive sliding tone

occurs if the volume is set to high, since the frequency shifter prevents the generation of a continuous tone.

If you use the circuit as an active speaker, for example with an MP3 player, the frequency shifter can be omitted. This will reduce the current consumption by nearly half.

(090675)

Internet Links

- [1] www.elektor.nl/elektorlive2009 (in Dutch)
- [2] www.dse.nl/~evoluon/historie-e.htm
- [3] www.elektor.com/090675

COMPONENT LIST Microphone & Output Amplifier

Resistors (SMD 0805 except P1,P2)

R1 = 220 Ω 1% 0.125W
 R2,R8,R9 = 2.2k Ω 1% 0.125W
 R3 = 10k Ω 1% 0.125W
 R4 = 1k Ω 1% 0.125W
 R5 = 3.3k Ω 1% 0.125W
 R6 = 6.2k Ω 1% 0.125W
 R7 = 8.2k Ω 1% 0.125W
 R10,R11 = 5.6k Ω 1% 0.125W
 R12 = 12k Ω 1% 0.125W
 P1 = 20k Ω 20% 0.250W, SMD, Vishay Sfernice type TS53YJ203MR10
 P2 = 10k Ω 20% 0.250W, SMD, Bourns type 3310Y-001-103L

Capacitors (SMD 0805, except C1,C21,C23,C27)

C1,C21,C23 = 33 μ F 20% 16V, SMD chip type 5x6mm
 C2 = 220nF 10% 50V, X7R
 C3,C10,C11,C20,C22,C24,C25 = 1 μ F 10% 16V, X7R
 C4 = 470pF 5% 50V, NP0
 C5,C6,C7 = 150nF 10% 50V
 C8,C9,C16,C17,C26 = 100nF 50V 10%, X7R

C12,C14 = 10nF 10% 50V, X7R
 C13 = 1.5nF 10% 50V, X7R
 C15 = 2.2 μ F 10% 50V, X7R
 C18,C19 = 100pF 5% 50V, NP0
 C27 = 220 μ F 16V 20%, SMD chip type 10x10mm

Inductors (SMD 0805)

L1,L2 = Murata type BLM21PG221SN1D (220 Ω at 100MHz, 50mA, 2A)
 L3 = Murata type BLM21PG600SN1D (60 Ω at 100MHz, 25mA, 3A)


Semiconductors

D1 = PMEG2010AET (SOT-23) (1A 20V SMD Schottky diode)
 IC1 = MAX9768ETG+ (TQFN-EP)
 IC2 = TS922ID (SO-8)
 IC3 = LP2980AIM5-3.3 (MA05B)

Miscellaneous



K1,K2,MIC1 = 2-pin pinheader, angled
 K3,P2 = 3-pin pinheader, angled
 LS1,BT1,BT2 = 2-pin pinheader, straight

2 battery holders for 2 AA cells
 Loudspeaker, 2W 8 Ω , e.g. Eurotec International type 59-F67.00-01FR
 Enclosure, dim. 165 x 100 x 32 mm, e.g. MULTICOMP type MCRH3165 (Farnell # 1520395)
 Switch, double pole double throw, 2A
 3.5mm stereo jack socket for panel mounting
 PCB # 090675-1, see www.elektor.com/090675

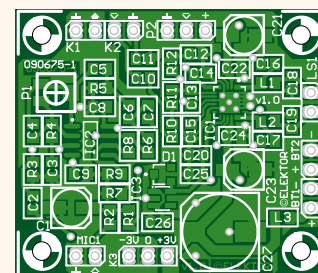

The 2.4 GHz Bandalyzer

See what's happening on the band

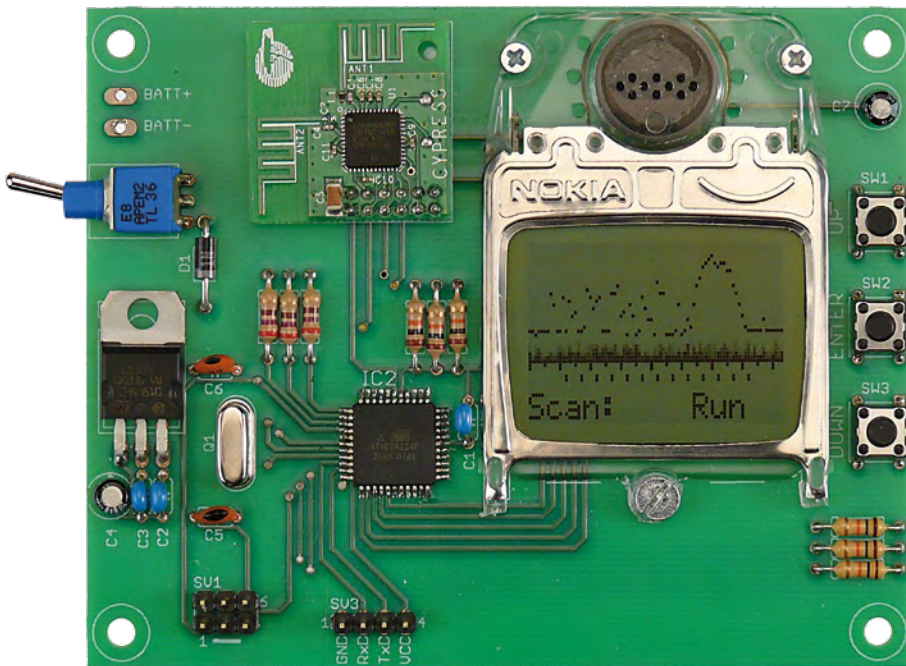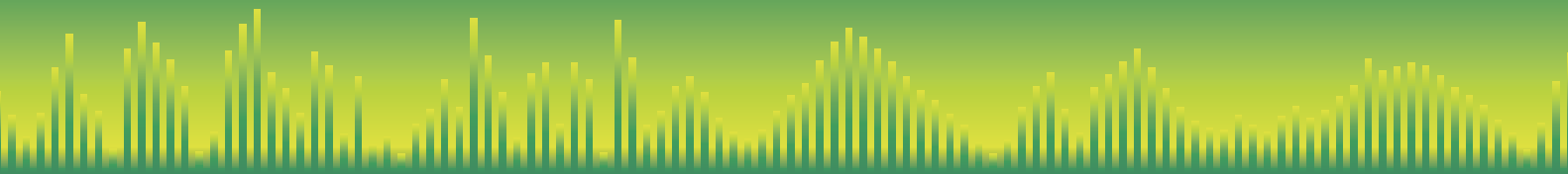

By Marcel Romijn (The Netherlands)

The 2.4-GHz band is frequently used nowadays for wireless links between all sorts of devices. This often leads to problems with wireless local area network (WAN) links when different networks close by operate on the same channel. With this handy portable scanner, you can quickly and easily see which frequencies are being used in your area and which channels you should avoid for your own wireless network links.

The world around us is full of electromagnetic signals. Some parts of the electromagnetic spectrum can be used without a licence. One section of the RF spectrum that has become very popular in recent years is the 2.4-GHz band, which is one of the Industrial, Scientific and Medical (ISM) bands ^[1]. Many applications make use of this band. To mention just a few: WiFi LANs, Bluetooth, wireless computer peripherals, transmitters for remotely controlled model cars and planes, wireless music players and loudspeakers, and so on. Interference sources such as microwave ovens also operate in or near the ISM frequency allocation.

With the increasing use of this band, the likelihood of unwanted interactions between these applications, or even interference, also increases. If you have a prob-

lem with interference, how can you track down the cause? One solution is to use a scanner that shows you which signals are being transmitted in the 2.4-GHz band, such as the 2.4-GHz spectrum analyzer published a few years ago in *Elektor* ^[2].

The 2.4-GHz scanner described here is based on that design, but it has a major advantage compared with the original design: it is implemented as a portable instrument with its own display, so you don't need a separate PC. A built-in microcontroller scans the 2.4-GHz band and shows the results on a graphic LCD screen. The scanner employs the same front-end module as the original design — a Cypress Semiconductors CYWUSB6935 — but the module is driven directly by the microcontroller via the SPI interface, which considerably boosts the scanning rate.

How it works

The scanner works exactly the same way as the previously published 2.4-GHz spectrum analyzer.

Only the received signal strength indication (RSSI) portion of the CYWUSB6935 module is used here (see the block diagram in **Figure 1**). The microcontroller first tunes the frequency synthesizer to one of the channels in the 2.4-GHz band and waits until the front-end module indicates the signal strength in the selected channel. Then it switches to the next channel and repeats the measurement process. As soon as all the channels in the band have been scanned this way, the measured data is used to plot a scan on the LCD screen. To avoid missing fast-changing signals, each channel can be scanned several times in succession.

Features

- Scans all 84 channels of the 2.4-GHz band approximately 20 times per second
- Displays the maximum value measured in each channel
- Each frequency channel can optionally be measured several times in succession
- The entire 2.4-GHz band can optionally be scanned several times in succession
- 3.3 V operating voltage, stabilized by a low-drop voltage regulator
- Serial port for future expansion
- Built-in transceiver module allows the unit to be used for other (wireless) applications

The circuit

The circuit (see **Figure 2**) is quite straightforward and consists of several main components: a microcontroller (IC2) that handles the control tasks, the CYWUSB6935 module (MOD1) for scanning the 2.4-GHz band, a Nokia 3310 LCD module for output (NOKIA3310), and three pushbuttons (S1 to S4) for input. As the CYWUSB6935 module and the LCD module both have an operating voltage of 3.3 V, we decided to operate the microcontroller at this voltage as well. A low-drop voltage regulator provides a clean 3.3 V supply voltage, even when the circuit is powered from four AA or AAA cells (dry cells or rechargeables).

As already mentioned, the CYWUSB6935 module and the LCD module are driven by the microcontroller via the SPI bus. Connector K1 is also connected to the SPI bus to allow the microcontroller to be programmed or reprogrammed.

The serial port of the microcontroller can be accessed via connector K2. This port could potentially be used to let the circuit communicate with the outside world, although it is not used in the present scanner design. Note that this port also operates with 3.3-V signals.

The supply voltage of the scanner is also available on connector K2. This could potentially be used to power a MAX3232. In the other direction, this connector could be used to provide the circuit with a stabilized 3.3-V supply voltage, but in this case the voltage regulator would need to be omitted.

Instead of using this circuit as a scanner, it would be possible to use two assembled circuit boards to implement a wireless link (optionally with bidirectional communication). In this case the microcontroller could be used to perform the more difficult tasks, such as driving the CYWUSB6935, while a simple protocol could be used on the serial port. One of the units could be built without the LCD module and fitted in a robot, while the other unit could be used to view the robot's parameters and send commands to the robot. There are lots of potential applications, and we're sure that Elektor readers can come up with even more ideas.

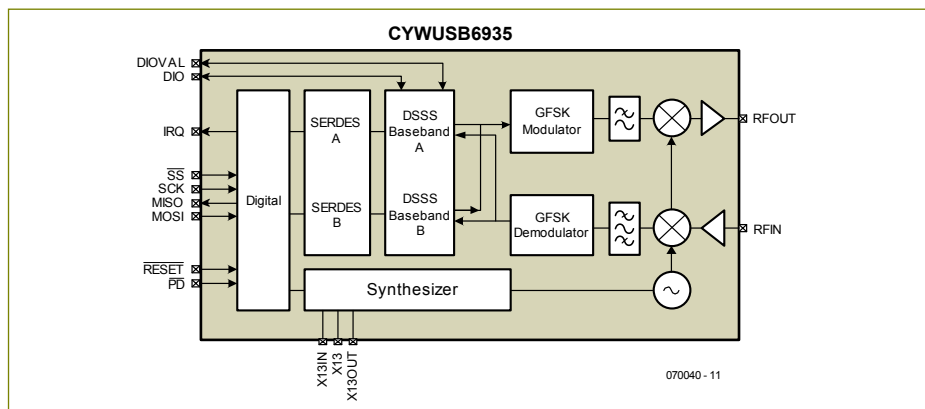


Figure 1. Block diagram of the Cypress CYWUSB6935 WiFi data transceiver.

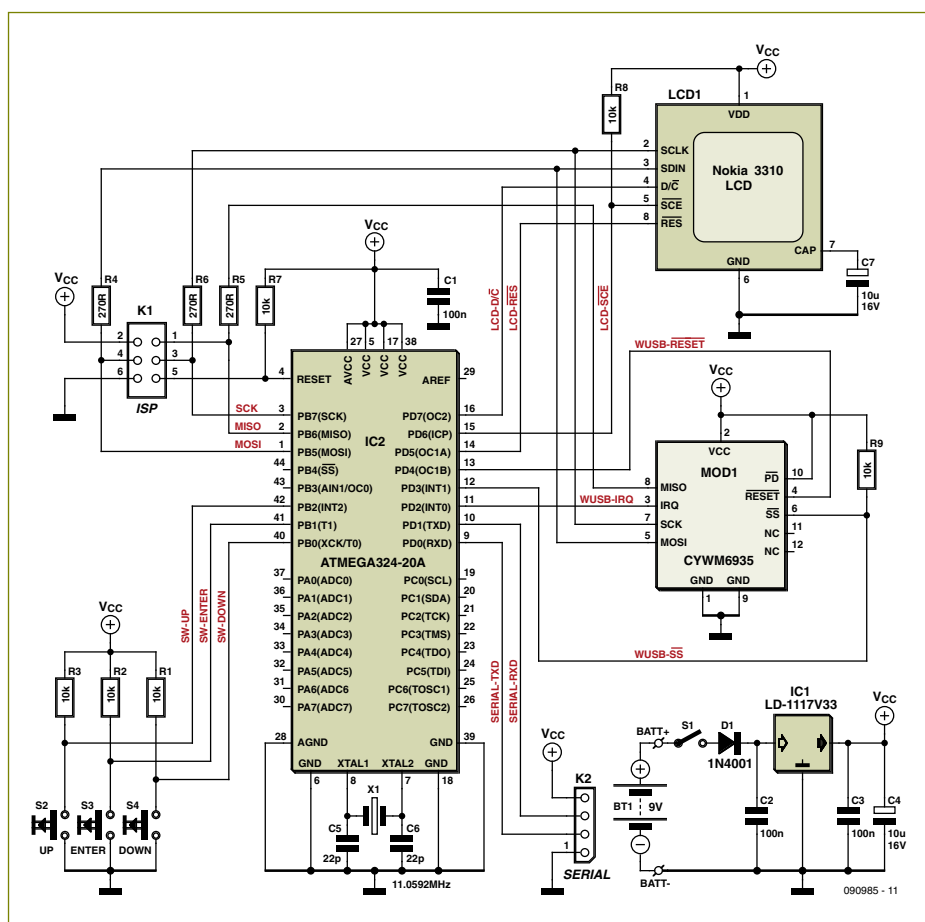


Figure 2. The main components of the circuit are an ATmega324, a Cypress WiFi module, and a display module from a Nokia 3310 mobile phone.

COMPONENT LIST

Resistors

R1,R2,R3,R7,R8,R9 = 10k Ω
R4,R5,R6 = 270 Ω

Capacitors

C1,C2,C3 = 100nF
C4,C7 = 10 μ F 16V radial
C5,C6 = 22pF

Semiconductors

D1 = 1N4001
IC1 = LD-1117V33 (ST Microelectronics)
IC2 = ATmega324-20A (programmed, Elektor Shop # 090985-41)
MOD1 = CYWM6935 module (Farnell # 1319925/1321748; RS Components # 382-620)

Miscellaneous

X1 = 11.0592MHz quartz crystal
K1 = 6-pin (2x3) pinheader
K2 = 4-pin pinheader
S1 = miniature switch
S2,S3,S4 = pushbutton, 5mm, PCB mount
12-pin (2x6) connector for MOD1, lead pitch 2mm
LCD for Nokia 3310 mobile phone (search 'Nokia 3310 display' on Ebay)
9V battery with clip-on leads, or 4 AA or AAA cells with holder
Project software # 090985-11 and Eagle file for PCB # 090985-1, available free from [4]

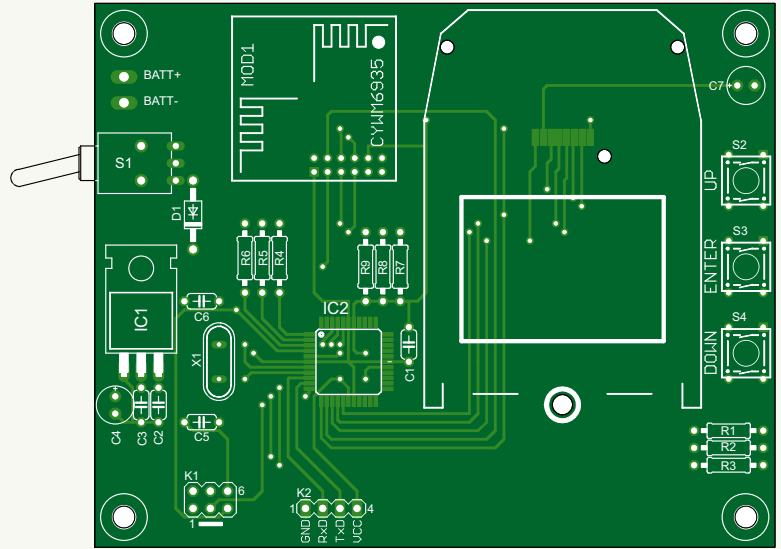


Figure 3. The spacious layout of the PCB makes assembly easy.



Figure 4. The display module consists of the actual display and a keypad section.

Construction

The author designed a PCB for the scanner (Figure 3) with a fairly spacious layout, so assembling the board should not present too many problems. Only one SMD component is used: the microcontroller, which comes in a 44-lead TQFP package.

The CYWUSB6935 module is ready to use and only has to be plugged into a header. Note however that the pin spacing is 2.00 mm instead of the usual 2.54 mm (0.1 inch).

You can buy the LCD module on the Internet at various sites, including eBay. The module comes with a flexible circuit that includes the contacts for the telephone keypad (see Figure 4). Remove the flexible circuit and saw the plastic substrate in two along the red lines shown in Figure 5. Be careful not to saw off the eyelet just below the display, since it is used for fitting the display. To ensure that the display contacts are correctly aligned on the PCB, there is a plastic tab on the display that fits into a hole in the PCB. The LCD module can be fitted securely to the PCB with two M2 screws at the top and an M3 (3 mm) screw at the bottom, as can be seen in Figure 6.

Start the assembly process by fitting the microcontroller, since it is an SMD com-

ponent. Soldering this IC requires a steady hand and a soldering iron with a fine tip. First secure the IC at one corner by soldering one lead in place, then align it precisely and solder the remaining leads. You can remove solder bridges between the leads afterwards with a bit of desoldering braid. After this, all of the other components can be fitted. Make sure that electrolytic capacitors C4 and C7 and diode D1 are fitted with the right polarity. The final assembly steps are to attach the LCD module to the board and plug in the CYWUSB6935 module. A 9-V battery provides an adequate source of operating power.

The firmware

The microcontroller can be programmed via connector K1. Note that the microcontroller has a supply voltage of 3.3 V, so it must be programmed using 3.3-V signals. The Atmel STK500 development module can be set to operate at 3.3 volts, so the microcontroller can be programmed using this module without any problems. If you only have a 5-V programmer, you will have to adapt the voltage level. You can use a MAX3392 for this as described in [3], or you can use a level shifter built from discrete components. The software is available on the Elektor website [4] as a free download. For readers who would rather not program the microcon-

troller themselves or are not able to do so, a pre-programmed IC is available from the Elektor Shop (item # 090985-41).

The user interface

Once the firmware has been loaded into the microcontroller, the unit will display the main menu after it's switched on. The screen shows several options, which you can navigate using the buttons.

The Up and Down buttons move the cursor, while the Enter button executes the selected menu command. From the main menu, you can start the scanner, adjust the display parameters, or show information about the CYWUSB6935 module and the firmware. If you change any of the display settings, such as the contrast, you can store the new settings in the microcontroller EEPROM so that they will be used automatically the next time.

If you switch on the scanner while holding the Up button pressed, the display parameters are reset. If you hold the Enter button pressed while switching on the unit, the scanner enters the Contrast menu directly after it starts up, and you can then use the



Figure 5. Saw through the plastic substrate along the red lines marked on this photo.



Figure 6. The display module is fitted to the PCB with two M2 screws and an M3 screw.

Up and Down buttons to adjust the contrast. The author has noticed that the standard display settings yield an unreadable result with some display modules. The spectrum of the 2.4-GHz band is displayed in the scan mode. The frequency

scale is indicated by tick marks directly below the spectrum plot. In most areas the ISM section of the 2.4-GHz band is divided into 84 channels from 2.4000 GHz to 2.4835 GHz, and the LCD module just happens to have 84 columns. The centre fre-

Links and References

[1] Wireless links, Elektor January 2009

[2] 2.4 GHz WiFi Spectrum Analyzer, Elektor June 2007

[3] Universal User Interface Module, Elektor December 2008

[4] www.elektor.com/090985

Advertisement



Take out a free subscription to E-weekly now

Do you want to stay up to date with electronics and computer technology? Always looking for useful hints, tips and interesting offers? Subscribe now to E-weekly, the free Elektor Newsletter.

Your benefits:

- The latest news on electronics in your own mailbox each Friday
- Free access to the News Archive on the Elektor website
- You're authorized to post replies and new topics in our forum



Register today on

www.elektor.com/newsletter

Menu Control

The main menu is pictured at the top here.

The Setup and About menu items each have a submenu.

The submenu 'Setup' has five options:

Use the first three menu items to adjust the contrast, bias, and temperature coefficient of the LCD module.

Use the EEPROM Store menu item to save the settings in the microcontroller EEPROM. When the scanner starts up, the saved values are read from the EEPROM and used to configure the LCD module.

The final menu item, Back, returns you to the main menu.

If you select About from the main menu, the following three options are displayed:

The Transceiver menu item shows information about the CYWUSB6935 module in the unit, including the unique manufacturing number:


The Firmware menu item shows the firmware version number.

If you select Scan in the main menu, scanning is started (lower picture):

The scanner starts up in Run mode, in which it constantly scans the entire 2.4-GHz band and shows the results on the LCD module. The maximum reading for each channel is saved and displayed. After a few seconds, you can easily see how the 2.4-GHz band is being used.

In the scan picture, you can see that WiFi band 1 is being used by a device that occupies approximately 20 channels. This is the author's wireless music player. You can also see a somewhat weaker signal in WiFi band 6. This is probably the wireless local network of one of the author's neighbours. In addition, a fairly strong continuous signal can be seen in channel 51. This is a narrow-band signal, and it is constantly present. The author was not able to determine the origin of this signal.

There are no signals in the channels above

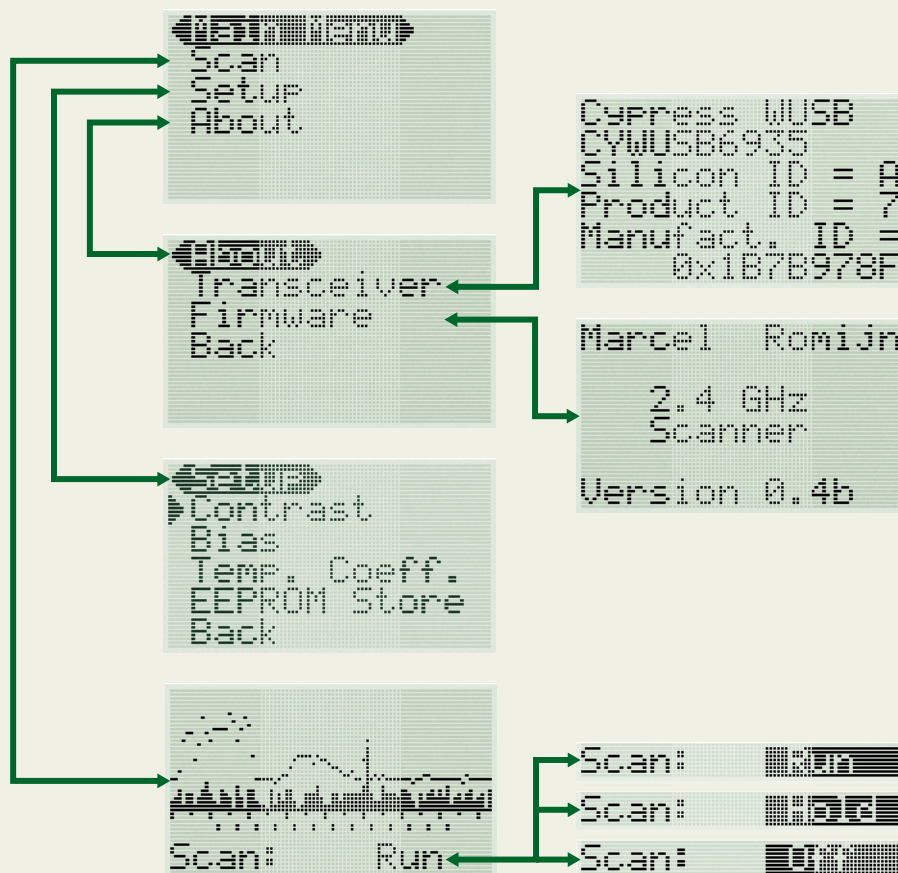

channel 52. Here you can see the maximum noise floor level.

The scanner menu appears at the bottom of the screen. You can use the Up and Down buttons to navigate through this menu. Depending on the selected menu item, you can initiate an action or adjust a setting.

Use the first menu item to set the scan mode. It can have the values Run, Hold, and Off. Press Enter to select a different scan mode. This is indicated by displaying the selection in reverse video. Use the Up and Down buttons to select the desired setting. Press Enter again to save the setting, after which you can continue navigating through the submenu.

The next menu item controls whether the peak values (the 'limits') are shown (Show) or hidden (Hide).

Use the following menu item to reset the peak values. If you press Enter with this menu item selected, the peak values are reset immediately. This is a menu item that performs an action directly.

The following menu item indicates how many times each channel should be measured before the scanner switches to the next channel. The highest reading of the repeated measurements is used.

The next menu item is similar, but instead of indicating how many times the measurement is repeated for each channel, it indicates how many times the entire 2.4-GHz band should be scanned before the results are displayed.

The final menu item exits the scanner settings submenu and returns to the main menu.

quencies of the 13 WiFi channels are also indicated below the tick marks.

A single-line menu that can be used to set the scanning parameters is located at the

bottom of the screen. Just as with the regular menu, the Up and Down buttons can be used to navigate through this menu, while the Enter button can be used to perform an action or set a value.

The menu interface is described in more detail in the Menu Control inset.

(090985)

Computer digital audio interface

By Joseph Kreutz (Germany)

Computer motherboards and lots of other computer devices are fitted with digital audio inputs and outputs in S/PDIF format, but which only produce or accept a TTL-level signal. Despite their undoubted usefulness, opto-interfaces are usually lacking. The project described in this article is intended to make up for this shortcoming.


The receiving part comprises a transformer-isolated S/PDIF electrical interface, based on the receiving section of IC3, an SN75179B or equivalent differential driver/receiver. This part of the circuit is arranged in such a way as to produce a zero output signal if there is no input signal present. The opto receiver IC2 is a TORX173. Logic gates IC1b to IC1d are wired to form an OR gate to steer the signals to the TTL output, from where they will be applied to the equipment intended to receive them. Needless to say, the optical and electrical input can't both be used at the same time, since otherwise it would be impossible to decode and use the signals. The function of IC1a, along with D1, D2, and the R2/C1 and R3/C2 networks, is to indicate if such an error condition arises, in which case the LED lights to indicate the problem.

Transformer TR1 is hardly difficult to make: a primary of six turns of enameled wire (0.3–0.5 mm dia.; AWG # 28–24) and a secondary of 12 turns of the same wire are wound onto an Epcos L44-X830 ferrite ring (12.5 mm dia.). Any ferrite ring with $\alpha = 2200 \text{ nH}/\sqrt{\text{turn}}$ will do.

The TTL signal from the computer device is applied to the driver section of IC3. The inverting output is applied to transformer TR2 via C6 and R7. TR2 uses the same ferrite ring as TR1, but has 20 turns for the primary and eight for the secondary. You'll need to make sure you connect its primary in reverse phase, to make up for the signal inversion introduced by IC3. The non-inverting output of IC3's driver section is connected to a TOTX173 opto-transmitter. Naturally, there's no problem at all about using the electrical and optical digital outputs at the same time.

Building this circuit requires no special comments. Each IC needs to be decoupled by a 0.1 μF capacitor as close as possible to its supply pins, and overall decoupling of the circuit at lower frequencies will be taken care of by a 10 μF , 16 V electrolytic capacitor. The 5 V supply rail can be derived from the computer equipment where the interface is going to be installed.

(090611-I)

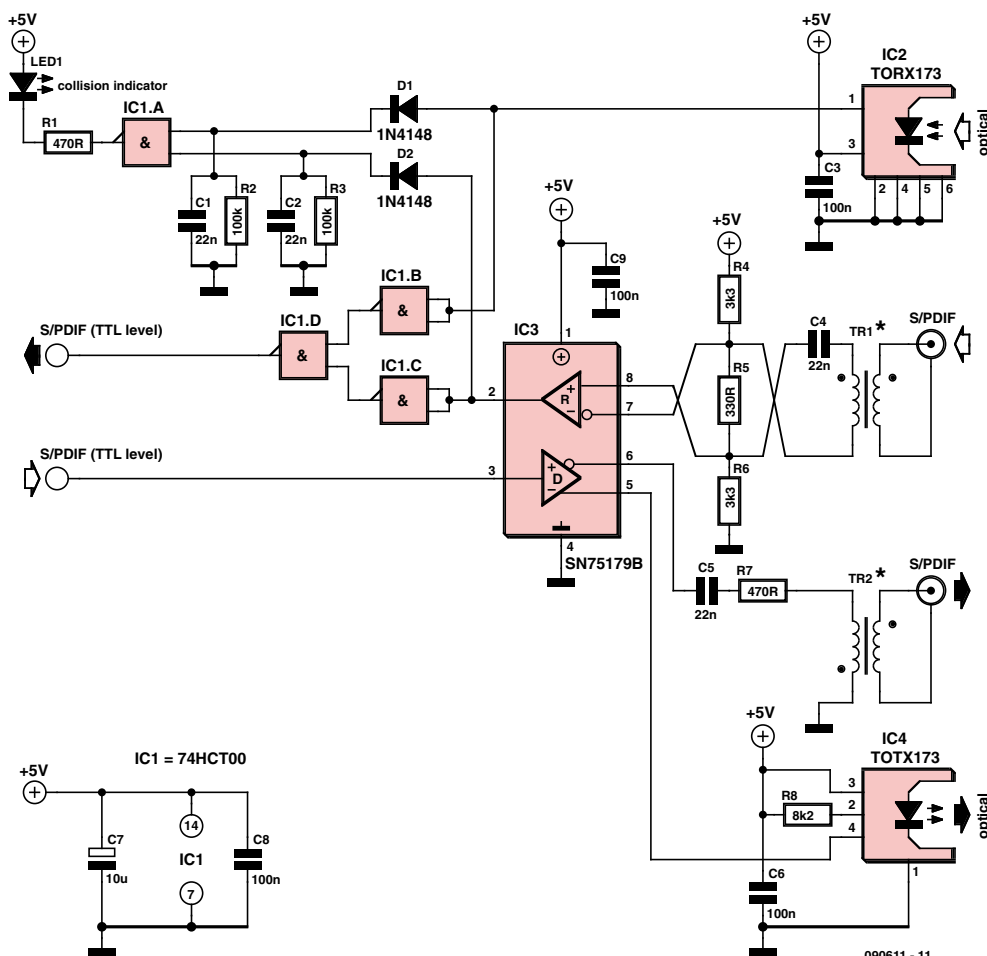

Blinded by the Light?

Lamp PFC investigated

By Ton Giesberts (Elektor Labs) & Clemens Valens (Elektor France)

When the load of a power supply is not purely resistive but reactive, or worse, non linear, the current through the load may not have the same shape as the voltage across it, and a phase difference between voltage and current will exist. In this case the apparent power drawn by the load is larger than the real or active power consumed by it. The ratio between the real power and the apparent power is called the power factor. When its value drops too low, problems arise.

A low power factor is a problem for energy providers, not the users, because they only pay the real power consumed. Energy providers have to assure that their power supply systems are capable of safely providing the total apparent power demand of all users. Since the apparent power is always higher than the real power, the supply system (AC grid) has to be over dimensioned, which is expensive. More power also means higher losses in the form of heat and consequently more resources are necessary to produce the real power. Non-linear loads also create harmonics that produce excess heat and may cause interference in other equipment. It should be clear by now; we want a power factor of 1 (say, one), i.e. apparent power should equal real power.

High volume energy users like industrial plants actually have to pay for the apparent power they use but households generally don't. Industrial users sometimes install special equipment to control their power factor striving to approach the value 1. This is called power factor correction (PFC). The European standard IEC 61000-3-2 ^[1] sets detailed limits for a consumer (not professional) load up to and including 16 A per phase connected to the public AC grid. **Table 1** shows the subdivision into four classes A, B, C and D of which the last two are the most interesting to us. All electrical equipment marketed to European consumers must comply with this standard.

Linear and non-linear loads

Most loads are not purely resistive. Incandescent light bulbs are, but as soon as there is a bit more involved the load becomes a complex impedance. Many loads have motors and these are typically inductive loads. That's why the real current usually lags the line voltage. The phase difference, often called phi (Φ in Greek), between the current and the voltage is a measure for the power factor. As a matter of fact, when the current and the load are both perfect sine waves then the power factor is simply equal to $\cos(\Phi)$ (**Figure 1**). This is why the power factor is also called $\cos \phi$, even though this is incorrect when the wave shapes involved are not perfect sines. But when they are, the power factor can be corrected by adding a capacitor (or banks of them) in parallel with the load, and that's exactly what professional users sometimes do. Thanks to the capacitors they keep their energy bills down.

Today, electrical loads are becoming increasingly more complex and many have even gone non-linear, i.e. the current is no longer a linear function of the AC grid voltage. This happens as soon as rectifiers and switched mode power supplies enter the arena, which is the case for most of our modern household electronics like computers, TV sets, fluorescent lighting and LED light bulbs, etc. Non-linear currents have harmonics that can cause problems when capacitors are used to improve the power factor. In certain cases the harmonics in combination with these capacitors may result in resonances producing overvoltage situations and heat, potentially damaging equipment.

Power factor correction of non-linear loads requires other techniques than simply adding a capacitor to the load. It can be done passively with (bulky) filters that suppress the harmonics produced by the load. Another approach is active PFC, a method that adds electronics circuitry to the load to make it look more passive.

Measuring the power factor

To measure a load's power factor you need to measure the real or active power with a wattmeter and the effective load current I_{rms} and the effective voltage V_{rms} across the load. The product $I_{\text{rms}} \times V_{\text{rms}}$ is the apparent power and the power factor PF is the real power divided by the apparent power. Most people do not have the necessary equipment to measure these quantities properly and besides it's a dangerous operation if you cannot isolate the load from the AC power lines.

Elektor labs have done some measurements of Class C equipment (lighting) using the circuit from **Figure 2**. A variac (variable transformer) was used to isolate the load from the AC power line and a 100:1 oscilloscope probe (special high-voltage version) was used to measure the voltage at the load. The 10 Ω resistor was a 5 W type. If you do not have these tools, please do not try to repeat our measurements, **it can be lethal!**



Our oscilloscope was a LeCroy 9410 capable of displaying in real time the Fourier series (magnitude and phase) of one of the traces. We used that feature on the current measurements to visualize the harmonics. In all experiments I_{rms} was measured with a Fluke 187 true rms multimeter.

Some real measurements

To illustrate the effect of a load on the power factor we first measured a traditional incandescent 100 watt light bulb. This is a pure resistive load and the PF should be 1. **Figure 3** shows the results: the current is perfectly in phase with the voltage and has the same shape; it is indeed a resistive load hence $PF = 1$. Note that the phase trace shows two peaks for the third and seventh harmonic, even though the magnitudes of these harmonics are very small.

The reason is the distortion of the AC power line voltage wave shape which is not a perfect sine wave at all.

Next we measured a fluorescent tube (36 W TL-D made by Philips). The traces in **Figure 4** show a reactive load, although not perfect as the current wave shape is clearly distorted around the zero crossings. The Fourier traces show a clear third harmonic and a small fifth. Nevertheless, the current is very reactive and may be corrected with a capacitor (which was absent in our test setup). Ignoring the harmonics the PF for this tube is about 0.5 because the phase difference between the current and the voltage is about 60° and $\cos(60) = 0.5$.

When we started measuring on compact fluorescent lamps (CFLs), also known as energy saving lights, things became more interesting. We looked at three different models, two recent ones (a Philips PLE-C PRO 11 W and an unknown 11 W model found in a product from a well-known Swedish furniture manufacturer) and a several years old but still working lamp (20 W Isotronic 10112). **Figures 5 to 7** show the results that look surprisingly similar and strange at the same time. These wave shapes are typical for these kinds of lights and show their switching nature.

Determining the power factor from such traces is difficult unless you have access to the Fourier series that goes with them. The trick is to first determine the effective value of the in-phase fundamental frequency of the current and then divide it by the measured effective current I_{rms} . For the Philips PLE-C the magnitude of the fundamental is about 700 mV across $10\ \Omega$ with a phase difference of 20 degrees. Hence, the in-phase current is $(700\text{ mV}/10\ \Omega) \times \cos(20) = 66\text{ mA}$ and its effective value is $66\text{ mA}/\sqrt{2} = 47\text{ mA}$. The I_{rms} value we measured for this lamp was 67 mA, which gives us a PF of 0.70 for this lamp. Similar reasoning gives us a PF of $81/107 = 0.76$ for the Isotronic bulb and $56/76 = 0.73$

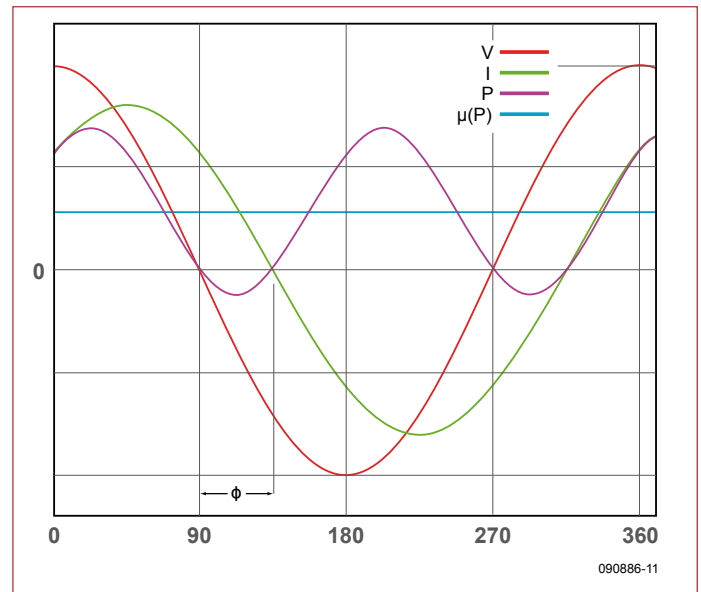


Figure 1. The relation between voltage, current and power factor Φ . $P = VI$ and $\mu(P)$ is the average value of the power P . (source: Wikipedia)

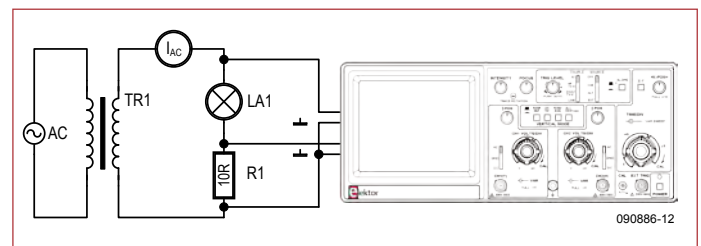


Figure 2. Experimental setup to determine some power factors.

for the Ikea lamp.

From the CFL to the LED lamp is just a small step. The LED lamp is making big progress in market share (in quality too, but not as spectacular) and many of you will have one or more at home. The

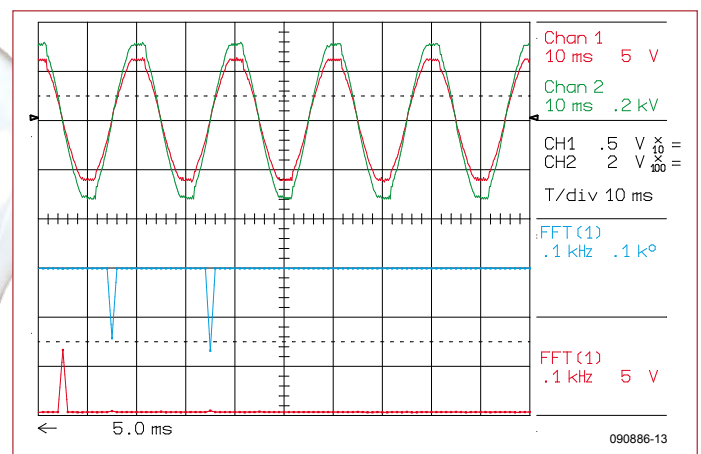


Figure 3. Results from a 100 W incandescent lamp. This was a 220 V model and the measured I_{rms} was 440 mA.

POWER FACTOR CORRECTION

Table 1. Equipment classification	
Class	Description
A	Balanced three-phase equipment; household appliances, excluding equipment identified as class D; tools, excluding portable tools; dimmers for incandescent lamps; audio equipment. Equipment not specified in one of the three other classes shall be considered as class A equipment.
B	Portable tools, arc welding equipment which is not professional equipment. (Professional equipment is equipment not available to the consumer.)
C	Lighting equipment.
D	Equipment having a specified power less than or equal to 600 W, of the following types: personal computers and personal computer monitors; television receivers.

Source: IEC 61000-3-2

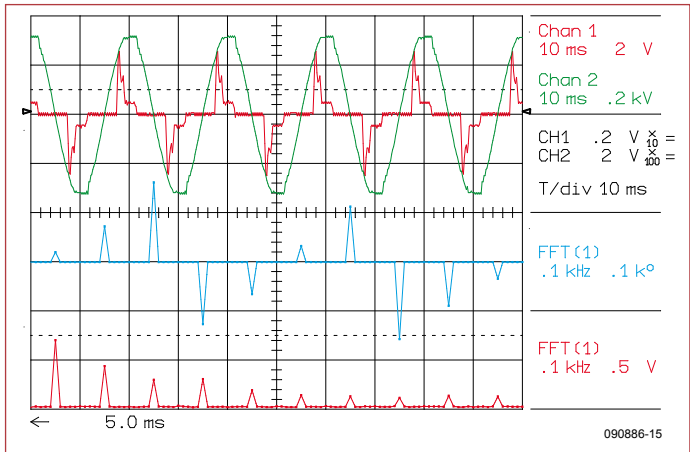
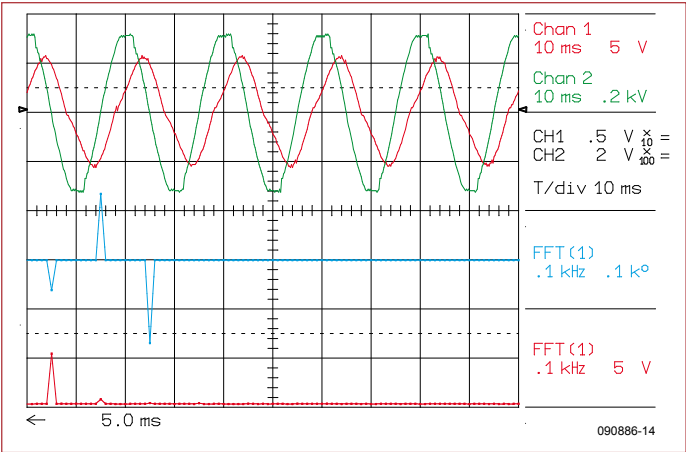


Figure 4. A reactive load in the form of a 36 W fluorescent tube; $\cos(\Phi) = 0.5$. $I_{rms} = 352$ mA.

Figure 5. An 11 W PLE-C PRO CFL from Philips. $I_{rms} = 67$ mA.

traces in **Figures 8 and 9** show the results for two models we had lying around, a monochrome one and a three-color lamp with indi-


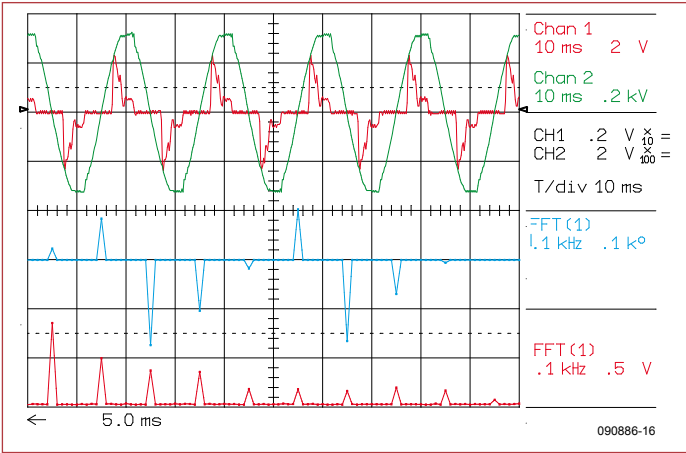


Figure 6. As Figure 5, but now for the Ikea lamp. $I_{rms} = 76$ mA.

vidual remotely controllable colors. These lamps were both from that widely known brand called “Made in China”.

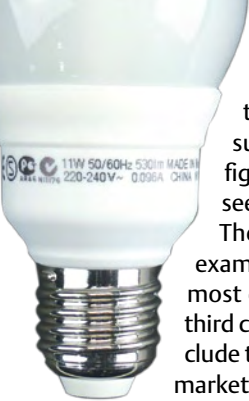The current traces are very spiky, due to the little bit of power consumed by these lamps, but they result in a very wide spectrum. For these lamps, $PF = 20/34 = 0.59$ (monochrome) and $12/28 = 0.43$ (three-color).



Do they pass?



IEC 61000-3-2 subdivides lighting equipment (Class C) into devices consuming up to and including 25 W and those that consume more. For both subclasses maximum figures have been set for harmonic currents, see **Table 2**.

The three CFL lamps and the two LED lamps examined in the lab all have strong harmonics, most of which do not respect the values in the third column of **Table 2**. Should we therefore conclude that these lamps are illegal on the European market? Probably not, as there is a second clause for lamps that consume up to and including 25 W — see (and try to understand) the fourth column of **Table 2**. This clause

Table 2. Limits for class C equipment

Harmonic order	Maximum permissible harmonic current		
	Active input power > 25 W	Active input power ≤ 25 W	
n	% of input current at fundamental frequency	mA/W	The third harmonic current, expressed as a percentage of the fundamental current, shall not exceed 86 % and the fifth shall not exceed 61 %; moreover, the waveform of the input current shall be such that it begins to flow before or at 60°, has its last peak (if there are several peaks per half period) before or at 65° and does not stop flowing before 90°, where the zero crossing of the fundamental supply voltage is assumed to be at 0°.
2	2	-	
3	30 × power factor	3.4	
5	10	1.9	
7	7	1.0	
9	5	0.5	
11	3	0.35	
13 ≤ n ≤ 39 (odd harmonics only)	3	3.85/n	

Source: IEC 61000-3-2

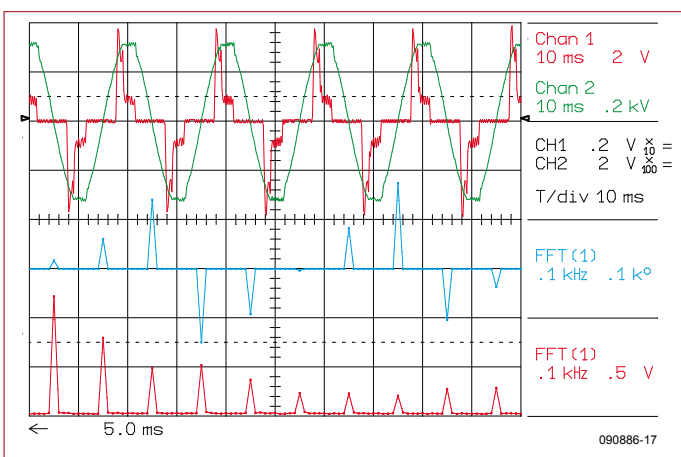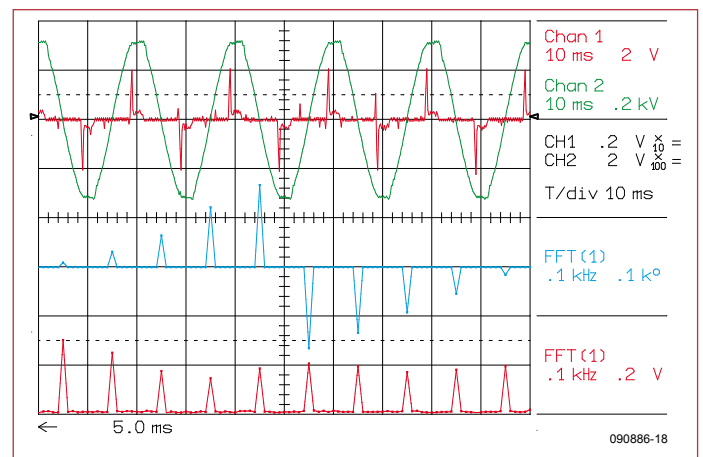Figure 7. Similar to Figures 5 and 6; data obtained from an old 20 W Isotronic CFL. $I_{rms} = 107$ mA.Figure 8. This el-cheapo monochrome LED lamp exhibits an almost flat current spectrum yet seems to be conform to IEC 61000-3-2. $I_{rms} = 34$ mA.


only mentions harmonics three and five and allows much higher values, so our lamps probably all pass thanks to this clause. It makes you wonder about the point of these clauses, as it actually seems hard to produce something non-compliant.

Also, the lab measurements did not respect the test conditions specified in IEC 61000-3-2 and admittedly instruments were not carefully calibrated; we just did some quick and dirty measurements using the available AC power line with noise and all. Yet the results are surprising and they are probably not that far off the mark.

Should you worry about all this? Probably not. Even if you light ten or more of these lamps at the same time, you still consume relatively little power and their influence on the total household power factor is likely to remain limited. Still, you are polluting the AC power line voltage.




(090866-1)

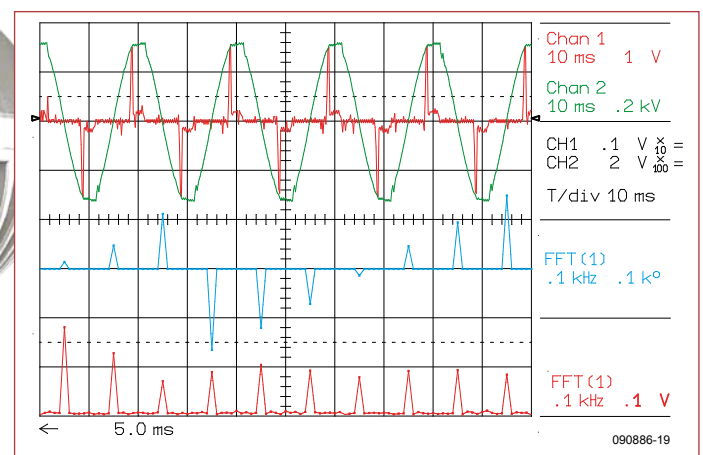[1] IEC 61000-3-2 2005-11 (third edition). www.iec.chFigure 9. The spectrum of the remote controlled three color LED lamp is as bad as the one of the LED lamp from Figure 8. $I_{rms} = 28$ mA.

The ATM18 Radio Computer

Using the SI4735 DSP radio chip

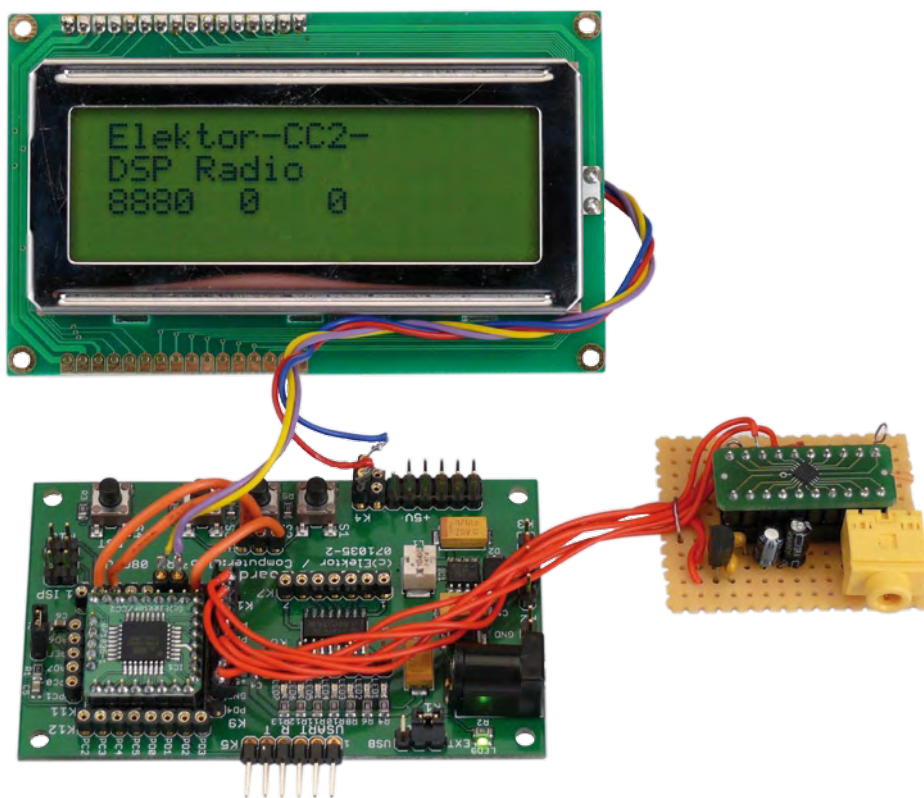By Burkhard Kainka and
Wolfgang Rudolph (Germany)



Once upon a time radio reception was so simple. You just needed three components and a set of headphones. Best reception was after sundown, with an aerial stretching the length of the garden and a little patience you could pull in lots of stations. Nowadays you can do a similar job using the computing power of thousands of transistors crammed into a tiny chip.

One of the earliest types of radio receiver was the detector receiver. A coil together with a variable capacitor took care of frequency selection. A small chunk of crystal that you might dig up in your back garden served as a signal rectifier. Hook up a long wire out of the window for the aerial, add a set of high impedance headphones (2 x 2,000 Ω) and you were in business. In those days it was the cutting edge of technology. In time the crystal detector was superseded by the more reliable diode. Gone were the days of probing the crystal surface with the tip of a fine wire (cat's whisker) to find a defect in the crystal lattice where the best rectifier effect was produced. In time valves made way for transistors and radio front-ends eventually became populated by high frequency RF transistors. A big leap in radio performance came about at the introduction of the highly sensitive superhet radio which was not improved upon for many years. Also the complex method of signal

conversion using one or more intermediate frequencies remained unchanged. A classic radio design of this era used coils, variable capacitors, IF filters and a host of other components. Many of the important receiver properties such as spurious response rejection, selectivity and large-signal rejection etc depend largely on the type of filters used in the design. With increasingly sophisticated technology all the processes such as AM and FM demodulation, stereo decoding and RDS information recovery were performed by highly-integrated specialized chips. Eventually we saw the introduction of one-chip radios, first for AM and then later FM so that when we set out to build a radio using these components there was hardly any building left to do.

A Software Radio

More recently came the idea of a Software Defined Radio (SDR). This was a completely new concept which had little in common

with traditional radio design. SDR uses computer software to carry out the functions usually performed by the receiver hardware. Receiver parameters can be changed 'on the fly' with minimum time delay and almost at will. We have already shown in Elektor what's achievable in a Software-defined-Radio design. With the hardware reduced to a minimum you will find no conventional RF components on the PCB. The intermediate frequency (IF) is digitised by the computer sound card for further processing. The SDR program running on a computer takes care of the rest. Adjustable bandwidth, different demodulation techniques, automatic level control, in fact there are very few parameters that cannot be altered. At the end of the chain a D/A converter in the sound card outputs the demodulated audio to a set of active speakers.

DSP Radio

While the first wave of SDRs were defined

Main features of the SI4735

- VHF range: 64–108 MHz
- LW range: 153–279 kHz
- MW range: 520–1710 kHz
- SW range: 2.3–21.85 MHz
- PLL with integrated VCO
- Automatic frequency control (AFC)
- Automatic gain control (AGC)
- Integrated LDO voltage regulator
- Digital FM stereo decoder
- Programmable reference frequency
- Digital volume control
- RDS support
- Optional digital audio output
- 2 or 3 wire interface
- Supply voltage 3.3 V typ.
- Outline 3 x 3 x 0.55 (mm), 20 pin QFN



Figure 1. The 3 mm x 3 mm radio.

(as the name suggests) in software i.e. from a program running in a computer so the more recent wave of digital radio chips have appeared which do not use a computer and are therefore not really SDRs in the original sense of the term. Processing of the receive signal is performed in the chip using a digital signal processor (DSP). The external controller just interprets user commands and tells the radio chip what it should do. As an extreme example of this concept we see here a 3 mm x 3 mm chip which just requires an aerial, a power supply and two active speakers to make a stereo VHF receiver. Very little additional hardware is required, a coil and a capacitor are all that are necessary for VHF reception. We will use the Elektor ATM18 AVR board as the controller for the radio.

DSP ICs operating at RF are usually thought of as expensive and power hungry beasts but that cannot be said of the SI4735 from Silicon Labs (www.silabs.com). This is a DSP receiver containing all the necessary RF stages; frequency synthesizer, A/D converter, DSP and D/A converter all squashed into a tiny SMD package! The chip shown in Figure 1 is a complete AM/FM receiver. The AM band extends from 153 kHz (Long wave) up to 21.85 MHz (13-m short wave band), with switchable bandwidth filters and a particularly sophisticated gain control section. VHF reception covers the 64 MHz to 108 MHz band with an integrated stereo decoder and RDS output. The chip also supplies information indicating signal strength (RSSI) in dBμV and signal-to-noise ratio (SNR) in dB of the received signal. The SI4735 could be used as a RF signal level measurement receiver.

The chip has a good specification which makes it ideal for use in the design of travel radios, clock radios or MP3 players and mobile telephones which are now increasingly being offered with built-in radio receivers. The first travel radio design featuring DSP chips from SI is already available. The object of the exercise here of course is not to buy a ready built radio but to find out just how easy it is to make our own. First off we need some form of microcontroller to allow input of data to the chip and which can dis-

play information such as receive frequency, volume etc. This is where our ATM18 AVR board comes in, together with the SI4735 we can build a really versatile receiver with very little additional outlay.

The block diagram of the chip in Figure 2 shows the layout of a typical IQ type of receiver, similar to that which was used in our shortwave receiver. In this case however the signal decoding is performed not by external PC software but via a DSP built-in to the chip. An external microcontroller acts as a control interface with the user.

Interface to the ATM18 AVR board

You will only need a few hook-up wires to connect the supply voltage, reset sig-

nal and I²C Bus from the ATM18 AVR board to the radio board before you have a fully functioning VHF receiver. The IC produces a surprisingly good audio output signal and the receiver stage has good sensitivity even with a short antenna. The only additional stage necessary is a stereo amplifier. A set of active speakers such as those used on a PC will do. Those of you wishing to tune in to AM broadcasts can do so later by just making a few simple changes to the receiver.

The chip is supplied in a QFN outline package which is so tiny it is difficult to solder. The solution is to use a carrier board with the chip pre-mounted (Figure 3). The carrier has the same footprint as a 20-pin DIP IC so it can either be mounted using a cor-

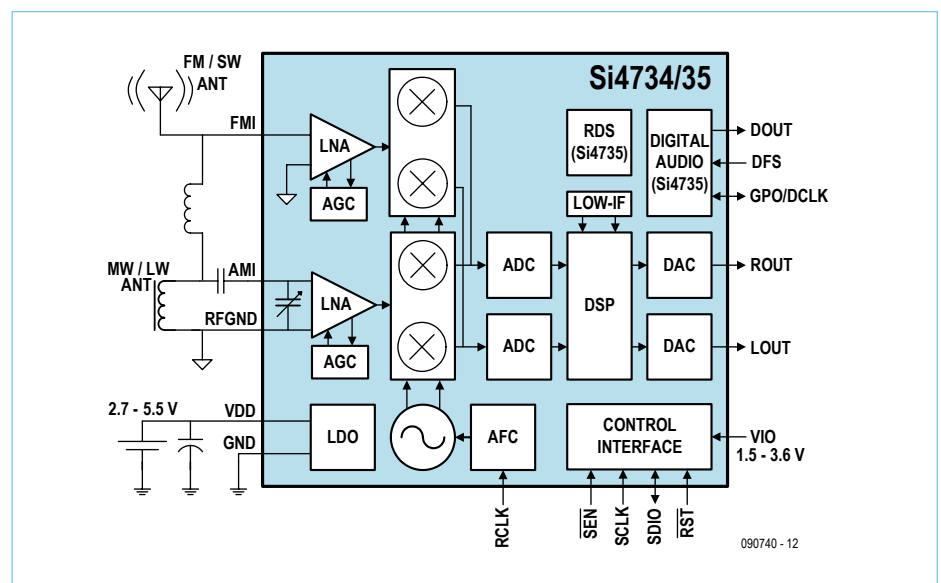


Figure 2. The SI4735 block diagram (source : www.silabs.com).

Listing 1. Initialisation and setup

```

Config Timer0 = Pwm , Prescale = 1 , Compare A
  Pwm = Clear Down
Start Timer0
Pwm0a = 128 'Xtal/2/(255) = 31373 Hz OC0A/ PD6

Ddrd.4 = 1          'Reset SI4735
Waitms 100
Ddrd.4 = 0
Waitms 100

Ffm = 8880          'Start freq FM *10 kHz
Vol = 63            'Volume 0...63
...

Sub Fm_start()
  Init_fm
  Waitms 200
  Refclock
  Waitms 5
  Rx_volume
  Waitms 5
  Fm_tune_freq
End Sub


Sub Init_fm()
  I2cstart
  I2cwbyte 34
  I2cwbyte &H01
  I2cwbyte &H00
  I2cwbyte &H05
  I2cstop
End Sub

Sub Refclock()
  I2cstart
  I2cwbyte 34
  I2cwbyte &H12
  I2cwbyte &H00
  I2cwbyte &H02
  I2cwbyte &H01
  Ref = 31373
  H = High(ref)
  L = Low(ref)
  I2cwbyte H
  I2cwbyte L
  I2cstop
End Sub

Sub Fm_tune_freq();
  I2cstart
  I2cwbyte 34
  I2cwbyte &H20
  I2cwbyte &H00
  H = High(ffm)
  L = Low(ffm)
  I2cwbyte H
  I2cwbyte L
  I2cwbyte &H00
  I2cstop
End Sub

Sub Rx_volume()
  I2cstart
  I2cwbyte 34
  I2cwbyte &H12
  I2cwbyte &H00
  I2cwbyte &H40
  I2cwbyte &H00
  I2cwbyte &H00
  I2cwbyte Vol
  I2cstop
End Sub

```

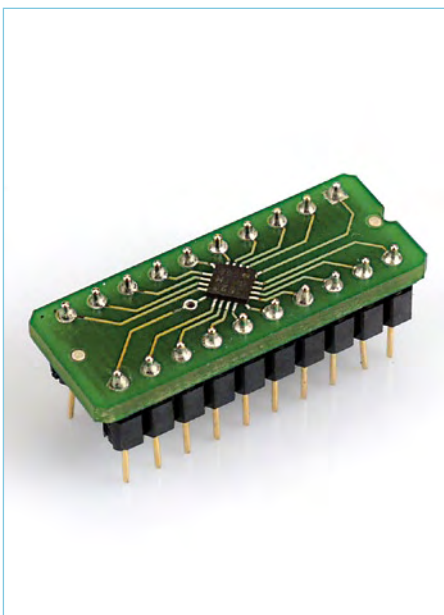

responding socket or by just soldering flying leads. To complete the receiver circuit shown in Figure 4 you need to add a few resistors, a fixed inductor and two diodes. The two Schottky diodes protect the input from large RF impulses so are not strictly necessary for operation. The circuit can be built on a small square of prototyping perfboard.

The IC requires a supply voltage of 3.3 V on pins VDD and VIO. NB: VDD can only withstand 3.6 V maximum! Make sure that it is not accidentally connected to the 5 V supply.

Figure 3.
The SI4735 is soldered to a carrier board.

The SI4735 has a number of digital interfaces but the one we are using here is the I²C bus. This requires just two wires, one for SDA and one for SCL. These carry commands to the IC and receive status information back from the IC to the ATM18 AVR board (ATmega88). In addition a connection to the IC's reset input is necessary with a pull-up resistor to the 3.3 V. This acts as a level shifter when the port output of the ATM18 AVR board is switched between high impedance (High) and low impedance (Low), this is normal practice for the I²C bus signals.

Apart from this the receiver needs a clock to use as a tuning reference. A 32.768 kHz watch crystal is typically used here but the chip can accommodate other frequencies. The value of the reference clock is sent to the chip during initialisation. Its minimum value is 31.130 kHz and maximum is

Listing 2. Station search and Status display

```

Sub Fm_seek_freq_up()
  I2cstart
  I2cwbyte 34
  I2cwbyte &H21
  I2cwbyte &H0C
  I2cstop
End Sub

Sub Fm_seek_freq_down()
  I2cstart
  I2cwbyte 34
  I2cwbyte &H21
  I2cwbyte &H04
  I2cstop
End Sub

Sub Fm_tune_status()
  I2cstart
  I2cwbyte 34
  I2cwbyte &H22
  I2cwbyte &H3
  I2cstop
  I2cstart
  I2cwbyte 35
  I2crbyte Status , Ack
  I2crbyte R1 , Ack
  I2crbyte R2 , Ack
  I2crbyte R3 , Ack
  I2crbyte R4 , Ack
  I2crbyte R5 , Ack
  I2crbyte R6 , Ack
  I2crbyte R7 , Nack
  I2cstop
  Freq = 256 * R2
  Freq = Freq + R3
  Rssi = R4
  Snr = R5
  Lcdpos = 2 : Lcdline = 3 : Lcd_pos
  Lcdtext = Str(freq) + " " : Lcd_text
  Lcdpos = 8 : Lcdline = 3 : Lcd_pos
  Lcdtext = Str(rssi) + " " : Lcd_text
  Lcdpos = 12 : Lcdline = 3 : Lcd_pos
  Lcdtext = Str(snr) + " " : Lcd_text
End Sub


Sub Fm_rsq_status()
  I2cstart
  I2cwbyte 34
  I2cwbyte &H23
  I2cwbyte &H00
  I2cstop
  I2cstart
  I2cwbyte 35
  I2crbyte Status , Ack
  I2crbyte R1 , Ack
  I2crbyte R2 , Ack
  I2crbyte R3 , Ack
  I2crbyte R4 , Ack
  I2crbyte R5 , Ack
  I2crbyte R6 , Ack
  I2crbyte R7 , Nack
  I2cstop
  Rssi = R4
  Snr = R5
  Lcdpos = 8 : Lcdline = 3 : Lcd_pos
  Lcdtext = Str(rssi) + " " : Lcd_text
  Lcdpos = 12 : Lcdline = 3 : Lcd_pos
  Lcdtext = Str(snr) + " " : Lcd_text
End Sub

```

40 MHz, built-in dividers are used to generate a 32 KHz (approx) internal clock. It should be noted that overtones generated by higher frequency inputs can adversely affect the receiver performance so for this reason a reference clock of approximately 32 KHz was chosen. The ATmega88 has no problem generating it from one of its PWM outputs. Accuracy and stability of receiver tuning is therefore ultimately referenced back to the 16 MHz crystal used in the ATM18 AVR board.

The ATM18 AVR board also interfaces to an LC display using the signals from B1 and B2. Three pushbuttons are also wired to B0, B3

Figure 4.
The radio module connections to the ATM18 AVR board.

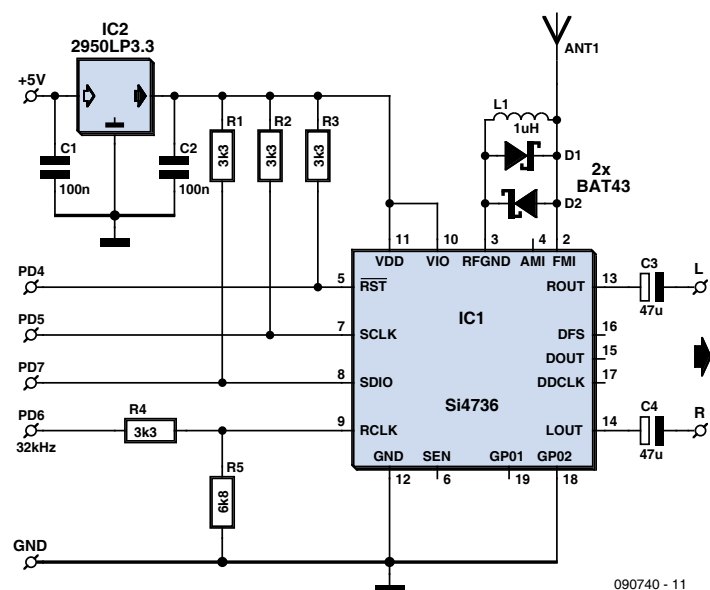

Detector

Even before diodes became commercially available it was possible to rectify HF signals using a type of envelope detector which can detect amplitude modulated RF signals. Firstly a small fragment of either galena (lead sulphide) or iron pyrite crystal is necessary. This crystal is held in a metal clamp which also serves as one electrical connection for this rudimentary 'diode'. The other connection takes the form of a thin pointed wire pressed lightly against the crystal surface (often with the help of a light spring). The tip is moved over the crystal surface by hand to find a 'point defect'. This is a spot in

the crystal where a vacancy or pair of vacancies has occurred in the crystal lattice.

This 'Schottky defect' as it became known indicates that the crystal detector was actually an early variant of the Schottky diode.

Naturally this 'defect' works just as well today for AM broadcasts as it did back at the dawn of the radio age and it shouldn't be too difficult to find a suitable crystal, they occur quite commonly in nature. It would make an interesting diversion and an electronic trip back in time to build such a set which after all is the root of all modern day radio sets.

and B4 these allow the following functions to be selected on the radio:

S1 to PortB.0: scan, short press scans upwards longer press scans downwards.
S2 to PortB.3: loudspeaker –
S3 to PortB.4: loudspeaker +

The display shows the receive frequency, signal level and signal to noise ratio.

Software

The software to control the radio chip is written in BASIC. Listing 1 shows part of the software which takes care of initialising and chip set-up. After Start the SI4735 requires a reset pulse which is performed by DDRD.4 of the data direction register. This port pulls the reset pin momentarily low and then releases it. After reset the chip is ready for communication over the I²C bus. Its I²C address is 34.

The SI4735 is now initialized to receive either FM or AM signals by sending the corresponding commands. The Init_FM subroutine defines the analog stereo output and the external clock input. The ATmega88 generates the clock from its PWM output A from Timer 0. The clock has a frequency of 31.373 Hz and this information is provided in the RefClock subroutine so that the radio can calculate the divisor. Using FM-Tune-Freq the desired frequency is represented as a multiple of 10 KHz so

that 88.8 MHz is sent as 8880.

That is basically all that is required to get the receiver up and running. The output volume level can also be defined and this will be given a value in the range of 0 to 63.

The start frequency is given as 88.8 MHz. This can be changed to any other desired frequency. In operation it is necessary to use the internal 'station search' (Listing 2)

station it isn't necessary to change the frequency display but signal strength will vary so by periodically calling Fm_rsqs_status the most recent receive signal parameters are fetched and sent to the display.

Work in progress

Looking at the versatility of this chip it really would be difficult to make use of every one of its features in any single application. With a bit of imagination you could use this chip in radio designs and experiment with totally different user interfaces. How about a single-button concept using a pot or rotary encoder? Direct frequency input is possible as well as station presets. A timer controlled radio will make sure you don't miss any of your favorite programmes. The RDS capability of the SI4735

also allows the display of station identification, radio text information, time of day and much more provided that the necessary software is in place to decode the information.

It's remarkable that advances in technology at one time took all the thinking work out of radio set construction or at least made the process much less interesting. Now with the versatility of a device like the SI4735 we are faced with a whole different set of challenges and it's suddenly become interesting again.

(090740)



Figure 5. Status display on the LCD.

procedure to change the received station. A short press of pushbutton S1 will call Fm_seek_freq_up searching upwards for a station, while a long press calls Fm_seek_freq_down to search downwards.

The frequency of the new station is read by using Fm_tune_status. In addition there are other internal registers which store more information. Especially interesting is the signal strength (RSSI) and signal to noise ratio (SNR) of the received signal. These values are written to the display when the new station is found (Figure 5). Once on-

NEW

DISTANCE LEARNING COURSE

Programming Embedded PIC Microcontrollers

➔ using Assembly, C and Flowcode


In this course you will learn how to program an embedded microcontroller. We will start with the absolute basics and we will go into a lot of detail. You cannot learn about software without understanding the hardware so we will also take a close look at the components and schematics. At the end of the course you will be able to design your own embedded applications and write the appropriate software for it.

Special introductory price
for Elektor subscribers
\$70 DISCOUNT
www.elektor.com/distancelearning



Contents:

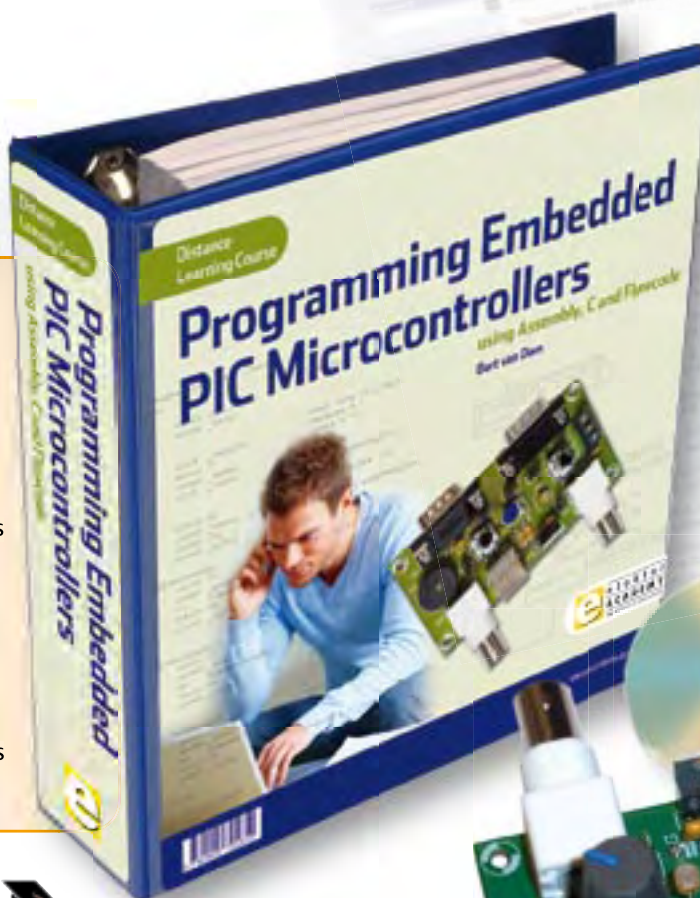- Background
- Digital Ports
- Serial Communication (RS232)
- Analog Signals
- Pulse Width Modulation
- Timers/Counters/Interrupts
- Memory
- LCD Display
- I²C Communication
- SPI Communication
- USB Communication
- Configuration (Fuses)
- Answers to the assignments
- Appendix



Your course package:

- Courseware Ring Binder (800 pages)
- CD-ROM including software and example files
- Application Board
- Support at Elektor Forum
- Elektor Certificate

Price: \$645.00

Please note: to be able to follow this course, E-blocks hardware is required which you may already have (in part). All relevant products are available individually but also as a set at a discounted price. Please check www.elektor.com/distancelearning for further information.




Further information and ordering at
www.elektor.com/distancelearning

TTL Bluetooth Dongle

Wireless data comms made easy

By Steffen Graf (Germany)

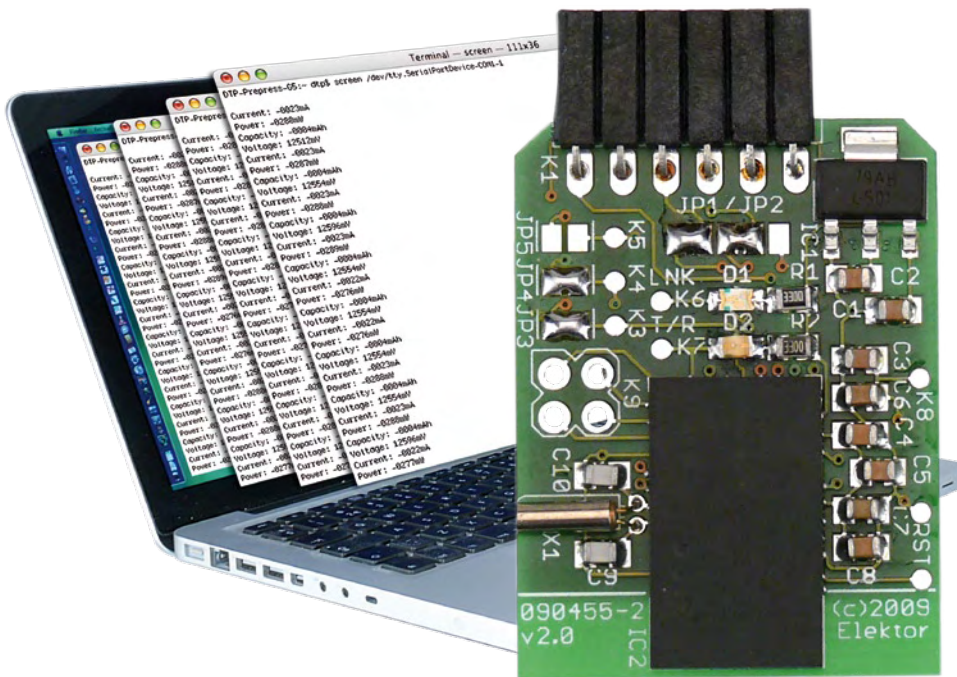Need to connect your circuit to a PC to transfer measurement values or data? How about wirelessly? If you think that would be way too complex, think again. The solution offered here is a Bluetooth device which from your circuit's point of view looks just like a UART with a PC (or other device) attached to the other end. It's as simple as plugging in a USB to TTL cable but without the wires!



that plugs into a free USB port and provides the PC with Bluetooth connectivity. The circuit here provides the same connectivity as a USB to TTL cable i.e. all the UART connections are available to connect to the microcontroller in the external circuit. In use it is only necessary to wait for the PC to recognize the Bluetooth module – and it's ready to go! Again on the PC side a terminal emulation program can be used (or some other PC software which can send and receive data from a COM port).

The Bluetooth chip used here is the LM9838 [2] from National Semiconductor. This SMD device is particularly small (it is thinner than the BTM-222 module used in 'Bluetooth with the ATM18' project described in the December 2009 edition of *Elektor*). A block diagram of the chip showing the UART interface is given in **Figure 1**. The RF transceiver and Bluetooth stack necessary for the (relatively complex) Bluetooth communication is integrated in the chip. Also included is an EEPROM to store configuration data.

The chip can of course be directly mounted (using hot air only) on the finished circuit PCB but a more flexible solution is to mount it on its own small PCB and bring out the UART connections and power supply to a 6-way connector compatible with the type of connector used for a standard TTL to USB cable. This allows the module to be used in place of the serial cable to give an instant Bluetooth RF communication link.

It is often the case that a designer needs to connect a circuit or some equipment to a PC to transfer data or measurement values. One of the simplest methods is to make use of the computer's serial port but fewer and fewer desktops and hardly any mobile PCs are equipped with an RS232 or parallel printer port these days. The favored port is now via the USB connector but from a hardware designers point of view this is not the simplest solution. There are not too many microcontrollers available with an integrated USB port so additional hardware is the minimum requirement. One solution is to use a specialist USB interface chip which can be driven from a UART in the external controller circuit; it then translates the TTL signal levels to USB data. Alternatively this hardware can be encapsulated into a cable to make a USB to TTL serial cable like the one described in *Elektor* (by FTDI and avail-

able from the *Elektor* shop as item number 080213-91 [1]). On the PC side this creates a virtual COM port through which the external circuit can be accessed. Now with a terminal emulation program running on the PC, bytes of information from the external microcontroller system can be displayed on the screen and commands can be sent to the external system from the PC keyboard. You may be using the latest computer and the most recent version of Windows but that's just the way it has been done for years!

Who needs cables anyway?

This project describes an alternative method using more up-to-date interface technology. Almost every mobile PC is now supplied with a built-in Bluetooth interface but even if yours is not equipped with one (or you prefer to use a desktop PC) then you can easily buy a Bluetooth stick for a few bucks

The PCB

For consistency we have used the same type of connector and pin assignments as were used in the adapter cable mentioned above. This means that existing *Elektor* projects such as the battery monitor [3] or the *Elektor* ATM18 Testboard (see **Figure 2**) can directly use this Bluetooth dongle and con-

Features

- SPP Protocol fully Integrated 'on chip' (other Bluetooth devices behave as if they are connected via a serial cable)
- No configuration necessary in slave mode, Plug & Play like a USB to TTL cable
- Module can be configured as master via the UART allowing two modules to communicate
- Communication up to 921600 Baud (configurable from 2400 to 921600 Baud using jumpers or software)
- 5 V supply uses an on-board voltage regulator
- Pin compatible with the USB to TTL adapter cable from FTDI
- Direct interface with microcontroller (3.3 V) possible
- UART including handshake signals
- 2 LEDs indicating Bluetooth link status and traffic
- Expansion with an external audio codec possible
- Low power mode using optional 32 kHz crystal

nect wirelessly to a PC without the need to write a single line of program code!

The small PCB contains the minimum number of external components necessary for the chip. There is a voltage regulator and a quartz crystal (see the circuit diagram in **Figure 3** and the PCB layout in **Figure 4**). The crystal (and its loading capacitors C9 and C10) are not strictly necessary and need only be fitted if you want to make use of the module's low-power mode. Pad 27 (32K+) must be connected to GND if the low power mode is not used. In this case C10 can be replaced by a 0 Ω resistor.

The module is configured using both solder bridges and software. Jumpers JP1 and JP2 allow easy swapping of the Rx/D and Tx/D lines to connector K1 without the need to modify the PCB.

A combination of jumpers fitted at JP3 to JP5 defines the serial communication speed. It can be set to either 9600, 115200, 921600 Baud or 'Read from NVS' (see Table). The 'Read from NVS' (Non-Volatile Storage) mode uses the value stored in EEPROM. This value is usually 9600 Baud.

Using the 'Simply Blue Commander' ^[4] software tool running on a PC allows you to configure the module from a PC via a UART interface (note, only 3.3 V supply allowed!). The baud rate can be set in the range from 2400 to 921600 Baud, other parameters such as parity, stop bits and flow control can also be programmed.

LEDs D1 and D2 indicate the units Bluetooth status; D1 is lit when the unit is not connected to another Bluetooth device and D2 flashes to indicate communication with another Bluetooth device otherwise it remains lit.

Provisions have been made on the PCB layout for the connection of an audio channel to the module. With the addition of an external audio codec this would allow the module to form the basis of a Bluetooth headset.

A bit more background

Communication with a PC is just one of the more basic applications of this Bluetooth dongle. With two modules it is possible to build a wireless link connecting two circuits. There is no doubt that Bluetooth is an increasingly popular interface found

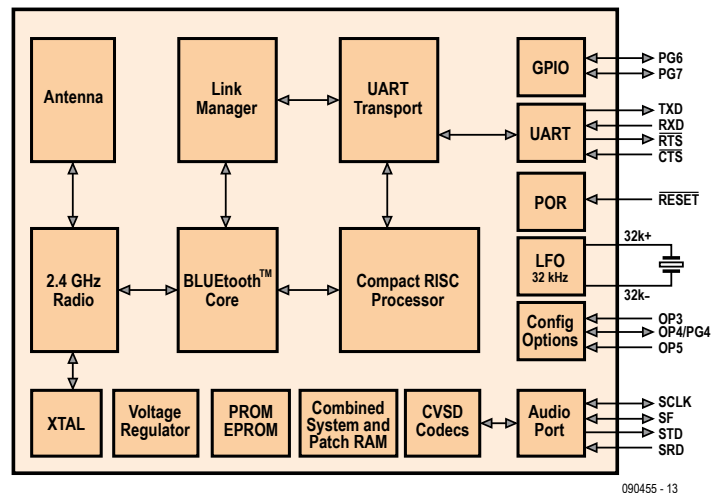


Figure 1. Block diagram of the Bluetooth chip (reproduced from the National Semiconductor data sheet [2]).



Figure 2. The connector used on Existing Elektor projects for connection of the USB to TTL cable from FTDI [1] will also plug into the Bluetooth-Dongle.



Figure 3. The dongle circuit diagram. Jumpers JP3 to JP5 define the communication baud rate.

Table 1. Baud rate selection

Baudrate	JP3	JP4	JP5
9600	Fitted	Open	Fitted
115200	Fitted	Fitted	Open
921600	Fitted	Fitted	Fitted
Read from NVS	Fitted	Open	Open

COMPONENT LIST

Resistors (all 0805)

R1,R2 = 330Ω (1%)
R3..R5 = 1kΩ (1%)

Capacitors (all 0805):

C1-C5 = 100nF
C6..C8 = 2μF2
C9,C10 = 22pF

Semiconductors

D1 = LED, blue, SMD
D2 = LED, red, SMD
IC1 = LMS8117-AMP3.3
IC2 = LMX9838SB

Miscellaneous

X1 = 32.768kHz quartz crystal (CL = 6pF, 20ppm)

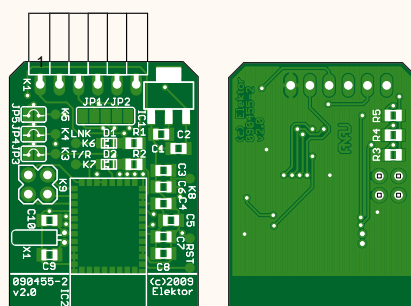


Figure 4. Component placement on the small PCB.

K1 = 6-pin SAL pinheader, 2.54mm pitch,
right angled
PCB, see www.elektor.com/090455

on mobile phones, PDAs and other mobile devices and it is necessary to invest some time studying the protocols if you intend to make full use of the communication possibilities. Next we will go on to explore just some of the more basic operations. Detailed information of Bluetooth ^[5,6] and the chip ^[2,7] can be found on the Internet.

Much like communications over Ethernet based networks Bluetooth also has many abstract layers to control the exchange of information. In the following description we only refer to the protocols and profiles implemented in the Bluetooth chip, there are a whole lot more described in the Bluetooth specification!

At the lowest physical layer Bluetooth uses radio channels in the 2.4 GHz ISM band to send and receive data. The use of fast frequency hopping reduces the effects of interference and error detection techniques make communication more robust. With this method of communication the stream of data is divided up into individual packets prior to transmission and then reassembled in the receiver in the correct order. This is taken care of by the so-called L2CAP (Logical Link Control and Adaptation Protocol). At another layer above the software takes care of simultaneous execution of applications and manages connections to other devices. At this level the GAP (Generic Access Profile), establishes links and governs which device has access to which service. At another level up are the SDAP (Service Discovery Application Profile) and SPP (Serial Port Profile). SDAP detects Bluetooth devices and can determine which protocol the device understands and establishes links. The Serial Port Profile or SPP is of particular interest in our application here, it uses the RF link to produce a virtual serial data cable between two Bluetooth devices with the usual UART signals at either end to control data flow. This serial link is relatively easy to configure and simple to use. The path does have a relatively high latency (in the region of a few milliseconds) but this should not cause too much of a problem in the majority of applications using digital data transfer.

Communication set up

From a user's point of view to establish a Bluetooth link one of the devices assumes a

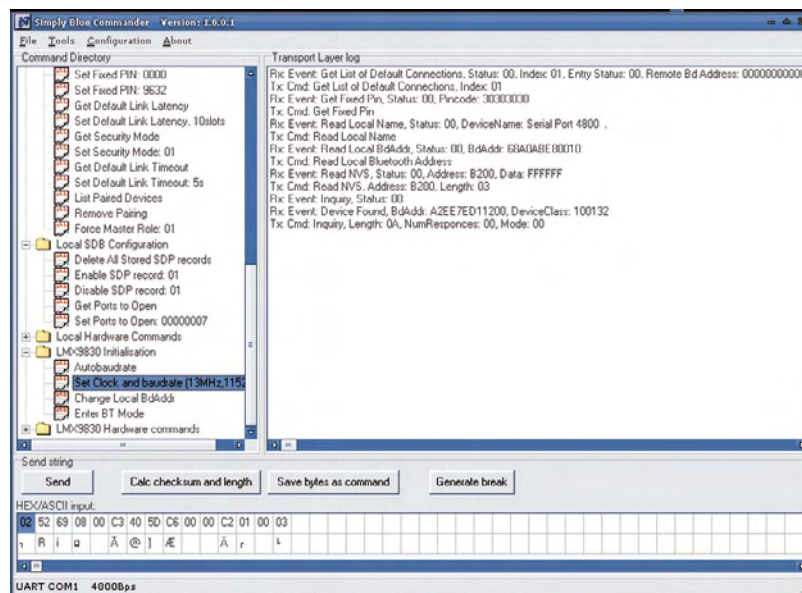


Figure 5. The PC tool 'Simply Blue Commander' allows request generation from its menu.

role as master and issues a 'request' message. For this to occur it is necessary to send the corresponding instruction (in hexadecimal) to the UART in the Bluetooth chip. An interpreter is integrated in the chip.

The other 'slave' device responds by sending a Bluetooth 'confirm'. When this is received by the master device it is converted into the corresponding hex code sequence and sent out from the master's UART.

Request (and confirm) messages always use the following (hexadecimal) format:

Start byte	02
Type ID	1 Byte
Opcode	1 Byte
Data Length	2 Bytes (Low byte first)
Checksum	1 Byte
Data	X Bytes
Stop byte	03

The Type ID can be 52 (Request), 43 (Confirm) or 69 (Indication) which denotes the transfer of additional information.

So the following sequence illustrates a typical communication exchange (opcodes and data bytes are shown in *italics*):

Devices in range receive inquiry request:
02,52,00,03,00,55,0A,00,00,03

A typical reply would be for example:
02,43,00,01,00,44,27,03
02,69,01,09,00,73,**B4,EE,7E,D1,12,00,10**,01,32,03

02,43,00,01,00,44,00,03

The sequence '**B4,EE,7E,D1,12,00**' shown in bold is the unique hardware address of the target Bluetooth device. This address is assigned by the device manufacturer much like the MAC address of a network adapter or network interface card.

Now the name of the target device can be requested:
02,52,02,06,00,5A,**B4,EE,7E,D1,12,00,03**

A typical reply would be:
02,43,02,12,00,57,00,**B4,EE,7E,D1,12,00,0A,54,65,73,74,44,65,76,69,63,65,03**
Which contains the Bluetooth address again and then the name of the device (5 4,65,73,74,44,65,76,69,63,65 = the ASCII hex codes for 'TestDevice')

Now using SDAP we can find out all the services available. First we must send an SDAP connection request:

02,52,32,06,00,8A,**B4,EE,7E,D1,12,00,03**

If the connection is successful the received reply is: 02,43,32,01,00,76,32,03

Next all the services can be interrogated or as shown here just the available SPP service:

02,52,35,02,00,89,01,11,03

A typical reply:
02,43,35,20,00,98,00,01,02,10,01,11,01,18,**42,6C,75,65,74,6F,6F,74,68,20,53,65,72,69,61,6C,20,50,6F,72,74,20,31,00,03**

Once again the profile's name is shown in bold:

42,6C,75,65,74,6F,6F,74,68,20,53,65,72,69,61,6C,20,50,6F,72,74,20,31 = Bluetooth Serial Port 1

Now it is established that the device can talk and understand 'SPP' a connection can be configured using SPP connection request:

02,52,0A,08,00,64,01,**B4,EE,7E,D1,12,00,01,03**

The correct PIN is now sent (default value '0000'):

02,52,75,08,00,D2,**B4,EE,7E,D1,12,00,04,30,30,30,30,03**

The Bluetooth address is included and also the sequence 30,30,30,30 = 0000 i.e. the PIN

Finally the UART is switched to 'transparent' mode:

02,52,11,01,00,64,01,03

The Bluetooth chip now stops interpreting the serial data as commands and just passes the data on 1:1.

(090455-l)

Internet Links

- [1] www.elektor.com/080213
- [2] www.national.com/ds/LM/LMX9838.pdf
- [3] www.elektor.com/080824
- [4] www.national.com/analog/wireless/lmx9838

- [5] <http://bluetooth.com/Bluetooth/Technology/Works>

- [6] www.elektor.com/992041

- [7] www.national.com/appinfo/cp3000/files/SBK/AN1699_LMX9838SWUG.pdf

- [8] www.elektor.com/090455

Parts Selection

The step from builder to designer is a large one, especially for hobbyists. I remember (in the days when dirt was new) collecting parts to copy something I saw in a magazine. I really enjoyed that, especially when I actually got it to function. But after a while, I wanted to create new things on my own... to come up with an idea that was new (to me at least) and make it work. And I think that there are a lot of Elektor readers who have a similar ambition (there are, *Ed.*).

Where's the Beef?

Designing is not just putting things together. Although you can learn a lot doing that. I recall taking a rescued 3" speaker and taping it to the end of a 3" diameter cardboard tube taken from an old roll of wrapping paper. I was surprised how much better the speaker sounded. So I started building strange and wonderful speaker enclosures from scrap wood and whatever speakers I could scrounge. I had absolutely no clue about what I was doing. I was just combining things, not designing.

I believe my first real design was an audio generator. It was a 555 timer followed with three 7490 decade counters/dividers. This generated four signals a decade apart in frequency (the 555 frequency and 1/10, 1/100 and 1/1000 frequencies). So by adjusting the 555 timer over just one decade, I had 5 decades of signals. I still have it and it still works.


In order to build this I had to select the parts. In this case, it was pretty simple. I needed a 555 timer and 3 decade counters. But I had to understand what I needed, in order to specify the parts. And I had to fit the design to match the parts. For example, I needed 5 volts for TTL. I could have used CMOS parts and been more flexible in power requirements. But I chose TTL because they would drive LEDs easier (of course I had blinking LEDs!).

Parts is Parts

There is a perpetual money shortage for hobbyists. This means that there is an instinctive desire to re-use old parts and force-fit parts on hand into a design. Unfortunately, this results in projects that perform poorly or not at all. And in many cases, it's not the idea that's bad, it's that the parts don't work well together.

For example, suppose you want to amplify a signal from a microphone before it goes to the main amplifier. You take your trusty LM741 op-amp, wire it up for a gain of 10, apply +5 volts and connect it to the 600 ohm audio amplifier input. There's no output from the 741. Why? Theoretically, the 741 might operate from only +5 volts but it's usually run at ± 10 volts, minimum. But the real problem is that the 741 has really poor output drive. It loses 5 volts from each power rail when driving 2 kohms. So if you had ± 10 volts to the part, the output would be a maximum of ± 5 volts into 2 k Ω . Driving 600 ohms with only +5 volts is an exercise in futility.

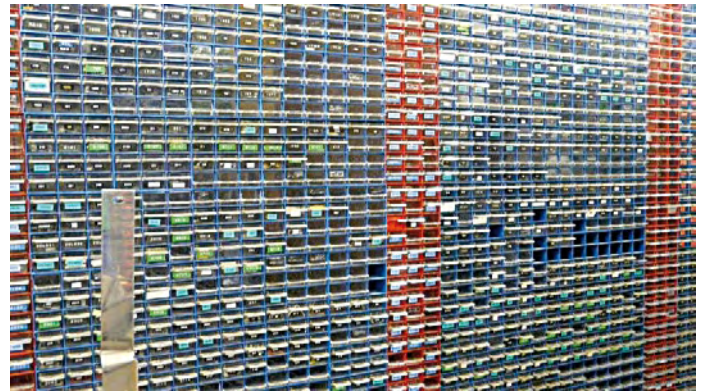Another example. You have a 40 MHz oscillator that you want to divide down to 20 MHz. You hook it up to a 74LS74 flip-flop configured as a divide-by-2. You know this divider circuit works because you've used it before and seen it published. But it doesn't want to do anything. This is because the 74LS74 can only run with an input less than 25 MHz.



Penny-wise, Pound-foolish

Basically, hobbyists get into trouble by trying too hard to save a few dollars in parts costs. One way of getting a handle on expenses is to set a price for your own labor. If your time is worth only \$5.00 an hour, it isn't cost effective to spend four hours trying to force-fit a part, when you can order a different part for \$3.00 and \$5.00 shipping. The critical assumption here is that you have to understand exactly what part you need to succeed. This means you have to be able to read the part specifications that are provided by the manufacturer.

Nowadays, getting this information is trivial. Most parts suppliers have direct links to the data-sheets on the web. Of course, you have to know what features are important to your design. Generally, these are pretty self evident... power supply voltage, frequency response, distortion, input resistance, etc. should be things you know. Other specifications like PSRR (Power Supply Rejection Ratio) are usually defined someplace by the manufacturer. Originally, these were in the front of the databook. But databooks (hard-copy and electronic) are becoming things of the past (unfortunately). It's useful to look these terms up so you will have some understanding of them (when design something that needs a high PSRR).

Naturally, there is satisfaction in resurrecting old parts. And sometimes it's entertaining to just assemble things and tinker. But personally, I much prefer to have something that works and works well. So, if you want to be serious about making things that perform, then you will have to choose parts rather than re-use parts.

The Proof of the Pudding

In order to choose the proper part you have to know what parts are available. So, subscribe to free newsletters and learn what different manufacturers are selling. Did you know that National Semiconductor has a series of audio op-amps with less than 0.00003% distortion? The LME49710 costs about \$2.65 each. Or how about Analog Devices AD5930? It's a completely programmable, virtually self-contained, sweep generator that creates low distortion, 2-phase sine waves in 3 Hz steps to 25 MHz. And it has a lot of extra features, including a fixed-frequency option. It costs under \$14 each. (A project is in the works.)

Yes, it's fun to design your own complicated circuit and it's satisfying to make it work and you can learn a lot. But if your goal is to get the most out of your time and money, then choosing the proper part for your project becomes important. While it's a poor workman that blames his tools, a good workman uses the proper tool to begin with.

(091084)

“Elektor? Prescribed reading for our R&D staff because that’s where we need professional guidance for microcontroller technology.”

– Frank Hawkes, 39, development engineer –



**11 Issues
including the
summer double
issue for just
\$39.95***

Electronics at all the right levels

**Secure a head start in electronics
with a subscription!**

Advantages to subscribers

- Cheaper than 11 issues from the newsstand:
Save 57% off the cover price of \$92.45
- With every issue subscribers get up to **40% discount** on selected Elektor products
- No lines, travelling, parking fees or ‘sold out’;
Elektor is mailed to you every month
- Always up to date – read your copy before everyone else

* Offer available in US and Canada only. Canada add \$11 per year.

www.elektor.com/usa • Phone 860-875-2199

Or use the subscription order form near the end of the magazine.

elektor
electronics worldwide

Hexadoku

Puzzle with an electronics touch

Feel like solving a puzzle again? Here's another Hexadoku that hopefully allows you to escape from those daily tribulations for a while. Send the hexadecimal numbers in the grey boxes to us and enter the prize draw for a fine set of Elektor vouchers. Have fun!

The instructions for this puzzle are straightforward. In the diagram composed of 16×16 boxes, enter numbers such that **all** hexadecimal numbers 0 through F (that's 0-9 and A-F) occur once only in each row, once in each column and in each of the 4×4 boxes (marked by the thicker black lines). A number of clues are given in the puzzle

and these determine the start situation.

All correct entries received for each month's puzzle go into a draw for a main prize and three lesser prizes. All you need to do is send us the numbers in the grey boxes. The puzzle is also available as a **free download** from www.elektor.com.

Solve Hexadoku and win!

Correct solutions received from the entire Elektor readership (all editions worldwide) automatically enter a prize draw for one Elektor Shop voucher worth US\$ 150.00 and three Elektor Shop vouchers worth US\$ 55.00 each.

We believe these prizes should encourage all Elektor USA & Canada readers to participate!

Participate!

Please send your solution (the numbers in the grey boxes) by email to hexadoku@elektor.com – Subject: **hexadoku 02-2010** (please copy exactly). Include with your solution: full name and street address.

Alternatively, by fax or post to:

Elektor Hexadoku, 4 Park Street, Vernon CT 06066, USA.

Fax 860-871-0411.

The closing date is March 1, 2010.

Prize winners

The solution of the December 2009 Hexadoku is: **F1482**.

The E-blocks Starter Kit Professional goes to: Mark Lucas (UK).


An Elektor SHOP voucher goes to: Wolfgang Beckmann (Germany), Keijo Kiirikki (Finland), K. D. Reinartz (Germany).

Congratulations everybody!

1			C		3				5		7				F
	7	3		C	E	4			1	6	A		5	2	
E			5		F		G	7		2		1			9
		B		1							F		G		
		8											E		
4		9	1	8		E			7		2	G	3		6
	E	D	F	3		C			8		G	4	1	B	
A	6	7			4		F	1		3			9	C	D
8	F	A			7		6	3		9			B	D	C
	B	5	6	9		3			2		7	F	4	1	
7		1	3	F		D			6		B	9	2		E
		C											7		
		F		E							C		8		
9			7		A		C	2		1		B			5
	A	2		6	5	8			9	G	E		F	7	
C			G		9					F		E			2

1	4	8	9	C	3	D	A	2	E	5	7	B	0	6	F
2	B	D	C	6	5	F	7	9	0	A	8	4	E	3	1
0	6	F	E	9	1	8	2	D	4	B	3	5	C	7	A
5	3	7	A	0	E	4	B	F	6	1	C	D	9	2	8
6	7	2	B	1	D	A	C	8	9	F	4	3	5	0	E
A	5	E	D	4	6	9	0	B	7	3	1	C	F	8	2
C	F	1	4	8	2	3	5	A	D	0	E	7	B	9	6
9	8	3	0	E	B	7	F	C	5	2	6	1	A	4	D
3	A	B	6	F	9	5	D	4	1	C	0	2	8	E	7
F	2	C	7	3	0	E	6	5	8	D	A	9	4	1	B
E	1	9	5	A	8	2	4	3	B	7	F	0	6	D	C
D	0	4	8	B	7	C	1	6	2	E	9	A	3	F	5
4	D	6	1	5	F	B	9	0	C	8	2	E	7	A	3
B	9	5	3	7	A	6	E	1	F	4	D	8	2	C	0
8	E	0	F	2	C	1	3	7	A	9	B	6	D	5	4
7	C	A	2	D	4	0	8	E	3	6	5	F	1	B	9

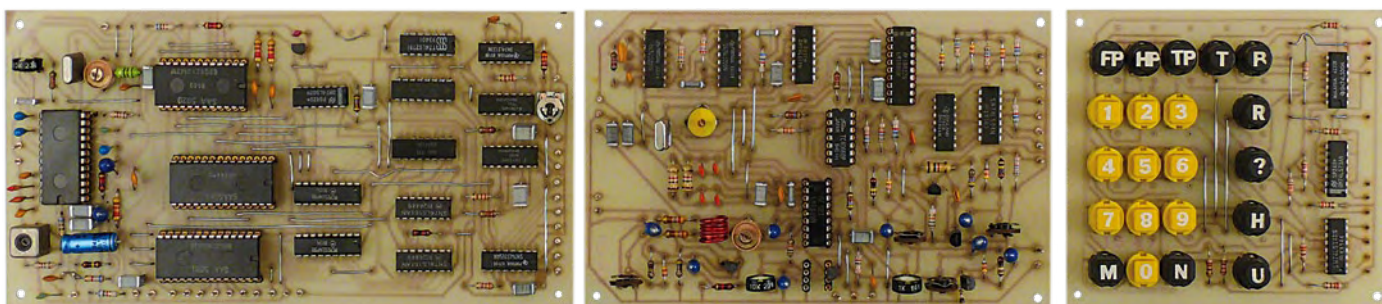Notice. The competition is not open to employees of Elektor International Media, its business partners or associated publishing houses.



Elektor Teletext Decoder (1981)

By Jan Buiting (Elektor UK/US Editorial)

Some of you may be surprised to read this but I don't have to do an awful lot to catch items for presenting on the Retronics page(s) of Elektor — the vintage stuff usually comes to me after a phone call or an email best typified as “lady-of-the-house sez it must go, or else ...”. Recently I've also heard these: “Our new management feels the equipment is surplus to their requirements...”; “... my attic's starting to creak” and “... such a pity it goes to waste”. To which I say *keep 'm coming* as we have lost most prototypes of Elektor projects published over the past 40 years or so.

Teletext, an information service based on text and simple graphics all carried via analog TV broadcasts, did take a few years to develop out and mature into a standard (with lots of ifs, buts and hiccups in different countries). It started in 1970 when creative BBC and IBA engineers agreed that the 25 picture lines in the field blanking period of a TV signal were suitable for conveying ‘information’ instead of just being invisible to viewers at home, as well as mainly black on the oscilloscope. They succeeded in filling this vacant area with up to 15 characters per line to convey “internal program information”. When in 1972 the BBC's experimental *Teledata* service was launched the capacity had risen to an impressive 32 characters per line. Later that year a conflict of standards occurred when the IBA launched its very own *Oracle* system, to which the BBC responded by renaming its version to *Ceefax* (‘see facts’). After two years of polite rivalry and customer frustration up and down the country, the IBA, BBC and BREMA were marshaled by the GPO into agreeing on a standard for teletext, essentially combining the best of *Oracle* and *Ceefax* while adding color

and simple graphics (no fancy stuff — not even Pacman level). Again two years later the ‘tests’ were ended and the definitive standard laid down. The system was quick to spread across Europe, viewers calling up pages by the 100 K's every day showing weather information, stock exchange lists, airport arrivals/departures and traffic announcements.

Wherever's a dearth there's also an opportunity. I've no evidence of affordable TVs with built-in teletext functionality by around 1980, and the few decoders on the market at the time required major surgery to the TV set. Elektor in 1981 filled the gap by publishing a DIY TT decoder that could be connected between the aerial and the TV set — so no TV in pieces on the carpet!

The Elektor system comprised three circuit boards. The first, described in the October 1981 issue along with a general introduction to the teletext system, contains the decoder using state-of-the-art LSI chips with fine names like VIP (SAA5030), TAC (SAA5041), TIC (SAA5020) and TROM (SAA5051) — thanks for those great acronyms, people at Philips/Signetics! As with most LSI, you kind of glue it all together and follow the datasheet for the most part. I personally remember those SAA50xx ICs were horribly expensive and difficult to get.

The control board described in the November 1981 issue was mostly an interface between the user keyboard and the decoder proper. It contained a bunch of 74LS TTL ICs like shift registers, timers and flip-flops. Rather unexpectedly, the article series seemed to veer off course by suggesting to feed the video output of the decoder to a suitable point in the TV set. Several add-on circuits were shown and hints were given to isolate the TV set from the AC power lines. Fortunately, in December 1981 the original

promise of ‘no tinkering with the TV set’ came true with the description of the video control board. This contained ICs like the LM1889N VHF modulator and the LM1886N RGB decoder, both of which achieved stardom later as they were cheap and an easy way of getting through to the TV screen without opening the family's prize possession. The ‘aerial way’, finally, came at a great expense in the form of yet another board, this time for the ‘teletext receiver’, comprising a commercial VHF/UHF TV tuner module and a TDA2541 IF amp/demodulator chip. The obvious missing link to the project, a three-voltage power supply, was published in February 1982.

The complete Teletext decoder was a mammoth project covering about 25 densely filled B&W pages in Elektor and it must have cost a small fortune to construct exactly as detailed in the magazine. The articles had the complete PCB artwork printed at full scale for everyone to etch their single-sided circuit boards at home. Like my friend Eric Post who kindly supplied a fully assembled decoder, neatly assembled, wired and installed in a Teko box (not pictured here). The ETDD was a fine example of Elektor and its keen readers being ahead of the market, as TV sets with internal teletext were rare and/or expensive at the time. Hence a fully a working teletext decoder was sure to impress friends and neighbors with important information like snow levels on the Chamonix skiing slopes or the zloty exchange rate!

Today, teletext is in the final phase of being killed off by the Internet and digital TV, with many providers folding after about 30 years — starting, ironically, in the UK. It's proof that Latin ‘tele’ means ‘far’ in terms of distance, not time.

(090762)

Retronics is a monthly column covering vintage electronics including legendary Elektor designs. Contributions, suggestions and requests are welcomed; please send an email to editor@elektor.com

ELEKTOR SHOWCASE

To book your showcase space contact Strategic Media Marketing Inc.

Tel. 1-978-281-7708

Fax 1-978-281-7706

Email ElektorUSA@smmarketing.us

HAMEG® Instruments

A Rohde & Schwarz Company

- ✓ Oscilloscopes
- ✓ Power Supplies
- ✓ Radio Frequency Measuring Instruments
- ✓ Programmable Measuring Instruments

Great Value in
Test & Measurement

www.hameg.com

MICROENGINEERING LABS, INC.

www.melabs.com

*PICBASIC PRO™ Compiler
for PIC® MCUs*

Development tools for
PIC® microcontrollers,
including Software, Device
Programmers, Prototyping
Boards, Experimenter
Boards, Serial Displays, and Books.



MICROENGINEERING LABS, INC.

www.melabs.com

Serial Displays

Software and hardware
products for embedded
development, including
BASIC Compilers for
PIC® MCUs, Experimenter Boards, Device
Programmers, Books, and other resources.



Pololu

Robotics & Electronics

Electronics
Controllers & sensors
Cables & batteries
Discrete components
Jrk 21v3 USB Motor Controller
with Feedback, item #1392: **\$44.95**

Mechanical parts
Wheels & casters
Motors & servos
Robot chassis
RP5 Tracked Chassis Yellow
item #1059: **\$49.95**

www.pololu.com

Save 10%
on motor controllers
with coupon code
ELEKTORMC23

7 in 1 Scope !

CircuitGear CGR-101™ is a
unique new, low-cost PC-based
instrument which provides the
features of seven devices in
one USB-powered compact box:
2-ch 10-bit 20MS/sec 2MHz
oscilloscope, 2-ch spectrum-
analyzer, 3MHz 8-bit arbitrary-waveform/standard-
function generator with 8 digital I/O lines. It also
functions as a Network Analyzer, a Noise Generator
and a PWM Output source. What's more – its
open-source software runs with Windows, Linux
and Mac OS's!

Only \$180

Saelig
UNIQUE ELECTRONICS

1-888-7SAELIG
info@saelig.com
www.saelig.com

SchmartBOARD™
www.schmartboard.com

Earn Cash and Free Products

bob
basic overlay board for NTSC & PAL

Automatic text scroll & crawl · 'TTL-232' & SPI control ports
Any size for custom fonts · Vector & bitmap graphics

DECADE ENGINEERING
www.decadenet.com

AVIT RESEARCH

www.avitresearch.co.uk

USB has never been so simple...
with our USB to Microcontroller Interface cable.
Appears just like a serial port to both PC and
Microcontroller, for really easy USB connection to
your projects, or replacement of existing RS232
interfaces.



See our webpage for more
details.

BLACK ROBOTICS

www.blackrobotics.com

Robot platforms and brains for
research, hobby and education.



- Make your robot talk!
- TalkBotBrain is open-source
- Free robot speech software
- Robot humanisation technology
- Mandibot Gripper Robot

ByVac

www.byvac.com

- PIC32 With BASIC
- ARM With Forth
- USB to I2C
- Serial Devices
- VT100 LCD Displays



DECIBIT CO.LTD.

www.decibit.com

- Development Kit 2.4 GHz
- Transceiver nRF24L01
- AVR MCU ATmega168



www.elektor.com

products and services directory

SHOWCASE YOUR COMPANY HERE

Elektor Electronics has a feature to help customers promote their business, Showcase - a permanent feature of the magazine where you will be able to showcase your products and services.

- For just \$385.00 + VAT (\$35.00 per issue for eleven issues) Elektor will publish your company name, website address and a 30-word description
- For \$550.00 + VAT for the year (\$50.00 per issue for eleven issues) we will publish the above plus run a 3cm deep full colour

image - e.g. a product shot, a screen shot from your site, a company logo - your choice

Places are limited and spaces will go on a strictly first come, first served basis. So-please fax back your order today!

I wish to promote my company, please book my space:

- Text insertion only for \$385.00 + VAT
- Text and photo for \$550.00 + VAT

NAME: ORGANISATION:

JOB TITLE:

ADDRESS:

..... TEL:

PLEASE COMPLETE COUPON BELOW AND FAX BACK TO 1-978-281-7706

COMPANY NAME

WEB ADDRESS

30-WORD DESCRIPTION

.....

.....

.....

.....

ElektorWheelie




Elektor's DIY self-balancing vehicle

Everyone agrees that the internal combustion engine is coming to the end of its life cycle. However, you don't need to go to the expense of a Prius or Tesla to experience the future of transportation devices. If you would prefer something more personal (and don't mind turning a few heads), why not build the astonishing ElektorWheelie?

First take two electric motors, two rechargeable batteries and two sensors, then add two micro-controllers, and the ElektorWheelie is ready to transport you in style to your destination.



Demo video on
www.elektor.com/wheelie

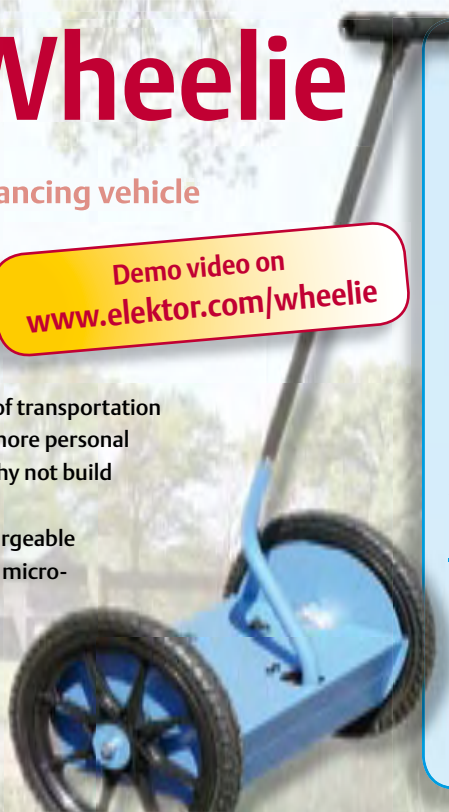

Characteristics

- Two 500 W DC drive motors
- Two 12 V lead-acid AGM batteries, 9 Ah
- Two sixteen-inch wheels with pneumatic tyres
- H-bridge PWM motor control up to 25 A
- Automatic power off on dismount
- Maximum speed approx. 11 mph (18 km/h)
- Range approx. 5 miles (8 km)
- Weight approx. 35 kg

The kit comprises two 500-watt DC drive motors, two 12-V lead-acid AGM batteries, two 16-inch ABS wheels, casing, control lever and assembled and tested control board with sensor board fitted on top.

Art.# 090248-71 • \$2275.00*

* Prices include tax, exclude shipping and handling.

Elektor US
4 Park Street
Vernon CT 06066
USA
Phone: 860-875-2199
Fax: 860-871-0411
E-mail: sales@elektor.com

Further information and ordering at www.elektor.com/wheelie

Going Strong

A world of electronics
from a single shop!



Specially designed for
electronics enthusiasts!
www.elektor.com/organizer

Complete with a free pen and SMD-tool

Elektor Personal Organizer 2010

Do you already have a diary for the coming year? If you don't, you can end your search now. We have exactly what you need: a diary specially designed for electronics enthusiasts. The Elektor Personal Organizer 2010 makes planning your appointments a real pleasure, and you always have ready access to have handy information that everyone who works with electronics needs to know. In addition to the usual features such as an appointments calendar, address book and notes pages, this organizer has around 40 pages packed with useful information for you as an electronics specialist, both professionally and in your leisure time. For example, there is an extensive collection of formulas and tables for calculating current and voltage, component descriptions, physical constants, connector pin assignments, and much more. This organizer also includes information on international trade fairs related to electronics and computer technology.

ISBN 978-90-5381-247-1 • \$40.20



Circuit design and programming

Complete practical measurement systems using a PC

This book covers both hardware and software aspects of designing typical embedded systems based on personal computers running the Windows operating system. It's use of modern techniques in detailed, numerous examples has been designed to show clearly how straightforward it can be to create the interfaces between digital and analog electronics, programming and Web-design. With an emphasis on learning by doing, readers are encouraged by examples to program with ease; the book provides clear guidelines as to the appropriate programming techniques "on the fly".

292 pages • ISBN 978-0-905705-79-8 • \$46.00




Learn more about C# programming and .NET

C# 2008 and .NET programming

This book is aimed at Engineers and Scientists who want to learn about the .NET environment and C# programming or who have an interest in interfacing hardware to a PC. The book covers the Visual Studio 2008 development environment, the .NET framework and C# programming language from data types and program flow to more advanced concepts including object oriented programming.

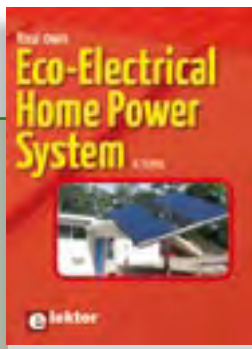240 pages • ISBN 978-0-905705-81-1 • \$47.60



Home electric power

Your own Eco-Electrical Home Power System

This book provides the semi-technical, power-conscious homeowner a place to begin in the quest for home electric power. Both the essential principles and detailed information on how to build or maintain a home electric system off the utility grid are presented in an easy-going style. This booklet will help you to safeguard or develop your own home electricity supply. It contains step-by-step calculations, practical details, examples, electric system problems with remedies and much more.

96 pages • ISBN 978-0-905705-82-8 • \$26.70




New!

Several case studies included

PIC Cookbook for Virtual Instrumentation

The software simulation of gauges, control-knobs, meters and indicators which behave just like real hardware components on a PC's screen is known as virtual instrumentation. In this book, the Delphi program is used to create these mimics and PIC based external sensors are connected via a USB/RS232 converter communication link to a PC. Case studies of virtual instruments are detailed including a compass, an oscilloscope, a digital and analogue thermometer and virtual displays for cars and aircraft.

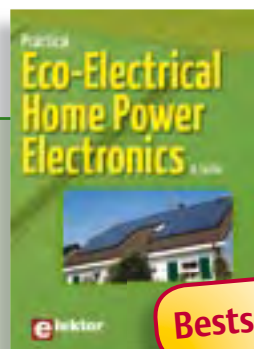264 pages • ISBN 978-0-905705-84-2 • \$47.60



Bestseller!

Look into the electronics of eco-power

Practical Eco-Electrical Home Power Electronics

This book is a sequel to *Your own Eco-Electrical Home Power System* and goes deeper into the electronics of photovoltaic and thermal solar technologies, wind power conversion, inverter circuits, and loads such as electronic lighting. Power electronics circuit theory is presented while analyzing commercial circuits, including little-known converters and subtleties such as snubbers and leakage inductance. The book also offers in-depth coverage of power system strategizing for optimal efficiency and utility, including a 170 V DC bus, commercial solar charger design with detailed circuit explanations, wind generator electric machine electromechanical theory, wind converter design requirements and the series-L zero-current-switching converter and power supplies found inside loads connected to home power systems and their potential problems and consequences for inverters.

192 pages • ISBN 978-0-905705-83-5 • \$40.20

More information on the Elektor Website:

www.elektor.com

Elektor US

4 Park Street

Vernon CT 06066

USA

Phone: 860-875-2199

Fax: 860-871-0411

E-mail: sales@elektor.com

elektor




See the light on Solid State Lighting

DVD LED Toolbox

This DVD-ROM contains carefully-sorted comprehensive technical documentation about and around LEDs. For standard models, and for a selection of LED modules, this Toolbox gathers together data sheets from all the manufacturers, application notes, design guides, white papers and so on. It offers several hundred drivers for powering and controlling LEDs in different configurations, along with ready-to-use modules (power supply units, DMX controllers, dimmers, etc.). In addition to optical systems, light detectors, hardware, etc., this DVD also addresses the main shortcoming of power LEDs: heating. Of course, this DVD contains several Elektor articles (more than 100) on the subject of LEDs.

ISBN 978-90-5381-245-7 • \$46.00

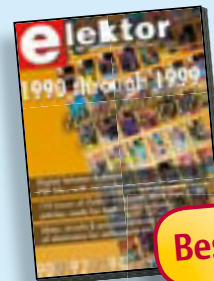

Bestseller!

110 issues, more than 2,100 articles

DVD Elektor 1990 through 1999

This DVD-ROM contains the full range of 1990-1999 volumes (all 110 issues) of Elektor Electronics magazine (PDF). The more than 2,100 separate articles have been classified chronologically by their dates of publication (month/year), but are also listed alphabetically by topic. A comprehensive index enables you to search the entire DVD. The DVD also contains (free of charge) the entire 'The Elektor Datasheet Collection 1...5' CD-ROM series, with the original full datasheets of semiconductors, memory ICs, microcontrollers, and much more.

ISBN 978-0-905705-76-7 • \$111.30



Modern technology for everyone

FPGA Course

FPGAs have established a firm position in the modern electronics designer's toolkit. Until recently, these 'super components' were practically reserved for specialists in high-tech companies. The nine lessons on this courseware CD-ROM are a step by step guide to the world of Field Programmable Gate Array technology. Subjects covered include not just digital logic and bus systems but also building an FPGA webserver, a 4-channel multimeter and a USB controller. The CD also contains PCB layout files in pdf format, a Quartus manual, project software and various supplementary instructions.

ISBN 978-90-5381-225-9 • \$23.40




Completely updated

Elektor's Components Database 5

The program package consists of eight databanks covering ICs, germanium and silicon transistors, FETs, diodes, thyristors, triacs and optocouplers. A further eleven applications cover the calculation of, for example, LED series droppers, zener diode series resistors, voltage regulators and AMVs. A colour band decoder is included for determining resistor and inductor values. ECD 5 gives instant access to data on more than 69,000 components. All databank applications are fully interactive, allowing the user to add, edit and complete component data. This CD-ROM is a must-have for all electronics enthusiasts.

ISBN 978-90-5381-159-7 • \$40.20

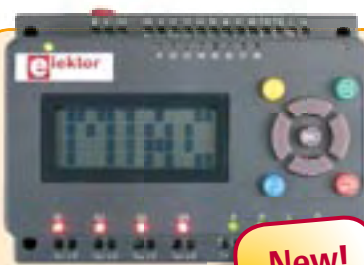

New!

MIAC for Home Automation

(January 2010)

A MIAC is an industrial programmable logic controller (PLC) that can be used in a wide variety of electronic systems. Internally it has a powerful 18F4455 PIC microcontroller which is connected directly to a USB port. As a result it can be easily programmed using either Flowcode, C or assembly. The article in Elektor's January 2010 issue shows how to implement a simple home automation system with an alarm by using three MIACs.

Populated PCB in enclosure

Art.# 090278-91 • \$248.40




Bestseller!

Preselector for Elektor SDR

Elektor's Software Defined Radio (SDR) is deservedly popular. The performance of a receiver depends to a large extent on its input filters. A selective input circuit improves antenna matching and immunity to interference from other strong signals. This preselector allows the use of up to four filters, tuned under software control using varicap diodes. A tuned loop antenna is also described that lets you use our SDR without an outdoor antenna.

Kit of parts, contains partly populated board, coil formers, ferrite rod with coils

Art.# 090615-71 • \$75.90

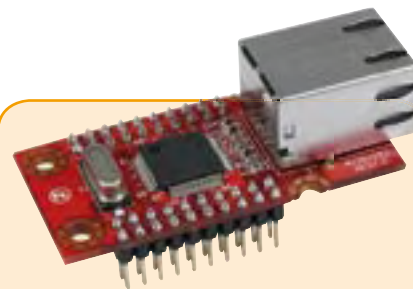

R32C Web Server

The R32C microcontroller goes Internet! A small add-on module for the application board from our September 2009 issue combines a TCP/IP chip plus Ethernet interface, a network connection with built-in transformer and status LEDs. This handy combination makes it child's play to implement a web server and many other Internet applications without getting involved in complexities such as TCP/IP protocols. Free downloads of an Open Source driver, a short web server program and other sample software complete this attractive proposition.

PCB, populated and tested WIZ812MJ module with W5100 chip

Art.# 090607-91 • \$29.10



OBD2 Analyser NG

The compact OBD2 Analyzer in the June 2007 issue was an enormous success — not surprising for an affordable handheld on-board diagnostics device with automatic protocol recognition and error codes explained in plain language. Now enhanced with a graphical display, Cortex M3 processor and an Open Source user interface, the next generation of Elektor's standalone analyser sets new standards for a DIY OBD2 project. The key advantage of the OBD2 Analyser NG is that it's self-contained and can plug into any OBD diagnostic port.

Kit of parts including DXM Module, PCB SMD-prefitted, case, mounting materials and cable

Art.# 090451-71 • \$135.50

February 2010 (No. 14)

\$

+ + + Product Shortlist February: See www.elektor.com + + +

January 2010 (No. 13)

USB Magic Eye

090788-1 Printed circuit board 16.00

090788-41 ...ATtiny2313-20PU, programmed 16.00

MIAC for Home Automation

090278-91 ...Populated PCB in enclosure 248.40

Dimmer with a Micro

090315-41 ...PIC12F629A, programmed 12.30

December 2009 (No. 12)

Preselector for Elektor SDR

090615-71 ...Kit of parts, contains partly populated board,
coil formers, ferrite rod with coils 75.90

Top-of-the-Bill Lights Sequencer

090125-1 PCB, bare (master module) 17.50

090125-2 PCB, bare (lamp module) 3.80

090125-41 ...Controller (PIC18F2550)
for main PCB, programmed 23.40090125-42 ...Controller (PIC12F508-I/SN)
for lamp unit, programmed 3.80

The Vikings Are Coming!

080948-71 ...Kit of parts: bare PCB and
bluetooth module BTM222 38.30

Minimalistic Time Switch

090823-41 ...PIC12F683-I/SN, programmed 10.50

November 2009 (No. 11)

Solder Station 'Plus'

090022-41 ...PIC18F4520, programmed 18.60

AVR-Max Chess Computer

081101-1 Printed circuit board 20.90

081101-41 ...Programmed controller ATmega88 18.60

081101-71 ...Kit of parts incl. PCB,
programmed controller and components 48.30

R32C Web Server

080082-71 ...Application Board with SMD parts prefitted,
plus all other components 200.90080928-91 ...R32C Starter Kit: processor board populated and tested,
Toolchain on CD 43.60090607-91 ...PCB, populated and tested WIZ812MJ module
with W5100 chip 29.10

October 2009 (No. 10)

Pocket Preamp

080278-71 ...Kit of parts 104.90

Digital Barometric Altimeter

080444-41 ...PIC18F2423, programmed 24.20

September 2009 (No. 9)

R32C Application Board

080082-71 ...Kit of parts Application Board with SMD parts prefitted,
plus all other components 200.90080928-91 ...R32C Starterkit: Processor board populated and tested,
Toolchain on CD 43.60

OBD Analyser NG

090451-71 ...Kit of parts including DXM Module, PCB SMD-prefitted,
case, mounting materials and cable 135.50

Battery Monitor

030451-72 ...LC display 17.80

080824-1 Printed circuit board 20.90

080824-41 ...Programmed controller LPC2103 26.70

Bestsellers

Books

1 ➡ **Practical
Eco-Electrical Home Power Electronics**
ISBN 978-0-905705-83-5 \$40.202 ➡ **Your own
Eco-Electrical Home Power System**
ISBN 978-0-905705-82-8 \$26.703 ⬆ **PIC Cookbook for Virtual Instrumentation**
ISBN 978-0-905705-84-2 \$47.604 ➡ **C# 2008 and .NET programming**
ISBN 978-0-905705-81-1 \$47.605 ➡ **Elektor Personal Organizer 2010**
ISBN 978-90-5381-247-1 \$40.20

CD/DVD-ROMs

1 ➡ **DVD Elektor 1990 through 1999**
ISBN 978-0-905705-76-7\$111.302 ➡ **DVD LED Toolbox**
ISBN 978-90-5381-245-7 \$46.003 ➡ **ECD 5**
ISBN 978-90-5381-159-7 \$40.204 ➡ **USB Toolbox**
ISBN 978-90-5381-212-9 \$32.105 ⬆ **FPGA Course**
ISBN 978-90-5381-225-9 \$23.40


Kits & Modules

1 ⬆ **Preselector for Elektor SDR**
Art.# 090615-71 \$75.902 ➡ **R32C Webserver**
Art. # 080082-71 \$29.103 ➡ **R32C/111 Starterkit**
Art. # 080928-91 \$43.604 ➡ **R32C Application Board**
Art. # 080082-71\$200.905 ➡ **OBD2 Analyser NG**
Art. # 090451-71\$135.50

Order quickly and securely through
www.elektor.com/shop
 or use the Order Form near the end
 of the magazine!



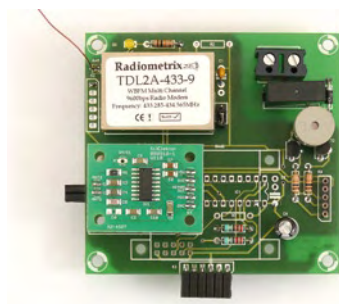Elektor US
 4 Park Street
 Vernon CT 06066
 USA
 Phone: 860-875-2199
 Fax: 860-871-0411
 E-mail: sales@elektor.com




ATM18 VisiOLED

This doorbell has a few features seen in top of the range Miami condos only: visitors have their RFID card scanned at the entrance and the house owner sees a photo of the visitor on an OLED display. A button push opens the door. This ambitious project employs the now famous Elektor ATM18 microcontroller board (from April 2008) and the associated RFID reader (June 2009). The free software is open to extension and expansion!



Three-channel DMX512-A Receiver

The DMX512-A system is used in many of today's lighting systems installed in theatres and concert halls. The same is also increasingly applied for outside lighting of large buildings. In this project a DMX-512 lights control is realized with the aid of a Texas Instruments MSP430 microcontroller. It handles the DMC communication as well as controlling three LED power drivers using pulsewidth communication. A DIP switch allows the DMX address to be set.

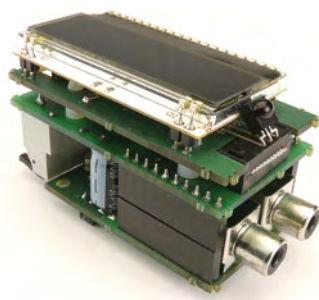

Mini Class D Amplifier

Although switching audio power amplifiers are now well established, home constructors often find themselves restricted to simple circuits. The switching audio amp in the March 2010 edition of Elektor is small, neatly designed and comes with a number of extras. The circuit is based around a MAX9744 and outputs 2 x 20 watts at an efficiency of 94%. The project has built-in volume and tone control as well as a backlit LCD. No knobs... everything is adjusted using a remote control!

*Article titles and magazine contents subject to change; please check the Magazine tab on www.elektor.com.
The March 2010 issue of Elektor USA is published on Thursday, February 11, 2010.
Elektor is available on subscription or from selected Borders and Barnes & Noble bookshops in the USA and Canada.*

www.elektor.com www.elektor.com www.elektor.com www.elektor.com www.elektor.com www.elektor.com

Elektor on the web

All magazine articles back to volume 2000 are available online in pdf format. The article summary and parts list (if applicable) can be instantly viewed to help you positively identify an article. Article related items are also shown, including software downloads, circuit boards, programmed ICs and corrections and updates if applicable. Complete magazine issues may also be downloaded.

In the Elektor Shop you'll find all other products sold by the publishers, like CD-ROMs, DVDs, kits, modules, equipment, tools and books. A powerful search function allows you to search for items and references across the entire website.

Also on the Elektor website:

- Electronics news and Elektor announcements
- Readers Forum
- PCB, software and e-magazine downloads
- Time limited offers
- FAQ, Author Guidelines and Contact



Name/Company				
Street & No.				
City/State/Zip			Country	
Tel			E-mail	
F102	Date	-	-	Signature

Verification code:

Phone: 860-875-2199
Fax: 860-871-0411
E-mail: sales@elektor.com
www.elektor.com

Verification code:

Phone: 860-875-2199
Fax: 860-871-0411
E-mail: sales@elektor.com
www.elektor.com

**Yes, I want to subscribe
to Elektor US for 1 year***

- ☐ Standard Subscription for \$39.95 (11 issues)
- ☐ Plus Subscription for \$54.95
(11 issues plus the Elektor Volume 2009 DVD-ROM)

Name/Company				
Street & No.				
City/State/Zip			Country	
Tel			E-mail	
F102	Date	-	-	Signature

ORDERING INFORMATION

To order contact customer service:

Phone: 860-875-2199
Fax: 860-871-0411
Mail: Elektor US
4 Park Street
Vernon CT 06066
USA
E-mail: sales@elektor.com
On-line at www.elektor.com

Customer service hours: 8:00 AM–4:30 PM Monday–Thursday. Voice mail available at other times.
When leaving a message please be sure to leave a daytime telephone number where we can return your call.

PLEASE NOTE: While we strive to provide the best possible information in this issue, pricing and availability are subject to change without notice. To find out about current pricing and stock, please call or email customer service.

COMPONENTS

Components for projects appearing in Elektor are usually available from certain advertisers in the magazine. If difficulties in obtaining components are suspected, a source will normally be identified in the article. Please note, however, that the source(s) given is (are) not exclusive.

PAYMENT

Orders must be prepaid. We accept checks or money orders (in US \$ drawn on a US bank only), VISA, Mastercard, Discover, and American Express credit cards. We do not accept C.O.D. orders.
We also accept wire transfers. Add \$20 to cover fees charged for these transfers.

TERMS OF BUSINESS

Shipping Note: All orders will be shipped from Europe. Please allow 3–4 weeks for delivery. Shipping and handling via airmail: US \$20.00 per order. **Returns** Damaged or miss-shipped goods may be returned for replacement or refund. All returns must have an RA #. Call or email customer service to receive an RA# before returning the merchandise and be sure to put the RA# on the outside of the package. Please save shipping materials for possible carrier inspection. Requests for RA# must be received 30 days from invoice. **Patents** Patent protection may exist with respect to circuits, devices, components, and items described in our books and magazines. Elektor accepts no responsibility or liability for failing to identify such patent or other protection. **Copyright** All drawing, photographs, articles, printed circuit boards, programmed integrated circuits, diskettes, and software carriers published in our books and magazines (other than in third-party advertisements) are copyrighted and may not be reproduced (or stored in any sort of retrieval system) without written permission from Elektor. Notwithstanding, printed circuit boards may be produced for private and personal use without prior permission. **Limitation of liability** Elektor shall not be liable in contract, tort, or otherwise, for any loss or damage suffered by the purchaser whatsoever or howsoever arising out of, or in connection with, the supply of goods or services by Elektor other than to supply goods as described or, at the option of Elektor, to refund the purchaser any money paid with respect to the goods.

SUBSCRIPTIONS (US & CANADA ONLY)

Subscription rates (1 Yr.)

Standard Subscription: \$39.95
Plus Subscription: \$54.95

Canada add \$11 per year for postage

All subscriptions begin with the current issue. Expect 3–4 weeks for receipt of the first issue. Subscriptions, renewals, and change of address should be sent to:

Elektor US
4 Park Street
Vernon CT 06066
USA

E-mail: sales@elektor.com

Order subscriptions on-line at www.elektor.com/subs

Subscriptions may be paid for by check or money order (in US \$ drawn on a US bank only). We accept Mastercard, VISA, Discover and American Express credit cards.

For gift subscriptions, please include gift recipient's name and address as well as your own, with remittance. A gift card will be sent on request.
Subscriptions may be cancelled at any time for a refund of all unmailed issues.

Does your subscription expire soon?


Renew it online at www.elektor.com/renew

310 Circuits



Creative solutions for all areas of electronics

The 30x series of Summer Circuit compilation books have been bestsellers for many years. The 11th volume is available now! 310 circuits, tips and design ideas in one book form a treasure trove for every area of electronics: audio and video, hobby and modelling, RF techniques, home and garden, test and measurement, microcontrollers, computer hardware and software, power supplies and chargers – plus of course everything else that does not seem to belong in any of these categories. 310 Circuits for the first time has a section exclusively on robots and robotics. This book contains many complete solutions as well as useful starting points for your own projects. Both categories and anything in between represent a veritable fountain of inspiration for cultivating your own ideas and learning about electronics.

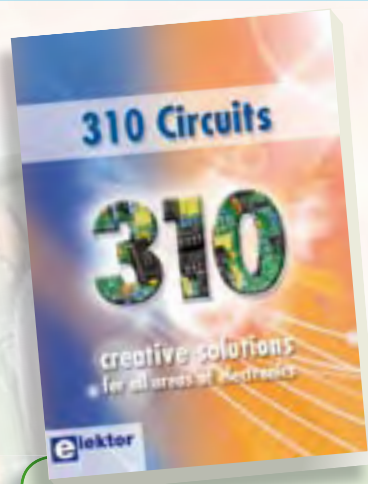

544 pages • ISBN 978-0-905705-78-1
\$48.30

Elektor US
4 Park Street
Vernon CT 06066
USA
Phone: 860-875-2199
Fax: 860-871-0411
E-mail: sales@elektor.com

Further information and ordering at www.elektor.com/shop

INDEX OF ADVERTISERS

Avit Research, Showcase www.avitresearch.co.uk	78	MikroElektronika. www.mikroe.com	3
Beta Layout www.pcb-pool.com	33	Paia Electronics, Showcase www.paia.com	47, 78
Black Robotics, Showcase www.blackrobotics.com	78	Parallax www.parallax.com	17
ByVac, Showcase www.byvac.com	78	Pololu Corporation, Showcase www.pololu.com	47, 78
Decade Engineering, Showcase www.decadenet.com	78	Saelig, Showcase www.saelig.com	19, 78
Decibit Co. Ltd, Showcase www.decibit.com	78	Schmartboard, Showcase www.schmartboard.com	78
DLP Design www.dlpdesign.com	47	SparkFun Electronics www.sparkfun.com	88
ExpressPCB www.expresspcb.com	11	Showcase	78, 79
Hameg Instruments, Showcase www.hameg.com	78		
Jameco www.jameco.com/unwrap	9		
Linx Technologies. www.linxtechnologies.com	2		
Microengineering Labs, Inc., Showcase www.melabs.com	78		

**Advertising space for the issue of 11 March 2010
may be reserved not later than 16 February 2010**

with Strategic Media Marketing, Inc. - 2 Main Street -
Gloucester, MA 01930 - USA - Telephone 1.978.281.7708 -
Fax 1.978.281.7706 - e-mail: ElektorUSA@smmarketing.us to whom all
correspondence, copy instructions and artwork should be addressed.



Let your geek shine.

Meet Steven Kennedy, SparkFun customer and high school teacher. In one of his classes, Steven helps his students discover the world of physical computing by encouraging them to explore all the facets of engineering – whether it is electrical, mechanical, or aeronautical. Using SparkFun products, Steven's class has created projects ranging from a homemade pick-and-place machine to a robotic arm.

Whether you're looking for tutorials to get started in electronics, or a way to inspire your students, the tools are out there. Create an environment of invention, and let your geek shine too.



Sharing Ingenuity
WWW.SPARKFUN.COM

©2010 SparkFun Electronics, Inc. All rights reserved. All other trademarks contained herein are the property of their respective owners. For more information about Steven's class and projects, please visit www.youtube.com/user/OPHSTech or www.opschools.org.