

6-VALVE TOP BAND TX.

PRACTICAL 1/6 WIRELESS

OCTOBER
1960



CONTENTS

RADIO SHOW REPORT
COMPREHENSIVE GUITAR
AMPLIFIER
H.F. ONE-VALVER
SIMPLE COMMUNICATIONS SYSTEM
MAINS DUAL-WAVE 2
ETC. ETC. ETC.



RADIO & TV TABLES

"NEWSTEAD" (as illustrated). This contemporary "Slimline" TV Table is finished in highly polished walnut veneer. Measures 19" x 13" x 20" high.

Price £3. 7. 6 (inc. P.T.)
"CHATSWORTH". Finished in highly polished walnut veneer. Measures 19" x 14" x 21" high.

Price £4. 0. 0 (inc. P.T.)
"WELBECK" (as illustrated) measures 20" x 20" x 20" and is fitted with self-adjusting gliders.


Price £3. 15. 0 (inc. P.T.)
"SHERWOOD" will accommodate the largest television receivers, measures 23" high x 25" wide x 22" deep.

Price £5. 5. 0 (inc. P.T.)
"SENIOR", of ample dimensions (18" x 24" x 25" high).

Price £4. 18. 9 (inc. P.T.)
All are supplied packed flat ready for instant assembly and with the exception of the Welbeck and the Chatsworth have easy running 2" castors.



*The symbol
of extra
High Quality*

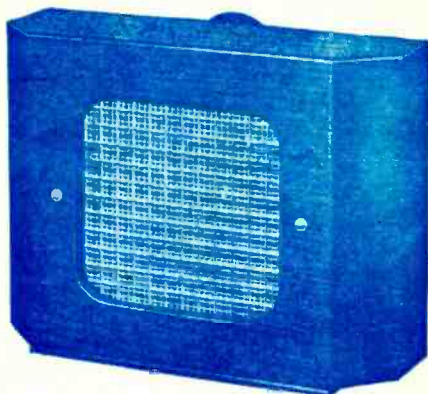

Stentorian
EXTENTION SPEAKERS

These well designed speakers demonstrate the traditional Whiteley quality at really competitive prices. This range of extension speakers has finger-tip volume control, is superbly finished in polished walnut veneer and provides excellent reproduction.

WHITELEY ELECTRICAL RADIO CO. LTD.
MANSFIELD . NOTTS

WITH THE
EXCLUSIVE
FINGER-TIP
VOLUME
CONTROLS

'BUDE' 60/-
'BEDFORD' 72/-
'BRISTOL' 86/6

Prices include P.T.

ERSIN MULTICORE SOLDERS

for a first class joint every time

Ersin Multicore contains 5 cores of extra-active, non-corrosive Ersin Flux. Prevents oxidation and cleans surface oxides.

SIZE 1 CARTON
5/-

**HANDYMAN'S
CARTON**

Suitable for 200 average joints. **6d.**



Wherever precision soldering is essential, manufacturers, engineers and handymen rely on MULTICORE. There's a MULTICORE SOLDER just made for the job you have in hand. Here are some of them.

SAVBIT TYPE 1 ALLOY

A specially formulated alloy to reduce the wear of soldering iron bits. Contains 5 cores of non-corrosive Ersin Flux and is ideal for all soldering purposes.

SIZE 1 CARTON 5/-
Available in three specifications.



**HOME CONSTRUCTORS
2/6 PACK**

In addition to the well-known Home Constructors Pack (containing 19ft. of 18 s.w.g. 60/40 alloys) a similar pack is now available containing 40ft. of 22 s.w.g. 60/40 alloy especially suitable for printed circuits.



**BIB WIRE STRIPPER
AND CUTTER**

Strips insulation without nicking wire, cuts wire cleanly, splits extruding flex. **3/6 each**




**SPECIAL FOR THE "HAMS"
RADIO STATION**

Illustrated

$\frac{1}{8}$ inch detachable bit soldering instrument
List No. 70

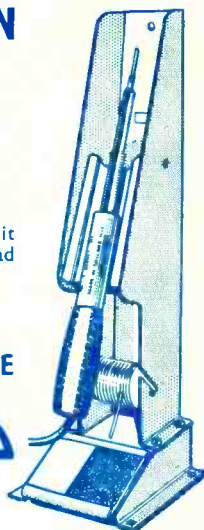Combined Protective Unit with Wiper/Abrasion Pad and Solder Reel
List No. 700



Apply **SALES & SERVICE**

ADCOLA
(Regd. Trade Mark)

**GAUDEN ROAD
CLAPHAM HIGH ST.
LONDON, S.W.4**

Telephones:
MACaulay 4272 - 3101


British & Foreign
Patents. Registered
Designs, etc.

Telegrams:
"SOJJOINT, LONDON"

MULTICORE SOLDERS LTD.,

MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS. (BOXMOOR 3636)

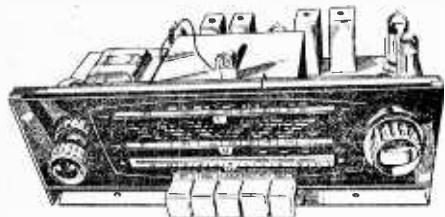BRAND NEW AM/FM (V.H.F.) RADIOGRAM CHASSIS AT £13.6.8 (P. & P. 10/-)



Some dusty (but working) chassis at £10 (carr. 10/-). Tapped input 220-225 v. and 226-250 v. A.C. ONLY. Chassis size 15 x 6 1/2 x 5 1/2 in. high. New manufacturers. 12 mths. guarantee. Dial 1 1/2 x 4 in. in black and yellow. Pick-up. Extension Speaker. Ae., E., and Dipole sockets. Five "piano" push buttons—OFF L.W., M.W., F.M. and Gram. Aligned and tested. With all valves and O.P. Transformer. Tone Control Fitted. Covers 1,000—1,900 Mc.; 200-500 Mc.; 88-89 Mc/s. Valves E290 rect., ECH81, EF89, EABC80, EL84, ECC85. 10 x 6 in. ELLIPTICAL SPEAKER. 20/-, to purchasers of this chassis. Speaker and Cabinet to fit chassis (table model), 47/6.

TERMS:—(Chassis) £4.16.8 down +10/- carr. and 6 Monthly Payments of 30/-, or with Cabinet and Speaker £5.9.2 down and 7 Monthly Payments £1.12.2.

COSSOR/EMI 10in. TV tube type 108K. Brand new and boxed. ONLY 30/- (carr. 3/6).

BATTERY ELIMINATOR. Converts your Battery Set to Mains. For 4 Low Consumption Valves (96 range). 90 v. 15 mA. and 1.4 v. 125 mA. 42/6 (2/6 post). 200-250 v. A.C. Size 5 1/2 x 3 1/2 x 2 in. Also for 250 mA. 1.4 v. and 90 v. 15 mA at same price. Specify which, or give Valve line-up.


50 SILVERED MICA AND CERAMIC CONDENSERS, 10/- 50 RESISTORS, 5/-, ALL DIFFERENT VALUES, 21 TUBULAR CONDENSERS (7 values 0.001 to 0.1 mf), 4/6.

FULLY BUILT BATTERY OPERATED TRANSISTOR RECORD PLAYER FOR

£7.19.6 (3/6 P. & P.)

Cossor printed circuit 4-transistor amplifier; Garrard 45 r.p.m. battery player type BA1; speed control Cabinet size 11 x 9 x 5 1/2 in.; less than 8 1/2 lb. inc. batteries. Requires two Ever Ready AD28 batteries.


Complete kit £5.14.6 post paid.

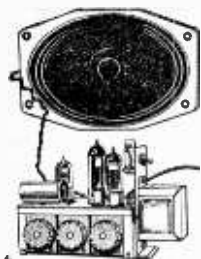

3-VALVE AMPLIFIER (INC. RECT.). Capable of giving 6 watts. Mains and output transformers. Valves ECC83, EL84, and E280. 3 Controls, volume, bass and treble. On/Off switch. Fully guaranteed. Chassis size 6 1/2 x 3 x 2 1/2 in. 6 in. round or 7 x 4 in. elliptical speaker, state which. Not suitable for microphone input.

67/- (3/- p. & p.)

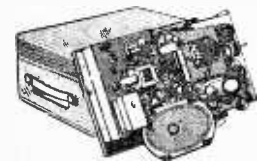TAPE RECORDER ASSEMBLED TO B.S.R. MONARDECK



A QUALITY ARTICLE. Valves E730, ECC83, ECL82, DM70, Acos Crystal "mike", 850ft. Tape and extra spools. 3 1/2 in./sec. Mike and Radio inputs; Vol. on/off tone, Ext. I.S. and Monitor. Fast forward and reverse. Cannot be accidentally erased. Magic Eye Indicator. 7 x 4 in. Speaker. Four separate chassis assembled to base of 14 x 11 1/2 x 7 in.

the Monardeck to fit into cabinet of PRICE for Recorder and Deck Assembly, as above (without Cabinet), £16.10.0 (10/- p. & p.), Cabinet £3 (5/- carriage). Enquiries invited for any of the parts.

See additional advertisement on page 524

GLADSTONE RADIO 58A HIGH STREET, CAMBERLEY, SURREY. Tel. 22791
Also at 3 Church Road, Lawrence Hill, Bristol 5 and 247 New Road, Portsmouth, Hants.
Camberley closed Saturdays, Bristol and Portsmouth closed Wed., afternoons.

"READY TO USE" ITA CONVERTER



Separate gain controls. Valves PCF80 and PCC84. Switch position ITA (1)—ITA (2)—BBC. Bakelite moulded cabinet 8 1/2 x 4 x 6 in. £5.5.0. P. & P. 3/-.

LISTEN WITHOUT INTERFERENCE



Fully built V.H.F./F.M. Tuner for £5.10.0 (3 - post). Covers 88-98 Mc/sec. Wired, aligned and tested. 4 Mullard valves; for use up to 40 miles from transmitter. FRINGE MODEL for above this (5 valves), £6 (p. & p. 3/-). External H.T. and L.F. supplies reqd. for both of foregoing. BUT, a complete V.H.F. set, four valves, with mains transformer amplifier, rectifier and speaker (with above frequency coverage) can be supplied for ONLY £8.5.0 (4/- carr.). Cheap room dipole 10/-, 300 ohm twin feeder, 6d. yd. All with 12 months' guarantee.



GRAMOPHONE AMPLIFIER with 5in. SPEAKER. On Fabric-covered Baffle 12 1/2 x 5 in. Mains and Output Transformers, Metal Rectifier, ECL82 Valve, Tone and Volume Controls.

On/Off switch. Plenty of Volume. Fully Guaranteed. Two Knobs supplied. Ready to play. Useful for Stereo.

ONLY 57/-, post 3/-



BEREK BATTERY RADIO IN MAKER'S CARTON. Valves DK90, DF96, DAF96, DL96. Requires Ever Ready battery B108 or battery elim. for converting to mains operation—see adjacent item. Two Short Wavebands 2.5 to 7 Mc/s and 6.5 to 17 Mc/s. Cabinet 12 x 7 1/2 x 6 in. ONLY £5 (3/6 p. & p.). MW and SW £5.4.0 plus 2/6 p. & p.). Available as kit.

AUTOMATIC RECORD CHANGERS COLLAR CONQUEST with manual play also. 4-speed. A.C. mains 200-250 v., see illus.

£7.10.0 (5/- P. & P.)

B.S.R. UAS 4-speed auto-changer. £6.10.0 (5/- carr.) or with Stereo Head, £6.12.6 (5/- carr.).

All with Crystal Turnover Head.



ALL ITEMS GUARANTEED 12 MONTHS—B.V.A. VALVES

3 MONTHS
Send 6d (stamps will do) for our illustrated catalogue of the above items and others. All New Goods. Delivered by return. Terms:—One-third down and balance plus 7/6 in four equal monthly payments. Postage with down payment (C.O.D. 2/- extra).
SEE SPECIAL TERMS FOR A.M./F.M. CHASSIS AND TAPE RECORDER.
Posted Orders to Camberley Please.

R.S.C. HI-FI TAPE RECORDER KIT

REALISM AT INCREDIBLY LOW COST. CAN BE ASSEMBLED IN HALF AN HOUR

The Recorder incorporates the Latest Collaro Studio Tape Transcriber. The Linear LT45X High Quality Tape Amplifier listed £12.12.0 High Flux P.M. Speaker listed 30/- empty Tape Spool, a Reel of Best Quality Tape listed 22/6 and a Handsome Portable carrying Cabinet finished in Two-tone covering, size 18 x 13 x 8in. high, listed £41.0.0. and circuit. Total cost if purchased individually approximately £40. Performance equal

to units in the £60-£80 class. Send S.A.E. for leaflet.

25 1 GNS. 2 Carr. 17/6


H.P. TERMS. Deposit £5.7.6 and 12 monthly payments 2 gns. Cash price if settled in 3 mths.

TELEVISION RECTIFIERS. 250v. 200mA. small size. Only 8 9es. **RE-ENTRANT SPEAKERS.** Tannoy, 8 watt, 7.5 ohms. Only 22/6 each. **Parmeko Horn Type,** 10 watt, 15 and 200 ohm matching. 59/6. R.C.A. 20 watt, 15 ohms or 200 ohms, 6 gns.

HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP STAGES

Two input sockets with associated controls allow mixing of "mike" and gram, as in A10. High sensitivity. Includes 5 valves, ECC83, ECC83, EL84, EL84. High Quality sectionally wound output transformer specially designed for Ultra Linear operation, and reliable small condensers of current manufacture. **INDIVIDUAL CONTROLS FOR BASS AND TREBLE "L" and "CUT."** Frequency response — 3 D.B. 30-30,000 c/c.s. Six negative feedback loops. Hum level 60 D.B. down. ONLY 23 millivolts INPUT required for FULL OUTPUT. Suitable for use with all makes and types of pick-ups and microphones. Comparable with the very best designs. For **STANDARD or LONG PLAYING RECORDS.** For **MUSICAL INSTRUMENTS** such as **STRING BASS, GUITARS, etc., OUTPUT SOCKET** with plug provides 300 v. 30 mA. and 6.3 v. 1.5 A. For supply of a **RADIO FREQUENCY UNIT,** DEPOSIT 24/3, and 9 monthly payments of 24/3. Send S.A.E. for illustrated leaflet detailing Ready-to-assemble Cabinets, Speakers, Microphones, etc., with cash and credit terms.

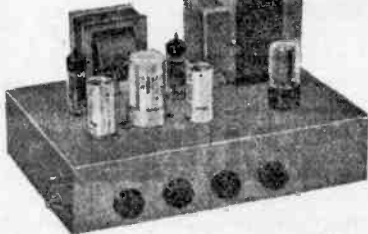

Only **8 Gns.** Carr. 10/-

If required louvered metal cover with 2 carrying handles can be supplied for 18/9. **TERMS ON ASSEMBLED UNITS, DEPOSIT 24/3, and 9 monthly payments of 24/3.** Send S.A.E. for illustrated leaflet detailing Ready-to-assemble Cabinets, Speakers, Microphones, etc., with cash and credit terms.

R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER

A complete set of parts for the construction of a stereophonic amplifier giving 5 watts high quality output on each channel (total 10 watts). Sensitivity is 50 millivolts, suitable for all crystal stereo heads. Ganged Bass and Treble Controls give equal variation of "Hifi" and "cut". Provision is made for use as straight (monaural) 10 watt amplifier. Valve line-up ECC83, ECC83, EL84, EL84, EZ81. Outputs for 2-3 ohm speakers. Point-to-point wiring diagrams and instructions supplied. Send S.A.E. for leaflet.

8 Gns. Carr. 10/-

R.S.C. BATTERY CHARGING EQUIPMENT

ASSEMBLED CHARGERS

- 6 v. 1 amp. 19/9
 - 6 v. or 12 v. 1 amp. 29/9
 - 6 v. 2 amps. 29/9
 - 6 v. or 12 v. 2 amps. 33/9
 - 6 v. or 12 v. 3 amps. with ammeter. 59/9
- Above ready for use. With mains and output leads. Carr. 3/6.



Assembled 6 v. or 12 v. 4 amps.

Fitted Ammeter and variable charge rate selector. Also selector plug for 6 v. or 12 v. charging. Louvered steel case with stoved blue hammer finish. Fused **69/9** and ready for use with Carr. 5/- mains and output leads. **TERMS:** Deposit 13/3 and 5 monthly payments 13/3. Carr. 3/9.

All for A.C. Mains 200-250 v., 50 ccs. Guaranteed 12 months.

BATTERY CHARGER KITS

- Consisting of Mains Transformer, F.W. Bridge, Metal Rectifier, well ventilated steel case. Fuses, Fuse-holders, Grammet panels and circuit. Carr. 3/6 extra.
- 6 v. or 12 v. 1 amp. 24/9
 - As above, with Ammeter. 32/9
 - 6 v. 2 amps. 25/9
 - 6 v. or 12 v. 2 amps. 31/6
 - 6 v. or 12 v. 2 amps. inclusive of Ammeter. 42/9
 - 6 v. or 12 v. 4 amps. 53/9
 - 6 v. or 12 v. 4 amps. with Ammeter and variable charge rate selector. 59/9.
- CHARGER AMMETERS.** 0-1.5 a., 0-3 a., 0-4 a., 0-7 a., 0-25 a., 0-60 a. 8/8.

HEAVY DUTY CHARGER KIT

612 v. 6 amps, variable output. Consisting of Mains Transformer 0-200-230-250 v. F.W. (Bridge) Selenium Rectifier; Ammeter. Multi-Position Switch with Knob; Panels. Plugs, Fuses, Fuseholder and circuit. 59/9. Carr. 4/8.

R.S.C. MAINS TRANSFORMERS

- Interleaved and Impregnated. Primaries 200-230-250 v. 50 c/s. Screened **TOP SHROUDED DIPOL THROCGH**
- 250-0-250 v. 70 mA. 6.3 v. 2 a. 5 v. 2 a. 17/9
 - 350-0-350 v. 80 mA. 6.3 v. 2 a. 5 v. 2 a. 18/9
 - 250-0-250 v. 100 mA. 6.3 v. 2 a. 6.3 v. 1 a. 19/9
 - 250-0-250 v. 100 mA. 6.3 v. 3.5 a. C.T. 22/9
 - 250-0-250 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 25/9
 - 300-0-300 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 25/9
 - 350-0-350 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 25/9
 - 350-0-350 v. 100 mA. 6.3 v. 4 a. 4 a. C.T. 0-4.5 v. 3 a. 25/9
 - 350-0-350 v. 150 mA. 6.3 v. 4 a. 5 v. 3 a. 29/9
- FULLY SHROUDED UPRIGHT**
- 250-250 v. 60 mA. 6.3 v. 2 a. 5 v. 2 a. Midget type 21-3-31n. 17/11
 - 250-0-250 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 26/9
 - 300-0-300 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 26/9
 - 350-0-350 v. 130 mA. 6.3 v. 4 a. 5 v. 3 a. 26/9
 - for Mullard 510 Amplifier 35/9
 - 350-0-350 v. 150 mA. 6.3 v. 4 a. 5 v. 3 a. 35/9
 - 425-0-425 v. 200 mA. 6.3 v. 4 a. C.T. 6.3 v. 4 a. C.T. 5 v. 3 a. 49/9

FULLY GUARANTEED We can quote for special types singly or in any quantity

- FILAMENT TRANSFORMERS**
All with 200-250 v. 50 c/s. primaries 6.3 v. 1.5 a. 5/9; 6.3 v. 2 a. 7/6; 0-4-6.3 v. 2 a. 7/9; 12 v. 1 a. 7/11; 6.3 v. 3 a. 8/11; 6.3 v. 6 a. 17/6; 12 v. 1.5 a. twice. 17/6.
- OUTPUT TRANSFORMERS**
Midget Battery Pentode 66:1 for 35A. 6/2
- Small Pentode, 5000 Ω to 3 Ω 3/9
 - Small Pentode 7/8,000 Ω to 3 Ω 3/9
 - Standard Pentode 5,000 Ω to 3 Ω 5/6
 - Standard Pentode 7/8,000 Ω to 3 Ω 5/6
 - 10,000 Ω to 3 Ω 5/6
 - Push-Pull 10-12 watts 6V6 to 3 Ω or 15 Ω 18/9
 - Push-Pull 10-12 watts to match 6V6 to 3-5-8 or 15 Ω 18/9
 - Push-Pull EL84 to 3 or 15 Ω 18/9
 - Push-Pull 15-18 watts. 6L6, KT66 22/9
 - Push-Pull for Mullard 510 Ultra Linear 29/9
 - Push-Pull 20 watts. sectionally wound 6L6, KT66, etc., to 3 to 15 Ω. 47/9

ELIMINATOR TRANSFORMERS

- Primaries 200-250 v. 50 c/s. 15/9
- 120 v. 40 mA. 5-0-5 v. 1 a. 15/9
- 90 v. 15 mA. 4-0-4 v. 500 mA. 9/9

SMOOTHING CHOKES

- 150 mA. 7-10 H 250 ohms. 11/9
- 100 mA. 10 H 200 ohms 9/9
- 80 mA. 10 H 350 ohms 9/9
- 60 mA. 10 H 400 ohms 4/11

CHARGER TRANSFORMERS

- All with 200-230-250 v. 50 c/s Primaries:
- 0-9-15 v. 1 a. 11/9; 0-9-15 v. 2 a. 14/9; 0-9-15 v. 3 a. 16/9; 0-9-15 v. 5 a. 19/6; 0-9-15 v. 6 a. 23/9.

AUTO (Step up/Step down) TRANS.

- 0-110/120-230/250 v. 50-80 watts. 13/9;
- 0-110/120-200/230/250 v. 150 watts 27/9.

MICROPHONE TRANSFORMERS

- 120:1 high grade, clamped. 6/8; 120:1 Potted, Mu-metal screened. 9/8.

R.S.C. A12 STEREOPHONIC AMPLIFIER KIT

A complete set of parts to construct a Stereo amplifier with an undistorted output total 6 watts. For A.C. mains input of 200-250 v. Outputs for matched 2-3 ohm speakers. Sensitivity 130 m.v. Ganged Vol. and Tone Controls. Preset balance control. Full instructions and point-to-point wiring diagrams supplied. Only good quality Carr. and pkg. 5/- components and latest high grade valves used. Exceptionally realistic reproduction can be obtained at ample volume for the home, as can be demonstrated in typical surroundings at our County Arcade premises. A really sensational offer.

4 Gns.

STEREO EQUIPMENT OFFER. Comprising A12 Kit, 2 matched 8in. L/Speakers, and Acos 70Ck Stereo head. Carr. 7/7 with sapphire stylus suitable most pick-ups.

PICK-UP ARMS complete with HI-FI turnover crystal head. Acos GP54. Limited number brand new, perfect, at approx. half price. Only 29/11.

ACOS CRYSTAL MICROPHONES. Mic40 stand or desk. Listed 45/-, Only 27/9 38-1 Stick types, listed 5 gns. Only 39/6

R.S.C. 30 WATT ULTRA LINEAR HIGH FIDELITY AMPLIFIER A10

A highly sensitive Push-Pull high output unit with self-contained Pre-amp. Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 db. down. Frequency response -3 db. 30-30,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 807 output valves. All components are chosen for reliability. Six valves are used EF86, EF85, ECC83, 807, 807, GZ33. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUTDOOR FUNCTIONS, etc. For use with Electronic ORGAN, GUITAR, STRING BASS, etc. For standard or long-play records OUTPUT SOCKET PROVIDES L.T. and H.T. for a RADIO FEEDER UNIT An extra input with associated vol. control is provided so that two separate inputs such as Gram and Mike can be mixed. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains and has output for 3 and 15 ohm speakers. Complete kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. If required cover as for A8 can be supplied for 18/9. The amplifier can be supplied, factory built with 12 months guarantee, for £13.19.6.

11 gns. Carr. 10/- TERMS: DEPOSIT 31/9 and 9 monthly payments of 31/9.

FULL RANGE OF LINEAR AMPLIFIERS ALWAYS IN STOCK.

R.S.C. BATTERY TO MAINS CONVERSION UNITS

Type BM1. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2 1/2 in. approx. Completely replaces battery supplying 1.4 v. and 90 v. where A.C. mains 200-250 v. 50 c/s is available. Suitable for all battery powered receivers requiring 1.4 v. and 90 v. This includes latest low consumption types. Complete kit with diagrams, 39/9. or ready to use, 46/9.




Type BM2. Size 8 x 5 1/2 x 2 1/2 in. Supplies 120 v. and 90 v. and 50 v. 40 mA. and 2 v. 0.4 a. to lamp. fully smoothed. Thereby completely replacing both H.T. batteries and L.T. 2 v. accumulators when connected to A.C. mains supply 200-250 v. 50 c/s. SUITABLE FOR ALL BATTERY RECEIVERS normally using 2 v. accumulator. Complete kit of parts with diagrams and instructions. 49/9, or ready to use, 59/6.

R.S.C. 3-4 WATT A7 HIGH-GAIN AMPLIFIER For 200/250 v. 50 c/s. Mains input. Appearance and Specification, with exception of output wattage, as A5 amplifier. Complete Kit with diagrams, £3.15.0. Carr. 3/6.

R.S.C. BRADFORD, MANCHESTER AND LEEDS (Leeds) Ltd.

COLLARO JUNIOR 4-speed single player units and Hi-Fi crystal pick-up with turnover head, £3.19.6. B.S.R. UAS 4-SPEED) AUTO-CHANGERS with Stereo/Monaural pick-up head, £7.19.6. Carr. 5/- TERMS: C.W.O. or C.O.D. No C.O.D. under £1. Post 1/9 extra under £2. 2/9 extra under £5. Open 9 to 6. Weds. until 1 P.m. Trade supplied. S.A.E. with all enquiries. Mail Orders to 29-31 Moorfield Road, Leeds 12. Callers to 5 and 7 County (Mecca) Arcade, Briggate, Leeds 1. and 8-10 Brown Street (Market Street), Manchester 2, or 56 Morley Street (next to Majestic Ballroom), Bradford.

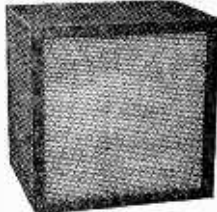12in. 10 WATT HIGH QUALITY LOUD-SPEAKER IN POLISHED WALNUT FINISHED CABINET



Gauss 12,000 lines. Speech coil 3 ohms or 15 ohms. Only £4.19.6 Carr. 5/- Terms: Deposit 11/3 and 9 monthly payments of 11/3. 12in. 20 WATT HI-FI LOUD-SPEAKERS with HI-FI pre-amplifier. Size 18 x 18 x 18in. Finish as above. Terms: Deposit 17/9 and 9 monthly payments of 17/9. Only £7.19.6. Carr. 8/6.

R.S.C. 45 WATT A5 HIGH-GAIN AMPLIFIER



A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest high fidelity pick-up heads, in addition to all other types of pick-ups and practically all 'mikes'. Separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 70db. down, 15db. of Negative feedback is used. H.T. or 300 v. 25 mA. and L.T. of 6.3 v. 1.5 a. is available for the supply of a radio Feeder Unit or Tape-Deck pre-amplifier. For A.C. mains input of 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Chassis is not alive. Kit is complete in every detail and includes fully punched chassis (with baseplate) with Blue hammer finish and point-to-point wiring diagrams and instructions. Exceptional value at only £4.15.0, or assembled ready for use 25/- extra, plus 3/6 carr. or Deposit £2.6 and 5 monthly payments of 22/6 for assembled unit.

R.S.C. PORTABLE GUITAR AMPLIFIERS

Junior 5 watts High Quality Output. Separate Bass and Treble 'Cut' and 'Boost' controls. Sensitivity 15 m.v.. Twin inputs. High Flux 8in. Loudspeaker 'built-in'. Handsome, strongly made Cabinet (size approx. 14 x 14 x 7in.) finished in satin walnut, and fitted carrying handle. H.P. Terms. Deposit £1 and 9 monthly payments of £1. Senior 10 watts High Fidelity output. Separate Bass and Treble 'Cut' and 'Boost' controls. Twin separately controlled high gain inputs. Used on two instruments such as Guitar and String Bass can be used at the same time. Two loudspeakers are incorporated, a high Flux 12in. for Bass notes and a 7 x 4 in. elliptical for Treble. Cabinet is well made and finished satin walnut. Size approx. 18 x 18 x 18in. H.P. Terms. Deposit £4.9 and 9 monthly payments of 34/9. £8-19-6 Carr. 7/6

15 Gns. All models for 200-250 v. Carr. 10/- A.C. mains.

SPECIAL TRANSISTOR OFFER. T81 Brimar. Brand new. Perfect. 3 for 10/9

AM/FM RADIOGRAM CHASSIS for 200-250 v. A.C. mains only. 3 wavebands. V.H.F., Medium and Long Built in Ferrite rod aerial. Attractive glass dial size 16in. long by 4in. high. Valve line up EF85, ECC81, ECC85, EAB00, EL84, EZ80. High quality output of up to 4 watts. Overall size 16in. x 4in. x 5in. Only £12.19.6. Carriage 10/-

PLISSEY DUAL CONCENTRIC 12in. 15 ohms HIGH FIDELITY SPEAKER (12,000 lines) with built-in tweeter (completely separate elliptical speaker with choke, condensers, etc.) providing extraordinarily realistic reproduction when used with our A8 or similar amplifier. Rates 10 watts. Price only £5.17.6.

HI-FI CRYSTAL PICK-UP HEADS. (Turnover type with sapphire stylus). HGP59. Standard replacement for Garrard and B.S.R. B.S.R. Full-F, Garrard GC2, 19/9. B.S.R. Stereo/Monaural 39/11.

P.M. SPEAKERS. 2-3 ohm 2in. Perdio 21/9. 5in. 17/9. 8in. 16/9. 8in. 16/9. 8 x 5in. 25/9. 10in. 29/9. 10 x 12in. 29/11. 10in. W.B. 'Stentorian' 3 or 15 ohms type HF1012 10 watts, hi-fidelity type. Recommended for use with our A8 Amplifier. £4.10.9. 12in. Plessey 3 ohms 10 watts (12,000 lines) 59/6. TWEETERS. Plessey 30 19/9. 15n 25/9.

GLA MINIATURE 2-3 WATT GRAM AMPLIFIER. For use with any single or auto-change unit. Output for 2-3 ohm speaker. For 200-250 v. 50 c.p.s. A.C. mains. Overall size 11 x 2 1/2 x 2 1/2 in. Controls: Vol. and Tone with switch. Guaranteed 12 months. Only 59/6.

SUPERHET FEEDER UNIT. Design of a high quality Radio Tuner Unit (specially suitable for use with any of our Amplifiers). Delayed A.V.C. employed. The W.Ch. Sw. incorporates Gram position. Controls are Tuning, W.Ch. and Vol. only 250 v. 15 mA. H.T. and L.T. of 6.3 v. 1 amp. required from amplifier. Size of unit approx. 9-8-7in. high. Simple alignment procedure. Point-to-Point wiring diagrams, instructions and priced parts list with illustration. 2/6. Total building cost £4.15.0. For descriptive leaflet send S.A.E.

COLLARO CONQUEST 4-SPEED AUTO-CHANGER with high fidelity Studio pick-up. Latest model. For 200-250 v. 50 c.p.s. A.C. mains. Our price £6.19.6. Carr. 5/6

SPECIALIST IN THE SUPPLY OF NEW GUARANTEED VALVES, TRANSISTORS AND GERMANIUM DIODES
BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1.

Telephone: PRIMROSE 9090.

EXPRESS POSTAL SERVICE ALL ORDERS DESPATCHED SAME DAY AS RECEIVED. FOR ONLY 2/6 EXTRA TELEPHONE FOR THAT URGENT ORDER TO BE DESPATCHED IMMEDIATELY BY OUR SPECIAL C.O.D. SERVICE.

Table listing electronic components such as valves (OA2, OB2, OZ2, IA3, IA5, IA7GT, IC5, ID5, ID6, IG6, IH5GT, IL4, ILDS, ILN5, INSGT, IRS, IS4, IS5, IT4, IU5, 2A3, 2A7, 2P, 2X2, 3A4, 3A5, 3B7, 3D6, 3Q4, 3CSGT, 3SA, 3R4Y, 5U4G, 5V4G, 5Y3G, 5Y3GT, 5Z3, 5Z4G, 5Z4GT, 6A7, 6ABG, 6AB7, 6AB8, 6AC7, 6AG5, 6AK5, 6AL5, 6AM6, 6AQ5, 6AT6, 6AV6, 6B7, 6BBG, 6BBGT, 6BA6, 6BE6, 6BG6G, 6BH6, 6BJ6, 6BQ7A, 6BR7, 6BS7, 6BW6, 6BW7, 6BX6, 6C4, 6CSG, 6C6, 6CB) and other parts like resistors, capacitors, and diodes.

NEW MULLARD AMPLIFIER BOOK.

HOW TO BUILD THE LATEST DESIGNS, 9/3d. post free.

VOLUME CONTROLS

All with Long Spindle and Double-pole Switch, 4/6 each. 10K 25 K 50 K 100 K 1/4 mg. 1/2 mg. 1 meg. 2 meg

DRM1B 13/- RM-1 5/3
DRM2B 15/6 RMF-2 7/6
DRM3B 15/6 RM-3 7/9
LW7 2/11 RM-4 19/-
RM-0 7/11 RM-5 14/-

METAL RECTIFIERS

Full List with ratings free for S.A.E. 14B130 35/- 14RA 1-2-8-3 21/-
14B261 11/6 (FC31)
14RA 1-2-8-2 17/6 16RD 2-2-8-1 12/-
14A100 27/- (FC10) 16RE 2-1-8-1 8/6
14A124 28/- 16RC 1-1-16-1 8/6

CONDENSERS

32 mfd., 350 v. 2/6
200 mfd., 275 v. 4/-
100x200 mfd., 275 v. 9/6
Wire-ended tubular 32 mfd., 450 v. 3/9


8 x 8 mfd., 450 v. 3/-
16 x 16 mfd., 450 v. 4/-
32 x 32 mfd., 350 v. 4/-
8 x 16 mfd., 450 v. 3/9

Standard Can 8 x 8 mfd., 400 v. 3/6
60 x 250 mfd., 275 v. 9/6
100x400 mfd., 275 v. 12/6
100 mfd., 275 v. 3/-
Post/Packing Charge 6d. per item. Orders over £3 post free. C.O.D. 2/6 extra. Full List, with Terms of Business, 6d. Any parcel insured against damage in transit for only 6d. extra. Shop Hours 8.30-5.30. Early Closing Saturday.

POLICE - AIRCRAFT - HAM RECEIVER 1392

15 VALVE SUPERHET. Frequency 95-150 Mc/s (2 to 3 metres). Valve line up: 1st and 2nd R.F. amp. VR.136 (EF.54), 1st Local Oscillator VR.65 (SP.61), 2 Oscillator Multipliers VR.136 (EF.54), 3 I.F. Amp. VR.53 (EF.39), A.G.C. 6Q7, Output 6J5, Muting VR.92 (EA.50), Noise Limiter VR.92 (EA.50), B.F.O. 6J7, Mixer VR.136 (EF.54), De Mod. 6Q7. Slow motion tuning, normally crystal controlled, or tuneable over 95-150 Mc/s. Power supply required: 240-250 volts at 80 mA, 6.3 volts at 4 amps. Size 19 x 10 x 10in. Standard Rack Mounting.

PRICE COMPLETE
ONLY
£65.0
Carriage 15/-

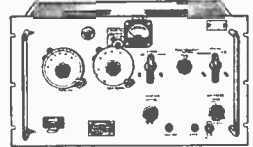

LIGHT-WEIGHT HEAD-SET. These H.S. 30 phones are the smallest used by the U.S. Air Force 2500 Imp. using soft rubber miniature ear moulds for maximum music and voice reproduction of the finest quality. Supplied free is a small transformer unit with cord and plug which steps impedance up to 4,000Ω. ONLY 15/- P. & P. 2/6.

POCKET MULTI-METER. BRAND NEW. 2,500 Ω p.p.v. Multi range: 6/30/120/300/1,200 v. A.C., ditto D.C. 0-1K, 0-1 megohm; 400 Micro-A., 12 mA, 300 mA—0 to +64 db 5-ranges; 3in. x 4in. x 1in. Large clear dial. Leads supplied. Our Price 70/- p.&p. 2/6.

MICROPHONES. BRAND NEW. Throat magnetic 4/6; Throat carbon 3/6; No. 8 carbon with switch 8/6; No. 7 moving coil 6/6; Tannoy power mikes only 5/-. Crystal mike 22/6.

COSSOR OSCILLOSCOPE. A truly magnificent first grade L.F. oscilloscope incorporating a hard valve time base, speeds 1-5-40 milliseconds, easily extended for a few shillings to 3 c.p.s. to 30 k.c.s. speeds. Has high-class amplifier with fine and coarse gain controls. Brightness and focus controls, X and Y shifts. 115 v. and 230 v. Mains power pack fully fuse protected. Empyis 21in. tube ACE 10 size 19in. x 7in. x 12in. Only 20 in stock so first come first served. Genuinely cost £59 each, our price £12.10.0. Carr. 15/-.

MORSE CODE SET. High frequency buzzer. Provision for Headphones. Complete with morse code alphabet and battery. Only 10/6. P. & P. 1/6. Sensitive earphone 3/6 extra.

POCKET VOLT TEST METER. Two D.C. ranges: 0-250 v. and 0-25 v. Complete with test prods. and leather case. Very limited quantity. Only 12/6. P. & P. 1/6.



Complete station (as illus.) comprising: 19 Set, Supply Unit, Control Box, Headphones, Microphone, Morse Key, Variometer, Short Wave and V.H.F. Aerials and Bases and full set of leads. All for only £9. Carr. 25/-.

TWO TRANSISTOR POCKET RADIO with Miniature Speaker

Anyone can build it!

This powerful pocket radio gives reception over the entire broadcast band. Complete with all parts, including 2 transistors, exclusive ferrite rod, miniature speaker tuning condenser, plastic case, wiring diagram, and step by step instructions. Size 4 1/2 x 1 1/2 x 3ins. P. & P. 1/6. Battery 1/- extra. ONLY 27/6.



PORTABLE TRANS-RECEIVER SETS Consisting of trans receiver covering 7-9 Mc/s, range up to 10 miles, complete with 5 valves, headphones, microphone, junction box and 6ft. telescopic aerial. Only requires 120 v. and 3 v. dry battery.

ONLY **60/-** Per Set. P. & P. 4/- Batteries 20/- per Set.



TWO FOR £6 Post Free.

R.F. CONVERTERS R.F. 24 covers 20-30 Mc/s, switched tuning 22/6. R.F. 27 covers 65-85 Mc/s, variable tuning 29/6. Circuits supplied. P. & P. 3/6 on each.

VARIABLE TRANSFORMERS

Input voltage 230 v., continuously variable output from 0-230 v. These variable transformers are of advanced mechanical design offering long life, moderate temperature rise, high efficiency and linear output voltage. Direct-reading dial with large white numerals for accurate output voltage selections. Supplied complete. Model B.5 Current rating 5 amps. £9.00 Model B.10 Current rating 10 amps. £18.5.0 Model B.20 Current rating 20 amps. £32.10.0



ALL FULLY GUARANTEED

ACCUMULATORS. 2 volts 16 A.H. (unspillable). Ideal for 6 and 12 volts supply, etc. Brand new. Original cartons. Size 4in. x 7in. x 2in. 5/6 each. P. & P. 1/6. 3 for 15/-. P. & P. 3/6. 6 for 27/6. P. & P. 5/-.

T.C.S. RECEIVER. 1.5 to 12 Mc/s. 7-valve superhet, built like a dream. Panel controls: R.F. Gain, A.F. Gain, C.W. Pitch, band-switch, mod.-C.W. switch, power switch, ground and aerial posts, M.C. or crystal frequency switch, speaker jack, card holder to log 30 stations, hand vernier tuning knob turning a large etched calibrated plate behind half lined window, anti-backlash gears used. Used condition. £8.10.0. Carriage 15/-.

U.S.A. WHIP AERIALS. 12ft. 12/6. P. & P. 2/6. 1 mA. METER, 2in. round, 17/6. P. & P. 1/6.

CRYSTAL DIODES 6/- per doz. P. & P. 1/-.

PORTABLE TRANS-RECEIVER No. 18. A self-contained Trans/Receiver for Telephone and C.W. Range approx. 10 miles. Freq.: 6-9 Mc/s (50-33.3 metres). Valve line-up: 3 A1P-12, 2 AR-8, 1 ATP4. Complete with aerial, H.T. and L.T. meter and all accessories. Weight 2 lb. Size 8 x 10 x 17in. Only 80/- Carr. 10/-.

COMPLETE HEADPHONE & MICROPHONE ASSEMBLY A must for every Constructor and "Ham", consists of moving coil, padded headphones, "press to talk" microphone. 10/- P. & P. 3/6.

SPARE VALVE KIT Here's a gift for all 38 and 19 Set owners! Case containing 4 ARP12 & 1 ATP4 valves. Only 10/- P. & P. 2/6.



WIRELESS SET No. 19. MK. II.

This most famous Army Trans/Receiver covers 2-8 Mc/s. (150-37 metres) in two bands and 230-240 Mc/s. V.H.F. Has an intercom. amplifier. Designed for 12 and 24 volt operation. Uses a 6-valve superhet receiver, I.F. being 465 kcs., and a 6-volt transmitter designed for voice and C.W. operation. Incorporates test and tuning meter for voltages, aerial loading and current tests. Panel Controls: Frequency tuning, P.A. tuning, Gain control, M.C.W., C.W., R.T. switch. Het-tone, netting, off-on, Quench, aerial—A.V.C.—L.T.—H.T.—Drive tests. Supplied complete with 15 valves and instruction book.

SET ONLY **65/-** Carr. 10/-



Callers: 87 Tottenham Court Road, London, W.1
Mail Orders: (Dept. P) 32a Coptic Street, London W.C.1
Telephone: MUSEUM 9607

FULLY ILLUS. CATALOGUE 1/3 Post Free.

Stern's fidelity

TAPE RECORDERS



All prices quoted provide for the COMPLETE RECORDER including CRYSTAL MICROPHONE and 1,200 ft. Spool of Tape.

There are no better value for money Tape Recorders on the market—if you can't call and hear them, send S.A.E. for fully descriptive leaflets.

Each Model incorporates the highly successful HF/TR3 Amplifier (described opposite) thus ensuring truly "Hi-Fi" record and playback facilities.

**BEFORE YOU BUY
—YOU SHOULD
HEAR THESE**

**RECORDERS. THEY ARE COMPARABLE
TO THE MUCH HIGHER-PRICED MODELS**

MODEL CR3/S Incorporates the New COLLARO "STUDIO" TWIN TRACK 3-speed Deck H.P. Terms: Deposit £7.18.0 and 12 months of £2.17.11 **£39.10.0**

MODEL CR3/T Incorporates the very popular 3-speed COLLARO Mk. IV "TRANSCRIPTOR" Deck which has both upper and lower tape tracks. H.P. Terms: Deposit £9.10.0 and 12 months of £3.9.8. **£47.10.0**

MODEL TR3/Mk. VI Incorporates the New £49.10.0 TRUVOX Mk. VI TWIN TRACK 2-speed Tape Deck H.P. Terms: Deposit £9.18.0 and 12 months of £3.12.7.

TAPE AMPLIFIERS and PRE-AMPLIFIERS PRESENTED FROM MULLARD DESIGNS

MODEL HF/G2A-D

A complete self-contained Tape Recorder chassis incorporating Loudspeaker and comprising the Model HF/G2A Amplifier connected to the Garrard Tape Deck. Operates at 3in./sec. speed and supplied fully tested and ready for immediate operation, designed for easy fixing into a portable case or cabinet, only four fixing screws being required. **£25.0.0** (Including a 4in. spool of Long Play Tape.) Terms, Dep. £5.0.0, 12 months £11.6.8.

Alternatively we offer Complete Kit of Parts to build the HF/G2A Amplifier with the ASSEMBLED AND TESTED GARRARD TAPE DECK for **£22.0.0**

Deposit £4.8.0, 12 months £11.2.3.

The Model HF/G2A is available separately for

(a) COMPLETE KIT OF PARTS **£11.0.0**

(b) ASSEMBLED **£12.15.0**

MODEL HF/TR3 TAPE AMPLIFIER


(Mullard Type "A" design)

A very high quality Amplifier incorporating 3-speed treble equalisation using the latest FERROXUBE POT CORE

INDUCTOR, FOR COLLARO-TRUVOX-BRENELL-WEARITE or MOTEK Tape Decks.

Has GILSEN Output Transformer includes separate Power Supply Unit.

KIT OF PARTS **£12.15.0**

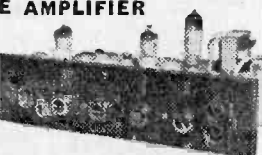

OR ASSEMBLED **£16.10.0**
H.P. Deposit £3.6.6 and 12 months at £11.4.2.

FOR THE HOME CONSTRUCTOR

SPECIAL 'COMBINED ORDER' PRICES


- (a) The COLLARO "STUDIO" TAPE DECK and our Mullard Type "C" PRE-AMPLIFIER and Power Unit Assembled and Tested. **£29.10.0**
- (b) As above but TYPE "C" PRE-AMPLIFIER supplied as complete KIT OF PARTS. **£26.10.0**
- (c) The COLLARO Mk. IV TAPE DECK and the MULLARD TYPE "C" PRE-AMPLIFIER and Power Unit assembled, tested. **£35.0.0**
- (d) As (c) but Type "C" as COMPLETE KIT OF PARTS. **£32.0.0**
- (e) The TRUVOX Mk. VI DECK and the assembled Type "C" Pre-amplifier and Power Unit. H.P. Deposit £3.0.0, and 12 months £2.18.8. **£40.0.0**
- (f) As above but Type "C" as complete KIT OF PARTS. **£36.10.0**
- (g) The BRENELL Mk. V DECK and the assembled Type "C" Pre-amplifier and Power Unit. H.P. Deposit £9.4.0, and 12 months £3.7.8. **£46.0.0**
- (h) As (g) but Type "C" as complete KIT OF PARTS. **£43.0.0**
- (i) THE WEARITE 4A DECK with TYPE "C" assembled and tested. H.P. Deposit £11.4.0, and 12 months £4.2.1. (Carriage and Insurance on above quotes 10% extra.) **£56.0.0**

ALL THE ABOVE CAN BE SUPPLIED IN A PORTABLE CASE FOR £5.10.0 extra. THUS FORMING A COMPLETE PORTABLE PRE-AMPLIFIER.

FULLY DESCRIPTIVE LEAFLETS ON ALL OF ABOVE ARE AVAILABLE—BUT PLEASE ENCLOSE S.A.E. AND STATE WHICH LEAFLET IS REQUIRED.

MODEL HF/G2P-D

THE IDEAL "LINK" TO ADD FULL TAPE RECORDING FACILITIES TO HIGH QUALITY HOME INSTALLATIONS. RADIOGRAMS, etc. Comprises the HF/G2P Tape Pre-amplifier fitted to the Garrard Tape Deck, operates at 3in./sec. speed, connects into the tape input channel or pick-up sockets of existing Amplifier or Chassis. COMPLETE WORKING UNIT, containing 4in. spool of Long Play Tape. PRICE **£23.15.0** Terms, Dep. £4.15.0, 12 months £11.4.10.

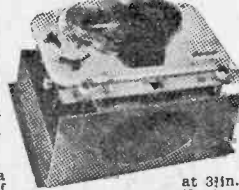

Alternatively we offer Complete Kit of Parts to build the HF/G2P Pre-amplifier with the ASSEMBLED AND TESTED GARRARD TAPE DECK for **£20.15.0**

separately for the ASSEMBLED AND TESTED GARRARD TAPE DECK for **£20.15.0**, 12 months £11.0.5.



PRICE **£29.15.0**

The Pre-amplifier Model HF/G2P is available separately for (a) Complete Kit of Parts **£9.10.0**, (b) Assembled **£11.5.0**.

MULLARD TYPE "C" TAPE PRE-AMPLIFIER—ERASE UNIT

The "Hi-Fi" link to add full tape recording facilities to High Fidelity home installations. Incorporates FERROXUBE POT

CORE PUSH FULL OSCILLATOR and 3-speed treble equalisation by FERROXUBE POT CORE INDUCTOR, FOR WEARITE-COLLARO-TRUVOX-BRENELL or MOTEK TAPE DECKS.

Includes separate power Supply Unit. OR ASSEMBLED KIT OF PARTS **£14.0.0**

H.P. Deposit £3.8.0 and 12 months £1.4.11

(Excluding power unit £11.15.0 and £14.10.0 respectively).



- (a) COMPLETE KIT to build the HF/TR3 Amplifier, together with the COLLARO "STUDIO" DECK, ASSEMBLED AND TESTED. **£25.10.0**
- (b) As above but with HF/TR3 supplied ASSEMBLED and TESTED. **£29.0.0**
- (c) COMPLETE KIT to build the HF/TR3, together with the Mk. IV COLLARO "TRANSCRIPTOR" TAPE DECK. H.P. Deposit £5.16.0, and 12 months £2.2.6. **£30.15.0**
- (d) As above but HF/TR3 supplied ASSEMBLED and TESTED. **£34.10.0**
- (e) COMPLETE KIT to build the HF/TR3, together with the NEW TRUVOX Mk. VI TAPE DECK. H.P. Deposit £7.0.0, and 12 months £2.10.5. **£36.0.0**
- (f) As above but HF/TR3 supplied ASSEMBLED and TESTED. **£39.10.0**
- (g) COMPLETE KIT to build the HF/TR3 AMPLIFIER with the BRENELL Mk. V TAPE DECK. H.P. Deposit £7.18.0, and 12 months £2.17.11. **£41.10.0**
- (h) As above but HF/TR3 supplied ASSEMBLED and TESTED. **£45.0.0**
- (i) H.P. Deposit £9.0.0, and 12 months £3.6.0. **£55.0.0**
- (j) THE WEARITE 4A DECK with assembled and tested HF/TR3 Amplifier including WEARITE Head Lift Transformer. H.P. Deposit £11.0.0, and 12 months £4.0.8. **£56.0.0**
- Carriage and Insurance on each above is 10% extra. Attractive PORTABLE CASE is available to accommodate the TRUVOX or COLLARO TAPE DECKS and we offer it, together with ROLA/CELESTION 10 x 8in. LOUDSPEAKER—ACOS CRYSTAL MICROPHONE—and 1,200ft. SPOOL E.M.I. TAPE—ALL FOR £9.10.0. Carriage and Insurance 5% extra.

STERN RADIO LTD.

STERN'S MULLARD DESIGNS

Designed by MULLARD—presented by STERN'S strictly to specification

COMPLETE KIT OF PARTS— MULLARD "5-10" MAIN AMPLIFIER

For use with the MULLARD 2-valve pre-amplifier with which is undistorted power output of up to 10 watts is obtained. We supply SPECIFIED COMPONENTS AND NEW MULLARD VALVES, including PARMKO MAINS TRANSFORMER and choice of the latest Ultra-Linear PARMKO or the PARTRIDGE Output Transformer. PRICE COMPLETE KIT (PARMEKO Output Trans.) **£10.00**

Alternatively we supply ASSEMBLED and TESTED **£11.10.0**

ABOVE INCORPORATING PARTRIDGE OUTPUT TRANSFORMER, **£1.6.0 EXTRA**



MULLARD'S PRE-AMPLIFIER TONE CONTROL UNIT

Employing two EF86 valves, and designed to operate with the MULLARD MAIN AMPLIFIERS, but also perfectly suitable for other makes.

PRICE COMPLETE **£6.6.0** ASSEMBLED AND TESTED **£8.0.0**

KITS OF PARTS

Supplied strictly to MULLARD'S SPECIFICATION and incorporating:

- Equalisation for the latest R.I.A.A. characteristics.
- Input for Crystal Pick-ups, and variable reluctance magnetic types.
- Input (a) Direct from High Imp. Tape Head (b) From a Tape Amplifier or Pre-amplifier.
- Sensitive Microphone Channel. ● Wide range BASS and TREBLE Controls.



COMPLETE MULLARD "5-10" AMPLIFIER

The popular and very successful complete "5-10" incorporating Control Unit providing up to 10 watts high quality reproduction. Only Specified Components and new MULLARD VALVES are supplied including PARMKO MAINS TRANSFORMERS and choice of the latest PARMKO or PARTRIDGE ULTRA-Linear Output Transformers.


KIT OF PARTS **£11.10.0** OR ASSEMBLED and TESTED **£13.10.0**

HIRE PURCHASE (Assembled Amp. only). DEPOSIT **£2.14.0** 12 months at 19/10. ABOVE INCORPORATING PARTRIDGE OUTPUT TRANS. **£1.6.0 extra.**



COMPLETE MULLARD "3-3"

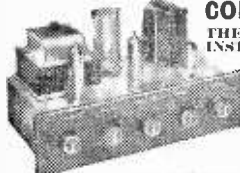THE IDEAL AMPLIFIER FOR A SMALL HIGH QUALITY INSTALLATION PROVIDING EXCELLENT REPRODUCTION OF UP TO 3 WATTS OUTPUT. COMPLETE KIT **£7.10.0** OR ASSEMBLED and TESTED **£8.19.6** (plus 6/6 carriage and insurance) H.P. Terms: Deposit **£2.0.0** and 8 Months at **£1.0.0**. Complete to MULLARD'S SPECIFICATION including Mullard valves and a PARMKO OUTPUT TRANSFORMER.



STEREO "3-3" MAIN AMPLIFIER

Comprises two MULLARD 3-3 Main Amplifiers on one chassis. Operates with MULLARD STEREO PRE-AMPLIFIER. Output power 6 watts. Inputs for Crystal Pick-up and Radio Tuner.

KIT OF PARTS **£10.0.0** OR ASSEMBLED **£11.15.0**

COMPLETE STEREO AMPLIFIER

Meets the many requests for a low priced but good quality Stereophonic Amplifier. Output power is 4 watts and suitable for Crystal Pick-ups.

KIT OF PARTS **£8.10.0** OR ASSEMBLED **£10.10.0**

!! RECORD PLAYERS !!

THE LATEST MODELS ARE IN STOCK, MANY AT REDUCED PRICES

SEND S.A.E. FOR ILLUSTRATED LEAFLET
B.S.R. MONARCH A8 4-speed mixer Autochanger with Crystal Pick-up **£6.19.6**

THE NEW COLLARO MODEL RP594 4-speed Single Record Player. Studio Cartridge. **£9.18.9**

THE COLLARO "CONQUEST" 4-speed Autochanger Studio Pick-up. **£7.10.0**

THE COLLARO 4-speed Single Record Player. Studio Pick-up. **£6.9.6**

THE NEW B.S.R. Model UA12 in Stock. A4 "SPEED" MIXER AUTOCHANGER. **£8.7.6**

UA12 also available incorporating the B.S.R. STEREO Pick-up, plays L.P. and 78 Records. **£10.10.0**

GARRARD MODEL TA/Mk.II 4-speed Player fitted high output Crystal Pick-up. **£8.10.0**

GARRARD MODEL RC/210. Autochanger 4 speeds. High output. Crystal Pick-up. **£10.10.0**

Carriage and Insurance on each above, 5/- extra.

H.P. TERMS AVAILABLE ON EQUIPMENT OVER £9. DESCRIPTIVE LEAFLETS AVAILABLE FOR ALL EQUIPMENT. PLEASE SEND S.A.E.

Dept. P.W. 109 FLEET ST., LONDON, E.C.4

Telephone: FLEET STREET 5812/3/4

PRICE REDUCTIONS

(a) The KIT OF PARTS to build both the "5-10" Main Amplifier and the 2-valve PRE-AMP CONTROL UNIT. **£15.15.0**

(b) The "5-10" and the 2-stage PRE-AMP both ASSEMBLED and TESTED H.P. Dep. **£3.16.0** and 12 months of **£1.7.8**. **£18.18.0**

(c) The KIT OF PARTS to build the DUAL-CHANNEL "3-3" AMPLIFIER and the DUAL-CHANNEL PRE-AMPLIFIER CONTROL UNIT. **£21.10.0**

(d) The DUAL-CHANNEL "3-3" AMPLIFIER and the DUAL-CHANNEL PRE-AMPLIFIER CONTROL UNIT BOTH ASSEMBLED and TESTED **£25.0.0**

H.P. Terms: Deposit **£5** and 12 months of **£1.16.8**.

(e) THE KIT OF PARTS to build one "5-10" MAIN CHANNEL and the DUAL-CHANNEL PRE-AMP CONTROL UNIT. **£21.10.0**

(f) ONE "5-10" AMPLIFIER and the DUAL-CHANNEL PRE-AMPLIFIER both ASSEMBLED and TESTED **£25.0.0**

H.P. Terms: Deposit **£5**, 12 months of **£1.16.8**.

(g) KIT OF PARTS to build two "5-10" MAIN AMPLIFIERS (incorporating Parmeko Output Transformers) and the DUAL-CHANNEL PRE-AMPLIFIER CONTROL UNIT. **£31.0.0**

(h) TWO "5-10" AMPLIFIERS and the DUAL-CHANNEL PRE-AMPLIFIER CONTROL UNIT BOTH ASSEMBLED & TESTED **£36.0.0**

H.P. Terms: Deposit **£7.4.0**, 12 months **£2.12.0**.

Carriage and Insurance 7/6 extra. Prices quoted are subject to **£1.6.0** extra for Partridge Transformer.

STEREO DUAL CHANNEL PRE-AMPLIFIER



This model incorporates two Mullard 2-valve Pre-Amplifiers combined into a Single Unit, enabling it to be used for both STEREO-PHONIC or MONAURAL operation. It is designed primarily to operate with our range of MULLARD MAIN AMPLIFIERS but will also operate equally well with any make of Amplifiers requiring an input of 250 mVols.

COMPLETE KIT **£12.10.0** ASSEMBLED AND TESTED **£15.0.0**

OF PARTS H.P. £3 Dep. and 12 mths. at **£1.2.0**

MULLARD FOUR CHANNEL MIXER UNIT

Will be available late September, both as COMPLETE KIT OF PARTS and as ASSEMBLED and TESTED UNIT.

Incorporates two input channels for Microphones, one for Crystal Pick-up and a fourth for Tape or Radio.

FULLY DESCRIPTIVE LEAFLET AND PRICES available late September.

Mk.II "Fidelity" FM TUNING UNIT

An attractively presented Unit incorporating MULLARD PERMEABILITY TUNING HEART and corresponding Mullard valve line up. FOR THE CONSTRUCTOR **£10.10.0** ASSEMBLED **£14.5.0**

A SPECIAL CASH OFFER !!

This very attractive PORTABLE AMPLIFIER CASE together with a good quality GRAM AMPLIFIER and a matched P.M. SPEAKER. ALL for ONLY **£8.7.6** (Plus 7/6 Carr. & Ins.)

The Amplifier consists of a 2-stage design incorporating 3 modern B.V. valves and has separate BASS and TREBLE CONTROLS.

The Portable Case will also accommodate almost any make of Autochanger and is attractively finished in Mushroom Grey Rexine. WE ALSO SUPPLY SEPARATELY:

(a) The 2-stage (plus Rectifier) AMPLIFIER **£4.2.6**

(b) The PORTABLE CARRYING CASE **£3.17.6**

(c) 6in. P.M. SPEAKER 18/9 Carriage and Insurance 4/- extra.



FURTHER HUGE PURCHASES DIRECT FROM SOURCE

13 CHANNEL TV'S

TABLE MODELS, FAMOUS MAKERS. Complete with all valves and tubes. Unequaled in value. They are untested and not guaranteed to be working order.

AMAZINGLY POPULAR IDEAL SECOND SETS

- 12" - £3.19. (p. & p.) 12/6
14" - £6.19. (p. & p.) 15/-
17" - £9.19. (p. & p.) 17/6
12" 5 CHANNEL TV'S 45/- (p. & p.) 13/6
14" 5 CHANNEL TV'S 85/- (p. & p.) 19/6

TUBES DIRECT FROM OUR FACTORY

Due to the increasing demand for our wide range of C.R.T.S. and our efficient handling methods we offer unbeatable value.

REGUNDED TUBES have new Guns, Getters, Aquadag Coating, Bases, etc. TOP QUALITY GUARANTEED

Table with columns for 6 MONTHS REVACUUMED, 12 MONTHS REGUNDED, and 18 MONTHS BRAND NEW TYPES. Lists various tube models like 6X4, 6X5, 6X6, etc. with prices.

Record Players Carriage 4/-
COLLAR CONQUEST 4-speed 4/546... £5 19 0
EMI 4-speed Stereo... £8 19 0
B.S.R. (A14) AUTOCHANGERS... £7 19 0
B.S.R. (U8) AUTOCHANGERS... £8 15 0
GARRARD R120D MK11... £9 7 6

4-SPD. RECORD PLAYERS
Latest B.S.R. T10 Turntable, together with lightweight Starr Galaxy dual sapphire crystal turnover pick-up head. Truly amazing value £3.10.0

External/Internal ITV Converters with power pack
Hammered finish. Very compact. Gain and Trimming controls. Listed at £7.7. Carriage 2/6. OUR PRICE 39/-

TRANSISTORS
REDSPOT Now Only 3/6. WHITE SPOT 4/8
DIODES General purpose, famous make, 8d. 8/- doz. GEX44 type, 3/9.

SPECIAL OFFERS

- U8 Stereo Changers R.S.R. famous Monarch autochangers, fitted with quality stereo cartridge. Truly amazing value £5.19.0
MAINS AMPLIFIERS 3 valve (10F3, 10F14, U19), 3 watt x in. sound-speaker, in two tone cases with controls. Ideal for record players, P.A. work, etc. 49/-
Loudspeakers TOP MAKES—MANUFACTURER FRESH
2 1/2in., 1 1/2"; 8in., 1 1/2"; 3 1/2in., 1 1/2"; 5in., 1 1/2"; 8in., 1 1/2"; 8in., 2 1/2"; 10in., 2 1/2"; 12in., 2 1/2"; 7 x 4in. elliptical, 1 1/2"; 9 x 4in. elliptical, 2 1/2"; 10 x 4in. elliptical, 2 1/2"; 8in. Stentorian 3.75-15 ohms HF1012, 99/8; 12in. Closed Field, 27/6. STOP PRESS—4 x 12in. HI-FI speakers, 49/-
PM SPEAKERS Surplus 3 ohm Tested, top makes, performance guaranteed. 6in. 9/- 5in. 11/- 7X4 13/- 10in.

RECTIFIERS

- For Chargers, selenium, full wave, 12 volt, 3-4 amp. 9/6; (Carr 1 1/2); 250 v. no. wa., 5/-; RM1, 6/8; RM2, 8/-; RM3, 9/-; RM4, 15/8; RM5, 21/-; 14A50 17/-; 14A97, 22/-; 14A100, 25/-; 16RC1-1/16-1, 7/9; 18RA1-1/16-1, 7/9; 18RD2-2-8-1, 14/-; 14RA1-2-8-2 17/-; 14RA1-2-8-3, 20/-
100 RESISTORS 6/6
100 CONDENSERS 10/-
Miniature Ceramic and Silver Mica Condensers. 3 pF to 10,000 pF. LIST VALUE OVER 25. VALVES ALL GUARANTEED 3 MONTHS
PL81 SOILED 4/6 EY51 SHORT ENDS 4/6
4 Transistor Amplifiers ONE WATT—From a single 6v. all-day battery. Latest 6ET15 Power Transistor. In PUSH-PULL Two-Transistor, High Gain pre-amplifier stages. Output 3 Ohms. £3.19.0
1 Watt Transistor Stage 6V of 6ET15 1 watt Power Transistors (listed 50/-). PUSH-PULL INPUT AND OUTPUT TRANSFORMERS, 4 Transistor Amplifier circuit. 45/-

VALVES BY RETURN OF POST

10% DISCOUNT SPECIAL OFFER TO PURCHASERS
of any SIX VALVES marked in black type (10% p. dozen). Post: 1 valve, 6d., 2-11, 1/-.

NEW LOW PRICES GUARANTEED 3 MONTHS

FREE TRANSIT INSURANCE. All valves are new or fully guaranteed ex-Government or ex-military origin. Satisfaction or Money Back Guarantee on goods if returned unused within 14 days.

Large table listing various vacuum tube models and their prices. Columns include model numbers like 6X4, 6X5, 6X6, 6X7, etc., and their corresponding prices.

TECHNICAL TRADING CO.
ALL ITEMS 5% + POST FREE IN DOZENS. (Callers always welcome). LIST OF 1000 SNIPS 6d. P.O. BOX 21 (W) 350-352 FRATTON ROAD, PORTSMOUTH.

THIS MONTH

Don't miss the October issue of these other famous PRACTICALS!

OUT NOW

FREE inside
PRACTICAL HOUSEHOLDER

16-page Colour Booklet

MAKING, FIXING AND FITTING

Packed with do-it-yourself guidance on essential jobs in the home.



OUT SEPT. 22nd

FREE inside
PRACTICAL TELEVISION
(Monthly 1/6d.)

Large size BLUEPRINT
and complete Wiring Diagram for the
'OLYMPIC' 17"
TELEVISION RECEIVER



OUT SEPT. 15th

FREE inside
PRACTICAL MOTORIST

6-in-1 POCKET GUIDE AND CALCULATOR


Includes at-a-glance, erasable sections for Route-Plotting, Servicing Record and Petrol Consumption—plus M.P.G. Ready Reckoner . . . Average Speed Calculator . . . Starting Troubles and their Remedies.

AND 16-PAGE PULLOUT GUIDE "THE BEST USED CAR FOR YOUR MONEY"

MAKE SURE OF YOUR COPIES NOW!

LONDON'S NEW WALK-AROUND "Service with a smile" SHOP!

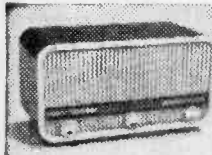ALSO 24 HOURS MAIL-ORDER DESPATCH SERVICE




Only £5.10.0
Build this beautiful "Symphony" radio for only £5.10.0. Sturdy, exceptionally well finished cabinet with horizontal dial. Covers

all medium and long waves. Good selectivity and very good quality reproduction. For A.C. mains 200/250 volts. All high quality parts, gold insert knobs, etc. No knowledge needed—our **SIMPLE CONSTRUCTION ENVELOPE** makes it as easy as A, B, C. All our parts tested. **CAN BE BUILT FOR ONLY £5.10.0** including construction envelope and everything down to the last nut and bolt. Post and packing 4/- extra. C.O.D. 2/6 extra. (Parts sold separately. Components price list 1/-.)

Only £10.19.6

Build this 7-transistor "Majorca" super-het portable with Car Radio aerial attachment. A very high quality design giving exceptionally good tone. Push-pull output. Can be built for only £10.19.6 including **SIMPLE CONSTRUCTION ENVELOPE**, makes construction as easy as A, B, C. Everything down to the last nut and bolt. Post and packing 3/6 extra. C.O.D. 2/6 extra. (Parts sold separately. Components price list 1/-.)

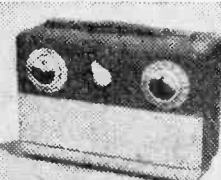

Only 35/-

The "Caronet" 2-transistor radio. Is very sensitive—ideal for Office, Bedroom, Holidays, etc. Fits in the palm of your hand.



Months' and months' listening off a 7d. battery. Can be built for only 35/-, including everything down to the last nut and bolt and our **SIMPLE CONSTRUCTION ENVELOPE** makes it easy as A, B, C. Post and packing 2/- extra. (C.O.D. 2/6 extra.) (Parts sold separately. Components price list 1/-.)



Only £8.17.6 BRAND NEW! the latest 4-speed Autochanger, B.S.R. UA14, as illustrated, few only. Our Price £8.17.6. P.P. 3/6. **BRAND NEW!** the B.S.R. 4-speed Autochanger, UA8, few only left. Our Price £6.19.6. P. & P. 3/6. **BRAND NEW!** the COLLARO Junior 4-speed record player. Our Price 75/- P. & P. 3/6. **BRAND NEW!** COLLARO "Conquest" 4-speed Autochanger. Our Price £7.19.6. P. & P. 3/6.



ONLY 97/6
The famous "Caby" TEST-METER. We recommend these multi-range meters as being accurate and well made. Ranges cover A.C. D.C. and resistance. New in box with test prods and instructional booklet. Our Price 97/6. P. & P. 2/6.

ROBERTS ELECTRONICS OF LONDON (Dept. PW2)

398 HARROW ROAD, LONDON, W.9.
Telephone CUNningham 0323
Open 9.30 a.m. until 6 p.m. including Saturdays.
(We don't close for lunch)

COME AND LOOK AROUND—NO OBLIGATION. WE ALSO OPERATE 24 HOURS MAIL-ORDER SERVICE.

FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?
ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the *B.I.E.T. School of Electronics*, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

We definitely Guarantee "NO PASS—NO FEE"

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £20 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Incorporating E.M.I. Institutes)
(Dept. SE/21), 29 Wright's Lane, London, W.8

WHICH IS YOUR PET SUBJECT?

- Mechanical Eng.
- Electrical Eng.
- Civil Engineering
- Radio Engineering
- Automobile Eng.
- Aeronautical Eng.
- Production Eng.
- Building, Plastics
- Draughtsmanship
- Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

- A.M.I.Mech.E.
- A.M.I.C.E.
- A.M.I.Prod.E.
- A.M.I.M.I.
- L.I.O.B.
- A.F.R.Ae.S.
- Sec.
- A.M.Brit.I.R.E.
- Famity & Guilds
- Gen. Cert. of Education
- Etc., etc.

PRACTICAL EQUIPMENT

Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, Etc..
A.M.Brit.I.R.E. City & Guilds Radio Amateurs' Exam.
R.T.E.B. Certificate
P.M.G. Certificate
Practical Radio
Radio & Television Servicing
Practical Electronics
Electronics Engineering
Automation

INCLUDING TOOLS!

The specialist Electronics Division of *B.I.E.T.* (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T. SCHOOL OF ELECTRONICS



POST COUPON NOW!

■ Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES"
■ (Write if you prefer not to cut page)
■ NAME.....
■ ADDRESS.....
■ SUBJECT OR EXAM THAT INTERESTS ME..... (SE/21)

THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD

EASY AS A.B.C. TO BUILD

The new, exciting De Luxe "Gold Star" Pocket Radio in beautiful moulded plastic case— This model is a highly sensitive, self-contained set covering all medium waves. Uses modern miniature "button-base" valve and specially designed high efficiency coil. Exceptionally easy to build from our step-by-step plans—the case is supplied ready drilled! Size of radio only 4 1/4 in. x 2 1/4 in. x 1 1/4 in.!

37/6



2/- extra. (Parts sold separately, priced parts list 1/6.)



Our engineers have designed a novel Wrist-Watch Radio using latest Transistor Technology. Size only 1 1/4 in. x 1 in. x 1/4 in.!!! — "Feather-weight"—yet gives clear, crisp, personal-phone reception over all medium waves. Tiny battery inside lasts months—costs 5d. No snags, anyone can build it in an hour or two using our pictorial step-by-step simple plans. All parts supplied (including case and strap) for only 29 6 (add 2 6 Post, etc.). C.O.D. 2/- extra. (All parts sold separately, priced parts list 1/6.) Send Now!

Can Be Built for 47 6. Build this exceptionally sensitive high efficiency personal phone radio. Uses unique assembly system and can be built by anyone without any radio knowledge whatever in 45 minutes. Handsome black-crackle steel case with specially made black and gold dial with stations printed. Size of radio only 6 1/4 in. x 5 in. x 3 in. Covers all medium and long waves. H.T. consumption only 1 to 1.5 mA. Ideal for Bedroom, Garden, Holiday, etc. BUILD THE "SKY-ROMA" NOW! Total building cost—everything down to the last nut and bolt, 47 6 (Postage, etc., 2/-) with full set of clear, easy-to-follow plans. (Parts sold separately. Priced parts list and plans 1/6.) C.O.D. 2/- extra.



47/6



The sensational "Silvertone" model! A highly compact self-contained miniature "button-base" valve pocket radio at absolute "rockbottom" building cost! Covers all the medium waves with the very latest circuitry bringing in stations from all over Europe—without fuss. Easy as A.B.C. to assemble, using our step-by-step instruction manual. Size only 4 1/4 in. x 2 1/4 in. x 1 1/4 in.—a fascinating little pocket radio. We can supply all the parts including beautiful two-tone case, detachable aerial, instruction book, screws, wire, etc., for only 29 6 (plus 2/- post and packing). C.O.D. 2/- extra. (Parts sold separately, priced parts list 1/6.)

29/6

THIS TRANSISTOR SET Can Be Built For Only 29 6. The "Sky-Scout" Pocket two-stage transistor set, size only 1 in. x 3 1/4 in. x 4 1/4 in. Covers all medium waves and works entirely off tiny "penlight" battery which costs 6d, and fits inside case. All parts tested before despatch. Can be built for 29 6, plus 2/- Post and Packing. INCLUDING CASE, TRANSISTOR, STEP-BY-STEP PLANS FOR ABSOLUTE BEGINNERS, nuts, bolts, etc. (C.O.D. 2/- extra.) Parts sold separately, priced parts list and plans 1 6. VERY SIMPLE TO BUILD.

29/6



This amazing "Tiny-Tim" model—no larger than a match box—costs nothing to run—ever! No batteries! No Valves! No complete electricity! Will never run down or burn out. Uses the latest TRANSISTOR TYPE GERMANIUM DIODE, receives local stations anywhere—without extra aerial. Clear, Crisp Tone. No snags, anyone can build it within an hour using our step-by-step instruction book, etc., for only 17 6, plus 2/- Post and Packing (C.O.D. 2/- extra). (Parts sold separately, priced parts list 1 6.)

17/6

Anyone can build this beautiful precision Pocket Radio in an hour or two. No knowledge whatever needed. Our simple pictorial plans take you step-by-step! Remarkably sensitive—covers all medium waves. Inc. Luxembourg, Home Light. Size only 2 1/4 in. x 3 in. x 5 1/4 in.—Not a Toy! But a Real, Personal-phone, Valve Radio with Detachable Aerial! IDEAL FOR BEDROOM, GARDEN, etc. We supply ALL parts necessary, together with plans, etc., for the special price of 39 6, plus 2/6 post and packing. (C.O.D. 2/- extra.) BUILD YOURS NOW! (All parts sold separately, priced parts list 1/6.) Send Today! Money refunded if parts returned intact within 7 days.

39/6


Choice of beautiful walnut veneered cabinet or Ivory bakelite. This is the lowest possible price consistent with high quality. No radio knowledge whatever needed... can be built by anyone in 2-3 hours, using our very simple, easy-to-follow diagrams. The terrific new circuit of the "Ocean-Hopper" covers all medium and long waves, has razor-edge selectivity and exceptionally good tone. Price also includes ready drilled and punched chassis, set of simple-to-follow plans—in fact everything! Parts tested before despatch! Uses standard octal-base valves. (Low running costs—approximately 18 watts.) Size 12 in. x 6 in x 5 in. Build this long-range powerful midjet NOW. TOTAL BUILDING COST INCLUDING PLANS, P.C. 25 7 6. (Post and Packing 3/6). Parts sold separately. Priced parts list and plans 1/6. C.O.D. 2/- extra.

107/6



under 7 ozs.—yet it is a THREE-STAGE receiver covering all medium waves, working entirely off a "penlight" battery. Every part tested before despatch! SPECIAL STEP-BY-STEP PLANS FOR ABSOLUTE BEGINNERS. Total building cost including case, transistors, etc.—everything down to the last nut and bolt—ONLY 45/- with plans. Postage, etc. 2/- (C.O.D. 2/- extra.) (Parts sold separately. Priced parts list and plans 1/6.) RUSH YOUR ORDER TODAY!

45/-

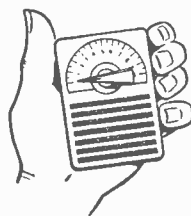

Two-Transistor Pocket Set. Can Be Built for 45/- BUILD THE "SKY-ROMA" NOW! VEST-POCKET TWO TRANSISTOR RADIO which gives a superb performance and is highly sensitive. Weighs under 7 ozs.—yet it is a THREE-STAGE receiver covering all medium waves, working entirely off a "penlight" battery. Every part tested before despatch! SPECIAL STEP-BY-STEP PLANS FOR ABSOLUTE BEGINNERS. Total building cost including case, transistors, etc.—everything down to the last nut and bolt—ONLY 45/- with plans. Postage, etc. 2/- (C.O.D. 2/- extra.) (Parts sold separately. Priced parts list and plans 1/6.) RUSH YOUR ORDER TODAY!

CONCORD ELECTRONICS

210, Church Road, Hove, Sussex

Dept. PW23

Orders receive prompt attention. Cheques accepted. Cash on delivery 2/- extra. Please print name and address in block letters. Suppliers to Schools, Universities, Government and Research Establishments. Complete range of components and valves stocked. Regret no C.O.D. abroad. DEMONSTRATIONS DAILY AT WORKS.

Tel: Mitcham 6201

Open Daily to Callers

R S T

All Valves Brand New
and Fully Guaranteed

211 STREATHAM ROAD, MITCHAM, SURREY

Special 24 Hour Express Mail Order Service

0Z4	5/9	6CH6	12/-	10C2	27/10	32	13/6	CCH35	21/-	ECL83	12/6	HL23DD		PCL82	11/6	U251	17/6	
1A5	6/-	6ESGT	10/-	10F1	26/2	35A5	10/6	CL4	12/6	ECH82	12/6		10/6	PCL83	12/6	U281	20/-	
1A7	14/6	6F1	15/6	10F3	17/6	35L6GT	10/6	CL33	18/6	EF9	21/-	HL41	12/6	PEN4A	17/6	U282	22/-	
1D5	14/-	6F6	6/9	10F9	12/6	35W4	8/-	CY1	15/9	EF22	17/6	HL41DD		PEN4A	17/6	U301	22/6	
1D6	10/-	6F7	15/-	10LD3	12/6	35Z3	10/-	CY31	15/9	EF36	7/6		13/6	PEN4D		U329	17/6	
1H5	10/6	6F12	4/9	10LD11	15/-	35Z4	7/6	D41	12/6	EF37	8/6	HL42DD			22/6	U339	19/-	
1L4	6/-	6F13	17/6	10P13	21/-	35Z5	9/6	D42	12/6	EF37A	8/6		13/6	PL33	18/6	U403	11/6	
1LN5	4/6	6F14	17/6	10P14	20/-	40SUA	15/-	D63	3/6	EF39	5/-	HY90	8/-	PL38	23/9	U404	10/-	
1N5	10/6	6F15	14/9	11D3	17/6	41STH	23/6	D77	5/6	EF40	15/-	IW4/35010-		PL81	14/9	U801	29/-	
1R5	9/-	6F17	12/-	11D5	17/6	42	15/-	D152	4/-	EF41	9/3	IW4/50010-		PL82	8/-	U4020	15/6	
1S4	8/6	6F33	5/6	12A6	6/6	43	15/-	DAC32	10/6	EF42	10/6	KBC32	9/6	PL83	10/6	UABC80	8/-	
1S5	9/-	6H6	2/6	12A8H	10/-	50C5	15/-	DAF91	7/6	EF50(E)	3/6	KF35	8/6	PL820	21/6	UAF42	9/6	
1T4	5/6	6J5GT	4/6	12AT6	9/6	50CD6G		DF33	10/6	EF50(A)	4/-	KL32	10/6	PM2A	12/6	UB41	9/6	
1T5	10/6	6J6	7/6	12AT7	8/-	50L6GT	21/-	DF91	5/-	EF80	7/6	KLL32	11/6	PM2HL	14/6	UBC41	9/6	
2D21	10/6	6J7GT	9/6	12A77	9/-	61BT	17/6	DF92	7/-	EF85	6/6	KL35	9/6	PM22A	13/6	UBF80	9/6	
2X2	5/-	6K7G	3/-	12A77	9/-	61SPT	17/6	DF96	9/6	EF86	11/-	KT2	7/6	PM24M	21/6	UBF89	8/6	
3A5	12/6	6K7GT	10/6	12A77	9/6	62BT	17/6	DF97	9/6	EF89	10/-	KT32	10/-			UCC85	10/-	
3D6	14/6	6K8GT	12/6	12BA6	9/-	77	12/6	DH63	10/-	EF91	4/9	KT33C	10/-	PM202	16/-	UCH42	9/-	
3Q4	8/-	6K25	19/6	12BE6	9/6	78	12/6	DH76	7/6	EF92	5/6	KT36	28/6	PY31	16/6	UCH81	9/-	
3Q5	10/6	6L1	15/6	12EJ	17/6	80	12/6	DH77	8/3	EF93	7/6	KT41	22/6	PY32	15/6	UCL52	12/6	
3S4	8/-	6L6	7/6	12J7GT	9/6	88	12/6	DH77	8/3	EF93	7/6	KT44	13/6	PY80	8/6	UCL83	13/6	
3V4	9/-	6L18	12/6	12K7GT	8/6	78	12/6	DH107	13/6	EF95	15/6	KT55	22/6	PY81	7/6	UF41	9/-	
5R4GT	9/-	6L19	21/-	12K8GT	12/6	85A2	12/6	DH719	7/6	EL31	12/6	KT61	18/6	PY82	8/-	UF42	11/6	
5U4G	7/-	6L34	10/-	12Q7GT	8/6	150B2	12/6	DK91	9/-	EL32	5/6	KT63	8/6	PY83	8/6	UF80	9/6	
5V4	9/6	6/30L2	10/-	12S47	8/-	150B3	15/-	DK92	9/6	EL33	12/6	KT66	17/6	PZ30	18/6	UF85	9/-	
5Y3GT	8/6	6LD3	9/6	12SC7	8/-	185BT	32/-	DK96	10/-	EL35	12/6	KT71	9/-	QP25	14/6	UF89	8/6	
5Z3	10/-	6LD20	15/6	12SH7	8/6	303	7/6	DL33	9/-	EL37	18/6	KT74	12/6	QP230	17/6	UL41	9/-	
5Z4G	10/-	6N7GT	7/6	12SH7	4/-	304	7/6	DL35	12/6	EL38	23/9	KT76	12/6	QP21	12/6	UL44	24/6	
6A7	18/6	6M1	10/6	12S7	4/-	305	7/6	DL92	8/6	EL41	10/6	KT101	25/-	R10	21/6	UL46	21/-	
6A8	10/6	6M2	10/6	12SK7	8/-	328	7/6	DL94	9/-	EL42	10/6	KTW61	7/6	R19	19/6	UL84	9/6	
6ABB	9/-	6P1	17/6	12SQ7	11/6	329	7/6	DL96	9/6	EL81	14/9	KTW62	7/6	SD6	8/6	UU6	20/11	
6AJ8	9/6	6P25	19/6	12SN7	17/6	807	7/6	EA50	2/-	EL84	7/-	KTW63	7/6	SP4	14/6	UU7	15/-	
6AK5	8/-	6P28	26/-	12Z3	15/6	955	4/6	EAC90	7/-	EL85	10/6	KTZ41	8/-	SP42	3/6	UUB	26/-	
6AK8	7/6	6Q7GT	10/6	13D3	12/6	5763	7/6	EAC91	7/6	EL90	8/6	KTZ63	10/6	SP61	3/6	UY21	15/6	
6AL5	6/6	6SA7GT	7/6	14H7	12/6	9002	7/6	EAF42	10/-	EL91	5/-	L63	4/9	T41	22/6	UY41	7/6	
6AM1	4/9	6SG7	7/6	14R7	12/6	9003	7/6	EB41	7/6	EM80	10/-	LNJ309	15/-	TDD4	17/6	UY85	7/6	
6AM5	5/6	6SH7	6/6	14S7	21/-	AC4/PEN		EB81	10/-	EM81	10/-	LZ319	12/6	TDD13C		VP28	17/6	
6AN5	7/6	6S17	5/6	15A2	17/6	AC5/PEN	22/6	EB91	5/-	EY81	10/6	MH4	8/6			VP48	17/6	
6AQ5	8/3	6SK7	7/6	15D2	23/9	AC6	21/-	EBF80	9/6	EY84	10/6	MHD4	17/6	TH41	23/9	W17	8/6	
6AQB	9/3	6SL7GT	6/6	19AQ5	10/6	ACTP	32/-	EBF89	9/6	EY91	9/6	MHL	10/-	TP22	17/6	W76	7/-	
6AT6	8/3	6SN7GT	5/6	19B6G24	4/-	ACHL	12/6	EBL21	22/-	EZ35	7/6	MKT4 (57)		TP25	17/6	W81	5/-	
6AU6	10/6	6U4GT	11/6	20D1	12/6	AC/PEN		EBL31	21/6	EZ40	7/6	MS4B	17/6	U14	15/9	W142	9/-	
6B7	10/-	6U5	7/6	20D2	23/6	AC/PEN		EC90	9/6	EZ41	7/6	MSP4	17/6	U16	10/-	W719	7/6	
6B8	4/-	6U7	7/6	20F2	26/6	ACTH1	34/9	EC91	9/6	EZ80	7/6	MU14	9/-	U18,20	10/-	W727	7/6	
6BA6	7/6	6V6G	5/-	20L1	26/6	ACVPI	17/6	ECC31	10/-	EZ81	7/6	MX40	17/6	U22	10/-	X18	11/6	
6BE6	7/6	6V6GT	8/-	20P1	26/-	ACVP2	17/6	ECC32	10/-	EZ90	7/6	N18	8/-	U24	29/6	X61M	21/-	
6BG6G	21/-	6X4	5/-	20P3	23/-	ACVPI	17/6	ECC33	5/-	FC2	21/-	N19	8/-	U25	14/6	X65	23/9	
6BJ6	7/6	6X5GT	5/-	20P5	22/6	ACVPI	17/6	ECC34	15/-	FC13	17/6	N37	18/6	U26	12/6	X66	21/-	
6BR7	15/-	7C5	8/-	25L6GT	9/6	AC2/PEN	21/-	ECC35	8/6	FC13C	21/-	N78	17/6	U31	9/6	X78	21/-	
6BW6	6/6	7C6	8/-	25Y5	10/-	ECC40	21/-	ECC40	21/-	FW4,500		N108	18/-	U33	21/-	X79	21/-	
6BW7	6/6	7D5	15/-	25Z4	10/-	ECC81	8/-	ECC81	8/-	FW4,800		N142	9/6	U35	21/-	Y61	10/6	
6BX6	7/6	7D6	15/-	25Z6	10/6	ECC82	9/6	ECC82	9/6			N147	18/6	U37	25/-	Y63	9/-	
6BY7	7/6	7D8	15/-	27SU	17/6	ECC83	9/6	ECC83	9/6			N150	10/6	U45	21/-	Z21	12/6	
6C4	6/6	7H7	8/-	30	13/6	ECC84	9/6	ECC84	9/6	GZ30	10/6	N153	11/6	U47	21/-	Z63	7/6	
6C5GT	8/6	7K7	10/6	30C1	12/6	ECC85	9/6	ECC85	9/6	GZ32	11/6	N153	11/6	U50	8/6	Z66	19/6	
6C6	6/6	7Q7	11/6	30F5	11/6	ECC91	5/6	ECC91	5/6	GZ34	13/6	N329	10/-	U52	7/6	Z77	4/9	
6C9	12/6	7R7	12/-	30FL1	10/6	ECF80	12/6	ECF80	12/6	H30	5/6	N727	7/6	U76	7/6	Z152	8/6	
6C10	12/6	7S7	10/6	30L1	11/6	ECF82	12/6	ECF82	12/6	H63	9/6	N729	8/-	U78	7/6	Z179	7/6	
6CD6G	27/6	7Y4	7/6	30P4	22/-	ECH21	22/-	ECH21	22/-	HBC90	9/6	P2	10/-	U142	8/-	ZD152	9/6	
6D1	8/-	8D3	5/6	30PI2	11/6	ECH42	10/-	ECH42	10/-	HL92	6/6	PCC84	9/6	U145	15/-			
6D2	5/-	9BW6	14/9	30PI6	11/6	ECH35	9/-	ECH35	9/-	HL13DD	10/-	PCF80	10/6	U147	7/-			
6D3	15/-	10C1	18/-	30PL1	15/-	ECL80	9/-	ECL80	9/-	HL23	12/6	PCF82	9/6	U191	20/-			
						CBL1	17/6	CBL1	17/6									
						CBL31	21/-	CBL31	21/-									

METAL RECTIFIERS

RM1	6/-	18RA	1-1-8-1	4/6	16RE	2-1-8-1	8/6
RM2	8/-	18RA	1-1-16-1	6/6	18RA	1-2-8-1	11/-
RM3	9/-	16RC	1-1-16-1	88/6	14A86		17/-
RM4	16/6	14RA	1-2-8-2	18/-	14A97		23/6
RM5	22/-	14RA	1-2-8-3	21/-	14A100		24/-

CATHODE RAY TUBES


Type 43/69 £10.0.0

Type 36/44 £8.10.0

TERMS OF BUSINESS C.W.O. or C.O.D.
2/9 PACKING CHARGE ON ALL C.O.D.
ORDERS. POSTAGE 3d. PER VALVE.

OBSOLETE VALVES A SPECIALITY.
QUOTATIONS GIVEN ON ANY TYPE
NOT LISTED.

BEULAH ELECTRONICS

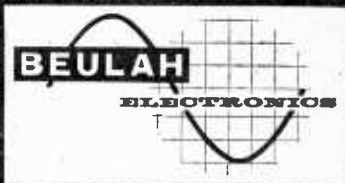

offer a highly competitive Range of

TEST EQUIPMENT!



MODEL 0-12U/F Laboratory 5" OSCILLOSCOPE

Here's an instrument to give laboratory service at less than utility 'scope price! The large flat screen ensures great accuracy and facilitates observation. An outstanding feature is the use of a patented sweep circuit of exceptional range which covers 10 c/s. to over 500 Kc/s in five steps, many times the sweep range of other 'scopes. Gold-plated printed-circuit. Large 5in. Flat Screen. Wide Band Amplifier for TV and F.M. Servicing. Vertical Bandwidth 3 c/s. to over 5 mc/s. Electronically stabilised power supply

£44 complete with 48-page Handbook plus carriage.

MODEL 0-12U (in Kit Form) £34. 15s.

MODEL V-7A/F VALVE VOLTMETER

Internationally Famous

Performance and professional appearance equal to many higher priced instruments. Gold-plated printed-circuit. High Input impedance (11 megohms). The V-7A measures A.C. volts (0-1.5, 5, 15, 50, 150, 500, 1,500) R.M.S. and A.C. volts (0-5, 14, 40, 140, 400, 1,400 and 4,000) pk-to-pk. D.C. volts (0-1.5, 5, 15, 50, 150, 500, 1,500). Ohms (with 10 ohms centre) X1, X10, X100, X1000, X10K, X100K and X1 megohm.



£19 complete with 32-page Handbook.

MODEL V-7A (in Kit Form) £13

BEULAH

ELECTRONICS TEST EQUIPMENT IS CONSTRUCTED FROM THE FAMOUS

HEATHKIT SERIES

FACTORY ASSEMBLED!

FACTORY WIRED!

FACTORY TESTED!

Officially approved by

DAYSTROM LTD.

DEFERRED TERMS ON MOST ITEMS GLADLY ARRANGED ON REQUEST. ASK FOR DETAILS.



MODEL AG-9U/F AUDIO SIGNAL GENERATOR

Wide Band (10 c/s. to 100 Kcs.). Less than 1% distortion (20 c/s.-20 Kc/s.). High grade 200 μ A f.s.d. meter with large scale for precision measurement. An invaluable instrument for hi-fi audio and many ultra-sonic and I.F. applications requiring an almost perfect sine-wave signal, without the necessity of expensive filters. The instrument has a very well-designed power supply which includes a double-wound mains transformer with a very effective smoothing circuit. Eight different switch selected voltage ranges covering from 0-0.003 f.s.d. to 0-10V. f.s.d.

£26. 3s. complete with 24-page Handbook

MODEL AG-9U (in Kit Form) £19. 3s. 0d.

MODEL O.S. 1/F New Low Priced Service OSCILLOSCOPE

This is an ideal light and compact portable 'scope for the serviceman, the overall dimensions being 5in. x 8in. x 14 1/2in. long at a weight of 10 1/2 lbs.

Specification

Time Base 10 c/s. to 100 K/c/s. and 50 c/s. sine wave sweep. X amp. Sensitivity 1 V/cm. at 1 Kc/s. Calibration 1 v., 10 v. and 50 v. peak to peak available on front panel. Valve Complement. 2-ECF80, 2-EF80, 1-ECC82, 1-EZ80, C.R. Tube 1-3AFP1 or equivalent (2 1/2in. dia.). Power Requirements, 200-250 volts, 40-60 c/s. A.C. 40 watt (fused).

£26. 7s. 6d. plus carriage

MODEL O.S.1 (in Kit Form) £18. 19s. 6d.



PLEASE SEND CASH WITH YOUR ORDER NOW OR ASK FOR ILLUSTRATED LEAFLETS TODAY stating instruments in which you are interested.

DIRECT T.V. REPLACEMENTS LTD.

Dept. PW/10

138 Lewisham Way, New Cross, London, S.E.14

(The Largest Stockists of specialised TV Replacements in Great Britain)

SOLE DISTRIBUTORS for



TIDeway 6666

Day and Night Service: TIDeway 6669

Here are some of the other top-grade instruments available, **FACTORY ASSEMBLED, WIRED AND TESTED** in the "Heathkit" range—

Resistance/capacitance Bridge C-3U F.....	£13 2 6
MODEL C-3U (in Kit Form).....	£7 19 6
Audio Valve Millivoltmeter AV-3U/F.....	£19 19 6
MODEL AV-3U (in Kit Form).....	£13 18 6
Audio Wattmeter AW-1U/F.....	£19 19 0
MODEL AW-1U (in Kit Form).....	£13 18 4
Electronic Switch S-3U/F.....	£15 15 0
MODEL S-3U (in Kit Form).....	£9 18 4

A.C./D.C. Multimeter Kit

Ranges: D.C. volts 0-5, 0-50, 0-100, 0-500, 0-1,000. A.C. volts 0-5, 0-50, 0-100, 0-500, 0-1,000 D.C. milliamps 0-5, 0-100, 0-500. Ohms 0-50,000 with internal batteries. 0-500,000 with external batteries. Measures A.C./D.C. volts, D.C. current and ohms. All the essential parts including metal case, 2in. moving coil meter, selected resistors, wire for shunts, range selector, switches, graduated scale and full instructions, price 19/6, plus 2/6 post and insurance.



TRANSISTORISED STETHIOSCOPE

Trace signal right through: Radio, T.V., Tape amplifier, Hi-Fi, etc.—simplest way to fault find—carry it like a fountain pen—all parts including transistor barrel crystal, everything except battery, 12/6 plus 1/6. Battery 6d.—data included or separately 1/6.



UNIQUE OPPORTUNITY TO BUILD FINE TRANSISTOR SET

Construct your own consisting of cabinet approx. size 41 x 31 x 1 1/2 in. with handle and embellishment as illustrated, turning dial, tuning condensers and easy to follow constructional data. Price 22/6 plus 2/6 post and insurance.



Now you can build a pocket transistor set as currently being sold at 17 gns. We can supply all necessary parts at highly competitive prices. Alternatively build your own circuit. Circuit diagram and constructional data supplied separately, 1/6.

Building A Scope



5in. oscilloscope tube American made Type No. 3FP7. Octal base 6.3 v. 0.6 amp heater, electrostatic deflection. Brand new and guaranteed, 15/- each, plus 1/6 post and insurance. Complete with circuit diagram.

"Dim and Full" Switch

Particularly useful for controlling photoflood lamps which have only a short life at full brilliance. This toggle switch has three positions; the first position puts two lamps in series at half brilliance for setting up, the second position is off and the third position full brilliance for the operation shots. Also useful for controlling night lights, heaters, etc., etc. Price 3/9 each, post 9d. Circuit diagram included.


Morganite Potentiometers

Single and 2-gang types available. Standard size with good length spindle, all new and better. Single types, 1/- each, values available: 5K, 10K, 25K, 50K, 100K, 250K, 1 meg., 2 meg. 2-gang types, 2/- each—values available: 5K ± 5K, 10K ± 10K, 1 meg. ± 1 meg., 2 meg. ± 2 meg.



PHILIPS TRANSCRIPTION UNIT

Philips AG 2009 Record Player, 4 speed. Ideal for the enthusiast. Pick-up arm wired for stereo, fine adjustment on all four speeds. Continuously variable pick-up weight (2.12gms.). Supplied with Philips Hi-Fi crystal type AG5019 for micro-groove and 78 r.p.m. Frequency response 30-15,000 c/s. Pick-up lifting and lowering device, individually balanced heavy turntable. Muting switch. Can be used with any amplifier or radio set. Complete with monaural pick-up £10, 10.0, or 2 gns., deposit and 20 fortnightly payments of 10/-. Available also with stereo head, diamond or sapphire stylus. Prices on request.

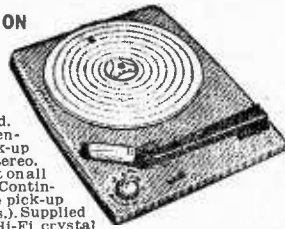

The Taylor Meter Model 127A




A pocket size meter but with a big scale and a sensitivity of 20,000 Ohms per volt D.C., therefore an ideal unit for television servicing — robustly made and complete with leads and prods—20 ranges as follows: D.C. current 50 micro-amps. to 1 Amp. D.C. voltages—0-1,000 volt in seven ranges (25 KV. with external probe, optional extra). Volts A.C.—0.2-500 in six ranges. Ohms—0-20 Ohm in three ranges (self-controlled).

Self-contained, 3 1/2 in. movement. Price £10 or 10/- deposit and 21 fortnightly payments of 10/-. Non-callers add 5/- carriage and insurance.

TRANSISTOR LOUDSPEAKER RADIOS

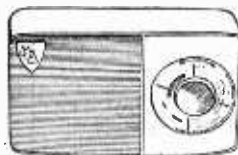
Results Guaranteed. Nothing can be more disappointing than to find that despite care in making up, your little radio just will not work. This is unlikely to happen with our kits, but if it does, send it in for service, we guarantee good results.



Two Models

Pocket 3 for strong signal areas, uses two transistors and one diode, price 27/6. Pocket 4 uses three transistors and one diode and has refinements for receiving weak stations, price 42/6. Every kit complete to last and bolt, with proper case, tuning condenser, and miniature loudspeaker. Our kits do not need external aerials, also they may be built in stages to car radio output. Post and insurance 2/6.

Making a Solder Gun

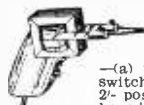

A 7-second solder gun of the type costing £3-£4 was described in "Practical Mechanics". Only two essential parts are required (a) the transformer and (b) the push switch. These we can supply at 11/6, plus 2/- post. The rest of the parts you will have in your own "junk" box. Copy of the article concerned given free with the kit.


Component Storage Drawers

Stout board construction these drawers are ideal for small parts. Supplied complete with simple erection instructions—1/6 each or 12 drawers each 6 x 21 x 6 1/2 in., 13/6, post 2/-.



Hi-Fi Snip Infinite Wall Baffle

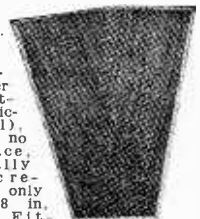Nicely veneered and polished. Corner fitting (attaches to picture rail). Takes up no floor space. Gives really fantastic results with only low-price 8 in. speaker fitting for tweeter. Only 45/- each, carriage and insurance 3/6.



Speaker Bargain



12in. Hi-fidelity loudspeaker. High flux. Permanent magnet type with standard 3 ohm speech coil. Will handle up to 12 watts. Brand new by famous maker. Price 32/6, plus 3/6 post and insurance.

Yaxley Switches


1 Pole 3 Way.....	1/6
1 Pole 5 Way.....	2/6
1 Pole 11 Way.....	2/6
1 Pole 12 Way.....	3/-
2 Pole 2 Way.....	2/6
2 Pole 4 Way.....	2/6
2 Pole 6 Way.....	2/6
2 Pole 12 Way.....	4/6
3 Pole 3 Way.....	1/6
3 Pole 6 Way.....	3/6
4 Pole 4 Way.....	3/-
6 Position Shorting.....	3/-
6 Pole 3 Way.....	2/6
6 Pole 3 Way.....	3/6
8 Pole 2 Way.....	2/6
8 Pole 3 Way.....	2/6
12 Pole 2 Way.....	2/-

Miniature Microphone

American made. Dynamic type, real bargain at 2/6, plus 6d. postage.




Charging Switchboard

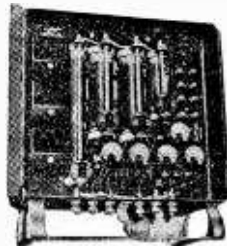

Offered at about one-twentieth of original cost. This is an ex-Government switchboard. It contains three reverse current relays, one voltmeter, one main ammeter, two secondary ammeters and three variable resistors for controlling circuits. These are original cases. Price £215.0, carr. 10/-.

Suppressor Condenser

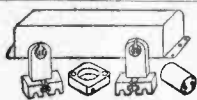Stop your drill or other appliances interfering with your or your neighbours' radio or television. Simple instructions given. 1.6 each. 12/- dozen.



Fluorescent Light Bargain
Kit of parts comprising: choke, two lamp holders, starter holder and starter, 40 watt, 18/6, 80 watt, 23/6. Plus 2/- post and insurance.

W.D. Circuit Details

Diagrams and other information extracted from official manuals. All 1/6 per copy, 12 for 15/-.

A.1134	R.109
BC.348	HRO Receiver
BC.312	R28/ARC5
R.103A	R116/A
BC.342	RA.1B
RA.1B	AR88D
R.208	AN/APA-1
R.1155	78
R-1124A	76
R-1132A/R-1481	R.T.18
R-1147	CAY.46-AAM-
R-1124A	RADAR
R-1092	A.S.B.3
R-1355	Indicator 62A
B.C.1206-A/B	Indicator A.S.B.3
B.455-A (or-B)	Indicator 62
B.454-A (or-B)	Indicator 6K
B-456-M-A (or-B)	R.F. unit 24
Transmitter T1154	R.F. unit 25
Fifty-eight walkie talkie	R.F. unit 26
Frequency meter	R.F. unit 27
B.C.221	Wireless set No. 19
	Demobbed valves

Another Battery Charger Bargain
Components Would Cost More

Car Battery Charger—ready-made high output battery charger in stove enamelled sheet steel louvered case. New, complete and ready to work. Rated at 12 v. 5 amps, and variable rate selector for trickle charging, also a meter to show charging rate. Suitable for 230/250 A.C. mains. Special snip price of 65/-, plus 3/6 post and ins.



Motor Snip

Miniature motor 2 1/2 in. long x 1 1/2 in. diameter, laminated poles and armature, separate winding for reversing. Operates off 20-30 v. D.C. or off A.C. mains through stepdown transformer. Original cost at least £3 each. Snip price for one month only 8/6, plus 1/6 postage and insurance.




Transistor Set Cabinet

Very modern cream cabinet, size 5 1/2 x 3 x 1 1/2 in. with chrome handle, tuning knob and scale. Price 7/6, plus 1/6 postage and packing.

Re-gunned Tubes

We offer television tubes which have had new gun assemblies, new getters, new screens and have virtually been rebuilt as new.

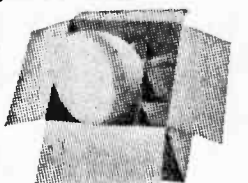12in. £4.19.6
14in. £5.9.6
17in. £5.19.6
Non-callers please add 10/- carriage and insurance.




Cabinet Snip




This fine cabinet as illustrated but less control board and knobs is available at a special snip price of 12/6, plus 3/6 post and insurance. Size is 13 1/2 x 9 x 4 in. and it is nicely covered in two tone I.C.I. fabric.

Fine Chassis by Armstrong

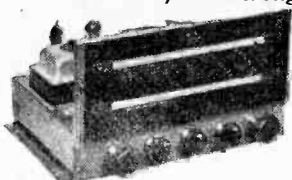

The AF208 handbuilt to the traditional Armstrong standard is ideal for building into a new set-up or for bringing that old favourite up to date.
FM 87-108 Mc/s. AM 187-570 mtrs, 5 watts output—15db neg. feedback—separate base and treble—2 compensated inputs (for pickup—frequency response 30-22 thousand C.P.S. Plus or minus 2 db. Tape, record and playback facilities. Price 22 kns. or H.P. terms on request.

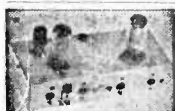

Band III Converters

Suitable Wales, London, Midlands, North, Scotland, etc. All the parts including 2 EF80 valves, coils, fine tuner, contrast control, condensers and resistors. (Metal case available as an extra.) Price only 19/6, plus 2/6 post and insurance. Data free with parts or available separately, 1/6. Please send two more kits, the one you sent last week is performing magnificently. We receive this sort of letter every day of the week, so if you have hesitated because you thought our kits too cheap you need hesitate no longer.

SPECIAL THIS MONTH

Twin Twisted Lighting Flex—equivalent 14/36, rubber insulated, cotton covered, 12/6 per 100 yard coil.

Moving Coil Meters
0-500 microamp 2 1/2 in. flush 17/6
250-0-250 microamp 2 1/2 in. surface 97/6
750 microamp 2 1/2 in. surface 17/6
5-0-5 milliamper 2 1/2 in. flush 17/6
0-30 milliamper 2 1/2 in. flush 17/6
0-100 milliamper 2 1/2 in. flush 15/-
0-300 milliamper 2 1/2 in. flush 15/-
0-500 milliamper 2 1/2 in. flush 15/-

Unbreakable Mains Lead type of lead fitted to electric razors makes fine lead for test meters and any other devices where subject to continuous bending. Twin figure eight construction, soft cream p.v.c. covered. Normally costs 2/- per yard. Three 6ft. leads for 2/-.

Filament Transformer, 6.3 v., 11 amp, 6/6.

0.3 Amp Dropper—tappings marked 200/220/250, 3/6.

Output Transformer—standard pentode—4.6, multi ratio, 6/6.

Bi-metal Strip with heavy duty contact—ideal for thermostat, fire, lamp, etc., 2/6.

Neon Lamp—midget wire ended, ideal mains tester, etc., 2/-, ex Govt., 1/6.

5 amp, 12 v. full-wave Charger Rectifier, normal price 17/6. Price 10/-, plus 1/6 post and ins.

Install those extra points, 3.029 twin flat T.R.S. cable. Big purchase enables us to sell this at 45/- per 100 yds., carriage 8/6.

Head Phones, DLR5. Ideal crystal sets, etc., 8/6, plus 2/- post.

Goodmans Multi Ratio Output Transformer, 8 watt, 8 ratios, from 12-1 to 72-1 Centre tapped for push/pull, 7/6, plus 1/6.
Ditto, unbranded, 6/6, post 1/-.

Cold Cathode Valve CV413, Voltage regulator or trigger switch—unused but ex-equipment, 2/6 each.

Tag Panels, Ideal for constructors, experimental circuits, etc., 3 of each of 12 different types, 5/-, post 1/6.

Belling Lee 2BA fully insulated terminals for mounting through metal panels, 1/6 each.

Terminal Heads, insulated 4BA, 2-do. 0.1 mFd., 350 v. Small tubular metal cased condensers made by Dублиer, 2/6 doz.

50 Assorted Resistors, Well mixed and useful values 1/2 and 1 watt, 5/- for 50. Ditto, but 1 watt, 6/6 for 50.

Mains Transformer, Standard 230 v. input 250-0-250 at 80 mA., 6.3 v. at 5 A., 12/6, post 1/6.

Toggle Switch, Standard metal body, type with round dolly, fixing ring and on/off indicating plate, 1/3 or 12/- doz.

Metal Rectifier, 250 v. 60-80 milliamps, ideal for mains set or instrument or to replace that expensive valve, 4/6.

Screened Cable, Rubber covered flexible with metal braiding, ideal for microphone or gramophone extensions, 4d. per yd., 30/- per 100 yds.

ELECTRONIC PRECISION EQUIPMENT LTD.

★ Orders received by post are despatched from our warehouse, Dept. 7, 66 Grove Road, Eastbourne, and to save time, please post your order to this address. Please include enough for postage. Callers, however, should use one of the following addresses:

Electronics (M.P.) Ltd.,
329 High Street North,
Moor Park, E.12
Phone: Hford 1011
Half day Thursday

Electronics (Ruislip) Ltd.,
42-46 Windmill Hill,
Ruislip, Middx.
Phone: RUISLIP 5780
Half day Wednesday

Electronics (Croydon) Ltd.,
266 London Road,
Croydon.
Phone: CRO 6558
Half day Wednesday

Electronics (Finsbury Park) Ltd.,
29 Stroud Green Rd.,
Finsbury Park, N.4.
Phone: ARCHWAY 1049
Half day Thursday

"Basic Electricity"

LOTS & LOTS of



TINKERS, TAILORS,
SOLDIERS, SAILORS,
AIRMEN, APPRENTICES & Ordinary Chaps
like You and Me Are Learning
BASIC ELECTRICITY & BASIC ELECTRONICS

"Basic Electronics"

THIS NEW **PICTURE BOOK** WAY

Why don't you too?

read what HOBBIES WEEKLY says:—

- ★ "... such a wonderful means of learning . . ."
- ★ "... there can be no better gift from father to son . . ."
- ★ "... The visual aid system is employed in such a manner as to make one's journey through the cartoon-type illustration pages an exciting passage of easily assimilated knowledge . . ."

and what THE A.E.U. MONTHLY JOURNAL says:—

- ★ "... The publishers of this set of books describe them as 'a brilliant new illustrated course' in the subject, and I am inclined to agree with them . . ."

COUPON - SEND NOW!

please send me your FREE prospectus describing your four
ILLUSTRATED COURSES of ELEMENTARY TECHNICIAN TRAINING

BASIC ELECTRICITY (5 PARTS) — BASIC ELECTRONICS (6 PARTS)
BASIC SYNCHROS AND SERVO MECHANISMS (2 PARTS)

In preparation **BASIC RADAR (5 PARTS)** *Ready 1961*

NAME _____

ADDRESS _____

To THE TECHNICAL PRESS LTD.
112 WESTBOURNE GROVE
LONDON W.2.

BARGAINS EVERY MONTH! DON'T MISS THESE!

TV TUBES!


**REPLACEMENT REBUILT
12 MONTHS' GUARANTEE**
Terms available over 20 weeks
Carr. & Ins. 15/6

21" TUBE £8.10.0
17" TUBE £7.10.0

**£2 ALLOWED ON
OLD TUBE**

12" 14" 15" TUBES
£5.10.0

**£1 ALLOWED ON
OLD TUBE**

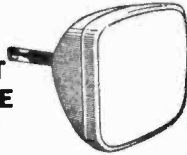

TELEVISIONS! 17" Complete

19 Gns.

Cash or Terms as follows: £7 deposit and 20 weekly payments of 15/-. Carr. and Ins. 25/-.

ITV/BBC. Beautifully styled polished cabinets. These are table models with the option of contemporary legs fitted (2 gns. extra). 17in. rectangular tube guaranteed for 12 months. Valves and chassis guaranteed for 3 months. (Chassis salvaged but reconditioned.) Where possible personal collection is advised.


RECORD PLAYER CABINETS!

for **STEREO** sound!
WITH EXTENSION
SPEAKER CABINETS
99/6 or Terms



1960 Show Model Portable, in two tone colours. Extension speaker cabinet secured in lid. Size 18 x 14 x 8½ in. high. This stereophonic

player retails complete, at 35 gns. in the shops today. Ins. and Carr. 5/6.

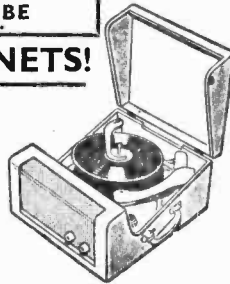

Monarch 4-speed Autochanger, £6.19.6, 7 x 4in. Elliptical Speaker 15/9, and our Mk. D.1 Portable Amplifier, 59/6.

**R.P.2
59/6**

or Terms

Made by famous manufacturer. In polka dot cloth with clipped lid and carrying handle. Size 16 x 14½ x 8½in. deep. Carr. & Ins. 4/6. Will take B.S.R.



19/9
OR
TERMS

R.P.8

This contemporary cabinet in two-tone grey rexine is ideal for the modern home. Added attraction is the cream plastic speaker fret. Press button lid, lock. Fittings for screw in legs. Internal measurements 14½ x 18 x 8½in. deep. Carr. and Ins. 5/6.

SUPER CHASSIS!

79/6

OR TERMS!

Five valve superhet chassis incl. 8in. P.M. Speaker. Four control knobs (tone, volume, tuning, w/change). Four wavebands. A.C. Carr. and Ins. 5/6.

SUITABLE TO CONNECT WITH RECORD CHANGERS

B.S.R. MONARCH 4-speed autochanger £6.19.6
COLLARO CONQUEST 4-speed autochanger £6.19.6

TAPE RECORDER CABINET! and COMPLETE TAPE RECORDER!



**DE-LUXE MODEL
ONLY 29/9**

Beautifully made Tape Recorder Cabinet. Size 13 x 10½ x 7in. Covered in two-tone coloured rexine cloth. Stylish design. Carrying handle and detachable lid. Easily adapted to Record Player Cabinet. P. & P. 4/6.

LIST PRICE 29 gns.

Now only **18 Gns.**

Famous Manufacturer's Unrepeatable Value



Huge purchase allows us to offer at this amazing price. Beautifully styled rexine covered cabinets.

Colours: Red, Grey, Black. Storage space for 4 tapes, mike and lead. Incorporating latest B.S.R. Deck. LOOK AT THESE EXPENSIVE FEATURES Record playback switch and rewind with interlocking device to prevent accidental erasure. Tone and volume controls. Superimpose and electronic eye. Ample power output 3.5 watts. Small overall size 14½ x 14½ x 7½in. Lightweight, 21 lbs. Playing time 1½ hours. 5½in. standard tape. Terms. Carr. and Ins. 12/6. Microphone 27/6 extra. Tapes 19/9.

TAPE RECORDER AMPLIFIER

Compact, well designed 5-valve amplifier. Output 3.5 watts. Valve line up—ECC83. Double triode first audio amplifiers. ECL82 Triode pentode further audio amplifier and output valve. 6BW6 Bias and erase oscillator, EM84 record level, indicator. EZ80 H.T. rectifier. Input for mike, radio and gram. Controls: record playback volume and on/off playback tone. Dia. 8½ x 3 x 4½in. Ins. and carr. 4/6. Terms. Knobs 2/6 per set. Beautifully perspex dial plate, 3/6. Completed with sockets for mike. Radio and superimpose switch. **£7.19.6**

AMPLIFIERS

Mk. D.1. Brand new. Latest design with printed circuit. Dimensions 7 x 2½ x 5in. A.C. only. Mains isolated 3 watts output. Incorporating EL84 as high gain output valve. Volume and tone controls. 59/6. Knobs 2/6 extra. P. & P. 2/6.
Mk. D.3. De luxe model! Printed circuit. Latest design. Dimensions 7 x 2½ x 5in. A.C. only. Mains isolated 3-4 watts output. Incorporating the latest ECL82 triode pentode output valve giving higher undistorted output. Volume, treble and bass control. 89/6. Knobs 3/6 extra. P. & P. 3/6.

DUKE & CO. 621/3 Romford Rd., Manor Pk. E.12 ILF 6001/3
(LONDON) LTD.

The decision is YOURS. To be a success in your chosen career; to qualify for the highest paid job . . . to control a profitable business of your own. ICS home-study courses put your plans on a practical basis; teach you theory and practice; give you the knowledge and experience to take you, at your own pace, to the top.

Choose the *RIGHT* course :

RADIO & TELEVISION ENGINEERING
INDUSTRIAL TELEVISION

RADIO & TELEVISION SERVICING
RADIO SERVICE AND SALES

VHF/FM ENGINEERING : ELECTRONIC
COMPUTERS & PROGRAMMING

ICS provides thorough coaching
for professional examinations:


Brit. I.R.E., City and Guilds Tele-
communication Technicians. C. & G.
Radio & TV Servicing (R.T.E.B.);
C. & G Radio Amateurs.

LEARN AS YOU BUILD

Practical Radio Courses

Gain a sound up-to-professional-standards knowledge of Radio and Television as you build **YOUR OWN** 4-valve T.R.F. and 5-valve superhet radio receiver, Signal Generator and High-quality Multi-tester. At the end of the course you have three pieces of permanent and practical equipment and a fund of personal knowledge and skill. ICS Practical Radio courses open a new world to the keen Radio amateur.

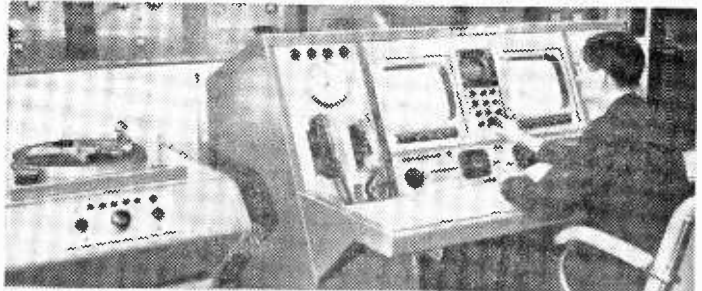*Technical
Training
in Radio,
Television
and
Electronics
Engineering
with*



THERE ARE ICS COURSES TO MEET YOUR NEEDS AT EVERY STAGE OF YOUR CAREER. FILL IN AND POST THIS COUPON TODAY.

You will receive the FREE 60 page ICS Prospectus listing examinations and ICS technical courses in radio, television and electronics PLUS details of over 150 specialised subjects.

Other ICS courses include:
MECHANICAL, MOTOR,
FIRE, ELECTRICAL &
CHEMICAL ENGINEERING.
FARMING, GARDENING.
ARCHITECTURE &
WOODWORKING.
SELLING & MANAGEMENT.
ART. PHOTOGRAPHY,
etc., etc.,

PLEASE STATE ON COUPON SUBJECT YOU ARE INTERESTED IN . . .



INTERNATIONAL CORRESPONDENCE SCHOOLS
(DEPT. 170), INTERTEXT HOUSE, PARKGATE RD., LONDON, SW11

PLEASE SEND FREE BOOK ON _____

NAME _____

ADDRESS _____

OCCUPATION _____ AGE _____

10.60

RETURN-OF-POST SERVICE

AMPLIFIER BARGAINS

LEAK POINT ONE PLUS PRE-AMP. Brand new in maker's carton. List £12.00. OUR PRICE £10.00.
QUAD MAIN AMPLIFIER WITH PRE-AMPLIFIER. Brand new in maker's cartons. List £42.00. OUR PRICE £32.00.
 Only one each of the above available. Any can be supplied on H.P. Terms.

LATEST TEST METERS

	Cash Price	Deposit	Hire Purchase Mthly/Pmts.
AVO Model 8	£23.10	0	£4.14 0 12 of £1.14 6
AVO Model 8 with leather carrying case	£27. 8. 0	£5. 8. 0	12 of £2. 0. 4
AVO Model 7	£19.10	0	£3.18 0 12 of £1. 8. 8
AVO Model 7 with leather carrying case	£23. 8. 0	£4.12. 0	12 of £1.14. 6
AVO Multiminor	£29.10	0	£1.18. 0 12 of 14/4
AVO Multiminor with leather carrying case	£31. 9. 0	£2. 5. 0	12 of 17/-
TAYLOR Model 127A	£10. 0. 0	£2. 0. 0	12 of 15/-
CABY A-10	£24.17. 6	£1. 7. 6	3 of £1. 6. 8
CABY B-20	£26.10. 0	£2. 0. 0	3 of £1.13. 4

Full details of any of the above supplied free on request.

TAPE DECKS

	Cash Price	Deposit	Hire Purchase Mthly/Pmts.
B.S.R. TD2	£9.19. 6	£1.19. 6	12 of 15/-
COLLARO STUDIO	£15.10. 0	£3. 2. 0	12 of £1. 2. 9

All cartage free.
 All components in stock for the Mullard Tape "C" Pre-Amplifier Kit. Fully detailed list available.

TRANSISTORS

ALL BRAND NEW STOCK—NOT SURPLUS
MULLARD—Aud. OC70, OC71, 14/- each; OC72 Audio Output Matched pair, 34/-; RF, OC44, 26/-; OC45, 24/-
MAZDA—XB102, XB104, Audio, 10/- each; XC101 Audio Output, Matched pair, 34/-; RF, XA101, 23/-; XA102, 26/-; XA103, 18/-; XA104, 18/-.

BLANK CHASSIS

The very latest blank chassis for the home constructor. Packed flat for easy and safe posting. These are made in bright tinplate and have the top plate and four side channels packed flat complete with nuts and bolts for assembly. The top plate is completely flat for easy drilling before assembly. Earth connections can be made directly by soldering. Available in the following sizes: 7 x 5 x 2in., 4/8, post 1/3. 10 x 5 x 2in., 5/3, post 1/4. 10 x 7 x 2in., 6/-, post 1/8. 14 x 5 x 2in., 7/3, post 1/8. 14 x 7 x 2in., 8/9, post 1/8.

CATHODE-RAY TUBES

BRAND NEW STOCK. NOT REBUILDS. 12 MONTHS' GUARANTEE.
 We can supply all BVA branded tubes at the new reduced prices. This includes Brimar, Cossor, Emscope, Emitron, Ferranti, G.E.C., Mazda and Mullard. Full list of all available types sent on request.

STEREO COMPONENTS

Morganite ganged potentiometers as specified for the Mullard circuits. Lot/Anti-Loz, 500k, 1 meg., 2 meg. Loz/Loz, 250k, 1 meg., 2 meg. Lin/Lin, 500k, 1 meg. All 10/6 each.
 Dented Chassis for the Mullard circuits. All drilled with printed front panel.
 Three Valve Stereo Amplifier, 22/-. Seven watt Stereo Amplifier, 24/6. Stereo Pre-Amplifier, 24/6.
 Pick-up cartridges. B.S.R. TC88 £2.4.11. Ronette DC284, £3.19.6. Both are turn-over types for Stereo, LP and 78 records.

ILLUSTRATED LISTS

Illustrated lists are available on LOUDSPEAKERS, TAPE DECKS, TEST GEAR, RECORDING TAPES, GRAMOPHONE EQUIPMENT. Any will be sent free upon request.

HIRE PURCHASE TERMS are available on any time. Repayments may be spread over 3, 6 or 12 months. Details as follows: Three months: Deposit 6/- in the £. Service charge 5 per cent but minimum charge of 10/-. Six and Twelve months: Deposit 4/- in the £. Service charge 10 per cent, but minimum charge 20/-.
TERMS OF BUSINESS. Cash with order or C.O.D. We charge C.O.D. orders as follows. Up to £3, minimum 2/8. Over £3 and under £5, 1/6. Over £5 no charge. Postage extra on CASH orders under £3.

AMPLIFIER KITS

We have full stocks of all components for the Mullard 510, Mullard 2 and 3 valve Pre-Amplifiers, GEC 912 Plus. Fully detailed list on any of these sent upon request.
 Instruction Manuals. Mullard. All Mullard Audio Circuits in "Circuits for Audio Amplifiers", 9/6. GEC 912, 4/6. All post free.

GRAMOPHONE EQUIPMENT

ALL LATEST MODELS	Cash Price	Deposit	Hire Purchase Mthly/Pmts.
RECORD CHANGERS			
COLLARO Conquest (Studio O PU)	£7.19. 6	£1.12. 0	6 of £1.4.7
GARRARD RC210 (GC8 PU)	£9.19. 6	£1.19. 6	12 of 15/-
GARRARD RC88	£26. 8. 0	£3. 6. 0	12 of £1.4.0
GARRARD RC98 (GC8 PU)	£21.8. 8	£3.15. 0	12 of £1.7.3
B.S.R. UA8 Monarch (TC8 PU)	£7. 5. 0	£1. 9. 0	6 of £1.2.8
B.S.R. UA14 Monarch (TC8 PU)	£28.18. 0	£1.15. 0	12 of 18/7
B.S.R. UA14 Monarch (TC88 Stereo/LP/78)	£29.18. 0	£1.18. 0	12 of 15/-
SINGLE RECORD PLAYERS			
GARRARD TA (GC8 PU)	£3.10. 0	£1.14. 0	12 of 13/-
B.S.R. TU9 (TC8 PU)	£4.10. 0	£1. 5. 0	3 of £1.5.0
COLLARO RP384 (O, P or T PU)	£28.18.11	£1.15.11	12 of 13/7
COLLARO RP394 (O, P or TPU)	£29.18. 9	£1.18. 9	12 of 15/-
E.M.I. (Acco Stereo PU)	£26.15. 0	£1. 7. 0	12 of 10/8
TRANSCRIPTION UNITS			
COLLARO 4F/200 (TX88 PU)	£28.13. 0	£3.15. 0	12 of £1.7.4
COLLARO 4F/200 Motor only	£23.18. 3	£2.15. 3	12 of £1.0.5
GARRARD 4HF (GC8 PU)	£28. 9. 9	£3.15. 9	12 of £1.7.0

Matched list of the above can be supplied for stereo working. See our Gramophone Equipment List for details.

JASON FM TUNER KITS

Three Jason F.M. Tuner kits with variable tuning are now available to the home constructor. Brief details are given here and our illustrated list is available free.
MOST IMPORTANT. We take great pains to see that every item needed is included in our kits and also that all items are entirely suitable in every way. This should be borne in mind when comparing prices.
 Hire Purchase Terms are available on any kit.
INSTRUCTION MANUALS. All our kits include the instruction manual, but this can be supplied separately if required. Data Publications booklet, describing FMT1, 2, and 3. 2/10; J.T.V.2, 3/10; Mercury 2, 3/10. All post free.

STANDARD TUNERS

FMT1. Supplied complete with a chassis-panel assembly fitted with a solid hammer finished panel and glass dial. Four EF91 valves are used and an external power supply is required. Complete kit £25.9.6. Power Pack kit £21.0.
FMT2. This is a new version of the FMT1 and is supplied with a complete cabinet-chassis assembly which can be mounted in a cabinet or stood on a shelf. The circuit employs four EF80 valves and the power supply can be built into the cabinet if desired. Complete Kit less power supply £27.17.6. Kit with power supply £29.16.0.

FRINGE TUNER

FMT3. This is a fringe tuner using the same cabinet assembly as the FMT2 described above. The tuner is fitted with variable AFC and uses five EF80 and one ECC91 valves. Kit less power supply £29.18.6. Kit with power supply £31.18.0.

F.M./TV SWITCHED TUNERS


Kits for two new Jason F.M./TV Sound switched tuners are now available. Both incorporate the latest "Fireball" Turret Tuner which gives switch positions for the three BBC Programmes as well as ABC and ITA TV Sound. A.F.C. is fitted to ensure freedom from drift.
JTV2. This tuner is complete with power supply in a cabinet which can be used either for shelf or cabinet mounting. Complete kit £14.14.0.
MERCURY 2. This is similar to the JTV2 but has no provision for a power supply. It is mounted on a small chassis with printed front panel and is intended for cabinet fixing. Complete kit £10.10.0.
IMPORTANT. When ordering JTV2 and Mercury 2 kits it is essential to give the TV channels and F.M. stations required on the tuner.

WATTS RADIO 54 CHURCH STREET, WEYBRIDGE, SURREY
 Telephone: Weybridge 4556
 (MAIL ORDER) LTD.
 Please note: Postal business only from this address

HARVERSON SURPLUS CO. LTD.

83 HIGH STREET, MERTON, S.W.19. CHERRYWOOD 3985/6/7

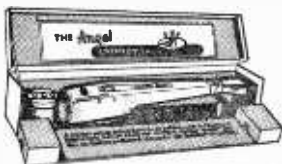THE WORLD FAMOUS E.M.I. ANGEL TRANSCRIPTION P.U. (Model 17A)




A Pick-up for the connoisseur originally priced at £17.10.0. The last remaining few offered at **£4.10.0** Plus P. & P. 5/-

1/6 H.P. MOTOR

140 Watt (Approx. 1/6 H.P.). Series wound, 220/250 volt 50 cycle motor. Off load 14,000 rev/min. on load 8,500 rev/min. Ideal small saw, sewing machine etc. 30/- post free.



MONAURAL AMPLIFIER

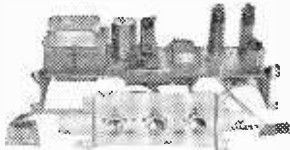


This amplifier as illustrated made by a leading manufacturer. Mullard valves—ECC83, EL84 x EL84, EZ80. Bass Treble and Volume on remote panel. Elegant Knobs. OUR PRICE one month only **£4.16.6** plus P. & P. 3/6.

WHY NOT VISIT US ?

Our new retail premises at 83 High Street, Merton, London S.W.19 are London's biggest walk around shop. 1,000's of bargains all enthusiasts welcome, no obligation to buy. 1 min. South Wimbledon Tube


HARVERSON T.R.F. EASY FOUR KIT

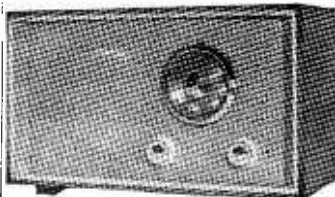

All parts and theoretical wiring diagram only. OUR PRICE **£4.0.0** Plus P. & P. 3/6.

EXTENSION SPEAKER

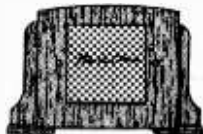An attractive cabinet 8 x 6 x 2in. fitted with 3 ohm 5in. speaker complete with lead, a few only. **19/6** P. & P. 2/6.



TAPE RECORDER

- ★ CONTEMPORARY Red and White Tygan Cabinet, Size 13½ x 14½ x 9½ inches.
 - ★ B.S.R. DECK.
 - ★ MAGIC EYE tuning.
 - ★ INPUTS for RADIO and MIKE.
 - ★ VOLUME and TONE Controls.
- This instrument has to be seen and heard to be believed. Complete with ACOS Xtai Mike. **ONLY 18 gns.**

AM/FM RADIOGRAM CHASSIS

- ★ By famous manufacturer. ★ 220/250 volts A.C. ★ Coverage 1000-1900 m, 200-500 m, 88-98 Mc/s. ★ Tuned by 5 "Piano Keys"—Off, LW, MW, FM and Gram. ★ Sockets for P.U., Ae, E, Extn. Spkr. and Dipole. ★ Tuning and tone controls fitted. ★ Valves, ECH81, EF89, EABC80, EL84, ECC85 and EZ80.
- 50 Only at ridiculous price of **12 gns.** plus 8/6 P. & P.

STEREOPHONIC AMPLIFIER £5.10.0

Complete with 2 Loudspeakers

Plus 4/6 P. & P.

This is a compact amplifier embodying the latest features and giving a high standard of reproduction, with ample volume. Supplied complete with valves (ECL82, ECL82, EZ80), panel, knobs, etc., and two specially selected 3Ω matched loudspeakers. We only have a few, and we will never be able to repeat this offer at such a low price! Don't risk disappointment! Order now!

TRANSISTOR

TRANSISTOR by leading manufacturer. First Grade Equivalent OC44. For one month only, the first 100 customers 8/6 post free. 6 for 50/-

PICK-UP CARTRIDGE BARGAINS

STUDIO P	17/6
ACOS HIGH G.	17/6
E.U. POWER POINT	12/6
RONETTE	18/6
G.C.Z.	16/6

THIS MONTH'S OFFER

Plessey 6 x 4in. 3Ω Loudspeaker, 14/- each. 7 x 4in. Goodmans, 16/6. 25 amp 2½in. flush mounting meters, new, 7/6.

12 Assorted Pots. Wire wound and carbon. Switched and unswitched—all useful sizes at 15/- the dozen. Plus P. & P. 1/-.

60 Milliamp Chokes at per 2/6 each.

AMAZING SCOOP—Cossor 10in. Tubes. 108 K. New and Boxed, 15/- plus 6/- P. & P.

Twin Padded, Grey, Maroon Tracer Mains Lead. Usually 10d. per yard. Our price 15/- per 100-yard coil.

IF YOU DO NOT SEE WHAT YOU WANT ON THIS PAGE WE WILL GET IT FOR YOU

Write (enclosing S.A.E. please) for our list of small parts and accessories for the Constructor. Trade willingly supplied.

Practical Wireless

VOL. XXXVI, No. 644, OCTOBER, 1960

Editorial and Advertisement
Offices:

PRACTICAL WIRELESS

George Newnes, Ltd., Tower House,
Southampton Street, W.C.2.

George Newnes Ltd., 1960

Phone: Temple Bar 4363.
Telegrams: Newnes, Rand, London.
Registered at the G.P.O. for trans-
mission by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year

Inland - - - - £1.3.0 per annum
Abroad - - - - £1.1.6 per annum
Canada - - - - 19s. per annum

Contents

	Page
Editorial	485
Round the World of Wireless	486
Six-Valve Top-Band Tx	488
Resonant Capacity Checker	491
Low Drift V.H.F. Receiver	493
On Your Wavelength	499
Radio Show, 1960	500
Exhibitors at the Radio Show	503
Short-wave Listeners' Log—2	504
Radio Construction for the Beginner	507
Comprehensive Guitar Ampli- fier	509
Mains Dual-wave 2	512
An H.F. One Valve	516
Six Valve 9W Amplifier	521
Simple Communications Sys- tem	525
Combined Receiver and Signal Generator	529
Inexpensive P.A. Equipment... ..	533
Club News	538
Four Transistor T.R.F. Receiver ..	541
Letters to the Editor	545

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2. Owing to the rapid progress in the designs of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless."

P.W. "POCKET SUPERHET" —FREE BLUEPRINT

OUR technical staff have recently concluded the design of a 6-transistor receiver—the P.W. "Pocket Superhet"—and the first article describing the construction will appear next month. Each copy of the October issue will contain also a large blueprint (15in. x 24in.) which will be given away free, although the normal price is 5s. 0d. The blueprint contains the circuit diagram and large, detailed, chassis wiring diagrams as well as a complete list of parts required to build the set. The diagrams are extremely clear; the performance of the set excellent, and even the newcomer to radio-construction should be able to build the receiver with little difficulty. Miniature parts have been used throughout resulting in the small size of the receiver (5½in. x 3in. x 1½in.) which has also been made possible by very careful circuit design and layout.

It is an oft-voiced criticism of home-constructed equipment that the final "finish" is poor; this criticism will not be made of the P.W. "Pocket Superhet" for the October issue will also contain details of a special offer of a lightweight plastic case, a calibrated dial and a chrome-plated handle which will give the completed receiver a professional appearance. The demand for the October issue will be great; be sure to order your copy *now*.

COMMERCIAL RADIO

THE Government's recent announcement of the setting up of an inquiry into the future of sound and television broadcasting in this country has aroused speculation as to whether commercial radio will soon make its appearance. Mr. Reginald Bevins, Postmaster-General, said the terms of reference of the Broadcasting Committee were sufficiently wide to allow it to consider whether a third or other broadcasting organisation should be provided in addition to the BBC and ITA.

The terms of reference are: "To consider the future of the broadcasting services in U.K., and the dissemination by wire of broadcast and other programmes and the possibility of television for public showing; to advise on the services which should in future be provided in the U.K. by the BBC and the ITA; to recommend whether additional services should be provided by any other organisation; and to propose what financial and other conditions should apply to the conduct of all these services".

It is evident that the work of the Committee will, for the most part, be centred on the development of television broadcasting where many technical and economical factors have to be taken into account. Nevertheless, the future of sound broadcasting must be carefully considered; at present the BBC has a monopoly and it may be argued that the introduction of a commercial network would mean improved standards. The task of the Committee is difficult and two years are expected to elapse before its report appears; its publication will be awaited with interest.

Our next issue, dated November, will be published on October 7th

Round the World of Wireless

POTENTIAL AND CURRENT NEWS

Broadcast Receiving Licences

THE following statement shows the approximate number of Broadcast Receiving Licences in force at the end of June, 1960, in respect of wireless receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland. The numbers include Licences issued to blind persons without payment.

Region	Total
London Postal	774,356
Home Counties	727,259
Midland	535,015
North Eastern	590,943
North Western	499,424
South Western	435,471
Wales and Border Counties	261,786
Total England and Wales	3,825,254
Scotland	445,690
Northern Ireland	131,254
Grand Total	4,402,198

Budapest Industry Produces More


INDUSTRIAL output in Budapest has risen 15 per cent in the first four months of this year, compared to the corresponding period last year, according to the Hungarian capital's Central Statistics Office.

Almost half the increase came through an average rise of 7 per cent in productivity. In the instruments industry productivity went up by 12 per cent. Increased output in the chemical industry and the electrical machinery industry was especially significant, says the report.

Average monthly income for workers in the city is now 1,482 forints, compared to 1,450 forints twelve months ago.

Formation of Steelworks Automation Unit

ASSOCIATED ELECTRICAL INDUSTRIES LIMITED and Davy-United Limited announced recently the formation of a jointly-financed Steelworks Automation Unit to apply new automatic control techniques to the processing both of steel and of non-ferrous metals. The problems involved in full automation in the steel and allied industries are too complex for any single existing manufacturing organisation to deal with adequately

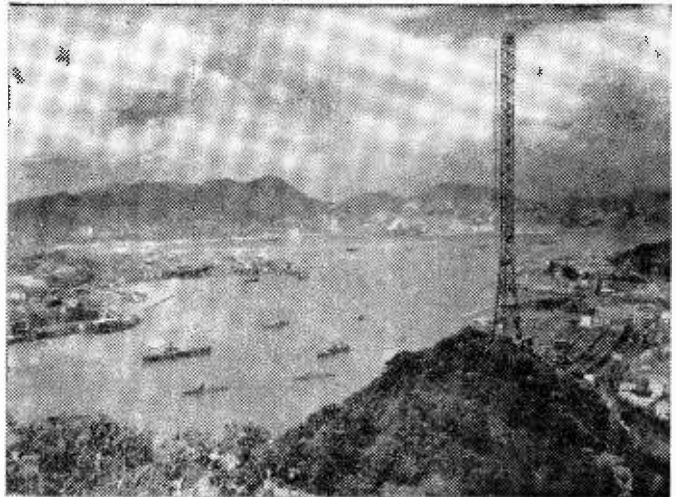

Radio Hong Kong's new VHF/FM broadcasting station which went on the air recently uses four Marconi 5kW FM transmitters in two parallel pairs. This illustration is a view of Hong Kong harbour showing the 135ft tower on Mount Gough which supports the quadrant aerial.

within its own resources, and AEI has therefore allied with Davy-United to establish this combined unit, which has been specifically organised with such problems from the stage of the initial design study to the commissioning of a fully-operational production system in a plant.

The new Steelworks Automation Unit will undertake comprehensive automation projects which can be expected to offer considerable long-term benefits in improved productivity and economy of operation. Such projects will include the combination of advanced servo controls with computers to ensure optimum performance of rolling mills and associated plant.

The AEI/Davy-United Steelworks Automation Unit has its headquarters at Mill Road, Rugby, with representatives both at Davy-United Ltd., Sheffield, and at AEI Heavy Plant Division, Rugby.

New Hong Kong Station

RADIO HONG KONG'S new VHF/FM broadcasting station, which went on the air last month, uses four Marconi 5kW FM transmitters in two

parallel pairs to ensure the reliability required for unattended operation. The station, which is situated at Mount Gough, was planned, built and installed, and will be serviced by Cable and Wireless Ltd. on behalf of the Hong Kong Broadcasting Service.

The parallel pairs system was originally developed by Marconi's Wireless Telegraph Company Ltd. for use on remote transmitter stations, not easily accessible other than on foot.

Two transmitters in parallel are used on each programme instead of the more usual use of a main and a lower power standby transmitter. Should one transmitter fail, then the other continues to radiate the programme at quarter power without the break which occurs while the stand-by is switched on. This also obviates the need for equipment to change over to the stand-by transmitter.

New Ekco Electronics Factory

WORK has already started in the partly completed Ekco Electronics Works, Ashington Road, Rochford, Essex. Production of the specialised equipment

marketed by Ekco Electronics Ltd. has been transferred from Ekco Works, Southend-on-Sea, and the Electronics Installation and Service Department have moved into the new factory. Production of radar and associated equipment will be transferred from Malmesbury (Wilts.) to the new works, thus centralising the whole electronics production enterprise at Rochford.

The total area of the first stage of the factory is about 44,500 sq ft, and work is already in progress on the next stage on the 13-acre site.

"Talking" Books for the Blind

A BRITISH development in tape recording and play-back techniques will give the blind of this country the most advanced talking book machines in the world.

Talking books—books read aloud by specially selected readers recorded on long-playing gramophone records—have for many years played an important role in the lives of the blind, especially the elderly and the bed-ridden. The current membership of the library is in excess of 6,500, and the circulation figure for the last financial year was well over two million individual discs.

Now the service is to be radically improved by the introduction of tape recording and a revolutionary type of play-back machine which possesses a number of basic advantages over the present disc reproducer.

The result of almost twenty-five years' research and development by the R.N.I.B. and St. Dunstan's, this machine has been designed to be, in operation, the very essence of simplicity. Amplifier, loudspeaker and drive mechanism are housed in one compact case, controls have been reduced to one ON/OFF—VOLUME switch and one START/STOP lever and facilities have been incorporated for headphone listening when required.

Philips, Italy, all set for 17th Olympiad

PHILIPS s.p.a., the Italian branch of the international electrical concern, is playing a big part in the arrangements now under way for the opening of the 17th Olympiad in Rome next month.

In the Olympic Village—home of the contestants and HQ of the Press—200 radio sets and 150 TV sets with 21-inch screens have been installed to enable athletes and Press to follow every detail of the Games. This should prove a popular service, for quite often several events will be taking place at the same time in as many different locations.

In the medical centre will be a working range of Philips X-ray and electro-medical appliances.

The company's P.A. equipment—a complete installation already exists in the main Olympic Stadium—will relay results and announcements.

Philips will also floodlight the Colosseum and the Trinita dei Monti. About 400 sodium lamps will be used for the lighting of the Colosseum alone.

Radio Magazine for Denmark

THE Danish State Broadcasting Company is planning to publish Denmark's first radio magazine. It is expected to appear at the beginning of 1961.

British Equipment Used at U.S. Democratic Convention

PERSONAL paging equipment manufactured by the British Multitone Electric Company Limited, and supplied by the Company's Canadian subsidiary,

was installed at the request of the Democratic National Committee at their recent Convention at Los Angeles. The pocket receivers were carried by Democratic officials and delegates, TV, network and News service personnel. These enabled individuals to be called immediately at any time during crucial moments of the proceedings and at any place in or near the huge sports arena.

The Multitone pocket receivers, each of which operates on its own frequency, weigh only 5oz. and standard equipment enables up to 400 individuals to be contacted from one central transmitter.

Reliability in Electronics

A W.S. 12-channel VHF Telemetry Transmitter was found on the beach by a holidaymaker five weeks after the aircraft, in which it has been installed, had crashed into the sea. The impact of the crash evidently threw the transmitter out of its seating, but despite this and its subsequent five weeks in the sea water, it was found on test to be up to full performance specification, and only superficially damaged.

The transmitter, in the same state as when it was recovered on the beach, is being displayed by W.S. Electronics Limited at the Farnborough Air Show.




One of the new gadgets shown by the Canadian Army during a press visit to Camp Gagetown, New Brunswick, was a helmet with built-in radio receiver which has its aerial running over the helmet as seen on the left in the illustration. A conventional helmet may be seen on the right.

Six-Valve Top-Band Tx

10 WATT UNIT WITH "ANODE AND SCREEN" MODULATION

By R. Dowling

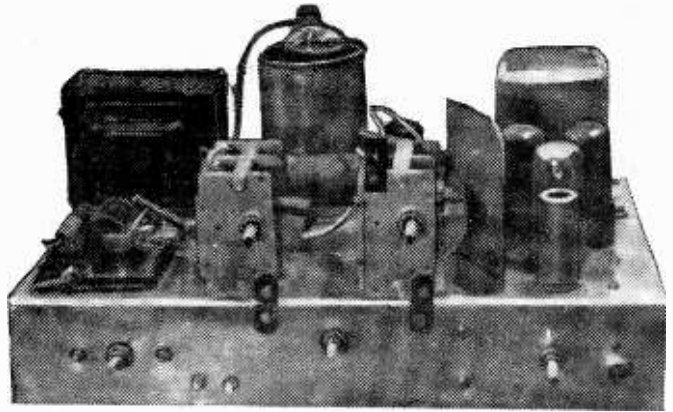

The completed transmitter.

THIS transmitter is designed for use in the amateur "top band"—that is, the band extending from 1.8Mc/s to 2Mc/s. The maximum input power to the power amplifier permitted by the G.P.O. on this band is 10W, and accordingly this represents the maximum input power of the transmitter described.

The transmitter was built primarily for telephony operation and it was decided at the outset that "high-level" (i.e. anode and screen) modulation should be employed. This method is generally considered more satisfactory than efficiency

modulation systems, and certainly has the advantage of requiring no elaborate or tricky setting-up procedure.

The R.F. Section

The R.F. section of the transmitter is extremely simple, and consists of a 615 triode as a Clapp variable-frequency oscillator feeding an 807 tetrode power amplifier (Fig. 1). The variable condenser controlling the V.F.O. frequency is fitted with a "Muirhead" type of slow-motion drive, as found on the well-known RF26 and RF27 units.

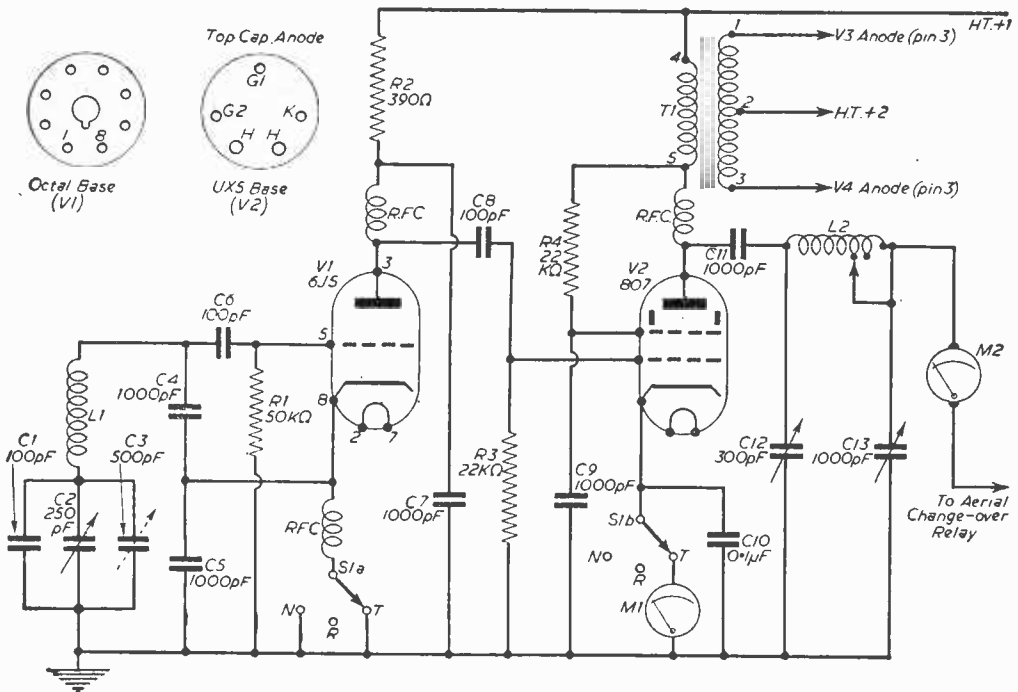


Fig. 1.—The V.F.O. and power amplifier.

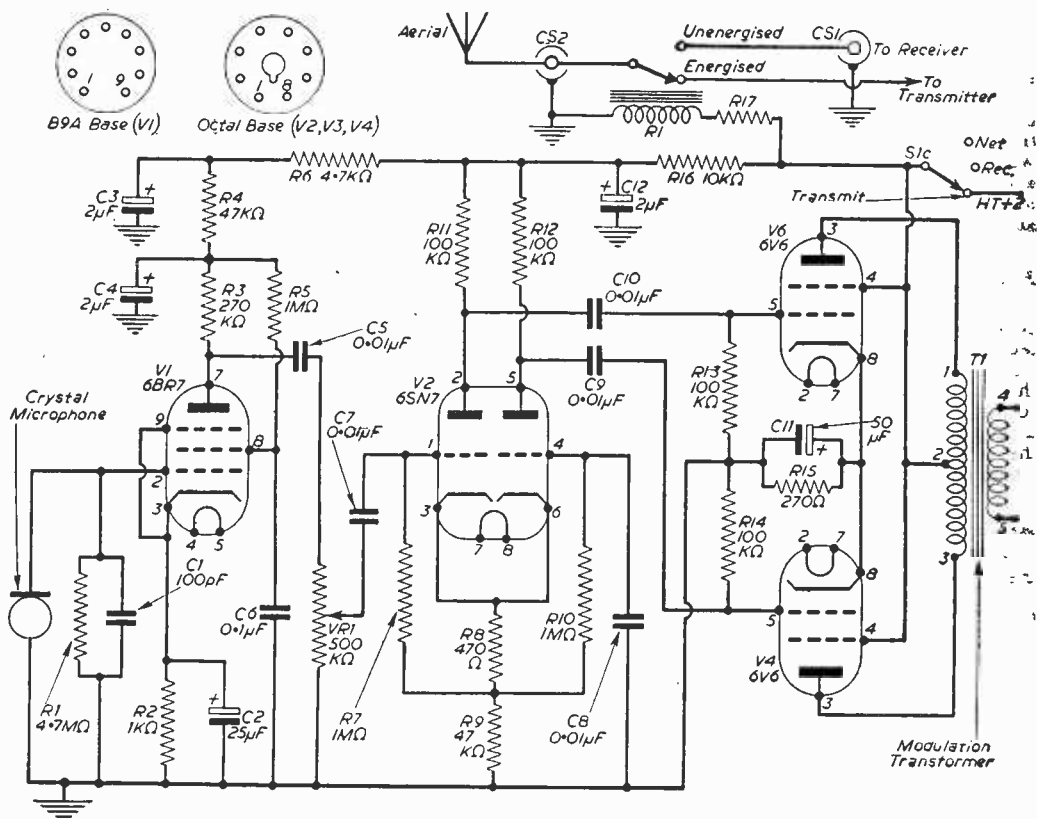


Fig. 2.—Circuit of the modulator.

It will be seen from the circuit diagram that the method used to match the output of the transmitter to the aerial system is the versatile "π-section". If difficulty is experienced in obtaining the 1000pF variable condenser required on top-band for aerial loading, a quite satisfactory alternative is a broadcast type 500pF twin-gang condenser with the two sections wired in parallel. This method was, in fact, used by the writer in the design shown here. By means of the π-section it will be found possible to match the output of the transmitter into almost any type of aerial; the exact method of tuning up is given later in the article under the heading "operating details."

The Modulator

The modulator employs a total of four valves (Fig. 2). The first valve (6BR7) is the pre-amplifier; the input circuit of this valve is designed for a crystal microphone. A crystal microphone is a

high impedance device, and consequently no matching transformer is required between the microphone and pre-amplifier grid circuit.

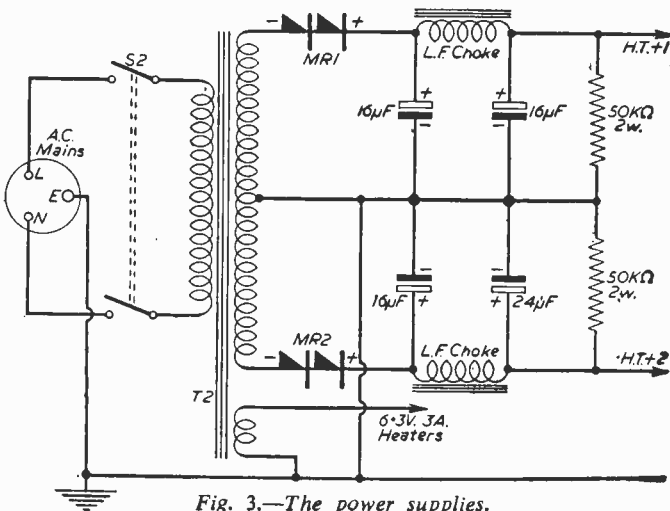


Fig. 3.—The power supplies.

The output of the 6BR7 is fed to the 6SN7 double-triode phase-splitter, which in turn feeds the grids of the 6V6 push-pull output valves. These are arranged to operate in class AB1: the common cathode resistor of 270Ω gives the cathode a bias of about 17V with respect to grid. The modulation transformer used in the equipment shown here was an ex-Government type, having a primary anode-to-anode impedance of $6,000\Omega$ and a secondary impedance also of $6,000\Omega$. However, any similar transformer should prove quite suitable.

Power Supplies

Separately smoothed power supplies are used for powering the R.F. section and the modulator section, as a precaution against frequency modulation of the carrier. Half-wave rectification is used; this makes it possible to use a single mains transformer having 300-0-300V and 6·3V windings arranged as shown in Fig. 3. The rectifiers used in the original were miniature contact-cooled types which performed very satisfactorily in operation.

Aerial Change-over

Aerial change-over is accomplished by means of the relay R1. This is a high impedance relay

($2,000\Omega$) and is energised from the modulator H.T. line via a suitable dropping resistor. Thus, when the function switch is in the "net" or "receive" positions the relay is unenergised and the aerial goes to the receiver. In the "transmit" position, H.T. is applied to the modulator H.T. line and the relay switches the aerial across to the transmitter.

Construction

The size of chassis used for the original transmitter was 14in. x 8in. The most suitable gauge of aluminium to use is 16s.w.g.; any lighter gauge tends to afford too little rigidity, and difficulty will be experienced in making the V.F.O. stable.

It is suggested that the power supply section be built first of all, since this will have to be completed in any case before the modulator or R.F. stage can be tested. No difficulty should be experienced in making the power supply section work satisfactorily, provided that good quality components are used. This applies particularly to the electrolytic smoothing condensers; "surplus" condensers are best avoided unless they have been rigorously tested. Good quality insulated sleeving should be used on all connecting wires and leads.

(To be continued)

PARTS LIST FOR FIG. 1.

Resistors:

R1 50k $\frac{1}{2}$ W. R3 22k $\frac{1}{2}$ W.
R2 390 Ω $\frac{1}{2}$ W. R4 22k 1W.

Capacitors:

C1 100pF. C10 0·1 μ F (350VW).
C2 250pF Var. C11 1,000pF*
C3 500pF pre-set. C12 300pF Var. (or
C4 1000pF* twin-gang 150pF with
C5 1,000pF* sections ganged).
C6 100pF. C13 1,000pF Var. (or
C7 1,000pF. twin-gang 500pF with
C8 100pF. sections ganged).
C9 1,000pF.

(C4, 5 and 11 are silvered mica).

Miscellaneous:

L1 42 turns 22s.w.g. enamelled wire, close-wound on lin. dia. former.
L2 80 turns, 24s.w.g. cotton-covered wire, close-wound on lin. dia. former; tapped at 40, 50, 60, 70 turns. (The various tapings should be tried until satisfactory loading is achieved.)
T1 Modulation transformer (see text).
One I.O. valveholder. V2 807.
One UX5 valveholder. S1 (a), (b)—function
M1 50mA f.s.d. meter. switch (see text).
M2 500mA f.s.d. R.F. REC All 2·5mH R.F.
meter. chokes.
V1 6J5.

PARTS LIST FOR FIG. 2.

Resistors:

R1 4·7M $\frac{1}{2}$ W. R6 4·7k $\frac{1}{2}$ W.
R2 1k $\frac{1}{2}$ W. R7 1M $\frac{1}{2}$ W.
R3 270k 1W. R8 470 Ω $\frac{1}{2}$ W.
R4 47k $\frac{1}{2}$ W. R9 47k $\frac{1}{2}$ W.
R5 1M $\frac{1}{2}$ W. R10 1M $\frac{1}{2}$ W.

R11 100k $\frac{1}{2}$ W. R15 270 Ω 3W.
R12 100k $\frac{1}{2}$ W. R16 10k 1W.
R13 100k $\frac{1}{2}$ W. R17 see text.
R14 100k $\frac{1}{2}$ W. VR1 500k Var.

(R11, 12 and 13 are of 5 per cent tolerance)

Capacitors:

C1 100pF. C7 0·01 μ F 350VW.
C2 25 μ F 12VW. C8 0·01 μ F 350VW.
C3 2 μ F 350VW. C9 0·01 μ F 350VW.
C4 2 μ F 350VW. C10 0·01 μ F 350VW.
C5 0·01 μ F 350VW. C11 50 μ F 50VW.
C6 0·1 μ F 350VW. C12 2 μ F 350VW.

Miscellaneous:

Microphone socket (coax or jack type).
CS1 } coax output
CS2 } sockets.
T1 Modulation transformer, Collins type 7R3.
One B9A valveholder.
Three I.O. valveholders.
Two three-way tag strips.
Two coaxial sockets.
S1 (c) function switch (see text).
R1 Aerial change-over relay (high impedance).

PARTS LIST FOR FIG. 3.

S2 Double-pole double-throw switch.
T2 Mains transformer: 300-0-300V 100mA;
6·3V 3A.
MR1 Contact-cooled (or selenium) rectifier;
300V 60mA.
MR2 As MR1 but 300V 100mA rating.
Three 16 μ F capacitors (electrolytic), 450VW.
One 24 μ F capacitor (electrolytic), 450VW.
Two 5H L.F. chokes.
Two 50k (or 47k) 2W resistors.

Resonant Capacity Checker

THE "UNKNOWN" CONDENSER IS USED TO TUNE AN R.F. OSCILLATOR

By J. Gray

THE bridge method of determining capacity is well known, and is used for both large and small condensers. When small capacities only are to be determined there is a generally less known method which can give results to a high degree of accuracy. This requires adjusting a tuned circuit to resonance with a signal of fixed frequency, adding the unknown condenser, and noting what shift in capacity is required to restore resonance. By this means the readings obtained can very nearly equal the accuracy with which the instrument is calibrated. For normal purposes, readings from about 2pF to 400pF or 500pF will be useful, and can be directly shown upon two scales. One scale covers about 2pF to 45pF, with an accuracy of reading against calibrations of about 1pF. The other scale covers about 50pF to 450pF.

A capacity tester of this kind is intended primarily for condensers used in radio frequency parts of a circuit. That is, the capacity range of trimmers, or small variable condensers, the value of small fixed condensers such as are used in tuned circuits, and low stray capacities such as may arise in switching circuits, valveholders and wiring, etc.

Battery or Mains

For dry battery running, the circuit in Fig. 1 is satisfactory. Small 22½V and 1½V batteries will have a very long life. The whole unit can be constructed in any convenient case.

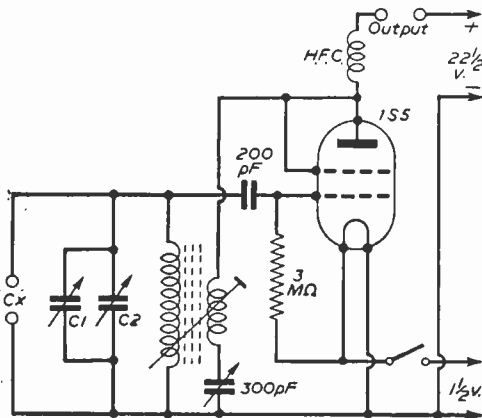


Fig. 1.—A battery circuit.



A completed unit.

If A.C. mains operation is preferred, the circuit in Fig. 2 will be found suitable. It should be noted that the 12-6V heater transformer also provides H.T. through a small rectifier. For smoothing, C3 and C4 can be any 25V or similar electrolytics, as high voltage condensers are not needed. There is little point in providing an increased H.T. voltage. Practically any 13V or 12-6V valve will be satisfactory. As phones are used to listen to the heterodyne note it is absolutely essential that the unit is isolated from the mains, and preferably earthed. No mains switch need be included, as it can be plugged into the supply as required.


For the ranges mentioned, C1 is 50pF, and C2 is 500pF. Air dielectric condensers of good quality are necessary. Those with semi-circular plates giving changes of capacity proportional to angular movement, are most suitable. Other condensers are satisfactory, but markings will be less uniform.

The unknown condenser Cx is joined to two terminals. These are best on an insulated panel, to avoid capacity between the condenser, or its leads, and a metal panel.

When the circuit is to be resonated against the output of a signal generator, the coil can be of any inductance covering about 500kc/s to 100kc/s with a parallel capacity of about 500pF. In many parts of the country resonance may be checked against the 200kc/s Light Programme, and a signal generator is then unnecessary. In this instance, the coil can best have an adjustable core, so that resonance at 200kc/s can be achieved with C1 fully closed, and C2 nearly closed. An ordinary long wave coil with reaction is suitable, turns being removed until resonance is obtained.

Calibration

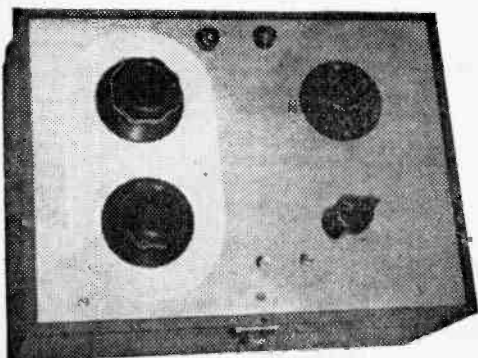For direct calibration, a few ceramic or silver mica condensers of low tolerance and known value



Another view of the capacity checker.

are required. Ceramic condensers can be obtained to a tolerance of 0.25pF. Silver mica condensers can have a tolerance of 2 per cent. It is unlikely that there will ever be any need for readings to a higher accuracy than this.

It will be remembered that condensers can be combined in series or parallel, to obtain other values. For example, two of 100pF in parallel will be 200pF, while two of 100pF in series will be 50pF. This will help in obtaining other check points.

With phones connected and sufficient reaction to provide a heterodyne note, the unit is tuned to zero beat with the signal generator, C1 being at maximum capacity, and C2 just below this, as in Fig. 3. Condensers of small value, up to about 45pF are then joined across the terminals. In each case C1 will have to be opened to obtain zero beat, and the capacity is marked on the scale. The negative sign is used because the calibration is effectively in terms of decreasing capacity. After closing C1 to restore resonance, C2 is similarly calibrated values up to about 450pF being used. The positions of intermediate marks can be estimated, after obtaining as many actual calibration

marks as possible. Markings towards the extreme maximum or minimum capacity settings must be obtained by calibration, as the change in capacity will not be uniform here.

Measuring Unknowns

To find an unknown capacity, first check that resonance is obtained with the signal generator or broadcast station, with the two variable condensers. Provided the circuit is resonated at the generator frequency, as shown by the absence of a note in the phones, the readings of C1 will not be influenced by the setting of C2. For example, if the coil is made to operate on 250kc/s, and the generator is not tuned exactly to this frequency, this will have no effect on the readings of C1, provided C2 is adjusted to resonance with no condenser connected.

When measuring values which will fall on the scale of C2, it is simplest to set the C2 dial, then tune the signal generator for resonance. It is only

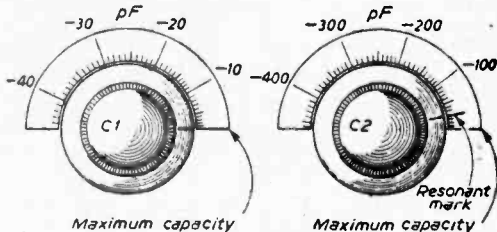


Fig. 3.—Capacity dials.

necessary that the dial upon which measurement is to be made should be at the correct resonant mark, before connecting the unknown condenser.

All values are simply read directly off the appropriate scale, the negative sign being ignored.

If test leads are necessary, these should be short. The earth lead is connected, and the other lead placed in its position and the capacity measured. The free lead should then be attached to the wiring or other stray capacity to be measured, taking care not to alter the test lead positions unduly. The difference in readings is then the required capacity.

Accuracy

It will be realised that the accuracy of readings depends on the accuracy of calibration, and upon C1 and C2 being unchanged. A case is thus necessary to give protection, and avoid dust on the condenser plates. Condensers C1 and C2 should also be of high quality, if possible, rigidly wired, and clear of batteries or other items which may move.

The scales on the capacity dials will be linear if the condensers used give capacity changes proportional to angular movement but even with non-linear condensers, it will be possible to estimate values of capacity between scale markings.

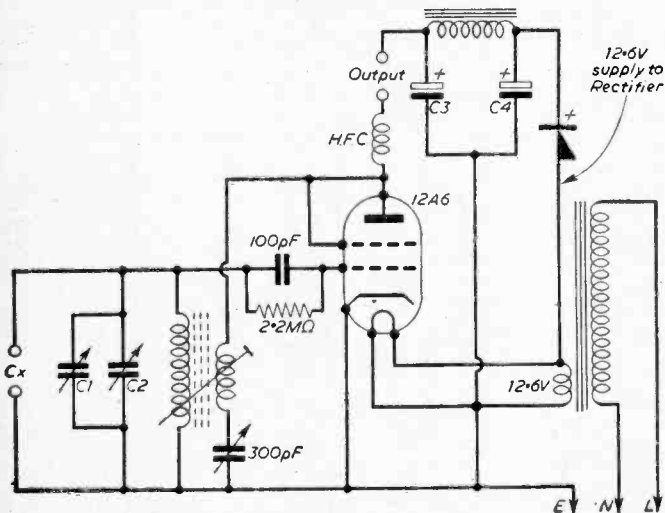



Fig. 2.—A circuit for A.C. mains.

Low Drift V.H.F. Receiver

CHASSIS AND WIRING DETAILS

By E. H. Berny

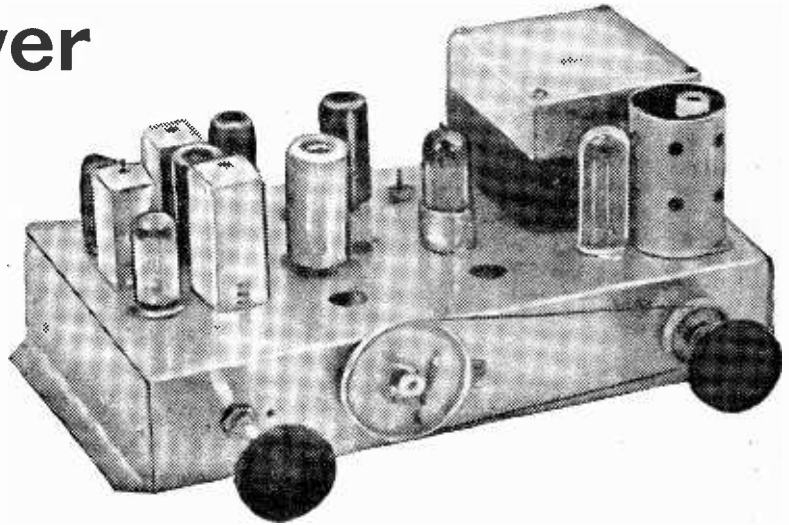(Continued from page 419 of the September issue)



THE type of aerial required for this receiver will depend on local reception conditions and on the number of I.F. stages used. A "picture rail" aerial can be formed from a length of flat twin p.v.c. flex by parting the conductors at one end for a length of 2ft 6in. and extending them horizontally

along a picture rail to form a simple dipole 5ft long, the remainder of the flex being used as a down lead to the receiver.

A dipole with reflector for fitting in a loft is easily made from a length of timber and some pieces of metal tube of $\frac{1}{4}$ in. or $\frac{3}{16}$ in. diameter as shown in Fig. 10. It is quite satisfactory to lay this upon the rafters and no special mounting arrangements are necessary. The dipole should of course be sited perpendicular to the direction of the transmission and the downlead should be ordinary 80 Ω co-axial. The magnitude of the signal obtained depends almost entirely on the height of the dipole above the ground.

Tuning Indicator

For general purpose listening it is satisfactory to tune the receiver by ear, the operation being carried out not for the greatest volume but for freedom from distortion. For critical listening, however, it may be preferred to employ a tuning indicator and this can easily be added if desired. The EM34 is a suitable valve, having a double display requiring only 5V for zero shadow angle on the more sensitive side. Fig. 11 shows how it should be connected. It will be convenient to fit the valve with its holder and associated resistors, except R33, at the end of about 12in. of flexible four core cable, the other end being taken into the

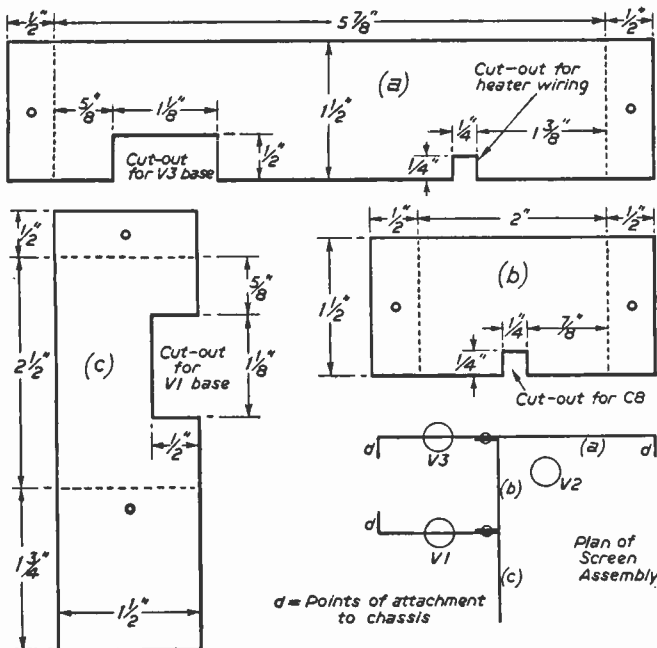


Fig. 4.—Dimensions and assembly of the screens.

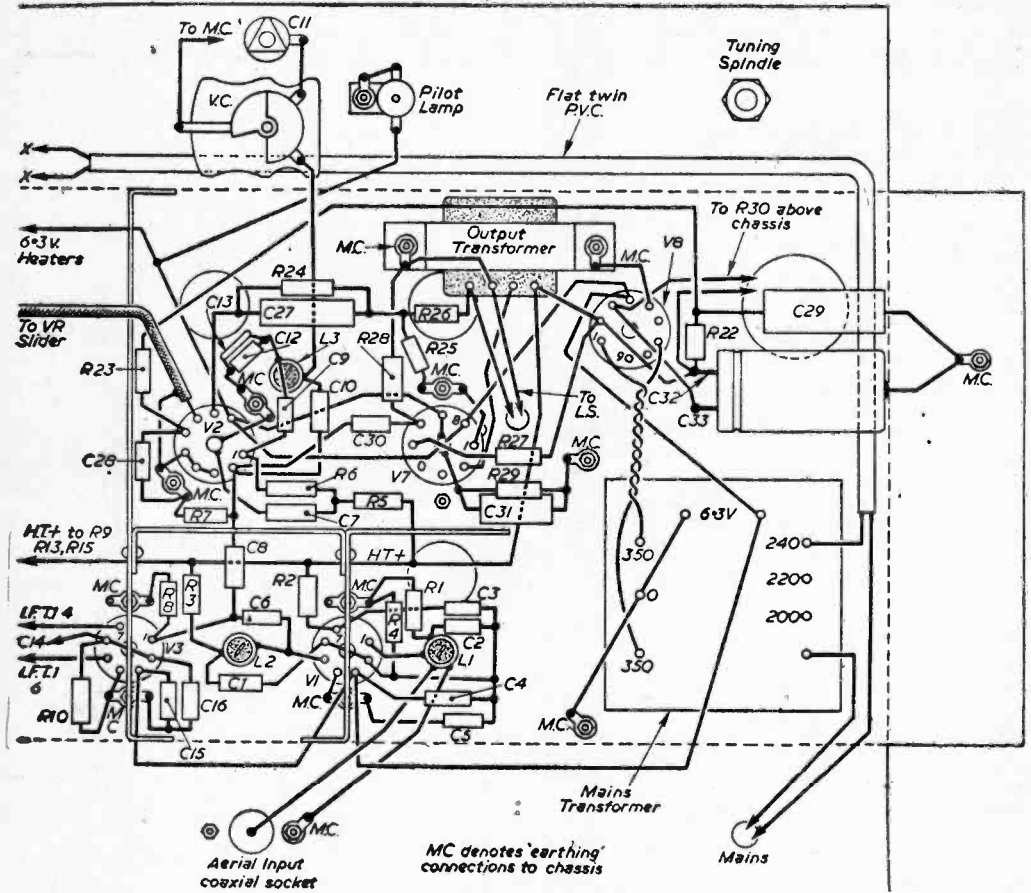


Fig. 5.—Wiring diagram (see also Figs. 6 and 7).

chassis and connected appropriately. The indicator can then be fitted in any desired position in the cabinet. Resistor R33 should be mounted close up to the negative end of C26.

A more exact indication can be obtained, using practically any type of "magic eye" by connecting its control grid to the junction of C23 and R21. The voltage at this point is zero when the receiver is exactly in tune and the valve must be arranged as a null point indicator. First connect the control grid to earth and insert a 50k wire wound potentiometer between cathode and earth as in Fig. 11; adjust the slider for zero shadow angle in the indicator. The effective resistance between cathode and earth may now be measured and the potentiometer replaced by a fixed resistor of the same value. Transfer the grid to the control point, omitting R33. There will be dimming of the display due to loss of volts between target and cathode but serviceable brilliance will be obtainable with most valves.

I.F. Alignment

The receiver can be aligned without instruments if necessary but the preferred method requires an

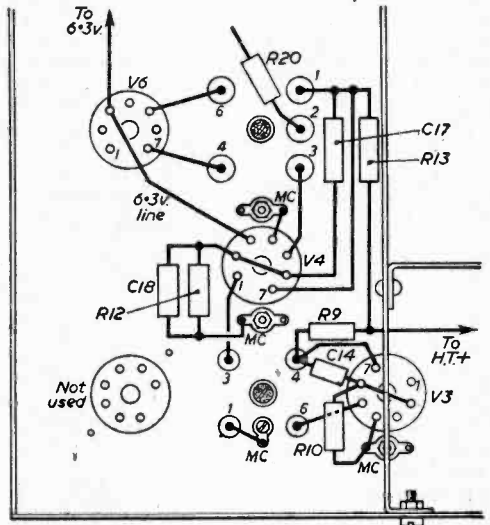


Fig. 6.—Wiring of single stage I.F. amplifier.

AM signal generator and a valve or high resistance voltmeter—20,000 Ω /V for preference.

When the receiver is first switched on, a check should be made to see that the correct voltages appear at all the valve electrodes and that the negative feedback circuit is correctly connected. This check should be made outside TV viewing hours if possible as with incorrect voltages or connections it is possible to fall into neighbourly disfavour by causing patterning on Band III television. If all is well connect the meter on the 10V range across C26 and inject an unmodulated signal at 10.7Mc/s at the grid of V4. Adjust the primary (top core) of the detector transformer and both cores of the IFT2 for maximum reading on the meter. This signal from the generator should be reduced progressively as the circuits come into line so that the meter shows no more than about 5V. Transfer the generator to the grid of V3 and adjust both cores of IFT1. Now connect the meter between earth and the junction of C23 and R21 (point Z in the circuit diagram) and adjust the bottom core of the detector transformer for zero reading. This adjustment will affect the tuning of the primary which should be retuned for maximum; only a slight adjustment should be necessary. The acceptance bandwidth of the I.F. amplifier should now be checked by moving the generator slowly over the range 10.4 to 11Mc/s, with injection at V3 grid and the meter between point Z and earth. A maximum voltage should be observed at 10.6, zero at 10.7 and a maximum of reverse polarity at 10.8Mc/s. Check that the two maxima are of equal magnitude and equidistant from zero.

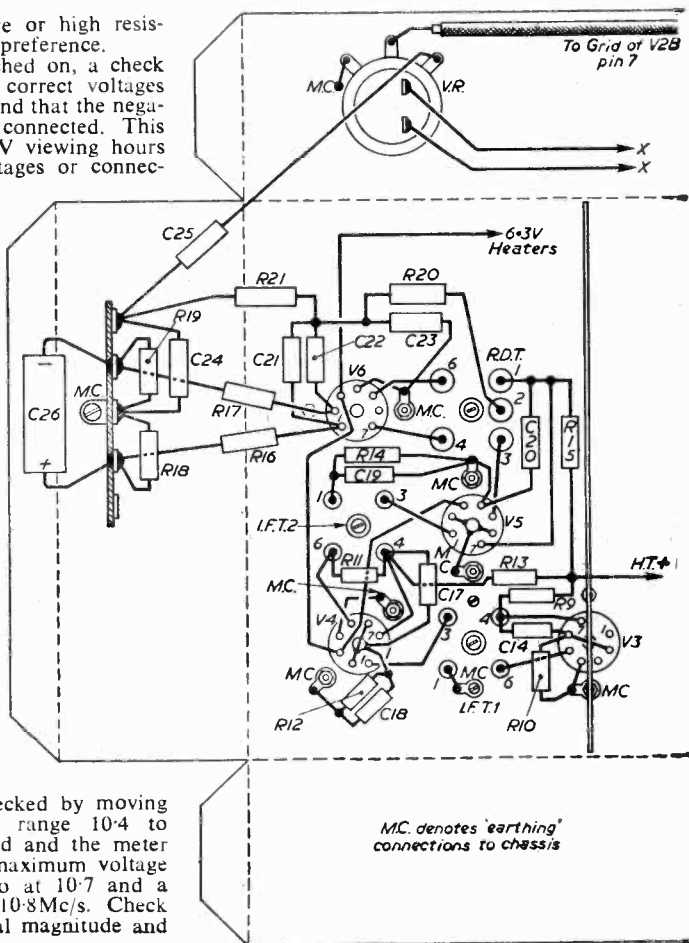


Fig. 7.—Wiring of two-stage I.F. amplifier and ratio detector.

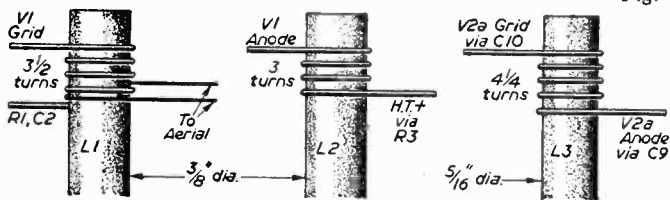


Fig. 8.—Coil winding details.

position between the two maxima that must be found.

Oscillator Tuning

The oscillator tuning may be adjusted with a signal generator or on a BBC transmission; the latter is perhaps easier. Commence with C11 at about half

If there is only one I.F. stage, signal injection should commence at V3 grid.

When manipulating the bottom core of RDT, it should be noted that the two maxima and centre zero occur over a relatively small portion of its travel and that if the correct position is overrun, further core movement will have no observable effect. It is the zero

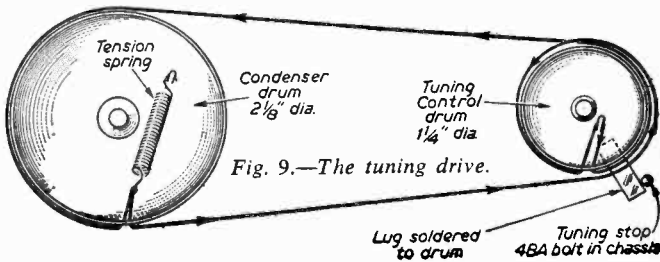


Fig. 9.—The tuning drive.

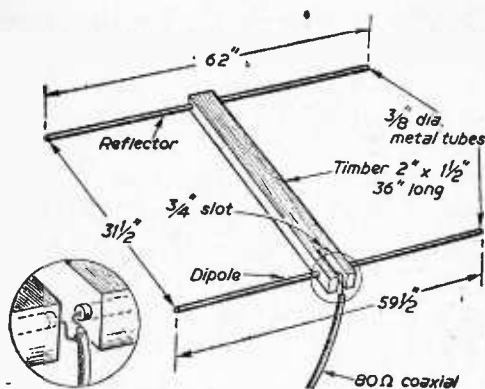


Fig. 10.—Simple loft aerial.

capacity, VC about 10deg open and the core of L3 fully engaged. Connect an aerial, advance the volume control and withdraw the core of L3 very slowly till the lowest frequency transmission to be received (normally the Light programme) is heard. Check by reference to the

published programme that it is in fact this transmission. Rotate VC and check its range: if insufficient, it can be increased by unscrewing C11 a little and if this pushes the Light programme off the lower end of the range, it can be brought back by screwing in the core of L3. If the range is too great, the reverse procedure applies. Adjust finally so that all the stations to be received are distributed neatly within the tuning range.

R.F. Stage

Select a transmission about the centre of the tuning range and adjust the cores of L1 and L2 for maximum reading on the meter connected across C26. The transmission must be attenuated in some way for this operation so that the meter reading does not exceed about 5V; alternatively, a signal from the generator can be used.

Drift Test

The oscillator should now be checked for long term drift. Place the receiver on the bench, right side up and raised $\frac{1}{4}$ in. from the surface to allow ventilation below the chassis so that operating conditions are simulated. Connect the meter across C26 and switch on. After 15 minutes, tune accurately to a transmission; examine after one

(Continued on page 518)

COMPONENTS LIST FOR FIGS. 1 AND 2 LAST MONTH.

Resistors: (all $\frac{1}{2}$ W unless otherwise stated)

R1—47k.	R18—10k 10 per cent.
R2—4.7k.	R19—10k 10 per cent.
R3—1k.	R20—68 Ω .
R4—150 Ω .	R21—27k.
R5—4.7k.	R22—47k.
R6—10k.	R23—0.22M.
R7—22k.	R24—3.3k.
R8—1k.	R25—22 Ω .
R9—4.7k.	R26—330 Ω .
R10—150 Ω .	R27—470 Ω .
R11—47k.	R28—0.47M.
R12—150 Ω .	R29—360 Ω , 1W.
R13—4.7k.	R30—2.5k, 10W.
R14—47k.	R31—1M.
R15—47k.	R32—1M.
R16—1k 10 per cent.	R33—1M.
R17—1.5k 10 per cent.	VR—1M with switch.

Capacitors:

C1—1,000pF ceramic.
C2—1,000pF ceramic.
C3—1,000pF ceramic.
C4—1,000pF ceramic.
C5—1,000pF ceramic.
C6—47pF ceramic.
C7—2,000pF ceramic.
C8—2.2pF ceramic (see text).
C9—300pF ceramic.
C10—22pF ceramic.
C11—3/30pF air spaced trimmer.
C12—8.2pF ceramic, N. 750K \pm 0.5pF.
C13—15pF silver mica \pm 0.5pF.
C14—0.01 μ F ceramic or non-inductive paper.
C15—2,000pF ceramic.
C16—2,000pF ceramic.
C17—0.01 μ F ceramic or non-inductive paper.
C18—0.01 μ F tubular ceramic.
C19—47pF mica or ceramic.
C20—0.001 μ F ceramic/non-inductive paper.

C21—300pF mica or ceramic.
C22—300pF mica or ceramic.
C23—300pF mica or ceramic.
C24—2,000pF ceramic.
C25—0.01 μ F paper.
C26—8 μ F electrolytic, wire ended.
C27—25 μ F 25VW electrolytic.
C28—47pF ceramic.
C29—8 μ F electrolytic, 500VW.
C30—0.01 μ F paper.
C31—25 μ F 25VW electrolytic.
C32—
C33—
VC—Tuning capacitor 3-15pF. (Jackson type C804).

Valves:

V1 EF91—B7G Base with screen.
V2 ECC81—low-loss, ceramic, B9A Base with screen.
V3 EF91—B7G Base with screen.
V4 EF91—B7G Base with screen.
V5 EF91—B7G Base.
V6 EB91—B7G Base.
V7 EL42—B8A Base.
V8 EZ80—B9A Base.

Transformers:

IFT1, IFT2—10.7Mc/s I.F. transformers. (Denco).
RDT—10.7Mc/s ratio detector transformer. (Denco).
OPT—Output transformer 9,000 Ω : 3 Ω .
Power—Input 200-240V. Output 350-0-350V 80mA, 6.3V, 0.3A.

Coil Formers:

L1, L2— $\frac{1}{8}$ in. diameter, $\frac{1}{2}$ in. dust core.
L3— $\frac{1}{8}$ in. diameter, $\frac{1}{2}$ in. dust core.

Easy-to-build kit-sets of



highest quality at lower cost

HI-FI F.M. TUNER

Tuning range 88-108 Mc/s. For your convenience this is available in two units sold separately as follows: Tuner Unit (FMT-4U) with 10.7 Mc/s I.F. output £3.2.0, inc. P.T.). I.F. Amplifier (FMA-4U) complete with cabinet and valves (£10.10.6).
Total £13.12.6



F.M. TUNER

HI-FI 16W. STEREO AMPLIFIER Model S-88

10mV. basic sensitivity (2 mV. available, £1 extra). Ganged controls. Stereo/Monaural gram. radio and tape recorder input. Push-button selection. Two-tone grey metal cabinet. £25.5.6



S.33

6-TRANSISTOR PORTABLE Model UXR-1

Pre-aligned I.F. transformers, printed circuit, 7 x 4in. high-flux speaker. Real hide case. £14.18.6



S-88

DUAL-WAVE TRANSISTOR RADIO UJR-1

This sensitive headphone set is a fine introduction to electronics for any youngster. £2.16.6



DX-40

RES.-CAP. BRIDGE Model C-3U

Measures capacity 10pF to 1,000µF resistance 100Ω to 5 MΩ and power factor. 5-450 v. test voltages. With safety switch. £7.19.6



UXR-1

AUDIO SIGNAL GENERATOR Model AG-9U

10 c/s to 100 kc/s. switch selected. Distortion less than 0.1% 10 v. sine wave output metered in volts and dB's. £19.3.0

VALVE VOLTMETER Model V-7A

Measures volts to 1,500 (D.C. and R.M.S.) and 4,000 pk. to pk. Res 0.1Ω to 1,000 MΩ. D.C. input impd. 11MΩ. Complete with test prods, leads and standardising battery. £13.0.0



OS-1

Portable 2 3/4" SERVICE 'SCOPE Model OS-1

Compact portable 'scope ideal for servicing and general work. Y amplifier sensitivity 10 mV/cm; response ± 3 dB 10 c/s-2.5 Mc/s. Time base 15 c/s-150 kc/s. Printed circuit. Case 7 1/2 x 4 1/2 x 12 1/2 in. long. Wt. only 10 1/2 lb. £18.19.6



SSU-1

5 in. OSCILLOSCOPE Model O-12U

Has wide-band amplifiers, essential for TV servicing, F.M. alignment, etc. Vertical freq. response 3 c/s. to over 5 Mc/s. without extra switching. T/B covers 10 c/s to 500 kc/s. in 5 ranges. £34.15.0

NEW MODELS include:

Grid Dip Meter, GD-1U, £9.19.6

Transistorised Grid Dip Meter, £9.18.6


Tape Amplifier—

Mono (TA-1M) £16.14.0

Stereo (TA-1S) £22.4.0

'PACKAGED DEALS' of Hi-Fi

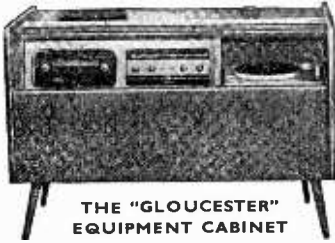Equipment including TAPE DECKS (Collaro or Truvox), RECORD PLAYERS (Collaro or Connoisseur and DECCA ffs PICK-UPS. Write in to see how these deals save you further money.



THE "GLOUCESTER" EQUIPMENT CABINET

6-W STEREO AMPLIFIER Model S-33

3 watts per channel, 0.3% distortion at 2.5 w/chnl. 20dB N.F.B. Inputs for Radio (or Tape) and Gram., Stereo or Monaural, ganged controls. £11.8.0 Sensitivity 100 mV.

TRANSCRIPTION RECORD PLAYER RP-1U

4-speed A.C. motor. Ronette Stereo/Mono pick-up. Complete with plinth. £12.10.0

HI-FI SPEAKER SYSTEM Model SSU-1

Ducted-port bass reflex cabinet "in the white". Twin speakers. With legs £11.12.6. £10.5.6

"HAM" TRANSMITTER Model DX-40U

from 80-10 m. Power input 75 w. C.W., 60 w. peak C.C. phone. Output 40 w. to aerial. Compact and self-contained. Prov. for V.F.O. £29.10.0

AMATEUR TRANSMITTER Model DX-100U

Covers all amateur bands from 160-10 metres. Self-contained including Power Supply Modulator and V.F.O. £78.10.0

"GLOUCESTER" EQUIPMENT CABINET

46 1/2 x 30 x 21 in. deep. Mk.1 houses Record Player, Stereo Amplifier, F.M. Tuner, records, etc. Mk.11 will house a Tape Deck in addition. Left in the white for finish to personal taste. Mk. 1 ... £15.18.6 Mk. 11 ... £17.8.6

"COTSWOLD" HI-FI SPEAKER SYSTEM KIT

Acoustically designed enclosure "in the white", 26 x 23 x 15 1/2 in., housing a 12in. bass speaker with 2in. speech coil, elliptical middle speaker and pressure unit to cover the full frequency range of 30-20,000 c/s. Complete with speakers, cross-over unit level control, etc. £19.18.6

COMPLETE MATCHED STEREO OUTFIT

Includes record player, amplifier and twin speaker systems (pedestal speaker legs optional £42.10.0 £2.14.0 extra).

"CHEPSTOW" EQUIPMENT CABINET

Ideal cabinet for small rooms or armchair operation. Houses Record Player, F.M. Tuner and Stereo Amplifier. £10.10.0

SINGLE CHANNEL AMPLIFIER, MA-12

10-12 watt Hi-Fi amplifier. Extremely low distortion and wide frequency range. £9.19.6

STEREO CONTROL UNIT, USC-1

Luxury model with press-button inputs to suit any pick-up or tuner and most tape-heads. Output 1.3 v. R.M.S. per channel. Printed circuit construction. £17.19.6

STEREO HEAD BOOSTER, USP-1

Ideal for boosting tape-head output and low output pick-ups (e.g. £5.19.6 Decca ffs).

VAR. FREQ. OSCILLATOR VF-1U

From 160-10 m. Ideal for our DX-40U and similar transmitters. £10.12.0 Price less valves £8.19.6.

Prices include free delivery UK Deferred Terms available on orders over £10

Please send me FREE CATALOGUE (Yes/No).....

Full details of model(s).....

NAME

ADDRESS


PW10

DAYSTROM LTD.

DEPT. P.W.10, GLOUCESTER, ENGLAND

A member of the Daystrom Group, manufacturers of the WORLD'S LARGEST-SELLING ELECTRONIC KITS

More for less...

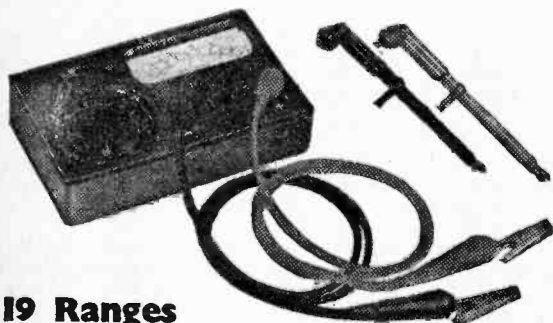

19 Ranges

D.C. Voltage	A.C. Voltage
0-100mV.	0-10 V
0-2.5 V.	0-25 V.
0-10 V.	0-100 V.
0-25 V.	0-250 V.
0-100 V.	0-1000 V.
0-250 V.	
0-1000 V.	
D.C. Current	
0-100μA	
0-1mA	
0-10mA	
0-100mA	
0-1A	
Resistance	
0-20,000Ω	
0-2MΩ	

List Price: **£9:10s.**

complete with Test Leads and Crocodile Clips.

Leather Case if required: 39/-

Size: 5½ x 3½ x 1½ in.

Weight: 1½ lb. approx.

Designed to offer the widest possible range of accurate and reliable measurements at the lowest possible price, the versatility and usefulness of the Multiminor are now further extended by specially designed leads. These new leads, available at no extra cost, will accept crocodile clips or PRODCLIPS.

The Multiminor takes full advantage of the possibilities of printed circuit techniques to achieve outstanding compactness and economy of weight. The scale is clear and open. The fine red colour pointer and effectively damped movement facilitate easy and rapid reading.

For use in Radio, TV, Electronics, Motor Vehicles, domestic appliances, workshop equipment, you'll find the Multiminor a great little meter!

Use PRODCLIPS with the MULTIMINOR (Pat. No. 748811)

These cleverly designed spring-loaded insulated prods are the complete answer to a long-standing problem. Press the trigger to open, release to grip. Keep your hands free no matter how difficult of access your test points may be.

15/- per pair.

...with the

MULTIMINOR

Write now for illustrated literature to:—

AVO LTD

AVOCET HOUSE - 92-96 VAUXHALL BRIDGE ROAD
LONDON - S.W.1

VIctoria 3404 (12 lines)

A MEMBER OF THE METAL INDUSTRIES GROUP OF COMPANIES

be TRANSISTOR-WISE! be POCKET-WISE!



"RECO" MIDDY ONE

(Medium and Long Waves.) Size 4½ x 3½ x ¾ in. Variable regen. control, Vari Q Ferrite Rod Aerial. "Sonotone" Dynamic Earpiece. Months of listening pleasure from 1½ volt pencil. Complete Kit with EDISWAN TRANSISTOR and easy build plans, 39/6, post 1/6. Data 1/6.

"RECO" PUSH-PULL FOUR TRANSISTOR KIT

(Medium and Long Waves with two S/W Coils FREE upon request.) Case size as PPS. New improved circuit. 3in. High Grade Moving Coil Speaker. Bias sensitivity volume control. Ferrite Rod Aerial. Gleaming Pale Blue Polystyrene Case with contrasting Speaker Grille in Red. Complete Kit with 4 best grade EDISWAN TRANSISTORS and 3 volt battery, £5.3.6, p.p. 2/6. Data 1/6.



"RECO" PUSH-PULL FIVE TRANSISTOR KIT

(Size 6½ x 4½ x 1½ in.) Medium, Long Waves and Trawler Band. Indoors or outdoors this brilliant radio brings Home and Continental Stations to your finger-tips. High Grade 3in. Moving Coil Speaker. Regenerative receiver with EDISWAN TRANSISTORS, XC101's (350mw) Push-pull Output Stage. High Gain Ferrite Rod Aerial. Gleaming Pale Blue Polystyrene Case with Contrasting Speaker Grille in Red. Complete Kit with easy build diagrams, etc., £6.9.6, p.p. 2/6. Data 2/6. (Free with kit). A customer in Dorset writes—"Makes fine car radio."

"RECO" SUPER TRANSIGEN FOUR

Medium and Long Waves. Four first grade EDISWAN TRANSISTORS, XA104, XB113, XC101, XC101. High gain Ferrite rod aerial. 3in. High Flux Moving Coil speaker. Performance as Transigen Three but with extra stage for speaker output. Case as PP5. Complete kit, with 4½ volt battery, £5.3.6. Post, etc., 2/6. Data 2/6.

"RECO" TRANSIGEN THREE TRANSISTOR KIT

(Case as PP5.) (Medium, Long Waves and Trawler Band.) Fitted Super High Gain Ferrite Rod Aerial. R.F. Stage, EDISWAN TRANSISTORS. On test: tuned in Home, Light, Third, Radio Luxembourg, A.F.N. and many others at good listening level. The Prototype was tested at approximately 50 miles from nearest transmitter. Complete Kit, with super dynamic miniature earpiece, 79/6, p.p. 2/6. With B.A. rep. 75/-, if reception conditions warrant, a small speaker may be fitted under red speaker grille.



"RECO" SENSITONE THREE (5 stage reflex) Medium and Long Wave


Uses latest Ediswan Transistors (XA104, XB113, XC101) for sensitivity and selectivity. Improved R.F. stage for greatly increased gain. On test tuned in (50 miles London) Home, Light Radio Luxembourg and many others on inbuilt ferrite rod aerial. Fitted volume/sensitivity control. Appearance as Transigen-3. Easy-build practical wiring diagrams. After Sales Service to help you if you go wrong. Fitted with a full coned 3in. moving coil speaker. Complete kit including long-life battery, 89/6, post, etc., 2/6. Circuit and parts price list 1/6.

AFTER SALES SERVICE FOR YOUR GUIDANCE

RADIO EXCHANGE CO.

27 HARPUR ST., BEDFORD.
Name, address BLOCK letters please.

Telephone 2367
Closed 1 p.m. Saturdays.

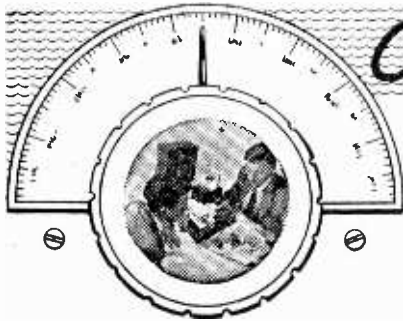

On Your Wavelength

BY THERMION

Image Intensification

NO doubt many radio enthusiasts saw the picture on BBC TV of specimens under the electron microscope at very large magnification.

A deal of research was necessary before the technique finally proved possible, however. Normally, the electron microscope can be viewed only in the dark by one person at a time.

One method to eliminate viewing in the dark is to transfer the image electronically to cathode ray tubes remote from the microscope and if possible to intensify the image; the problems involved in doing this have been discussed for many years. The operation of the new intensifier relies on the increase in the conductivity of selenium which occurs when it is bombarded by high energy electrons. The efficacy of the intensifier was clear from the excellent TV pictures, and, no doubt, it will now be possible to employ closed-circuit television with electron microscopes where large audiences are involved.

Aerial Masts

MOST listeners to radio and many who view television tend, I find, to take the technical side for granted. I was therefore particularly interested to come across details of the construction of aerial masts. Since the construction of the Sutton Coldfield television mast ten years ago the BICC Group have provided most of the high masts and towers for BBC and ITA networks. One of the latest in this sequence, a 750ft stayed steel mast weighing 215 tons overall, commands an impressive view of the English Channel from the cliffs at Hougham nr. Dover.

The mast has a triangular cross section, each side measuring 6ft 6in. with solid round steel legs braced together by steel angle lattice work. The mast is carried on a steel pedestal which rests on a 22ft square concrete block foundation. A 2in. diameter steel ball recessed into the bearing surface provides registration.

Steel wire stays with a tensile strength of 110/120 tons per square inch provide the requisite support, adequate allowance being made for the most severe weather con-


ditions. They are anchored to concrete blocks varying between 19 and 73cu yd in volume. The heaviest individual stay weighs 2½ tons and had to be lifted to a height of 650ft.

F.M. Results

Most constructors—some very technically minded—do not seem to realise that poor results on F.M. may often be attributed to a poor aerial system.

Curious effects sometimes occur due to reflection. In one case which I investigated, "ghosting" was only present at certain times. Investigation eventually proved this to be caused by the rise and fall of a nearby gas reservoir. When the reservoir was fully charged signal reflection occurred from near the top, which of course, disappeared completely when some of the gas was discharged and the height of the reservoir decreased. The opposite effect occurred in another case. It was found that the reflected signal was being used, and as the reservoir decreased in height so the signal became fainter and eventually disappeared until the reservoir was recharged with gas!

There is no simple solution. Nothing can be done in the set itself to cure the trouble, and in extreme cases it is often necessary to sample the signal conditions around the area in which the aerial can be erected until the best conditions are found. A highly directional aerial is essential, and if virtually zero pickup from the side of the aerial is a necessary factor, then two three- or four-element arrays may need to be mounted side-by-side spaced by about half wavelength and connected together via a coaxial transformer or similar arrangement. Certainly in a "difficult" location, some experimenting with the position of the aerial is worth while.

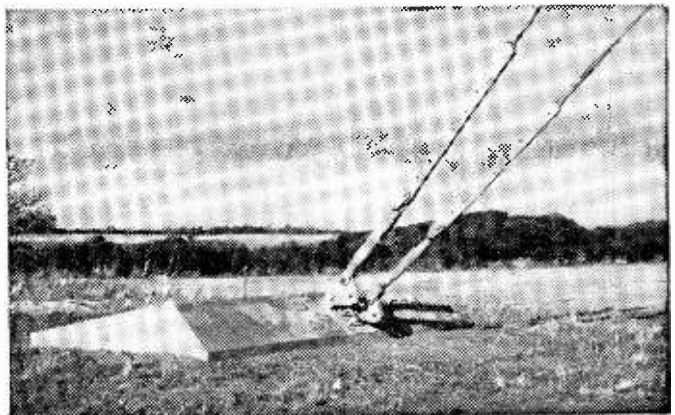

One of the concrete blocks anchoring two stays in the ITV mast at Hougham.

RADIO SHOW 1960

A review of some of the products shown at Earls Court this year


BELLING & LEE LTD.
STAND NO. 63

Distribution equipment was one of the main features on this stand. This equipment has been installed successfully in many locations throughout the country to provide radio and television signals to towns, villages, housing estates, schools, etc. The "Belling-Lee" main distribution station is assembled from standard basic units to meet individual requirements and is enclosed in a stove-enamelled case. It operates either directly from the mains power supply or via a 50-64V supply superimposed upon the coaxial line.


A range of aerials and accessories for radio, television, and VHF/FM was also exhibited.

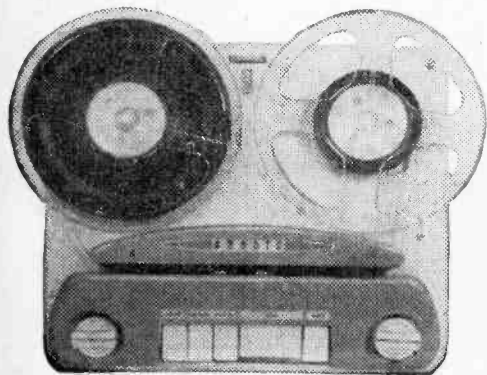A. F. BULGIN & CO. LTD. **STAND NO. 66**

A large range of new and established products was to be seen on this stand, many lines having originated from last year's show. The Technical staff were on hand to give visitors information concerning the component range and other exhibits. Among the many new components to be seen were the Multi-Legend Multi-Lamp Signal Fittings. These are for use for panel-mounting, having a number of internal I.E.S. lamp sockets and adjustable light-barriers with a choice of legends, digits, and characters in a full choice of colours for successive or together lighting.



The Collaro tape transcriber.

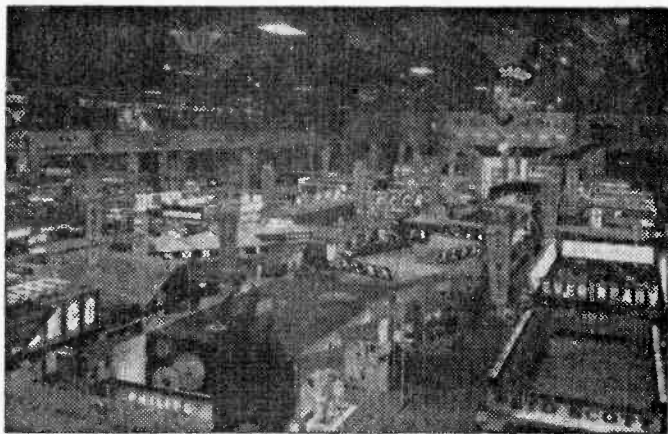

A view of the stands at last year's Show.

BRIMAR ELECTRONICS LTD. **STAND NO. 104**

On this stand was exhibited a comprehensive range of valves and low H.T. valves for car radios, with a wide range of types suitable for AM/FM radio receivers and hi-fi sound systems. A selection of cathode ray tubes suitable for domestic and industrial applications was also on display.

COLLARO LTD. **STAND NO. 38**

On this stand was shown a range of gramophone units and tape equipment. In the tape deck field the "Studio" deck was again featured. In its latest form this deck is a single direction twin-track machine operating at speeds of 1 $\frac{1}{2}$, 3 $\frac{1}{2}$ and 7 $\frac{1}{2}$ in./sec. Space is provided so that a third head for monitoring or stereo can be fitted. The latest addition to the range of record reproducing equipment was displayed, namely the "Studio" C60 record changer. This is a four speed automatic record changer which will play any size record from seven inches to twelve inches. The motor is of a new design and is a true four pole variety. Also on show was the Collaro transcription unit TRP594.

DAYSTROM LTD. **STAND NO. 112**


The Daystrom stand this year displayed several new models, on show for the first time. Of special interest to amateur constructors was a grid dip meter Model GD91U. This can be used for checking the resonant frequency of tuned circuits without removing components. The new Heathkit model was a four-wave seven transistor portable, Model RSW-1. This set operates on short, medium and "trawler" wavebands and has a dual-aerial system consisting of an internal ferrite rod type for medium and "trawler" bands and an integral telescopic aerial for the two short wave bands.

DYNATRON RADIO LTD. STAND NO. 52

As in previous years, Dynatron exhibited a wide range of radiograms, record players and tape recorders. Among the new additions was the Oxford RG17. This radiogram reproduces stereo and monophonic records of all sizes and speeds. A 9-transistor portable radiogram which reproduces records of all sizes and speeds, the Safari RG23 will provide music wherever you are. Three high quality transistor radios were displayed and the first tape recorder to be introduced in the Dynatron range, the Cordova.

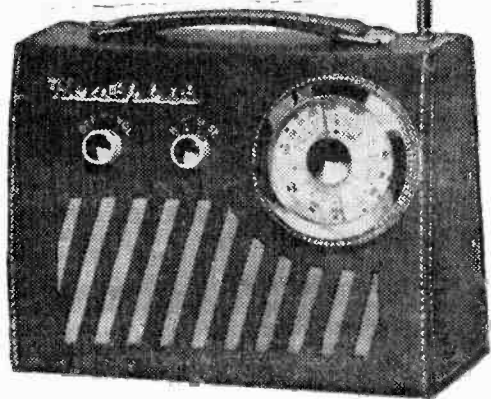A. H. HUNT (CAPACITORS) LTD. STAND NO. 49

On this stand were all types of miniature and standard capacitors for all radio, television, electronic and electrical industrial applications. This firm also exhibited a new condenser using as a dielectric metallised paper with a special film in working voltages




The Heathkit seven transistor portable Model RSW-1. (Daystrom Ltd.)

up to 1,000 D.C. at temperatures from (-40) deg C to (+100) deg C. A number of special types of condenser for horizontal and vertical mounting on printed circuit board was also of interest to visitors.

KOLSTER-BRANDES LTD. STAND NO. 22

A large range of radiograms, record players, tape recorders and television sets was shown on this stand. Among the new radio models shown were the Gavotte RN10 and the Romance light-weight transistor portable with car sockets, push button controls and a high sensitivity speaker, Model RP21. A new stereophonic radiogram the Barcarolle RG20 was displayed and this model incorporated twin speakers and piano-key controls. A portable tape recorder model, RT20, has a 4-stage amplifier magic eye record level indicator and wide range tone control. It also has a wide frequency response.

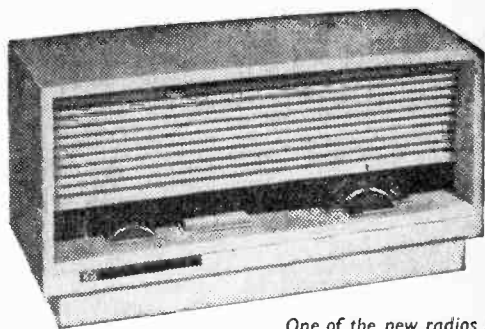


One of the new radios by Kolster-Brandes Ltd., the Gavotte RN10.

J. & A. MARGOLIN LTD. STAND NO. 44

Among the many products on this stand was the new Dansette Transistor Radiogram, model TRG. This is a fully transistorised and battery operated model. The radio unit comprises of six transistors and one diode, with push-pull output at 600mW. It has a 5in. speaker with a high gauss magnet. Record players for every purpose were on show, ranging from battery operated transistorised models for use out of doors or in caravans to the more conventional mains operated units with higher outputs. Also among the exhibits on this stand were a mono radiogram and two transistorised portable radios.

MULTICORE SOLDERS LTD. AND MULTIMUSIC LTD. STAND NO. 7J

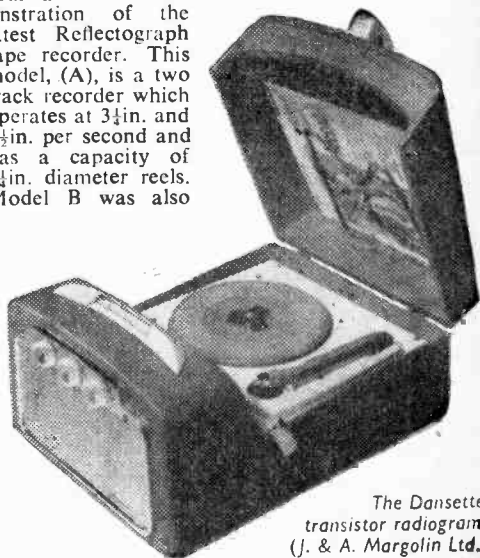Visitors to this combined stand were able to hear a stereo demonstration of the latest Reflectograph tape recorder. This model, (A), is a two track recorder which operates at 3½in. and 7½in. per second and has a capacity of 8½in. diameter reels. Model B was also



The Dansette transistor radiogram. (J. & A. Margolin Ltd.)

on show; this has all the features of Model A but is a four-track instrument providing a playing time at $3\frac{1}{2}$ in./sec of 12 hours 48mins. This model does not take stereo recordings, but by the addition of an external amplifier, will reproduce any $\frac{1}{2}$ -track or $\frac{1}{4}$ -track pre-recorded stereo tape. Both models A and B incorporate a new Multimusic tape deck.


A new Multicore accessory shown for the first time was the Bib tape recording kit. This incorporates the already established Bib recording tape splicer complete with a supply of extra cutters. Among the other Multicore products displayed was the Ersin Multicore 5-core solder in standard alloys and gauges.

REDICORD LTD. STAND NO. 123

Record players were the main feature of this stand. Among those displayed was the Nevin stereo record player, which is an ideal unit for a small flat. A Garrard magazine tape deck can be fitted as a combined unit. "The Calypso" battery transistor record player proved popular with teenagers. This is a lightweight portable with a zipp wrap-around case finished in bright red, black or white. A portable tape recorder, the "Reditape", using the latest Garrard magazine tape deck with a French-designed amplifier also proved popular.

TAPE RECORDERS (ELECTRONICS) LTD. STAND NO. 3

The Tape Recorder Centre, as this stand was known exhibited a comprehensive range of Sound tape recorders and accessories for every type of pocket. The popular "Sound Studio" and "Sound Prince" were shown with new features and four-track, de luxe versions of both models were available for maximum tape economy. The "Sound Master" is a new three-speed, four-track tape recorder which comprises a full high fidelity reproducing equipment with separate record and playback amplifiers. The stand was visited by many prominent personalities during the Show. A four-track version of the "Studio", the sound "Studio De Luxe" was also displayed on the stand.

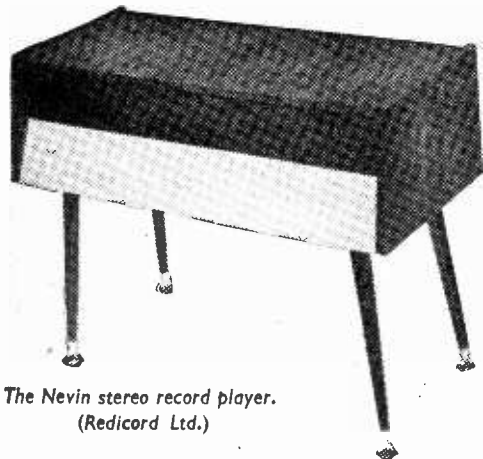

*The Nevin stereo record player.
(Redicord Ltd.)*



*A four-track version of the "Studio", the sound "Studio De Luxe".
(Tape Recorders [Electronics] Ltd.)*

THE TELEGRAPH CONDENSER CO. LTD. STAND NO. 42

The T.C.C. exhibit was a selection of new and established products, emphasis being on the progress made in the development of new condensers, printed circuits and ceramics over the past year. For equipments meeting with extremes of temperature conditions an extensive range of tantalum-anode electrolytics were shown. The Ceramic Division of the Company was represented by a display of formers, tubes, plates and rods, stand-off and lead-through insulators and terminals, hermetic seals, and an extensive range of fuses. Several types of printed circuits were on show on the stand and miniature paper tubulars suitable for hearing aids and transistor assemblies were in both metal clad and wax protected constructions.

WHITELEY ELECTRICAL RADIO CO. LTD. STANDS NOS. 69 & 304

A range of Stentorian high fidelity products was displayed and demonstrated on the Whiteley stands. This range of loudspeaker was available with a variety of cone constructions. The Radio Sonde as used by the British and many foreign meteorological offices was featured together with a display of equipment manufactured for the Post Office and Services Departments. In the Audio Hall, stand 18, high quality sound reproducing equipment could be heard.

Exhibitors at the Radio Show

	Stand No.		Stand No.
A.E.I. Sound Equipment Ltd., Crown House, Aldwych, W.C.2	308	Gainsborough Tape Recorders, 189 Northcote Road, Battersea, S.W.11	301
Admiralty, Dept. of C.N.I., West Block (Ground), S.W.1	407	Garrard Engineering and Manufacturing Co. Ltd., Newcastle Street, Swindon, Wilts.	56
Aerialite Ltd., Castle Works, Stalybridge, Cheshire	13	General Electric Co. Ltd., Magnet House, Kingsway, W.C.2	32 and 322
Air Ministry, Lacon House, Theobalds Road, W.C.1	406	General Post Office, Headquarters Buildings, St. Martins-le-Grand, E.C.1	403
Alan-Markovits Ltd., Emblem House, Sussex Road, Hove	115	Goodmans Industries Ltd., Axiom Works, Wembley, Middlesex	220 and 316
Alba (Radio and Television) Ltd., 52/70 Tabernacle Street, E.C.2	16 and 306	Gramophone Co. Ltd., Hayes, Middlesex	42 and 323
Amplion Ltd., 175/185 Cricklewood Lane, N.W.2	54	Greater London Fund for the Blind, 2 Wyndham Place, W.1	414
Antiference Ltd., Bicستر Road, Aylesbury, Bucks.	17	Hacker Radio Ltd., Norreys Drive, Cox Green, Maidenhead, Berks.	113
Argosy Radiovision Ltd., Eastern Avenue West, Romford, Essex	61	Hobday Ltd., Christopher, 98/102 Broadway, Leigh-on-Sea, Essex	221
Associated British Tape Recording Clubs Ltd., 7/8 Norfolk Street, Strand, W.C.2	412	Home Maintenance Ltd., Blyth Road, Hayes, Middlesex	118
Associated Electrical Industries Ltd., 155 Charing Cross Road, W.C.2	21	Hunt (Capacitors) Ltd., A. H., Bendon Valley, Garratt Lane, S.W.18	49
Associated Television Ltd., A.T.V. House, 17 Great Cumberland Place, W.1	74	Iliffe and Sons Ltd. (Wireless World/Electronic Technology), Dorset House, Stamford Street, S.E.1	204
Barclays Bank Ltd., 54 Lombard Street, E.C.3	203	Independent Television Authority, 14 Princes Gate, S.W.7	74
Belling and Lee Ltd., Great Cambridge Road, Enfield, Middx.	63	J-Beam Aerials Ltd., Westonia, Weston Favell, Northampton	5
Bernards (Publishers) Ltd., The Grampians, Western Gate, W.6	125	Keith Prowse and Co. Ltd., 90 New Bond Street, W.1	1
Bowmaker Ltd., Bowmaker House, Lansdowne, Bourne-mouth, Hants.	216	Kerry's (Great Britain) Ltd., Warton Road, Stratford, E.15	19
Brenell Engineering Co. Ltd., 1a Doughty Street, W.C.1	311	Kolster-Brandes Ltd., Footscray, Sidcup, Kent	22
British Broadcasting Corporation, Broadcasting House, W.1	408, 409 and 410	Labgear Ltd., Willow Place, Cambridge	25
British Radio Corporation Ltd. ("His Master's Voice"), 105 Judd Street, W.C.1	33	Le Great and Co., 58 Fairfield Street, S.W.18	122
British Radio Corporation Ltd. (Marconiphone), 105 Judd Street, W.C.1	47	Lee Products (Great Britain) Ltd., Elpico House, Longford Street, N.W.1	55
Brimar Electronics Ltd., Footscray, Sidcup, Kent	104	Linguaphone Institute Ltd., Linguaphone House, 207/9 Regent Street, W.1	109
Bulgin and Co. Ltd., A.F., By-Pass Road, Barking, Essex	66	Lloyds Bank Ltd., 71 Lombard Street, E.C.3	4
Bush Radio Ltd., Power Road, Chiswick, W.4	51 and 60	Lustraphone Ltd., St. George's Works, Regents Park Road, N.W.1	309
Casian Ltd., 37 Grafton House, Golden Square, W.1	219	McMichael Radio Ltd., Langley Park, Slough, Bucks.	53
Cathode Ray Tubes Ltd., 758/760 Bristol Road, Selly Oak, Birmingham	30	Margolin Ltd., J. and A., 112/116 Old Street, E.C.1	44
Charterhouse Credit Co. Ltd., Surrey House, Scarbrook Road, Croydon, Surrey	8	Markovits, I., Premier House, 8 Golden Square, W.1	120
Chorlton and Co. Ltd., L., 5 Church Street, Prescott, Lancs.	217	Martins Bank Ltd., 68 Lombard Street, E.C.3	105
Cole Ltd., E. K., Ekco Works, Southend-on-Sea, Essex	58	Mercantile Credit Co. Ltd., Argyll House, 246/250 Regent Street, W.1	208
Collaro Ltd., Ripple Works, By-Pass Road, Barking, Essex	38	Merryfield Ltd., Andrew, 29/31 Wrights Lane, Kensington, W.8	314
Co-operative Wholesale Society Ltd., 1 Balloon Street, Manchester 4	7	Macropolitan Police, New Scotland Yard, S.W.1	402
Cosmocord Ltd., Acos Works, Eleanor Cross Road, Waltham Cross, Herts.	310	Midland Bank Ltd., Poultry, E.C.2	12
Cossor Radio and Television Ltd., 71 Endell Street, W.C.2	57	Mullard Ltd., Mullard House, Torrington Place, W.C.1	40
Daystrom Ltd., Bristol Road, Gloucester	112	Multicore Solders Ltd., Multicore Works, Hemel Hempstead, Herts.	71
Decca Record Co Ltd. (Radio and Television), Ingate Place, Queenstown Road, Battersea, S.W.8	35 and 303	Murphy Radio Ltd., Welwyn Garden City, Herts.	23
Design Furniture Ltd., Carnwath Road, Fulham, S.W.6	103	National Provincial Bank Ltd., 15 Bishopsgate, E.C.2	101
Domain Products Ltd., Domain Works, Barnby Street, N.W.1	214	Newnes Ltd., Geo. (Practical Wireless/Television), Tower House, Southampton Street, W.C.2	117
Dubilier Condenser Co. (1925) Ltd., Ducon Works, Victoria Road, N. Acton, W.3	62	Nottingham Electronic Valve Co. Ltd., Kenrick Street, Netherfield, Nottingham	218
Dynatron Radio Ltd., St. Peter's Road, Furze Platt, Maidenhead, Berks.	52 and 313	Odham Press Ltd. (Electrical and Radio Trading), 96 Long Acre, W.C.2	111
E.M.I. Records Ltd., E.M.I. House, Manchester Square, W.1	65	Perdio Ltd., Perdio House, Bonhill Street, E.C.2	41
E.M.I. Sales and Service Ltd., Hayes, Middx.	24	Perth Radios Ltd., Marten House, 39/47 East Road, N.1	205
Econasign Co. Ltd., 19/21 Palace Street, S.W.1	121	Peto Scott Electrical Instruments Ltd., Addlestone Road, Weybridge, Surrey	27
Electric Audio Reproducers Ltd., The Square, Isleworth, Middx.	319	Philco (Overseas) Ltd., 30/32 Grays Inn Road, W.C.1	45
Elizabethan (Tape Recorders) Ltd., Bridge Close, Old Church Road, Romford, Essex	26	Philips Electrical Ltd., Century House, Shaftesbury Avenue, W.C.2	10 and 320
Emerson Electronics Ltd., Brent Crescent, North Circular Road, N.W.10	50	Pilot Radio and Television Ltd., Television House, Eastcote, Ruislip, Middlesex	11
Ever Ready Co. (Great Britain) Ltd., Hercules Place, Holloway, N.7	307	Petrie Ltd., 21 Noel Street, W.1	108
Expert Gramophones Ltd., 78 Balham High Road, S.W.12	34	Plessey Co. Ltd., Vicarage Lane, Ilford, Essex	73
Ferguson Radio Corporation Ltd., Thorn House, Upper St. Martin's Lane, W.C.2	39 and 324	Practical Wireless	117
Ferranti Radio and Television Ltd., 41/47 Old Street, E.C.1	48	Practical Television	117
Fidelity Radio Ltd., 11 Blechynden Street, W.11	20	Print and Press Services Ltd. (Tape Recording and Hi-Fi Mag.), 7 Tudor Street, E.C.4	321
Field and Co. Ltd., N. and S. B., (Record Housing), Brook Road, Wood Green, N.22	116		
Fountain Press (prop. British Periodicals Ltd.), 46/47 Chancery Lane, W.C.2	124		

	Stand No.		Stand No.
Radio and Allied Industries Ltd. (Sobell), Langley Park, Slough, Bucks.	64	Tape Recorders (Electronics) Ltd., 784/788 High Road, Tottenham, N.17.	3
Radio Gramophone Dev. Co. Ltd., Eastern Avenue West, Mawneys, Romford, Essex.	29	Telegraph Condenser Co. Ltd., Wales Farm Road, North Acton, W.3.	42
Radio Society of Great Britain, New Ruskin House, Little Russell Street, W.C.1.	411	Teleng Ltd., Teleng Works, Church Road, Harold Wood, Essex.	107
Radio and Television Retailers' Association (R.T.R.A.) Ltd., 15/17 Godge Street, W.1.	201	Telerection Ltd., Antenna Works, Weymouth, Dorset.	28
Regentone Radio and Television Ltd., Eastern Avenue West, Mawneys, Romford, Essex.	59	Telesurance Ltd., 14 Windmill Street, W.1.	9
Redicord Ltd., 46/47 Frith Street, W.1.	123	Territorial Army (65th Signal Regiment), 79/85 Worship Street, E.C.2.	413
REPS (Tape Recorders) Ltd., 118 Park Road North, South Acton, W.3.	305	Trader Publishing Co. Ltd. (Wireless and Electrical Trader), Dorset House, Stamford Street, S.E.1.	110
Roberts' Radio Co. Ltd., Creek Road, East Molesey, Surrey	70	Tricity Finance Corporation Ltd., Great Cambridge Road, Enfield, Middlesex.	36
Rola Celestion Ltd., Ferry Works, Summer Road, Thames Ditton, Surrey.	213 and 312	Trix Electrical Co. Ltd., 1/5 Maple Place, Tottenham Court Road, W.1.	37
Rose Projects Incorporated, Station Approach, Bourne End, Bucks.	119	Truvox Ltd., Neasden Lane, N.W.10.	317
Seicol Products Ltd. (Gala Records), 114/116 Charing Cross Road, W.C.2.	202	Ultra Radio and Television Ltd., Television House, Eastcote, Ruislip, Middlesex.	15
Slingsby Ltd., H. C., 89/97 Kingsway, W.C.2.	31	Valradio Ltd., Browells Lane, Feltham, Middlesex.	114
Sloss, Andrew, Ben Nevis Works, Belmont Site, Stranraer, Scotland.	102	Vulcan Finance Facilities Ltd., Lombard House, Great Charles Street, Birmingham 3.	207
Southgate Tubular Products Ltd., 148 Chase Side, Southgate, N.14.	210	Walter Instruments Ltd., Garth Road, Morden, Surrey.	72
Standard Telephones and Cables Ltd., Connaught House, 63 Aldwych, W.C.2.	14	Westminster Bank Ltd., Post Office Court, 10 Lombard Street, E.C.3.	18
Star Newspaper Co. Ltd., 12/22 Bouverie Street, E.C.4.	404	Wireless for the Bedridden Society, 55a Welbeck Street, W.1.	67
Stella Radio and Television Ltd., Astra House, 121/123 Shaftesbury Avenue, W.C.2.	6	Whiteley Electrical Radio Co. Ltd., Radio Works, Victoria Street, Mansfield, Notts.	69 and 304
Southern Television Ltd., The Southern Television Centre, Northam, Southampton.	74	Walsey Electronics Ltd., Cray Avenue, St. Mary Cray, Orpington, Kent.	43
Symphony Amplifiers Ltd., 16 King's College Road, N.W.3.	302		

Short-wave Listeners' Log — 2

PRACTICALLY every short wave or all-wave receiver will cover some of the Amateur Bands, and there is a good deal of interesting activity on these frequencies. As a guide to tuning, the approximate wavelengths and frequencies of the most popular Amateur Bands are as follows:

166 — 150m	1.8 — 2.0Mc/s
86 — 80m	3.5 — 3.8Mc/s
42.8 — 41m	7.0 — 7.3Mc/s
21.4 — 21m	14.0 — 14.35Mc/s
14.3 — 14m	21.0 — 21.45Mc/s
10.7 — 10m	28.0 — 30.0Mc/s

These bands are usually referred to in broad terms, either by frequency or wavelength. For example, as 80, 40, or 20m bands, and so on. The 160m band is also called "Top Band". With this in mind, the bands can usually be easily identified, even on simple home-constructed receivers, especially as they are well spaced. References to the band or frequency used are often made by the amateurs who are working.

For most interesting listening, the characteristics of the various bands should be kept in mind. The 160m band is usually best for fairly short range, or ground wave communication. Amateurs are also limited to 10W, here, but quite long distances are occasionally worked, despite this. The 80m band is extremely popular for medium range work, and is often very busy. On 40, some locals can often be heard, and there is the possibility of distant (Dx) reception. For general Dx work, the 20m band is popular. Many USA and other overseas amateurs run considerable power on this band, and a fair number of Dx catches can often be made. The 15m band (actually 21 —

21.45Mc/s) and 10m band are virtually dead at some times of day, but offer extreme Dx reception when conditions are favourable.

Activity is usually strongest at week ends. Early on a Sunday morning, until afternoon, the 80m band is usually very busy, with 160 and 40 also in use. Later in the day, 20 and 15 are likely to become more active. The 40m band suffers bad interference from commercial stations, especially towards late afternoon and evening. Because of this, amateurs may be heard using the band early, when it is clear.

For an easy attempt at Dx reception, attention can be given to the 20m band. Due to the time difference of far countries, real Dx will occasionally be heard in these bands when there is little local activity.

Long distance reception is not usual on 160 or 80, but these bands generally offer the best chance of hearing Amateurs within a range of a few hundred miles. Some use 100 or 150W on bands other than 160, and are able to provide very strong signals. Any attempt to receive unusual or distant stations is most likely to be successful if listening is confined to weak signals. With a home-built or uncalibrated receiver, it is wise to note down the limits on the various bands, when they are tuned in. The bands can then be found easily again, and long range Dx can be listened for at times when there is little crowding or interference from local transmitters.

The English language is extensively used by Amateurs all over the world, and as a result quite an extensive log of stations can soon be compiled. Conditions vary according to time of day and season, but a quick check over the bands will soon show what to expect.



PORTABLE TRANSISTOR Record Player BARGAIN OFFER

- ★ 6v. operation (2E/R Type 800 Batts.)
- ★ 1 watt Push Pull Output
- ★ 4 Latest G.E.C. Transistors
- ★ Garrard Fidelity Gram. Unit



Size: 11 x 8 1/2 x 6 in.
Colour: 2 Tone Red/White with Polka Dot relief. Alternative Blue/Eawn with Polka Dot relief.

CABINET incl. Motor Board and 7 x 4 in. Speaker, £11.19.6. Carr. 2/6.

GARRARD BA1 Gram. Unit, 45 r.p.m., £2.19.6. Carr. 2/6.

RECORD PLAYER BARGAINS

All brand new latest 4-speed Models—fully guaranteed.


SINGLE PLAYERS—B.S.R. (TU9) with FUL-FI, P.U. 90/-; Collaro Junior with latest GP 67-12 Xtal, 90/-; Garrard TA Mk.2 with GCS Head, £7.19.6; Garrard 4HF Transcription Unit, £18, carr. 3/6.

AUTO CHANGERS—B.S.R. (UA8), £6.19.6; UA8 Stereo, £7.19.6; UA14, £7.19.6; Collaro Conquest, £7.19.6; Garrard RC121/4D Mk.2, 91 gns., carr. 4/6.

GARRARD RC210 4-speed Autochanger Model with latest features and GCS Plug-in Head only 10 gns., carr. 4/6. This model just released.

E.M.L.—4-speed Single Player with Auto Stop-Start Dual Turnover Cartridge for Stereo and Monaural L.P. and 78—Bargain Buy at £6.19.6, carr. 3/6.

RECORD PLAYER CABINETS

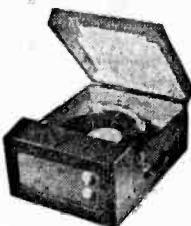

Contemporary styled, rexine covered cabinet in two-tone fawn and brown, or mottled red with white polka dot. Size 18 1/2 x 13 1/2 in. 9 in., fitted with all accessories, including baffle board and anodised metal feet. Space available for all modern amplifiers and auto changers, as above, etc. Uncut record player mounting board 14 x 13 in. supplied. Cabinet Price £3.3.0. Carr. and Ins. 3/6.

2 VALVE, 2 WATT AMPLIFIER

Two stage ECL82 with vol. and neg. feedback. Tone controls A.C. 200/250 v. with double-wound Mains trans. Complete with knobs, etc., ready wired to fit above cabinet, £2.17.6. P. & P. 1/-; 8 in. Speaker and matching trans. 22/-, P. & P. 1/6.

RECORDING TAPE BARGAINS

EMI 1st grade. Brand new sealed boxes.
Standard Long Play
3in., 175ft. .. 7/- .. 260ft. .. 9/-
5in., 600ft. .. 19/- .. 850ft. .. 25/-
5 1/2in., 850ft. .. 25/- .. 1,200ft. .. 31/6
7in., 1,200ft. .. 31/6 .. 1,800ft. .. 45/-
SPECIAL PURCHASE: 8mm tape, new, boxed: 3in. 3/-; 5in. 3/6; 5 1/2in. 4/-; 7in. 4/6.

SPECIAL PURCHASE: Famous manufacturers 1st grade tape in sealed white boxes.
Standard Long Play
5in., 800ft. .. 15/- .. 850ft. .. 19/6
5 1/2in., 850ft. .. 16/6 .. 1,200ft. .. 22/6
7in., 1,200ft. .. 21/- .. 1,800ft. .. 32/6
Plastic Tape Reels, special offer. Manufacturers' surplus. 3in. 2/8; 5in. 3/-; 5 1/2in. 3/3; 7in. 3/6.

CRT. HTR. ISOLATION TRANSFORMERS

New improved types, low capacity, small size and tag terminated, A.C. 200/250 v. Secondaries 270, +25%, +50%, 1000Ω, for 2 v., 4 v., 6.3 v., 12.6 v. and 25 v. tubes. EA Type 12/8 each. P. & P. 1/6.

Complete RECORD PLAYER KIT

3 UNITS Bargain Price
£7.19.6 Carr. 4/-

Send*for full details now

REDUCED PRICES	VALVES	ALL GUARANTEED
1T4 6/-	ECH42 10/6	EZ80 7/6
1F5, 185 7/6	ECL80 10/6	E261 7/6
354, 3V4 7/6	ECL82 10/6	MU14 9/-
6Z4 10/6	EF80 8/-	PC94 9/6
DAF96 9/-	EF86 12/6	PCF80 9/6
DF96 9/-	EF91 5/-	PC143 12/6
DK06 9/-	EL41 9/6	P151 12/6
DL96 9/-	EL84 8/6	P182 9/6
EABC80 8/6	EY61 9/6	PL88 10/6
ECP80 9/6	EY86 10/-	U25 12/6

TRANSISTORS - BVA 1st GRADE

REDUCED PRICES		GEO	
Mazda	Mullard		
XA101 14/8	OC70 9/6	GET114 9/8	
XA102 16/6	OC71 12/6	GET115 12/8	
XA103 15/-	OC72 15/-		
XA104 18/-	OC44 22/6	Newmarket	
XB192 10/-	OC45 21/-	'Goldtop'	
XC101 10/8	OC16 49/6	V15/10P 15/-	

Germanium Diodes, OA70 2/8, GEX34 4/-, GD4 3/6


RE-GUNNED TV TUBES

New Reduced Prices
New Heater, Cathode and Gun Assembly fitted to all tubes. Reconditioned virtually as new. Now 12 months' guarantee on highest stands—as used by our own Service Dept.
12in. £5. 14in. £5.10.0. 17in. £6.
Mullard and Mazda types ex-stock Carr. and Ins. 10/-
10/- Part Exchange allowance on your old tube.

7 VALVE AM/FM RADIOGRAM CHASSIS

Valve Line-up: ECC85, ECH81, EF89, EABC80, EL84, EM81, EZ80.

Three Waveband and Switched Gram position. Med 200-500 m., Long 1,000-2,000 m., VHF/FM 88-95 Mc/s. Philips Continental Tuning insert with permeability tuning on FM and combined AM/FM IF transformers, 400 kc/s and 10.7 Mc/s. Dust core tuning all coils. Latest circuitry including AVC and Neg. Feedback. Three watt output. Sensitivity and reproduction are of a very high standard. Chassis size 13 1/2 x 6 1/2 in. Height 7 1/2 in. Edge Illuminated glass dial 1 1/2 x 3 1/2 in. Vertical pointer. Horizontal station names. Gold on brown background. A.C. 200/250 v. operation.

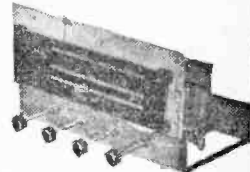

Aligned and tested ready for use. £13.10.0. Carr. & Ins. 5/-
Complete with 4 Knobs—walnut or ivory to choice. Indoor FM Aerial, 3/6 extra.
Three ohm P.M. speaker only required. Recommended quality speakers.
10in. Rola (Heavy Duty) 30/- 8in. Goodman special cons. 21/6. Post & Pkg. 1/6.
As previously announced fresh supplies are now being received, but we regret some slight delay may be experienced in fulfilling orders for this popular item.

ONLY A FEW ITEMS ARE LISTED FROM OUR COMPREHENSIVE STOCK
WRITE NOW FOR FULL BARGAIN LISTS, 3d.



RADIO COMPONENT SPECIALISTS

70 Brigstock Road, Thornton Heath, Surrey

Phone: THO 2188. Hours 9 a.m.—6 p.m. 1 p.m. Wed. Open all day Saturday. By Thornton Heath Station.

Terms: C.W.O. or C.O.D. post and packing up to 1 lb. 7d.; 1 lb. 1/1; 3lb. 1/6; 5lb. 2/-; 10lb. 2/9

THE LINEAR LI/10

A 10-WATT HIGH FIDELITY ULTRA LINEAR AMPLIFIER WITH INTEGRAL PRE-AMP

Full advantage has been taken of latest component miniaturisation developments to produce a 10-watt Hi-Fi push-pull amplifier incorporating tone control pre-amplifier stages within the measurements of $9 \times 7 \times 5$ ins. In addition two high impedance input sockets are provided for microphone and gram., etc. With selector switch and vol. control, five B.V.A. valves are employed ECC83, ECC83, EL84, EL84, EZ81. H.T. and L.T. power supply point is included for a radio tuner.

FREQUENCY RESPONSE

± 1 d.b., 30-20,000 c.p.s.

MAXIMUM POWER OUTPUT

In excess of 14 watts.

SENSITIVITY

L.P. 220 m.v. for 10 watts. 78 r.p.m. 220 m.v. for 10 watts. Radio/Microphone 40 m.v. for 10 watts.

TREBLE LIFT CONTROL

+ 10 d.b. to -22 d.b. at 12,000 c.p.s.

BASS CONTROL

+14 d.b. to -10 d.b. at 50 c.p.s.

HUM LEVEL

Referred to maximum output and including integral pre-amp.—70 d.b.

NEGATIVE FEEDBACK

21 d.b. in main loop.



HARMONIC DISTORTION Less than 0.1% measured at 8 watts at 1000 c.p.s. Weight 10 lbs. Power consumption 90 watts. For 200-230-250 v. 50 c.p.s. A.C. mains. Outputs for 3- and 15-ohm speakers. Chassis finish stoved Gold hammer.

HIGHEST QUALITY! Retail Price

MAXIMUM RELIABILITY! AT A PRICE YOU CAN AFFORD.

13 GNS.

Send S.A.E. for descriptive literature.

TRADE ENQUIRIES to

Also Available—THE L.45.A compact High Quality 4-5 watt amplifier. Size approx. 7.5-5.5 in. high. Sensitivity is 28 millivolts so that the input socket can be used for either microphone or gram., tape, radio tuner, etc. B.V.A. valves used are ECC83 EL84, EZ80. Controls are: Vol. Treble and Bass with mains switch. The Tone controls provide full compensation for long playing records. Output matching for 3 ohm loudspeaker. Retail price £5.19.6.

THE LT45 TAPE DECK AMPLIFIER.

A complete unit (power pack and oscillator incorporated) ready for connection to A.C. mains. 3 ohm loudspeaker and practically any make of deck. Negative feedback equalization adjustment by multi-position switch for 3 $\frac{1}{2}$, 7 $\frac{1}{2}$ and 15 in. per set. Retail price 12 gns.

DIATONIC 10-14 WATT. High Fidelity amplifier with integral pre-amplifier. Retail 12 gns.

CONCHORD 30 WATT. Hi-Fi amplifier with two separately controlled inputs. Retail 16 gns.

L/3 STEREO PHONIC AMPLIFIER. Sensitivity 150 m.v. Output 3 watts on each channel. Retail 7 gns.

L/5 STEREO AMPLIFIER. 5 + 5 watt. 12 gns.


LINEAR PRODUCTS LTD. ELECTRON WORKS, ARMLEY, LEEDS.

CONSTRUCTORS CORNER

Construction price includes valve and one coil covering 40-100 m.
 ● Can be converted to 2v. or 3v.
 ● Receives speech and music clearly from all over the world.
 Send 2/- for diagram and price list.

Explore the world on short-wave radio (10-100m)

FOR ONLY **35/-**

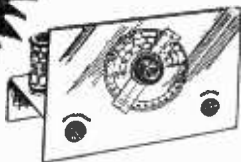

TRANSISTOR POCKET RADIO

Two-stage circuit using variloopstick coil.

- Ideal for the beginner.
- Can be built in 30 minutes.
- Works for months off 7d battery.
- Fits into palm of your hand.



The ideal low-cost transistor pocket radio for the beginner.
 Send 2/- for data and list of components.

ONLY **30/-**

CRYSTAL RECEIVER

Covers M/W Band

All components including case for **12/6**

idea. for the beginner

Post and packing: Under 10/- add 9d.; under 40/- add 1/6; over POST FREE

ENSURE SUCCESS WITH R.C.S.

SENSATIONAL RESULTS WITH 2 TRANSISTORS

- ★ No aerial or earth.
- ★ Dial tuning with mini .0005.
- ★ Drilled chassis, colour coded, components, simple layout for beginners.
- ★ Special small case fits shirt pocket.
- ★ Soldering iron and pliers are only tools needed.



Finest results ever obtained with 2 transistors and diode layout. The ideal radio to carry with you everywhere. PARTS PRICE LIST & EASY LAYOUT PLANS, 2/-. Total building cost, including transistors, wire, etc. **62/6**

BUILD THIS AMAZING RADIO

- ★ Sturdy metal case
- ★ No holes to drill.
- ★ Detachable rod aerial
- ★ All batteries self contained
- ★ Can be built in 1 hour
- ★ Covers medium waves
- ★ Loud clear tone.
- ★ Selective tuning.
- ★ All parts are sold separately.

This delightful set is designed to give you a completely personal portable radio. Bronze-finished case. Ideal for the beach the bedroom, the office—in fact anywhere.
 Send 2/- for wiring diagram and component price list.



FOR ONLY **35/-**

Trade Enquiries Welcomed

R.C.S. PRODUCTS (RADIO) LTD. 11 OLIVER RD., LONDON, E.17

Mail Order Only

Radio Construction for the Beginner

THE FIRST OF A NEW SERIES

By D. B. Kidd

THE use of so-called "breadboard" circuits by experienced constructors is too well known to need comment. However, no one seems to have gone to the trouble of explaining their uses to the beginner. This is presumably because he is expected to drift into the practice sooner or later after going through the mill of routine construction using solder, metal chassis, etc.

Mechanical Joints

In terms of valve radio, this attitude is perhaps understandable, since wood is an indifferent insulator at the high voltages used, but in terms of transistor (solid state) radio, the objections no longer hold and, provided certain precautions are taken, mechanical contacts at the voltages commonly used for transistor radio are almost as efficient as soldered connections. While efficient soldering ensures a first-class electrical joint, poor soldering will often hide a bad connection and so turn mere failure into insoluble mystery.

If the beginner can be guaranteed some success from the start, he may persevere long enough to learn the knack of good electrical soldering and so enter the ranks of enthusiastic constructors.

Aims of the Series

The present article has been written with this aim in view, and the others which are scheduled to follow it as a series will be along the same lines. It will be assumed that the beginner has a strictly limited supply of both tools and money, so the articles will also fulfil (to the best of the writer's ability) the following conditions.

(a) Each construction will be a logical advance on the one before it.

(b) No mathematics will be employed except where it cannot be avoided.

(c) Components, materials, etc., will be of the least possible number and cost.

(d) All components used for one circuit will be usable in the circuits which follow, unless it is found impossible to do so by the author.

(e) No soldered junctions will be used.

The illustration (Fig. 1) shows most of the materials required for Constructions Number One, which is a simple crystal set.

The Breadboard

The term "breadboard" means, of course, any wooden board on which improvised circuitry is arranged with the minimum of

soldered connections, but the one proposed will be, for a variety of reasons, not far off the size of a real breadboard.

The reader will therefore have to look around for the first requirement—a piece of wood, between $\frac{1}{4}$ in. and $\frac{1}{2}$ in. thick, from which a rectangle roughly 7 in. x 11 in. can be cut. Some latitude may be allowed here but the reader should regard 6 in. x 10 in. as a minimum if he intends to follow the series right through. There is no need to pay a great deal for the wood. However, it is wise to ensure that the wood chosen is sound, not split, warped, or badly knotted. It should be reasonably soft wood, exhibiting a straight grain.

Hardboard

The next requirement is a piece of ordinary 3/16 in. hardboard (or plywood of similar thickness) from which a rectangle roughly 7 in. x 5 in. can be cut. The size is not really very important, but it will be an advantage if the length of the hardboard equals the width of the wood, as in the above case.

All the angles should be checked to ensure that true rectangles are obtained, and also that the sides of the wood are at right-angles to the main faces. The hardboard is to be fastened to one side of the board to form a simple "panel" (see Fig. 2).

A medium glasspaper should now be applied to the edges of the hardboard to remove saw-burrs,



Fig. 1.—Most of the materials which will be required for constructing the crystal set to be described next month are seen here.

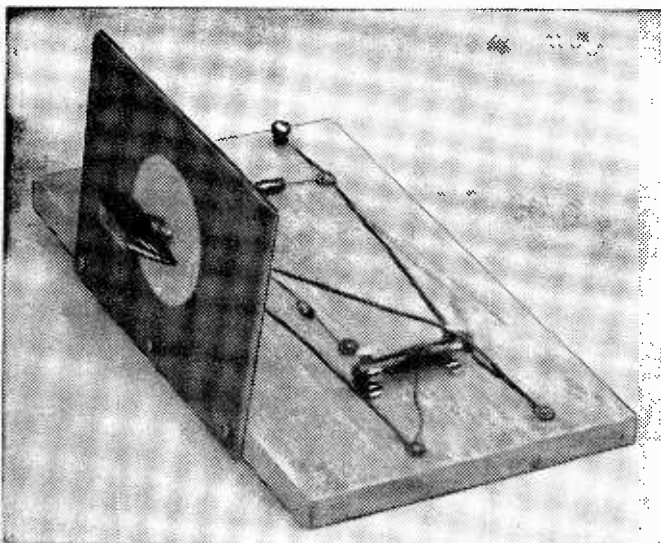


Fig. 2.—The crystal set constructed on the "breadboard."

and the same more vigorously, to all faces of the wood to obtain a thoroughly clean effect. Lastly, the better of the two main surfaces of the wood is selected and given a final treatment with fine glass-paper until a flat, smooth finish is obtained. This surface must be kept uppermost when fitting the hardboard panel.

The panel is fixed by means of two or three brass woodscrews and as these are to provide most of the electrical contacts as well, the reader will require a few dozen of them, together with the same number of small brass washers. It is important that brass screws and washers should be used; steel ones are most unlikely to prove satisfactory.

For the first circuit to be tried, the panel requires to be fitted centrally on one of the long sides of the completed breadboard (see Fig. 2). The screws will need to be "started" in the hardboard since it has a tough surface. Anything with a sharp steel point will do for this job. Two, or at the most, three, screws are sufficient to fix the panel, a brass washer being slipped on to each one before tightening up to prevent damage by the screw-head to the hardboard.

The reader is now ready to start on the first project—a simple crystal receiver, without, it is hoped, having to spend too much money.

Materials

- 1 A few yards of standard gauge p.v.c. covered connecting wire, solid rather than stranded.
- 2 Two spring tool-clips, with the two small wood-screws provided ($\frac{3}{4}$ in. in height).
- 3 One fixed capacitor of $0.01\mu\text{F}$.
- 4 One variable condenser of $0.0005\mu\text{F}$ (solid dielectric type rather than air-spaced).
- 5 One germanium diode.

6 A piece of ferrite rod, at least $1\frac{1}{2}$ in. long after any broken edges have been ground smooth again.

7 Two ounces of enamelled coil-wire, about 34s.w.g.

8 A pair of high-impedance headphones, fitted with two wander plugs.

9 Two small hexagonal sockets for the wander plugs, one red and one black (these may be obtained from some large stores).

10 A few square inches of the very fine glass-paper, called "flour" grade by the iron-mongers.

11 One knob, preferably of the pointer type, to fit a $\frac{1}{4}$ in. spindle.

With the above materials to hand, the reader is in a position to commence the first construction.

(To be continued)

ANNIVERSARY LECTURE

THE first of the Ultra Anniversary Lectures is to be given in the Recital Room of the Royal Festival Hall on September 14th. The speaker is Professor Arthur Porter, M.Sc., Ph.D., who is Dean of Engineering at the University of Saskatchewan.

Professor Porter's subject on September 14th will be "The Evolution of Instrumentation" and he will interpret the term "instrumentation" in a comprehensive way, as the measurement, manipulation and control of physical variables, with particular emphasis on control system technology.

A brief history of instrumentation will show how the developments of automatic control systems on the one hand, and analogue and digital computers on the other, have converged until the present, when many complex processes involve completely integrated controllers involving human operators, computers, automatic regulators and servomechanisms.

Some consideration will be given to the methodology of information theory and its application to control system technology. Since the problem of how to utilize information most effectively has profound implications and the real need for information is to predict the future, the applications of this concept to the control of processes will be considered. The method of prediction through the application of physical (or mathematical) models will be discussed with special reference to automatic controllers and in this context the basic significance of feedback will be illustrated.

A limited number of tickets for this lecture is available from the Public Relations Officer of Ultra Electric (Holdings) Ltd., at Western Avenue, Acton, W.3., and anyone interested in taking this opportunity of hearing Professor Porter should make written application to the above address.

Comprehensive Guitar Amplifier

A COMPLETE UNIT WITH TREMOLO, ETC.

By B. L. Phillips

THE unit to be described has been expressly designed for use with electric guitars, electric string bass or similar musical instruments. It is essentially a high gain, high power amplifier with its own power supply, and has an added refinement only normally found in expensive commercial amplifiers of this type; namely an electronic tremolo or vibrato unit. The circuit is in two sections, one being the power pack and power output stages, the second is the vibrato unit and pre-amplifier stages. These two items are on separate chassis, and are interconnected by a plug and socket arrangement. The pre-amplifier chassis carries all the volume and vibrato controls, input jacks and switches and is really the "control" panel. This is mounted somewhere on the cabinet top for easy access, whilst the power chassis can be mounted conveniently on the cabinet floor. The choice of cabinet is left to the constructor, but some details of cabinet mountings are given in the text as a guide.

Common Housing

As is normal with all amplifiers used with musical instruments, the loudspeaker is housed in the same cabinet as the amplifiers. The maximum power output is in the region of 15W peak, so a good 10in. or 12in. speaker is essential. Two 8in. speakers of a similar type can be used together, or even one 8in. singly, but a small speaker will not do true justice to the complete equipment and is easily overloaded. The unit may be used with a high impedance microphone, but it is emphasised here again that the response of the amplifier is really adjusted for guitar, etc., and is not intended for quality music or speech reproduction. The bandwidth required for amplifying the electric guitar is much narrower than that required for speech or music, and the true tone of the plucked guitar string is achieved by using a relatively narrow band amplifier. Further information will be given later.

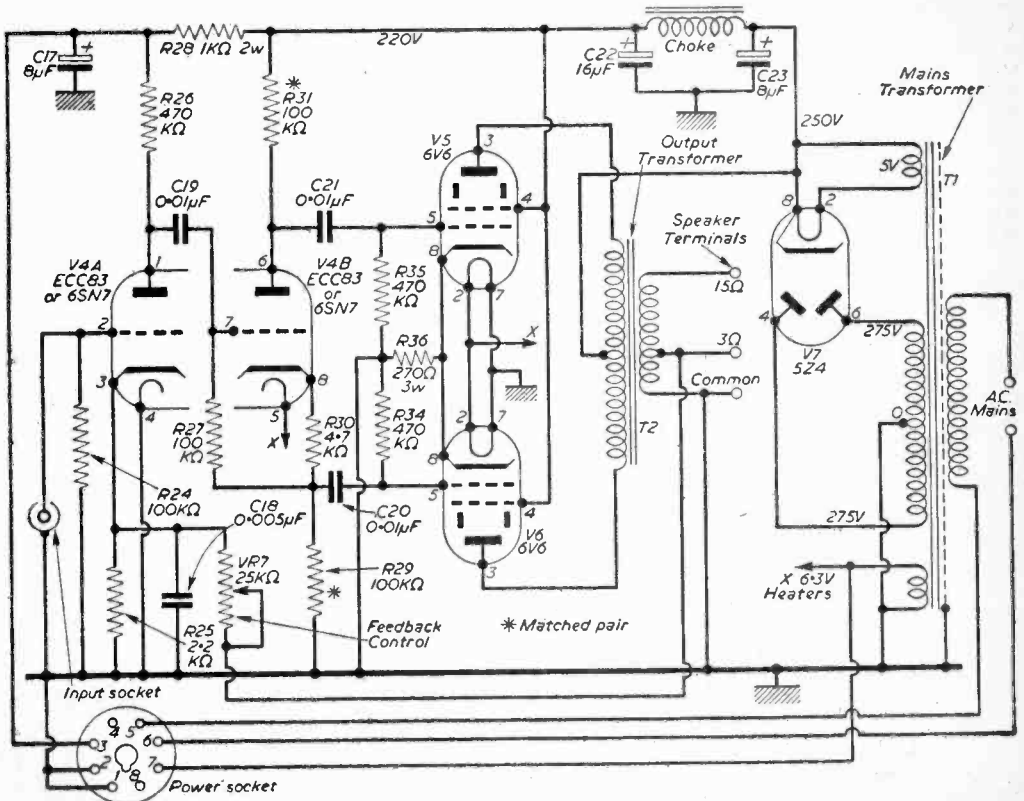


Fig. 1.—Circuit of the power unit and output stages.

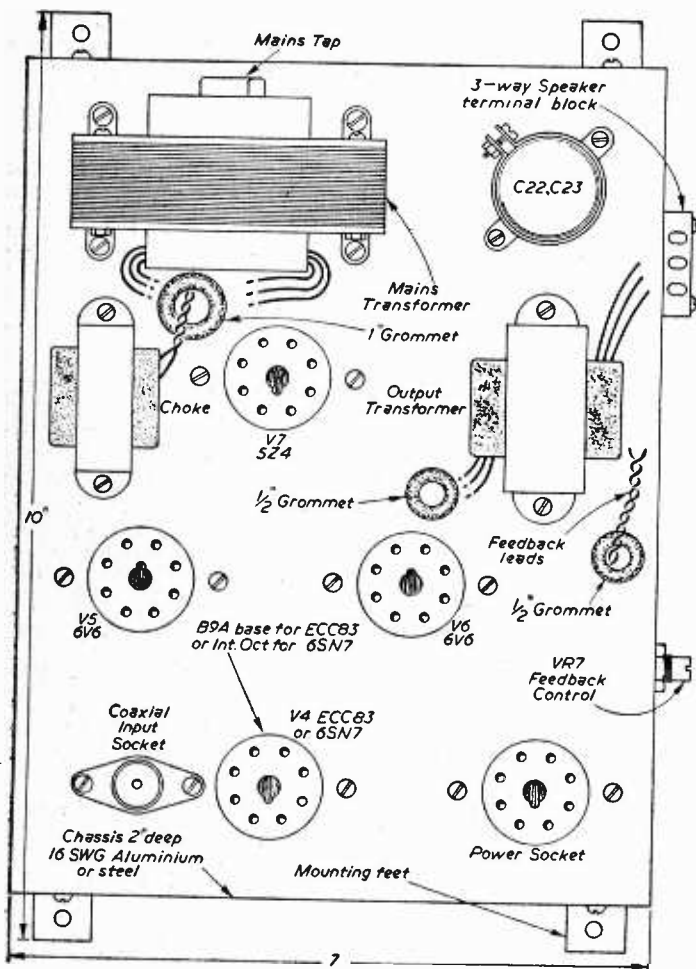


Fig. 2.—Plan view of the power chassis.

The Power Chassis

The circuit diagram is given in Fig. 1 and consists of the mains transformer, rectifier and smoothing circuits, the two output valves and transformer, and the driver and phase inverter stages. Wiring is in no way critical, except that the output anode leads must be as short as possible, and as far away from the input as possible. It will be noticed that either the B9A based ECC83 or octal based 6SN7 may be used in the driver/phase inverter position; results being the same for either type. All the octal bases require a 1½ in. hole, the B9A base being ¾ in. diameter. Figs. 2 and 3 gives the general layout of main components above and below the chassis. A tag-strip having two earthed mounting tags and a minimum of five connecting tags is used to support the small components associated with the input stages. Wiring here is in no way critical, and any convenient under-chassis layout may be used. The feedback control and speaker output terminations are mounted on one wall of the chassis, which is

2 in. deep. Four mounting feet are shown for fixing the chassis down to the cabinet base, but if a ready-made chassis with "lattice" fixing holes is available these may be used instead.

It is suggested that this chassis be made up first, then the following checks can be made for correct operation.


Tests

Insert the valves and short the mains switch leads on the power socket (pins 5 and 6). Leave the earth and feedback leads off the speaker output terminations, connect a speaker of 3Ω impedance to the 3Ω output tags. Switch on and allow to warm up for a few seconds. After quick checks for obvious faults, touching the input socket tags. Switch on and allow to warm up for a few seconds. After quick checks for obvious faults, touching the input socket tags. Switch on and allow to warm up for a few seconds. After quick checks for obvious faults, touching the input socket tags. Switch on and allow to warm up for a few seconds. After quick checks for obvious faults, touching the input socket tags.

Note: If the speaker is of 15Ω impedance, then the feedback leads will go across this 15Ω output. Further details of adjustment are given later. Finally, check the heater and high tension voltages if possible; they should be within 20 per cent of those on the diagram. One last word on this unit: the 0.005μF capacitor across the feedback line and chassis is essential and must not be omitted. It corrects for phase shift at ultrasonic frequencies and makes certain that the feedback is negative at all frequencies in the pass-band of the amplifier.

The Pre-amplifier & Vibrato Chassis

This unit consists of the audio pre-amplifiers to bring the guitar input up to a level suitable for feeding the main output stages, and the vibrato oscillator and mixer stages for the "tremolo" effect. The two amplifier stages are quite conventional and do not require any explaining. Some additional negative current feedback is employed on the final stage by not having the cathode resistor bypassed. The tone control circuit is a simple top-cut type and is placed between the two stages. The three volume controls are in parallel across the grid of the first amplifier, resistive stoppers of 100k each are employed to avoid undue interaction of one input on another. Wiring in all these stages should be as short as possible, and only one earth tag used for all earthy connections at each stage.

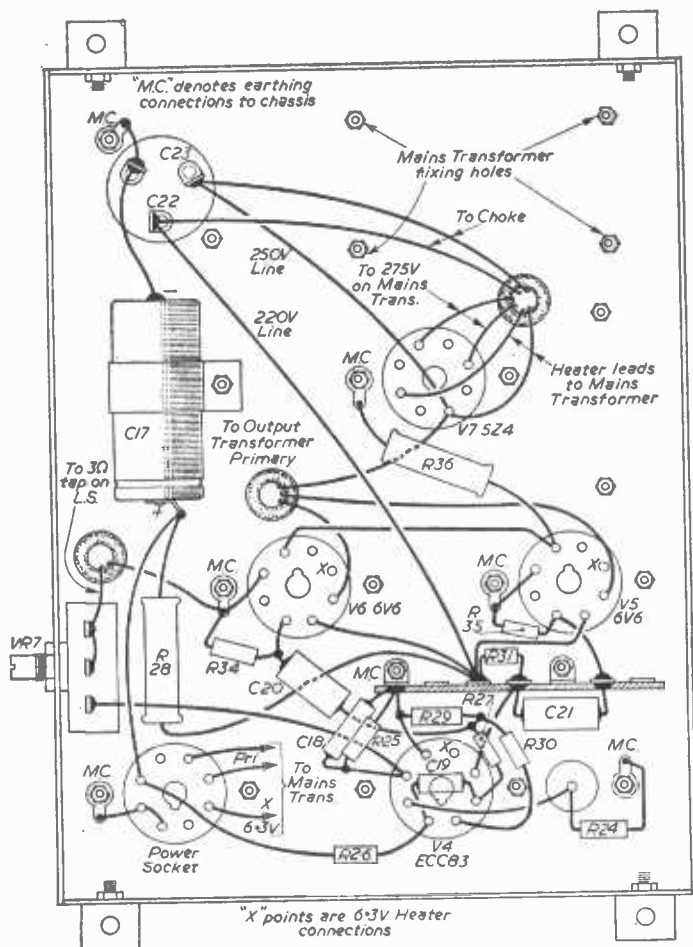

It is best to use the B9A based valves as specified in this unit, because of their compact size, but as stated earlier, if a constructor has a number of 6SN7's to hand, these may be used, but the chassis size will have to be increased. If 6SN7's are used a matching pentode for the vibrato unit is the 6K7 metal.


Tremolo Oscillator

This is a high gain triode, with the feedback taken from anode to grid via a phase changing network of capacitors and resistors. The oscillator develops a sine-wave output, the frequency of which depends upon the capacity/resistance ratio; thus one resistor in the feedback chain is made variable and governs the frequency of the output (which governs the "speed" of the tremolo effect). To avoid interaction between the oscillator and external connections, a buffer amplifying stage is placed between it and the mixer pentode. As the oscillator output is high, little gain is needed from this amplifier, hence heavy current feedback is used in the cathode circuit, and the output from the oscillator is taken from a low potential point across a 50k potentiometer.

(To be continued)


Fig. 3.—Underchassis wiring of the power unit.

Fig. 4 (below).—Circuit of the pre-amplifier and the vibrato unit.

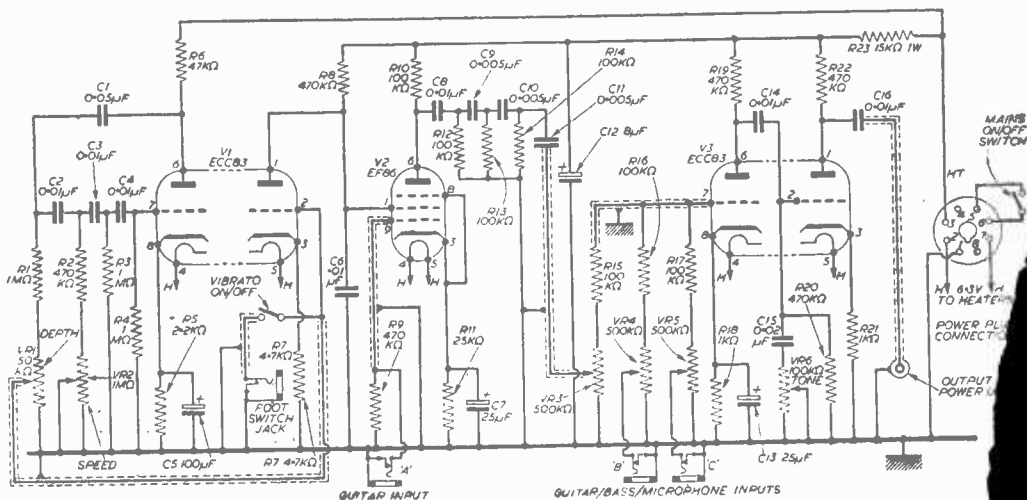

Mains D

A T.R.F. CIRCUIT
SELECTIVITY AND

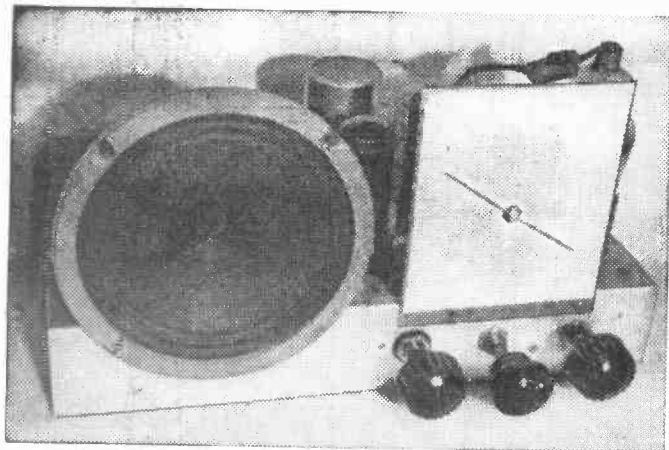

The completed receiver.

THIS receiver tunes long and medium waves and is particularly suitable for beginners, as construction and wiring are very straightforward, and no aligning of tuned circuits is required. The two valves are available at very low cost, and the complete receiver can be built at small expense, but nevertheless gives good results.

The Circuit

The circuit is shown in Fig. 1. A dust-cored dual-wave coil gives best results with the simplest form of wavechange switching. Reaction is con-

trolled by adjusting the detector screen grid voltage, this being adopted instead of a variable reaction condenser in order that the mains on/off switch can be operated as well with the single knob. The 8D2 and 12A6 valve heaters receive current from a 12.6V transformer. The actual combined heater consumption of these valves is only 0.35A, so a dial light may be added, if desired, without overloading the 0.5A transformer secondary. A 1A or 1A transformer is equally suitable. If 6.3V valves such as the 6J7 are to hand, these can be used instead of the 8D2, being equivalent except for the base and heater rating. Similarly, a 6V6 or other 6.3V valve can then be used in the output stage. A 6.3V transformer is then necessary, and the output valve cathode bias resistor should be modified to suit. 270Ω being used for the 6V6 type, but, if valves and heater transformer are to be purchased,

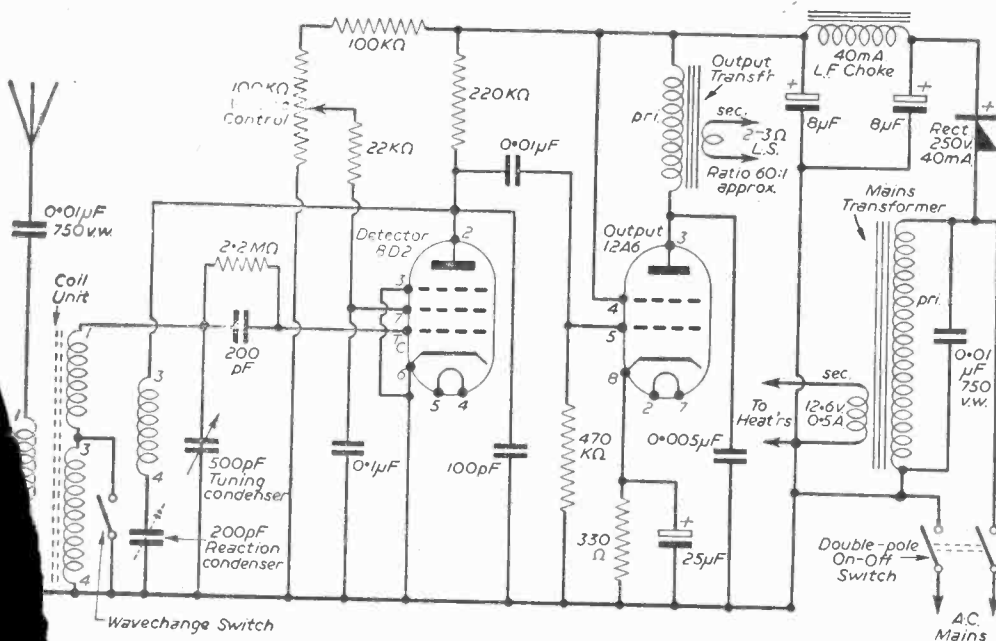


Fig. 1.—The circuit diagram of the receiver.

Dual-wave 2

WITH REACTION TO IMPROVE SENSITIVITY

By F. Gee


building cost will be reduced by using the 8D2 and 12A6.

The type of smoothing choke, and current rating of the choke and rectifier, are of little importance, provided they can handle at least 40mA. A 45mA or 60mA choke or rectifier would thus be suitable. If smoothing condensers of larger capacity are to hand, they can be used, and it is not necessary that both these components be of the same capacity. A combined condenser (such as 8 plus 16μF) is equally suitable.

The mains voltage isolating condenser in series with the aerial should be of high voltage rating, as must the condenser in parallel with the mains

COMPONENTS LIST

8D2 valve British 7-pin holder.
 12A6 valve. Octal holder.
 QR11D (Osmor) coil, or other dual-wave coil with aerial coupling and reaction.
 500pF air-spaced tuning condenser. Drum, cord, drive and spring.
 100k potentiometer with 2-pole switch.
 Fixed condensers: 100pF, 200pF, 0.005μF, 0.01μF 250VW, 25μF 25VW, two 8μF 350VW or similar, 0.1μF 250VW, two 0.01μF 750VW.
 12.6V ½A or similar mains transformer
 5in permanent magnet speaker with mains pentode output transformer.
 250V 40mA or similar rectifier.
 40mA or similar smoothing choke.
 Resistors: 330Ω 1W, 22k ½W 100k ¼W, 220k 1W, 470k or ½M ¼W, 2.2M ¼W.
 Single-pole wavechange switch.
 Three control knobs.
 200pF pre-set condenser

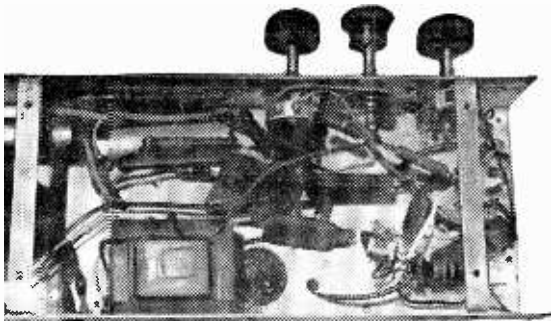

The underchassis wiring.

transformer primary. A leakage resistance of even several megohms in the 0.01μF coupling condenser between valves will allow a positive voltage to reach the 12A6 control grid, and upset proper working. For these reasons, three high quality mica 0.01μF condensers are recommended for these circuit positions.

Preparing the Chassis

A chassis about 10½in. x 4½in. with 2in. runners will be convenient. The parts can usually be arranged to fit a ready-drilled surplus chassis. If the chassis is undrilled, the valveholder holes can be made with a washer cutter, valveholder punch or cutter, or by drilling rings of small holes, and cleaning up with a half-round file.

A metal dial plate about 3½in. x 4½in. is bolted to the front runner of the chassis. A clearance hole for the tuning condenser spindle is drilled in

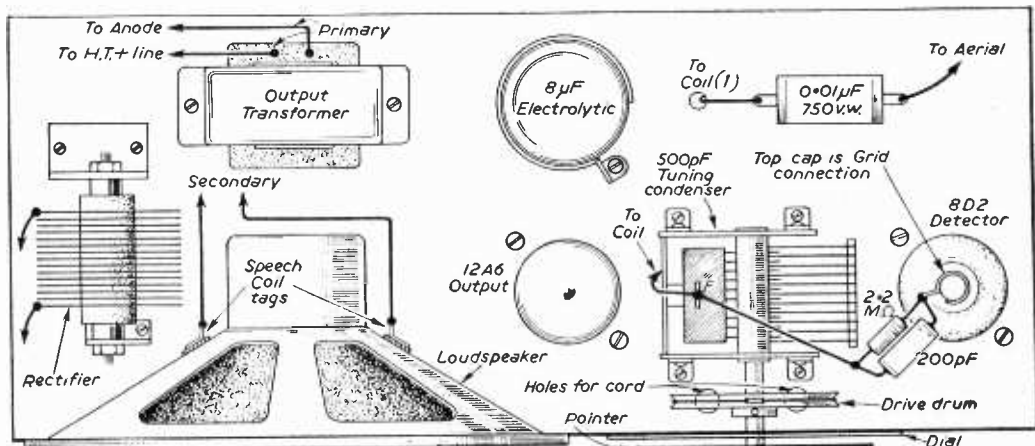


Fig. 2.—The above-chassis layout.

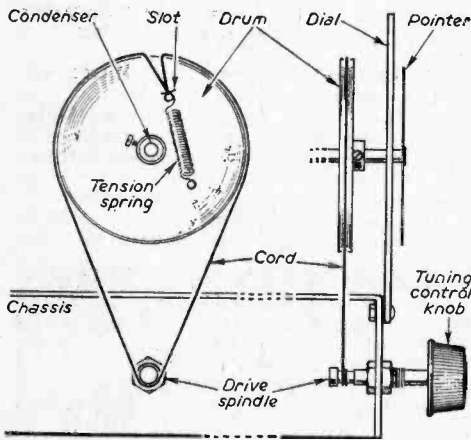


Fig. 3.—The tuning drive.

this plate at the correct height. The condenser is bolted down by means of small brackets, as shown in Fig. 2, the spindle projecting to take the pointer. The way in which the drive is arranged will be clear from Fig. 3. The bush holding the tuning control knob spindle is fixed to the front runner directly below the condenser spindle. Two clearance holes are then drilled for the cord, as shown in Figs. 2 and 3. The dial should be removed, and the drum is placed on the condenser spindle, its slot being at the top, with the condenser half closed. A length of nylon or other drive cord is then given a full turn round the spindle, taken up through the chassis, and round the drum. The ends pass through the slot, and are tied to the spring, which is under tension. The drive should work smoothly and easily, without the cord fouling the chassis, and the full 180deg movement of the condenser should be possible. If not, loosen

the drum set-screw to adjust it as required. The loudspeaker is also bolted to the front of the chassis, a small section being cut out to accommodate the frame here. If a little extra height is unimportant, the speaker can be attached by means of brackets, and an aperture in the chassis will then not be required. Parts above the chassis are located approximately as in Fig. 2. The rectifier fins are vertical (to assist air circulation); metal brackets being cut to hold it in this position. When wiring to the

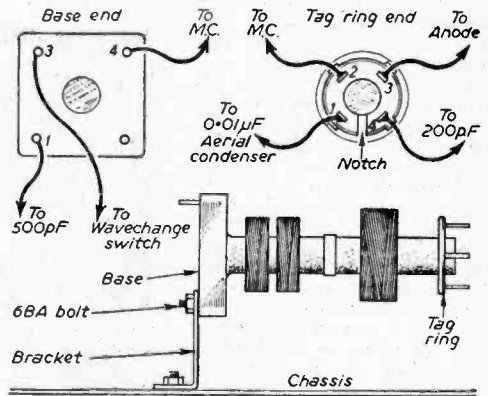


Fig. 5.—Tuning coil connections.

rectifier, assure that the positive end goes to the smoothing choke, and negative to the 0.01µF condenser and mains switch. Leads pass from the speaker speech coil tags to the secondary of the output transformer. If the transformer has wire ends, take these directly to the speaker tags. The secondary is of low resistance, and the actual ends of the winding may issue from the bobbin, ready for soldering to the

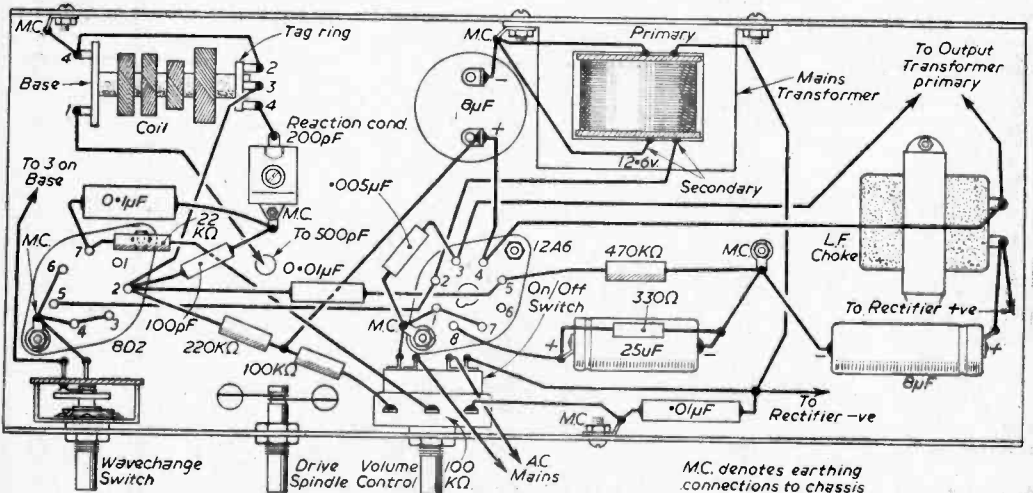


Fig. 4.—Underchassis wiring diagram.

speaker. The primary is of thin wire, and primary connections may be taken to tags on the transformer, or to thin, insulated flexible leads. The receiver cannot work if the transformer is wrongly connected.

Under the Chassis

Wiring and components below the chassis are shown in Fig. 4, points marked "M.C." being soldered to tags bolted in place. The mains leads should be of good quality twin flex. They run against the chassis, and out through a rubber grommet fitted in a hole in the back runner. It is best to use two-colour flex, and take the chassis side of the circuit to mains neutral, drawing current from a 3-pin plug. This will reduce chances of modulation hum, and also prevent the chassis being connected to the live main.


Connections should be reasonably short and direct, and it is wise to use insulated sleeving on all the leads. Note that the three large condensers have their negative tags taken to chassis.

The 200pF pre-set condenser has one tag bolted to the chassis, the condenser being raised so that it is not shorted. The second tag of this condenser is wired to point (4) at the tag ring end of the tuning coil.

The coil is best left off until other wiring is completed, and it is mounted clear of the chassis by means of a small bracket as shown in Fig. 5. At this end of the coil four pins project—(1) (3) (4) and (6). A lead from the fixed plates of the tuning condenser passes down through the chassis to pin 1, as shown

in Fig. 4. The pin marked 3 goes to the wavechange switch, and pin 4 to the chassis but pin 6 is not used.

At the other end of the coil is a tag ring, and this is wired as shown in Figs. 4 and 5. The connection from point 1 to the 0.01μF aerial condenser passes through the chassis. A short throw-out aerial consisting of about 6ft of thin insulated flex can be soldered to the second tag of this condenser, or a lead can be attached to a socket, so that an aerial can be applied. The actual aerial connection must be carefully insulated from the

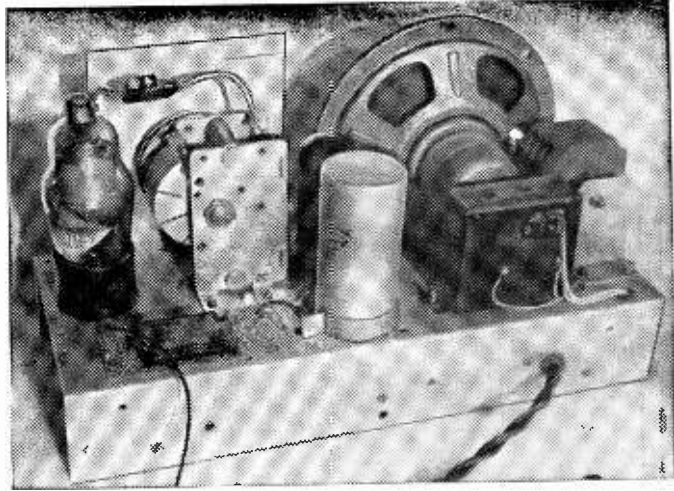

Rear view of the receiver.

chassis, and the condenser must not be omitted because it is intended to keep mains voltages out of the aerial.

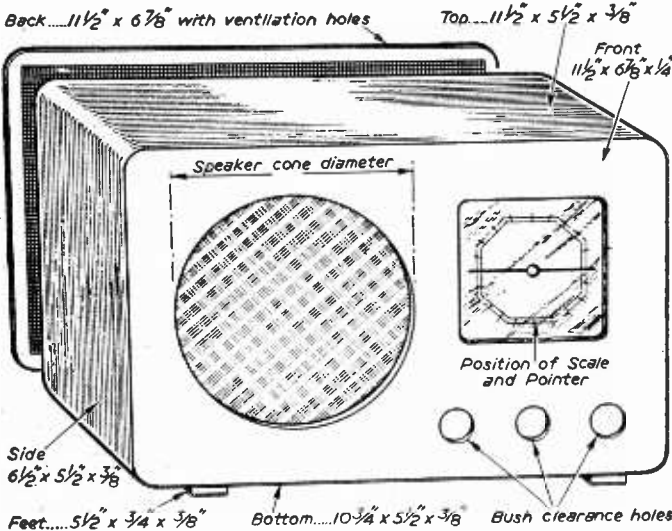


Fig. 6.—Making a cabinet.

Adjustments

The actual wavelengths covered depend, to some extent, on the position of the coil core, which can be adjusted from each end by means of a small screwdriver or insulated tool. If a metal blade is used, withdraw this after each adjustment. A coverage of about 200m to 550m on the M.W. band will be most useful, and the core position has most influence towards the high wavelength end of the band.

When the 100k potentiometer is rotated clockwise, sensitivity increases, being at maximum a little way in advance of full rotation. It is only necessary to adjust the 200pF pre-set condenser, using an insulated tool, until smooth reaction is obtained over each tuning range. If satisfactory reaction

(Continued on page 546)

An H.F. One Valver

SHORTWAVE, WORLD-WIDE,
RECEPTION

By I. Macdonald

RECENTLY I have been experimenting with one and two valve circuits for H.F. work. The main intention was to build a reliable low powered battery portable for the 15m band. After trying many circuits, already designed for the purpose, it was decided to try one of home design. The circuit finally decided upon was that which is now to be described.

Plans for an extra stage were developed. However, when the results of the 3D6 were heard, it was thought that this second stage would be undesir-

able. This assumption was proved to be correct, as the performance of the first stage is more than sufficient for the purpose. Stations from all parts of the globe have been detected on it. As an example a Russian broadcast station was received at strength six to seven with no form of aerial in circuit. Also, many amateur CW stations have been heard at all times of the day and night.

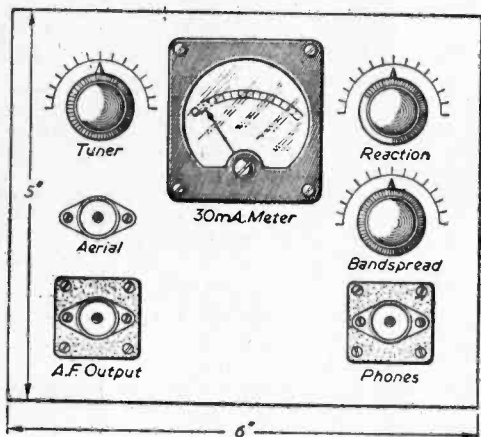



Fig. 1.—The front panel.

able. This assumption was proved to be correct, as the performance of the first stage is more than sufficient for the purpose. Stations from all parts of the globe have been detected on it. As an example a Russian broadcast station was received at strength six to seven with no form of aerial in circuit. Also, many amateur CW stations have been heard at all times of the day and night.


Coil

The coil L1 is home made. Many commercial organisations manufacture suitable types that would work equally well. The description is for the benefit of those who wish to wind one of their own.

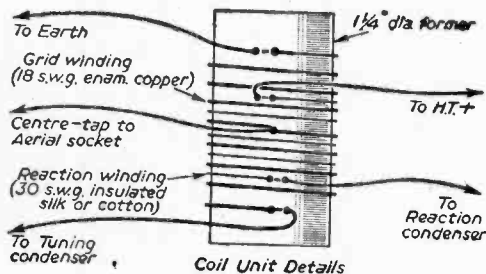A former 1½ in. in diameter and approximately 2 in. long is required. It may be made of porcelain or cardboard or any good stiff insulating material.



Coil Unit Details

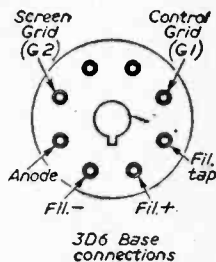

3D6 Base connections

Fig. 2 (left)—Coil details.

Fig. 3 (right)—Valve base connections.

The Valve

The 3D6 is basically an A.F. tetrode with a centre-tapped filament at 1.4V per section. In this circuit, it has been modified to be used as an R.F. triode. The screen grid has been strapped to the anode to form a common electrode which will serve as a triode anode. This valve requires an H.T. of between 90 and 120V. The chosen H.T. will depend on the volume of sound required by the listener. It is suggested that a filament voltage of 3 be used. This of course means that the tapped filament is eliminated. Pins 1 and 8 are the filament connections. A key to the other pin connections is shown in Fig. 3.

Leaky Grid System

A leaky grid system is employed. This being an old favourite of many enthusiasts. It is also a very reliable and inexpensive detector circuit.

The grid capacitor is 200pF in value and must not be less than 100VW for perfect safety. The grid leak resistor is between 2 and 2.5M ΩW.

Reaction Circuit

The reaction circuit employed is commonly known as "anode reaction". It consists of a 0.0003μF solid dielectric variable capacitor in series with a coil, specially wound on the main coil former. If this coil is connected the wrong way round the set may not function; instead a permanent hum may be heard. In this case, all that is required, is to reverse the coil connections.

The 30mA meter is connected in series with the anode of the 3D6. This meter is of great assistance when controlling the reaction. When too

much reaction is used, the meter may read as high as 20mA, or more, depending on the emissive state of the valve. For stable T.R.F. listening with this circuit the meter should read 2mA to 2.5mA. This is the required H.T. current used by the 3D6 while operating under these conditions. If the

Audio Output

The A.F. output is obtained from the anode of the valve. The use of the U.S.W. choke will help to eliminate unwanted noises. The output is powerful enough to operate outdoors and a small loudspeaker may be used as an alternative to headphones. The primary of the loudspeaker transformer is connected in series with the choke instead of the 'phones. The use of a speaker will reduce sensitivity to a small extent but this factor is compensated by better tone.

As seen from Fig. 4, provision for a future audio stage is made by including an extra coaxial socket in the construction. This socket is the A.F. output socket.

A piece of Paxolin lin. is used as a base for the 'phones output socket. The screen of the coaxial cable in this case goes straight to the free end of the choke. The H.T. cable is terminated at a suitable point inside the chassis and the centre of the 'phones coaxial is soldered to this terminal. This wiring allows the H.T. positive to flow to the choke through the 'phones directly. When the 'phones are unplugged then no current will flow in the H.T. line. This eliminates the use of an H.T. switch. No provision is made for

a switch in the L.T. circuit, the L.T. being switched when the 3V cell is disconnected.

Power Requirements

A suitable source of pure D.C. will be required to operate this circuit. Many types of surplus

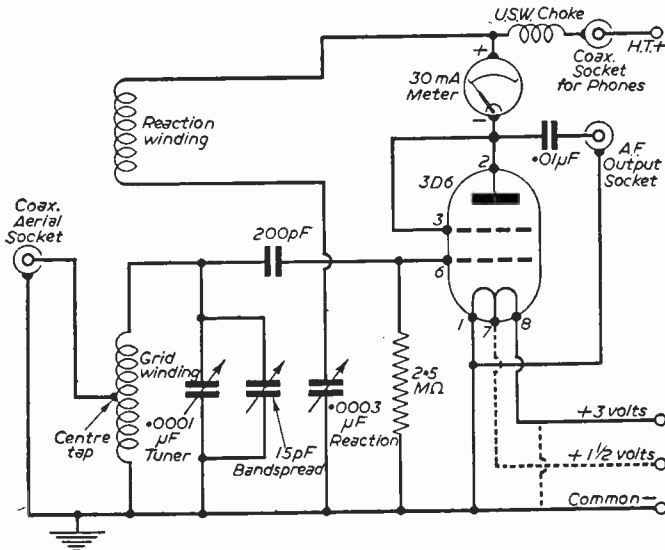


Fig. 4.—The circuit diagram.

meter does not read at all or reads below 1.75mA, then the reaction is too low and should be increased until the meter reads the correct current. This fact can also indicate that no voltage is reaching the anode owing to a component failure.

Battery Failure

The use of the meter will be of great value. Therefore, it is recommended that you should include it in the circuit. Constructors may tend not to use it as it means extra expense. A 30mA meter is quite inexpensive and will add to the appearance of the instrument.

Tuning Controls

The tuning capacitor is a 0.0001μF of the solid dielectric variety also. A 15pF air-spaced capacitor is wired in parallel to act as a bandspread condenser. Great care should be exercised when purchasing the latter. You may discover to your dismay that the moving vanes are loose and erratic. This factor will produce poor tuning as well as noisy conditions. Always ensure that the moving vanes of such a capacitor are tight and sound before purchasing.

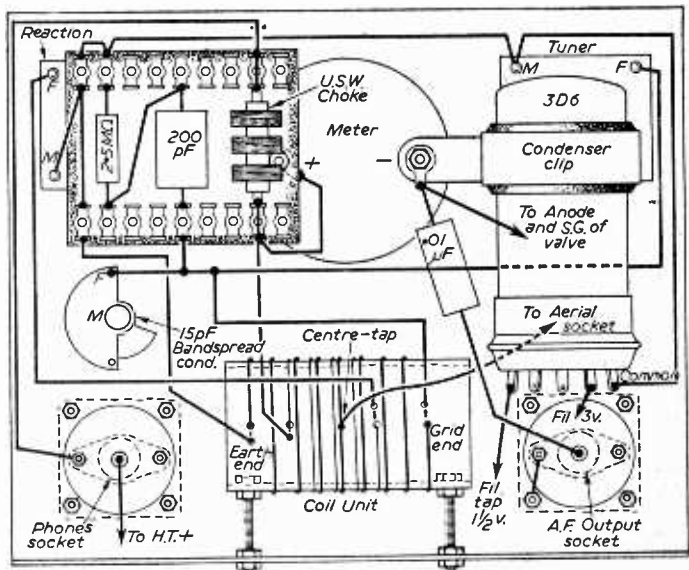


Fig. 5.—The wiring diagram.

"battery" eliminators are sold today. These devices although saving the operator much future expense, cause extra maintenance troubles. For those constructors who already possess an eliminator, the required potentials are as follow: H.T. 90-120V; LT 3-1½V, this depends on the filament circuit preferred. Many battery manufacturers supply combined H.T.-L.T. batteries which would make the set entirely portable. Your local dealer will be only too pleased to answer your battery requirements and will supply your needs at reasonable cost.

Construction

As the circuit is very small and simple, few details of construction are really required. The cabinet used is 6in. x 5in. x 2½in deep. It is cut from 18s.w.g. sheet aluminium. A brief idea of the required dimensions will be seen in Fig. 1. It was felt that full description was quite unnecessary as most constructors will prefer to use a cabinet design of their own in any case.

At convenient spaces on the front panel, three tag mounting strips should be fixed. The wiring of the components is not very critical. The only factor to bear in mind is to keep all wiring as short as possible. A suggested layout for wires is shown in Fig. 5.

COMPONENTS LIST.

1—3D6 valve.	1—15pF air-spaced variable capacitor.
1—Condenser Clip.	1—Coil (see text and Fig. 2).
1—30mA 2in. meter.	1—U.S.W. choke.
1—0.0003μF variable capacitor.	1—2 to 2.5M ½W resistor.
2—Coaxial sockets.	1—200pF fixed capacitor 100VW.
1—B8G valve base.	1—0.001μF 250VW. Dielectric variable capacitor.
Cabinet, nuts, bolts, solder, wire, etc.	

Low Drift V.H.F. Receiver

(Continued from page 496)

hour to check that the tuning has been maintained. If it has not, note carefully whether the correction required to bring the set into tune is an increase or a reduction in the capacity of VC. If a reduction is required, the negative co-efficient in the parallel

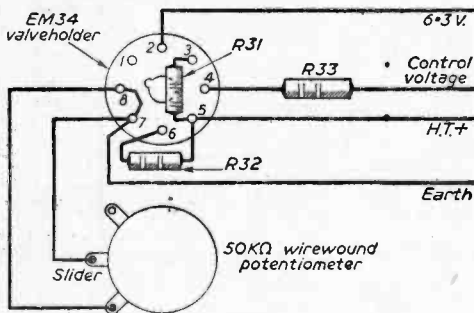


Fig. 11.—Wiring of EM34 tuning indicator.

combination C12, C13 must be increased; if the correction is positive it must be reduced. Any alteration in the value of C12 must be balanced by an alteration in C13 (zero co-efficient) so that the total capacity of the combination remains between 20 and 24pF. The adjustment is not as critical as it sounds and if the receiver is built as specified, the values given in the circuit diagram should be satisfactory.

Alignment Without Instruments

The set can be aligned fairly easily without instruments. If this is to be done, it is advisable to use pre-tuned I.F. and detector transformers, and it will be necessary to fit, temporarily at least, a sensitive tuning indicator such as 6E5 or EM34 for use in place of the high resistance or valve volt-

meter. It should be arranged as previously described with a 50k potentiometer in the cathode circuit and the control grid cable should be fitted with a crocodile clip. Clip the control grid cable to the negative end of C26 and set the cathode potentiometer for maximum shadow angle. Connect a good aerial and proceed as for adjustment of oscillator tuning. Select the strongest transmission that can be found and after checking that it is in fact a BBC transmission, adjust the cores of the I.F. transformers and the top core of RDT for maximum response as shown on the indicator. Now clip the grid to earth and adjust the potentiometer for zero shadow angle. If an EM34 is being used, this means zero on the more sensitive side of the display. Transfer the indicator grid to point Z and adjust the bottom core of RDT for zero output. Re-adjust the top core for maximum response as previously described.

Tests

An approximate acceptance bandwidth test can now be carried out. With the indicator adjusted for zero angle and the grid connected to point Z, tune the receiver slowly "through" a transmission. The two maxima will be observed as equal and opposite deflections of the display each side of the centre zero.

With pre-tuned transformers, the adjustments required will be limited to those necessary to counteract differences in circuit stray capacitances and will be slight. Without pre-tuning, the operation is more difficult but may be achieved satisfactorily within close range of a transmitter or at a greater distance if the receiver has two I.F. stages. The procedure is, the same but the transmission when first received will probably be weak and distorted and will have to be tuned carefully by ear till it is strong enough to show on the tuning indicator. Move the transformer cores each a little at a time and do not make any large movement of any that does not increase the signal. There will be no guarantee of course, that the intermediate frequency finally arrived at is correct, but it is not likely to be far out and the error should not affect the performance of the receiver.

(To be continued)

Examine it
FREE
on 7 DAYS
APPROVAL

RADIO, TELEVISION & ELECTRICAL REPAIRS



AMAZING 'KNOW HOW' BOOK Saves You Pounds

Here is just the practical, at-a-glance guidance YOU need, whether you wish to know how to service radio and TV sets, install lighting points, or repair any domestic appliance, from a bell or an iron to a vacuum cleaner or washing machine. Explains basic principles and working of modern radio and TV sets and electrical appliances. Shows how to test for faults, carry out maintenance and repairs by the most modern methods. Special section on the operation and servicing of frequency modulated receivers. See this great volume NOW on 7 days' FREE APPROVAL. 480 pages. Over 400 illustrations. Yours (if kept) for 21/- (Standard Edition) or 23/- (De Luxe, superb leathercloth).

**ALL THIS—AND MORE
IN ONE GREAT
VOLUME!**

Comprehensive Contents include:


Current, Voltage and Resistance. Coils, Capacitors and Valves. Basic Radio-receiver Circuits. Preliminary Tests. Instruments for Set Testing. Locating Faults. Dynamic Testing. Tuned Circuit Alignment. Noises, Interference, Distortion and Instability. Components. Loudspeakers, Pick-ups. Gramophone Motors. Frequency Modulation. Television Circuits and Test Gear. Television Faults, Symptoms and Cures. Aerials and Pre-Amplifiers. Maintenance of Domestic Electric Wiring. Small Appliances. Fires and Space Heaters. Vacuum Cleaners and Polishers. Rewinding Small Motors. Cookers and Boiling Plates. Washing Machines. Refrigerators. Electric Water Heaters. Battery Charging, Testing and Repairs, etc.

ESSENTIAL TO EVERY SERVICE ENGINEER, ENTHUSIAST AND HANDYMAN!

Getting the best from RADIO AND TV SETS

Here is expert advice that will enable you to make the necessary adjustments or repairs in order to get the best possible performance from any radio or TV set.

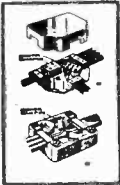
All you need to know about DOMESTIC WIRING



Learn from these helpful pages how to carry out all kinds of installations and extensions—with efficiency and safety! Complete guidance on conductors, insulation, safety regulations, conduits, cables, earthing, practical work, fuses, flexible cords, etc.

BASIC RADIO CIRCUITS

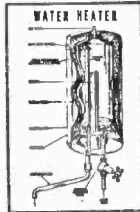All you want to know about circuits, so that you can find your way around modern sets without hesitation. How components form various types of set: gives circuits for 1-valve receiver, 3-valve receiver, battery TRF receiver. 4-valve superhet, Universal sets, etc.



FIRES & SPACE HEATERS


Full, easy-to-follow instructions for servicing small domestic fires—whether of the radiant, reflector or convector type.

WATER HEATING

All you should know about the various types of electric water-heaters and how to install them and keep them in perfect working order. Advice that will save you POUNDS!

TRACKING DOWN TROUBLE

This grand book is invaluable for tracing faults in radio and TV sets. Tells you all you want to know—from how to carry out Preliminary Tests to how to align R.F. and I.F. circuits. Shows how to carry out Dynamic Testing. Also shows how to trace the causes of Noises, Distortion and Instability and deal with the trouble. Gives detailed information on Components and Loudspeakers and how to deal with any faults that may develop.

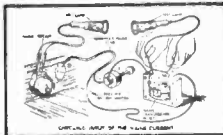

See how to maintain
**Vacuum Cleaners
and Floor Polishers,
Refrigerators, Cookers
and Boiling Plates,
Washing Machines, etc.**
Do your own
BATTERY CHARGING
Here are clear, complete instructions.

DO THIS NOW!

Fill in form and post in 2d. stamped, unsealed envelope to Dept. E.B.35, Odhams Press Ltd., Basted, Sevenoaks, Kent. Book comes to you on FREE APPROVAL; if satisfied you send remittance, otherwise return book in 8 days. Offer applies in U.K. and Eire only, closes October 31.

POST FORM TODAY!

Dept. E.B.35, Odhams Press Ltd., Basted, Sevenoaks, Kent
Please send me, WITHOUT OBLIGATION to PURCHASE, "Radio, Television and Electrical Repairs".
Within 8 days I will EITHER return book in good condition postage paid, OR send remittance for cash price.
Cross out Edition NOT wanted: Standard (21/-)/DeLuxe (23/-)
Delete words NOT applicable: I am (a) houseowner, (b) tenant in house or flat, (c) temporary resident, (d) single (e) married. (f) over 21. (g) under 21.

Your signature _____
*(If under 21, signature of father; if married lady, signature of husband)


NAME _____
Full Postal ADDRESS _____
E.B.35/Oct. 60 _____

Firmly affix
2d. stamp
in margin

WEYRAD

COILS AND TRANSFORMERS FOR A 2-WAVE TRANSISTOR SUPERHET WITH PRINTED CIRCUIT AND FERRITE ROD AERIAL

- LONG AND MEDIUM WAVE AERIAL—RA2W
On 6 in. rod, $\frac{7}{8}$ in. diameter, connections to 6-Tag Ring, 208 pF tuning 12/6
OSCILLATOR COIL P50/IAC
Medium wave in screening can. For 176 pF tuning condenser 5/4
1st AND 2nd I.F. TRANSFORMERS—P50/2CC
470 Kc/s operation with 250 pF tuning in cans. $\frac{1}{8}$ in. diameter by $\frac{3}{4}$ in. high 5/7
3rd I.F. TRANSFORMER—P50/3CC
Last stage transformer to feed diode detector. Size as P50/2 6/-
DRIVER TRANSFORMER—LFD2
Upright mounting with six connecting tags— $1\frac{1}{8}$ in. x $\frac{7}{8}$ in. x $1\frac{3}{4}$ in. 9/6

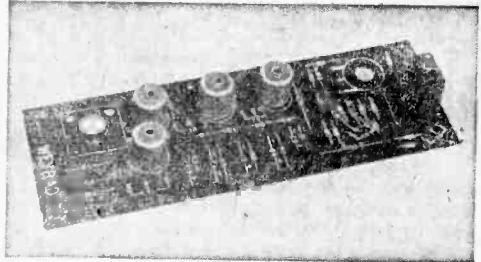

PRINTED CIRCUIT—PCA1

Size $2\frac{3}{4}$ in. x $8\frac{1}{4}$ in. Ready drilled and printed with component positions 9/6

THESE COMPONENTS ARE APPROVED BY TRANSISTOR MAKERS AND PERFORMANCE IS GUARANTEED.

Constructor's Booklet with full details, 2/-.

WEYMOUTH RADIO MANUFACTURING CO., LTD.
CRESCENT STREET, WEYMOUTH, DORSET


KINGSMERE SUPPLIES LIMITED

Insured Post 1/-, over £2 Free. (Export extra.)
Single valves, post 6d.

MAIL ORDER HOUSE

TERMS: Remit with Order or C.O.D.
Cash refund guarantee!

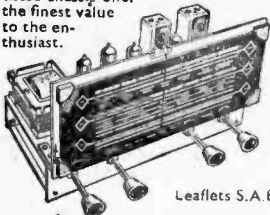Built to the highest specifications, these chassis offer the finest value to the enthusiast.



Leaflets S.A.E

ALL BRITISH RADIOGRAM CHASSIS 3 WAVEBANDS 5 MULLARD VALVES
ECH81, EF89, EBC81, EL84, EZ83
Brand new and guar. A.C. 200/250 v. Short - Medium - Long Gram. P.U. High Q dust core coils. Latest circuit technique. AVC and neg. feedback. 4 watts. Chassis size $13\frac{1}{2}$ x 6 x 7in. high. Aligned and calibrated ready for use. Quality at Low Cost. Chassis isolated. H.P. Dep. £5 and five monthly of £1.

OUR PRICE £9.90

Matched Speakers, 5in., 6 $\frac{1}{2}$ in., 8in., 17/6 ea. 10in. 25/-.



BRAND NEW AND BOXED

OUR PRICE POST FREE
£6.15.0
4 SPEED MODEL UAB

GARRARD 4-SPEED HIGH FIDELITY UNITS

Autochanger 121 Mk.11 £9.19.6
Single Player TA Mk.11 8 gns. Price inc. plug-in, normal heads. Stereo hds. £2 ex.
Transcription 4 HF 17 gns.

BRAND NEW

OZ4	6/-	6BA6	7/6
IR5	7/6	6BE6	7/6
ISS	7/-	6C4	5/6
IT4	6/-	6D6	6/-
2X2	3/6	6F6G	7/6
3Q5	9/-	6G6	5/6
3S4	7/6	6H6	3/6
3V4	7/6	6I5	5/6
5U4	7/6	6J7G	6/6
5Y3G	7/6	6K6GT	6/6
5Z4G	9/6	6K7G	5/-
6AC7	5/-	6K8G	7/6
6AG5	5/-	6N7M	6/6
6AL5	5/6	6O7G	7/6
6AM6	5/-	6SA7M	6/-
6AT6	7/6		
6B8G	5/-		

VALVES

6SJ7M	6/6
6SN7GT	6/6
6U5G	7/6
6V6G	6/6
6X5G	6/-
12A7	8/-
12AU7	7/6
12AX7	7/6
12K7GT	6/6
12Q7GT	6/6
25Y5G	9/6
35L6	9/6
30Z4	9/6
807	7/6
807A	5/6
954	1/6
Y56	2/6
DAF96	8/6

Matched Pairs 1/- extra

EL41	9/-
EL84	8/6
EM81	9/6
EY51	9/6
EY86	10/-
EZ40	7/6
EZ80	7/-
EL148	1/6
HABC80	
ECL80	10/6
ECL82	10/6
EF39	5/6
EF41	9/6
EF80	7/6
EF91	5/-
EF92	5/-
PCF34	9/6
PCF80	9/6


PLASTIC RECORDING TAPE

Long Play		Standard	
7in. reel, 1,800 ft.	32/6	7in. reel, 1,200ft	21/-
5 $\frac{1}{2}$ in. reel, 1,200ft.	22/6	5 $\frac{1}{2}$ in. reel, 850ft.	17/6
5in. reel, 850ft.	19/6	5in. reel, 600ft.	15/-
3in. reel, 225ft.	7/6		
Spare Plastic reels all sizes 3/-			
"Instant" Bulk Tape Eraser and Head De-fluxer, 200/250 v. A.C.. 2/6. Leaflet, S.A.E.			

SETS OF VALVES

24/6	IR5, IT4, ISS, 354 or 3V4.
29/6	DK96, DF96, DAF96, DL96.
29/6	6K8, 6K7, 6Q7, 6V6, 5Z4 or 6X5.
39/6	ECH42, EF41, EBC41, EL41, EZ40.
39/6	ECH81, EF89, EBC81, EL84, EZ80.
39/6	12K8, 12K7, 12Q7, 35L6, 35Z4.
39/6	UCH42, UF41, UBC41, UL41, UY41.
39/6	UCH81, UF89, UBC81, UL84, UY85.

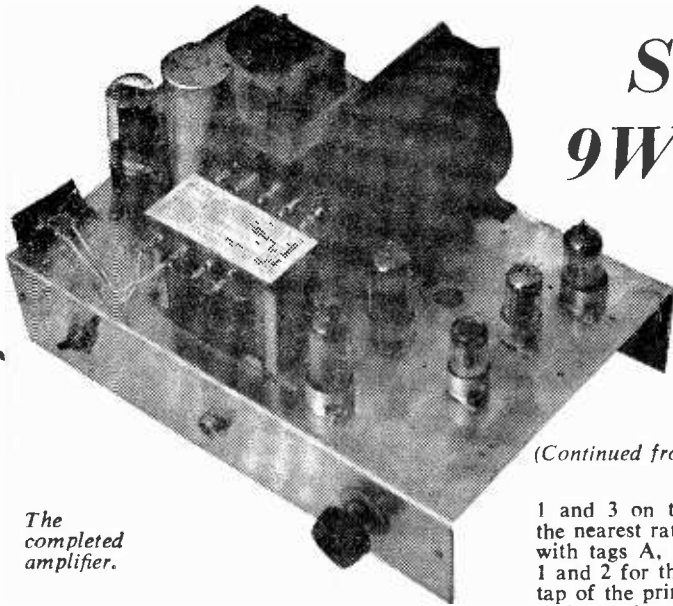25 FOAMCOURT WAY, FERRING, WORTHING, SUSSEX



The completed amplifier.

Six Valve 9W Amplifier

A VERSATILE, HIGH
OUTPUT, CIRCUIT

By F. G. Rayer

(Continued from page 394 of the September issue)

THE smoothing chokes used for the amplifier should be of generous current carrying capacity and surplus chokes can be obtained at low cost. The actual inductance of the choke is of no importance, provided it is several Henrys. It must be rated to carry 120mA or more. With a 300V transformer, the choke should not be more than about 80Ω to 100Ω resistance. With a 350V transformer it can be about 400Ω.

Output Transformer

The specified transformer is suitable for outputs up to 10W, and provides a large number of optional ratios, to suit 2/3Ω, 7½Ω, and 15Ω speakers. The anode-to-anode load required is approximately 10,000Ω. With a 15Ω speaker, the nearest ratio is 27:1, obtained by using tags A, C and E on the primary, and 3 and 4 on the secondary. For a 7½Ω speaker, the nearest ratio is 35:1, requiring the use of tags A, C and E on the primary, and

1 and 3 on the secondary. For a 2/3Ω speaker, the nearest ratio is 50:1, and this will be obtained with tags A, C and E used for the primary, and 1 and 2 for the secondary. In all cases the centre-tap of the primary is wired to the 16μF condenser, and equal ratios each side to the output valve anodes. The secondary tags are connected to the output sockets provided for loudspeaker connecting purposes.

Surplus or other output transformers can be used, provided they can carry a minimum of 60mA in each half of the primary, and are of a suitable ratio for the speaker. Very small transformers cannot be used because their rating would be too low.

Amplifier Cover

To make the cover, two wooden ends are cut from ¼in. to ½in. wood, as shown in Fig. 4. Each is the same width as the chassis, and about 8in. high. If the chassis has end runners, the wooden ends are screwed to these from inside. If not, they are screwed to the smaller pieces of wood mentioned, which in turn fit inside the chassis ends.

A piece of perforated metal about 24in. long, and wide enough to overlap the wooden ends, has

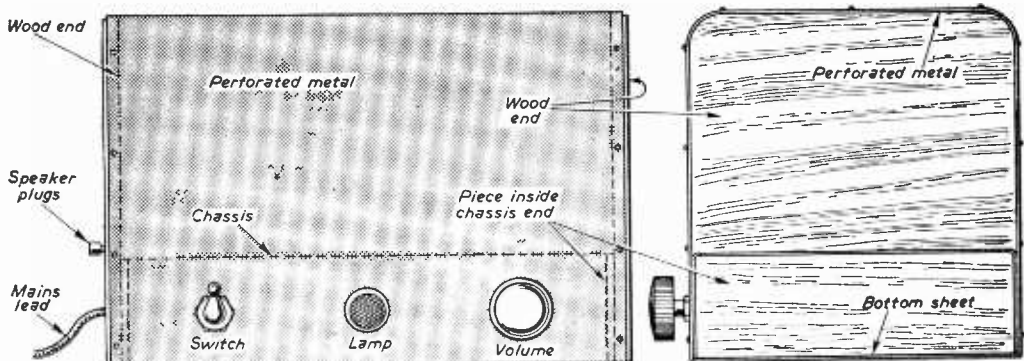


Fig. 4.—The case of the amplifier.

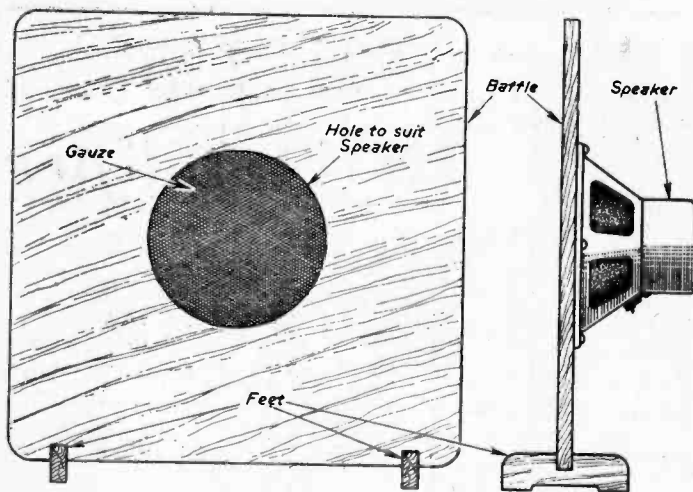


Fig. 5.—A baffle for the loudspeaker.

holes cut to clear switch, lamp holder bush, and volume control bush. The nuts are then removed from these items, so that they can be used to clamp the perforated metal to the front of the chassis.

The metal is then taken up, across the top, and down the back, being drawn tight and fixed with small screws. Small holes are needed to clear the input socket and terminal. A metal sheet is cut to cover the bottom of the chassis, and screwed to the wood.

Clearance holes are bored opposite the speaker sockets. A hole is also required for the mains lead. The amplifier can be serviced, if necessary, by merely removing the perforated metal, the wooden ends serving as rests so that it can be placed in an inverted position.

If a 3-pin plug is to be used for supplies, wire the amplifier chassis to earth, using the large pin for this. The switch should be in the red lead. When current is drawn from a 2-pin plug, the chassis is *not* wired to either mains lead.

Speaker

Various forms of cabinet can be used, and it is not proposed to cover the construction of these here. If no such cabinet is available, it is possible to use a flat baffle of the kind shown in Fig. 5. This consists of a single stout board, mounted on feet large enough to prevent it tipping over.

It will be remembered that small speaker units will be unable to handle the full output of the amplifier, so that it is necessary to use a model rated to handle at least 9W. The cone diameter is measured, and the hole in the baffle is cut out to agree with this. The speaker is then firmly screwed to the board, gauze being used to protect the cone.

The actual size of the baffle is in no way critical, except that a large baffle will give better bass response. However, a baffle 24in. x 24in. will be satisfactory for general purposes, and this size is illustrated. The board should be thick—at least $\frac{1}{2}$ in. minimum. If plywood is used it must

be free from loose pieces which would cause buzzing noises. This trouble is not likely unless the baffle has been allowed to become damp.

It is in order to use two or more speakers, with a cross-over circuit to obtain improved frequency response or to mount the speaker off-centre so that the distance from it to the edges of the baffle is unequal in each direction.

Using the Equipment

With a microphone or similar unit, sound from the loudspeaker must not reach the microphone with any strength, or howling will be caused. The minimum distance between loudspeaker and microphone depends on the volume control setting, the degree to which the microphone is directive, and other points, but can easily be

found by experiment if necessary.

The lead carrying the input to the amplifier must be screened, the screening being connected to chassis. This can be arranged by any of the methods already described. A single, screened lead is frequently employed, the braiding acting as the second conductor, or earthed return.

The input impedance of the amplifier is 100k, this giving reduced susceptibility to hum, etc., compared with extremely high impedances. Moving coil microphones require the usual matching transformer, as they are of low impedance.

Pocket Transistor T.R.F.

FROM correspondence which we are receiving, it is evident that some readers are experiencing difficulty in obtaining the materials for the tuning coils used in the above receiver (which was described in the July and August issues). These coils are wound on ferrite pot-core assemblies, Type 9A, obtainable from Denco (Clacton) Ltd., 357/9, Old Road, Clacton-on-Sea, Essex. The windings are of 5/47 Litz wire which can be obtained from Post Radio Supplies, 33, Bourne Gardens, London, E.4.

Miniature transistor I.F. coils differ from these coils in the number of turns used, but they may be used for experiments with inductive tuning.

Advertisement Price

THE three-speed Transistor Record Player advertised by Lasky's Radio on page 332 of the August issue was priced at £19 19s. 6d.; readers should note that this price should have been £9 19s. 6d.

"POST HASTE" — "POST FREE"

JASON F.M. TUNER KITS

We are the Authorised Jason Dealer and the whole kit is as supplied by them. You can therefore safely return to Jason for alignment without them rejecting it for non-standard components.

We can also align for the standard charge.

- FMT1 is the standard variable tuner for cabinet mounting, unpowered. Supplied complete with four EF91 valves ... **£6.16. 0**
 Hire purchase Deposit **£1.8.6** and 6 monthly Instruction book, 2/6 extra. **£1. 1. 4**
- FMT1 Power pack with ready drilled chassis kit ... **£2. 1. 9**
- FMT2 is a new tuner in a green modern case, which can be used for shelf or cabinet mounting, and has space for power supplies if required. Supplied complete with four EF80 valves ... **£7. 6. 6**
 Hire purchase Deposit **£1.10.6** and 6 monthly **£1. 2. 8**
- FMT2 With power. Complete kit ... **£9. 2. 0**
 Hire purchase Deposit **£1.18.0** and 6 monthly Instruction book, 2/6 extra. **£1. 7. 4**
- FMT3 is the Fringe version and should be used when further than 70 miles from transmitter. Supplied complete with 6 valves ... **£9. 3. 6**
 Hire purchase Deposit **£1.17.6** and 6 monthly **£1. 7. 8**
- FMT3 With power. Complete kit ... **£10.19. 0**
 Hire purchase Deposit **£2.5.0** and 8 monthly Instruction book, 2/6 extra. **£1. 4. 3**

NEW JASON SWITCHED TUNERS

The JTV/2 and Mercury 2 are both of the pre-set station type with the addition of BBC and ITA sound. They use the latest "Fireball" turret and the A.F.C. ensures freedom from drift. The Mercury 2 is for cabinet mounting with external power supplies. The JTV/2 has the same tuning heart, with power supplies mounted in a case. This again can be used for shelf or cabinet mounting. The JTV/2 cannot be supplied less power.

- JTV/2 Complete with valves and book ... **£14.14. 9**
 Hire purchase Deposit **£3.4.9** and 12 monthly **£1. 1. 1**
- Mercury 2 Complete with valves and book ... **£10.16. 6**
 Hire purchase Deposit **£2.4.6** and 8 monthly **£1. 4. 0**
 Power pack for Mercury 2 in kit form ... **£2. 1. 9**
 Instruction book for switched tuners, 3/6.

IMPORTANT

Required channels must be specified. All Jason kits can be supplied less valves. To find the cash price, less valves, deduct 7/6 per valve.

A more detailed price list can be sent upon request.

ALL JASON TUNERS ARE ON DEMONSTRATION

GRAMOPHONE EQUIPMENT

- B.S.R. Monarch TC8H, cartridge ... **£6.15. 0**
 Hire purchase Deposit **£1.7.0** and 6 monthly **£1. 1. 4**
- Collaro Conquest "O", cartridge ... **£7.15. 0**
 Hire purchase Deposit **£1.11.0** and 6 monthly **£1. 4. 0**
- Garrard TA Mk.2 GCB, cartridge ... **£8.10. 0**
 Hire purchase Deposit **£1.14.0** and 6 monthly **£1. 6. 0**
- Garrard 4HF, GCB, cartridge ... **£18. 9. 9**
 Hire purchase Deposit **£3.19.9** and 12 monthly **£1. 6. 7**
- Philips AG209, AG3016, cartridge ... **£10.10. 0**
 Hire purchase Deposit **£2.2.0** and 8 monthly **£1. 3. 6**
- Connoisseur 2-speed Transcription unit ... **£16.13. 1**
 Hire purchase Deposit **£3.13.1** and 12 monthly **£1. 3. 10**
- Garrard TPA12, Pick-up arm, less cartridge ... **£4. 9. 6**
- Garrard GCS10, Stereo cartridge ... **£1.12.10**
- Garrard GCB, Mono cartridge ... **19/7**
- Collaro "R", Stereo turn over cartridge ... **£3.19. 6**
- Acos 71/5, Stereo cartridge with diamond ... **£2.12.10**
- B.S.R. Mono turn over cartridge ... **£1. 9. 9**
- Garrard SPG3, new stylus gauge, 0-12 grammes ... **19/6**

For further information please write for manufacturers' list.

TAPE EQUIPMENT

- Collaro Studio Deck. 3 speed, 3 motors, 7in. spools. Pause control space for third head, piano keys, counter.
 List price **£17.10.0** OUR PRICE **£14. 0. 0**
 Hire purchase Deposit **£3.0.0** and 12 monthly **£1. 0. 2**

- Tape Amplifier for Studio Deck. Completely assembled by famous maker. NOT A KIT. Full wiring plans to connect to deck. Magic Eye, Radio and Mic inputs, Mixing and Superimposing ex L/S socket. Low level input tone control. Can be used as amplifier. EF86, ECC83, 2—EL84, EM84, EZ80, OA81. 3 watts output. CASH PRICE **£10.10. 0**
 Hire purchase Deposit **£2.2.0** and 8 monthly **£1. 3. 6**

- Tape Recorder Case to house the above Deck and Amplifier. Two tone colour ... **£5. 5. 0**
 EMI speaker, 10 x 5in., to fit case ... **£1. 5. 0**
 1200ft. Brand Five Tape, 25/-; Crvstal Mic, 40 mic, 1 set of knobs and plates for amplifier, 12/6; Screened input plugs, 4/6 each. **£1. 7. 0**

- The above Recorder complete to PERSONAL SHOPPERS ONLY for ... **£35. 0. 0**
 Hire purchase Deposit **£7.0.0** and 12 monthly **£2. 11. 4**
 This machine is a first-class job and illustrated sells at **£41. 0. 0**

SEND FOR MAKER'S ILLUSTRATED LEAFLET

- B.S.R. Monardeck TDI 3½ i/s. One motor, 5½in. spools. List price **£12.12.0** OUR PRICE **£9.15. 0**
 Hire purchase Deposit **£1.19.0** and 6 monthly **£1. 9. 4**
- Collaro Tape Heads, Record/Playback and Erase ... **37/6 pair**

TRANSISTORS

ALL MANUFACTURED BY MULLARD

	List Price	OUR PRICE	
OC44 Mixer ...	26/-	12/-	+ Red Spot
OC45 I.F. ...	23/-	12/-	+ A.F. 5/-
OC71 Audio ...	14/-	8/6	+ "
OC72 Audio ...	17/-	8/6	+ "
OC78D Driver ...	17/-	10/-	+ White spot
OC78 Audio ...	17/-	10/-	+ R.F. 6/-

TEST METERS

- CABY A10 D.C. volt (Sensitivity 2000 ohms per volt), 10v, 50v, 250v, 500v, 1000v.
 A.C. volt (Sensitivity 2000 ohms per volt), 10v, 50v, 250v, 500v, 1000 volt.
 Resistance ohms 10K, 1 meg. ohm.
 D.C. current, 0.5mA, 25mA, 250mA.
 Will also measure decibels. Size 5 x 3½ x 2½in.
 PRICE **£4.17.6**

- CABY B20 D.C. volt (Sensitivity 10,000 ohms per volt), 0.5v, 2.5 volt.
 D.C. volt (Sensitivity 4000 ohms per volt), 10v, 50v, 250v, 1000 volt.
 Resistance ohms 2K, 200K, 2 meg, 20 meg ohm.
 D.C. current, 100 micro/A, 2.5mA, 25mA, 250mA/A.
 Will also measure decibels. Size 6 x 4 x 2½in.
 PRICE **£6.10.0**

WE PAY ALL POSTAGE AND INSURANCE
ALL ORDERS DEALT WITH SAME DAY
MONEY WILL BE REFUNDED IF REQUESTED

SURBITON PARK RADIO, 48 Surbiton Road, Kingston upon Thames, Surrey

(Established over 30 years)

Telephone: KIN 5549

HOURS: 9 a.m. to 6 p.m. 1 p.m. Wednesday.


OPEN ALL DAY SATURDAY—WE DO NOT CLOSE FOR LUNCH

Gladstone Radio

PUSH-PULL AMPLIFIER £4.17.6 (3/6 P. & P.)


Suitable for crystal mike input

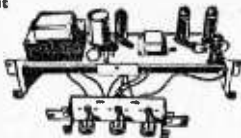Brand new by famous manufacturer. 200-240 A.C. mains. Bass, treble and vol. controls flying panel. With valves EZ80, ECC83 and 2-EL84 giving full 8 w. Chassis 12 x 3½ x 3½ in. With o.p. trans. for 2-3 ohm speaker.



SIX TRANSISTOR SUPERHET KIT £8.19.6

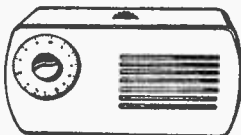Med. and L.W.; Printed Circuit; Instruction Book. Internal aerial. All items supplied separately. Write for price list. Battery, 9 v., PP4, 2/6.



COMPLETE TAPE RECORDER FOR ONLY £19.19.0

B.S.R. deck. Two-tone leatherette case. Acos crystal mike. 850ft. tape, extra spool. On/Off Tone and Vol. 7 x 4in. Speaker. 1½ hrs. playing time. Single speed 3½ in./sec., fast forward and reverse, mike and radio inputs, ext. speaker socket; cannot be accidentally erased, 13½ x 12 x 8in. Weight 20 lbs. 12 months guarantee. Carr. 7/6 extra. Terms: £6 down and 6 monthly payments of 50/-.

RADIOGRAM CHASSIS by famous manufacturer

Chassis 16½ x 6½ x 7in. high. Dial in red, gold and brown. 18 x 4in. 1000-2000M; 200-550M and 6-18Mc/s. 4 knobs in front. Ferrite rod aerial; Tone control; Ext. L.S.; P.U.; Ac and E sockets. Gram. mains socket 200-225 v. and 226-250 v. A.C. Valves ECH81, EBF80, ECC83, two EL84 in push-pull. GZ30 rect. Fine value for money at £7.10.0 (7/6 carr.). A cheaper Radiogram Chassis for £6.10.9 (7/6 carr.). Chassis 16½ x 5½ x 6in. high. Dial in gold and brown 15½ x 4½ in. 4 knobs, two at each end. Tone; ext. L.S.; P.U.; Ac; Earth. Valves EZ40, ECH42, EF41, EL41, EBC41. Also by the manufacturer of above chassis.

Cossor Battery Eliminator for 35/- (2/6 post). 90 v. at 12mA and 1.4 v. at 125mA. In two units to take the place of existing batteries.

COMPLETE V.H.F./A.M. RADIO FOR £12.12.



Brand new set, in superb walnut cabinet (size 19 x 8½ x 14½ in. high). Covering 80-100 Mc/s, 16-49 M., 200-500 M. and 1,200-2,000 M. Mains trans. 200-250 v. with 3 tappings. Ferrite rod aerial for A.M. Controls: volume on/off, tone, tuning, w/change. Gram. and ext. speaker position provided. Fully guaranteed. Post and packing 10/- extra. Terms: £3.12.0 down (inc. carr.) and 5 monthly payments of £2. Indoor V.H.F. aerial 10/- extra, cash.

FOR ADDRESSES SEE THE OTHER ADVERTISEMENT FOR GLADSTONE RADIO ON PAGE 465.

Let I.C.S. train YOU!



COURSES ON:-

RADIO and TELEVISION SERVICING . ELECTRONICS EXAMINATION COURSES FOR:-

- **C. & G. & Radio TV Servicing Certificate** (R.T.E.B.)
- **C. & G. Radio Amateurs' Exam.** (Amateurs' Transmitting Licence)
- **British Institution of Radio Engrs., etc.**
- Whether you plan to have your own business, to become an electronics engineer or to take up a career in industry, an I.C.S. Course will help you to succeed. You learn at home in your own time, under expert tuition. Moderate fees include all books.



LEARN - AS - YOU - BUILD

Practical Radio Course

- A basic course in radio, electronic and electrical theory backed by thorough practical training. You build a 4-valve T.R.F. and a 5-valve superhet radio receiver, signal generator and multi-tester.
- Other Learn-as-you-Build radio courses are available

MULTI-TESTER

(Sensitivity 1,000 ohms per volt)

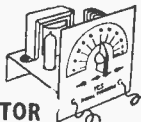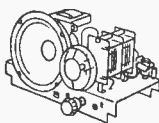

- **5-VALVE SUPERHET RECEIVER**
- **RF/AF SIGNAL GENERATOR**

Post this Coupon TODAY!

for FREE book on careers in Radio, etc., and full details of I.C.S. Courses.

INTERNATIONAL CORRESPONDENCE SCHOOLS

(Dept. 171), Intertext House, Parkgate Road, London S.W.11.

Please send book on.....

Name..... Age.....
(Block Letters please)

Address.....

Occupation..... 10-60

INTERNATIONAL CORRESPONDENCE SCHOOLS

Simple Communications System

A THREE VALVE, THREE STATION CIRCUIT

By P. Rushen

THE equipment described here was designed primarily to meet the communications requirements of a local establishment.

It was required to provide an easily operated two-way communication system between an office and two other points within the same building. A call system was also required which would enable the "Master station" to call either or both of the subsidiary stations. As an additional facility, two-way communication between the two subsidiary stations was made possible, with the "Master station" being able to "listen in" to the conversation if so required.

The Master Unit

Except for the speakers and operating switches of each sub-unit, the entire system is contained within the Master unit (Fig 1). The mains transformer T3 should be capable of giving, in conjunction with V3, a D.C. line voltage of approximately 220 at a D.C. load current of 55mA, and a 6.3 filament supply of 2A. The output transformer T2 is required to match the output valve, in this case an EL84, into a 3Ω voice coil load. A turns ratio of approximately 45:1 would be suitable here.

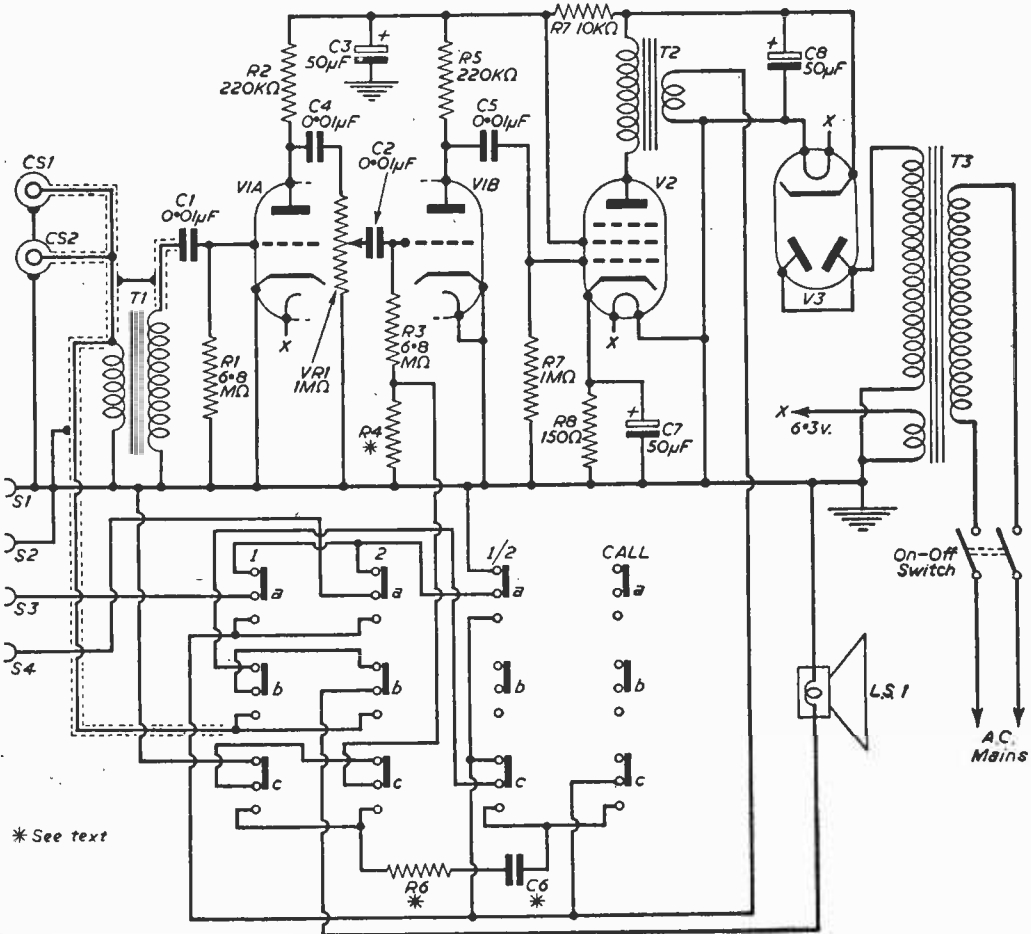


Fig. 1.—Circuit of the master unit.

The input transformer T1 in the original unit had a ratio of 75:1, but a ratio no higher than that necessary to produce an adequate output is all that is required for this purpose. A good bass response is not required and a high inductance

unscreened "banana" type. CS1 and 1¹, CS2 and 2¹ are coaxial screened types.

The Speak/Listen switches on the sub-units connect the loudspeaker to the output transformer in the Listen position and to the input transformer in the Speak position. The switches are non-latching spring loaded, with return to the Listen position. The screening shown is essential and orientation of the input transformer will almost certainly be necessary, in fact it may be found necessary either to screen the transformer completely or have it as a separate unit, well removed from the main unit and any other mains wiring adjacent to it.

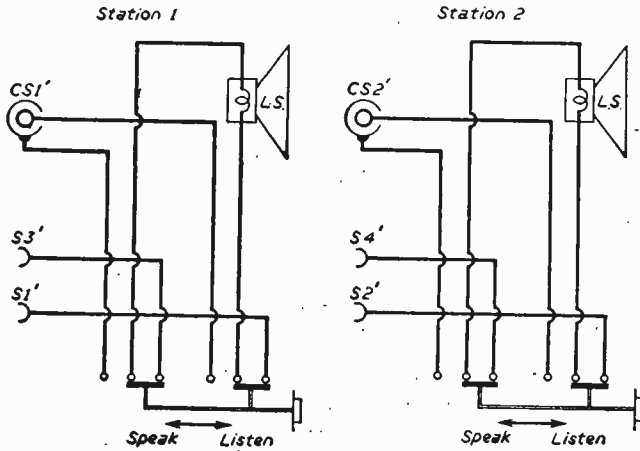


Fig. 2.—Slave unit circuitry.

secondary will give "hum" trouble. An alternative method of connection for the input transformer is shown in Fig. 4. For a transformer ratio of 45:1, Rx should be about 3,300Ω and Ry chosen for optimum output with minimum hum.

Control Switch

A four-section "press button" or "piano key" type switch is required. Although the full requirement of the unit only partly fills a four-button, three-pole changeover type, it is likely that the four switches will have at least three changeovers on each and they are therefore shown as such, with the sections not in use unconnected. Only the key 1/2 is a latching one, keys 1, 2, and Call are non-latching. Key 1/2 is released when either key 1 or 2 is operated. The Call key is non-releasing. A simple modification can usually be made to any full latching switch to produce the required arrangement.

Speaker LS1 and the speakers of Stations 1 and 2 can be any type of moving-coil loudspeaker, although small ones are recommended for convenience. For sound-balance and consistent "Call" operation, similar speech-coil impedances are desirable although not essential.

Sockets S1, 2, 3 and 4 on the Master unit and S1¹, 2¹, 3¹ and 4¹ on the sub-units are of the single

tone. It will be seen that R4 is short-circuited (via 1c and 2c,) a precautionary measure, taken to avoid both the possibility of accidental "calls" and that of unwanted feedback across R4 during operation. The "Call" button, operated by itself thus has no effect.

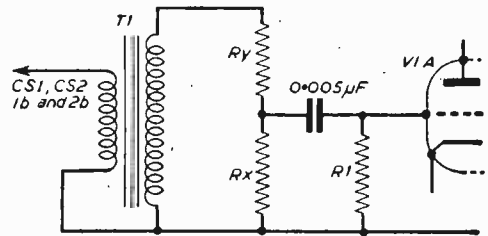


Fig. 4.—Alternative connections for the input transformer.

To call a sub-station, the operator presses the appropriate key or button and "Call" button together, release them both and awaits a reply.

Key 1/2

This is a latching key and when latched enables stations 1 and 2 to communicate with each other via the Master unit. The Master unit operator can listen in to this two-way conversation by pressing the "Call" button, which will now connect his loudspeaker to the output transformer via "Call" c, 1/2c, 1b and 2b.

Key 1

This is the Master unit operator's switch for communication with Station 1. It is non-latching and connects LS1 alternately to the output trans-

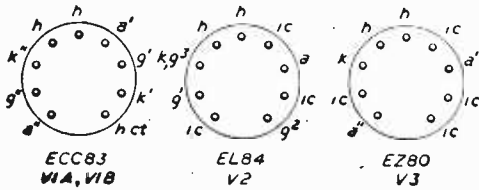


Fig. 3.—Valve base details.

(Continued on page 542)

You can't help earning more!

WITH NEWNES

Radio & Television Servicing




NEW 1960 Edition in 6 volumes FREE FOR 7 DAYS

This New Edition of Newnes Complete Library of Servicing Data is exactly suited to your needs. Here in six packed volumes are all the circuits, component and layout diagrams you must have for speedy, efficient repair work, tuning and general maintenance—over 2,300 models pre-1954 right up to 1960. All the famous makes below are included—everything you want for years to come. If you've never seen previous editions be sure to see this one!

TELEVISION, RADIO, RECORD REPRODUCERS, TAPE RECORDERS

All these popular makes—

Ace, Alba, Ambassador, Argosy, Armstrong, Baird, Banner, Beethoven, Berec, Brayhead, Bush, Capitol, Champion, Channel, Collaro, Cossor, Cydon, Dansette, Decca, Defiant, Dynatron, E.A.R., Eddystone, Ekco, Elizabethan, E.M.I., Emerson, English Electric, Ever Ready, Ferguson, Ferranti, G.E.C., Grundig, H.M.V., Invicta, K-B., McCarthy, McMichael, Marconiphone, Masteradio, Motorola, Murphy, Pageant, Pam, Perdio, Peto Scott, Philco, Phillips, Pilot, Portadyne, Pye, Pye Telecommunications, Radiomobile, Rainbow, Raymond, Regentone, R.G.D., Robert's Radio, Sobell, Spencer-West, Stella, Strad, Ultra, Valradio, Vidor, Walter, Webcor.

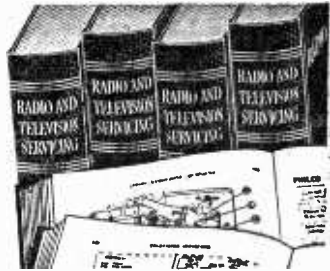

Important Reference Data on Valve and Picture Tube Bases and Equivalents. B.B.C. and European Broadcasting Stations. TV and VHF/FM Channel and Stations.

**OVER
2,300
POPULAR
MODELS**

MORE THAN

3,800

Circuit & Component
Layout Diagrams

OVER

3,750 Pages

**2 Years' Free
Postal Advisory
Service**

*Increases your earnings
FOR YEARS TO COME*

An investment
for every reader
of Practical Wireless

Ready for instant use are thousands of diagrams—TV receivers from single band sets to latest 13-channel 110°-tube models, including transportables, and combined TV/FM sets. Also radios, including Transistor and VHF/FM models, Radiograms, Portables, Transistor Personals, Tape Recorders, Car Radios, Record reproducers (including Stereo).

Practical Guidance on Modern Circuit Developments. Fault-finding and Alignment. Servicing Tape Recorders. Aerial Installation. Electrical and Car interference suppression. Servicing Transistor and VHF/FM Radios. Printed-wiring sets. Servicing Equipment. Salvaging Picture Tubes, etc.

POST NOW No Cost-No Obligation

GEORGE NEWNES, LTD., 15-17 Long Acre, London. W.C.2

Please send me Newnes RADIO AND TELEVISION SERVICING without obligation to purchase. I will return it in 8 days or send 11/- deposit 8 days after delivery, then twenty monthly subscriptions of 11/- paying £11 11s. 0d. in all. Cash price in 8 days is £11.

Name _____

Address _____

Occupation _____

Your Signature _____

(Or Your Parent's Signature if under 21)

RV117

Tick (✓) where applicable

HouseOWNER	<input type="checkbox"/>
Householder	<input type="checkbox"/>
Living with Parents	<input type="checkbox"/>
Lodging Address	<input type="checkbox"/>


MAXI-Q

REGD.

"WE COULD BLIND YOU WITH SCIENCE"
on the technical superiority of our coils but
are sure you would prefer us just to say

"WE GUARANTEE THEM"!

Coverage from 3.8 to 2,000 metres in 7 ranges—
 Each coil is packed in an aluminium container
 which may be used as a screening can for the
 coil itself—Brass threaded adjustable iron
 cores—Colour coded moulded polystyrene
 formers—Chassis/Plug-in Technical Bulletin
 DTB.1 1/6—Dual Purpose Technical Bulletin,
 DTB.4 1/6—Colour Code Identified Coils:
 BLUE Signal Grid Coil with Aerial Coupling
 winding—YELLOW Signal Grid Coil with
 intervalve coupling winding—GREEN Grid Coil
 with reaction and coupling windings—RED
 Superhet Oscillator for I.F. of 465 Kc/s—WHITE
 Superhet Oscillator for 1.6 Mc/s. Prices range
 from 4/1 to 4/9 each. Five Colour Glass Scale,
 Back Plate, Pointer, Pulleys and Cord for use
 with 315pF tuning condensers. Coverage (1)
 150-400 Kc/s; (2) 530-1600 Kc/s; (3) 1.5-4 Mc/s;
 (4) 4-12 Mc/s; (5) 10-30 Mc/s; Price 15/-.

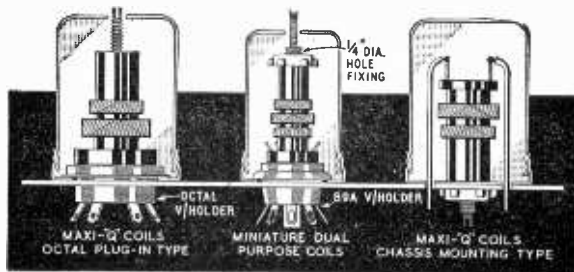

GENERAL CATALOGUE covering full range of components send 1/4d. in stamps or P.O. PLEASE SEND S.A.E. WITH ALL ENQUIRIES.

DENCO (CLACTON) LTD. (Dept. P.W.), 357/9 Old Road, Clacton-on-Sea, Essex

LASKY'S RADIO



LASKY'S CAR RADIO

12 v. operation, transistor output, medium and long wave. Can be built complete with loudspeaker for £12.10.0, post 3/6. Booklet 2/6 (refunded if you order).

BUILD THE COSSOR "TRAVELLER'S FRIEND"

4-transistor pocket s/het. Uses 9 v. PP4 battery, covers 190-550 metres, power o.p. 30 MW. All components including 2 1/2 in. Speaker, Case (6 x 3 1/2 x 1 1/2 in.) etc. £7.19.6, post 2/6.

LASKY'S 100-page COMPONENTS CATALOGUE, price 2/-, post 6d., Our latest 12-page Bargain Bulletin included free or available separately price 6d.


THE "VANCOUVER" 3 TRANSISTOR POCKET RADIO

Plus germanium diode on printed circuit, size 3 1/2 x 4 x 1/2, incorporating ferrite rod aerial. Tunable over medium and long waves. Extremely simple to build. KIT OF PARTS 39/6 Post 1/6

Circuit diagram 1/6 (supplied free with Kit).



LABGEAR AUDIO OUTPUT METER KIT

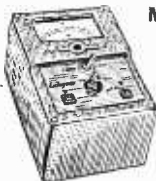

Two ranges: 25 milliwatts to 1 watt, 1 watt, to 10 watts. Accuracy 5% and matched for 3, 15 and 600 ohms. Ideal for constructors hi-fi enthusiasts, engineers.

Complete kit including full step-by-step instructions, circuit, data, etc. 59/6, post 1/6.

3-SPEED TRANSISTOR RECORD PLAYER

CAN BE BUILT FOR £9.19.6

Carr. 7/6.

6-volt operation. For all L.P. and standard records.



All components available separately

AMPLIFIER. 300 milliwatts push-pull output, using two OC71 and two OC72 transistors. Fully assembled 79/6, Knobs 3/6 extra.

LOUDSPEAKER. 30 ohms, 7 x 4 in. elliptical matched to Amplifier. 25/-.

3-SPEED TURNTABLE 6 volt, with rubber mat and speed adjustment, complete with t.o. crystal cartridge and two sapphire styli. 79/6.

CARRYING CASE as illustrated, handsome two-tone finish, size 17 in. deep, 14 in. wide, 5 1/2 in. high, well made and finished. 49/6.

Batteries extra.

207 EDGWARE ROAD, W.2 Near Praed Street PAD 3271/2
 Both addresses open all day Saturday.

42 TOTTENHAM COURT ROAD, W.1 MUS 2605
 All Mail Orders to Lasky's Radio Dept. PW, 207 Edgware Road, London W.2

Combined Receiver and Signal Generator

A NOVEL, FOUR-VALVE
CIRCUIT DESIGN

By J. Severn

(Continued from page 434
September issue)


THE coils used in this unit can easily be home constructed.

One coil is shown in Fig. 4, and all are similar, except for the number of turns. Four-pin plug-in coils can be used, with a holder to match. These are available in 6-ribbed type, and have a diameter of approximately 1½ in. over the ribs. There is some latitude in the size and type of formers, gauge of wire, and exact number of turns used, and changes need not reduce efficiency, as the coils do not have to gang with others.

Referring to Fig. 4, (1) is the top of the tuned winding, (2) is a tapping on this winding, and (3) is the earthed end of the tuned winding. Lead (4) is the beginning of the aerial coupling winding, which ends at lead (3). Approximately ¼ in. clear space is left between tuned windings and aerial coupling, on each coil. All the leads are taken directly down to the pins, and soldered at the tips. Each coil is made in the same way, so that any can be inserted in the holder.

Coil Winding Details

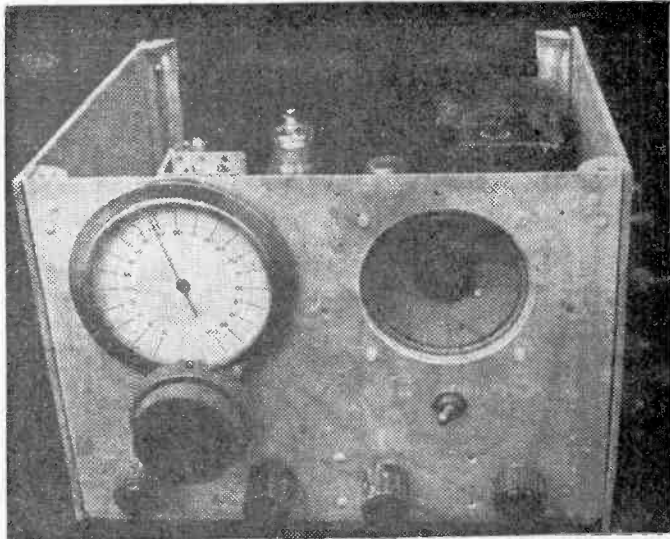The exact coverage, especially with the very small coils, will depend somewhat upon wiring. However, coils made as follows will usually be satisfactory. If necessary, turns may be added to



The completed unit.

any coil to increase the wavelength tunable, or removed to reduce the minimum wavelength.

Approximately 13-30m. 7 turns 20s.w.g. spaced about 6 turns/in., tap ¼ turn from (3). Coupling 4 turns 28s.w.g.

Approximately 30-60m. 16 turns 24s.w.g. spaced about 10 turns/in., tap ¼ turn from (3). Coupling, 8 turns 28s.w.g.

Approximately 60-100m. 30 turns 24s.w.g. side by side, tap 1 turn from (3). Coupling, 15 turns 30s.w.g.


Approximately 100-200m. 55 turns 24s.w.g. side by side, tap 1½ turns from (3). Coupling, 25 turns 32s.w.g.

If a 10m coil is required, this will need approximately 3½ turns of 18s.w.g., occupying about 1 in. winding space, with tap about ¼ turn from (3), and 2 turns of 28s.w.g. for coupling. To secure best results, as many turns as possible should be used, provided the 10m band can be covered. It may also be necessary to experiment with the position of the cathode tap.

Dust Cores

Coils for use above 200m can best be made by taking a miniature dust-cored coil, with aerial coupling, and adding two or three turns of fine wire, to obtain a tapping point. The junction between existing winding and additional turns will furnish the cathode tap, and the end of the additional turns will be point (3). The turns should be on top of the existing winding, or very near it, and in the same direction, so that they can be regarded as a continuation of the winding. As most such coils are wound with Litz it is very difficult to tap the actual winding itself. These coils will fit inside short wave plug-in formers. The actual bands covered may be adjusted initially, if necessary, by modifying the position of the core.

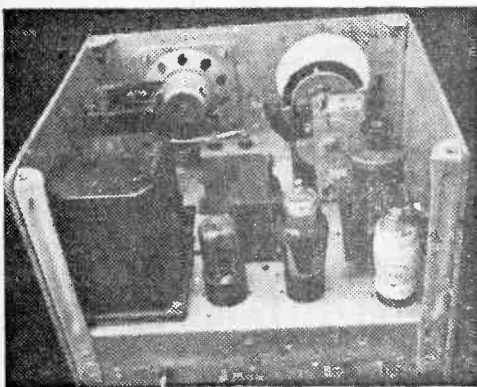An air-cored coil for wavelengths above 200m can be made by winding 100 turns of 32s.w.g. enamelled wire on a former like those used for



Rear view of the unit.

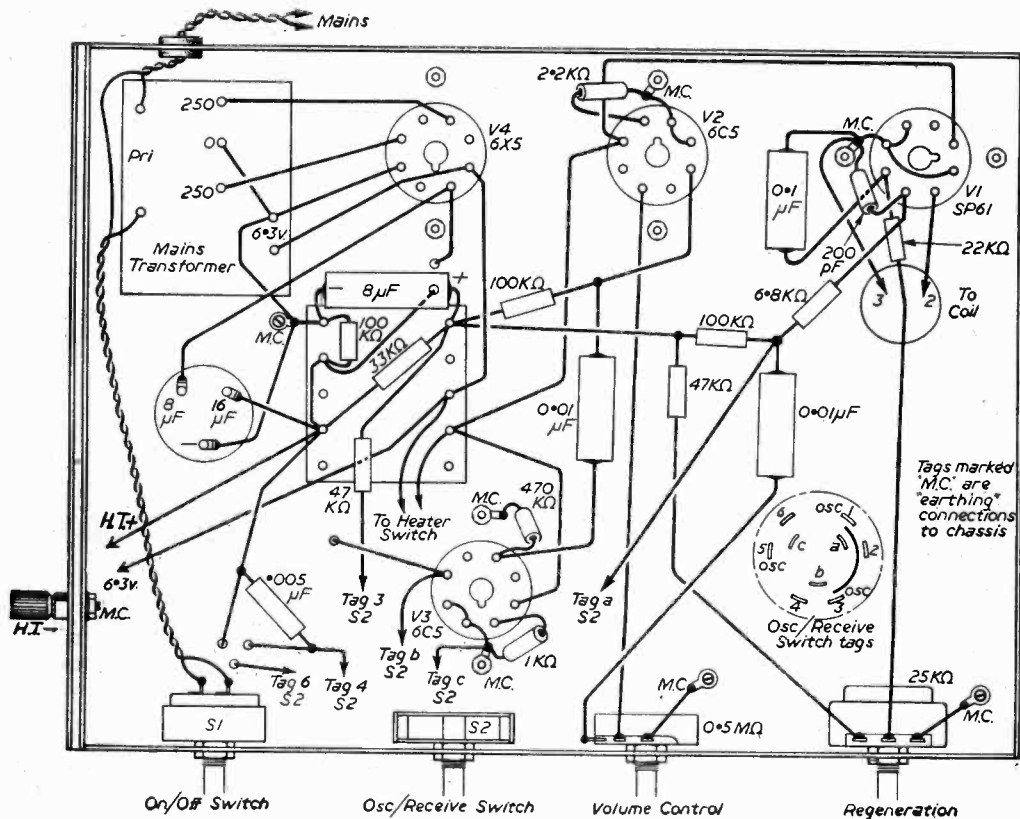


Fig. 3.—The wiring plan.

the S.W. coils, with tap $1\frac{1}{2}$ turns from (3), and 40 turns of 36s.w.g. for coupling. But for these wavebands dust-cored coils are recommended.

Aerial, Etc.

If other than a short wire is used for the aerial, a small pre-set or fixed condenser should be joined in series with it, at the aerial terminal shown in Fig. 2 (last month). A 100pF or 50pF pre-set is most suitable, as its capacity can be adjusted to suit the aerial.

For reception, put the oscillate/receive switch in the appropriate position, and ensure that the heater switch is closed. The regeneration control should give a smooth build up of sensitivity, until oscillation begins, with all coils. If not, the positions of the cathode taps may require modifying, to suit the SP61 actually in use. If oscillation is generally weak or absent, this valve may be in poor condition. Correct regeneration is essential for long range reception.

To test for oscillation, set the switch to oscillate, and loosely couple a receiver to the coil circuit. A test lead can be used, or a lead from the receiver aerial socket can be placed near the coil, or looped round the aerial terminal. Adjustment of the equipment as explained will then allow the modulated R.F. signal to be tuned in.

Calibration points should be drawn up for the

coils. This can be achieved by using the equipment as receiver and generator. Stations tuned in will give direct calibration points. If the switch is then set to oscillate, the generated signal will be heard on a receiver. Leaving the generator/receiver tuning untouched, the receiver

is tuned to lower wavelength, until the 2nd harmonic is heard on twice the frequency, or half the wavelength, of the original signal. Then receiver tuning is then left, and the generator tuning is adjusted until its fundamental is heard on the receiver. This gives a calibration point at twice the frequency (or half the wavelength) of the original station. By repeating this procedure, calibration points throughout the ranges of the coils can soon be found.


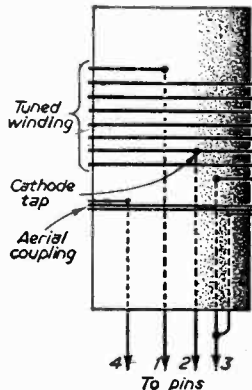


Fig. 4.—Details of the plug-in coils.

COSSOR 17" TELEVISIONS & RADIOS

PAY US A VISIT FOR SUPER SALE BARGAINS

at half original price ! ! ! ! !

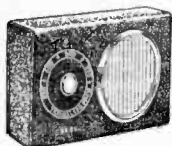

BUILD IT YOURSELF !
THE FAMOUS COSSOR
 (Traveller's Friend) Transistorised
£7.19.6 **POCKET RECEIVER**
 P. & P. 2/-
 In leatherette case

This set can be built for £7.19.6. Size 6 x 3½ x 1½ in. Weight 17 ozs. This set covers medium waveband 190/500 metres intermediate frequency. 470 kc/s using 4 transistors (Ediswan) and 2 diodes on a printed circuit board, plus a 2½ in. moving coil speaker. Instruction book with point to point wiring diagram, 2/6 each. Batteries, PP4 (Ever Ready) 2/- each.

COSSOR BATTERY PORTABLE SPECIAL



£6.19.6
 P. & P. 3/6

A printed circuit, 5in. speakers are features of this battery portable. An internal ferrite rod aerial for L and M Bands. A polythene wrapper provided to protect receiver. Width 10in., height 6½in., depth 5½in.


**MICROPHONES - LOUDSPEAKERS
 TRANSFORMERS - ALL COMPONENTS**

In fact we have the lot. Send for details and prices.

COSSOR BATTERY PORTABLE

£7.19.6 P. & P. 3/6

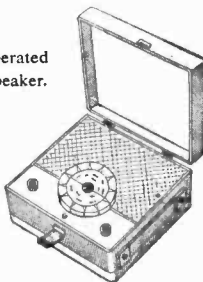This extremely sensitive battery operated set has a printed circuit and 5in. speaker. A frame aerial fitted in the lid gives high quality listening on L. and M Bands.




CARTRIDGES

- Collaro Studio O .. 18/-
- Collaro Studio P .. 18/-
- B.S.R. .. 18/-

6-TRANSISTOR RADIO KIT

£9.15.0

P. & P. 1/6

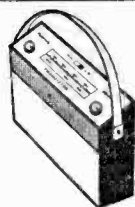

6 transistor-printed circuit, ferrite aerial, 5in. speaker, push-pull output, with 3 I.F. stages, and driver stage. Range MW 180-550 metres, LW 1,200-2,000 metres. Wooden case attractively covered in Blue and Grey washable vinyl.

CONVERT THAT TV TO ITV 37/6

with our **COSSOR TURRET TUNER ZB2** 2-valve cascade R.F. amp, using one 7AN7 valve. One freq. Changer 8A8. Output from converter - sound 10-1 mc/s, vision 13-6 mc/s. LIST PRICE 7 gns.
 Fitted with aerial panel, fine tuning control. Brand new in carton with full instructions and circuit. Suitable for use in sets made by: Coscor, Argosy, Baird, Decca, Murphy, Peto-Scott, Phillips, Philco, Regentone, R.G.D. and Stella. Both Birmingham and London channels available.



"SUPER-THREE"
 Transistor Pocket Radio

Printed circuit technique using 2 Surface Barrier type transistors, one A.F. Trans and one Diode. Ferrite aerial, fully tunable on LW and MW. Uses 2 U.16 1½ volt batteries. And easily assembled by the beginner. Kit of Parts Complete

39/6
 P. & P. 1/6

LABGEAR OUTPUT METER

£2.19.6 Complete Kit P. & P. 2/-

At last a Meter at the right price for the home constructor. An accurate Audio Power Output Meter. Two ranges 25mW to 1W and 1W to 10W. Accuracy 5% matched for 3, 15, 600 ohms with inst. and tech. data. New 3in. 0-1mA meter.



NOT GOVERNMENT SURPLUS

COSSOR RECORD PLAYER KIT

We can now supply the following parts to build this unit:
 (1) Player Case.
 (2) Garrard Motor B.A.I.
 (3) Knobs, Plugs, etc.
 Suitable for 7in. 45 r.p.m.s.

£3.9.6
 P. & P. 5/-

17in. TUBE BARGAIN

Type CME/1702 90° by Mazda. Not surplus. Heater (amps) 0-3, Heater (volts) 12-6 (Seconds).

SPECIAL PRICE
£3.19.6
 P. & P. 10/-

FERGUSON VHF/FM TUNER

This F.M. adaptor is completely self-contained and can be fitted to any A.C. mains radiogram or radio with P.U. sockets. Valves 2-EF80's, ECF80. Input 200-250v. A.C. range 80-98 Mc/s. Greatly Reduced

£13
 P. & P. 2/-

YOUR EXISTING RADIOGRAM OR RECORD PLAYER CHANGED TO STEREO BY OUR STEREO ADAPTOR

Tech. Data 2 valves EF80 and EL84. Switch control for Stereo and Mono. Dual volume and tone control. Output 3 ohms, suitable for use with Acos GC/71, GP/73 and Garrard GC/10. Complete with wiring diagram.

£2.19.6
 P. & P. 2/6

WIRECOMP ELECTRONICS

378 HARROW ROAD, LONDON, W.9. TEL.: CUNNINGHAM 9530


Hours of business: 9 a.m. to 6 p.m. Open all day Saturday. Opposite Paddington General Hospital. Buses 18B & 36 pass the door

HIGH QUALITY SPEAKERS with foam surrounds by **Wharfedale**

HERE ARE THREE FROM THE LARGE
RANGE OF MODELS IN PRODUCTION


8/145

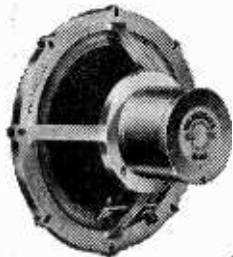Specially designed for use in acoustic columns. Low fundamental resonance, smooth response due to foam suspension and fitted with aluminium voice coil and centre dome for extended high frequency response. Powerful magnet system giving high sensitivity. Bass Resonance 45/55 c/s. Flux Density 14,500 gauss. Total Flux 60,000 maxwells. Price (inc. P.T.) 139/11.



SUPER 12/FS/AL

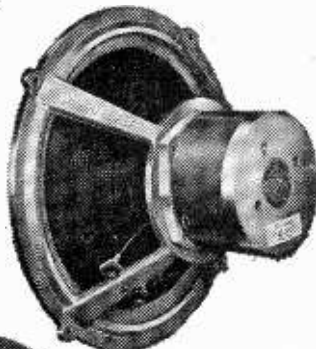Bass Resonance
30/38 c/s.
Flux Density
17,000 gauss.
Total Flux
190,000 maxwells.
Price 350/-




10 in. BRONZE/FSB

Bass Resonance 30/38 c/s.
Flux Density 10,500 gauss.
Total Flux 41,500 maxwells.
Price (inc. P.T.) 105/11.

FOAM SUSPENSION

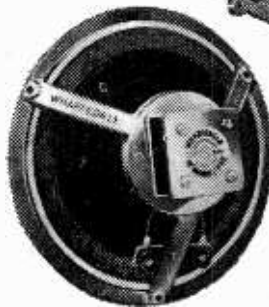is used on all the above units. Its resilience reduces the incidence of distortion at low frequencies, and the softness improves dissipation of middle and high frequency vibrations at the edge of the cone, resulting in all-round improvement in the smoothness of response.



Illustrated, descriptive leaflet and cabinet construction sheet
free on request

Wharfedale

WIRELESS WORKS LTD
IDLE BRADFORD YORKS.

Telegrams: 'Wharfedel', Idle, Bradford.
Telephone: Idle 1235/6

Electronics FLEET ST. Ltd

Dept. B

152/3 Fleet St., London, E.C.4. Tel. FLE 2833
Business Hours: Weekdays, 9-6. Saturdays, 9-1.

ASTOUNDING OFFER

AVANTIC BEAM-ECHO EQUIPMENT

DL7-35 POWER AMPLIFIER

Accepted as one of the finest amplifiers produced. Power output 54 watts peak. Distortion 0.05% d. at 20W sine wave output. Inter mod distortion 0.7% at 20W output. Freq. response 5 c/s to 30 kc/s, load impedance 4 ohm, 8 ohm, 16 ohm. Switch selected. Hum level—85DB at 20W output. Makers' price 30 gns.

OUR PRICE £16.19.6

P. & P. 12/6

SP21 STEREO PRE-AMP

Twin channel pre-amp, designed for DL7-35 amplifier, ideal for mono or stereo, stereo balance control, 6 inputs each channel. Tuner tape p/up. Freq. response 40 c/s to 15 kc/s ±10DB, bass and treble control, loudness control and numerous refinements. Makers' price £28.10.0.

OUR PRICE £16.19.6

or two DL7-35 amplifiers and one SP21 pre-amp for 47 gns.

SPA11 STEREO AMP

Twin amplifier and pre-amp. p/pull output, 10W peak each channel. distortion 1% total harmonics at 7 watts imp., 4, 8 and 16 ohms. Tape recorder o/p/ut 100 m/v, bass and treble controls. Makers' price 28 gns.

OUR PRICE 19 gns.

SPECIAL OFFER FOR STEREO ENTHUSIASTS

2 Avantic DL7-35 power amplifiers as above and the Avantic SP21 stereo pre-amp control unit as below, the 3 items

OUR PRICE NOW 47 gns.

Carriage and packing 30/-. The last of this wonderful offer.

LIMITED NUMBER



F.M. Tuner by the Ferguson Company. An attractive and compact unit in gold finish hammered metal case 10in. wide, 7 1/2in. deep, 2 1/2in. high. Neat escutcheon and tuning dial. Has own power supply. Uses two EF80, one ECF80.

2 Germanium diodes and metal rectifier. Coverage 87.6 m/cs. (continuously). Will feed into any amplifier or radio.

AT THE AMAZING PRICE OF
2/6 Post and Packing.

£13.19.6

BRAND NEW T.V. TUBES, CHEAPER THAN REBUILDS

All brand new in famous maker's cartons. (1) 17in. rectangular aluminumized 6.3 HRTS. 0.3A current; max. anode voltage 16 kV. Usual price £17/5/0. **OUR PRICE £7.19.6.** Crating and carr. 15/-. (2) 14in. rectangular Tube, 6.3 heaters; 0.3 amp. current; max. anode 14kV; ion trap; external conducting coating; B12A base. £7.9.6. Crating and carriage 12/6. (3) Ferranti T12/44 12in. magnetic white fluorescence; 4 v. heater; max. anode 10 kV. As used in many TV receivers. Original price £17.15.0. **OUR PRICE £2.19.6.** Crating and carr. 12/6. (4) Ferranti 9in. Tube, round white fluorescence, 4 v. heater, max. anode voltage 7 kV. **OUR PRICE £2.5.0.** Crating and carr. 11/6.



Inexpensive P.A. Equipment

COMPLETE CONSTRUCTIONAL INFORMATION

By V. E. Holley

(Continued from page 397, September issue)

As mentioned in the previous article a very satisfactory mike can be made cheaply from one of the crystal inserts available on the surplus market.

Procedure: Cut pieces of thin plywood to size 6in. x 3in., sufficient in number to make a stack 1in. high and, with a fretsaw, cut them to the shapes and sizes shown in Fig. 7 (given last month). Take the first piece of ply, cover the hole with a circular piece of thin perforated zinc $2\frac{1}{2}$ in. in diameter and place the second piece of ply on top. Stick the two together with resin glue and, when it is dry, add the third and subsequent layers of ply except the last. When all are glued together, the insert can be fitted into the case thus formed. The front outer rim should be bedded on to three or four small pieces of sponge rubber and the back of the insert should then be slightly below the level of the surrounding wood. Fit the switch and the coaxial socket in the positions shown and wire up with small diameter screened wire. It is important to ensure that the screening is as thorough and complete as possible. The switch should be of the sliding type and should be wired so that in the "off" position it short circuits the microphone, thus silencing the amplifier.

The mike can now be tested on the amplifier and if all is well, a piece of thin sponge rubber sheet should be laid on the back of the insert and the back of the case glued in position. It is unlikely that the case will ever need to be re-opened but if the constructor dislikes such finality, the back can be secured with small brass screws.

Finishing

First fit a circular piece of cardboard into the opening at the front of the mike to prevent the entry of foreign matter. Round off all the corners of the case and make everything smooth with glass-paper. Wood dye of any desired colour may now be rubbed in and the final finish can be produced by the application of clear varnish. Two or three coats will be required with a light rub down between each. The result is a robust and serviceable instrument of reasonable appearance which will withstand rough handling or accidental falls without damage.



The completed equipment in its case.

Cables

The microphone cable must be efficiently screened. The resistance is unimportant but there must not be too much capacity between the conductors or there will be a loss of the higher frequencies when long runs are used. Coaxial cable of 80Ω impedance is ideal though not quite so easy to handle as some of the more flexible kinds of screened cables.

Pre-Amplifier

As stated last month, no pre-amplification is necessary for many purposes. When it is, as for instance in concert work, it is usually obtained from the mixer and pre-amplifier unit incorporated in the record player to be described. There are occasions, however, when it is unnecessary or inconvenient to use the record player and a small battery powered pre-amplifier may be constructed. This is completely self-contained and arranged so that it can be connected on the "magic box" principle in any mike cable where it will give a gain of 40 times. It is particularly useful for such occasions as providing amplification for an after-dinner speaker, where it will usually be necessary to employ a long cable and to station the operator at the main amplifier. The speaker too, is liable to be at a greater distance from the microphone than usual, so that additional gain is essential. If the pre-amp is used within a few feet of the mike, it will boost the signal well above the level of any extraneous noises which may be picked up later on in the cable.

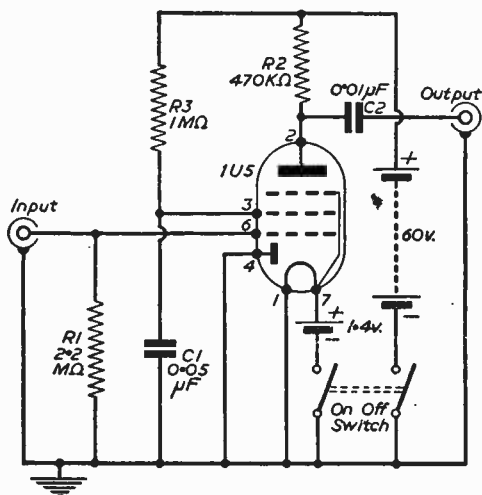


Fig. 8.—Circuit of the battery pre-amp.

Circuit

The very simple circuit is given in Fig. 8. The valve which is a 1U5 is very suitable for this purpose, having an internal structure specially designed to avoid microphony; the pre-amp can thus be handled or moved when in use without interference to the signal. The H.T. current drain is $160\mu\text{A}$ which is supplied by two 30V deaf-aid batteries in series. They have a useful life of about 60h before the voltage falls to 45, when they should be renewed. They have a very good life, too, especially if the pre-amp is kept in a dry place at room temperature when not in use. Filament current is supplied by a single cell; its working life is only 10 to 12h, but as replacement is quick, cheap and easy, it has not been thought worthwhile to accommodate anything larger.

Construction

The unit is constructed in a box made of 18s.w.g. aluminium to the measurements given in Fig. 9. No attempt has been made at miniaturisation and all components with the exception of the H.T. battery are standard. The shelf on which the valve is mounted is secured by two self-tapping screws through the sides of the case and all the wiring can be done before it is fitted. Input and output are indicated appropriately by flush and surface mounted coaxial sockets respectively. Note that the centre connection of the output socket is cut short. The heat of soldering to the remaining stub will soften the polythene and a plug should be inserted in the socket to prevent displacement. The switch may be any double pole component of suitable physical size. The valve should be packed on either side with pieces of sponge rubber so that it will not be dislodged if the amplifier is accidentally dropped or knocked. The H.T. battery compartment is formed from a piece of aluminium cut to the measurements given in Fig. 9 and riveted to the bottom of the case. It is best to place the batteries in position before locating the point of attachment so that a reasonably tight fit can be obtained to

prevent them from moving about in-use. The side of the compartment adjacent to the battery terminals should be wrapped with insulating tape before fitting. Fig. 10 shows the layout in detail.

When assembly is complete, the box should be placed face downwards on a sheet of 18s.w.g. aluminium and a lid marked out. This should be given a "turn-down" all round of $\frac{1}{8}$ in. and it can then be secured to the box with self-tapping screws. One at each side will be sufficient.

Battery Connections

To ensure noise-free operation, the connections to the H.T. batteries should be soldered. The filament cell will need more frequent replacement and it is convenient to have contact connections. For the positive, thin cardboard about 3in. x $1\frac{1}{2}$ in. should be folded double and a piece of thin brass or tinplate threaded through slits cut in one thickness as shown in Fig. 10. The two thicknesses can then be glued together to retain the brass strip firmly and the whole cemented into the amplifier

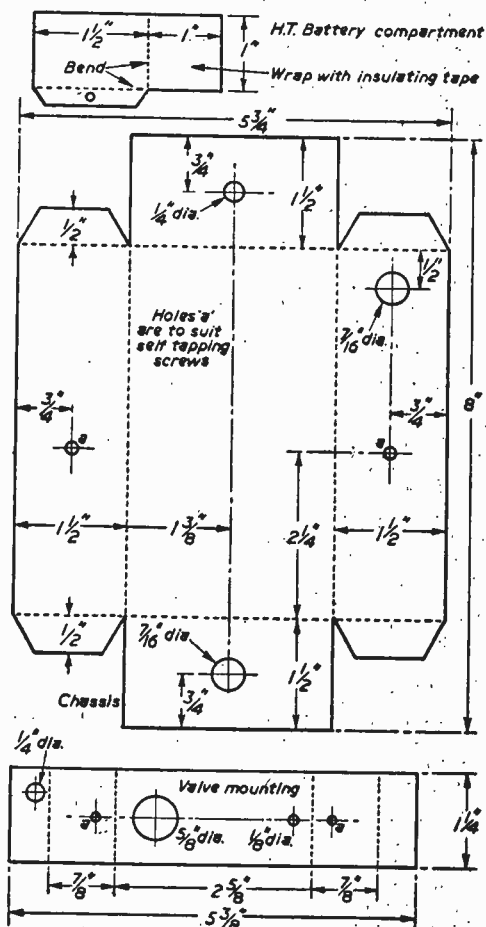


Fig. 9.—Details of the pre-amp housing.



A NEW-PRACTICAL WAY of UNDERSTANDING

Radio • Television • Electronics

Including: Transistors; VHF/FM; Hi-Fi equipment; Computers; Servo-mechs; Test Instruments; Photo-electrics; Nucleonics, etc.

FOR ... Your Career ... Your Own Business ... An Absorbing Hobby

Radiostructor—an organisation specialising in electronic training systems offers a new self-instructional method using specially designed equipment on a "do-it-yourself" basis.

You learn by building actual equipment with the big kits of components which we send you. You advance by simple steps, performing a whole series of interesting and instructive experiments—with no complicated mathematics! Instructional manuals employ the latest techniques for showing the full story of electronics in a practical and interesting way—in fact—you really have fun whilst learning! Post the coupon below, now, for full details.—

RADIOSTRUCTOR

LEADS THE WORLD IN ELECTRONICS TRAINING

POST NOW

To RADIOSTRUCTOR (Dept. G82)
READING, BERKS.

Please send brochure, without obligation, to:

★ Name _____

Address: _____

★ **BLOCK CAPITALS PLEASE**
(We do not employ representatives)

The least expensive way to high fidelity is an *Armstrong* chassis

JUBILEE Mk 2 (illustrated) 29 gns.


The new and improved version of the famous Jubilee chassis. V.H.F. with automatic frequency control, and medium and long bands. Separate tone controls. Tape record and playback inputs. The improved amplifier provides 8 watts push-pull output.

STEREO 44 27 gns.

A stereo and mono chassis providing 8 watts output and covering the full VHF and medium bands. Stereo and mono inputs for pick-ups, tape record and playback. Separate tone controls and dual volume control for ease of balancing.

AF 208 22 gns.

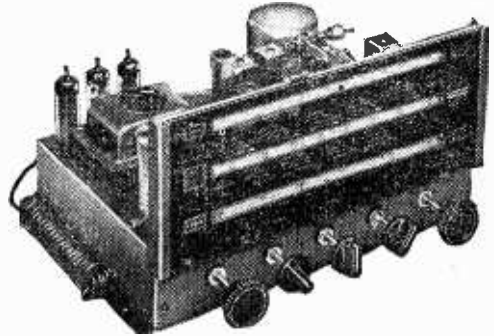An AM/FM chassis, of 5 watts output, covering the VHF and medium bands. Although an economically priced chassis this has the same superior finish and components as our more expensive models.



A large part of the cost of a radiogram relates to the cabinet (and purchase tax). Use an existing cabinet and replace the old unit with an Armstrong chassis or fit a chassis into a new cabinet or convenient bookshelves. In this way your expenditure goes wholly into the quality of reproduction.

The name **ARMSTRONG** is the registered trade mark of **ARMSTRONG WIRELESS & TELEVISION Co. Ltd.,** WARLTERS ROAD, LONDON N.7. Tel.: NOR 3213

Post this coupon or write for free catalogue or call at our Showroom for full demonstration and professional advice on your installation. Open 9—5.30 weekdays, 9—5 Sats.

NAME _____
ADDRESS _____
POC _____

SELENIUM RECTIFIERS

F. W. BRIDGE	H.T. Types H.W.
6/12 v. 1 a... 3/11	150 v. 40 m.a. .. 3/19
6/12 v. 2 a... 6/11	250 v. 60 m.a. .. 3/11
6/12 v. 3 a... 9/9	250 v. 80 m.a. .. 5/11
6/12 v. 4 a... 12/3	250 v. 80 m.a. .. 5/11
6/12 v. 6 a... 15/3	250 v. 250 m.a. .. 12/9
6/12 v. 10 a... 25/9	CONTACT COOLED
6/12 v. 15 a... 35/9	250 v. 30 m.a. H.W.
24 v. 2a. .. 14/9	6/11, 250 v. 75 m.a.
	F.W. (Bridge) 8/11

B.S.R. MONARDECK TAPEDECKS. Speed 3 1/2 in. per sec. High quality recording heads, 9 gns. Carr. 5/-
Suitable polished veneered walnut carrying case for above 39/6. (Space for amplifier.)

EX-GOVT. CASES. Size 14-10-8 1/2 in. high well ventilated, black crackle finished, undrilled cover. IDEAL FOR BATTERY CHARGER OR INSTRUMENT CASE. OR COVER COULD BE USED FOR AMPLIFIER. Only 9/6, plus 2/- postage.

HI-FI 10 WATT AMPLIFIERS. Slightly store soiled but guaranteed unused and in perfect order. Fitted Mullard valves. Dual inputs for "mike" and gram., etc. Bass and Treble Controls. High sensitivity and quality. For 6/6
200-250 v. A.C. Carriage 7/6. **25.19.9**

COLLARO STUDIO TAPF
Transcriptors, limited number **15gns.** Carr. 5/- 3 motors incorporated. Virtually no Wow or Rumble. Position for extra Record/Playback head for stereo. Accurate digital rev. counter. 3 speeds. Linear LT45—Tape Amplifier, suitable for above. Switched negative feedback equalisation for different speeds. Superb quality at up to 4.5 watts. For **12gns.**
200-230-250 v. A.C. mains. 12gns.

SIGNAL GENERATORS



Type C.T.53 by Wayne Kerr. Complete with charts. **SUITABLE FOR ALIGNING V.H.F. RADIO or TV RECEIVERS.** 3.9 to 300 megacycles. Output 1 micro-volt to 300 millivolts. Vernier Tuned, 6 Band Coil, Turret Potted "C" Core Transformers. Seven 6T6 Valves. Stabilised H.T. All voltage supplies including mains R.F. filtered. External mod. by sine wave from 50 c.p.s. to 10 Kcs. or pulses down to 1 μ sec. Worth approx. £100. Only 17 gns. Carr. 10/- or on H.P. terms

MICRO-AMMETERS. 2in. diam. 250-0-250 micro-amps. 15/9. 3in. diam. 0-50 micro-amps. 39/6. 3 1/2 in. diam. 0-500 micro-amps. 58/6

RELAYS. Carpenters' Type. Polarised. 2 times 9,500 turns at 1,685 ohms. 19/6. Miniature Moving Coil Differential Type. Single pole 2-way, or centre stable. Two coils each 350 ohms. Minimum operating current 140 micro-amps, nominal 400 micro-amps maximum 8 milli-amps. Two way contact current 100 mA at 50 v. A.C. or D.C. Size 1 1/2 x 1 1/2 in. approx., 19/6. Miniature Type G.E.C. 670 Sealed, wire ends, 4c/overs, platinum M1085, 18/9.

SPECIAL OFFER EX-GOVERNMENT SELENIUM RECTIFIERS. 24 v. 15 amp. with large square cooling fins. 29/11 each.

EX GOVT. SMOOTHING CHOKES. 200 mA., 3-5 H., 50 ohms. Parmeko 9/9; 100 mA., 5 H., 100 ohms 3/11; 150 mA., 10 H., 50 ohms 9/9; 80 mA., 20 H., 900 ohms 5/9; 120 mA., 12 H., 100 ohms 8/9; 50 mA., 50 H., 1,000 ohms 6/9; 100 mA., 10 H., 100 ohms 6/9; 60 mA. 5-10 H., 250 ohms 2/11.

EX GOVT. MAINS TRANSFORMERS
Primaries 200-250 v. 50 c.p.s. A.C.
250 v. 60 m.a. 6.3 v. 2 a. .. 10/11
270-0-275 v. 100 m.a. 6.3 v. 7 a. 5 v. 3 a. .. 21/9
300-0-300 v. 60 m.a. 6.3 v. 2 a. .. 11/9
300-0-300 v. 100 m.a. 6.3 v. 2 a. 5 v. 2 a. .. 18/9
350-0-350 v. 160 m.a. 6.3 v. 5 a. 5 v. 3 a. .. 27/9
0-10-20-25 v. 24 a. (Govt. rating) .. 79/6
Carriage 15/-.

2 VOLT ACCUMULATORS

Varleys small size 4 x 3 1/2 x 1 1/2 in., 2 v. 14 A.H., brand new. 6/9 ea., 3 for 15/6.

FIELD TELEPHONES



With bell. Require only small battery. Suitable for office, factory, warehouse, or outdoor intercommunication. 59/6 each.

R.S.C. BRADFORD MANCHESTER (LEEDS) LTD. and LEEDS

TERMS: C.W.O. or C.O.D. No C.O.D. under £1. Post 1/9 extra under 28. 2/9 extra under 85. Open 9 to 6. Weds. until 1 p.m. Trade supplied. S.A.E. with all enquiries. Mail Orders to 29-31 Moorfield Road, Leeds 12. Callers to 5 and 7 County (Mecca) Arcade, Briggate, Leeds 1. and 6-10 Brown Street (Market Street), Manchester 2. or 56 Morley Street (next to Majestic Ballroom), Bradford.

case as shown. For the negative connection, cut a piece of brass or tinfoil to the shape shown and slide it under the cardboard casing at the bottom of the cell, making a soldered connection to the exposed end. Withdrawal will be facilitated if the end has a turn-up of about $\frac{1}{8}$ in.

Operation

The pre-amplifier is quite capable of continuous operation and can be left switched on as long as the main amplifier is working. It can, of course, be switched on and off as required if it is desired to conserve the batteries, but if this is done the volume control on the main amplifier must first be turned down or the operation of the switch will produce loud noises.

The increased gain now available is more than can be used and opportunity can be taken to improve the quality of the results by applying maximum negative feedback. Even with this reduction of gain, however, care must be taken to avoid acoustic feedback or "howl". The microphone, the construction of which has been described, is markedly directional and provided it is kept a few feet behind the loud speakers and the latter do not face a large reflecting surface, trouble will not normally be encountered. It is advisable when

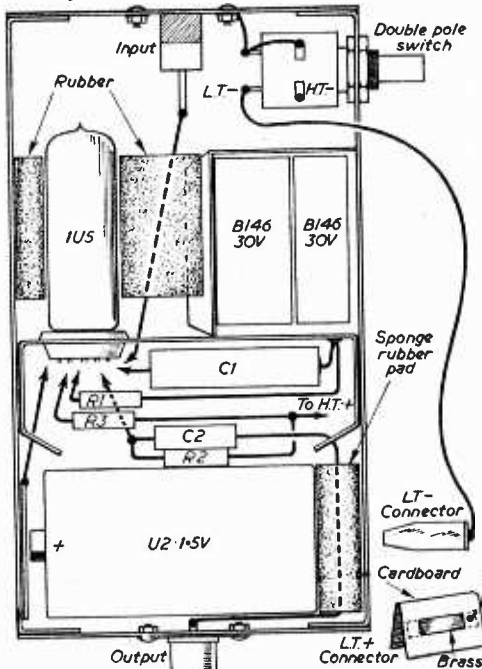


Fig. 10.—Layout of pre-amp.

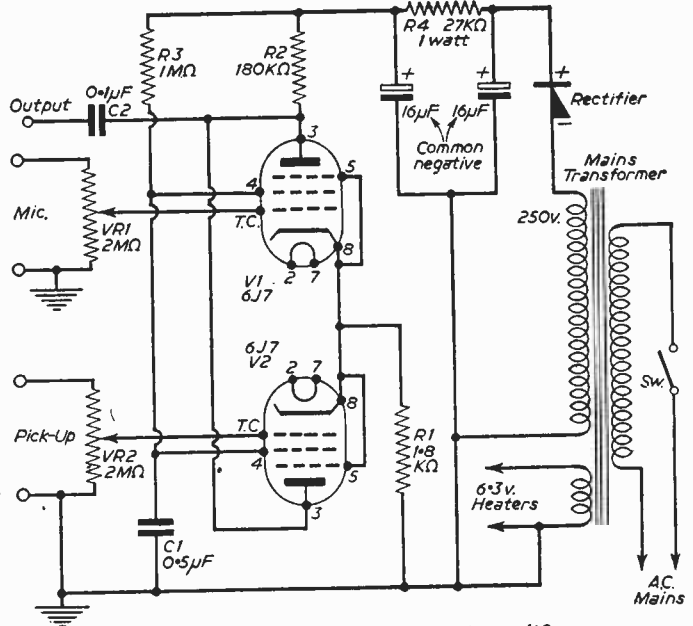


Fig. 11.—Circuit of the mixer and amplifier.

installing the equipment to test for acoustic feedback with the room or hall empty. If it is then satisfactory, it can safely be assumed that all will be well when the audience is present.

To provide music for dancing, etc., a record player must be added to the equipment and as speech facilities will be required concurrently with music, a mixer unit must be provided. For convenience of portability and to minimise the number of cables required, the mixer and pre-amp, with its own power supply, is fitted inside the player and provision is made also for the power supply to the main amplifier. The mixer and pre-amplifier will first be described.

Circuit

The circuit is given in Fig. 11. It will be seen that the two inputs are completely isolated and the setting of one control can have no effect upon the other. The two valves, which are of the metal type, work into a common anode load but as the anode resistance of the 6J7 is very high (about 3M) no isolating resistors are required between them. The gain of 120 times obtainable with this circuit is unnecessarily high and it is therefore reduced to half by omitting the usual cathode by-pass capacitor. This also improves the linearity of the stage.

Each of the 2M volume controls is fitted with a mains switch; that on the music control makes the supply to the motor so that at the end of a record, the volume can be turned down and the motor stopped. The other controls the power supply to the mixer unit and remains "on" all the time the equipment is in operation. This means of course that the resistance in the grid circuit of V1 cannot, in operation, be reduced to zero; but what remains is insignificant and no break-through of speech on music will be experienced.

(To be continued)

Club News

REPORTS OF CURRENT ACTIVITIES

MITCHAM AND DISTRICT RADIO SOCIETY

Hon. Sec.: M. Pharaoh, G3LCH, "The Cannons", Madeira Road, Mitcham.

This year it is hoped to run a multi-operator station for both the phone and CW sections of the CQ DX contest. The CW section will be used as an NFD Operator Trial. It is also hoped by this means to find First and Second Operator teams for next year's NFD. The station will probably be under the call of G3LCH although this is not yet definite.

The Club call sign, G3OCT, was put on the air at the Mitcham Horticultural Society's summer show on July 16th. Equipment was lent by G3LCH and G3OCA for the H.F.-band station. A 2m station was also run by G3LSP/A.

SLADE RADIO SOCIETY

Hon. Sec.: Charles N. Smart, The Church House, High Street, Edrington, Birmingham 23.

On August 12th the club paid an informal visit to the Birmingham office of Airmec Ltd. to view a selection of modern electronic instruments. An informal discussion was held on August 26th, the subjects discussed being the club station and direction finding contests.

Future Events:

September 9th—"Transistor Applications" by Mr. J. A. Chandler and Mr. Wates of Associated Electrical Industries (Rugby) Ltd.

September 23rd—A display of members' apparatus to be judged for the Enterprise Trophy and the Craftsman's Cup.

SOUTH YORKSHIRE AMATEUR RADIO SOCIETY

Hon. Sec.: W. Farrar, Highbury Avenue, Bessacarr, Doncaster.

Meetings are now held on the second and fourth Thursdays of each calendar month. On July 28th, Cliff Staff, G3KPW, gave a talk on "Single Sideband". Morse practice is radiated on Sunday 9.30 a.m., Wednesday 9.30 p.m. and Friday at 8.00 p.m., on or about 1980kc/s.

Future Events:

September 22nd—A formal meeting.

October 27th—Annual Dinner.

SPEN VALLEY AMATEUR RADIO SOCIETY

Hon. Sec.: N. Pridem, 100 Raikes Lane, Birstall, near Leeds.

With the opening of the 1960/61 session the club have acquired new headquarters at The Labour Rooms, Railway Street, Cleckheaton.

The annual general meeting was held on July 6th.

Future Events:

September 14th—Modern methods of Radio communication.

September 28th—An evening of Music.

October 11th—Mullard Film Show.

October 12th—Visit to Trinity Works.

October 26th—Two Metre Technique.

November 9th—A visit to the BBC Studios, Leeds.

November 23rd—Receivers for F.M.

December 7th—Film Show.

WEST MIDDLESEX TAPE RECORDING CLUB

Hon. Sec.: H. E. Saunders, 20 Nightingale Road, Hampton, Middlesex.

A sale of tape recording gear was held at St. George's Hall, Lancaster Road, Southall on July 28th when over £30 was raised for auxiliary gear. An outdoor meeting was held on August 21st when the club visited Whipsnade Zoo. It is proposed to hold a Club Dinner or Supper early in October in the locality instead of in Town.

WIRRAL AMATEUR RADIO SOCIETY

40 Hamilton Square, Birkenhead.

On July 15th the Junior Section held a meeting and at 7.45 p.m. G2AMV gave a lecture on his equipment "G2AMV/M and /P". A lecture on 2m was given on August 5th and on August 19th an outside lecturer was entertained at the club.

WORTHING AND DISTRICT AMATEUR RADIO CLUB

Hon. Sec.: P. J. Robinson, G3KHF/T, 46 Hillview Road, Worthing, Sussex.

The club meets regularly on the second Monday of each month at 8 p.m. at the Adult Education Centre, Union Place, Worthing.

Future Events:

September 12th—Annual General Meeting.

COURSES OF INSTRUCTION, ETC.

BRADFORD TECHNICAL COLLEGE

Central Hall, Bradford 5.

A course of lectures in preparation for the City and Guilds or London Institute's Radio Amateurs' Examination will be held

during the forthcoming session on Wednesday evenings from 7 to 9 p.m. The lecturer will be D. M. Pratt, G3KEP. Further information and details of registration may be obtained from the General Office at the above address.

GRAFTON RADIO SOCIETY

Hon. Sec.: A. W. H. Wennell, Montem School, Hornsey Road, Holloway, N.7.

The club have again made arrangements with the L.C.C. Evening Institutes at Holloway for courses for the Radio Amateur's Examination and Morse for beginners to be held at the above school. Classes will be held on Mondays with repeat lectures on Tuesdays and Wednesdays. The course will commence on September 26th from 7 to 9 p.m. Enrolment will be on each evening of the week September 19th to 23rd between 7.30 and 9 p.m.

MANCHESTER EDUCATION COMMITTEE

Openshaw Technical College, Whitworth Street, Openshaw.

Classes for the R.A.E. examinations, written and Morse, have been arranged for first year and second year candidates, the latter being for those pupils who have passed part or all of the R.A.E. requirements. During this class constructional work may be carried out and the equipment tested, checked and calibrated under the college call sign.

RADIO SOCIETY OF GREAT BRITAIN

East London Branch.

28 Morgan Crescent, Theydon Bois, near Epping, Essex.

The following classes have been arranged for the coming session. Radio Amateur's Examination Course: Wednesday 7.15 to 9.15 p.m. This is an 8-month course for those intending to take the examination. Morse and Codes of Practice: Monday 7.30 to 9.30 p.m. This is a 6-month course for those who wish to learn Morse up to G.P.O. requirements for an amateur licence. These classes will be held at The Ilford Literary Institute, High School for Girls, Cranbrook Road, Ilford, Essex. The fees are 30s. for the R.A.E. course, 20s. for Morse and Codes of Practice and 35s. for both courses. Enrolments will be held from September 5th to 8th between 7 and 8.30 p.m. All correspondence should be addressed to Mr. C. H. L. Edwards at the above address.

An invitation is extended by this branch of the society for those interested to attend a lecture to be given by Capt. P. P. Eckersley entitled "Radio from the Beginning". This lecture will be held at the Town Hall, Ilford on Sunday, October 9th at 3 p.m.

READING AMATEUR RADIO CLUB

Hon. Sec.: G3EJA, "Peacehaven", 9 Holybrook Road, Reading.

The club has arranged with the local technical college to hold a course of lectures on amateur radio for the City and Guilds Examination. The lectures will be held at the E. P. Collier Evening Institute, Swansea Road, Reading on Wednesday evenings from 7 p.m. to 9 p.m. commencing the week beginning September 26th. Fees for the course will be, for those under 18 years of age, 10s., 18 to 21 years, 20s., and over 21 years, 35s.

WEMBLEY EVENING INSTITUTE

Copland School, High Road, Wembley.

Classes will be held on Mondays, Morse Practice from 7 p.m. to 8 p.m. and Radio Theory from 8 p.m. to 9 p.m. Enrolment will be held from September 12th to September 15th between 7.15 and 9.15 p.m. and classes will commence the following week.

JOIN THE PRACTICAL GROUP

PRACTICAL TELEVISION 1/6

Every Month

PRACTICAL MECHANICS 1/3

Every Month.

Devoted to Mechanics, Science and Invention.

PRACTICAL MOTORIST 1/6

Every Month.

PRACTICAL HOUSEHOLDER 1/3

Every Month

C.R.T. ISOLATION TRANSFORMERS

TYPE A. OPTICAL 85% and 50% BOOST. 2 V. OR 4 V. OR 6.3 V. OR 10.8 V. OR 18.3 V. MAINS INPUT. 12/6

TYPE A/2. HIGH QUALITY LOW CAPACITY 10/15 pF. OPTIONAL BOOST 35%. 50%. 75% MAINS INPUT. 16/6

TYPE B. MAINS INPUT. MULTI OUTPUT 2, 4, 6.3, 7.8, 10 and 13 VOLTS. BOOST 25% AND 50%. LOW CAPACITY. 21/-

TRIMMERS. Ceramic. 50, 50, 70 pF. Bd. 100 pF. 150 pF. 1/2; 250 pF., 1/6; 500 pF., 750 pF., 1/8. RESISTORS. Preferred values. 10 ohms to 10 meg. 1/4 w., 4d.; 1/2 w., 4d.; 1 w., 6d.; 1 1/2 w., 8d.; 2 w., 1l.-10g. HIGH STABILITY. 1/2 w., 1%; 2 w., 1%. Preferred values. 100 ohm to 10 meg. Ditto, 5%, 100 ohm to 5 meg., 8d.

5 watt - 1/3 WIRE-WOUND RESISTORS - 1/3 10 watt - 2/3 25 ohms-10,000 ohms - 1/6 15 watt - 2/6

PLASTIC RECORDING TAPE

Table with columns: Long Play 7in. reel, 1,200ft, Spare; 5in. reel, 1,200ft, Plastic; 5in. reel, 850ft, Reels; 3in. reel, 225ft, 7/6 3/- ea.

"Instant" Bulk Tape Eraser and Head Sander. 200/250 v. A.C., 27/6. Leaflet S.A.E.

O.P. TRANSFORMERS. Heavy Duty 50 mA. 4/6. Multitap push-pull, 7/6. Miniature, 384, 4/6. Push-Pull 10 w. 15/6. 20 w. 6K or 8K, 30/-.

MAIN TRANSFORMERS. 200/250 v. A.C. STANDARD. 200-0-250, 80 mA., 6.3 v. 3.5 a. tapped 4v. Rectifier 6.3 v. 1 a. 5 v. 2 a. or 4 v. 2 a. ditto, 350-0-350 ... 22/6

ALADDIN FORMERS and core, 1in. 8d.; 1in. 10d. 0.5in. FORMERS 987/8 and Cam T21/2. 1in. sq. x 3in. and 1in. sq. x 1 1/2in. 2/- ea., with cores. GOLD Midget Iron, 200/10v. or 200/40v. 25w. 24/-

"REGENT" 4 VALVE "96" RANGE VALVES



RANGE VALVES KIT PRICE £6. 6. 0. Carr. 4/-

PRINTED CIRCUIT BATTERY PORTABLE KIT

Medium and long wave. Powerful output. 6in. high Flux Speaker. T.C.C. Printed circuit and condensers. Components of finest quality clearly identified with assembly instructions.



1960 RADIOGRAM CHASSIS

THREE WAVEBANDS FIVE VALVES LATEST MULLARD S.W. 200 m.—550 m. ECH81, EF89, EBC81, L.W. 800 m.—2,000 m. EL84, E280. 12-month guarantee.

A.C. 200/250 v. 4-way switch; Short-Medium-Long-Gram. A.V.C. and Negative feedback 5 watts. Chassis 1 1/2 x 5 1/2 x 2 1/2in. Glass dial, horizontal or vertical wording, size 10in. x 4 1/2in. Aligned and calibrated. Isolated chassis. £9.10.0 Carr. & Ins. 4/6.

TERMS: Dep. £5.5.0 and five monthly of £1. MATCHED SPEAKERS FOR ABOVE CHASSIS. 5in. 17/6; 10in., 25/4; 12in., 30/4.

COLLARO CONQUEST HIGH-FIDELITY AUTOCHANGER 4-SPEEDS-10 RECORDS

Studio Pick-up OUR PRICE 7.19.6 post free Or with cabinet, speaker, and amplifier £11.19.6 Carr. 5/6

BSR MONARCH UM The Famous Autochanger. 4 speeds. £65.10 post free

ALUMINIUM CHASSIS. 18 s.w.g. un drilled. With 7 sides, riveted corners and lattice fixing holes. 2in. sides, 7 x 4in., 4/6; 9 x 7in., 5/6; 11 x 7in., 8/6; 13 x 9in., 8/6; 14 x 11in., 10/6; 15 x 14in., 12/6; 18 x 16 x 3in., 16/6.

HI-GAIN BAND 3 I.T.A. PRE-AMP KIT. Cascade circuit with valve ECC84. Price 29/6 With Power Pack. 49/6. Plans only 6d. Band 1 BRC version same prices.

GARRARD RECORD PLAYERS AUDIO PERFECTION

Designed to play 18, 33, 45, 78 r.p.m. Records 7in., 10in., 12in. Lightweight Xtal pick-up. GCS plug-in head. Stereo Wired. Single Play TA Mk II 8-8. Transcription 4 Hf £18. Auto Changer R.C. 210 £10-10-0. (Stereo heads £2 extra). Leaflets, S.A.E.

Volume Controls 80 ohm CABLE COAX

Long spindles. Guaranteed year. Midget 5K ohms to 2 Meg. No. Sw. D.P.Sw. 3/- 4/6 Linear or Log Tracks. Postage 1d. per yard Stranded open 3in. Losses cut 50% Fringe Quality 1/-yd Air Spaced.

COAX PLUGS ... 1/- LEAD SOCKET ... 2/- PANEL SOCKETS 1/- OUTLET BOXES ... 4/6 BALANCED TWIN FEEDER ... 6d. 80 or 300 ohms. DITTO SCREENED per yd ... 3/6. WIRE-WOUND POTS ... 3 WATT. Pre-set. Min. TV Type. All values 25 ohms to 25 K., 3/- ea. 30 K., 50 K., 4/-. Carbon 30 K., to 2 meg., 8/-. WIRE-WOUND 4 WATT Pots. Long Spindle. Values. 100 ohms to 50 K., 6/6; 100 K., 7/6.

I.F. TRANSFORMERS 7/6 pair.

465 Kcs. Slug Tuning Miniature Can. 2 1/2in. x 1 1/2in. x 1 1/2in. High Q and good bandwidth. By Pye Radio. Data sheet supplied. Write M800 I.F. 465 Kcs. 12/6 per pair. Westmouth St. I.F. 465 Kcs. 12/6 per pair.

NEW ELECTROLITIC. FAMOUS MAKES

Table with columns: TUBULAR, TUBULAR, CAN TYPES. Rows include 1/250v., 2/50/800v., 3/16500v., 4/450v., 5/250/12v., 6/100/270v., 7/850v., 8/8+8/450v., 9/2,500/3v., 10/16/50v., 11/8+8/800v., 12/32+32/250v., 13/32/450v., 14/8+16/450v., 15/64+120/275v., 16/50/25v., 17/16+16/800v., 18/64+120/375v., 19/50/50v., 20/32+34/250v., 21/100+200/275v. 12/6

SELENIUM RECTIFIER. 300 v. 85 mA. 7/6. CONTACT COOLED. 250 v. 50 mA. 7/6; 60 mA. 8/6; 85 mA. 9/6; 200 mA. 21/-; 300 mA. 27/6.

COILS Wreath "P" type. 3/- 4/- 5/- 999/- 1000/-

JASON F.M. TUNER COIL SET, 26/- H.F. coil, aerial coil, Oscillator coil, two I.F. trans. 10.7 Mc/s. Ratio Detector and heater choke. Circuit book using four 6AM6, 2/6. COMPLETE JASON F.M. KIT FMT1 25.5.0. Set of 4 Valves, £1.0.0. Details S.A.E.

FULL WAVE BRIDGE SELENIUM RECTIFIERS

2, 6 or 12 v. 14 amp., 8/9; 2 a., 11/3; 4 a., 17/6. CHARGER TRANSFORMERS. Tapped input 200, 250 v. for charging at 2, 6 or 12 v., 14 amps. 15/6. 2 amps., 17/6; 4 amps., 22/6. 200 v. input. Includes 200 v. TV TUBE equivalent books, 9/6. TOGGLE SWITCHES. S.P. 2/-, D.P. 3/6. D.P.D.T. 4/6. WAVECHARGE SWITCHES 5 p.u.-wave 2 water long spindle ... 8/6 2 p.u.-wave, or 3 p.u.-wave short spindle ... 2/6 2 p.u.-wave 4 p.u.-wave, 4 p.u.-wave long spindle ... 8/6 3 p.u.-wave, or 1 p.u.-wave long spindle ... 8/6 VALVEHOLDERS. Pax. Int. Oct. 4d. EF50, EA50 6d. B12A, CRT, I.T.S. Eng. and Amer. 4, 5, 6, and 7/6. B5A, B8G, B9A, 9d. BTG with can., 1/6. B9A with can., 1/8. CERAMIC EF50, B7G, B9A Int. Oct., 1/-. B/Cans. BTG, B9A 1/6.

CRYSTAL MIKE INSERT by Acco, precision engineered. Size only 1/2in. x 3/16in. 6/6.

RADIO COMPONENT SPECIALISTS OUR ONLY ADDRESS 337 WHITEHORSE RD., WEST CROYDON

Postal service 1/-, over £2 free. (Export Extra). C.O.D. 1/6 (Wed. 1 p.m.) THO 1665. Buses 133 or 68


GOOD COMPANIONS

MINIATURE TRANSISTORIZED SIGNAL GENERATOR TYPE 40

- ★ Up to 20 Mc/s on fundamentals.
- ★ R.F. and Audio Output, Attenuated.
- ★ Accuracy better than 2%.
- ★ Miniature size only 4½ in. x 3½ in.

PRICE NET **£5.15.0.** Battery 2/6 extra

Post (C.O.D. or C.W.O.), 2/6.

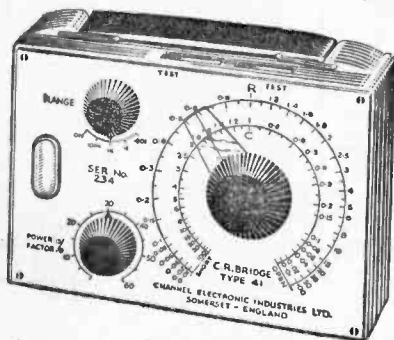

MINIATURE TRANSISTORIZED R.C. BRIDGE TYPE 41

- ★ Capacitance 5 μF to 20 μF.
- ★ Resistance 5Ω to 20 MΩ.
- ★ Magic Eye Balance Indicator.
- ★ Calibrated Power Factor Check.
- ★ Miniature Size—Light Weight.

PRICE NET **£5.10.0.** Battery 3/3 extra

Post (C.O.D. or C.W.O.), 2/6.

TRADE ENQUIRIES INVITED

SEND S.A.E. FOR LEAFLETS, OR ORDER TODAY, FROM—

CHANNEL ELECTRONIC INDUSTRIES LTD. DEPT. P., DUNSTAN RD. BURNHAM-ON-SEA, SOM.

Precision

miniature soldering iron

For mains or low voltage

6, 12, 24, 28, 50, 110, 200, 220, 240v.

- Fingertip control for transistors, printed circuits.
- 5 interchangeable bits slide on and off easily.

Ask for leaflet.


MODEL C.240 (230/240 volts)

29/6

A·N·T·E·X

7-B IDOL LANE LONDON EC3

Tel: MANsion House 2716

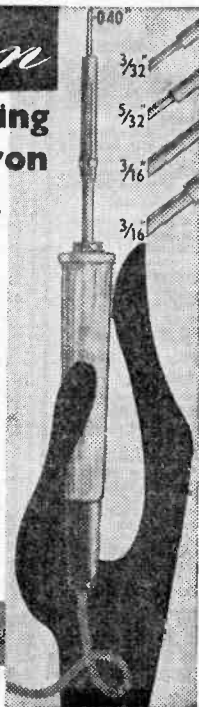

SOUTHERN RADIO'S WIRELESS BARGAINS

ATTACHMENTS for "18" Transreceivers. ALL BRAND NEW HEADPHONES, 15/6; HAND MICROPHONE, 12/6; AERIALS, 5/-; SET OF 6 VALVES, 30/-.

CONDENSERS. 100 Assorted. Mica Tubular, etc., NEW, 15/-.

CONTACTOR TIME SWITCHES. 2 impulses per sec. in case 11/6

REMOTE CONTACTOR. For use with above 7/6

LUBFRA HOLE CUTTERS. Adjustable ½" to ¾". For Metal, Plastic, etc. 7/6

MAGNETS. Strong Bar Type. 2" x ¼". 1/6 each.

MORSE TAPPERS. Midget Type, 2/9. Standard, 3/6. Heavy Type on Base, 5/6. ALL BRAND NEW.

PACKARD-BELL AMPLIFIERS. Complete BRAND NEW with Valves, Relay, etc., etc., 17/6 each.

QUARTZ CRYSTALS. Types F.T.241 and F.T.243, 2-pin, ¼ Spacing. Frequencies between 5,675 Kc/s. and 8,650 Kc/s. (F.T.243) 20 Mc/s. and 38.8 Mc/s. (F.T.241), 54th Harmonic, 4/- each. ALL BRAND NEW. TWELVE ASSORTED CRYSTALS, 45/-.

QUARTZ CRYSTAL CASES (F.T.241/243) 10/6 per dozen. RECORDING BLANKS. New "Emidisc", ready for use, 13/6/- each. Or 15 complete in metal case 4/-.

RESISTANCES. 100 Assorted useful values. New wire end, 12/6.

SPECIAL OFFER. 12 ASSORTED METERS. Slightly damaged. Mainly broken cases (perfect movements). Including 3 Brand New Aircraft Instruments, 12 for 45/-.

STAR IDENTIFIERS. Type 1 A-N Covers both Hemispheres, 5/6.

TRANSPARENT MAP CASES. Plastic. 14" x 10½". Ideal for Maps, Display, etc. 5/6


TRANSRECEIVERS. Type "38" complete with 5 valves, etc. New condition, untested by us, but serviceable, no guarantee, 22/6 each.

ATTACHMENTS for Type "38" Transreceivers. ALL BRAND NEW. PHONES, 15/6; THROAT MICROPHONES, 4/6; JUNCTION BOXES, 2/6; AERIALS, No. 1, 2/6; No. 2, 5/-; WEBBING, 4/-; HAVERSACKS, 5/-; VALVES, A.R.P.12, 4/6; A.T.P.4, 3/6. Set of FIVE VALVES, 19/- the set.

POST OR CARRIAGE EXTRA. FULL LIST OF RADIO BOOKS, ETC., 3d.

SOUTHERN RADIO SUPPLY LTD.

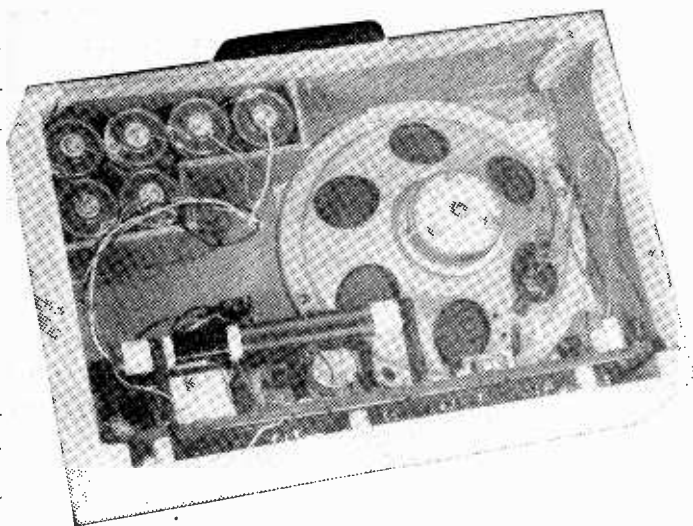11 LITTLE NEWPORT ST., LONDON W.C.2. GER. 6653



Four Transistor T.R.F. Receiver

MODIFICATIONS TO GIVE INCREASED R.F. GAIN

By D. Saull

(This receiver was described in our June Issue)

THE "Four Transistor T.R.F." receiver, a simple circuit for the beginner, described in the June issue, although possessing the quality of good selectivity and adequate volume in areas of average signal strength, may, in areas of poor signal strength not give sufficient audio output for comfortable listening.

Less Selectivity

Increased R.F. gain, at the expense of selectivity, and therefore greater audio output may be achieved by the modifications suggested in this article. As the tuning when using the original circuitry is sharp, it is felt that a little less selectivity for an increase in audio output might be an advantage in some reception areas.

Referring to the equivalent circuit in Fig. 1, R represents the input resistance of the first A.F. transistor reflected into the primary winding of the detector transformer. For good selectivity the tuned circuit must have a high value of Q, that is to say, the ratio of the reactive power to the real power must be large.

$$Q = \frac{\text{Reactive power}}{\text{Power dissipated}} = \frac{E^2/2\pi fL}{E^2/R} = \frac{2\pi fL}{R}$$

Therefore $2\pi fL$ should be large compared with R.

The forward resistance of the detecting diode is low and may, in this consideration, be ignored. The number of turns on the primary winding of the detector coil is 103 and the number on the secondary winding is 20. The turns ratio of this R.F. transformer is therefore $103/20 = 5:1$ (approximately).

Reflected Resistance

The resistance value reflected into the primary from the secondary circuit is in consequence multiplied by 5^2 , i.e. 25 times, and so the low resistance input to the first A.F. transistor is thus multiplied 25 times before it effectively appears connected across the second tuned circuit of the receiver. It does not damp the tuned circuit, keeping the Q high and the selectivity good.

Unfortunately, the 5:1 ratio of the R.F. transformer reduces the signal voltage appearing across

the tuned circuit by a factor of 5 in the secondary winding.

A compromise must thus be found between the signal level appearing across the secondary of the detector or R.F. transformer and the Q of the circuit. Putting this another way, a compromise between signal magnitude and selectivity is required.

Coils

Having understood our problem, the ultimate solution may simply be found by trial and error method with the following suggested circuit modifications, which call for rewinding the detector coil shown in Fig. 5 on page 146 of the June issue.

Rewind the coil with 103 turns as before but bring out a tap at the end of the second layer (50 turns) and also at the end of the third layer (75 turns). The taps may be brought out by twisting a loop in the wire and continuing winding. The circuit should now be modified to that shown in Fig. 2.

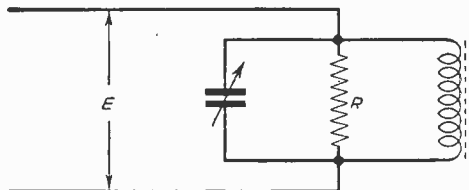


Fig. 1.—Equivalent of the input circuit.

The original secondary winding is now not required, and tap (a), (b) or (c) of the new coil may be used to obtain the best results. This arrangement gives the following turns ratios and the multiples of resistance appearing across the tuned circuit owing to the transistor input resistance, for respective taps:—

- Tap (a) 1:1 ratio—Transistor input resistance multiplied by 1.
- Tap (b) 1.4:1 ratio—Transistor input resistance multiplied by 2.
- Tap (c) 2:1 ratio—Transistor input resistance multiplied by 4.

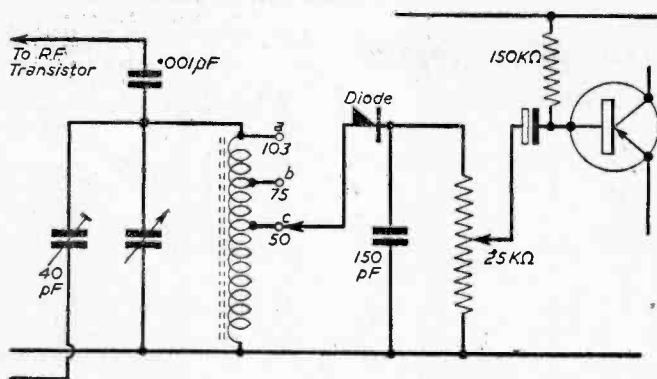


Fig. 2.—The modified input circuit.

Some readers have complained that, upon completing the construction of the receiver and switching on, only a loud hissing noise is heard at various positions of the tuning capacitor. This is caused by the reaction (40pF) capacitor being turned too fully inwards. It should first be set fully out and slowly screwed in until the signal is the loudest.

Capacitors

It is worth mentioning that "surplus" electrolytic capacitors may sometimes have a low capacity value, resulting in loss of volume. It is advisable to keep a spare capacitor, known to be in good condition, to use to check a suspected component. This may be done by holding, or clipping, the good capacitor across the suspected one. This particularly applies to the emitter and base bypass capacitors.

For the reader who is not too happy on the subject of reflected impedances and impedance matching in connection with transformers, the following explanation is offered.

The power into the primary and the power out of the secondary of a transformer must be equal (except for small losses). Considering the transformer in Fig. 3 with a turns ratio of N —i.e., N times more turns on one winding than on the other winding—and a resistance of $R\Omega$ with E volts across it in the smaller winding, looking into the

larger winding, there will be $(E \times N)$ volts across it and some effective impedance Z .

Now power = E^2/R watts, so the power in the smaller winding will be E^2/R watts and the power in the larger winding will be $(E \times N)^2/Z = E^2 \times N^2/Z$ watts. We have already said that both windings must carry the same power, therefore $E^2 N^2/Z = E^2/R$ (dividing both sides by E^2)

$$N^2/Z = 1/R \text{ (cross multiplying)}$$

$$Z = N^2 R$$

Or taking some practical figures for an example, let $N = 2$, $R = 100\Omega$ and $E = 10V$.

$$\text{Power in small winding} = E^2/R = 100/100 = 1W.$$

$$\text{Power in large winding} = (EN)^2/Z = (10 \times 2)^2/Z = 400/Z \text{ watts.}$$

The power in both windings must be equal, therefore

$$400/Z \text{ watts} = 1 \text{ watt}$$

$$\text{and, } Z = 400\Omega$$

or straight from our derived formula

$$Z = N^2 R = 2 \times 2 \times 100 = 400\Omega$$

Thus by using a 2:1 ratio transformer, with 100Ω resistance in the secondary winding, from the primary it looks like 400Ω —the square of the turns ratio of the transformer. This property has an important practical use when we require to connect the impedance in one circuit to a different impedance in another circuit.

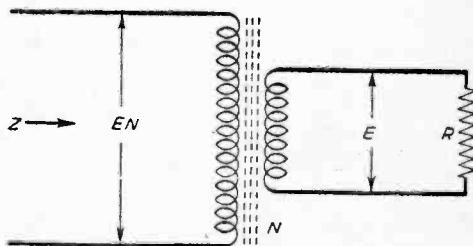


Fig. 3.—Simple transformer circuit.

SIMPLE COMMUNICATIONS SYSTEM

(Continued from page 526)

former via 2b, 1b, and 1/2c in the normal Listen position and to the input transformer via 2b when the key is pressed, S3 is connected to the output transformer via 1a and the "Call" circuit unearthed and completed by 1c.

Key 2

This enables the operator to communicate with Station 2. Like key 1 it is non-latching and in the Listen position completes the connection of LS1 to the output transformer. When the key is pressed LS1 is connected to the input transformer via 2b, S4 is connected to the output transformer via 2a,

and the "Call" circuit is unearthed and completed by 2c.

Points Worthy of Note

It may be necessary to have a capacitor across R4 to produce the right "Call" note. The value of this capacitor will best be found by trial and error in conjunction with R6 and C6.

Care should be taken to isolate the output transformer connections from all input circuitry, H.T. and anode connections to the primary may need to be screened and, for stability, the connections may be better one way round than the other.

Note.—Connecting cables CS1 to CS1' and CS2 to CS2' should be of the screened variety. All other inter-unit connections may be unscreened.

HOME RADIO OF MITCHAM

(Dept. P), 187 LONDON ROAD, MITCHAM, SURREY. MIT 3282

Shop Hours: 9 a.m.—6.30 p.m. Wednesday 9 a.m.—1 p.m.

Communications Equipment
We are stockists for the full range of EDDYSTONE short wave components and communications receivers, also KW Electronics transmitters and converters. Shipping arranged to any part of the world. Our detailed radio component catalogue is available. Price 2/-, post 9d.

BARGAIN OFFER

Don't miss this—of special interest to all constructors and engineers. 12 new assorted volume controls including switched and pre-set types. Really wonderful value. We receive many repeat orders for these. PRICE ONLY 6/-, post paid.

INEXPENSIVE HI-FI TAPE RECORDER KIT

Build yourself a high-fidelity tape recorder complete in smart portable cabinet for only £21.0.0. Easily assembled by even a complete novice in a few hours, and the use of a printed circuit amplifier gives guaranteed results every time. B.S.R. "TD2" Monadeck and TCC printed circuit amplifier. Full constructional data with wiring diagram and illustrations, etc. PRICE 2/6, post 6d. Full range of American "Brand Five" Ferro-dynamic recording tape in stock at very competitive prices. Brand new and individually boxed. S.A.E. for price list.

REPANCO COILS WITH DIAGRAMS

We carry in stock the full range of REPANCO high efficiency coils of all types. All are supplied boxed complete with diagrams, etc.
DRX1 High gain dual range crystal set coil, 2/6.
DRR2 High gain dual range coil with reaction winding, 4/-.
DRM3 Matched pair TRF coils dual range high gain, 8/-.
SH4 Matched pair dual range Superhet circuit coils, 8/-.
Individual "R" coils. Iron dust cored for maximum efficiency with small size. Complete with recommended circuits. Three types: Aerial (A), High frequency coupling (HF) and Oscillator (O) in the following ranges: RANGE 1—Long wave, RANGE 2—Medium wave, RANGE 3—Shipping 70 to 200 metres, RANGE 4—Short wave 10 to 50 metres. PRICE 3/3 each. PLEASE ADD 6d. post to order.

"GLOBE-KING" Short Wave Radio Kits



Now is the time to start this absorbing hobby. Explore the world from your own fireside with this wonderful little one-valve set. Real long distance reception at minimum cost. Recapture the thrill of pulling in those remote lands and all the countless amateurs chatting to each other. This set is built with top grade parts; do not confuse with cheap "ex govt." kits. Complete with three matched coils covering 10 to 100 metres, the kit costs £3.19.6. Send for leaflet today.

GOODMAN'S SPEAKERS



Bring your radio or Hi-Fi system to life with new sensational Goodman's AX10M 110 speaker. Superb 10in full range High Fidelity speaker with features that out-class all competition. Response 40 to 15,000 cycles, die cast chassis, 12,000 gauss magnet, aluminium voice coil, controlled edge diaphragm. In 15 ohms only. PRICE £5.0.0, plus 1/- part postage. Leaflet on request.

LINEAR BATTERY CHARGERS



Now is the time to instal a battery charger before the cold weather. For A.C. mains operation and all models fitted with ammeter. Strongly made and guaranteed for 12 months. Leaflet sent on request.
Model CL.1, 6 volt at 1 amp, 35/9.
Model CL.2, 6 or 12 volts at 1½ amps, 49/11.
Model CL.3, 6 or 12 volts at 3 amps, 75/-.
Model CL.5, 6 or 12 volts at 5 amps, 99/6.

Please add 2/- postage and packing

ARMSTRONG STEREO 12 Mk II HERE IT IS!


The most complete chassis ever produced. All on one compact chassis you have everything you want. Sensitive Medium and Long wave AM receiver with internal ferrite rod aerial. Full FM/VHF reception with automatic frequency control to keep it spot on tune, High Fidelity Monaural reproduction with 16 w. push-pull output High Fidelity Stereophonic reproduction with 8 watts push-pull output on each channel, independent wide-range Bass and Treble boost controls, facilities for tape recording and playback, built-in multiplex output for future stereo broadcasts, and hosts of other features. Why have lots of separate units with untidy wires and leads when this one super streamlined 1960 Tuner-Amplifier will do everything. Let us send you full details—or call for demonstration. PRICE 42 gns.

Full range of other Armstrong Chassis, Amplifiers, etc. in stock.

MULLARD "3-3" AND "510" AMPLIFIERS

These fine home constructor amplifiers are still recognised as the best in their class. Now available in Easy to Build kits with printed circuit main amplifier. These units can form the heart of a High Fidelity record player or radiogram unit. Constructional data with wiring diagrams 1/6 for each model. Detailed price lists available on request.

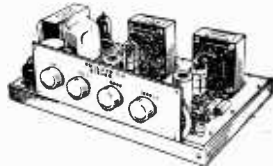We also stock all the components for the designs in the new MULLARD book "Circuits for Audio Amplifiers" including ready punched chassis, switches, Bulgin parts, front panels, etc. Book price 8/6, post 1/-. Detailed price lists of component parts 6d.



WE ARE PROUD TO ANNOUNCE THAT WE ARE APPOINTED STOCKISTS FOR THE WORLD FAMOUS HEATH KITS



HEADPHONES. New lightweight headphones, 4000 ohms and ideal for crystal sets, transistor sets, short wave reception, monitoring on tape, etc. Brand new and individually boxed, 15/-.
S. G. Brown type "F" high resistance, 37/6.
Ericsons as recommended by Eddystone, £2.15.0. Please add 1/- post to order.

We can offer from stock a full range of brand new genuine valves by Brimar, Marconi, Osram, Mazda, and Mullard. We also offer our special valves at very competitive prices, brand new, boxed, and guaranteed for 12 months. Please ask for complete list.

NYLON DRIVE CORD

Keep a reel of this Suffix nylon dial drive cord always handy. Non-stretch and non-slip and having high tensile strength. 25 yd. reels, 4/6, post paid

JASON TUNER KITS

Full range of the ever popular and well proved JASON Tuner Kits always in stock.

FMT.1, the original Standard FM/VHF tuner. Complete kit with valves, £7.7.6. FMT.2, new higher gain version with self-contained power pack and neat case. Complete kit, £9.8.0. FMT.3, special super fringe version with provision for A.F.C. Complete kit, £11.10.0. Mercury 2, Tuner for FM/VHF plus ITV and BBC TV sound channels. Switched tuning with new type turret. Complete kit, £11.0.0. JTV.2, similar to above but in neat shelf mounting cabinet and with own power pack. Complete kit, £14.14.0.

Leaflets on these kits on request.

UNIVERSAL AVOMETER MODEL D

Just released by the Air Ministry, these famous AC/DC Test Meters are a "snip" for anyone requiring a First Grade General Purpose Instrument. Normal Avometer size, 7 1/2 in. x 6 1/2 in. x 3 1/2 in., with carrying strap, indication being given on a 5 in. Mirror Scale. Thoroughly overhauled and complete with batteries and instructions. Provides 34 ranges of current, voltage and resistance, as follows:

D.C. Voltage	A.C. Voltage	D.C. Current	A.C. Current
150 mv.	7.5 v.	15 ma.	75 ma.
300 mv.	15 v.	30 ma.	150 ma.
1.5 v.	75 v.	150 ma.	750 ma.
3 v.	150 v.	300 ma.	1.5 amp.
15 v.	300 v.	1.5 amp.	7.5 amps.
30 v.	600 v.	3 amps.	15 amps.
150 v.	750 v.	15 amps.	
300 v.	1,500 v.	30 amps.	
750 v.			Resistance
1,500 v.			1,000 ohms.
			10,000 ohms.

ONLY £8.19.6 (carriage 3/6)

SELECTEST TESTMETER DIII. Manufactured by General Electric Co., and has exactly the same ranges as the Avometer Model D above, but has an even larger Mirror Scale. Size 9 x 7 x 5 1/2 in., with carrying strap. Thoroughly overhauled and in perfect order, with batteries and instructions. A real "snip" while they last, at ONLY £7.10.0 (carriage 3/6).

RECEIVER R 107. A few more of these fine receivers. 9 valves. 3 wavebands, covering 1.2-17.0 Mc/s (18-250 metres), incorporating built-in speaker and 2 power packs for use on 100-250 volts A.C. and 12 volts D.C. In magnificent condition, the finest we have yet had. ONLY £15 (carriage £1). A few sold sets for callers only at lesser prices.

COMMUNICATIONS RECEIVER R115. The famous Bomber Command receiver known the world over to be supreme in its class. Covers 5 wave ranges 18.15 to 7.5 Mc/s, 7.5 to 3 Mc/s, 1,500 to 600 kc/s, 500 to 200 kc/s, and 200 to 75 kc/s, and is easily and simply adapted for normal mains use. Full details being supplied. All sets thoroughly tested and in perfect working order before despatch, and on demonstration to callers. Fitted latest type super slow-motion tuning assembly. Have had some use but in excellent condition. ONLY £9.19.6. **A.C. MAINS POWER PACK OUTPUT STAGE.** For the above in black crackle case to match receiver, enabling it to be operated immediately, by just plugging in, without any modification. With built-in 8 in. speaker. £8.10.0. DEDUCT 10/- IF PURCHASING RECEIVER AND POWER PACK TOGETHER.

Send S.A.E. for illustrated leaflet, or 1/3 for 10-page booklet which gives technical information, circuits, etc., and is supplied free with each receiver. Add carriage 10/6 for Receiver, 5/- for Power Unit.

V.H.F. RECEIVER TYPE R.132. A superb 15 valve superhot receiver covering 95-150 Mc/s (2-3 metres), being fully tuneable over that range, with provision for Crystal Control. Has 2 stages of R.F., 3 of I.F., B.F.O., A.G.C., etc. Fitted with 2 in. square meter for Oscillator and Audio Signal checking. Size 19 in. x 10 in. x 10 in. Used, but in very good order, thoroughly air tested before despatch. Power supply required, 240-250 volts at 80 mA, and 6.3 volts at 4 amps. Complete with valves and circuit diagram. ONLY 79/6 (carriage etc., 10/6).

INTERCOM TELEPHONE SET. Two pairs of Brand New Headphones connected to Breast Microphones, with leads, etc. in fitted carrying cases. Supplies with 4 1/2 volt battery, 10 yards twin wire, and full instructions for connecting to make super intercom. ONLY 27/6 (post 3/6). Extra Wire 3d. per yard.

RCA 8 in. P.M. SPEAKER. In heavy black crackle metal case. Can be used as normal 3 ohms extension. Size 11 1/2 in. x 10 in. x 6 in. NEW IN MAKER'S CARTONS. ONLY 45/- (post 3/6).

POWER UNIT TYPE 3. Primary 200/250 volts A.C. 50 cycles. Outputs of 250 volts 100 mA, and 6.3 volts 4 amps. Fitted double smoothing, and 2 meters to read H.T. Current and Voltage. For normal rack mounting (or bench use) having grey front panel, size 19 in. x 7 in. BRAND NEW. ONLY 79/6 (carriage 7/6).

10/- CONSTRUCTION PARCEL. 10 Yards each of 6 colours wiring wire, solder, 24 each assorted Resistors and Condensers.

RESISTORS. 100 assorted values. New, 10/-.

CONDENSERS. 100 assorted mica and silvermica. NEW 12/6.

SPRAGUE CONDENSERS. Metal cased, wire ends. New 0.01 mfd. 1,000 volt, and 0.1 mfd. 500 volt, 7/6 per dozen. Special quotes for quantities.

MINIATURE MOTORS. Ideal for models. Will operate on 3-6 v. D.C. Size 1 1/2 x 1 x 1 1/2 in. plus fin. spindle. BRAND NEW only 7/6.

HARRIS ELECTRONICS

(LONDON) LTD.

138 Gray's Inn Road, London, W.C.1.

(Phone TERminus 7937)

Please include carriage costs on All items.

(Open until 12 M. Saturdays). We are 2 mins. from Highb. Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross.

STABQOIL by "ELECTRONIQUES"



1 1/2 x Full Size

HAVE YOU WRITTEN YET FOR DETAILS OF THIS UNIQUE NEW COIL DESIGN WITH THE BUILT-IN CAPACITY TRIMMER, TEMPERATURE COMPENSATION AND EXCEPTIONAL "Q"?


A 3d. STAMP WILL BRING COMPLETE DATA ON THESE OUTSTANDING COILS AND OTHER PRODUCTS.

ELECTRONIQUES


(FELIXSTOWE) LTD.,
RADIO WORKS, BRIDGE ROAD,
FELIXSTOWE, SUFFOLK. Tel.: 1100



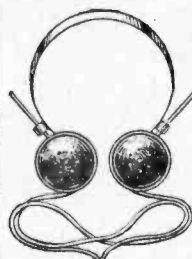SOLON INSTRUMENT SOLDERING IRON.
220/240 v., 25 w., 3/16 in. bit. 24/-, plus 8d. p. & p.



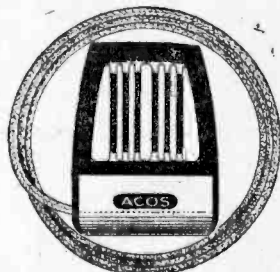High Impedance HEADPHONES
14/-, 1/- p. & p. With single earpiece and headband 8/-, 1/- p. & p. Hearing aid type phone 13/6, 8d. p. & p.



MICROPHONES. Acos Mic. 35 crystal (illustrated) 35/-, 1/3 p. & p. Acos Mic. 25-1 crystal, 25/-, 1/3 p. & p. Carbon hand mic. with switch 7/6, 1/3 p. & p.

LOUDSPEAKERS. All 3 Ω. 6 in. round, 22/-, 1/3 p. & p. 7 x 4 in. elliptical, 21/6, 1/3 p. & p. Polished walnut baffle, 10 x 7 1/2 in. for 7X4, 18/9, 1/- p. & p. Elac high fidelity, 9 x 5 in., 40/3, 1/3 p. & p.

KIRKMAN

(Dept. P.W.), 40 The Broadway, CRAWLEY, Sussex.

Letters to the Editor

The Editor does not necessarily agree with the opinions expressed by his correspondents

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of cover.

TRANSISTORS v. VALVES

SIR.—I feel I should protest against what Mr. D. J. L. of Kenton (July issue) says about the wrong class of reader, because I think I must be one of these.

Transistors open up a new field of construction for the beginner and I believe that there will, in the future, be two distinct classes of radio enthusiast—valve and transistor—both getting the same enjoyment out of a wonderful hobby. I suppose what Mr. D. J. L. meant by the wrong class was the fellows with limited knowledge of radio theory. Well let me tell him that we get as much enjoyment out of the hobby as he and his followers, and we do not envy them their knowledge.—T. DONACHIE (Eire).

STEREOPHONIC SOUND

SIR.—I have been interested in your articles on the above subject, and Mr. Richins' letter in the August issue. I, too, after having spent a large sum on equipment, have come to the conclusion that stereo is a waste of money.

One big drawback which I found was that there are many records which I hear on the radio and which I would like, but when I go to buy them I find that they are available only on mono discs. I would buy the disc if it were stereo, but after building the equipment I do not feel disposed to spend much on a disc if it is mono. Then again, radio is still one channel only, so that the amount of pleasure one can get from stereo is very limited.

Finally, as Mr. Hill says, why bother when the acoustics of the average room do not do full justice to it.—F. H. BARRINGTON (Hackney).

SIMPLE TRANSISTOR AMPLIFIERS

SIR.—I was very interested in the article under the above title in the June issue. After trying out some of the arrangements I have to point out one or two mistakes which occurred, as other readers may have been disappointed with their results. In Fig. 2 the collector load is shown as 470k. This is much too high and I found 4.7k was just about right. I even tried 3.9k which was hardly any different in results. In Fig. 4 the same slip also occurs, and I did drop this to 2.2k but as 4.7k also works here I assume that it was a draughting error and the decimal point was overlooked. Thank you for a very interesting monthly, and I only wish it were weekly.—F. R. TIMMINS (Eastbourne).

CROSS-OVER NETWORKS

SIR.—I recently came across a scheme which I do not seem to have read in your pages, and I would have thought it most important for beginners like myself. Cross-over networks for two loudspeakers are complicated and expensive, either to buy outright, or to make up and this idea dispenses with the large chokes, using in their place just one single fixed condenser. In the circuit which I was given an ordinary 2 μ F condenser was joined between the tweeter and the fitted speaker and it worked astoundingly well. Could not a table be prepared showing the cross-over frequencies with different capacities, as it seemed that when I used three or four 2 μ F condensers in parallel it gave a much lower cross-over and the top was much brighter.—R. JAMES (Liverpool).

INFORMATION SOUGHT

SIR.—I have recently experimented with one or two organ circuits, which I found in an old publication, and as there seems to be a dearth of such information, I would be glad if any reader could help me to find out two or three small details. I notice that most American electronic organs now use "sustaining" pedals, and I am interested to know what system is used, whilst "reverberation" also seems to be popular in the U.S.A. and I am told that this does not now use the mechanical system, but purely electronic. Perhaps we could have some information on these topics.—D. E. WORSLEY (N.W.).

LOUDSPEAKER DESIGN

SIR.—With reference to Mr. H. Pickering's article "Loudspeaker Design", PRACTICAL WIRELESS, August 1960, may I pass a few comments?

I do not presume to know anything more about speakers than Mr. Pickering but I do know that every day of the week there are highly trained, skilled, and fully qualified engineers whose sole job is to investigate and to experiment with various types, makes, and designs of speakers and speaker components. To further their experiments and investigations, thousands of pounds are being spent by the bigger manufacturers of various types of loudspeakers and it is often we see new types advertised. To read through Mr. Pickering's letter, one can but assume that he has never heard of such devices as the electrostatic loudspeaker. No, I'm afraid Mr. Pickering does not read the advertisements often enough, else he would see that the majority of loudspeaker manufacturers can now supply a customer with practically any desired type of speaker.

I suggest that Mr. Pickering should go to his local radio store and look around at the stock of speakers and I'm sure his eyes will be opened.—B. HALLAHAN (Cork).

COMPONENT

SIR,—I have recently become interested in radio as a hobby, but I have one everlasting complaint with component manufacturers. This is that while certain switch combinations are common, others are unobtainable. I have been constructing a multimeter from a 0.1mA meter, and while doing so, I have found it almost impossible to find the ratios which I want.

I would be pleased if the manufacturers brought out a full range of all combinations up to, say, 2 pole 20 way.

When talking to friends about this point, I found that I was by no means alone. They, and I, have had to buy switches which were not the actual combinations wanted, and sometimes found difficulty in using them.

I am sure that manufacturers would be quickly repaid for their trouble in producing these other combinations.—**M. BULLEN** (Eastleigh).

INTERFERENCE

SIR,—I agree with Mr. M. Reynolds (March issue), there should be a world conference as soon as possible for it will be madness to even try to get an uninterfered station on medium waves.

I recently tuned to a medium wave station on 208m but got three other stations of which not one was mine.

Some years ago there was a conference in which various stations were allotted certain frequencies, but this only stopped interference for two or three

years. What is the use of a conference if that is all it does? I should like to hear from any other people who agree with me.—**R. PARSONS** (Nun-eaton).

CRYSTAL SET RECEPTION

SIR,—On June 24 I picked up Radio Moscow on my crystal set. A few days later I heard Radio Moscow again, and also Prague Radio.

I would like to know if it is an unusual occurrence to receive radio signals on such a set from these distances.—**D. J. CONNOLLY** (Edinburgh 15).

NO. 19 SET

SIR,—With reference to Mr. Jackson's letter in the July issue of **PRACTICAL WIRELESS**, I recently purchased a No. 19 Mark II set. This has only two switches under the P.A. tuning dial and no R.F. gain control.

I have now removed the P.A. tuning completely, wiring a short-wave R.F.C. (removed from an old television tuner) between the grid of the first R.F. valve (6K7) and earth, connecting the aerial through a coaxial socket to the grid. The result, besides the ease of tuning, is increased sensitivity (and selectivity) and decreased noise level, this was possible to do as I have stripped the transmitter right out. In the place of the old P.A. tuning dial I have put a 200:1 slow motion tuning drive coupled to a two-gang 300pF tuning condenser, intended for use with a converter shortly to be built. — **G. C. GODDARD** (Wallington).


MAINS DUAL-WAVE 2

(Continued from page 515)

cannot be achieved, reverse connections to (3) and (4) at the end of the coil attached to the tag ring. The coil core positions will also influence reaction, but none of the adjustments is in any way critical. As there is only one tuned circuit, no loss of efficiency arises if the wavelength coverage is incorrect.

Cabinet and Safety

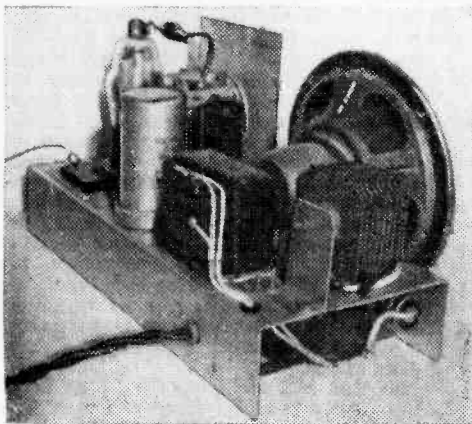With circuits of this type, the chassis is common to one mains lead when the receiver is switched



Another view of the receiver.

on. For this reason, it is wise to use a 3-pin plug, and take the chassis side of the circuit to mains neutral, as already mentioned.

If the receiver is operated from an adaptor or reversible 2-pin plug, it may be so connected that the chassis goes to the "live" main, which is at about 250V above earth. In these circumstances, an earth-return shock may be experienced if the chassis, or any metal item in contact with it, is touched. For this reason it is wise to include the receiver in an insulated cabinet, with a back. The cabinet should have an aperture covered with silk, for the loudspeaker. A further aperture should be positioned in front of the tuning scale, glass or other transparent material being held in place behind this by means of clips or adhesive. The tuning scale can be marked up with wavelengths, or stations.

When the receiver is inserted, the spindles and bushes fit into clearance holes in the cabinet front. Knobs should be chosen to cover the spindles and bushes completely. If the spindles are too long, they should be sawn shorter to suit. Flats may be filed on the spindles, and push-on-knobs used. If the knobs are held with grub screws it is considered good practice to fill the screw holes with wax or other insulating compound.

Cabinets suitable for receivers of this kind are available from time to time. Pleasing cabinets of simple design can also be constructed, if preferred, and Fig. 6 shows how one can be made. With the dimensions given, the cabinet will take a receiver 10½ in. x 6 in. x 5 in. If the chassis or speaker is larger than those given, the cabinet dimensions should, of course, be increased accordingly.

2-TRANSISTOR POCKET RADIO

INCORPORATING MINIATURE SPEAKER, PRINTED CIRCUIT, AND FERRITE ROD. A wonderful little instrument which fits snugly into a breast pocket. Size 3½ x 4½ x 1½ in. Tuneable over medium and long waves. Set of parts including Ivory coloured case, 2 transistors, and all necessary components to complete same (less batteries—available anywhere at 10d.).

22/6 Plus All parts sold separately. P. & P. 1/6. Point to point wiring diagram 1/6, free with kit. All transistors guaranteed 100%.



3-TRANSISTOR POCKET RADIO

INCORPORATING MINIATURE SPEAKER Plus Germanium Diode & PRINTED CIRCUIT

Size 3½ in. x 4 in. x 1½ in. Incorporating Ferrite Rod Aerial. Two Surface Barrier Transistors and one Audio. Tuneable over medium and long waves.

To build yourself **39/6** Plus 1/6 All parts sold separately. P. & P. Circuit diagram 1/6, free with kit. All transistors guaranteed 100%.



PUSH-PULL OUTPUT STAGE


Inclusive of transistors with input and output transformers to match 3 ohms speech coil, suitable for use with the above kit. Kit of parts including transistors. **19/6** Plus Post and All parts sold separately. P. & P. Point to point wiring diagram 1/6, free with kit.

CHANNEL TUNER

Will tune to all Band I and Band III stations. BRAND NEW by famous manufacturer. Complete with FCC84 and PCF89 valve (in series) L.F. 16-19 or 33-38. Also can be modified as an aerial converter (instructions supplied).

Complete with knobs.

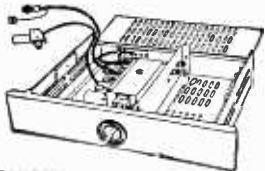32/6 Plus 3/6 P. & P. HEATER TRANSFORMER to suit the above. 200-250 v., 6/-, Plus 1/6 P. & P.



8-WATT PUSH-PULL AMPLIFIER

COMPLETE WITH CRYSTAL MIKE AND 8in. LOUDSPEAKER

A.C. mains 200-250 v. Size 10½ in. x 6½ in. x 2½ in. Incorporating 6 valves. H.F. pen., 2 triodes, 2 output pens and rectifier. For use with all makes and types of pick-up and mike. Negative feedback. Two inputs, mike and gram, and controls for same. Separate controls for Bass and Treble lift. Response flat from 40 cycles to 15 K/cs.,

+ 2db down to 20 K/cs. Output 8 watts at 5% total distortion. Noise level 40 db down all hum. Output transformer tapped for 3 and 15 ohm speech coils. For use with Std. or L.P. records, musical instruments such as Guitars, etc. **£4.19.6** Plus P. & P. 7/6. Or 20/- deposit Plus P. & P. 7/6, and 4 monthly payments of 23/-.



PORTABLE AMPLIFIER

On printed circuit for A.C. Mains 200/250 v. Size 4½ in x 3½ in. with tone and volume control. Valves: ECL82 and EZ70. **39/6** P. & P. 2/6

BUILT POWER SUPPLY UNIT

A.C. Mains 200-250 v. **21/-** Plus 3/6 P. & P. D.C. Output 250 v. at 75 mA. Also 6.3 v., 2 amp. heater winding.


WOLSEY 3-ELEMENT FOLDED DIPOLE

I.T.V. Aerial less mounting bracket for External use, complete with 12 vds. of coaxial cable. 15/-; 4 element, 17/6. P. & P. on above. 3.6.

BATTERY RECORD PLAYER & AMPLIFIER

Incorporating 45 r.p.m. "Starr" motor "Acos" crystal pick-up. 3 transistor push-pull amplifier complete with transistors. Output 500 milliwatts. 49/6. Plus 3/6 P. & P.

SIGNAL GENERATORS

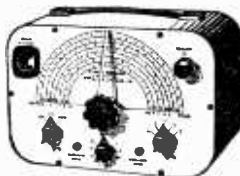


Cash **£6.19.6** or 25/- deposit and 6 monthly payments of 21/6. Post and Packing 5/- extra.

Coverage 100 Kcs-100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Metal case 10½ in. x 6½ in. x 5½ in. grey hammer finish Incorporating three miniature valves and Metal Rectifier. A.C. Mains 200/250 v. Internal Modulation of 400 c.p.s. to a depth of 30%; Modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch, variable A.F. output. Incorporating magic eye as output indicator. Accuracy plus or minus 2%.

Cash **£4.19.6** or 25/- deposit and 4 monthly payments of 21/6. Plus Postage and Packing 5/-.

Coverage 120 Kcs-84 Mc/s. Metal case 10½ in. x 6½ in. x 4½ in. Size of scale, 6½ in. x 3½ in. 2 valves and rectifier. A.C. mains 200-250 v. Internal modulation of 400 c.p.s. to a depth of 30%, modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch variable A.F. output and moving coil output meter. Grey hammer finished case and white panel. Accuracy plus or minus 2%

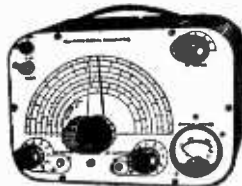

B.S.R. MONARCH UA8 WITH FUL-FI HEAD



4-speed plays 10 records 12½ in., 10 in. or 7 in. at 16, 33, 45 or 78 r.p.m. Intermixes 7½ in., 10 in. and 12 in. records of the same speed. Has manual play position; colour brown. Dimensions: 12½ in. x 10½ in. Space required above baseboard 4½ in. below baseboard 2½ in. Fitted with Ful-Fi turnover crystal head.

£6.19.6 Plus 5/- Postage & Packing With Stereo Head, **£7.19.6**, plus 5/- P. & P.

MAINS TRANSFORMERS

All tapped with Primaries 200-250 volts, 0-160, 180, 200 v., 60 mA., 6.3 v. 2 amps. 10/6, 280-0-280 v. mA. 6.3 v., 2 amp., 6.3 v. 1 amp., 10/6, 350-0-350 v. 70 mA. 6.3 v., 1 amp., 6.3 v., 2 amp., 10/6, 250-0-250 v. 70 mA., 6.3 v. 2 a., 10/6, Postage and packing on the above 3/-.

TRANSISTOR TESTER

For both P.N.P. and N.P.N. transistors incorporating moving coil meter. In metal case size 4½ in. x 3½ in. x 1½ in. Scale marked in gain and leakage. **19/6** Plus 2/6 Complete and ready for use. P. & P.


SURFACE BARRIER TRANSISTORS
Type SB305, 15 ohms, 7/6 each.

100% AUDIO TRANSISTORS. 5/- each.

F.M. TUNER UNIT

By famous German Manufacturer. Coverage 88-100 Mc/s. Complete with ECC85. Size 4½ in. x 2½ in. x 2½ in. **25/-** Plus P. & P. 1/6 Circuit diagram 1/-, free with unit. 10.7 Mc/s I.F. and Discriminator Coil, 4/- pair.

A.C./D.C. POCKET MULTI-METER KIT

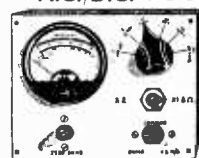

Comprising 2½ in. moving coil meter, scale calibrated in A.C./D.C. volts, ohms and milliamps. Voltage range A.C./D.C. 0-50, 0-100, 0-250, 0-500. Milliamps 0-10, 0-100. Ohms range 0-10,000. Front panel, range switch, wire-wound pot (for ohms zero setting), toggle switch, resistor and rectifier. In grey hammer finish case.

19/6 Plus P. & P. 1/6. Point to point wiring diagram 1/-, free with kit.

RADIO & T.V. COMPONENTS (Acton) LTD.

23 HIGH STREET, ACTON, LONDON, W.3
All enquiries S.A.E. Goods not dispatched outside U.K.

MISCELLANEOUS

YOU READ MUSIC?

Then how about making yourself an electronic organ? Constructional data available—full circuits, drawings and notes. It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.

Write NOW for free booklet and further details to C. & S., 20 Maude Street, Darlington, Durham.

SOUND RECORDINGS

TAPE/DISC/TAPE transfer. 1,800ft. American LP tape, 35/- p.f. UNIMIXER Mixing Units for quality. SOUND NEWS, 10, Clifford St., London, W.1.

RECEIVERS & COMPONENTS

TRANSISTOR BARGAINS. Brand new Mullard OC44 12/-, OC45 10/-, OC70 8/6, OC78 12/6 each matched. OC44/45 type 10/6, OC70/71 72 type 6/6. Red spot 3/9, white spot 5/6. D. B. CARTER (Electronics), 347, Ladbroke Rd., Sparkbrook, Bham 12.

GUARANTEED VALVES from 6d. Lists 3d. HAMILTON RADIO (W), 13, Western Road, St. Leonards, Sussex.

VOLTMETERS!!! AMMETERS!!! BARGAINS!!!

UNUSED, BOXED, GUARANTEED. EX. M.O.S. POST-FREE. AMMETERS. 2in. Dial, moving coil, with shunt, 5 milliamper basic movement, scaled 0-20, 8/6. 6in. dial, moving iron, 50 cycles, A.C., scaled 0-50, 23/-, 4in. dial, 50 cycles, A.C., scaled 0-30, 12/-. VOLTMETERS. 2in. dial, moving coil, 10,000 ohms resistance, D.C., scaled 0-50, 8/6.

SPEED ELECTRICS, Dept. PWL, Church Street, Basford, Nottingham, Tel. 75716

EX-GOV. VALVES, IT4 3/-, IL4 1/6, 89 6/-, OZ4 4/-, ECC81 4/-, 6SN7GT 5/-, 12A6 3/-, 12AH7 3/-, 1R5 3/-, 185 3/-, 6L6G 5/-, C.W.O., send for full list. WOODWARD, 16, Aubrey Road, Sherwood, Nottingham.

ANNAKIN

We offer the finest bargains:

Indicator No. 188A.—With VCR517 (6in. tube), 8—EF50, 3—EB34, 2—EA50 valves. All the usual controls, plus lots of parts-New. Boxed. A gift at 37/6 ea. carr. 7/6.

Prismatic Binoculars. By Karl Swartz. 8 x 26. Bloomed lens. Wt. 16 oz. NEW. No case. Our special price £7.19.6 ea.

VHF Recr. BC-624, 100-150 mc. With 12 valves. Less xtals and power pack. Only 32/8 ea. 5/- carr.

VHF Trans. BC-625, 100-150 mc. With 7 valves, 2 relays. Less xtals, 32/8 ea., 5/- carr.

Selenium Rectifiers, 500 v. 30 ma, 2/-, post 9d.

AF Transformers, 1-200 ohm., 1/-, post 11d. **Periscope Prisms,** 3/- pair, post 1/6.

Carbon Mikes, 3/- each, post 1/6. **Unit,** with 5—EF91, 1—EA91, 6—slug tuned coils, 53 small parts. (No sen.). Cheap at 15/- each, post 1/6.

Contact Assembly. Miniature, with 2 make contacts (platinum), 2/- ea., post 6d. **Chokes,** 10.H. 60 ma., 1K, 2/- ea., post 1/6. **Electric Motors.** Small 4-6 v., 6/- ea., post 6d.

Mail Order (Mainland) only. C.W.O. ONLY. Stamped addressed envelope for lists please! 25ASHFIELDPLACE, OTLEY, YORKS.

RATES: 5/6 per line or part thereof, average five words to line, minimum 2 lines. Box No. 1, extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., London W.C.2.

"WEYRAD" TRANSISTOR RECEIVER

COMPLETE KIT—LONG & MEDIUM WAVE, PUSH-PULL O.P., £8.17.6. CONSTRUCTORS BOOKLET 2/-
Send S.A.E. for Shopping List.

WESTHAM RADIO (SUPPLIES)
Rear of 176, Abbotshury Road
WEYMOUTH, DORSET

MULLARD TUBES, reclaimed, 6 months' guarantee. 9in., 30/-, 12-14in., 59/6, 17in., 79/6. All pictures tested. **FITTED FREE.** Picture shown to callers. Other makes, types, cheap. Salvaged spares for modern and obsolete sets. Prices from: Lot 17/6, EOT 7/6, Osc. Tr. 6/-, Mains tr. 10/-, Valves, 1,000 types in stock. EF91, EB91, 6J5 2/6, EF80, MF1, EF42 3/6. Save money. Send a S.A.E. with enquiries or for free list. "ST. JOHN'S RADIO" 156, John's Hill, S.W.11 (BAT9838).

TUBES 18 Months' Guarantee
MAZDA & MULLARD TYPES

12in. and 14in. 25.10.0
17in. 45.0.0
21in. 53/20 28.0.0 (return old tube £1 rebate)
Other Types—List Available.
TERMS C.W.O. Postage and Insurance 10/-
WILFORD RADIO SERVICE
(Dept. P.W.) 44 MAYFIELD GR., MEADOWS,
NOTTINGHAM

RESISTORS.—100 new, wire ended, assorted, all types, 7/6 box, post free. **COOK'S OF BEDFORD,** 29, St. Mary's Street, Bedford.

TRANSISTORS 3/6. Printed circuit and components. Crystal set parts. List 4d. **CARTER'S,** 578, Washwood Heath Road, Birmingham 8.

Precision Infinitely Variable Speed Gearboxes, 0 to 6000 r.p.m. driven by 1/4 h.p. 230 v. A.C. motor 26 (10/-). American Amplifiers, Mike input 2 x 2000 ohm output 24 input uses 1-12B7 and 2-6V6, 7 x 3 5In. 12/6 (less valves) (2/6). Kurman Relay, 8PDT 7000 ohms 3 amp contacts, 12/6 (1/8). Metal Rectifiers, 24 v. 12a. 20/- (3/6). 51t. P.O. Raoks, angle iron sides 19in. wide, 65/- (10/-). B.48 Communications Receivers 1.4 to 15.0 Mc/s continuous battery driven built-in speaker: 8 valves, £12.10.0 (10/-). B.47, same as above only 15 to 500 kc. and 10 valves, £9.10.0. B.C.610 Whip Aerials, 4 sections, 12ft. in. canvas bodied, 50/- (5/-). Heavy Insulated Bracket Mounts for above 26/- (5/-). BC-659 Transmitter Receivers crystal controlled 14 valves (less crystals and valves) 35/- (10/-). BC-659 Power Supply Units, vibrator type for attachment to Tx R. 6 v. or 12 v. input (less vibrator), 25/- (10/-). BC-659 Battery Box for attaching to Tx R. for man pack use, 7/6 (6/-). 50 watt Power Amplifier rack mounting, 250 v. a.c. input (1—MH4, 2—PA-25, 1—U50) with v/c and meter, less valves 35/- (35/-). AVO Portable Geiger Counters for Beta or Gamma Ray detection, new test batteries £13.0.0 (10/-). Laboratory Main Filter Units removes mains borne interference, 10/- (2/6).

40 PAGE LIST OF OVER 1000 ITEMS IN STOCK AVAILABLE—KEEP ONE BY YOU

American Operators Tables, black crackle, 36 x 22 x 3in. Jack boxes and articles under, ideal for many uses, 85/- (10/-). Germanium Diodes, GEX 35, 45, 55 or 66, all 2/6 each (paid). Elliott 0/1M/a moving coil meters, 2000 o.p.v., 2 1/2in. dia. Power Units, 1200 v. 200mA smoothed from 200/250v. a.c., 1 cwt. 26/11. Amount in brackets in carriage England and Wales.

We have large quantities of "Bits and Pieces" that we cannot list—please let us have your enquiries, we can probably help—everyone answered.

P. HARRIS, ORGANFORD, DORSET

RECEIVERS & COMPONENTS

(continued)

BATTERY CHARGER TRANSFORMER, 6/12 v., 3 amp. Tapped input 200/230/250 v. 15/8
FULL WAVE RECTIFIER for above 10/-
TRANSFORMER for 12 v. 1 amp charger 9/-
RECTIFIER 21 v. at 230 v. input, 65 watt TRANSFORMER, 240/250 v., 500 va 36/- suitable for soil warmer, etc. 18/-

Above transformers are all double wound.
AUTO-TRANSFORMER, 210/230/250 v., 500 va 36/-
All sent Post Free. Diagrams supplied

C. A. FRANCIS

15 NICKLEBY ROAD, CLANFIELD, Hants.

BENDIX RECEIVERS RA-10, 4-band superhet, 150kc/s-10Mc/s. 8 valves: 6SK7-RF; 6K8-Mixer; 2-6SK7-IF; 6R7-sec. det. 6C5-BFO; 6K6-OF; 6H6-noise lin. Built-in E.U. 2V. Clean. Size 6 1/2in. x 15 1/2in. Easily converted to mains as described on p. 453 Sept. 1957 "P.W." £4, p.p. 10/- E.W.S. CO., 69, Church Road, Moseley, Birmingham 13.

SPEAKER REPAIRS. Cones/Fields fitted. Clock Coils Wound. L.S. REPAIRS, Pluckley, Ashford, Kent.

FM-AM STEREO

Radiogram chassis - CB8

Paired output 6 watts Plain or Stereo Records. A hand-built quality unit with two speakers. ONLY £20.

BEL SOUND PRODUCTS CO., Marlborough Yard, London N.19
ARC. 5078

GET LUXEMBOURG clearly at last! Our attachment fits any radio. Complete and easy to fit. 3/11 each, post and packing 6d. **EDDY'S** 116 Alfreton Road, Nottingham.

"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure. **DIRECT TV REPLACEMENTS LTD.,** Dept PW/7/9, 138, Lewisham Way, S.E.14, Tideway 6666.

RECLAIMED VALVES, tested and perfect; huge stocks; all one price, 5/- plus 6d. postage each. Delivery by return. **LEWIS,** 46, Woodford Ave., Ilford, Essex.

KINGSLAND

ELECTRONIC COMPONENTS

Stupendous Offers

Insulated Radio Pliers. Screwdriver, Bench Vice, 4 Assd. 3ft. Screened Leads, 10/-, p. & p. 1/9.

Set of 4-Piece Two-way Screwdrivers in case. All Metal Plane. Junior Hacksaw, 10/8, p. & p. 1/8.

BARGAIN PACK. Pair Throat Microphones, 150. Assorted Screws, 2ft., 2in. Screened Lead with socket, one 5 Henry 200 mA Choke, 3 Electrolytic Condensers, 6 nob. 3 Toggle Switches, 6 Octave Valve Bases, 1 Waveband Switch, 6 Coax. Plugs, 6 Assorted Coils, 6 Cartridge Fuses, 6 Potentiometers, 6 W.V. Multipliers, Peston Lamp and Holder, Coil of Wire, 15/6, p. & p. 3/6.

New 115 v. Relay's 15 amp. 7/6, p. & p. 2/6. Instrument Rectifier with Circuits, 5/6, 6 v. or 12 v. Vibrators, 2/6 each, p. & p. 1/6. 6 Assorted Droppers, 5/-.

Loaded Chassis, 7/6 and 5/-, p. & p. 4/6. Mike and Pick-up Transformers. Ideal for Baby Alarms, 4/6, p. & p. 1/6.

100 Assorted Resistances, 5/-, p. & p. 1/9. New headphones, low impedance, ideal for crystal sets, etc., 4/6, p. & p. 1/8.

6 Assorted Potentiometers, 5/-, p. & p. 1/6.

182 KINGSLAND RD., SHOREDITCH, E.2. Tel.: SHO 6572. Sorry, U.K. only.

FOR SALE

TELEPRINTERS CHEAP, each complete with cover, large stock, new spare parts, fit tuned relay and receive. Printed message when absent. Box No. 29.

KITS, built complete. Details: 6. Hooker Rd., Heartsease, Norwich, Nfk.

Telephone Sets, 7/9. E. W.D. New condition, Morse tapper, switched, jack plugs, etc.: less phone. Post 3/6.

Rectifiers 2/9. Westinghouse. 250v. 100mA. Full or half wave. Salvage rntd. P. & P. 1/3. Insulating Tape 1/6 per roll. 75ft. x 1in. Good quality. Post on 1 tin, 9d.; post on 6 tins, 2/.

P.P. COMPONENTS LTD.

219 ILFORD LANE, ILFORD, ESSEX
Mail Order Only. Stamp for NEW Catalogue.

ANOTHER NEW low-priced Tape Bargain! 1,800ft latest polyester on 7in. reel. 32/6 p.p. 1/6. Also outstanding bargains in all other sizes 3in. to 4in. S.A.E. for list (includes American Audio Tape, BASF etc). Over 30 mint condition secondhand Tape Recorders and all new Recorders and Hi-Fi Equipment on NO INTEREST H.P. Terms. E. C. KINGSLEY AND CO. (Dept. P.W.) 132, Tottenham Court Road (near Warren St.), London W.1. EUS6500.

LOUDSPEAKERS 7in. x 4in. 7/6; 6 1/2in. 7/6; 8in. 10/-; Large stocks valves-transistor components and kits—Lists available. H.R. MAIL ORDER, 16, Regent Parade, Harrogate.

**BLANK CHASSIS
MADE TO ORDER
SAME DAY SERVICE**

Metalwork Dept.
H. L. SMITH & CO. LTD.
287-289 Edgware Road, London W.2
PAD. 5891-7595

FOR SALE. Cossor double beam oscilloscope type 339 with spare tube. 10 position timebase. 5 CPS to 250,000 CPS. Amplifier 10 CPS to 2,000,000 CPS. Good working order. Offers above £15 considered. Box No. 28.

1,000 COMPONENT BOXES each with 10 adjustable compartments 2in x 1 1/2in. x 1 1/2in. and press on lid. Ideal for nuts, screws, etc. 3/11 ea. 6 for £4, post free. JERVIS, 16, Manor Road, Brampton, Chesterfield.

100 BAYS of brand new adjustable steel shelving, 72in. high x 34in. wide x 12in. deep, stove enamelled, dark green, sent unassembled, six-shelf bay, £3/15/-. Sample delivered free, quantity discounts. N. C. BROWN LTD., Eagle Stenworks, Heywood, Lanes. Tel.: 69018.

COMPLETE SET of parts for making Radio, Multiester, etc. Perfect. Worth over £70. Going at only £45. Write R. SHEWARD, C/o I.C.S. LTD., 40, Parkgate Road, London S.W.11.

SPECIAL OFFER

In Stereogram Equipment and Cabinets.
Write for Lists.
A. L. Stamford Ltd. (Dept. F.29)
94/96 Weymouth Terrace,
Hackney Road, London E.2.



WANTED

WANTED Service Sheets No quantity too large. Highest prices paid. SULTAN RADIO, 29, Church Road, Tunbridge Wells, Kent.

A PROMPT CASH OFFER for your surplus Brand New Valves, Speakers, Components, Test Instruments, etc. R.H.S., 155, Swan Arcade, Bradford 1.

BEST price paid by return for new Valves and equipment. STAN WILLETTS, 43, Spon Lane, West Bromwich, Staffs. Tel.: WES 2392.

WANTED VALVES

All types for prompt cash. Must be new. State quantity.

WILLIAM CARVIS LTD.
103 North Street, Leeds 7

SERVICE SHEETS

SERVICE SHEETS for sale, all types, from 1/-. Free fault-finding guide with all service sheets. 100 TV Service Sheets covering 330 popular models, 18/6. Radio, TV, Electronic Books: s.a.e. lists/enquiries HAMILTON RADIO (W), 13, Western Road, St. Leonards, Sussex.

SERVICE SHEETS, TV 4/- ea. Radio 3/- ea. List 1/-. All orders dispatched on day received. Also Manuals for sale and hire. Mail orders only. SULTAN RADIO, 29, Church Road, Tunbridge Wells, Kent.

SERVICE SHEETS. — We have the largest stock of Radio and TV Sheets in the country for sale at 4/- ea. Why tolerate delay in obtaining your supplies when we will dispatch by return? 1960 Radio and Television Service Sheet List Now Ready, 1/-. Also Manuals for sale and hire List 9d. S.A.E. please. Mail orders only. S.P. DISTRIBUTORS, 11, Old Bond Street, London W.1.

SERVICE SHEETS. Largest stock Radio and Television Sheets north London, 4/- each with S.A.E. State make and model No. Circuit Diagrams only 2/6. Also Manuals for sale and hire. Radios over 20 years our speciality. All enquiries S.A.E. please. WYNDSOR TELEVISION, St. Albans Road, Barnet, Herts.

SERVICE SHEETS. Radio, TV 5,000 models. Lists 1/-. S.A.E. enquiries. TELRAY, 11, Maudland Bk., Preston.

FAULTFINDER FILES, showing common faults that each receiver is prone to and other useful servicing information. 2/- ea. List 9d., plus postage. S.P. DISTRIBUTORS, 11, Old Bond Street, London. W.1.

SERVICE SHEETS

RADIO and Television
Over 100,000. S.A.E. for List.
Large stock of obsolete Radio and Television Valves.
JOHN GILBERT RADIO
20 Extension
Shepherd's Bush Market, London W.12
SHE 3052

EDUCATIONAL

City and County of Bristol Education Committee
BRISTOL TECHNICAL COLLEGE

Principal: E. POOLE
B.Sc. (Eng.), M.I.Mech.E., M.I.Prod.E.

**SCHOOL OF NAVIGATION AND
SCHOOL OF MARINE RADIO & RADAR**

Head of School: H. C. PUZEY, Extra Master

The following courses are available:

3-4 months' preparatory courses leading to certificates of Competency as Master, 1st Mate and 2nd Mate, P.G. and Master and Mate, H.T. (Entry at any time.)

One Year's Pre-Sea Training Course for prospective M.N. Cadets. (Entry in September of each year.)

Courses for Marine Radio Officers leading to 1st and 2nd Class F.M.O. Certificates, also a 12-weeks' course for M.O.T. Radar Maintenance Certificate. (Entry in January, April, May and September.)

For further particulars apply to The Registrar, Bristol Technical College, Ashley Down, Bristol 7.

"HOW AND WHY" of Radio and Electronics made easy by a new, non-maths, Practical Way. Postal instruction based on hosts of experiments and equipment building carried out at home. New Courses bring enjoyment as well as knowledge of this fascinating subject. FREE brochure from: Dept. P.W. 12, RADIOSTRUCTOR, 40, Russell Street, Reading, Berks.

INCORPORATED Practical Radio Engineers home study courses of radio and TV engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text is free. The "Practical Radio Engineer" journal, sample copy 2/-. 6,000 Alignment Peaks for Superhets, 5/9. Membership and Entry Conditions booklet, 1/- all post free from the SECRETARY, I.P.R.E., 20, Fairfield Road, London, N.8.

LEARN RADIO AND ELECTRONICS the new practical way! Hosts of absorbing experiments carried out at home under expert guidance to teach you Radio in a new, enjoyable and interesting way. Construction, servicing and fault finding on equipment made easy for the first time! No previous experience needed. No mathematics used. Free brochure from: Dept. 11 P.W. RADIO-STRUCTOR, 40, Russell St., Reading, Berks

NEW!

LEARN

**RADIO & TV
SERVICING AND
ELECTRONICS**

and how to make and build your own equipment—using an exciting new practical apparatus course. Ideal for starting your own business or as a fascinating hobby.

FREE Brochure, without obligation,
RADIOSTRUCTOR Dept
G77

READING, BERKS
Britain's leading radio training organisation

(continued on next page)

EDUCATIONAL*(continued)*

WIRELESS. See the world as a Radio Officer in the Merchant Navy; short training period; low fees; scholarships, etc., available. Boarding and Day students. Stamp for prospectus. **WIRELESS COLLEGE**, Colwyn Bay.

Radio Television & Electronics

Learn at home with the World's largest home study organisation. **Brit.I.R.E.**; **City & Guilds**; **R.T.E.B.**, etc. Also Practical Courses with equipment. No books to buy.

Write for **FREE prospectus** stating subject to

I.C.S.

Intertext House, Parkgate Road,
(Dept. 541), London S.W.11

SITUATIONS VACANT

ELECTRICAL FITTERS and RADIO ELECTRICIANS

Vacancies exist in the Admiralty Surface Weapons Establishment Extension at Royal Naval Stores Depot, Copenacre, Havthorn, Wiltshire, for Electricians (Radio) and Electrical Fitters. Applicants for the former position should have at least five years' experience in the trade and for the latter must have completed a recognised apprenticeship.

2. The Establishment is located 8 miles from Bath. The work is interesting and varied, in modern test rooms and workshops, and is mainly concerned with the testing and modification of naval radio and radar equipment.

3. The commencing basic rate of pay is 189s. 8d. for a five day week. Further increases are granted according to merit. After a probationary period of not less than one month or more than three months, employees are considered for an initial award of merit pay up to 20s. 0d. a week which is back-dated to the date of joining. The amount of the award will vary according to relative ability. Maximum merit pay is 40s. 0d. After a qualifying period of service, all employees are eligible to be considered for permanent and pensionable employment.

4. Admiralty employment confers certain benefits, including paid sick leave entitlement, paid public holidays, and a fortnight's paid annual holiday.

5. Recreation and welfare facilities are available; an assisted travel scheme is at present in operation.

6. Applications, in writing, should be addressed to The Officer-in-Charge, Admiralty Surface Weapons Establishment Extension, Royal Naval Store Depot, Copenacre, Havthorn, Wiltshire.

SITUATIONS VACANT*(continued)*

Ministry of Aviation Electrical Inspection Directorate Electronic Inspectors

Required at Bromley, Kent; Woolwich and Greater London

Skilled men are invited to join the staff inspecting and testing computers, radar, radio, communications and other electronic equipments.

The work is interesting and affords opportunities for acquiring valuable experience in specialised fields. There are good prospects of promotion, and training facilities are available.

Applicants should have served an apprenticeship (or have had similar training) or have served in H.M. Forces in an appropriate trade. Candidates should be proficient in the use of standard test equipment including signal generators, oscilloscopes and bridges, and also be able to interpret drawings and specifications.

Annual leave is two weeks initially and three weeks after five years service in the grade. A paid sick leave scheme is in operation.

Canteen and social amenities are available.

Apply, giving qualifications, to

The Administrative Officer (L)
(PW) Electrical Inspection Directorate,
Ministry of Aviation, Golf Road,
Bromley, Kent

CITY, AND GUILDS (Electrical, etc.), on "No pass—no fee" terms. Over 95% successes. For details of Electrical Engineering, Applied Electronics, Automation, etc., send for our 148-page handbook, free and post free. **B.I.E.T.** (Dept 242A), 29, Wright's Lane, London. W.8.

SITUATIONS VACANT*(continued)*

A.M.I. Mech.E., **A.M.Brit.I.R.E.**, **City and Guilds**, **G.C.E.**, etc., bring high pay and security. "No pass—no pay" terms. Over 95% successes. For details of exams and courses in all branches of Engineering, Building, Electronics, etc., write for 148-page handbook, free **B.I.E.T.** (Dept. 242B), London W.8.

RADIO AND TV SERVICING, all aspects from basic principles. Guaranteed coaching for **City and Guilds**, **R.T.E.B. Cert.**, **Brit.I.R.E.**, etc. Study at home under highly qualified tutors. No books to buy. Write for **FREE Prospectus**, stating subject to:—**I.C.S.**, Intertext House, Parkgate Rd., (Dept. 541A), London, S.W.11.

ENGINEERS REQUIRED for public address amplifier maintenance by company operating from S.E.1 area. Ability to drive an advantage, salary according to age and proficiency. Five-day week and staff pension scheme. Apply for full details of age and experience. Box No 72, **DORLAND ADVERTISING LTD.**, 28, Heymarket, London S.W.1.

TV AND RADIO, **A.M.Brit.I.R.E.**, **City and Guilds**, **R.T.E.B. Cert.**, etc., on "No pass—no fee" terms. Over 95% successes. For details of Exams and Courses (including practical apparatus) in all branches of Radio, TV and Electronics, write for 148-page handbook, free. **B.I.E.T.** (Dept 242G), 29, Wright's Lane, London. W.8

HANDICRAFTS

JEWELLERY SIMPLY MADE. Catalogue Free. Brooches, Ear-clips, Rings, Marcasite. **WEBBS HANDICRAFTS**, 46, Burnway, Hornchurch, Essex.



A few excellent vacancies for men who can learn a skilled trade in today's R.A.F.

You can learn a trade worth having, in today's R.A.F. Your training is very thorough and gives you a skill at your fingertips for life. Pay compares very well with the equivalent jobs outside, and, if you are single, there's nothing out of your pay-packet for food or rent. Leave is a month a year, you get the chance to travel and you work with a fine lot of people.

Radar or Wireless Mechanics. Suitable candidates are now being accepted for thorough training on the latest radar and wireless equipment and its maintenance, fault-finding and repair.

Electrical or Instrument Mechanics. There are vacancies for suitable applicants to be trained in the skilled trades of electrical and instrument maintenance.

For full information write to:

**Central Recruiting Office (PW 728),
Victory House, Kingsway, London, W.C.2.**

TODAY'S TOP JOB IS THE R.A.F.

RADIO CLEARANCE LTD.

27 TOTTENHAM COURT RD., LONDON, W.1

The oldest Component Specialists in the Trade

Telephone: MUSEUM 9188 EST. 30 YRS.

TRADE ENQUIRIES INVITED

MOULDED TROPICAL PAPER CONDENSERS
Small, non-inductive, insulated, high-grade Capacitors 150 v. Wkg. 15 Mfd. 5%, 10d. 32 Mfd. 10% 8d. 2 Mfd. 10% 11d. 250 v. Wkg. 0.68 Mfd. 8d. 1 Mfd. 11d. 22 Mfd. 2% 1/4. 1 Mfd. 10% 1/7. 800 v. Wkg. 880 pF. 1,000 pF. 1,500 pF. 2,200 pF. 7d. each. 3,300 pF. 8d. 5,000 pF. 6,800 pF. .01 Mfd. 9d. each. 8,200 pF. 1/-. .022 Mfd. .03 Mfd. 10d. each. .047 Mfd. 2%. .05 Mfd. 11d. each. 1 Mfd. 11d. .22 Mfd. 1/7. 6 Mfd. 1/3 & 1/9. 750 v. Wkg. 470 pF. 10%. 820 pF. 1,500 pF. 2,000 pF. 8d. each. 5,000 pF. 6,800 pF. 8d. each. .022 Mfd. 10d. 1,000 v. Wkg. 1,500 pF. 8d. 6,800 pF. 10d. .01 Mfd. 1,500 v. 1/-. 12 Mfd. 1/-. 18 Mfd. 1/1 each.

VARIABLE GANG CONDENSERS
Twin Gang 20 pF. Ideal for F.M. 2 1/2 in. x 1 1/2 in. 2/-.
Twin Gang .0005 MFD. 2 1/2 in. x 2 in. x 1 1/2 in. Spindle 5/16 in. 4/-.
Min. Twin Gang. .0005 MFD. 2 1/2 in. x 1 1/2 in. x 1 1/2 in. Spindle 1/2 in. 5/8.
Min. Twin Gang. .0005 MFD. 2 1/2 in. x 1 1/2 in. x 1 1/2 in. Spindle 1/2 in. with trimmers 6/8.
AM/FM 2-Gang Condensers. 500-20 pF. 3/6.

DISC CERAMIC CONDENSERS 500 v. Wkg.
500 pF. .001 MFD. .002 MFD. .0025 MFD. .003 MFD. .005 MFD. 6d each. .01 MFD. 9d.

We have an extensive range of waxed paper condensers (average price 5d. each). Metallised paper condensers (average price 11d. each) and wire wound resistors 5/6/7-watt types (average price 1/- each).

The "MIRACLE" Super Six (transistor components), as advertised in the August issue, Page 316, and the electrolytic condensers as advertised in the September issue, page 457 are still available

STAMPED AND ADDRESSED ENVELOPE with any enquiry please. Please allow FULL Postage and Packing charges. TERMS OF BUSINESS: CASH WITH ORDER OR C.O.D. ON ORDERS OVER 10/-.

TRANSISTOR COMPONENTS

SUB MINIATURE ELECTROLYTIC CONDENSERS Most with sleeves, all at 2/3 each.
1 mfd. 50 v., .25 mfd. 15 v., .5 mfd. 50 v. 1 mfd. 10 v. 25 v., 2 mfd. 0 v. 15 v. 70 v., 4 mfd. 12 v., 5 mfd. 25 v., 6 mfd. 3 v. 6 v., 8 mfd. 3 v. 6 v. 15 v. 30 v. 10 mfd. 0 v. 25 v., 16 mfd. 3 v. 6 v. 30 v. 12 v. 15 v., 25 mfd. 12 v., 30 mfd. 3 v. 6 v. 12 v. 50 mfd. 6 v.

MINIATURE POLYSTYRENE CONDENSERS
10 pF. 100 pF. 500 pF. 1,000 pF. all 125 v. working, 8d. each. 220 pF. 300 pF. 470 pF. 660 pF. 1,000 pF. 1,200 pF. 4,900 pF. all 9d. each.

SUB MINIATURE TRANSISTOR COILS
Set of 3 I.F. Transformers 470 kc/s plus Oscillator coil.
As specified for Mazda Circuits 23/6 complete.
As specified for Mullard Circuits 23/6 complete.
4/6 each. WVO 470 kc/s. for Jackson or Plessey Gang WTC coil. WVO 470 kc/s. I.F. Transformers 4/-. each, 7/6 pair.

SUB MINIATURE CARBON POTS
5K, 50K, 250K, 330K, 1M, 2/- each, 5M with switching, 4/6. 5K, 1/6, 500K preset 1/-. 1M Transistor Pots, 2/-, 5K Transformer Pots, 1/6. Fully Moulded-Track Carbon Pots. diameter 1/4 in. short spindles, 2/8 each.
100Ω, 250Ω, 400Ω, 500Ω, 1K, 2K, 2.5K, 5K, 10K, 25K, 50K, 100K, 250K, 500K, 1M. SUB MINIATURE METALLISED PAPER CONDENSERS 10 v. x 1/4 in. 100 v. working.
.005 MFD. .0022 MFD. .002 MFD., .001 MFD., 8d. each. .02 MFD., .04 MFD., 9d. each.

TRANSISTOR GANG CONDENSERS
With intermediate screen and switch for long wave fine-tuning as specified for MULLARD Transistor Circuits 11/-.

SWITCHES ROTARY
Size 1 5/16 in. dia. .2 in. spindles. Price 2/11 each. 1 pole 10 way. 1 pole 12 way. 2 pole 2 way. 2 pole 3 way. 2 pole 4 way. 2 pole 5 way. 2 pole 6 way. 3 pole 3 way. 3 pole 4 way. 4 pole 3 way.

POTMETERS CARBON-HI-GRADE
Moulded Tracks. Dia. 1 in., 2 1/2 in. spindles, 5K, 10K, 25K. Linear only. 50K, 100K, 250K, 500K, 1M, 2M, Log or Linear, less switch, 2/6 each. With switch 4/6.

TRANSFORMERS
Audio Output Types 6,000Ω to 3Ω 3/6, 10,000Ω to 3Ω 3/9.
Universal CRT Boosters with tapped primaries 2 v. 6.3 v. 18 v. 25% boost all taps, 10/6. Filament transformers, centre tapped, 6.3 v. output, 1.5 amps., 5/9. 3 amp 9/6. Charging Transformers. Tapped all voltages 2 amp. 14/3, 4 amp. 16/6.

MODERN TV COMPONENTS
Perov Line O/P transformers, 10 Kv. U25 10/6. Frame O/P transformers to match 4/8. Scanning Coils to match 10/6, 90° types 12/6. Panel containing 6 preset pots 5/-. Smoothing Chokes, 2 Hy. 250 mA., 3/11. 1.9 Hy. 260 mA. 2/11. 1.3 Hy. 250 mA. 2/6. I.F.C. Metal Rectifier 250 v. 250 mA. 10/-, 3/4 Meg. 1 F.T. 1/6 ea. 3/8 Meg. 1 F.T. (link) 2/- ea. Masts 14 in., 17 in. and 21 in., 2/6, 3/6, 4/6 (plus 2/6 p.p.).

TV PEST CONTROLS
Knurled knob and 6BA fixing holes, diameter 1 in., 100Ω, 5K, 10K, 25K, 50K, 100K, 200K, 250K, 500K, 1.5M, 2M. All at 1/3 each. 25K wire wound 1/6.

EXPRESS ELECTRONICS

ROSEDALE LABORATORIES

KINGSWOOD WAY, SELSDON, SURREY

VALVES NEW, TESTED AND GUARANTEED

REDUCED PRICES

101	7/6	6RS7	10/6	16A5	9/6	BRF80	8/6	N37	10/6
102	8/-	6BW6	7/6	25A6GT	10/6	CC81	5/-	PCC84	9/-
103	8/-	6BW7	7/-	95L6GT	6/6	CC82	7/6	PCP80	9/-
1P1	7/6	6C10	9/-	25Z4G	9/-	EC83	7/6	PCP82	7/6
1FD1	8/-	6D2	5/6	30C1	8/-	PC84	9/6	PC182	8/-
1FD9	7/6	6F2	3/-	30L1	8/-	PCF80	10/6	PC181	12/-
1L4	6/6	6F2	3/-	35L6GT	9/-	PCF82	10/6	PL82	7/-
1P1	8/-	6H6GT	2/-	35W4	8/6	EC142	9/-	PY81	8/6
1P10	7/6	6K7G	8/6	35Z4GT	8/6	PC181	10/-	PY82	7/6
1P11	7/6	6K7G	7/6	6783	7/6	EC182	9/6	PY83	7/6
1P5	8/6	6N7GT	7/6	DAF91	7/6	EF41	9/-	R19	12/6
1B5	5/6	6E6G	7/6	DAF90	8/-	EF90	8/6	U32	7/6
1Q4	8/-	6X4	7/-	DF91	7/6	EF91	11/-	U76	7/6
384	7/6	6X5GT	8/-	DF96	8/6	EF92	3/6	U77	7/6
5V4	7/6	7B7	7/6	DR76	7/6	EL41	9/6	UB41	9/6
6BA6	7/6	6CS	7/6	DT77	7/-	EL41	5/6	UB42	9/6
5Y3GT	7/6	8D3	3/-	DH142	8/6	EL84	2/6	UF41	8/6
6Z4G	9/6	12A6H	10/6	DH150	10/-	EM34	7/6	UL41	8/6
6AK6	6/6	12AT7	5/-	DK91	7/6	EY51	10/-	UY41	7/6
6AL5	5/6	12AU7	7/6	DK96	8/6	KZ40	7/6	W76	6/6
6AM6	3/-	12AX7	7/6	DL82	7/6	EZ80	8/-	W142	8/6
6AT6	7/6	12BH7	10/6	DL84	7/6	EZ81	8/-	X17	7/6
6BA7	7/6	12CK7	6/6	DL96	8/6	KZ30	9/6	X142	9/-
6BE6	7/-	12K8GT11	8/6	EA80	8/6	NT1	8/6	X150	9/-
6BR7	9/6	12Q7GT	7/6	EH91	8/6	K16	8/-	Z77	3/-
				6RC41	10/-	N19	7/6	ZD17	7/6

VOLUME CONTROLS MIDGET SIZE LONG SPINDLES, D.P. switch.
3/6. 5 P., 3/8. Less switch, 2/6. Values 10K to 2M. Pro set 2/6.

MATCHED PAIRS

BL54 21/-, 6V6G 17/-, 6BW6 18/- per pair. Push Pull O.P. Transformers for above 3-15Ω 14/6. 12" P.M. Speakers 31/ 24/6. Baker's "Bellhurst" 12" 15Ω 15W, 30/- P. & R. 2/6. 12" Stereo Model 87/6.

SETS OF VALVES

DK91, DF91, DAF91, DL92 or DL94	19/6
102, 103, 1P1, 1FD1, 1P1	27/6
103, 1P1, 1FD1, 1P1	27/6
1B5, 1T4, 1B5, 384, or 5V3	19/6

Postage and packing 6d. Over £1 post free. C.O.D. 2/6



Safety first every time with these patented spring-loaded AVO Prodclips.

Cleverly designed for use as insulated prods, they are invaluable for reaching and holding test points which are difficult of access.

Suitable for use with AvoMeter, Multimeter and Avo Electronic Test Meter Leads. Post Free 15/- per pair.

AVO LTD - AVOCET HOUSE,
92-96 VAUXHALL BRIDGE ROAD, LONDON, S.W.1.
(Victoria 3404 (12 lines))


A MEMBER OF THE METAL INDUSTRIES GROUP OF COMPANIES

Premier RADIO

23 TOTTENHAM COURT ROAD, LONDON W.1
and at 309 EDGWARE ROAD, LONDON W.2

TEL.: MUSEUM 3451/2
TEL.: PADdington 6963

"THE MID-FI"

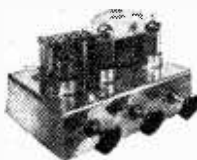

A NEW DESIGN
4 WATT AMPLIFIER KIT
MAY BE
BUILT FOR 95/- plus 3/-
p. & p.

A new circuit for the home constructor requiring a good quality medium powered Amplifier for reproduction of Records or F.M. Broadcasts. For use with Loudspeakers of 3 or 15 ohms impedance. Technical Specifications: separate bass and treble controls. Valve line-up EF86, EL84, EZ80. Voltage adjustment for A.C. mains from 200-250 volt. Negative feedback. Size 7 x 5 in., overall height 5in. Silver hammered finish Chassis. Instruction Book 1/-.



THE EASY-SIX

6-Transistor Battery Portable
MAY BE
BUILT FOR £9.15.0 plus 3/-
p. & p.

Ever-Ready PP7 Battery extra 3/3

STAR FEATURES ★ Six Mullard

Transistors ★ Internal Ferrite Rod Aerial ★ Provision for Car Radio Aerials ★ Sin. Loudspeaker ★ Printed Circuit, with component positions indicated ★ Pre-assembled Dial Assembly ★ 500 milliwatts push pull output. ★ Full medium and long waveband coverage ★ Attractive two-tone Blue/Cream Vynidex covered Cabinet, dimensions 8½ x 6½ x 3in. Weight, 3lb. with battery. Inst. book 1/6.

DRAMATIC PRICE REDUCTIONS

Avantic SP11. 10 watts (per channel) combined Stereophonic Amplifier and Pre-amplifier. Dimensions 14½ x 8½ x 4in.
Original Price 28 gns. OUR PRICE 19/gns. 7/6 p. & p.

Avantic PL621. 20 watt monaural amplifier, frequency response 10 c/s-30 kc/s ± 1db. L.S. impedance 4, 8 or 16 ohms. Dimensions 14 x 8½ x 4½in.
Original Price 29 gns. OUR PRICE 19 gns. 7/6 p. & p.

Avantic SP21. Stereophonic Pre-Amp. Control Unit designed for use with the DL7-35 Power Amplifier. Power requirements 6.3 v. at 1.3A. A.C., 350v. at 5mA D.C. Dimensions 14½ x 9 x 4in.
Original Price £28 10.0. OUR PRICE 16 gns. 7/6 p. & p.

Avantic DL7-35. Power Amplifier, power output 54 watts. peak. Valve line up: GZ34, 2—EL34, ECC83, EF86. L.S. impedance 4, 8 or 16 ohms switch selected. Dimensions 14½ x 9 x 8½in.
Original Price 30 gns. OUR PRICE 16 gns. 12/6 p. & p.

2-BAND RECEIVER

MAY BE BUILT FOR £5.10.0 plus 3/- packing and postage. This receiver uses the latest type circuitry and supplied complete with easy to follow point-to-point wiring diagrams, suitable for use on A.C. mains 200/250 v. When constructed the Receiver is housed in an attractive walnut finish Bakelite Cabinet or if required, Wooden Walnut Cabinet. Overall dimensions 12 x 6½ x 5½in. Instruction Books available separately. PRICE 1/-.



required, Wooden Walnut Cabinet. Overall dimensions 12 x 6½ x 5½in. Instruction Books available separately. PRICE 1/-.

PRACTICAL WIRELESS SERVICE MANUAL

A Complete Work on the Testing of all Types of Wireless Receivers and the Construction and Use of Test Instruments.

by F. J. Camm, Revd. by A. T. Collins.
21/-. Postage 1/-.

FUNDAMENTALS OF SEMI-CONDUCTORS by M. G. Scroggie.
23/-. Postage 1/-.

THE RADIO AMATEUR'S HANDBOOK, by A.R.R.L., 1960. 32/6. Postage 2/-.

TRANSISTOR PROJECTS, Gernsback Lib. 23/-. Postage 1/-.

THE A.R.R.L. ANTENNA BOOK, by A.R.R.L. 18/-. Postage 1/3.

SHORT WAVE RECEIVERS FOR THE BEGINNER, a Data Pub. 6/-. Postage 6d.

RADIO VALVE DATA, 6th Ed., compiled by "W.W." 5/-. Postage 9d.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-23 PRAED STREET,
LONDON, W.2

Phone: PADdington 4185.
Open 6 days 9-6 p.m.

FIRST-CLASS RADIO COURSES . . .

GET A CERTIFICATE!

QUALIFY AT HOME—IN SPARE TIME

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification. Prepare for YOUR share in the post-war boom in Radio. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs, Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A. M. I. P. E., A.M.I.Mech.E., Draughtsmanship (all branches) etc., together with particulars of our remarkable Guarantee of SUCCESS OR NO FEE!

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER
150,000 SUCCESSSES—

NATIONAL INSTITUTE OF
ENGINEERING
(Dept. 461), 148 HOLBORN,
LONDON E.C.1

S. Africa: P.O. Box 8417, Jo'burg.
Australia: P.O. Box 4570, Melbourne

CABINETS & HI-FI EQUIPMENT

We can supply any Cabinet to your own specification



"Bureau"
£16.10.0

This is only one example taken from our extensive range of stock cabinets. Write for our NEW 24 page fully illustrated catalogue on:

THE LARGEST RANGE OF CABINETS IN THE COUNTRY.
Equipment is also our speciality and we now offer, in a novel book form: A NEW EQUIPMENT COMPARATOR illustrating our range of radio chassis, speakers, tape decks, single players and autochangers.

SEND TODAY for a copy of these two books, which are absolutely FREE.

LEWIS radio

100 (PW1060) Chase Side
Southgate, N.14
Palmer's Green 3733

FOR VALVES - TUBES AND COMPONENTS - BY RETURN POST SERVICE



N73 19/11	UCC84 10/11	5V4 11/6	6U5G 8/6	10LD11 12/-	1457 17/-	35Z4GT 8/-
N147 14/6	5Y3GT 8/-	6U7G 8/6	10M12 23/3	15D2 7/9	42 42	8/-
N339 17/6	UCC85 9/6	6V6G 6/-	10P13 15/-	19A05 9/9	35Z3 16/7	8/-
OZ4 5/6	UCF80 29/10	6V6GT 7/9	10P14 19/3	20D1 15/3	35Z5GT 9/-	8/-
P61 3/6	UCH21 23/3	6X4 7/6	12A6 12/-	20F2 26/6	50C5 11/6	8/-
PABC80 13/11	UCH42 9/6	6A7 10/-	12A8 12/-	20L1 26/6	50CD6G 29/10	8/-
PCC84 8/6	UCH81 10/6	6ABG 9/-	12A6 12/-	20P1 26/6	50L6GT 8/6	8/-
PCC85 11/6	UCL82 11/6	6AC7 4/-	6.30L2 12/6	20P3 23/3	50L6GT 8/6	8/-
PCC88 23/11	UCL83 13/6	6AG5 5/6	7B6 10/6	20P5 23/3	75 10/6	8/-
PCC89 19/11	UF41 9/-	6AK5 5/-	7B7 8/6	25A6G 10/6	77 6/-	8/-
PCF80 8/9	UF42 17/3	6AL5 4/-	7B8 6/-	25L6GT 10/6	78 7/6	8/-
PCF82 11/6	UF80 13/11	6AM5 7/6	7C5 8/-	25Z4 9/6	80 8/6	8/-
PCF84 16/7	UF85 9/-	6AM6 4/-	7C6 8/-	25Z5 8/-	142B7 3/6	8/-
PCL82 11/6	UF86 17/11	6AQ5 7/6	7D6 13/6	25Z6 10/6	185B7 33/2	8/-
PCL83 13/6	UF89 9/-	6AT6 7/6	7H7 8/-	27S1 19/11	210DDT 4/6	8/-
PL38 26/6	UL44 10/6	6AU6 10/6	7Q7 9/-	30C1 10/6	210VPT 3/6	8/-
PL38 26/6	UL46 26/6	6BBG 4/-	7S7 9/6	30F5 10/6	30 10/6	8/-
PL38 26/6	UL48 9/-	6BA6 7/6	7Y4 8/6	30FL1 10/6	83 10/6	8/-
PL81 11/-	UU6 10/-	6BE6 7/6	8D2 2/9	30L1 19/11	301 10/6	8/-
PL82 8/6	UU8 26/6	6BH6 9/-	9D2 3/6	30L15 23/3	302 10/6	8/-
PL83 9/6	UY1N 12/6	6B16 9/-	10C1 17/3	30P4 15/-	304 10/6	8/-
PL84 12/7	UY41 7/6	6BR7 12/6	10C2 17/6	30P12 12/6	305 10/6	8/-
PL82 8/6	UY85 7/6	6BW6 9/6	10D2 12/-	20P16 9/6	306 10/6	8/-
PL82 8/6	VP133 15/-	6C4 4/6	10F1 12/6	30PL1 12/6	807 6/6	8/-
PL82 8/6	VR22(PM2A) 6/6	6C5 5/-	10F3 23/3	30PL1321/11 954 2/-	955 4/-	8/-
PY32 17/11	VR22 8/6	6CSG7 6/6	10F9 15/3	35L6GT 10/-	955 4/-	8/-
PY80 7/6	VP23 6/6	6C6 5/-	10F18 15/3	25Y5 9/6	956 3/6	8/-
PY81 8/6	VP41 8/6	6C7 9/6	10L1 15/11	35W4 7/6	5763 9/-	8/-
PY82 7/-	VR105/30 8/-	6C31 7/6				8/-
PY83 8/6	VR150/30 7/6	6D6 5/-				8/-
PY84 9/-	VU120A 3/6	6CH6 8/6				8/-
PY85 8/6	VU120B 3/6	6F6G 7/6				8/-
PY86 8/6	VU120C 3/6	6F6M 7/6				8/-
PZ30 19/11	VU120D 3/6	6F1 14/-				8/-
PEN4DD 26/6	VU120E 3/6	6F13 14/-				8/-
PEN4VA 10/-	VU120F 3/6	6F14 26/6				8/-
PEN25 6/-	VU120G 3/6	6F15 14/-				8/-
PEN45 10/-	VU120H 3/6	6F18 15/3				8/-
PEN46 7/6	VU120I 3/6	6F23 18/7				8/-
PEN383 23/3	W21 10/-	6F33 7/6				8/-
PE4220A 4/-	W76 7/6	6G6 2/6				8/-
PEN45DD 26/6	W77 8/6	6H6 2/6				8/-
PEN4 12/6	W101 8/6	6H6GT 2/6				8/-
PM12M 8/-	W61 6/-	6J5G 3/6				8/-
QP21 5/-	W61(M) 8/-	6J5GT 5/-				8/-
SP41 3/-	X22 12/6	6J5M 6/6				8/-
SP61 3/-	X41M 12/6	6L6 5/6				8/-
SP4/5 10/6	X101M 8/-	6I7G 6/6				8/-
SP4/7 10/6	Y23 7/6	6K7G 4/-				8/-
TP25 10/-	Z61 (4 pin) 8/6	6K7M 6/9				8/-
U10 9/6	Z309 7/6	6K8G 6/6				8/-
U14 8/6	Z359 7/6	6K6GT 7/-				8/-
U16 12/6	IA3 3/6	6K7GT 5/9				8/-
U22 8/-	IA7GT 12/6	6K8GT 10/-				8/-
U25 15/-	IC2 11/6	6K25 19/11				8/-
U26 10/-	IC5 12/6	6L6G 8/-				8/-
U37 26/6	IC5G 12/6	6LM 9/6				8/-
U45 15/-	ID5 9/6	6LG 7/6				8/-
U50 9/-	ID6 10/6	6LI 23/3				8/-
U76 8/-	IH5GT 9/-	6L18 11/6				8/-
U81 8/-	IL4 6/6	6L19 13/6				8/-
U81 8/-	ILD5 3/6	6LD20 15/11				8/-
U101 8/-	INS 10/6	6M1 17/3				8/-
U339 16/7	IR5 7/6	6N7GT 7/6				8/-
U403 16/7	IS4 10/6	6PI 19/3				8/-
U404 11/4	IS5 6/6	6P26 19/11				8/-
U404 11/4	IT4 5/6	6P28 26/6				8/-
U801 29/10	2C26 1/6	6Q7G 7/6				8/-
UABC80 3A5 12/6	3A5 12/6	6Q7GT 9/6				8/-
UAF42 9/6	3A8GT 6/-	6SA7GT 8/-				8/-
UB41 9/6	3D6 5/-	6S7 7/6				8/-
UBC41 8/6	3Q4 7/6	6SH7 4/6				8/-
UBC81 11/4	3Q5GT 9/6	6S17 8/6				8/-
UBF80 9/6	354 7/6	6SK7 6/-				8/-
UBF89 13/11	3V4 8/-	6SL7GT 8/-				8/-
UBL21 23/3	4D1 3/-	6SN7GT 7/6				8/-
UC92 13/3	5R4GY 9/6	6SQT 9/3				8/-
	5U4G 6/6	6U4GT 12/-				8/-

AUTOMATIC RECORD CHANGER UNITS

B.S.R. "Monarch" UA8, 4-speed unit with B.S.R. Ful-Fi cartridge, £6.19.6.
B.S.R. "Monarch" UA8, as above but fitted with B.S.R. Ful-Fi STEREO cartridge, £7.19.6.
B.S.R. "Monarch" UA12, 4-speed unit in green and cream, £8.19.6.
B.S.R. "Monarch" UA14, 4-speed unit in two tone grey, £8.19.6.
Collaro "Conquest", 4-speed fully mixing changer complete with studio "0" cartridge, £7.19.6.
Garrard RC120 4D Mk.2, 4-speed unit with manual control to enable records to be played singly fitted GC2 cartridge, £8.19.6.
Garrard RC121 4D, 4-speed unit with plug in pick-up head, £10.19.6.

SUNDRY SPECIALS

Semi air spaced co-axial cables, 6d. yd. 2 gang condensers AM/FM type, 3/9 each. High resistance headphones, 4,000 ohms, 13/6 pair. 2 mfd paper block condensers for X over, 9d. each. 1,200ft. reels of recording tape, 21/- each. Acos GP54 pick-up arm with cartridge, 27/6 each. Weller 100 watt soldering gun, 75/- . Line cord 3-way, 0.3 amp or 0.2 amp, 1/9 yd. JB "00" 2 gang condensers for Transistor kits, 9/6 each. Rola C25 2 1/2in. loudspeaker, 26/8 each. Telescop car radio aerials, wing fixing, 25/6 each. Solon 625 instrument iron, 25 watts, 24/- each.

TELEVISION TUBES - REGUNNED 12 MONTHS' GUARANTEE

MW31/74, £5.10.0; CRM-152B, £6; MW36 24, £5.10.0; CRM141, £5.10.0; CRM123, £5.10.0; MW43/69, £6; CRM171, £6. Carriage and insurance 10/- extra. Allowance on old tube if returned.

LATEST B.S.R. "MONARDECK" SINGLE SPEED

3 1/2 i.p.s., takes 5 1/2 in. spools. Simple controls. £9.19.6. Tapes extra. Carriage and Insurance 5/6.

SINGLE RECORD PLAYERS

Collaro Junior, 4-speed turntable and pick-up complete with crystal cartridge and sapphire styl, 75/- . E.M.I. Single Player, 4-speeds with automatic stop. Fitted with Acos STEREO turn-over cartridge, £6.19.6.

CATALOGUE

Our 1961 catalogue is now available, please send 1/- in stamps for your copy. Trade catalogue also available, please attach your business letter heading.

TERMS: Cash with order or C.O.D. Postage and Packing charges extra; as follows: Orders value 10/- add 1/-; 20/- add 1/6; 40/- add 2/-; £5 add 3/- unless otherwise stated. Minimum C.O.D. fee and postage 3/-. For full terms of business see inside cover of our catalogue. Personal Shoppers 9 a.m. to 5 p.m. Mon. to Friday; Saturday 10 a.m. to 1 p.m.



103 LEEDS TERRACE
 WINTOUN STREET
 LEEDS 7

REPANCO TWINETTE

A NEW REMARKABLE TWO TRANSISTOR PORTABLE RADIO FOR THE HOME CONSTRUCTOR

- ★ LOUDSPEAKER, 7 x 4in. ELLIPTICAL
- ★ TWIN FERRITE SLAB AERIALS
- ★ LONG AND MEDIUM WAVES
- ★ PROVISION FOR EXTERNAL AERIAL
- ★ SIZE 7 x 5 x 3in.
- ★ LOW BATTERY CONSUMPTION

Send now for Easy Wiring Plans and Component Price List, 1/6 (post free).

★ OTHER
REPANCO
EASY-TO BUILD RECEIVERS

	Envelope
The R.E.P. One-valve Radio	9d.
The Highwayman. A 4-valve Portable Radio	1/6
F.M. Tuner Unit. 5 Valves plus Tuning Indicator	1/6
Three Dee. 3-transistor Radio... ..	9d.
Mini-3, Mk. II, 3-transistor Pocket Radio	1/3
Mini-7, Mk. II, 7-transistor Pocket Receiver	1/6
Transeven, 7-transistor Portable Receiver	1/6
Major-7 7-transistor Portable Receiver	1/6
Transistor Car Radio Receiver	2/-
Transistor Amplifier and Feeder Unit Circuits	1/6

Please add towards postage.

For details of our Components send 6d. in stamps for our ★ 1960 Catalogue.

Mail order and Trade:
RADIO EXPERIMENTAL PRODUCTS LTD.
33 Much Park St.
COVENTRY
Tel.: 27114

Wholesale Inquiries and Export:
REPANCO LTD.
O'Brien's Buildings
203-269 Foleshill Rd.
COVENTRY
Tel.: 24224

GZAK: This Month's Bargains

AMERICAN "SIGNAL" MORSE KEYS

Type M100 with switch. This excellent, lightweight, fast key is currently priced in U.S.A. at \$6.85 (£2 10s.) and is offered at only 12/6, p. & p. 1/6.

AERIAL EQUIPMENT

TWIN FEEDER. 300 ohm twin ribbon feeder, similar K25, 6d. per yard. K35B Telcon (round) 1/6 per yard. Post on above feeder and cable 1/6 any length.

COPPER WIRE. 14 G., H/D 140ft. 17/-; 70ft. 8/6. P. & P. 2/- . Other lengths pro rata. Stranded 7/25, 140ft. 10/-; 70ft. 5/- . P. & P. 2/-.

RIBBED GLASS. 3in. aerial insulators, 1/6 each or 6 for 7/6. P. & P. 1/6.

CERAMIC FEEDER SPREADERS. 6in. type F.S. 9d. each or 8/- dozen. P. & P. 2/-.

CERAMIC "T" PIECES. Type A.T. for centre of dipoles, 1/5 each or 3 for 4/- . P. & P. 1/6.

2 METRE BEAM 5 ELEMENT W.S. YAGI. Complete in box with 1 x 2 1/2in. mast head bracket. PRICE 49/- . P. & P. 3/6.

SUPER AERAXIAL CABLE. 75 ohm, 300 watts; very low loss, 1/8 per yard. P. & P. 1/6. 50 ohm, 300 watt coax, very low loss, 1/6 yd. or 20 yds. 27/6. P. & P. 1/9.

HEADPHONES H.R. TYPE. 4,000 ohms., very sensitive. ONLY 12/6 pr. P. & P. 1/6. C.L.R. Type (low res.), 8/6. P. & P. 1/6.

Absorption WAVEMETERS. 3.00 to 35.00 Mc/s. in 3 switched bands, marked on scale. Complete with indicator bulb. **A MUST** for any Ham shack. ONLY 17/6, post free.

ROTARY CONVERTERS. 6 v. input, 250 v., 125 mA output. ONLY 17/6. P. & P. 3/- . 12 v. 490 v. 65 mA, 17/6. P. & P. 3/- . Also 12 v. D.C. MINIATURE, output, 360 v., 30 mA cont. or 310 v. 70 mA intermittent rating. 12/6 each or 22/- for 2. P. & P. 2/-.

CHAS. H. YOUNG LTD.

THE COMPONENT SPECIALISTS

Dept. "P", 110 Dale End, Birmingham 4. (CEN 1635)
(No C.O.D. under £1 please) (By return Service)

THE PUNCH YOU NEED!

HOLE PUNCHES

One Minute Type

3/8" diameter	4/9 ea.
1/2" " " " " "	5/6 "

Screw-up Type

1/2" diameter	6/- ea.
3/4" " " " " "	7/6 "
1" " " " " " "	7/3 "
1 1/4" " " " " "	7/6 "

Postage and packing 1/-

1 1/8" diameter	8/- ea.
1 1/4" " int. Octal	8/9 "
1 3/8" " " " " " "	10/- "
1 1/2" " " " " " "	11/3 "
1 3/4" " B9G	12/6 "
2 3/4" " Meter	18/- "

Post and packing 1/9

Owing to increased costs, all hole punches will go up as from 1st January, 1961. Buy now while stocks last.

Oliver & Randall Ltd.

Dept. P.W.

40, Perry Hill, London S.E.6

Tel.: FOrest Hill 8424

BOOKS FOR THE CONSTRUCTOR

REALISTIC HIGH FIDELITY. Hartley, 5/6, post free. 96 pages, 36 illustrations. The author sets out to achieve the maximum realism in sound.

HIGH FIDELITY STEREO GRAMOPHONE. Easterling, 5/6, post free. 96 pages, 33 illustrations. This book describes the construction of a complete unit for playing stereophonic records with absolute fidelity.

PRACTICAL TRANSISTOR RECEIVERS. Sinclair, 5/6, post free. 56 pages, 36 plans and illustrations. Over 50 different receivers described and illustrated from the simple single transistor to the more advanced types.

TRANSISTOR CIRCUITS No. 1. Gregory, 2/10, post free. 32 pages, 8 circuits, 24 plans and illustrations. Full constructional details are given for units suitable for the beginner as well as the more advanced constructor.

TRANSISTOR CIRCUITS No. 2. Sinclair, 2/10, post free. This second book gives circuit details and constructional data for a further number of transistorised units.

HIGH FIDELITY TAPE RECORDER. Sinclair, 2/10, post free. 24 pages, 15 illustrations. This book describes the construction of an elegant and high performance tape recorder with a frequency response of from 30 c/s to 12,000 c/s.

HIGH FIDELITY LOUDSPEAKER ENCLOSURES. Babani, 5/6, post free. 28 pages, 25 plans and illustrations. This is probably the most comprehensive book ever written on the subject.

BOYS' BOOK OF CRYSTAL SETS AND SIMPLE CIRCUITS. May, 2/10 post free. 96 pages, 24 illustrations and plans. The book is written and presented so as to enable anyone to make the twelve different sets, whilst having no previous experience of radio.

BEGINNERS' GUIDE TO RADIO. Camm. New and Revised Edn., 8/-, post free.

SERVICING TRANSISTOR RECEIVERS. Pettit, 6/6, post free. 72 pages, 44 diagrams. The book explains new servicing techniques as applied to transistorised equipment.

RADIO CONTROL OF MODELS. Sommerhoff, 5/6, post free. 80 pages, 43 diagrams and plates. The author has much to interest the enthusiast in this field.

SEND STAMP FOR LISTS (over 150 titles).

FREE with your order. Mullard valve data book, 1960 edition.

SELRAY BOOK CO.

60 HAYES HILL, HAYES, BROMLEY, KENT

H.A.C. SHORT-WAVE EQUIPMENT AND SHORT-WAVE KITS

Famous for over 25 years for S.W. Receivers and Kits of Quality.

H.A.C. were the original suppliers of SHORT-WAVE RECEIVER KITS for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, Hams, etc.

Improved designs with Denco coils: One-valve Kit, Model "C". Price 25/- . Two-valve Kit, Model "M". Price 50/- . New Addition: Model "K". Super sensitive "All Dry" Receiver. Special incl. price, Complete Kit, 77/-.

All kits complete with all components, accessories and full instructions. Before ordering call and inspect a demonstration receiver, or send for descriptive catalogue and order form.

POST THIS COUPON NOW!

"H.A.C." SHORT-WAVE PRODUCTS

(Dept. TH), 11 Old Bond Street, London W.1

Please send me FREE and without obligation your 1960 literature.

NAME _____

ADDRESS _____

Brand new, individually checked and guaranteed

VALVES

AC/CD	2/6	DL72	7/6	ESU208	8/3
AC/P	4/6	DL96	8/6	EY51	8/3
AC/PI	2/6	EI323	25/-	EY91	3/6
AC/SP2	4/6	EI224	6/6	EZ40	7/6
AC/SP5	4/-	EA50	1/6	EZ80	7/6
AC6/PEN	5/-	EAC91	4/6	FW4/500	6/6
AC/SP3	4/6	EB34	1/6	H30	5/-
AL60	6/-	EB91	3/7	H63	3/6
AR8	5/-	EBC33	6/-	KBC32	5/-
ARDD5	2/-	EC52	3/-	KFC5	5/-
ARP3	3/-	ECC32	4/-	KT2	4/-
ARP4	3/6	ECC81	6/6	KT31	8/-
ARP12	2/9	ECC82	6/9	KT33C	7/-
ARP24	3/6	ECC83	7/-	KT44	7/-
ARP21	5/6	ECC84	7/9	KT63	6/-
ARP34	4/6	ECC91	4/-	KT241	9/-
ATP4	2/9	ECL80	9/6	KTW62	7/6
ATP7	5/6	EF22	7/3	KTV63	6/6
AU1	5/-	EF32	5/-	L30	4/-
AU4	5/-	EF36	3/6	MH4	3/6
AW3	4/-	EF39	4/6	ML4	4/-
BL63	6/-	EF50	2/6	ML6	4/-
BT45	40/-	EF52	5/-	NPT42	5/3
BT9B	40/-	EF54	3/6	N3/PEN	6/-
D41	3/3	EF55	6/-	N34	8/-
D42	4/-	EF70	4/-	NR15A	3/-
D77	4/3	EF90	6/9	NT37	3/-
DA30	12/6	EF85	6/10	(4033A)	10/-
DAF86	8/-	EF86	9/-	OD3	5/-
DET5	15/-	EF89	8/9	P61	2/6
DET19	2/6	EF91	4/10	PCC84	8/6
DET20	2/6	EF92	5/-	PCC85	8/-
DF70	9/-	EL32	3/9	PCF80	8/-
DF72	7/6	EL35	9/-	PEN25	4/6
DF96	8/-	EL41	8/3	PEN46	5/6
DH76	4/9	EL84	8/3	PEN65	6/6
DK96	8/-	EL91	7/6	PEN220A	3/-
DL71	8/-	EM4	4/-		

PENDD/	1360	9/6
PL81	11/-	VR78 4/-
PL82	8/-	VR99 8/-
PL83	9/-	VR105/307/6 6AC7 4/3
		6AG5 4/6
PM4DX	3/-	6AG7 8/-
PT25H	7/6	6AJ7 4/3
PY82	8/-	6AK5 6/9
QP21	6/-	6AK6 7/6
QP25	5/3	6AK7 8/-
QVQO6-40	W31 7/-	6AM5 5/-
	Y63 5/-	6AM6 6/3
	Y66 45/-	6B8 5/6
	Y68 6/-	6BBG 2/6
	Y69 6/-	6C4 4/-
QS75/20	6/9	6C5 6/-
QS195/10	6/9	6C6G 4/6
QS108/45	6/9	6C8G 5/-
		6E5 5/-
QS150/15	6/9	6F6 7/-
		6F7 7/-
		6F8G 6/6
		6F9G 6/6
		6G2 2/6
		6G6G 3/-
		6H6GT 1/9
		6H6M 4/3
		6HA7 4/3
		6I5 3/6
		6J5G 3/3
		6L6 4/3
		6L7 7/6
		6K6GT 6/6
		6K7G 2/3
		6K7GT 5/3
		6K8G 6/6
		6L5G 6/-
		6L6 9/-
		6L7 4/6
		6L8 2/6
		6M7G 5/-
		6N7GT 7/-
		6O7G 6/3
		6R7G 7/6
		6R7GT 8/-
		6S7 6/-
		6S7G 5/6

6S7GT	6/-	35Z4GT	7/-	1626	4/6
6S8	5/-	3944	6/-	1629	4/6
6SH	5/-	53A	3/-	7193	1/9
6S17	6/9	58	6/-	6475	5/-
6S17G	6/6	59	6/-	8010AR	22/6
6S17G	5/6	71A	4/6	8013A	10/-
6S17GT	6/9	77	6/-	8020	6/-
6S2GT	4/6	78	7/-	9001	5/-
6S7	6/6	80	6/3	9003	5/6
6S7	6/6	82	8/-	9004	4/-
6S7	5/-	83V	12/-	9006	4/-
6S7	6/-	84	12/6		
6S7	5/6	85A1	12/-		
6S7	6/-	89	6/-		
6S7	7/6	2101F	3/-		
6S7	7/6	210VPT	6/-		
6S7	2/6	217C	17/6		
6S7	2/6	446A	14/-		
6S7	8/6	705A	17/6		
6S7	5/6	715B	97/6		
6S7	7/6	717A	8/6		
6S7	6/6	723A/B	45/-		
6S7	7/6	801	30/-		
6S7	7/6	803	22/6		
6S7	7/6	805	30/-		
6S7	22/6	807AMER	5/3		
6S7	2/-	807BR	3/9		
6S7	3/6	808	8/-		
6S7	4/6	813	67/6		
6S7	6/6	815	80/-		
6S7	4/9	816	30/-		
6S7	6/9	829A	30/-		
6S7	5/6	843	7/6		
6S7	7/6	861	15/-		
6S7	6/6	866A	10/-		
6S7	6/6	872A	35/-		
6S7	7/6	930	8/-		
6S7	8/6	954	2/-		
6S7	5/6	956	2/-		
6S7	30/-	1619	5/-		
6S7	5/6	1625	6/-		

Cathode Ray Tubes

3BP1	25/-
5BP1	35/-
5CP1	42/6
5CP7	45/-
VCRX258	(with scanning coil)

Photo Tubes

GL16	12/6
------	------

Special Valves

2J31	45/-
3A/1481	45/-
3J/170/E	£35
3J/192/E	£37.10
723AB	45/-
726A	27/6
ACT25	40/-
CV691	60/-
KR3	45/-
VX7110	15/-
VL417A15	1/-

AND MANY OTHERS IN STOCK, INCLUDING CATHODE RAY TUBES AND SPECIAL VALVES. All U.K. Orders below 10/-. P. & P. 1/-; over 10/-, 1/6; Orders over £2 P. & P. free. C.O.D. 2/- extra. Overseas Postage extra at cost.

T.C.S. Receivers. Made by Collins of U.S.A. In fully guaranteed working condition. 1.5-12 mcs. Line up: 12SA7 (1), 12SQ7 (1), 12A6 (2), 12SK7 (3). Power requirements 12 v. L.T., 225 v. H.T. £11.10.0. Carriage 12/6.

Specially Built Power Pack for the above. 230 v. A.C. mains, including 6X5GT valve, £3.15.0. Carriage 5/-.

Transmitter/Receiver No. 22. 2 mc. to 8 mc. Built almost exactly as No. 19 set but much more economical in battery consumption. Complete in fully working condition with power pack for 12 v., Headgear and Microphone assembly and Key, £9.19.6. Carriage 15/-.

Brand new original spare parts for AR88 Receivers. Please write your requirements.

Low Resistance Headphones, brand new, type CLR, 5/-. Balanced Armature, 7/6. P. & P. 1/-.

Telephone Handset. Standard G.P.O. type, new, 12/- P. & P. 1/6.

S.C.R. 522 Receivers (BC624) 100-156 Mc/s., including all valves, 25/- P. & P. 5/-.

H.T. Chokes made by Bendix Radio (U.S.A.), 3 Henrys 0.600A D.C. 25 ohms D.C. resistance 18,000 v R.M.S. 60 cycle test £1.12.6. P. & P. 6/- Ditto 10 Henrys 250 A. D.C. 90 ohms resistance 1,500 v. R.M.S. 60 cycle test 16/6. P. & P. 3/6.

Throat Microphones T 30 (U.S.A.), 3/6. P. & P. 1/6.


Carbon Inset Microphone, G.P.O. Type 2/6. P. & P. 1/-.

Transmitter Cabinet with door at back. 7 1/2 in. high, 29 in. wide, rack fitting etc. £17.10.0. Carriage £1.

Variometers for W/S No. 19. Fully tested and working, 12/6. P. & P. 2/6.

NEW PRODUCT OF TAYLOR

Model 127A
Pocket size
meter. Sensitivity
2 0 0 0 0
o.p.v. D.C.
1,000 o.p.v.
A.C. C. 2 0
Ranges.
D.C. current
50µA to 1
amp.
D.C. volts
0.3 v. —
1,000 v.
(2.5 kV by
probe).
A.C. volts
1 0 v. —
1,000 v.
3 resistance
ranges from
0-20 megohms (self contained). Meter
40µA 3 1/2 in. arc. Accuracy D.C. 3 %
A.C. 4%, ohms 5%. Dimensions 5 1/2 in. x
3 1/2 in. x 1 1/2 in. weight 14 ozs. Price £10
complete with instruction manual, test
plugs and clips. Leather case £1.12.0 extra.
Filament Transformers. Primary
0-190-210-230-250 v. 50 C. Sec. 1.25 v.
C.T. at 10 amps.; 2.25 v. C.T. at 10 amps.;
3 10.5 v. C.T. at 11 amps., 4,000 v.
insulation. Price £2.19.0. P. & P. 5/-.
Primary 0-190-210-230-250 v., 50 C.
Sec. 1 10 v. C.T. at 4.5 amps.; 2 10 v.
C.T. at 4.5 amps., 4,000 v. insulation
£1.16.0. P. & P. 5/-. Primary 230 v.
50/60 c. 67 v. amp. Sec. 1 6.3 v. 1-6
amps.; 2 6.3 v. C.T. 3 amps.; 3 6.3 v.
C.T. 3 amps.; 4 6.3 v. C.T. 3 amps.
£1.12.0. P. & P. 5/-.
Ferranti Transformer. Oil cooled,
20/19.5 K.V.A., 3 phase, 50 cycles. Primary
360/380/400/420/440 v. Secondary 2,700/
2,900/3,100/3,300/3,500 v., 2.1 amp.
Voltage regulation by simple switches on
primary and secondary. Weight 1,150 lbs.
Price £125.0.0. Carriage at cost.

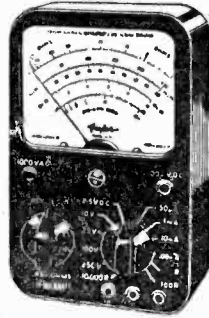

Driver Transformers. Primary 500 ohms imp. Sec. to match two 805 in push-pull. £1.7.6. P. & P. 5/-.

Rocary Transformer. 171 W 12 v. input, 1,600 v. 100 mA output, 30/- P. & P. 7/6.

Insulation Test Meter. Testing voltage adjustable up to 6,000 v. D.C. Mains supply 180/250 v. In wooden case £25. Carriage 10/-.

Vibrator Unit. 12 v./60 v. 35 mA. Exceedingly well filtered and smoothed, excellent for car radios. New including 6X5G valve and vibrator, 17/6. P. & P. 5/-.

Moving Coil Round Hand Microphone No. 13. 2 1/2 in. dia. with press switch. 12/6. P. & P. 1/-.

Complete Set of Strong Aerial Rods (American). Screw-in type MP49, 50, 41, 52, 53, total length 15ft. 10 in., top diameter 0.615 in., bottom diameter 0.185 in., together with matched aerial base. MP37 with ceramic insulator, ideal for car or roof insulator, £2.10.0, post free.

HRO Mains power pack, input 115/250 v. A.C.; output 250 v. 0.75 mA and 6.3 v. 3.5 amps. £3, inc. carr.

Avomins. Leather case. With leads, fully tested and guaranteed. W/ly batteries. 2,000 volt, D.C. £2.19.6. P. & P. 2/6.

Output Transformer in screening can give 9 different ratios 10:1 up to 120:1 for battery receivers or any high resistance pentodes used as output valves, 6/6. P. & P. 1/6.

P. C. RADIO LTD.
170 GOLDHAWK RD., W.12
Shepherds Bush 4946



Solve
that
Circuit
trouble!

PIFCO
Radiometer

Not only circuit tests but everything electrical can be tested with this handy compact meter. Tests H.T. & L.T. Valves, components, electrical appliances and car lighting systems, etc. May be used on A.C. & D.C. mains.

See the Radiometer at your dealer or write for illustrated leaflet to:—

PIFCO LTD.
WATLING STREET · MANCHESTER · 4

only
32/6
complete

NEW, GUARANTEED, PERFECT
RED 3/- SPOT
TRANSISTORS

WHITE SPOT, 4/6; GREEN/YELLOW, 5/6.
GET3, 8/-; OC70, 9/-; OC45, 16/6; TSL, 4/-; TS3, 12/6.
CRYSTAL DIODES, 1/-; Mullard OA81, 4/-; OA70, 4/-.
BRIMAR GD4 (GEX34), 4/-.

SET OF 5 TRANSISTORS & ONE CRYSTAL DIODE
(As specified in the Weyrad Circuit.) XA102, XA101, XB104.
Matched Pair XC101, plus one Crystal Diode. 58/6.

MULLARD: OC16, 54/-; OC44, 28/-; OC71, 14/-; OC72, 17/-; 2/OC72 (matched pair), 34/-; OC170 (Short Wave), 50/-; OCP71 (Photo Electric), 50/-.

EDISWAN: XA101, 23/-; XA102, 26/-; XA103, 15/-; XA104, 18/-; XB104, 10/-; XC101, 16/-; 2/XC101 (matched pair), 32/-; XA131, 35/-; 2/XC131 (matched pair), 34/-.

TRANSISTOR HOLDERS, 1/3. ARDENTE sub min., 1/8. FERRITE ROD: 6 x 1/2 in., 2/9; 3 x 5/16 in., 1/6.

CONDENSERS: Miniature, 0.01/150 v., 11d.; 0.1 mfd./100 v., 1/2; 0.035/200 v., 10d.; Standard size 0.01/1,000 v., 6d.; 0.1/500 v., 10d.;

Wire ended, 16 mfd./450 v., 2/4; 16-16/450 v., 4/-; 8-8/450 v., 2/9; 8-16/450 v., 2/9; 50 mfd./50 v., 1/9; 25 mfd./25 v., 1/9; 100 mfd./6 v., 2/3. Miniature, 25 mfd., 2/8; 50 mfd., 2/3; 8 mfd., 2/3; 2 mfd., 1/9.

SUB MINIATURE: 32 mfd., 25 mfd., 16 mfd., 8 mfd., 2 mfd. All 3/6; 100 mfd., 2/9.

TUNING CONDENSERS: Solid, dielectric, 500pF (0.0005 mfd.).

4/-; 300 pF, 3/9; 100 pF, 3/-. Miniature, 500 pF, 5/-.

RESISTORS: All values 10% ± w. 6d.; 1 watt, 9d.

BEGINNERS 1 VALVE: Circuit and plans, 11d. Kit, 35/-.

COILS: Repanco DR2, 4/-; DRX1, 2/6; Teltron HAX, 3/-.

All complete with circuits.

H.R. HEADPHONES (for Crystal Transistor or Valve Sets): Diploma, 17/6; IVALK, 14/-.

TAPE—SUPERIOR QUALITY: Standard PVC Base, 600ft. on 5in. spool, famous make, 17/6.

CONNECTING WIRE: Six assorted colours, 1 yard of each colour, 1/9; 2 yards of each colour, 2/9; 10 yards of each colour, 10/6.

OAKFIELD RADIO
THE TRANSISTOR PEOPLE

Mail Order Only

121 Macclesfield Road, Hazel Grove,
Stockport, Cheshire

THE
Skyranger
UNIVERSAL
CAR AERIAL

★ FITS ON WING SCUTTLE,
ROOF OR BOOT.


Heavy Duty **21/-**
Chrome on Brass

COMPLETE WITH 6ft. CABLE
STAN WILLETTS

43 Spon Lane,
West Bromwich, Staffs.

Tel.: 2392

Trade inquiries invited

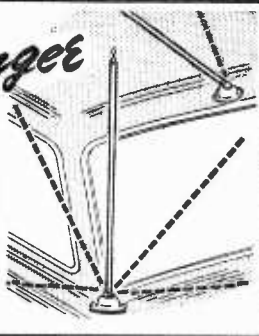

A television course
for you to study at home

Entirely new! Practical!
Bang up to date!

THE FAMOUS BENNETT COLLEGE OFFERS YOU THIS

An entirely new course of study based upon up-to-date techniques has now been prepared by The Bennett College.

The course is non-mathematical, and contains clear diagrams, starting from the very beginning (even including the basic principles of sound radio receivers, if desired) and covering all that you need to know!

This is what you've been looking for! A home-study course includes: production

of the signal, scanning and reproduction of picture from signal. Aerials, types and purpose. The cathode-ray tube. Time-base oscillators, and output circuits. Synchronisation. Video frequency amplifiers. The TV tuner, turret, incremental, etc. Television test gear. Television faults.

For more details, fill in the coupon below. Your studies cost little, the book you need is included in the cost.

To THE BENNETT COLLEGE (Dept. J104 TV Sheffield)

Please send me details of the new
TELEVISION SERVICING COURSE

NAME


ADDRESS

AGE

If you use a PARKING LIGHT you need **"LITON"**
AUTOMATIC PARKING LIGHT SWITCH

Controlled by a photoelectric cell sensitive to daylight. Turns lights on at dusk, off at dawn, AUTOMATICALLY!!!
A MUST for the MOTORIST without a garage. 6 or 12 volts.

Easy to build and install.

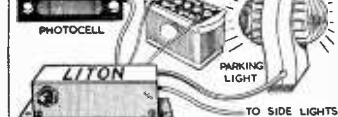

Kit of Parts

Ready Built 52/6

57/6

Photocells only

unmounted 12/6

mounted 25/-

also PHOTOELECTRIC BURGLAR ALARM—GARAGE DOOR OPENER—LIGHT SAVER. Kit of parts £4.12.6. Built: £5.10.0. Full details and circuit of any project—6d. stamp please.

"ST. JOHN'S RADIO"

156 St. John's Hill, London S.W.11

VALVES NEW! TESTED! GUARANTEED!

SETS 1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94... any 4 for 19/6
 DAF96, DF96, DK96, DL96... 4 for 27/6
 6K7G, 6K8G, 6Q7G, 6V6G, 6X5G, or 5Y3G ... 5 for 27/-

1A7GT	12/-	6L18	12/3	25Z4G	7/6	EBF89	8/9	EZ41	7/8	R19	13/6
1D5	8/-	6LD20	8/-	25Z6GT	9/6	EBL21	13/6	EZ30	6/3	T41	9/6
1NEGT	10/-	8P25	9/-	30C1	7/3	EC92	11/-	EZ81	7/-	U25	13/-
1NEGT	10/-	6Q7G	6/9	30L1	7/9	EC91	8/-	FW4500	5/5	U26	10/-
1R5	8/-	6Q7GT	9/6	35L2GT	9/6	EC92	6/6	GZ32	9/-	U50	6/9
1S4	8/6	6SL7GT	6/8	35L4GT	6/6	EC93	7/-	KT33C	7/-	U52	5/3
1S5	5/3	6SN7GT	4/9	35Z5GT	8/6	EC94	8/9	KT41	14/6	U76	6/6
1T4	4/-	6U4GT	11/-	50CD6G	26/9	EC95	8/3	KT44	9/-	U74	6/-
1L5	6/6	6V6G	5/-	50L6GT	8/9	ECF90	9/6	KT81	10/-	UABC90	7/9
3A5	10/8	6V6GT	6/6	185T	25/-	ECF82	8/6	KT63	6/6	UAF42	9/6
3C4	7/6	6X4	5/-	AZ31	9/6	ECH21	13/6	KT71	8/6	UBC41	7/9
3E4	6/-	8X5GT	5/6	B36	8/9	EC95	6/9	MU14	7/6	UBF80	9/6
3V4	7/-	7B7	7/6	CL33	13/-	ECH42	8/9	MX40	9/6	UBF89	9/6
5B4G	5/3	7C5	7/6	DAC92	10/-	ECH61	8/-	1R8	7/6	UBE21	13/6
5V4G	9/6	7C8	7/6	DAF93	7/3	ECL80	7/3	PCC84	7/9	UCC24	12/9
5Y3GT	9/9	7H7	7/6	DAF96	7/6	ECL82	10/-	PCC89	12/-	UCC85	7/6
5Z4G	7/9	7S7	9/9	DCC90	10/6	EP39	4/6	PCC80	7/3	UCF80	14/-
6L5	3/8	7Y4	7/-	DF33	10/-	EP41	8/3	PCF82	8/-	UCH21	13/6
6L5G	3/6	10C1	14/6	DF91	4/-	EP42	9/6	PE4	8/-	UJ42	8/6
6A95	8/-	10C2	17/6	DF96	7/8	EP80	6/6	PCL83	7/-	UCH81	8/6
6A76	7/3	10F1	15/6	DH76	5/6	EP85	6/6	PCL84	8/-	UCL82	10/9
6E8A	6/-	10P13	14/6	DH77	7/3	EP86	10/-	PENA4	11/-	UCL83	14/-
6E8B	6/-	12AH8	10/-	DK32	12/-	EP89	7/6	PEN36C	8/6	UP41	8/9
6E8C	6/6	12AT7	5/9	DK91	6/-	EP91	3/6	PEN45	9/-	UF42	6/6
6E8D	6/6	12AU7	6/6	DK92	8/6	EP92	4/6	PEN46	5/6	UF39	7/-
6E8E	9/9	12AX7	7/-	DK96	7/6	EL33	10/-	PL36	11/6	UL41	8/9
6E8F	9/9	12BA6	8/-	DL33	9/-	EL38	21/6	PL38	14/6	UL84	7/6
6E8G	8/6	12K7GT	5/6	DL35	10/-	EL41	8/6	PL81	9/6	UR1C	8/6
6E8H	8/6	12K8GT	11/6	DL82	8/6	EL42	9/6	PL82	7/6	UY21	11/3
6E8I	14/6	12M7GT	6/6	DL94	7/-	EL84	7/-	PL83	7/6	UY41	6/6
6F8G	6/6	12Z3	7/6	DL96	7/6	EM34	8/6	PL84	10/-	UY85	6/6
6F13	12/6	1487	16/9	EABC80	7/-	EM80	9/-	PY32	11/-	VP4B	9/6
6E14	17/6	19A95	7/6	EAF42	8/6	EM81	9/-	PY80	7/6	VP41	6/6
6E16	2/6	20E2	17/6	EB91	8/6	EM84	10/-	PY81	6/3	W76	5/6
6K7GT	5/-	20L1	17/6	EB93	3/9	EY33	8/6	PY82	7/-	W77	4/6
6K8G	6/9	25A6G	8/-	EBC41	8/6	EY86	7/9	PY83	7/9	X56M	11/6
6L1	15/-	25L6GT	9/-	EBF80	8/-	EZ40	6/9	PZ30	17/-	Z77	3/6

READERS RADIO
 24 COLBERG PLACE, STAMFORD HILL
 LONDON, N.16 STA. 4587

PADGETTS RADIO STORE

40 MEADOW LANE, LEEDS 11

Tel.: Cleckheaton 2866

Brand New Boxed American R.C.A. Transmitter and Receiver. Type CRV 52093A.TX. Type CRV 49083B.RX. Complete with five valves but less Valves! total weight 112 lbs. Instruction Manual free with the Sets. £4.0.0, carriage £1.5.0.

Special Valve Offer. 12 EF50 Valves. Removed from new sets. 6/6. Post free.

P.M. Speakers in perfect condition, as new. Removed from TV sets Rola, Celestian, Jodmans, E.C.T. 7 x 4, 6 x 4, 10". Small Phillips 10", 6in. Round 6". Post on Speakers. 2/6 each.

New TV Co-Axial Cable. Multi-strand, best make, 6d. per yard. 50 yards 20/-, 100 yards 37/6. All post free.

Valves Removed from TV Sets. All tested and are as good as new. 3 months' guarantee. Here are just a few. Send 3d. for up to date list.

EF90, 2/6. ECL80 5/-, 6SL7 2/9, 6SN7 2/9, PY81 5/-, PL81 5/-, 10P1 3/-, 20D1 5/-, 10P13 5/-, 10C2 3/-, 20P4 5/-, 185T 8/6.

Transmitter Type 1154, Model M. Complete with all valves and meters. Clean condition. 16/-, carriage 12/-.

Tube Unit Type 116. Complete with VCR97 tube. 7 EF50 Valves ECT. Sets in very good condition. 25/-, carriage 7/6.

Receiver Type 3645. The up to date 1355. Same valve and coil line up, less 5U4 and 6X5. 12/-, carriage 7/6. Sets in very good condition.

Special Offer. B.B.C. and I.T.V. 12in. good working order. Perfect tubes, not boosted TV sets. Bush, Pye, Ekco, Coscor, Ferguson, Ultra. £4.10.0, carriage 17/6. Tube in separate case.

REPANCO HIGH GAIN COILS

Dual Range Crystal Set Coil. Type DRX1.....	2/6
Dual Range Coil with Reaction. Type DRR2.....	4/-
Matched Pair Dual Range T.R.F. Coils, Type DRM3, pair.....	8/-
Pair Dual Range Supermet Coils, Type SH4, pair.....	8/-
Miniature Iron Dust Coiled Coils. Type "R".....	
Range Aerial H.F. Osc. 600-2,000m. RA1 RHF1 R01	
190-550m. RA2 RHF2 R02 each 3/3	
70-230m. RA3 RHF3 R03	
15-50m. RA4 RHF4 R04	
Ferrite Rod Aerial, Dual Range Type FR1.....	12/6
Miniature I.F. Transformers, Type MSE (465 Kc/s), pair.....	12/6
Standard I.F. Transformers, Type TCG (465 Kc/s), pair.....	13/6

Send S.A.E. for latest Repanco Component Catalogue.
RADIO EXPERIMENTAL PRODUCTS LTD.
 33 MUCH PARK ST., COVENTRY
 Tel. 62572

Morse Code operating . . .

. . . as a PROFESSION

45 years of teaching Morse Code is proof of the efficiency of the Candler system.

Send 3d. stamp for Payment Plans and full details of all Courses.

CANDLER SYSTEM CO. Dept. 510
 52b Abingdon Road, London, W.8
 Candler System Co., Denver, Colorado, U.S.A.

DID YOU KNOW

COYNE'S NEW

TROUBLE-SHOOTING SERIES TAKES HEADACHES OUT OF ALL SERVICING PROBLEMS!



Pin-Point
TV troubles in 10 minutes

Find the exact sound or picture trouble in ANY TV set from 700 possibilities! 300 pages; 300 diagrams; check charts! 31/6, Postage 1/-.

Pin-Point
Transistor troubles in 12 minutes



Trouble-shoot every type of circuit in ALL transistorized equipment! 525 pages; hundreds of illustrations; 120 check charts, 47/6, postage 1/4.

Simple Check Chart System Saves Time

These amazing practical handbooks with ENTIRELY NEW METHOD show you how to find the trouble in ANY TV, or transistor circuit FAST! Index tells you where to look; famous Check-Charts help you to pin-point the exact trouble in minutes! These on-the-job books quickly pay for themselves in profitable new business and valuable time saved!

SEND NO MONEY

Just mail coupon (or free trial). After 7 days send only low price or return books and pay nothing! If you keep both books send only £1 after 7 days and £1 a month until 73/-, plus 1/- postage is paid. If ordering one book, pay one half after seven days and the other half in 30 days.

FREE TRIAL OFFER Mail Coupon Now!

Mail Order Division, **SIM-TECH BOOK COMPANY**, Gater's Mill, West-End, Southampton, Hants.


- Rush 2-book PIN-POINT Series for 7-day FREE TRIAL per offer.
- I do not require both books, please send me the following book as per offer.
- TRANSISTORS, 47/6, plus postage.
- TV TROUBLES, 31/6, plus postage.

Name

Address

City..... County.....

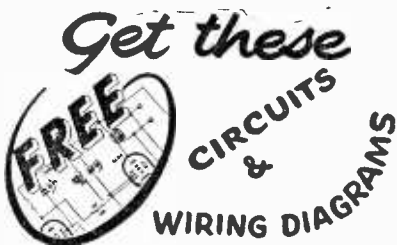Check here if enclosing full price; we pay postage. Same 7-day money-back guarantee.



T.R.F. Circuits
Battery Circuits
Portable Circuits
S'het Circuits
Mains Circuits
Filter Circuits

The selection of circuits
continually changing and
being added.

Send Postage 1/- (stamps)

OSMOR COILS are regularly used and recommended by designers writing in "Practical Wireless," "Wireless World" and "Radio Constructor." Why not follow the experts?

"Q Coils" All ranges
Potted Coils
F.M. COILS
TAPE COILS Speaker Cross-over Coils
ROD AERIALS
Coils and I.F.s for Transistor Circuits
SUB-MINIATURE COILS
Midget I.F. Trans. With ferrite cores



418 Brighton Road,
South Croydon.

Telephone: CRO 5148/9

VHF RECEIVER R1392D. Covers 95-156 Mc/s (2-3 metres). In-very good condition, complete with all 15 valves, circuit diagram, and air tested. Power supply required HT 250 v. at 80 mA., LT 6.3 v. at 4 A (P.U. Type 23A was used) 75/6 plus 10/6 carr.

MINIATURE 373 I.F. STRIPS.—Por F.M. tuner described in P.W. with 3 of EF91, 2 of EF92 and EB91. A fresh release enables us to offer these once again. BRAND NEW with circuit and full P.W. Reprint, 35/-, OR less valves, 12/6. Post either 2/6.

RECEPTION SET TYPE 208. Covers 10-60 Mc/s (5-30 metres). Containing 6 valves, 2-6K8G, 2-EF39, 7Q6G, 6V6G, metal rectifiers, built-in A.C. mains pack and 6 v. vibrator pack. Built-in 6in. speaker. Muihead slow motion drive, B.F.O. and R.F. stage, 2 Mc/s I.F. freq. Phone jack. Very good condition and air tested. Limited number 27.19.6, carr. 15/6.

R-1155-B. with latest drive, first-class condition, 29.19.6.
Mains Power Pack, 26.10.0. Data book, 1/3 post paid.

GIANT COMPONENT PARCEL. Contains 100 μ and 1 watt resistors, 50 HI Stab resistors, wire-wound resistors, carbon and W/W pots, 100 capacitors (mica, paper, Sprague, bias, variable, etc.), valveholders, tag strips, metal rectifiers, sleeving, etc. All components are unused. **GUARANTEED VALUE, 26/-,** plus 2/6 post.

CR100 COMMUNICATION RECEIVERS. Covers 60 Kc/s—30 Mc/s in 6 bands, 11 valves, 2 R.F. and 3 I.F. stages. Crystal gate, B.F.O. etc. Ready for 200-250 v. A.C. mains 21 watts output for 3 ohms speaker. **SUPERB CONDITION AND OUTSTANDING PERFORMANCE FOR ONLY 221.** S.A.E. for illustrated details.

AVOMETER MODEL 'D' 34 range testmeter. D.C. volts to 1.500 v. (10 ranges). A.C. volts to 1.500 v. (8 ranges). D.C. current to 30 A (8 ranges). A.C. current to 15 A (6 ranges). Ohms 0-1 k, 0-10 k. A robust instrument with 5in. mirror scale and cut out. With battery and leads. Guar. 28.19.6. Post 3/6.

G.E.C. SELECTEST. 34 range testmeter. D.C. volts to 1.500 v. (10 ranges). A.C. volts to 1.500 v. (8 ranges). D.C. current to 15A (6 ranges). A.C. current to 15A (6 ranges). Ohms 0-1k, 0-10k. A robust instrument with 5in. mirror scale and cut out. Complete with battery leads. Fully tested, 27.10.0. Post 3/6.

RCA AR-88 SPEAKERS. 3 Ω 8in. P.M. speaker in heavy gauge black cracked steel cabinet 11 x 10 x 6in. with rubber feet. A SUPER QUALITY unit. BRAND NEW, FOR ONLY 45/- Post 3/6.

CHARLES BRITAIN (RADIO) LTD.

11 Upper Saint Martin's Lane, London, W.C.2

TEmple Bar 0545

Shop Hours 9-6 p.m. (9-1 p.m. Thursday). Open All Day Saturday

NEW VALVES!

Guaranteed Set Tested
24 HOUR SERVICE

1R5, 1R5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94, SET of 4, 18/6.
DAF98, DF98, DK98, DL98, SET of 4, 26/6.

1D5	7/6	DL33	8/6	PCF82	7/6
1R5	5/6	DL35	9/6	PCL82	7/6
1S5	4/9	DL92	5/11	PCL83	10/6
1Y4	3/11	DL94	6/9	PCL84	7/6
3S4	5/11	DL96	6/11	PL36	10/9
3V4	6/9	EB41	7/6	PL38	14/-
5U4G	4/9	EBF80	8/-	PL81	8/9
5Y3GT	5/9	EBL21	12/6	PL82	7/-
5Z4G	7/6	ECC81	5/3	PL83	7/-
6K7G	2/-	ECC82	6/-	PL84	9/6
6K8G	5/3	ECC83	6/6	PY32	10/3
6Q7G	5/9	ECC84	8/3	PY80	7/6
6SL7GT	6/-	ECC85	8/-	PY81	5/9
6SN7GT	4/6	ECC86	9/-	PY82	6/3
6V6G	4/9	ECC82	9/-	PY83	7/3
6V6GT	6/3	ECH21	12/6	U25	12/6
6X5GT	5/-	ECH42	8/-	U26	10/-
12K7GT	5/3	ECL80	7/9	UABC80	7/6
12K9GT	11/-	EF41	7/9	UP42	8/9
12Q7GT	5/3	EF80	5/-	UBC41	7/3
35L6GT	9/-	EF85	6/-	UBF80	8/6
35Z4GT	6/-	EF86	9/9	UCC85	7/-
AZ31	8/9	EF89	7/-	UCH21	12/6
B36	6/3	EL41	7/3	UCH22	7/9
CL33	12/6	EL84	6/6	UCH81	8/-
DAC32	9/6	EY51	7/11	UCL82	10/6
DAF91	4/9	EY86	7/9	UCL83	13/-
DAF98	6/11	EZ40	6/3	UF41	7/9
DF33	9/6	EZ41	7/-	UF42	6/3
DF91	3/11	EZ80	6/-	UF89	6/6
DF96	6/11	EZ81	6/9	UL41	7/3
DH77	6/-	GZ32	8/9	UL84	7/-
DK32	11/3	MU14	7/-	UT21	11/-
DK91	5/6	PCC84	7/3	UY41	8/-
DK92	8/-	PCC89	11/6	UY85	6/3
DK98	6/11	PCF80	6/9	VP48	8/6

Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra. Any C.O.D. Parcel 2/6 extra. Office address, no callers.

GERALD BERNARD
CARR MANOR AVENUE
LEEDS 17

TRANSFORMERS

Suppliers to B.E.C., I.T.A. and leading radio manufacturers, single or long runs. Prompt delivery home and export.

Rewinds to all makes

H. W. FORREST (Transformers) LTD.

Shirley, Solihull, Warwickshire
Tel. SHIRLEY 2483

"GLOBE-KING"

WORLD-FAMOUS KITS AND RECEIVERS for the Radio Amateur and S.W. Listener. Catalogue Free, enclose stamp for Postage. Kits from 79/6 at your dealers, or direct from

JOHNSONS (RADIO)
ST. MARTINS GATE, WORCESTER

RES/CAP. BRIDGE 38/-
p. & p. 2/-

Checks all types of resistors, condensers 6 RANGES

Built in 1 hour. Direct reading

READY CALIBRATED

Stamp for details of this and other kits.

RADIO MAIL (Dept. DP)

Raleigh Mews, Raleigh Street, Nottingham

A 3d. stamp will bring you a copy of our latest

RADIO & TELEVISION COMPONENT Catalogue

JAMES H. MARTIN & CO.
FINSTHWAITE, NEWBY BRIDGE
ULVERSTON, LANCs.

12in. SPEAKER AND 5in. TWEETER by leading manufacturer. 75/-. This is less than half list price.

CUT PRICE TOOLS. 5in. side cutters' 5/6. 5in. plated round nose tapered pliers' 5/6. 7in. flat-nosed tapered pliers, 8/6. Pocket neon testers with retractable screwdriver, 5/-. 7in. combination pliers, 6/-. 8in. Steel Block Planes 11in. blade, 10/6. FULL SIZE H/S TWIST DRILLS. Set 7—1 to 1in. in Wallet, 6/-. Smaller size sets, 4/-. Set 13, 9/6. Set 17, 1 to 1 1/2 in., 15/6.

TRANSFORMERS. 230/50 v. 1 a. and 250/28-32 v. 4 a., 32/6 each.
STUDIO 0 CARTRIDGES. 21/-.
PAXOLIN PANELS. 12 x 6 x 1in., 3/6.
PAXOLIN TUBING. 1 1/2 x 3/16 x 72in., 17/6.

OUR FAMOUS TRANSFORMERS. Input 200/250. Output tapped 3 to 30 v. 2 a. or 5 v. 11, 17 v. 5 a. Each 24/6.

F.W. METAL RECTIFIERS. 126 volt, 1 a., 7/6; 3 a., 13/-; 4 a., 17/6; 6 a., 27/6; 24 v. 2 a., 23/6.

TOGGLE SWITCHES DPDT, 3/6.
MICRO SWITCHES. Make & Break, 5/6.
MAINS TRANSFORMER & RECTIFIER. Output 12 v. 1 a. D.C., 19/6; 30 v. 2 a., 33/6.

NICKEL NIFE BATTERIES. 1.2 v. 2.5 a. Size 3 x 2 1/2 x 1 1/2 in. 6/-, or 3 for 16/-, 4 for 21/-, practically everlasting.

EX WD MORSE KEYS. 3/6, 6/6 and 8/6.
RELAYS. We hold large stocks. Any contact combination and operating coil voltage supplied from 3-.

KEY SWITCHES from 3/-.

12 v. RELAYS. With 2 or 4 make contacts, 6/-, 2 for 11/6, 3 for 16/-, 4 for 21/-.

AMERICAN MADE P.V.C. TAPE. Finest quality. 800ft. reels, 19/-.

All items new, guaranteed and post free except where stated.

Lists/sent on request. Post orders only to THE

RADIO & ELECTRICAL MART
c/o P.O. BOX 15, G.P.O., TUNBRIDGE WELLS, KENT

TRANSISTORS

Red Spots, 3/3; White Spots, 4/-; Yell/GR, 5/-; Ediswan XB104, 8/6; XA103 (4 Mc/s), 10/-; XA104 (6.8 Mc/s), 12/-; Mullard OC70, 14/-; OC71, 14/-; OC72, 17/-; OC44, 26/-; OC45, 23/-; OC170 (70 Mc/s), 35/-; Newmarket V15/10P (10 watt power), 17/6; Diodes, 1/- and 2/6; Mullard Diode, 4/-; Electrolytics (sub. min. 15 v.) 2, 4, 8, 50, 100 μ f, 3/- ea.; Ardente Trans. D239, 8/6; D240, 8/6; D131, 12/6; D132, 12/6; T1079, 12/-; D167, 12/-; Headphones L.R. 8/6; H.R. 17/6; Resistors 10% col., 6d.; 5% col., 1/-; Desk Mike 31/6; Balance inserts (use as earpiece of speaker), 2/6; Transformer 250.0-250 v. 60 mA, 6 v. and 5 v., 15/-; Westalite Contact Rectifier 250 v., 60 mA, 7/6; Condenser, V. T.G. 0.0005, 6/6; 6 v. Vibrator Supply 120 v. 60 mA out, 12/6. Garrard Portable Record Player, cabinet, battery turntable 45 r.p.m. and pick-up; takes transistor amplifier, £3.10.0, plus carr. 3/3. Real bargain. Limited quantity. **TERMS**—Cash with order. Post extra, excess refunded. Morco Reflex Rx, best 2-transistor Receiver. Send 8d. stamps for notes.

MORCO EXPERIMENTAL SUPPLIES
8 & 10 Granville Street, Sheffield 2
Tel.: 27461

DO IT YOURSELF

Build your own electronic keyboard and play everything! Send for free leaflet. Guitar, cello, flute and trumpet are all easy. Write now...

C. & S., 20 Maude Street, Darlington, Co. Durham

BENSON'S BETER BARGAINS

MORSE KEY with buzzer, on board, wired for 41 v. battery, 8/6 (p.p. 1/6). **TELE "F"** intercom, sets, good condition, pair 66/-, post rec. G.L.B. **METERS** (100/4) with two centz-zero movements, 600 and 400 μ A, 8/6. **RELAYS**, 6/12 v., 2 heavy make contacts, on base, 3/6; or superior, bigger type, 7/6. **TRANSFORMERS**, Open, upright, input 200/260 v. Outputs:—250.0-250 v., 150 mA, 5 v., 3 A. and 8.3 v. 5 A., 25/-; input 110/230 v. Outputs:—6 v., 2 A. twice, shrouded, 10/6. Potted, "C" core: Input 250 v. Outputs:—6.3 v., 0.3 A. (1A. actual), twice, 8/6; Outputs: 510.0-510 v., 275 mA, 375.0-375 v., 83 mA, 5 v. 3 A., 4.3 v. 7 times (17 A.), 45/-; **CONDENSERS**, block, paper: 8 mfd. 250 Vv. 4/-; 600 Vv 8/-; 4 mfd. 2 kv. v. 7/6; 600 Vv. 8/6. Switch fuse splitter, DP. 15 A. 15/-; Panel fuseholders, 1/3; Panel Lampholders (Indicators), 1/6. **MONITOR 56**, triggered oscilloscope, comprising Indicator 248 and Power Unit 675, 250 v. A.C. input, with cables and controls. Cathode probe unit extra, 17/6. £8/10/- (Retail 15/-). **HEADPHONES**, CLR. 7/6. CR100 Noise Limiter assemblies with valve, 8/6. **NEW M.C.A. METERS**, 3 1/2 in. round dial, 50 μ A, 70/-; 200 μ A centre zero, 50/-; 1 mA, centre zero, 45/-; 1 mA, 55/-; 2 1/2 in. 1 mA, 22/6; 2 1/2 in. 300 mA, each 8/6; 2 1/2 in. M.1 20 v. A.C., 8/6; 300 v. A.C. 2 1/2 in. 15/-; **VIBRATORS**, Mallory G834C 12 v. 4-pin. 7/6; 6 v. 5-pin reversible, 7/6. R1155B, good condition, tested with handbook, 25 (Retail 10/-). **DRIVES**: slow-motion Avinability 200:1 ratio, scaled 0-100, 5/6. R1155 S.M. "N" type, new, 10/6. **VIBRAPAK**, 6 v. D.C. to 250 v. 60 mA, smoothed case, 22/6, 12 v. to 260 v. 60 mA, 21/- (p.p. 3/6). **DYNAMOTORS** (post 3/6), 12 v. to 250 v. 60 mA, 11/6; 6 v. to 250 v. 60 mA, 11/6. **CHOKES**, LP 10 H, 200 mA, 8/6; 100H, 60 mA, 8/6; 9H, 100 mA, 5/6; 10H, 250 mA, 12/6; Potted 10B, 100 mA, 7/6; "C", 5H, 400 mA, 10/6. R.F.E.27, good cond., 18/- (p.p. 3/6). **LIST AND ENQUIRIES** S.A.E. please. Terms, C.W.O. Postage extra. Imm. despatch. *Callers and post: W. A. BENSON (PW), 136 Rathbone Road, Liverpool, 15. SEP 6853. Callers: SUPERADIO (Whitechapel) Ltd., 116 Whitechapel, Liverpool, 1. ROY 1130.*

A.R.R.L. RADIO AMATEURS HANDBOOK 1960

New edition, 32/8. Postage 1/9
Fundamentals of Semi-Conductors by Scroggie, 23/-, postage 1/-
Stereo Handbook by Briggs, 10/6, postage 1/-
Hi-Fi Year Book 1960, 10/6, postage 1/-
Coil Design and Construction Manual by Sinclair, 5/-, postage 6d.
Ain in one Tape Recorder Book by Lloyd, 12/6, postage 1/-
Radio Circuits for Audio Amplifiers, 8/6, postage 10d.
R.S.G.B. Amateur Radio Call Book 1960, 3/6, postage 6d.
Radio Amateur Operators' Handbook 1960, 3/6, postage 6d.
Oscilloscope Techniques by Haas, 23/-, postage 1/-
Television Servicing Manual by King, 30/-, postage 1/3.

UNIVERSAL BOOK CO.
12 Little Newport Street, London, W.C.2
(adjoining Lisle Street)

Multimeter Kit 22/6, For Your 1mA meter, now includes instrument rec., 7 x 1% 1W Hi-Stabs, 3 x 1% Shunts, 1p. 11w. and SPCO switches, w.w. pot. 12 Ranges A.C./D.C. volts to 1000v., mA to 1 amp., ohms. With circuit, wiring diag., instructions. No adjustments to make.
1,900 o.p.v. Multimeter Kit, 45/-, With 1mA meter, 7 x 1% Hi-Stabs, 3 x 1% Shunts w.w. pot. 3p. 4w. and 1p. 11w. switches. Salford instrument rec. 15 Ranges A.C./D.C. volts to 600v., mA to 600 mA, ohms. With circuit and instructions. No adjustments to make.
Insulated Rectifiers, 1mA, 5mA, 7/6; 250mA, 14/6; 100A, 17/4. Ex. Govt. 5-50mA, 50A-1mA, 3/6.
Min. Neons with holder and resistor, 2/-.
Transistor Test Set, Measures Gain directly 0.50, 0.12 to 0.250. Base current 0-100 μ A. Collector current 0-5mA. Ready to use, less 9v. G.B. battery, with instructions, 41/-.
List of precision resistors, shunts, multi-meter components, etc. for S.A.E.
PLANET INSTRUMENT CO.
25 DOMINION AVENUE, LEEDS 7

Eddy's (NOTTM.) Ltd.

172 Alfreton Road, Nottingham

New or Surplus Valves—Guaranteed and Tested by Return Post.

AZ31	8/9	EL84	6/6	ID5	7/6
CL33	12/6	EL85	10/3	IR5	5/6
DAF91	4/9	EL91	4/6	IS5	4/9
DAF96	6/11	EY51	7/11	IT4	3/11
DF91	3/11	EY86	7/9	524G	7/6
DF96	6/11	EZ40	6/3	6K7G	1/11
DK92	7/6	EZ41	7/-	6K8G	5/3
DK96	6/11	EZ80	6/-	6B1E	5/11
DK91	5/6	EZ81	6/9	6B8G	2/11
DL96	6/11	GTIC	6/11	6C4	3/6
EAF42	8/-	PCC84	7/3	6C6	4/9
EB34	1/3	PCC80	7/-	6C9	9/6
EB41	6/11	PCL82	7/6	6CH6	9/-
E891	3/6	PCL83	10/6	6F3	6/9
EBF80	8/-	PEN36C	8/-	6J5	2/9
ECC40	19/11	PEN36A	12/6	6J5GT	3/9
ECC81	5/3	PL36	10/9	6J6	4/-
ECC82	5/11	PL81	8/9	6I7G	5/-
ECC83	6/6	PL82	7/-	6P28	9/6
ECC84	8/3	PL83	7/3	6A7M	5/6
ECH42	8/-	PY31	6/3	6S7M	4/9
ECL80	7/6	PY80	6/11	6S7M	5/-
EF36	3/6	PY83	7/3	6SN7GT	4/3
EF37	7/11	P61	2/3	604GT	10/6
EF40	13/3	UB41	8/-	6V6G	4/11
EF42	7/6	UF42	6/3	6V6GT	6/-
EF50	1/9	UL41	7/3	6V6M	8/6
EF80	5/-	UYIN	6/3	25A6G	8/-
EF86	9/9	UY41	6/3	25Z4G	7/6
EF89	7/-	VT52 (5 pin)	954	1/6	
EF91	3/6		2/6	955	3/6
EL42	9/3				

TRANSISTORS, Red Spot 3/9, White Spot 4/3, post 6d.

GERMANIUM DIODES 8d. each, 7/- dozen, post 6d.

NIFE ACCUMULATORS, Size 3 x 2 1/2 x 1/2 in., 7 amp hrs. 1.25 v. Weight 13 ozs. 1/11 ea., p. & p. 1/6 one only, add 9d. per cell.

HEADPHONE CORDS, High Quality 6ft. lengths 1/11 pair, post 6d.

THROAT MIKES 1/- each, post 6d. Could be used for electrifying musical instruments.

JACK PLUGS, Standard 1/11, post 9d.

DIMMER SWITCHES, Ideal for train speed regulators, 1/11, post 9d.

VIBRATORS, 12 v. 4 pin, 4/11, post 1/-.

HANDMIKES, Carbon 3/11, post 1/9.

VARIABLE CONDENSERS, .0005 Small twin gang, Built in slow motion drive, 8/11, post and packing 1/6.

CAR RADIO KITS, 7 Transistor Long and Medium, 2 watts output, R.F. stage and automatic gain control, 10 1/2 gns. p. & p. 5/- extra 6 or 12 volts (state which), Supplied with full instructions. Size 7 1/2 x 7 1/2 x 2 1/2 in. Speaker 17/11 extra.

GUITAR PICK-UP, "Elpico" Super Hi-Fi Non-acoustical universal fitting 3 x 1 1/2 x 1/2 in. High quality output. Complete with lead and plug. Full and easy instructions 49/11, post 1/-.

CRYSTAL SETS, Complete 2 wave bands high gain, good quality, 19/11, post and packing 2/-.

HEADPHONES, High Resistance to suit above crystal set. Good quality, 12/11, post and packing 2/-.

All above are New and Guaranteed.
Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customers risk. Post and Packing 6d. per valve extra. Over £3 free. C.W.O. or C.O.D. only. C.O.D. charge 3/- extra. S.A.E. with inquiries.

LOOK!
Transistor prices down again

Red Spot Transistors 3/6 each, 6 for 19/6.

White Spot Transistors 4/- each, 6 for 22/6.

Yellow/Green Transistors 4/9 each.

Red/Yellow Transistors 6/9 each.

Diodes 1/- each, 3 for 2/6, 12 for 8/6.

ALL SENT POST FREE BY **PETHERICK'S Radio Supplies**
22 High Street, Bideford, N. Devon

BBC - ITV - F.M. AERIALS

BBC (BAND D), 1. Telescopic loft, 19/6. External S/D, 26/3.
ITV (BAND 3), 3 Element loft array, 24/-, 5 Element, 32/6. Wall mounting, 3 Element, 33/9, 5 Element, 41/3.
COMBINED BBC - ITV, Loft 1+3 Element, 41/3, 1+5 Element, 48/9. Wall mounting, 1+3 Element, 56/3, 1+5 Element 82/9. Chimney and mast mounting units also available.
F.M. (BAND 2), Loft "H", 28/-, 3 Element loft, 52/6. S/D loft, 12/6. External S/D 26/3. State channel when ordering. C.W.O. or C.O.D. P.P. 2/6. Coaxial cable, 8d. yd. Coaxial plugs 1/3. Send 6d. stamps for illustrated lists.

K.V.A. ELECTRONICS (Dept. P.W.)
35, Godstone Road, Kenley, Surrey.

OUR SPECIALITIES: Transistors, Quartz Crystals, Valves & Miniature Components

Trade enquiries invited

CATALOGUES FREE ON REQUEST

Compare our prices

WE ARE ABLE TO SUPPLY MOST OF THE COMPONENTS USED ON CIRCUITS PUBLISHED IN THIS AND OTHER MAGAZINES AND BOOKLETS. WHERE THE EXACT ITEM IS NOT STOCKED WE CAN RECOMMEND A SUITABLE SUBSTITUTE IF AVAILABLE.

UNBEATABLE VALVE PRICES!

0A2	10/-	5V4	10/-	6F6	7/6	6SR7	6/-	12SG7	6/-	807USA	7/6	DL91	7/-	KTW61	6/6
OZ4	5/-	5X4G	10/-	6F8	7/6	6SS7	6/-	12SH7	6/-	AC/SG	10/-	DL94	7/6	KTW63	5/-
1A5	5/-	5T4	10/-	6F12	5/-	6U4	12/6	12SJ7	6/-	AC2PENDD	12/6	DM70	8/6	MVS PEN	
1A7	12/6	5Y4G	10/-	6F32	7/6	6U7	5/-	12SK7	6/-	AC/PEN		EB91	5/-		10/-
1C5	10/-	5Z3	10/-	6F33	5/-	6V6G	8/6	12SQ7	8/6	AC/VP1	10/-	EB33	6/6	MS PEN	10/-
1H5	10/-	5Z4G	8/6	6J5M	5/-	6V6GT	7/6	1457	14/-	AC/VP2	10/-	EF50	4/-	MU14	7/6
1L4	5/-	5Z4M	10/-	6J7M	7/6	6V6M	10/-	25A6	10/-	AR8	5/-	EL32	5/-	MX40	10/-
1LD5	5/-	6A7	9/-	6K7G	5/-	6X4	6/-	25L6	10/-	AZ31	10/-	EL33	12/6	N14	10/-
1LN	5/-	6AB8	10/-	6K7M	7/6	6X5GT	5/-	25Z4	9/-	EL33	12/6	EM34	7/6	PEN4VA	
1N5	10/-	6AC7	5/-	6K8M	10/-	7A7	9/-	25Z5	9/-	EL33	12/6	EM80	10/-		10/-
1R5	7/-	6AG5	5/-	6L6M	10/-	7D5	10/-	25Z6GT	10/-	CL33	12/6	EM81	10/-	PEN25	5/-
1S4	7/-	6AK5	6/-	6Q7G	7/6	7D6	10/-	2807	4/-	CY1C	10/-	EM85	11/-	PEN46	5/-
1S5	6/6	6AL5	5/-	6R7	6/-	7S7	9/-	35Z5	8/6	DAC32	10/-	FC4	10/-	PP36	10/-
1T4	6/-	6AM5	5/-	6SA7	7/6	7T4	7/-	42	7/6	DAF91	7/-	FW4/800		PX25	12/6
3A4	7/-	6AM6	5/-	6SC7GT	7/6	9D6	5/-	43	10/-	DCC90	9/-	GZ32	10/-	QP21	5/-
3A5	9/-	6BR8	4/6	6SG7	6/6	12AH7	6/-	50B5	10/-	DF91	7/-	GZ34	11/-	QP25	6/6
3D6	4/6	6BR7	12/6	6SH7	5/-	12AU6	9/-	50C5	10/-	DH63	7/6	HL23/DD		SP4	10/-
3Q4	7/6	6BW6	8/6	6S17	6/-	12BE6	10/-	75	10/-	DK32	12/6			TDD4	10/-
3Q5	9/-	6C4	5/-	6SK7	6/-	12J7	10/-	80	8/6	DK40	10/-	KT33C	8/6	U50	6/-
3S4	7/-	6D6	6/6	6SL7	6/-	12K8	10/-	83V	10/-	DK91	7/-	KT66	12/6	UCH42	10/-
3V4	7/6	6C5	5/-	6SQ7	6/-	12SC7	6/-	83	10/-	DK92	7/6				

Special reductions for sets of valves. Send for free lists. P.P. 6d. per valve. Orders above £3 post free. C.O.D. or C.W.O.

— STEREO 3D —

A NEW DESIGN which can be used with Stereo or Any Type of Record. Supplied with gold calibrated dials, knobs and leads, etc.

- ★ 2 WATTS PEAK OUTPUT PER SPEAKER
- ★ TONE, BALANCE AND VOLUME CONTROLS
- ★ MAINS OPERATED 110/250 v. D.C. COMPLETELY BUILT AND TESTED

£57.6 P.P. 2/6.

★ SPECIAL OFFER ★

9 x 6in. ELAC Speakers for use with above. 18/6 each, P.P. 1/-.

COLLARO 4-speed auto-changer, crystal turnover pick-up, STEREO head for use with the STEREO-3D.

£7.10.0 P.P. 3/6.

TRANSMITTER/RECEIVER ARMY TYPE 17, MARK II

Complete with Valves, High Resistance Headphones, Handmike and Instruction Book and circuit. Frequency Range 4.0 to 61 Mc/s. Range approximately 3 to 8 miles. Power requirements: Standard 120v. H.T. and 2v. L.T. Ideal for Civil Defence and communications.

BRAND NEW 45/- P.P. 5/-.

TYPE 38 TRANSMITTER/RECEIVER

Complete with 5 valves. In new condition. These sets are sold without guarantee, but are serviceable.

7 to 9 Mc/s 22/6 P.P. 2/6

Headphones 7/6 pair. Junction Box 2/6. Throat Mike 4/6. Aerial Rod 2/6.

★ VALVE REDUCTIONS ★

(WHEN PURCHASED IN SETS)

TP25, VP23, HL23/DD, PEN25 (or QP25) ...	25/-
1A7GT, 1N5GT, 1H5GT, 1C5GT (or 3Q5GT) ...	35/-
X66, KTW61, DH63, KT63, U50 ...	30/-
6K8G, 6K7G, 6Q7G, 5Z4G, 6V6G ...	32/6
1R5, 1S5, 1T4, 1S4 (or 3S4 or 3V4) ...	25/-
DK96, DF96, DAF96, DL96 ...	35/-
6K8G, 6K7G, 6Q7G, 25L6GT, 25Z5 (or 25Z6G) ...	35/-
12K8GT, 12K7GT, 12Q7GT, 35Z4GT, 35L6GT (or 50LGT) ...	40/-
12SA7GT, 12SK7GT, 12SQ7GT, 35Z4GT, 35L6GT (or 50L6GT) ...	32/6

P.P. 1/- per set of valves

ALL TRANSISTOR BABY ALARM

THE "BABY SITTER"



- ★ 100% Safe—Guaranteed
- ★ Fully Portable
- ★ No Mains—Battery Operated
- ★ Can be used over Any Distance
- ★ Battery life 3 to 4 months

★ USE IT AT HOME, TAKE IT ON HOLIDAY

Every Sound can be heard on large 5-inch Speaker COMPLETELY ASSEMBLED WITH BATTERY AND MICROPHONE

£5.10.0 P.P. 2/6

— BE WITH YOUR CHILDREN ALL THE TIME — (Illustrated leaflet free on request)

★ TRANSISTORS

A small selection from our complete list

— ALL BRAND NEW AND FULLY GUARANTEED —
 XB102, 7/6; XC101, 25/- pr.; XA131, 250 Mc/s, 35/-; XC141, (replaces OC16) 30/-; XA103, 12/6; XA104, 15/-; SB078, 7/6; SB305, 15/-; SB231, 15/-; OC44, 19/6; OC45, 18/6; OC71, 10/-; OC76, 15/-; OC75, 15/-; OC72 prs., 30/-; V15/10P, 15/-; V15/20P, 25/-; Red Spot, 3/6; White Spot, 5/-.

COMPLETE LIST FREE ON REQUEST

★ SPECIAL OFFER ★

Matched set of Mullard Driver and Output Transistors, OC78D and 2—OC78. Giving 400mW, very high quality. 37/6. P.P. 9d.

CRYSTAL MICROPHONES

- (1) ACOS 39-1 Stick Microphone with Stand and Screened Lead 35/6, P.P. 1/6
- (2) MIC 40 Desk Microphone with Fold-away Stand and Screened Cable 25/-, P.P. 1/6
- (2) MIC 45 New Style Hand Microphone with Screened Lead. Very sensitive 39/6, P.P. 1/6

PERSONAL EARPHONES

ALL MAGNETIC and GUARANTEED

- ★ Single Personal Earphone, medium impedance, as used on Major-2 and 3 etc. Complete with lead and earcup. 12/6, P.P. 6d.
- ★ Single Personal Earphone, low impedance, fitted with lead and sub-miniature Jack Plug..... 19/6, P.P. 6d.
- ★ Jack Sockets, 4/-; with Circuit Breaker Switch, 5/-
- ★ Medium Impedance Earphone, with lead fitted with Jack Plug 19/6, P.P. 6d.
- ★ Very High Impedance version for Perdio, etc..... 22/6, P.P. 6d.

HENRY'S (RADIO) LTD.

Opposite Edgware Road Tube Station, PADDINGTON 1008/9.

5 HARROW ROAD, EDGWARE ROAD, PADDINGTON, LONDON W.2

OPEN MONDAY to SAT. 9-6. THURS. 1 o'clock

SEE BACK PAGE

Practical Wireless

BLUEPRINT

SERVICE

ALL OF these blueprints are drawn full-size and although the issues containing descriptions of these sets are now out of print, an asterisk in the list below denotes that constructional details are available free with the blue print.

The index letters which precede the Blueprint Number indicate the periodical in which the description appeared. Thus PW refers to PRACTICAL WIRELESS; AW to *Amateur Wireless* and WM to *Wireless Magazine*.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to

PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2.

SPECIAL NOTE

THE following blueprints include some pre-war designs and are kept in circulation for those constructors who wish to make use of old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

Title	Number	Price
CRYSTAL SETS		
Junior Crystal Set	PW94*	2/-
Dual-wave Crystal Diode	PW95*	2/6

STRAIGHT SETS		
Battery Operated		
Modern One-valver	PW96*	2/6
All-dry Three	PW97*	3/6
Modern Two-valver	PW98*	3/6

SUPERHETS		
Mains Operated		
A.C. Band-pass Three	PW99*	4/-
A.C. Coronet-4	PW100*	4/-
A.C./D.C. Coronet	PW101*	4/-

MISCELLANEOUS		
The PW 3-speed Autogram	—*	8/-
The PW Monophonic Electronic Organ	—	8/-

TELEVISION		
The PT Band III converter	—*	1/6

Title	Number	Price
A.C. Fury Four	PW20*	2/6
Experimenter's Short Wave	PW30a*	2/6
Midget Short Wave Two	PW38a*	2/6
Band-Spread Three (Battery)	PW68*	2/6
Crystal Receiver	PW71*	2/-
Signet Two (Battery)	PW76*	2/6
Simple S.W. One-valver	PW88*	2/6
Pyramid One-valver	PW93*	2/5

BBC Special One-valver	AW387*	2/6
Short-Wave Two	AW429*	2/6
Short-Wave World Beater	AW436*	3/6

Standard Four Valve S.W.	WM383*	3/6
Enthusiast's Power Amplifier	WM387*	3/6
Standard Four Valve	WM391*	3/6
Listener's 5-Watt Amplifier	WM392*	3/6

QUERY COUPON

This coupon is available until 7th October, 1960, and must accompany all queries in accordance with the notice on our "Open to Discussion" page.

PRACTICAL WIRELESS, OCTOBER, 1960

"CONTINENTAL-6" COMBINED PORTABLE/CAR RADIO

★ ★ EQUALLY SENSITIVE ON MEDIUM AND LONG WAVE BANDS ★ ★

SPECIFICATION

- 425mW Push-Pull Output
- 6 "Top-Grade" Ediswan Transistors
- New Type Printed Circuit with all Components Marked
- Full Medium and Long Wave Tuning
- High "Q" Internal Ferrite Aerial
- Car Radio Adaptation AVC
- Slow Motion Fingertip Aiding
- "Hi-Fi" Quality Speaker
- Size $9\frac{1}{2} \times 7\frac{1}{2} \times 3\frac{1}{2}$ in. Weight $4\frac{1}{2}$ lb.

ALL COMPONENTS AVAILABLE SEPARATELY

Wherever you are

"First Class in every way"



ALL THE CONTINENTAL AND LOCAL STATIONS AT YOUR FINGERTIPS

CALL FOR DEMONSTRATION

★ STEP BY STEP FULLY ILLUSTRATED INSTRUCTIONS

★ ALL COMPONENTS GUARANTEED

Total Cost of all Components

£11.10.0 P.P. 3/6

including Cabinet, Battery Transistors, Car Radio, AVC and all necessary items.

★ SIMPLE TO CONSTRUCT

★ NO TECHNICAL KNOWLEDGE REQUIRED

★ WORTH DOUBLE WHEN BUILT

★ EXCELLENT RESULTS ANYWHERE

DESCRIPTIVE LEAFLET FREE ON REQUEST

★ NO EXTERNAL AERIAL OR EARTH—NO REACTION CONTROLS ★

★ COMPLETE STATION SEPARATION — EASY AS A B C TO BUILD AND A THRILL TO USE ★

MAJOR—2 (Two-Transistor Pocket Radio)

IDEAL FOR BEGINNERS



All components sold separately

- ★ 4-stage reflex
- ★ Medium wave; tunable
- ★ Very sensitive
- ★ No aerial or earth
- ★ Complete layout
- ★ Over 6 months on one battery
- ★ $4\frac{1}{2} \times 3 \times 1\frac{1}{2}$ in.
- ★ Weight only 4 oz.
- ★ Personal phone included

TOTAL COST **69/6** P.P. 1/6. NEW BOOKLET FREE

RECEPTION GUARANTEED ANYWHERE!

★ ★ NOT TOYS BUT REAL WORKING RADIOS! ★ ★

MAJOR—3 (Three-Transistor Pocket Radio)



(As described in R.C., Sept. '59)

- ★ 5-stage Reflex Circuit
- ★ No Aerial or Earth
- ★ Miniature Volume Control
- ★ 3 Ediswan Transistors
- ★ Medium Wave Tuning
- ★ Size $4\frac{1}{2} \times 3 \times 1\frac{1}{2}$ in.
- ★ Personal phone included

TOTAL COST **87/6** P.P. 1/6. NEW BOOKLET FREE

FANTASTIC OUTPUT, TERRIFIC RECEPTION GUARANTEED ANYWHERE

3-TRANSISTOR HEARING AID
High-gain circuit with built-in crystal microphone and battery. Includes miniature earphone. Size $3 \times 2 \times \frac{1}{2}$ in. All components, 89/6. P.P. 1/-.

RF, IF AND AUDIO SIGNAL TRACER
Ideal signal peaker or quick fault-finder for receivers, amplifiers, etc. Size $4\frac{1}{2} \times 3 \times 1\frac{1}{2}$ in. All components, with 'phones, 37/6. P.P. 1/6. Less 'phones, 32/6. P.P. 1/6.

250mW PUSH-PULL OUTPUT AMPLIFIER

For use with any 2, 3 or 4 transistor, earpiece or headphone radio to give room-filling volume on 3in. speaker. All components, including 2 Ediswan transistors, speaker, battery, special input socket to take earpiece plug, cabinet, etc., 59/6. P.P. 1/6. Ideal for use with Major-2 or Major-3.

RF AND IF SIGNAL GENERATOR
450kc/s to 3 Mc/s output. Ideal for alignment or fault-finding for all types of transistor radios. All components, 25/- P.P. 1/-.

TRANSISTORS

Fully guaranteed. Red Spot 3/6, White Spot 5/-. Free list and data of 50 types on request.

" PRACTICAL TRANSISTOR CIRCUITS "

Contains 14 circuits with diagrams for the home constructor. 1st edition, 2/-, post free.

WE ARE ABLE TO SUPPLY MOST OF THE COMPONENTS USED ON CIRCUITS PUBLISHED IN THIS AND OTHER MAGAZINES AND BOOKLETS. WHERE THE EXACT ITEM IS NOT STOCKED WE CAN RECOMMEND A SUITABLE SUBSTITUTE IF AVAILABLE.

2 WATT OUTPUT TRANSISTOR AMPLIFIER

For connection to any battery portable to give up to 2W output. Works from 12V battery. Ideal for car radio use. Size $4\frac{1}{2} \times 3 \times 2\frac{1}{2}$ in., uses power transistor. All components (less speaker), 52/6. P.P. 2/- Ideal for use with Continental 6, etc.

CRYSTAL MICROPHONES

Acos 39-1. Stick microphone with screened cable and stand, 39/6. P.P. 1/6.
Acos 40. Desk microphone with fold away stand and lead, 25/- P.P. 1/6.
Acos 45. New type hand microphone with screened lead, 39/6. P.P. 1/6.

TELESCOPIC CHROME AERIALS

(1) 7 sections, 3ft. 6in. open, 6in. closed, with clips, 12/6. P.P. 1/-.
(2) 9 sections, 5ft. 4in. open, 8in. closed, with clips, 17/6. P.P. 1/-.

SEE OTHER ADVT. INSIDE

HENRY'S (RADIO) LTD.

Opposite Edgware Road Tube Station. PADdington 1008/9

5 HARROW ROAD, EDGWARE ROAD PADDINGTON, LONDON W.2

OPEN MON. to SAT. 9-6, THURSDAY 1 o'clock

(Open all day Saturday)