ISSN. 0142-7229

electronics today

INTERNATIONAL

APRIL 1981 65p



MAKE YOUR OWN ELECTRONIC MUSIC!

Four superb projects inside

- DRUM SYNTHESISER/RHYTHM GENERATOR
- VISUAL SOUND ANALYSER
- SYNTHESISER MODULE
- GUITAR NOTE EXPANDER

PLUS

Electronics In Boats
First Steps In Programming
Pickup Cartridge Principles
Low Resistance Meter Project

BIGGER BETTER VALUE THAN EVER!

★OVER 25 CIRCUITS TO BUILD!
★SIX DIY PROJECTS ★OVER 110 PAGES

..NEWS. . . .PRO MICROPROCESSORS. . . .AUDIO. .

TRANSCENDENT POLYSYNTH

By brilliant design work and the use of high technology components the Polysynth brings to the reach of the home constructor a machine whose versatility and range of sounds is matched only by ready built equipment costing thousands of pounds. Designed by synthesizer expert Tim Orr and being featured in this issue of Electronics Today International, this latest addition to the famous Transcendent family is a 4 octave (transposable over 7½ octaves) polyphonic synthesizer with internally up to 4 voices making it possible to play simultaneously up to 4 notes. Whereas conventional synthesizers handle only one at a time.

The basic instrument is supplied with 1 voice and up to 3 more may be plugged in. A further 4 voices may be added by connecting to an expander unit, the metalwork and woodwork of which is designed for side by side matching with the main instrument. Each voice is a complete synthesizer in itself with 2 VCOs, 2 ADSRs, a VCA and a VCF (requiring only control voltages and a power supply, the voice boards are also suitable for modular systems). One of these voices is automatically allocated to a key as it is operated. There are separate tuning controls for each VCO of each voice. All other controls are common to all the voices for ease of control and to ensure consistency between the voices.

Although using very advanced electronics the kit is mechanically very simple with minimal wiring, most of which is with ribbon cable connectors. All controls are PCB mounted and the voice boards fit with PCB mounted plugs and sockets. The kit includes fully finished metalwork, solid teak cabinet, professional quality components (resistors 2% metal oxide or metal film of 0.5% and 0.1%), nuts, bolts, etc.

EXPANDABLE POLYPHONIC SYNTHESIZER



COMPLETE KIT

ONLY

£320 + VAT

(Single voice)

Plug in extra Voices — Kit price £52 + VAT (£48 + VAT if ordered with kit)

Cabinet size 31.1" x 19.6" x 7.6" rear 3.4" front

Kit also available as separate packs

	Pack		Price
ADSR IC CEM 3310 £4.00	POLY 1	Pair of PCB's for multiplex cct. K.B. contacts	£9.50
VCO IC CEM 3340 £6.00	POLY 2	IC's, IC sockets, Rs, Cs, for multiplex cct.	£8.20
	POLY 3	Superior quality keyboard	£32.25
	POLY 4	Contacts & bus bars	£12.00
0.1% 25 ppm M.F. Res £0.50	POLY 5	Double sided plated through PCB for digital control & pitch/gate generator cct.	£17.25
0.5% 25 ppm M.F. Res £0.25	POLY 6	Rs, Cs, heat sink for fitting to Pack 5	£10.50
	POLY 7	IC's, IC sockets, diodes for fitting to Pack 5	£31.30
	POLY 8	Double sided mother board (for plug in voices)	£18.90
30 ppm multilayer ceramic cap £0.50	POLY 9	Rs, Cs, connectors for mother board	£14.10
	POLY 10	IC's IC sockets, Trs, heat sinks for mother board	£13.10
ICs and details of all packs in our **FREE CATALOGUE**	POLY 11	PCB for master controls (left of section marked VOICES)	£18.80
	POLY 12	ICs, IC sockets, diodes, Trs, Rs, Cs for master control PCB	£9.30
	POLY 13	Pots, Switches for master control board	£11.80

	Pack		Price
	POLY 14	PCB for VOICE controls	£6.80
	POLY 15	Pots, switches, diodes, Cs for VOICE PCB	£4.80
	POLY 16	PCB for plug in voice	£8.20
	POLY 17	Rs, Cs, presets, connectors for one voice	£16.30
	POLY 18	ICs, IC skts, diodes for one voice	£27.50
	POLY 19	Transformer 0-120-240, 17-0-17, 0-7.7	£6.30
	POLY 20	Pitch bend control	£3.90
	POLY 21	Misc parts eg. jack sockets, knobs, mains switch etc.	£13.00
	POLY 22	Ribbon cable, ribbon cable connectors, mains cable	£8.45
	POLY 23	Fully finished metalwork and fixing parts	£25.60
	POLY 24	Solid teak cabinet	£25.80
	Total cost for individually purchased packs for single voice instrument		£355.15
	Complete kit for 4 voice expander including connectors		**£295.00**
	All prices VAT exclusive.		

POWERTRAN

OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!

POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE
ANDOVER, HANTS SP10 3NM

ANDOVER
(STD 0264) 64455

PRICE STABILITY: Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until May 31st, 1981, if this month's advertisement is mentioned with your order. Prices and VAT rate changes excluded.
EXPORT ORDERS: No VAT. Postage charged at actual cost plus £1 handling and postal documentation.
U.K. ORDERS: Subject to 15% surcharge for VAT. No charge is made for carriage or at current rate if charged.

SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.
SALES COUNTER: If you prefer to collect kit from the factory, call at Sales Counter. Open 9a.m. 12 noon, 1-4.30p.m. Monday-Thursday


MANY MORE KITS ON PAGE 8




Our thanks to Music Bank, 6 Erskine Road, London NW3, who provided the facilities for our cover photograph



Double dose of drumming p.75

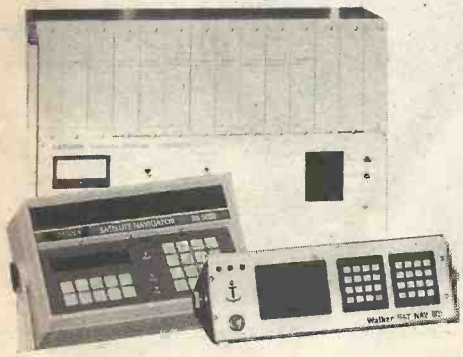

All at sea p.28

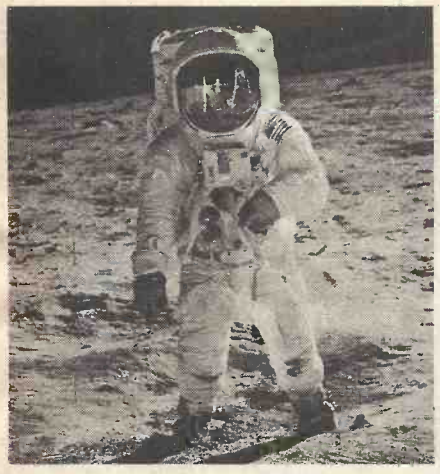

Interplanetary pix p.71

electronics today

APRIL 1981 VOL 10 NO 4 INTERNATIONAL

FEATURES

DIGEST	8	Read all about it
KIT REVIEW	17	Touch dimmer tested
ELECTRONICS IN BOATS	28	Boat Show reviewed
TECH TIPS	35	Readers' circuits
PICKUP PRINCIPLES	44	In the groove
MICROBASICS	55	Programming programmers
DESIGNER'S NOTEBOOK	66	CMOS safety
ASTROLOGUE	71	Aeronautics and artwork
AUDIOPHILE	82	The Reviewer's Return
SPOT DESIGNS	88	Tried and tested circuits
THE LEPTONS	91	A subatomic story

PROJECTS

VSCA	21	Audio display
LOW-OHM METER	40	Measure miniscule resistances
MUSICAL BOX	50	Shake it all about
NOISE GENERATOR	59	A Project 80 module
DRUM MACHINE	75	Sound design
GUITAR NOTE EXPANDER	95	Stretch your strings
READER'S DESIGNS	100	Caravan lights checker
FOIL PATTERNS	104	Board meeting

INFORMATION

EXHIBITION	10	We're coming to Bristol
NEXT MONTH'S ETI	15	What are we going to do next
BOOKS	27	Our technical book service
SUBSCRIPTIONS	63	Advance booking
ETIPRINTS	102	Give yourself a rub-down

EDITORIAL AND ADVERTISEMENT OFFICE

145 Charing Cross Road, London WC2H 0EE. Telephone 01-437 1002/3/4/5. Telex 8811896.

Ron Harris B.Sc.	Editor
Peter Green	Assistant Editor
Tina Boylan	Editorial Assistant
Paul Wilson-Patterson	Group Art Editor
Paul Edwards	Drawing Office Manager
Ray Marston	Project Editor
Steven Rowe	Advertisement Manager
Sally Holley	Advertisement Representative
T.J. Connell	Managing Director

OVERSEAS EDITIONS and their EDITORS: AUSTRALIA — Roger Harrison; CANADA — Halvor Moorshead; GERMANY — Udo Wittig; HOLLAND — Anton Kriegsman

ABC Member of the Audit Bureau of Circulation

MODMAGS LTD

PUBLISHED BY: Modmags Ltd., 145 Charing Cross Road, London WC2H 0EE

DISTRIBUTED BY: Argus Press Sales & Distribution Ltd. 12-18 Paul Street, London EC2A 4JS (British Isles)

PRINTED BY: QB Limited, Colchester

COVERS PRINTED BY: Alabaster Passmore

Electronics Today is normally published on the first Friday in the month preceding cover date. ☐ ©MODMAGS LTD 1981: All material is subject to worldwide copyright protection. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press. ☐ Subscription Rates: UK £11 including postage. Airmail and other rates upon application to ETI Subscriptions Service, Modmags Ltd, 145 Charing Cross Road, London WC2H 0EE.

Why the Sinclair ZX80 is Britain's best-selling

Built: £99.95

Including VAT, post and packing, free course in computing, free mains adaptor.

Kit: £79.95

Including VAT, post and packing, free course in computing.



This is the ZX80. A really powerful, full-facility computer, matching or surpassing other personal computers at several times the price. 'Personal Computer World' gave it 5 stars for 'excellent value'. Benchmark tests say it's faster than all previous personal computers.

Programmed in BASIC – the world's most popular language – the ZX80 is suitable for beginners and experts alike. And response from enthusiasts has been tremendous – over 20,000 ZX80s have been sold so far!

Powerful ROM and BASIC interpreter


The 4K BASIC ROM offers remarkable programming advantages:

* Unique 'one-touch' key word entry: the ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST, etc.) have their own single-key entry.
* Unique syntax check. A cursor identifies errors immediately.
* Excellent string-handling capability – takes up to 26 string variables of any length. All strings can undergo all relational tests (e.g. comparison).
* Up to 26 single dimension arrays.
* FOR/NEXT loops nested up to 26.
* Variable names of any length.
* BASIC language also handles full Boolean arithmetic, condition expressions, etc.
* Randomise function, useful for games and secret codes, as well as more serious applications.
* Timer under program control.
* PEEK and POKE enable entry of machine code instructions.
* High-resolution graphics.
* Lines of unlimited length.

Unique RAM

The ZX80's 1K-BYTE RAM is the equivalent of up to 4K BYTES in a conventional computer – typically storing 100 lines of BASIC.

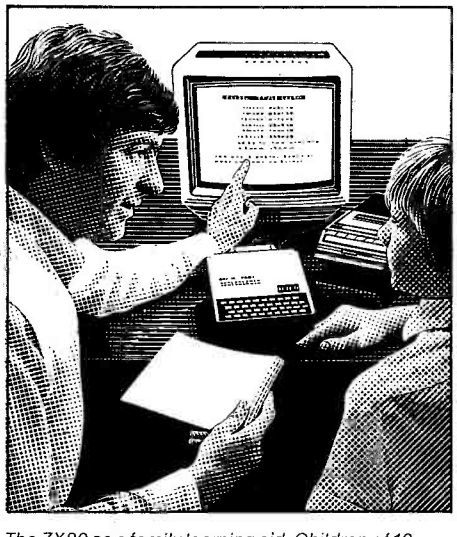No other personal computer offers this unique combination of high capability and low price.



The ZX80 as a family learning aid. Children of 10 years and upwards are quick to understand the principles of computing – and enjoy their personal computer.

The Sinclair teach-yourself BASIC manual

If the specifications of the Sinclair ZX80 mean little to you – don't worry. They're all explained in the specially-written 128-page book (free with every ZX80). The book makes learning easy, exciting and enjoyable, and represents a complete course in BASIC programming – from first principles to complex programs.

Kit or built – it's up to you

In kit form, the ZX80 is pleasantly easy to assemble, using a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9V DC nominal unregulated. If not, see the coupon.

Both kit and built versions come complete with all necessary leads to connect to your TV (colour or black and white) and cassette recorder. Plug in and you're ready to go. (Built versions come with mains adaptor.)

personal computer.

Now available for the ZX80...
New 16K-BYTE RAM pack



Massive add-on memory. Only £49.95.
The new 16K-BYTE RAM pack is a complete module designed to provide you – and your Sinclair ZX80 – with massive add-on memory. You can use it for those really long and complex programs – or as a personal database. (Yet it can cost as little as half the price of competitive add-on memory for other computers.)

For example, you could write an interactive or 'conversational' program to show people what your ZX80 can do. With 16K-BYTES of RAM, they could be talking to your computer for hours!

Or you can store a mass of data – perhaps in a fairly simple program – such as a name and address list, or a telephone directory.


And by linking a number of separate programs together into one giant, but modular, program, you can achieve the same effect as loading several programs at once.

We're also confident that it won't be long before you can buy cassette-based software using the full 16K-BYTE RAM. So keep an eye on the personal computer magazines – and brush up your chess perhaps!

The RAM pack simply plugs into the existing expansion port on the rear of the ZX80. No wires, no soldering. It's a matter of seconds and you don't need another power supply. You can only add one RAM pack to your ZX80 – but with 16K-BYTES who could want more!

How to order

Demand for the ZX80 exceeds all other personal computers put together! So use the coupon to order today for the earliest possible delivery. All orders will be despatched in strict rotation. We'll acknowledge each order by return, and tell you exactly when your ZX80 will be delivered. If you choose not to wait, you can cancel your order immediately, and your money will be refunded at once. Again, of course, you may return your ZX80 as received within 14 days for a full refund. We want you to be satisfied beyond all doubt – and we have no doubt that you will be.

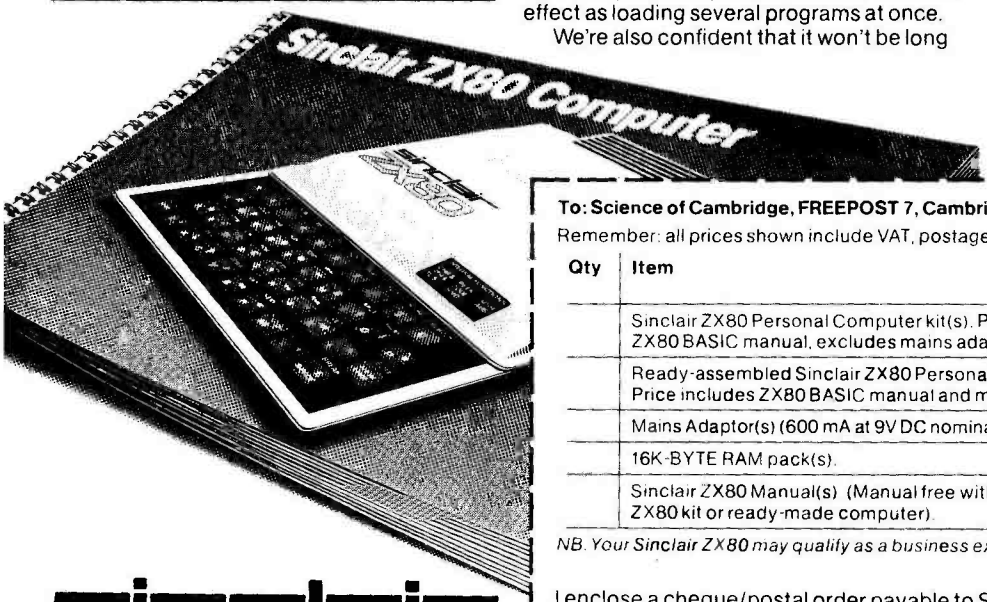

To: Science of Cambridge, FREEPOST 7, Cambridge CB2 1YY.

Remember: all prices shown include VAT, postage and packing. No hidden extras. Please send me:

Qty	Item	Code	Item price £	Total £
	Sinclair ZX80 Personal Computer kit(s). Price includes ZX80 BASIC manual, excludes mains adaptor.	02	79.95	
	Ready-assembled Sinclair ZX80 Personal Computer(s). Price includes ZX80 BASIC manual and mains adaptor.	01	99.95	
	Mains Adaptor(s) (600 mA at 9V DC nominal unregulated)	03	8.95	
	16K-BYTE RAM pack(s).	18	49.95	
	Sinclair ZX80 Manual(s) (Manual free with every ZX80 kit or ready-made computer)	06	5.00	

NB. Your Sinclair ZX80 may qualify as a business expense. **TOTAL: £**

I enclose a cheque/postal order payable to Science of Cambridge Ltd for £ _____

Please print

Name: Mr/Mrs/Miss _____

Address _____

FREEPOST – no stamp needed. ETI04

sinclair ZX80

Science of Cambridge Ltd.

6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Tel: 0223 311488.

ETI APRIL 1981

WATFORD ELECTRONICS

33/35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND
MAIL ORDER, CALLERS WELCOME
Tel. Watford (0923) 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.Os OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P ADD 50p TO ALL ORDERS UNDER £10. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE. ACCESS ORDERS WELCOME.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to all prices.

We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday. Ample Free Car Parking space available.

ELECTROLYTIC CAPACITORS: (Values are in µF) **500V:** 10 **52p**; 47 **78p**; **250V:** 100 **65p**; **63V:** 0.47, 1.0, 1.5, 2.2, 3.3 **8p**; 4.7 **9p**; 6.8, 10 **10p**; 15, 22, **12p**; 33 **15p**; 47 **12p**; 100, **19p**; 1000 **70p**. **50V:** 47 **12p**; 68 **20p**; 220 **24p**; 470 **32p**; 2200 **80p**. **40V:** 4.7, 15, 22 **9p**; 3300, **90p**; 4700, **120p**; **25V:** 1.5, 6.8, 10, 22 **8p**; 33 **9p**; 47 **8p**; 100 **11p**; 150 **12p**; 220, **15p**; 330 **22p**; 470 **25p**; 680, 1000, **34p**; 2200, **50p**; 3300, **76p**; 4700 **92p**; **16V:** 40, 47, 100 **9p**; 125, **12p**; 220 **13p**; 470, **20p**; 680 **34p**; 1000 **27p**; 1500, **31p**; 2200 **36p**; 3300 **74p**; 4700 **79p**.
TAG-END TYPE: 450V: 100µF **85p**; **70V:** 4700, **245p**; **64V:** 3300 **198p**; 2200 **138p**; **50V:** 3300 **154p**; 2200 **110p**; **40V:** 4700 **160p**; **25V:** 10,000 **320p**; 15,000 **345p**.

POLYESTER CAPACITORS: Axial Lead Type
400V: 1nF, 1n5, 2n2, 3n3, 4n7, 6n8 **11p**; 10n, 15n, 18n, 22n **12p**; 33n 47n, 68n **16p**; 100n, 150n **20p**; 220n **30p**; 330n **42p**; 470n **52p**; 680n **60p**; 1µF **68p**; 2µ2 **82p**; 4µ7 **85p**.
160V: 10nF, 12n, 39n, 100n **11p**; 150n, 220n **17p**; 330n, 470n **30p**; 680n, **38p**; 1µF **42p**; 1µ5 **45p**; 2µ2 **48p**; 4µ7 **58p**.
1000V: 1nF **17p**; 10nF **30p**; 15n **40p**; 22n **36p**; 33n **42p**; 47n, 100n **42p**; 470n **99p**.

POLYESTER RADIAL LEAD CAPACITORS: 250V:
10n, 15n, 22n, 27n **6p**; 33n, 47n, 68n, 100n **7p**; 150n, 220n **10p**; 330n 470n **13p**; 680n **19p**; 1µ **23p**; 1µ5 **40p**; 2µ2 **48p**.

TANTALUM BEAD CAPACITORS
35V: 0.1µF, 0·22, 0·33 **15p**; 0·47, 0·68, 1·0, 1·5 **16p**; 2.2, 3·3 **18p**; 4·7, 6.8 **22p**; 10 **28p**; **16V:** 2·2, 3.3 **16p**; 4.7, 6.8 10 **18p**; 15, **36p**; 22 **30p**; 33, 47 **40p**, 100 **75p**; **10V:** 15, 22, **26p**; 33, 47 **35p**; 100 **55p**; **6V:** 100 **42p**.

MYLAR FILM CAPACITORS
100V: 1nF, 2, 4, 4nF, 10 **6p**; 15nF, 22n, 30n, 40n, 47n **7p**; 56n, 100n, 200n **9p**; **50V:** 470nf **12p**.

CERAMIC CAPACITORS 50V
Range: 0·5pF to 10,000pF **4p**
0·01µF, 0·022µF, 0·033µF **5p**
0·047µF **5p**; 0·1µF, 0·2µF **7p**

SILVER MICA (Values in pF) 2, 3·3, 4·7, 6·8, 8·2, 10, 12, 15, 18, 22, 27, 33, 39, 47, 50, 56, 68, 75, 82, 85, 100, 120, 150, 180pF **15p** each
200, 220, 250, 270, 300, 330, 360, 390, 470, 600, 800, 820 **21p** each
1000, 1200, 1800, 2200 **30p** each
3300, 4700pF **60p** each

POLYSTYRENE CAPACITORS:
10pF to 1nF **8p**; 1·5nF to 12nF **10p**

MINIATURE TYPE TRIMMERS
2·6pF, 2·10pF **22p**; 2·25pF, 5·56pF **30p**; 10·88pF **35p**

COMPRESSION TRIMMERS
3·40pF, 10·80pF **20p**; 20·250pF **28p**; 100·580pF **39p**; 400·1250pF **48p**

POTENTIOMETERS: Rotary,sCarbon, Track. 0·25W Log & Lin.
470Ω, 680Ω, 1KΩ & 2KΩ (Linear only) Single Gang **29p**
5KΩ-2MΩ Single Gang Log & Lin. **29p**
5KN·2MΩ Single Gang D/P Switch **78p**
5KΩ-2MΩ Double Gang Log & Lin **89p**
Wire Wound Single Turn 1 Watt 200 20KΩ **115p**

SLIDER POTENTIOMETERS
0·25W log and linear values 60mm
5KΩ-500KΩ single gang **70p**
10KΩ-500KΩ dual gang **110p**
Self Stick Graduated Bezels **35p**

PRESET POTENTIOMETERS
0.1W 50Ω—5MΩ Miniature Vertical & Horizontal **7p**
0·25W 100Ω—3·3MΩ horiz larger **10p**
0·25W 200Ω—4·7MΩ Vert. **10p**
Cermet, Precision, multiturn, 0·75W ¾in 100Ω-100KΩ **89p**

RESISTORS — Erie make 5% Carbon Miniature High Stability, Low noise

RANGE	VAL	1-99	100+
¼W 2.2Ω-4.7M	E24	2p	1p
½W 2.2Ω-4.7M	E12	2p	1p
1W 2.2Ω-10M	E12	5p	4p
2% Metal Film 100·1MΩ		8p	4p
1%0.5W 51Ω-1M	E24	8p	6p

100+ price applies to Resistors of each type not mixed values.

JACKSONS VARIABLE CAPACITORS

DILICON		0 2 365pF with slow	
100/300pF	195p	motion Drive	450p
500pF	250p	0 0 208/176	395p
6·1 Ball Drive		with slow	
4511/DAF	160p	motion drive	450p
Dial Drive 4103		C804·5pF 10 15	
6 1/36·1	775p	25 50pF	280p
Drum 54mm	55p	100, 150pF	350p
0-1·365pF	325p	L 3x310pF	725p
00 2 365pF	395p	00·3x25pF	550p

RF CHOKES
1µH, 4.7, 10, 22, 33, 47, 100, 200, 470 **75p** each
1mH, 2·5, 5, 10 **35p each**
22mH, 33 **45p**; 43, 100, 120 **75p each**

VEROBOARD 0.1in

	Clad	Plain
2½ x 3¼"	66p	47p
2½ x 5"	75p	—
3¾ x 3¾"	75p	—
3¾ x 5"	88p	72p
3¾ x 17"	296p	210p
4¾ x 17"	390p	—

Pkt. of 100 pins **50p**
Spot face cutter **107p**
Pin insertion tool **147p**

VQ Board **150p**
DIP Board **330p**
Vero Strip **144p**

PROTO — DECa
Veroblack **375p**
S·Dec **350p**
Eurobreadboard **520p**
Bimboard 1 **785p**
Superstrip SS2 **998p**

VERO WIRING PEN + Spool **285**
Spare Spool **65**
Combs **6**

DALO ETCH RESIST PEN + Spare tip **90**

FERRIC CHLORIDE
1 lb bag Anhydrous **195p** + 40p P&P

ULTRASONIC TRANSDUCER
40KHz **395p** pr

COPPER CLAD BOARDS

Fibre Glass	Single-sided	Double-sided	SRBP
6" x 6"	90p	110p	95p
6" x 12"	150p	195p	

DIL PLUGS
14 pin **44p**; 16 pin **49p**
24 pin **88p**; 40 pin **295p**

Ribbon Cable 10 way & 20 way available

Soldercon pins 100 **60p**; 500 **275p**.

DIL SOCKETS (TEXAS) Low Wire

	Prof.	Wrap
8pin	10p	25p
14pin	10p	35p
16pin	10p	48p
18pin	16p	52p
20pin	22p	65p
22pin	25p	70p
24pin	30p	78p
28pin	35p	85p
36pin	—	105p
40pin	40p	109p

EDGE CONNECTORS (Double type)

.1	.156
2x10 way	85p
2x15 way	99p
2x18 way	115p 120p
2x22 way	130p 135p
2x25 way	149p 160p
2x30 way	170p —
2x36 way	194p —
2x40 way	210p —
2x43 way	232p —

DIODES

AA119	15
BA100	15
BY100	24
BY126	12
BY127	12
CRO33	250
OA9	40
OA47	12
OA70	12
OA79	15
OA85	15
OA90	8
OA91	8
OA95	8
OA200	8
OA202	8
1N914	4
1N916	5
1N4001/2	5
1N4003	6
1N4004/5	6
1N4006/7	7
1N4148	4
1N5401	16
1N5404	16
1N5406	17
IN5408	19
1S44	9
1S921	9
6A/100V	40
6A/400V	50
6A/800V	65

NOISE

Z5U	180

VARICAPS

BA102	50
BB105B	40
BB106	40
MVAM2	165
MVAM115	158

TRIACS

3A200V	54
3A400V	56
8A100V	60
8A400V	69
8A800V	115
12A100V	78
12A400V	82
12A800V	135
16A100V	103
16A400V	105
16A800V	220
25A500V	220
25A800V	295
T2800D	120

BRIDGE RECTIFIERS (plastic case)

	p
1A/50V	20
1A/100V	22
1A/400V	28
1A/600V	34
2A/50V	35
2A/200V	40
2A/400V	46
2A/600V	55
6A/100V	83
6A/400V	95
6A/600V	125
10A/200V	215
10A/600V	350
25A/200V	240
25A/600V	395
BY164	56
VM18 DIL	50

ZENERS
Range: 2V7 to 39V 400mW **8p each**
Range. 3V3 to 33V. 1·3W **15p each**

Thyristors

5A/40V	32
5A400V	40
5A600V	48
8A300V	60
8A600V	90
12A100V	78
12A400V	95
12A800V	188
BT106	150
BT116	180
C106D	38
TIC44	24
TIC45	29
TIC47	35
2N5062	32
2N5064	38
2N4444	130

DIAC

ST2	25

75 SERIES

75108	350
75150	140
75154	150
75450	95
75451	70
75454	225
75491	89
75492	95

COMPUTER ICs

2114·450n	185
2114·300n	245
2532·32K	£14
2708	350
2716·5V	450
4116	250
4315 Cmos	995
5532·250n	TBA
6502	875
6520	325
6522	570
6530	1350
6532	795
6545	1450
6551	785
6592	2572
6800	520
6805	670
6809	1550
6810	280
6821	315
6840	750
6850	315
6852	390
8080A	450
8085A	1100
81LS95	125
81LS96	125
81LS97	125
8212	210
8214	425
8251	475
8253	999
8726A	190
8T28A	195
8T95N	160
BT97N	150
AY-3-1015	420
AY-5-1013	385
AY-5-2376	750
MC1488	90
MC1489	90
MC14411	950
MC14412	1250
RO-3-2513U	600
SFF96364E	950
SFC71301	820
TMS2716-3V	1050
TMS4027	325
TMS6011	365
Z80CPU 2.5	650
Z80ACPU 4M	795
Z80P10	440
Z80AP10	575
Z80CTC	440
Z80ACTC	575
Z80SIO	TBA
Z80SIO	TBA
Z80Dart	TBA
Z80Adart	TBA

LINEAR ICs

702	75
709 14 pin	40
709C 8 pin	35
710	67
733	75
741 8 pin	17
747C 14 pin	78
748C 8 pin	36
753 8 pin	185
810	159
9400CJ	350
AY-1-0212	595
AY-1-1313A	660
AY-1-1320	225
AY-1-5050	99
AY-1-5051	180
AY-3-1015	550
AY-3-1270	840
AY-3-8500	390
AY-3-8910	850
AY-3-8912	950
AY-5-1224A	235
AY-5-1230	450
AY-5-1317A	630
AS-5-3500	350
AY-5-4007D	450
AY-5-8100	775
CA3011	110
CA3012	175
CA3014	157
CA3018	68
CA3019	70
CA3020	186
CA3023	191
CA3028A	80
CA3035	235
CA3036	115
CA3043	275
CA3045	365
CA3046	70
CA3048	214
CA3059	195
CA3075	213
CA3080E	85
CA3081	190
CA3085	95
CA3089E	215
CA3090AQ	375
CA3123E	150
CA3130	90
CA3140	48
CA3160	95
ICL7106	795
ICL7107	975
ICL8038CC	340
ICL8211A	150
ICM7204	550
ICM7205A	1150
ICM7207	475
ICM7215	1050
ICM7216AJ	1950
ICM7216B	1950
ICM7216C	1950
ICM7217A	790
ICM7224	785
ICM7555	89
LD130	452
LF351	49
LF356	90
LM10	395
LM301AP	26
LM308T	95
LM311	70
LM318N	200
LM324A	50
LM339	68
LM348	90
LM349	115
LM379	415
LM380	80
LM381N	145
LM382	125
LM384	140
LM386	99
LM387	120
LM389	99
LM733	99
LM1458	45
LM2917	195
LM3900	60
LM3909N	70
LM3911	125
LM3914	240
LM3915	240
LM3916	255
LM13600	138
M252AA	625
M253AA	1150
MC663	50
MC1204	250
MC1301	79
MC1303	88
MC1304P	260
MC1310P	150
MC1458	45
MC1488	90
MC1489	90
MC1494	694
MC1495	350
MC1496L	92
MC1596	225
MC1710	79
MC3302	150
MC3340P	120
MC3360P	120
MC3401	52
MC3403	135
MC3405	150
MFC6040	97
MK50398	635
MM5303	635
MM5307	1275
MM57160	520
MSM5526	820
NE515	275
NE529	225
NE543K	210
NE544	185
NE555	22
NE556	55
NE560	325
NE561	398
NE562B	410
NE564	435
NE565A	120
NE566	180
NE567V	170
NE570	450
NE571	420
RC4136D	110
S566B	275
SAB3209	425
SAB3210	275
SAS560	150
SAS570	150
SG3402	295
SL414A	275
SN76003N	240
SN76013	170
SN76013ND	130
SN76018	148
SN76023	170
SN76023ND	170
SN76033N	195
SN76115N	215
SN76131	125
SN76227N	95
SN76477	175
SN76680	120
SPB629	298
TAA621AX1	250
TAA661A	155
TAA700	250
TAD100	159
TBA120S	70
TBA540Q	220
TBA550Q	330
TBA641-A12 BX or BX11	250
TBA651	190
TBA800	90
TBA810	95
TBA820	70
TBA9200	260
TBA990Q	270
TCA270Q	260
TCA965	120
TDA1004	290
TDA1008	310
TDA1022	575
TDA1024	105
TDA1490	290
TOA2020	320
TDA2030	320
TL061CP	46
TL062CP	90
TL064CN	158
TL071CP	45
TL072CP	90
TL074CN	140
TL081CP	42
TL082CP	70
TL083CP	95
TL084CN	120
UAA170	170
UAA180	170
XR2206	360
XR2211	575
XR2266	750
ZN414	95
ZN423	195
ZN424E	130
ZN425E	415
ZN1034E	200
ZN1040E	685

TTL 74 (TEXAS)

7400	11
7401	11
7402	14
7403	14
7404	18
7405	36
7406	36
7407	17
7408	20
7410	17
7411	20
7412	25
7413	32
7414	30
7416	30
7417	30
7420	19
7421	38
7422	25
7423	28
7425	43
7426	32
7427	35
7428	35
7430	19
7432	27
7433	36
7437	32
7438	20
7440	18
7441	58
7442	58
7443	120
7444	116
7445	105
7446	132
7447	72
7448	75
7450	20
7451	20
7453	20
7454	20
7460	20
7470	40
7472	30
7473	35
7474	34
7475	56
7476	40
7480	52
7481	120
7482	75
7483	90
7484	99
7485	105
7486	33
7489	205
7490	42
7491	84
7492	50
7493	57
7494	85
7495	70
7496	80
7497	176
74100	130
74104	62
74105	62
74107	34
74109	60
74110	54
74111	68
74112	170
74116	198
74118	85
74119	120
74120	75
74121	35
74122	50
74123	65
74125	50
74126	45
74128	65
74132	55
74136	65
74141	75
74142	185
74143	250
74144	250
74145	90
74147	150
74148	125
74150	130
74151	70
74153	70
74154	120
74155	75
74156	75
74157	70
74159	165
74160	99
74161	99
74162	99
74163	99
74164	120
74165	120
74166	130
74167	205
74170	205
74172	375
74173	110
74174	100
74175	82
74176	90
74177	85
74178	110
74179	185
74180	90
74181	220
74182	88
74184	130
74185	130
74188	310
74190	130
74191	120
74192	120
74193	120
74194	102
74195	75
74196	80
74197	88
74198	160
74199	160
74221	150
74246	150
74247	151
74248	189
74249	189
74251	110
74265	66
74273	267
74278	249
74279	99
74283	149
74284	350
74285	350
74290	107
74293	135
74297	236
74298	185
74365	95
74366	95
74367	95
74368	95
74390	185
74393	185
74490	185

74L

74L00	68
74L30	60
74L47	380
74L75	145
74L85	349
74L121	168
74L123	325

74S

74S00	80
S04	73
S132	138
S138	240
S158	240
S188	210
S189	188
S194	300
S195	795
S241	640
S262	850
S287	325
S288	210
S470	325
S472	1150
S475	825

74LS

LS00	13
LS01	13
LS02	15
LS03	15
LS04	16
LS05	23
LS08	22
LS09	23
LS10	20
LS11	32
LS12	32
LS13	40
LS14	80
LS15	40
LS20	21
LS21	32
LS22	35
LS26	44
LS27	38
LS28	38
LS30	20
LS32	25
LS33	35
LS37	30
LS38	35
LS40	28
LS42	68
LS47	85
LS48	106
LS49	106
LS51	26
LS54	30
LS55	30
LS63	150
LS73	55
LS74	35
LS75	45
LS76	45
LS78	50
LS83	105
LS85	80
LS86	38
LS90	50
LS91	125
LS92	75
LS93	80
LS95	115
LS96	120
LS107	48
LS109	75
LS112	40
LS113	75
LS114	40
LS122	70
LS123	75
LS124	180
LS125	45
LS126	45
LS132	80
LS133	35
LS136	85
LS138	70
LS139	70
LS145	120
LS147	210
LS148	170
LS151	90
LS153	85
LS155	95
LS157	70
LS158	70
LS160	90
LS161	95
LS162	110
LS163	95
LS164	115
LS165	155
LS166	175
LS168	210
LS169	210
LS170	295
LS173	105
LS174	147
LS175	110
LS181	295
LS183	295
LS189	128
LS190	95
LS191	95
LS192	95
LS193	95
LS194	125
LS195	130
LS196	120
LS197	85
LS200	345
LS202	345
LS221	120
LS240	185
LS241	185
LS242	165
LS243	165
LS244	195

BF154	25
BF158	25
BF167	29
BF173	27
BF177	25
BF178	30
BF179	35
BF180	38
BF182	38
BF184	38
BF185	38
BF194	12
BF195	12
BF196	12
BF197	12
BF198	16
BF199	18
BF200	30
BF224A	25
BF244B	29
BF245	30
BF256A	35
BF256B	45
BF257	32
BF258	32
BF259	35
BF274	42
BF336	40
BF337	40
BF451	35
BF594	30
BF595	30
BFR39	23
BFR40	23
BFR41	23
BFR79	23
BFR80	25
BFR81	25
BFR98	105
BFX29	28
BFX81	45
BFX84	26
BFX85	28
BFX86	28
BFX87	28
BFX88	28
BFY18	50
BFY50	23
BFY51	23
BFY52	23
BFY53	32
BFY55	32
BFY56	32
BFY64	35
BFY71	20
BFY81	120
BRY39	40
BSX20	20
BSX26	34
BSX29	34
BSX78	45
BSY26	30
BSY95A	25
BU105	170
BU205	190
BU208	200
BU208	200
E421	250
MD8001	250
MJ490	90
MJ491	175
MJ2955	90
MJE170	150
MJE180	150

MJE340	54
MJE370	100
MJE371	100
MJ490	90
MJE520	65
MJE521	95
MJE2955	99
MJE3055	70
MPF102	66
MPF103	36
MPF104	36
MPF105	38
MPF106	40
MPSA05	22
MPSA06	25
MPSA12	32
MPSA55	30
MPSA56	30
MPSU02	58
MPSU05	55
MPSU06	55
MPSU52	65
MPSU55	60
MPSU56	60
MPU131	52
OC26	170
OC28	130
OC35	125
OC36	120
OC41	120
OC42	120
OC44	120
OC45	40
OC70	40
OC71	40
OC72	40
OC74	50
OC75	50
OC76	50
OC77	50
OC81	50
OC82	50
OC83	40
OC84	40
OC140	110
OC170	85
OC171	85
OC200	85
TIP29	34
TIP29A	36
TIP29B	56
TIP29C	60
TIP30	47
TIP30A	48
TIP30B	50
TIP30C	58
TIP31A	45
TIP31B	48
TIP31C	55
TIP32A	48
TIP32C	60
TIP33A	65
TIP33C	78
TIP34A	74
TIP34C	88
TIP35A	160
TIP35C	185
TIP36A	170
TIP36C	199
TIP41A	55
TIP41b	60
TIP42A	60
TIP42B	75

TIP120	90
TIP121	99
TIP122	99
TIP141	120
TIP142	120
TIP147	120
TIP2955	60
TIP3055	60
TIS43	32
TIS44	45
TIS45	45
TIS46	45
TIS59	50
TIS74	50
TIS90	30
TIS91	32
UC734	65
ZTX107	11
ZTX108	11
ZTX109	12
ZTX212	28
ZTX300	13
ZTX301	16
ZTX302	16
ZTX303	25
ZTX304	17
ZTX314	25
ZTX326	30
ZTX341	30
ZTX500	14
ZTX501	15
ZTX502	15
ZTX503	18
ZTX504	25
ZTX1	25
ZTX550	25
2N697	23
2N698	40
2N699	48
2N706A	19
2N708	19
2N918	35
2N1131	24
2N1132	24
2N1302	45
2N1303	60
2N1304	65
2N1305	60
2N1306	65
2N1307	65
2N1308	68
2N1613	30
2N1670	150
2N1671B	180
2N2160	295
2N2217	45
2N2218A	45
2N2219A	28
2N2220A	28
2N2221A	28
2N2222A	28
2N2297	45
2N2303	45
2N2368	25
2N2369A	18
2N2476	50
2N2483	27
2N2484	27
2N2492	50
2N2497	63
2N2646	45
2N2784	55
2N2904	28
2N2905A	26
2N2906	26
2N2907	26
2N2907A	26
2N2926G	10
2N3011	28
2N3020	45
2N3053	26
2N3054	58
2N3055	48
2N3108	45
2N3252	46
2N3302	30
2N3441	140
2N3442	140
2N3663	15
2N3702	10
2N3703	10
2N3704	10
2N3705	10
2N3706	10
2N3707	10
2N3708	10
2N3709	10
2N3710	10
2N3711	10
2N3713	140
2N3771	179
2N3772	195
2N3773	270
2N3819	22
2N3820	45
2N3822	65
2N3823	65
2N3824	65
2N3866	90
2N3879	150
2N3903	18
2N3904	18
2N3905	15
2N3906	17
2N4037	46
2N4041	40
2N4058	10
2N4061	10
2N4062	10
2N4064	115
2N4220	78
2N4234	48
2N4236	48
2N4264	24
2N4286	15
2N4289	18
2N4314	68
2N4400	18
2N4427	80
2N4859	78
2N4871	55
2N4898	135
2N4901	175
2N4921	55
2N4922	60
2N5102	145
2N5135	20
2N5136	20
2N5138	18
2N5172	18
2N5179	45
2N5180	45
2N5191	75
2N5305	24
2N5308	24
2N5457	36
2N5458	36
2N5459	36
2N5485	38
2N5777	45
2N5879	190
2N6027	32
2N6388	150
2SD234	75
3N128	112
3N140	112
40311

WATFORD ELECTRONICS

COMPUTER CORNER

SUPERBOARD II Series II. Ready built and tested. 50Hz, No Flicker. Incl. Manuals and Programme Cassette **£149**
POWER SUPPLY 5V/3A (incl. RF Modulator) for Superboard II (Ready-built and tested) **£20**
4K RAM (8 x 2114) **£14**
610 EXPANSION BOARD 8K RAM (Expandable to 24K). Ideal for Superboard, UK101, etc. **£150**
MICROTYPE CASE III, Black ABS case ideal for Superboard, UK101, NASCOM etc. **£25**
VIDEO GENIE based on TRS80. Utilises Z80 1.2K level II BASIC, 16K RAM, 64 x 48 Video Display, incl. Cassette Deck **£288**
SOUND UNIT for above (ready fitted) **£15**
LOWER CASE for above (ready fitted) **£35**
ACULAB FLOPPY with Wafers **£174**
EXPANSION BOX with RS232C **£199**
S100 16K Memory **£95**
S100 32K Memory **£135**
SUPERPRINT 800. 80 column Low Cost Impact Printer. 9½" paper width. Tractor/Friction Feed. Inputs for RS232, 20mA Loop, IEE-488, Centronics parallel all standard **£295**

EPSON TX-80S Dot Matrix, Tractor Feed **£285**
EPSON TX-80 Dot Matrix, Friction Feed **£285**
SEIKOSHA GP80A Uni-hammer, 80 Column, Impct Graphic, Dot Printer **Only £225**
SOFTY. Intelligent EPROM Programmer. Ready built and tested **£120**
SOFTY in kit form **£100**
SOFTY POWER SUPPLY (ready built) **£20**
TEX EPROM Eraser **£33**
UV141 EPROM Eraser with timer **£77**
KEYBOARD 756 Full ASCII coded **£39**
KEYPAD 4 x 4 matrix (Reed switches) **350p**
STACK PACK 10 x C12 High Grade Cassettes incl. the unique stackable drawers and labels **525p**
(p&p on the above items is extra)

SWITCHES
TOGGLE: 2A, 250V
SPST **33p**
DPDT **44p**
4 pole on/off **54p**

SUB-MIN TOGGLE
SPST on/off **54p**
SPDT c/over **60p**
SPDT c/off **85**
SPDT biased both ways **105**
DPDT 6 tags **75p**
DPDT centre off **88p**
DPDT biased both ways **145p**
DPDT 3 positions on/on/on **185p**
4 pole 2 way **205p**

SLIDE 250V:
DPDT 1A **14p**
DPDT 1A c/off **15p**
DPDT ½A **13p**
4 pole 2-way **24p**

PUSH BUTTON 6A
with 10mm Button
SPDT **99p**
DPDT **145p**
SPDT **99p**
DPDT **145p**
Mini Non Lock
Push to Make **15p**
Red, Blue, Grn., Push to Break **25p**

DIL SWITCHES
SPST: 4 way **85p**; 6 way **95p**; 8 way **115p**; 10 way **145p.**

ROTARY (Adjustable Stop) SWITCHES:
1 pole/2 to 12 way; 2 pole/2 to 6 way; 3 pole/2 to 4 way; 4 pole/2 to 3 way **45p**
ROTARY: Mains DP 250V 4A on/off **66p**
ROTARY: Make your own multiway switch. Shafting Assembly: Has adjustable stop. Accommodates up to 6 wafers **90p**
WAFERS: (Break before Make) 1 pole/12 way; **2p**/6 way; **3p**/4 way; **4p**/3 way; **6p**/2 way **66p**
Mains DP Switch 250V/2A to fit **45p**
Spacers **4p**; Screen **6p**

'O' CONNECTORS (Cannon type)

Plugs	Sockets	Covers	Ptc
9way	**95p**	**125p**	**150p**
15way	**135p**	**195p**	**170p**
25way	**198p**	**284p**	**185p**
37way	**290p**	**398p**	

CRYSTALS

100KHz	323
200KHz	370
455KHz	383
1MHz	323
1.008M	395
1.28MHz	392
1.6MHz	323
1.8MHz	323
1.8432MHz	362
2MHz	305
2.4576MHz	362
3.2768M	323
3.57954M	195
4.000MHz	290
4.032MHz	323
4.19430M	270
4.433619M	135
5.0MHz	355
5.185M	323
5.24288M	425
6.0MHz	323
6.144MHz	295
6.5536M	200
6.5536MHz	290
7MHz	290
7.168MHz	290
7.680M	323
8.0MHz	392
8.08333M	362
8.867237M	362
9.375M	323
10.0MHz	323
10.7MHz	323
12MHz	392
14.31818M	362
16.0MHz	290
18MHz	323
18.432M	323
20.0MHz	323
26.69MHz	290
27.648M	323
38.6667M	350
48.0MHz	323
100.00MHz	323
116.0MHz	300

Parts available for ETI Projects

TRANSFORMERS (Mains Prim. 220-240V)
6-0-6V, 9-0-9V; 12-0-12V 100mA **98p**
3VA: 0-6V 0-6V (PCB mounting) **175p**
5VA: 6V-.5A 6V-.5A; 9V-.4A 9V-.4A, 12V-.3A 12V-.3A; 15V-.25A 15V-.25A **220p**
12V: 4.5V-1.3A 4.5V-1.3A; 6V-1.2A 6V-1.2A; 12V-.5A 12V-.5A; 15V-.4A ⅓⅓V-.4A; 20V-.3A 20V-.3A **250p** (30p p&p)
24VA: 6V-1.5A 6C-1.5A; 9V-1.3A 9V-1.3A; 12V-1A 12V-1A; 15V-.8A 15V-.8A; 20V-.6A 20V-.6A **320p** (55p p&p).
50VA: 6V-4A 6V-4A; 9V-2.5A 9V-2.5A; 12V-2A 12V-2A, 15V-1.5A 15V-1.5A; 20V-1.2A 20V-1.2A; 25V-1A 25V-1A; 30V-.8A 30V-.8A **365p** (60p p&p).
100VA: 12V-4A 12V-4A; 15V-3A 15V-3A; 20V-2.5A 20V-2.5A; 30V-1.5A 30V-1.5A; 40V-1.25A 40V-1.25A; 50V-1A 50V-1A **820p** (74p p&p). (NB: p&p charge to be added above our normal postal charge.)

VOLTAGE REGULATORS

1A	TO3	+ve	−ve	
5V	7805	**145p**	7905	**220p**
12V	7812	**145p**	7912	**220p**
15V	7815	**145p**		—
18V	7818	**145p**		—

1A	TO220	Plastic Casing		
5V	7805	**60p**	7905	**65p**
12V	7812	**60p**	7912	**65p**
15V	7815	**60p**	7915	**65p**
18V	7818	**60p**	7918	**65p**
24V	7824	**60p**		

100mA	TO92	Plastic Casing		
5V	78L05	**30p**	79L05	**65p**
6V	78L62	**30p**		—
8V	78L82	**30p**		—
12V	78L12	**30p**	79L12	**65p**
15V	78L15	**30p**	79L15	**65p**

LM300H	**170p**	LM723	**38p**
LM305H	**140p**	TAA550	**50p**
LM309K	**135p**	TBA625B	**95p**
LM317K	**350p**	ZDA1412	**150p**
LM317H	**240p**	78H05 + 5V/5A	
LM323K	**550p**		**595p**
LM325N	**240p**	78HG +5V to +25V	
LM326N	**240p**	5A	**650p**
LM327	**270p**	79HG	**850p**

ALUM. BOXES WITH LID

	p
3x2x1"	65
4x2½x2"	85
4x2¾x1½"	85
4x2¾x2½"	103
4x4x1½"	85
4x4x2½"	120
5x4x2"	95
5¼x2¾x2½"	130
5¼x4x1½"	99
5¼x4x2½"	120
6x4x2"	120
6x4x3"	148
7x5x2½"	165
7x5x3"	180
8x6x3"	210

OPTO

LEDs with Clips	
TIL209 Red	13
TIL211 Grn.	17
TIL212 Yel.	18
TIL220 2" Red	14
2" Green, Yellow or Amber	18
2" High Bright Red	49
2" Flashing Red	48
2" Red/Green	46
Square LEDs, Red, Green, Yellow	30
LD271 Infra Red	40
SFH205 Detector	90
TIL32 Infra Red	65
TIL78 Detector	75
BARGRAPH: Red 10 segments	225
LS400	255
OCP71	120
ORP12	63
ORP61	85
2N5777	45

ISOLATORS

IL74	55
TIL111/2/4	90

PANEL METERS

FSD
60x46x 35mm
0-50μA
0-100μA
0-500μA
0-1mA
0-5mA
0-10mA
0-50mA
0-100mA
0-500mA
0-1A
0-2A
0-25V
0-50V AC
0-300V AC
"S" Meter
"VU"
445p each
4¼x3¼x1½"
0-50μA
0-100μA
0-500μA
595p each

7 Segment Displays

TIL307	675
TIL312 .3" CA	105
TIL313 .3" CC	105
TIL321 .5" CA	115
TIL322 .5" CC	115
DL704 .3" CC	99
DL707 .3" CA	99
DL747 .6" CA	180
.8" Orange CA	250
FND357 Red	120
FND500	115
3" Green CA	150
6" Green CA	215
3" ± 1 Red CA	150
3" ± 1 Green CA	150
DVM176	**1885**
LCD 3½ Digits	**675**
LCD 4 Digits	**750**
LCD 6 Digits	**850**

LS245	350	LS373	150	4016	35	4054	130	4175	120	4522	150
LS247	135	LS374	150	4017	70	4055	130	4194	115	4526	98
LS248	135	LS375	150	4018	78	4056	135	4408	790	4527	125
LS249	135	LS377	199	4019	42	4057	2850	4409	790	4528	100
LS251	130	LS378	140	4020	85	4059	575	4410	750	4529	150
LS253	85	LS379	215	4021	90	4060	110	4411	950	4530	90
LS257	85	LS384	250	4022	85	4061	1225	4412F	1250	4531	130
LS258	120	LS385	420	4023	24	4062	995	4412V	1520	4532	120
LS259	180	LS386	85	4024	60	4063	120	4415F	480	4534	510
LS261	460	LS390	140	4025	24	4066	46	4415V	850	4536	310
LS266	75	LS393	140	4026	170	4067	430	4419	280	4538	145
LS273	180	LS395	210	4027	45	4068	26	4422	570	4539	120
LS275	320	LS396	199	4028	92	4069	22	4432	1050	4541	150
LS279	85	LS398	275	4029	98	4070	25	4435	850	4543	150
LS280	250	LS399	230	4030	55	4071	25	4440	999	4549	395
LS283	80	LS445	140	4031	185	4072	25	4450	350	4553	399
LS290	130	LS447	195	4032	125	4073	25	4451	350	4554	192
LS293	130	LS490	245	4033	175	4075	23	4452		4555	85
LS295	215	LS668	105	4034	213	4076	85	4490F	350	4556	60
LS298	215	LS669	105	4035	95	4077	30	4490V	750	4557	425
LS299	420	LS670	270	4036	275	4078	28	4501	28	4558	174
LS300	175	LS673	750	4037	115	4081	26	4502	105	4559	450
LS302	175	LS674	850	4038	110	4082	25	4503	65	4560	199
LS320	270			4039	299	4085	90	4506	75	4561	104
LS323	460			4040	85	4086	90	4507	48	4562	525
LS324	200			4041	80	4089	150	4508	280	4566	195
LS325	320			4042	70	4093	55	4510	85	4568	299
LS326	330			4043	80	4094	210	4511	98	4569	195
LS327	315			4044	80	4095	95	4512	84	4572	36
LS346	185			4045	175	4096	95	4513	225	4580	495
LS347	150			4046	96	4097	340	4514	220	4581	320
LS348	190			4047	98	4098	115	4515	250	4582	135
LS352	185			4048	65	4099	150	4516	90	4583	105
LS353	185			4049	35	4160	115	4517	415	4584	55
LS365	85			4050	38	4161	115	4518	90	4585	99
LS366	85			4051	86	4162	115	4519	80	4597	330
LS367	85			4052	86	4163	115	4520	90	4598	390
LS368	80			4053	86	4174	110	4521	210	40106	99

CMOS

4000	14
4001	14
4002	15
4006	86
4007	19
4008	76
4009	46
4010	50
4011	18
4012	24
4013	43
4014	80
4015	82

TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics – now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians
Radio, T.V. Electronics Technicians
Radio Amateurs
Electrical Installation Work

Diploma Courses

Colour T.V. Servicing
CCTV Engineering
Electronic Engineering & Maintenance
Computer Engineering and Programming
Radio, T.V. and Audio, Engineering & Servicing
Electrical Engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE BOOK

To ICS, Dept. Z263, Intertext House, London SW8 4UU

Name _____

Address _____

_____

_____ Age _____

ICS

To ICS, Dept. 265F, Intertext House
London SW8 4UJ
or telephone 01-622 9911 (all hours)

DIGEST

OOPS

Digital Test Meter

Some constructors of the DTM (September '80) have reported problems with the DVM module blowing. This can be prevented by putting a 10M resistor in series with the IN HI pin of the module.


On page 83 the overlay for the resistance measurement board (bottom overlay) shows the common of R43, R44, R45 and C15 connected to IC7 pin 4. In fact IC7 pin 4 should go only to the −6 V takeoff point and C7 −ve. Cut the PCB track just above R45 (page 80 Fig.1 shows the correct wiring).

Vocoder

Two of the ICs in the Vocoder (September '80) are listed incorrectly. In the circuit diagram and Parts List for the internal excitation board, IC5 is a 4030 and IC6 is a 4006.

Breadboard 80

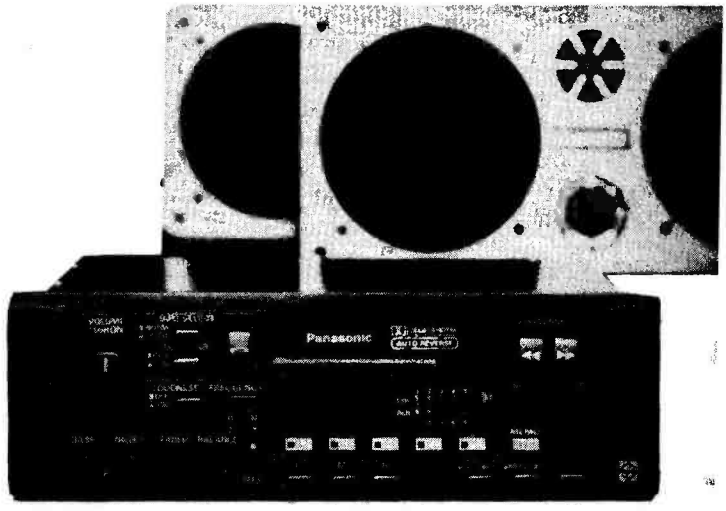In our report on Breadboard 80 (in the February News Digest), our reporter, no doubt overcome by the occasion, said that our celebrity guest was Brian Rix. In fact Mr Rix, a radio amateur, was at the show as a guest of Practical Wireless, to whom we offer our apologies.



Panasonic Car-Fi

Panasonic has introduced what it believes to be the first full hi-fi stereo car radio/cassette that will fit into a standard DIN size dashboard aperture. The CQ 973 combines microprocessor electronics with full hi-fi specifications and according to Panasonic it is the most advanced in-car system available.

For those of you who can afford the £395.95 price tag, the CQ 973 offers digital frequency readout, three waveband stereo radio, (LW/MW/FM), electronic preset tuning, auto-seek tuning, an auto-reverse cassette player with a Dolby Noise Reduction system, and an output of 100 W. The radio functions are all push-button controlled, with a total of 15 preset stations (five on each band); as an additional safety feature the driver can also keep his hands on the steering wheel and tune the radio by footswitch. The bright green digital frequency readout also functions as a clock, and at night all the major controls are illuminated.


The unit is fitted with normal/metal tape selection and both the fast forward and rewind buttons can be locked in. Separate bass, treble and loudness controls are provided. For further information on the CQ 973 and the rest of Panasonic's in-car entertainment range, contact any of Panasonic's authorised dealers.

Take It Anywhere

New from JVC is the CX 610GB, a 6" VHF/UHF portable colour TV/monitor. This compact unit can be taken anywhere; it is capable of PAL and SECAM TV reception so you can receive programmes in any country that has one of the following TV systems — PAL B, G, or I system and SECAM B, G, D, K, or KI system (both CCIR continental and OIRT standards). The CX 610GB's colour system automatically switches to the broadcast system being used and the corresponding sound IF frequency can then be selected. The set has a newly developed JVC precision in-line picture tube, giving excellent colour pictures, and its highly sensitive swivel antenna ensures good quality reception wherever you are. The flexibility of this unit is further enhanced by a four-way power supply — from the household mains, ordinary batteries, its own rechargeable battery pack or from a 12 V DC car or boat battery.

The CX 610GB can also function as an on-location video monitor when used in conjunction with a colour video camera and portable video recorder. You can even record off-the-air television broadcasts out-of-doors by connecting the CX 610GB to a portable video recorder. The recommended retail price is £259 (including VAT), and further information is available from JVC (UK) Ltd, Eldonwell Trading Estate, Staples Corner, 6-8 Priestley Way, London NW2 7AF.



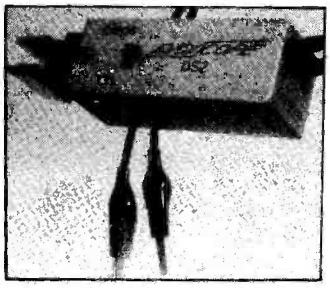

Logic Monitor

If you're in the business of developing or trouble-shooting digital circuits then you'll be interested in the Digiscope DS2 Logic Monitor. The device simply clips over any 14 or 16 pin DIL logic IC during operation, and indicates the state of each pin, either 0 or 1. Each pin has its state shown simultaneously on a 16-LED display, enabling circuit action and faults to be traced with ease. The DS2 is powered from either the circuit supply or an external source and draws negligible current from the IC under test, so circuit operation is unaffected. The input threshold is adjustable to suit either TTL or CMOS ICs. The monitor can also be used to check free packages; power is applied to the supply pins and since the DS2 pulls all the inputs high, operation can be checked by grounding the appropriate inputs and observing the effect. The DS2 is housed in a tough aluminium case and is suitable for use in industrial environments; the case is only 1" wide so several ICs may be checked side-by-side simultaneously. There is a range of accessories available including plugs and an extension lead for remote monitoring. The Digiscope DS2 costs £27.40 and further information is available from the manufacturers, J.E. Sinclare & Co., 82 Plumstead Common Road, London SE18 3RE.

Micro Talk

General Instrument Microelectronics have announced the introduction of a new speech synthesis chip, the SP0256. It's a 28 lead LSI device, designed to generate up to 256 discrete sequences of human speech or other complex sounds stored in its built-in 16K ROM. External expansion can increase the SP0256's repertoire to almost 3825 sequences. Commonly used sounds can be stored once and called from memory when necessary, reducing data storage requirements. Applications envisaged include warning systems, radar, test gear and security systems.

TRANSCENDENT 2000 SINGLE BOARD SYNTHESIZER

Designed by consultant Tim Orr (formerly synthesizer designer for EMS Ltd.) and featured as a constructional article in ETI, this live performance synthesizer is a 3 octave instrument transposable 2 octaves up or down giving sweep control, a noise generator and an ADSR envelope shaper. There is also a slow oscillator, a new pitch detector, ADSR repeat, sample and hold, and special circuitry with precision components to ensure tuning stability amongst its many features.

The kit includes fully finished metalwork, fully assembled solid teak cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or ½% metal film), and it really is complete — right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit — you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibreglass PCB printed with component locations. All the controls mount directly on the main board, all connections to the board are made with connector plugs and construction is so simple it can be built in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesizer comparable in performance and quality with ready-built units selling for many times the price.


Comprehensive handbook supplied with all complete kits! This fully describes construction and tells you how to set up your synthesizer with nothing more elaborate than a multi-meter and a pair of ears!

COMPLETE KIT ONLY £168.50 + VAT!



Cabinet size 24.6" x 15.7" x 4.8" (rear) 3.4" (front)

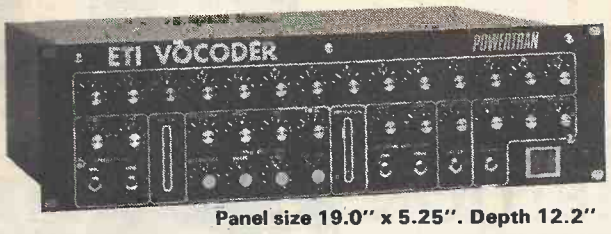COMING SHORTLY! 1024 NOTE COMPOSER/SEQUENCER — LESS THAN £100



Panel size 19.0" x 5.25". Depth 12.2"

ETI VOCODER

COMPLETE KIT ONLY £195 + VAT!


Kit includes FREE foot control and test oscillator!

Featured as a construction article in **Electronics Today International** this design enables a vocoder of great versatility and high intelligibility to be built for an amazingly low price.
14 channels are used to achieve its high intelligibility, each channel having its own level control. There are two input amplifiers, one for speech either from microphone or a high level source e.g. mixer or cassette deck and one for external excitation (the substitution signal) from either high or low level sources. Each amplifier has its own lever control and a rather special type of tone control giving varying degrees of bass boost with treble cut or treble boost with bass cut. The level of the speech and excitation signals are monitored by LED PPM meters with 10 lights — 7 green and 3 red which indicate the level at 3dB steps. There are three internal sources of excitation — a noise generator and two pulse generators of variable frequency and pulse width. Any of the internal sources and the external source can be mixed together. There is a voiced/unvoiced detector which substitutes noise for the excitation signal at the points in speech where the vocal chord derived sounds of the speaker are substituted for by the unvoiced sounds of sibilants, etc. There is a slew rate control which smooths out the changes in spectral balance and amplitude enabling a change of the speech into singing or chanting and other special effects. A foot switch is provided to permit a complete freeze in spectral balance and amplitude whenever required. An LED on this indicates when the freeze is in operation.
An output mixer allows mixing of the speech, external excitation and vocoder output. The majority of the components fit into the large analysis/synthesis board with the rest on 8 much smaller boards with the controls and sockets mounted on them for ease of construction. Connectors are used for the small amount of wiring between the boards.
The kit includes fully finished metalwork, professional quality components (all resistors 2% metal oxide) nuts, bolts, etc. — even a 13A plug!

TRANSCENDENT DPX MULTI-VOICE SYNTHESIZER

Another superb design by synthesizer expert Tim Orr published in Electronics Today International

COMPLETE KIT ONLY £299 + VAT!

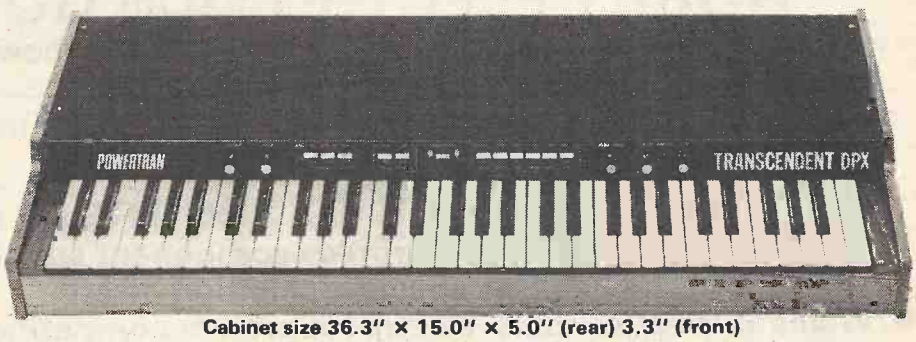

Cabinet size 36.3" x 15.0" x 5.0" (rear) 3.3" (front)

The Transcendent DPX is a really versatile 5 octave keyboard instrument. These are two audio outputs which can be used simultaneously. On the first there is a beautiful harpsichord or reed sound—fully polyphonic, i.e. you can play chords with as many notes as you like. On the second output there is a wide range of different voices, still fully polyphonic. It can be a straightforward piano as a honky tonk piano or even a mixture of the two! Alternatively you can play strings over the whole range of the keyboard or brass over the whole range of the keyboard or should you prefer — strings on the top of the keyboard and brass as the lower end (the keyboard is electronically split after the first two octaves) or vice-versa or even a combination of strings and brass sounds simultaneously. And on all voices you can switch in circuitry to make the keyboard touch sensitive! The harder you press down a key the louder it sounds — just like an acoustic piano. The digitally controlled multiplexed system makes practical touch sensitivity with the complex dynamics law necessary for a high degree of realism. There is a master volume and tone control, a separate control for the brass sounds and also a vibrato circuit with variable depth control together with a variable delay control so that the vibrator comes in only after waiting a short time after the note is struck for even more realistic string sounds.

To add interest to the sounds and make them more natural there is a chorus/ensemble unit which is a complex phasing system using CCD (charge coupled device) analogue delay lines. The overall effect of this is similar to that of several acoustic instruments playing the same piece of music. The ensemble circuitry can be switched in with either strong or mild effects.

As the system is based on digital circuitry digital data can be easily taken to and from a computer (for storing and playing back accompaniments with or without pitch or key change, computer composing, etc., etc.).

Although the DPX is an advanced design using a very large amount of circuitry, much of it very sophisticated, the kit is mechanically extremely simple with excellent access to all the circuit boards which interconnect with multiway connectors, just four of which are removed to separate the keyboard circuitry and the panel circuitry from the main circuitry in the cabinet.

The kit includes fully finished metalwork, solid teak cabinet, professional quality components (all resistors 2% metal oxide), nuts, bolts, etc., even a 13A plug!

POWERTRAN

MANY MORE KITS ON PAGE 107. MORE KITS AND ORDERING INFORMATION ON INSIDE FRONT COVER

All projects on this page can be purchased as separate packs, e.g. PCBs, components sets, hardware sets, etc. See our free catalogue for full details and prices.

Hobby Electronics BRISTOL EXHIBITION CENTRE '81

Hobby Electronics BRISTOL EXHIBITION CENTRE '81

Hobby Electronics BRISTOL EXHIBITION CENTRE '81

COMPUTERS ● AUDIO ● RADIO ● MUSIC ● LOGIC ● COMPONENTS ● CB

HOBBY ELECTRONICS GOES WEST

London has more than its fair share of electronics shows, but we know that electronics enthusiasts are by no means limited to the capital. For that reason the first annual Hobby Electronics Show is to be held in Bristol — centre of the South-West.

What's to see there?

- **major electronics component suppliers**
- **special exhibition offers**
- **Wales & West schools' electronic project competition (*has your school submitted an entry yet? Available from Hobby Electronics 81)**

TICKETS — at the door — **ADULT** : £1.00. **CHILD, STUDENT, OAP** : 50p.

GAMES ● KITS ● TEST GEAR ● MAGAZINES ● SPECIAL OFFERS ● BOOKS

OPEN DAYS :

Friday May 29th : 10am — 7pm ● Saturday May 30th : 10am — 6pm ● Sunday May 31st : 10am — 4pm

Order your tickets now from :
Exhibition Manager,
Hobby Electronics 81,
145 Charing Cross Road,
London WC2H 0EE.

Hobby Electronics BRISTOL EXHIBITION CENTRE '81



CARAVAN LIGHTS CHECKER

A project that will pay for itself in the first ticket from the police that you don't collect. Submitted by Graham Packer of Soutergate.

Many ETI readers, besides boring the pants off their neighbours with dreary electronics, are just as anti-social when it comes to cluttering up the highways with their sluggish caravans. Now that they (and their caravans) are in hibernation until summer, the time is at hand to reach for soldering iron and component catalogue and make amends.

Most caravans receive their power supply and lighting signals by way of a multiway plug and socket, terminating on a 'choc-block' terminal strip under the front seat/bed. This is where the 'guts' of the project goes. The cable is merely chopped and the large plastic box inserted. The display unit can be mounted anywhere that is visible from the driving mirror and double sided tape (the thick foamy kind) may be used to hold it on the wardrobe or side of the kitchen unit.

For once, no complicated electronics; just the most basic of electromagnetic devices, the relay, albeit in its more refined form of the reed insert. These reeds, originally developed for electronic telephone exchanges, need about 20 to 50 ampere turns to pull them in. The current drawn by a caravan sidelight, brakelight or indicator lamp can be found by calculation (or just asking people) and the correct number of turns wound around the reed.

Reed inserts may be obtained from a number of sources and be of dubious vintage. Therefore, it's best to wind on 40 or 50 turns of 22 swg insulated wire and check them out first with the test circuit shown.

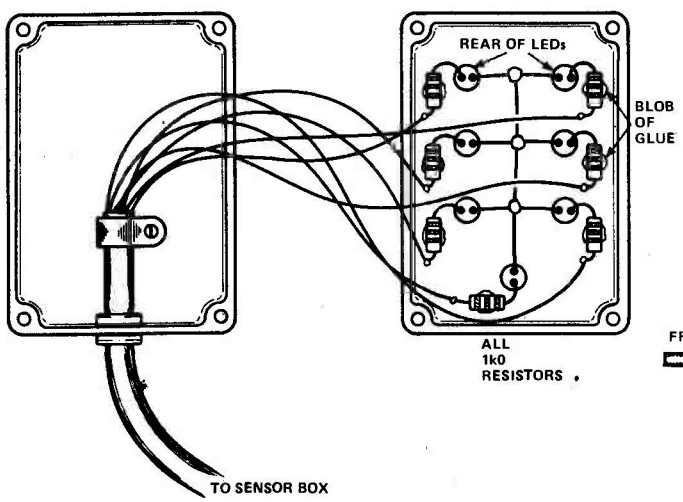


Fig. 1 Construction details of the display box.

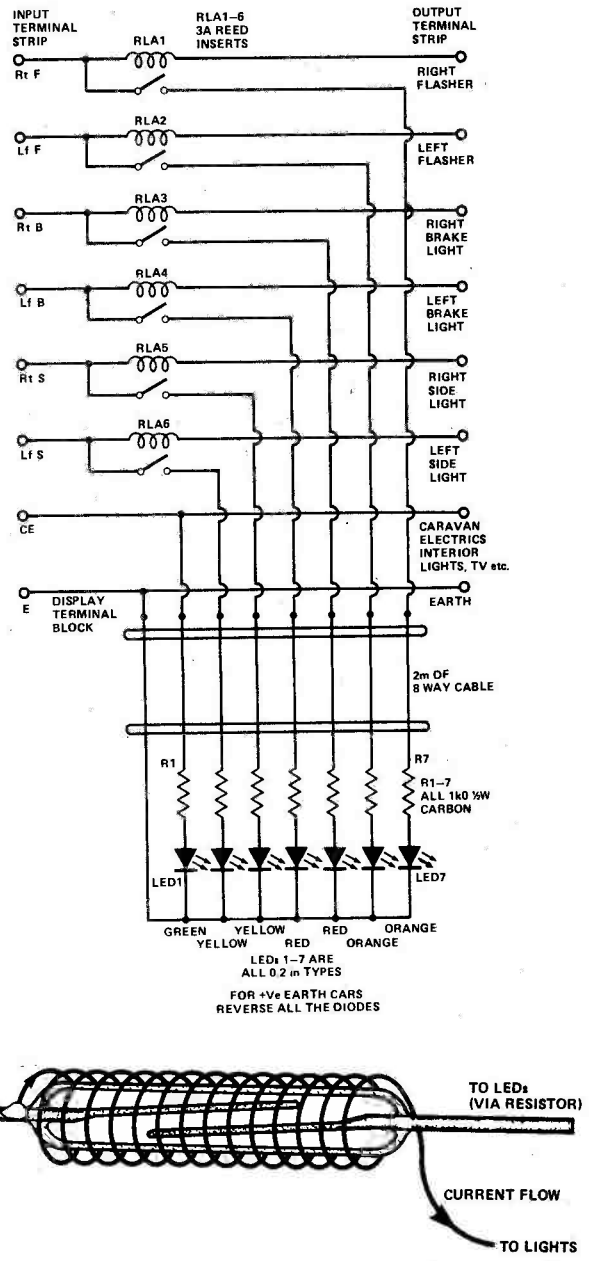


Fig. 2 Circuit diagram with relay assembly/wiring details.

Fig. 3 Construction details of the sensor box.


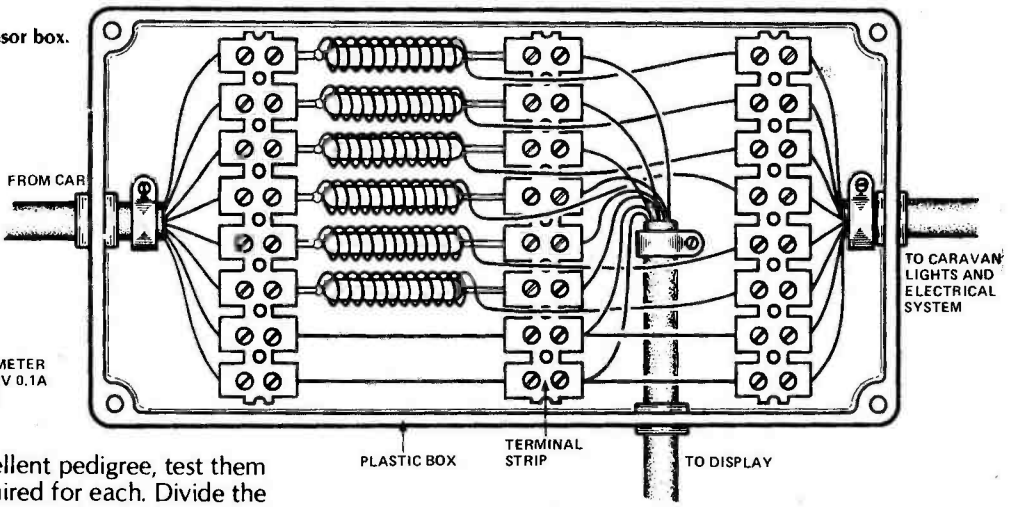


Fig. 4 This simple circuit can be used to check out reed relays.

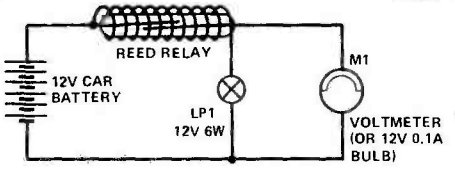

If the reeds do not have an excellent pedigree, test them and decide how many turns are required for each. Divide the ampere turns by the current to be drawn and there's the number you need. Add 25% for luck. As a rule of thumb, 6 W sidelights need about 40 turns in two or three layers, or 20 turns if they are fore and aft. You could put separate current sensors in each line and make your caravan look like a mobile Blackpool Illuminations! Brake and indicator lights need only 12 turns.

Solder one end of a length of 20 swg insulated wire to one end of a reed and wind carefully along its entire length. Be careful not to break the glass as it will slice into your fingers with the greatest of ease. Hold the reed in your left hand with the loose end of wire pulled taut by your little finger and apply cyanoacrylate (Superglue). Two days later it should be possible to remove the completed current sensing relay from your hand!

Install the reeds between the two choc-blocks as shown in the diagram by holding the terminal blocks on a flat surface to ensure that no twisting action takes place when the assembly is finally installed in its box. Cyanoacrylate may now be used to mount the complete assembly in its box. Complete the wiring and install in your beloved behemoth.

The green 'power-on-to-the-caravan' light only consumes 15-20 mA and as long as the caravan is being pulled daily (as it would be on holiday) the overnight drain is negligible.

A complete kit of parts, including solder and superglue is available from Packer Communications, Bridge End Barn, Soutergate, Cumbria LA17 7TW for £12.75 including post and VAT.

ETI

OSCILLOSCOPES

How to use them – How they work · by Ian Hickman

Oscilloscopes are essential tools for checking circuit operation and diagnosing faults, and an enormous range of models is available. But which is the right scope for a particular application? Which features are essential, which not so important? What techniques will get the best out of the instrument?

Ian Hickman, experienced in both professional and hobbyist electronics, has written this book to help all oscilloscope users – and potential users. After introducing basic principles for readers new to the subject, he explains in detail the features of typical simple and advanced real-time oscilloscopes, plus accessories such as probes and cameras. He advises on how to choose and operate scopes, and how to avoid common pitfalls; he also describes special-purpose instruments, from small portable scopes to storage scopes and spectrum and logic analysers. Finally, to give readers a better understanding of how oscilloscopes work, he explains the principles of the cathode-ray tube and basic scope circuitry.

NEW BOOK

Illustrated with many photographs and two-colour diagrams, the book will appeal to everyone who needs to know about oscilloscopes, from the school student to the graduate, from the hobbyist to the technician.

Available from your local bookseller or in case of difficulty from the Publisher.

BROADEN YOUR SCOPE NOW!

Cut out this coupon and return it to Patricia Davies, Marketing Manager, at the address below.

Please send me copy/copies of Oscilloscopes (Hickman) 0 408 00472 X Illustrated paperback. 128 pages (216 x 138mm) at £3.45 each.

I enclose a cheque/PO for £_____ in total payment

From

Address

_____ (ETI 4 81)

Newnes Technical Books
Borough Green, Sevenoaks, Kent TN15 8PH

ETIPRINTS

ETIPRINTS offer you the easy way to produce high quality printed circuit boards. Each ETIPRINTS sheet contains a set of etch resistant rub down transfers of the printed circuit board designs for several of our projects.

ETIPRINTS are made from our original artwork ensuring a neat and accurate board. We thought ETIPRINTS were such a good idea that we have patented the system (patent numbers 1445171 and 1445172).

PARTS LIST

040A	ETI 80 VCO/VCLFO	Feb 80
040B	ETI 80 PSU Tuning Fork Hi-Lo Filter Coin Toss	Feb 80
041A	Audiophile Driver Amp VCA Signal Tracer Heater Controller Main Board Electromyogram	Mar 80
041B	ETI 80 VCM Heater Controller Sensor	Mar 80
046A	ETI 80 Dual VCA 100 W Power Amplifier	Aug 80
046B	Capacitance Meter US Alarm BGM 100 W Amplifier Logic Tester 100 W Power Amp	Aug 80
047A	Digital Test Meter	Sep 80
047B	Vocoder Internal Excitation	Sep 80
	Speed Control DTM Switching Board RIAA Preamp	
047C	ETI 80 Envelope Shaper TV Sound Survival	Sep 80
048A	Sustain/Fuzz Box Flash Trigger FM Radio Control Receiver: (Top side) (Bottom side) FM Radio Control Transmitter	Oct 80
048B	Vocoder Slew Rate Control Vocoder Output Amp Vocoder Input Amp Vocoder PSU Vocoder LED PPM Display	Oct 80
048C	Cassette Interface ETI 80 Monitor Amp	Oct 80
049	AF Generator Multi-Option Board Space Invasion PSU	Nov 80

BUYLINES

Sheets for Sep 79, Dec 79, Jan 80 and April - July 80 are temporarily out of stock. Earlier ETIPRINT sheets are available.

Send a cheque for PO (payable to ETI) for £1.20 per sheet with details of the project for which you require an ETIPRINT, and the month and year of publication to:

ETIPRINTS,
ETI,
145 Charing Cross Road,
London WC2H 0EE.


HOW IT WORKS

Lay down the ETIPRINT and rub over with a soft pencil until the pattern is transferred to the board. Peel off the backing sheet carefully making sure that the resist has transferred. If you've been a bit careless there's even a 'repair kit' on the sheet to correct any breaks!

ETIPRINTS

The SENSATIONAL CROFTON Offer

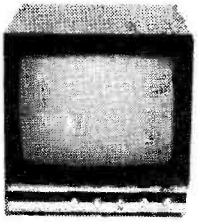9" metal cased monitors at the lowest price ever – £48.50 plus VAT and P & P.
P4 phosphor standard. P31 and P39 available at an extra £11.50 total.





Sony colour camera type 2010P only £375.00 total including VAT and P & P. 12v operation IV composite video out. adapter box and modulator available for £25.00 total when purchased with camera. Normally £69.50.

Ask for Crofton Mail Order Catalogue.

All major credit cards accepted.

All items subject to availability. The above prices include VAT. Carriage will be charged at cost.

Phone or write to

CROFTON ELECTRONICS LIMITED
35 Grosvenor Road, Twickenham, Middx TW1 4AD.
Tel: 01-891 1923/1513



68 LARGE PAGES

The larger Catalogue that means

FREE POSTAGE IN U.K.

ADDITIONAL DISCOUNTS

KEEN PRICES

GUARANTEED SATISFACTION

GOOD STOCKS

We pay postage

Semi-Conductors • I.C.s • Opto-devices • Rs and Cs in great variety • Pots • Switches • Knobs • Accessories • Tools • Materials • Connectors

ELECTROVALUE

FREE FOR THE ASKING

ELECTROVALUE LTD. (Dept. HE4) 28 St. Jude's Road. Englefield Green. Egham. Surrey TW20 0HB
Telephone: (STD 0784) (London 87) 33603. Telex: 264475

MICROPROCESSORS, MEMORIES, TTL

MICROPROCESSORS	
Z80 CPU	6.84
Z80 CTC	4.75
Z90 PIO	4.75
Z80 SIO-0	20.11
Z80 SIO-1	20.11
Z80 SIO-2	20.11
Z80 DART	13.44
Z80 DMA	17.62
Z80A CPU	8.23
Z80A CTC	5.78
Z80A PIO	5.78
Z80A SIO-0	24.17
Z80A SIO-1	24.17
Z80A SIO-2	24.17
Z80A DART	21.02
Z80A DMA	21.02
6800	3.82
6802	5.74
6809	18.94
6810	1.43
6821	1.93
6840	5.87
6850	1.95

MOS MEMORIES	
2708 1kx8 450ns	3.25
2716 2kx8 450ns	5.75
2114 1kx4 200ns	2.50
4027 4kx1 200ns	1.65
4116 16kx1 150ns	2.95
4116 16kx1 200ns	2.50

8-BIT CONVERTERS	
ZN425E(A/D)	3.50
ZN427E(A/D)	6.28
ZN426E(D/A)	3.00
ZN428E(D/A)	4.78
ZN429E(D/A)	2.10
Data Converter Handbook	1.00

TTL	
74LS 00	0.20
74LS 01	0.21
74LS 02	0.20
74LS 03	0.20
74LS 04	0.21
74LS 05	0.21
74LS 08	0.20
74LS 09	0.21
74LS 10	0.20
74LS 11	0.21
74LS 12	0.21
74LS 13	0.41
74LS 14	0.71
74LS 15	0.21
74LS 20	0.20
74LS 21	0.21
74LS 22	0.21
74LS 26	0.27
74LS 27	0.21
74LS 28	0.25
74LS 30	0.20
74LS 32	0.20
74LS 33	0.25
74LS 37	0.25
74LS 38	0.25
74LS 40	0.20
74LS 42	0.56
74LS 47	0.58
74LS 49	0.86
74LS 51	0.20
74LS 54	0.21
74LS 55	0.21
74LS 73	0.30
74LS 74	0.27
74LS 75	0.42
74LS 76	0.30
74LS 83	0.76
74LS 86	0.26
74LS 90	0.52
74LS 91	1.13
74LS 92	0.56
74LS 93	0.55
74LS 95	0.68
74LS109	0.36
74LS112	0.36
74LS113	0.36
74LS114	0.36
74LS122	0.63
74LS123	0.81
74LS124	1.49
74LS125	0.41
74LS126	0.41
74LS132	0.71
74LS136	0.41
74LS138	0.56
74LS139	0.56

TTL	
74LS145	1.06
74LS151	0.49
74LS153	0.49
74LS155	0.70
74LS156	0.70
74LS157	0.50
74LS158	0.56
74LS160	0.61
74LS161	0.61
74LS162	0.61
74LS163	0.61
74LS164	0.71
74LS174	1.06
74LS175	0.84
74LS181	2.10
74LS190	0.85
74LS191	0.85
74LS192	0.97
74LS193	0.97
74LS194	0.58
74LS195	0.58
74LS196	0.96
74LS197	0.96
74LS221	0.90
74LS240	1.41
74LS242	1.19
74LS243	1.19
74LS244	1.18
74LS245	1.69
74LS247	0.57
74LS248	1.05
74LS249	1.05
74LS251	0.64
74LS253	0.64
74LS258	0.56
74LS259	1.61
74LS273	1.37
74LS279	0.51
74LS283	0.63
74LS293	0.73
74LS366	0.54
74LS367	0.54
74LS368	0.54
74LS373	1.11
74LS374	0.70
74LS375	0.70
74LS377	1.37
74LS378	1.03
74LS379	0.78
74LS386	0.41
74LS390	0.96
74LS393	0.85


All devices brand new, full spec. and fully guaranteed. Please add 15% VAT (and 50p post and packing on orders under £10). All orders despatched by return of post. E.&O.E.

MIDWICH

Computer Co. Ltd., Hewitt House
Northgate Street, Bury St. Edmunds
Suffolk IP33 1HQ
Tel: (0284) 701321 Telex: 817682


PCB FOIL PATTERNS

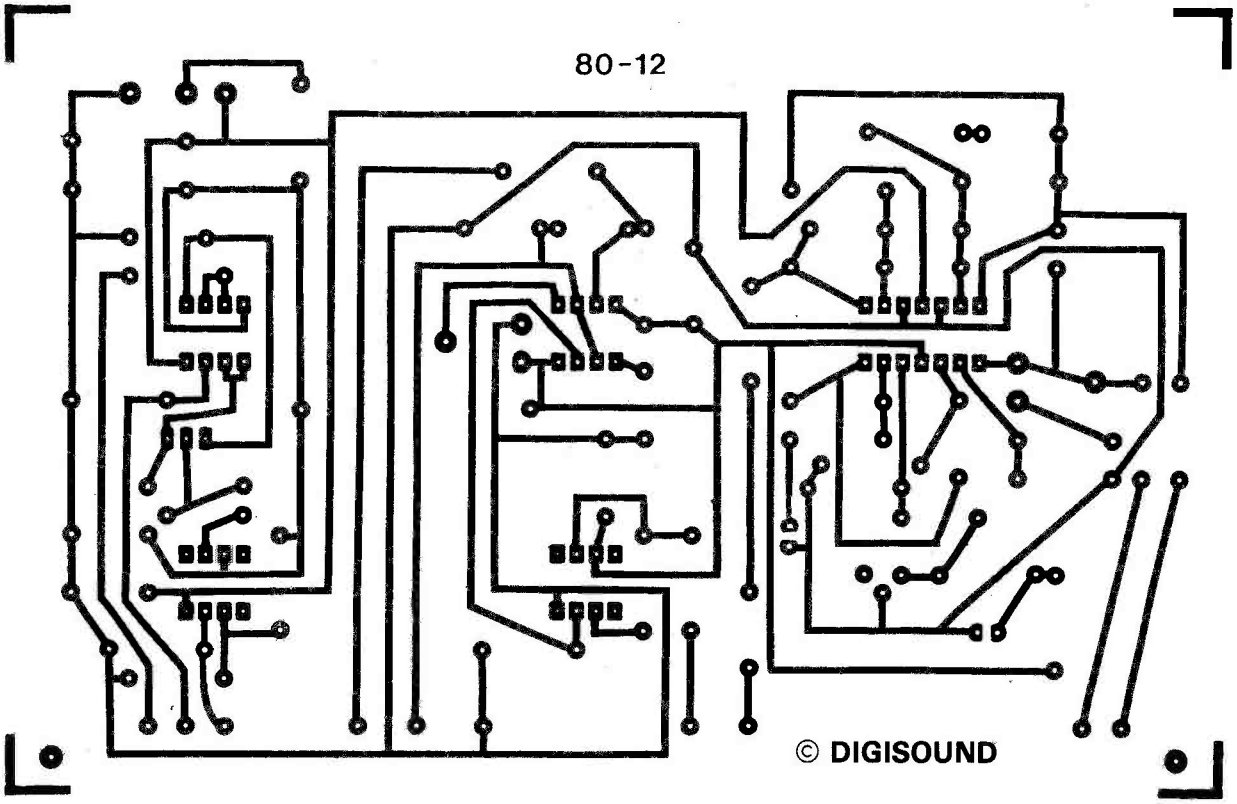
Please note that the foil pattern for the VCSA is too large to go into the magazine. A large SAE will secure a photocopy.




Above: Foil pattern for this month's Project 80 module. Note that Digisound hold the copyright on this board and firms may not reproduce the PCBs for sale.

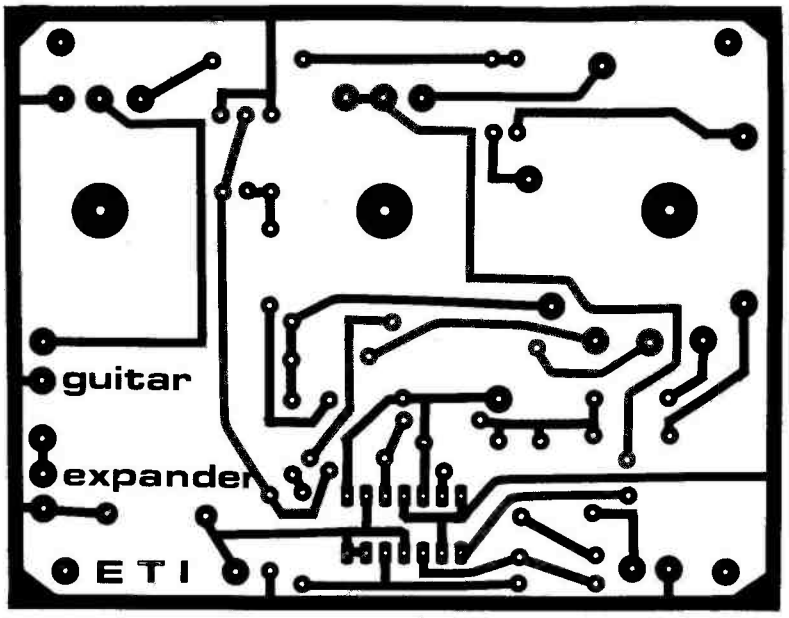
Right: Foil pattern for the guitar expander.



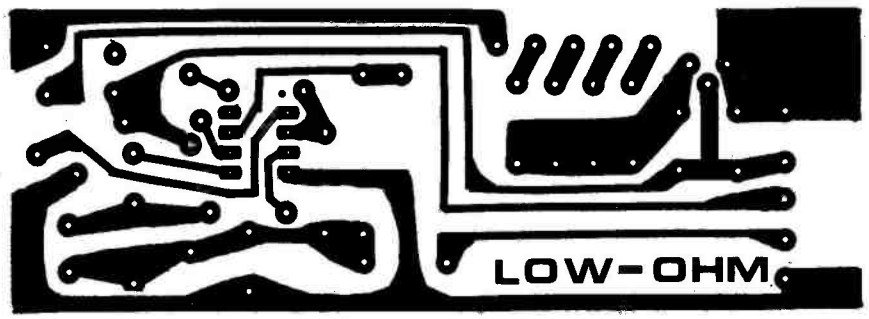


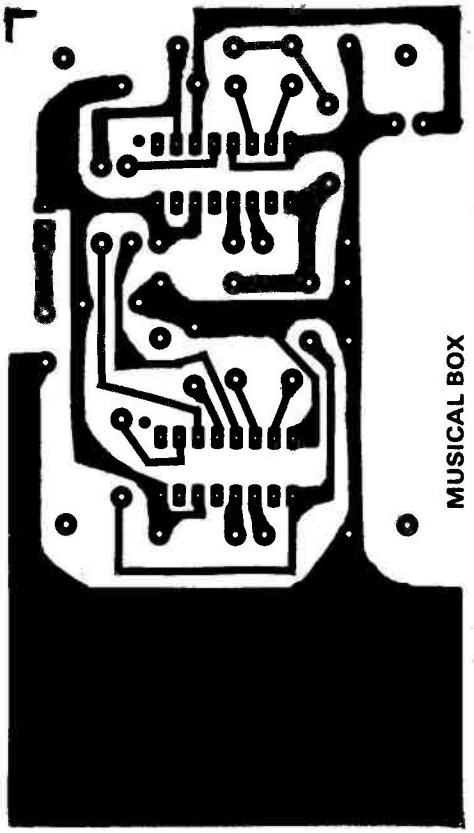

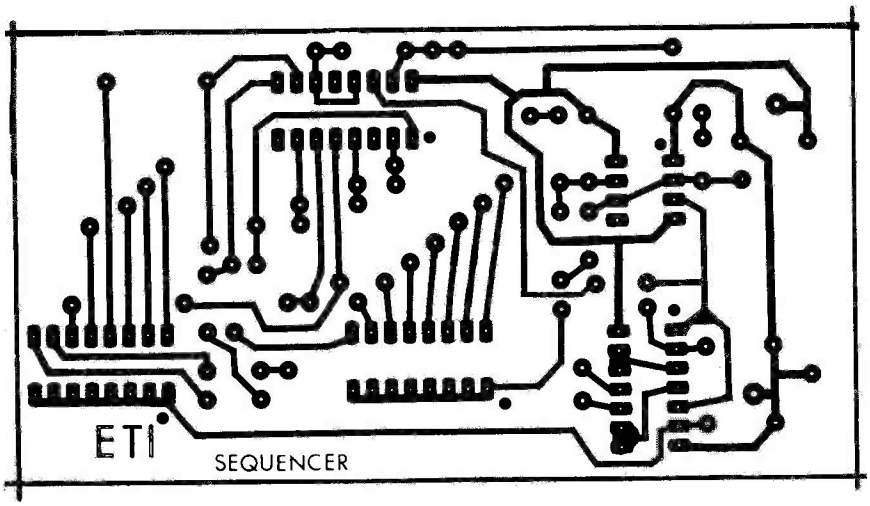Above: The Low-ohm Meter foil pattern.
Right: Musical Box PCB — this has been designed to fit into the specified case.



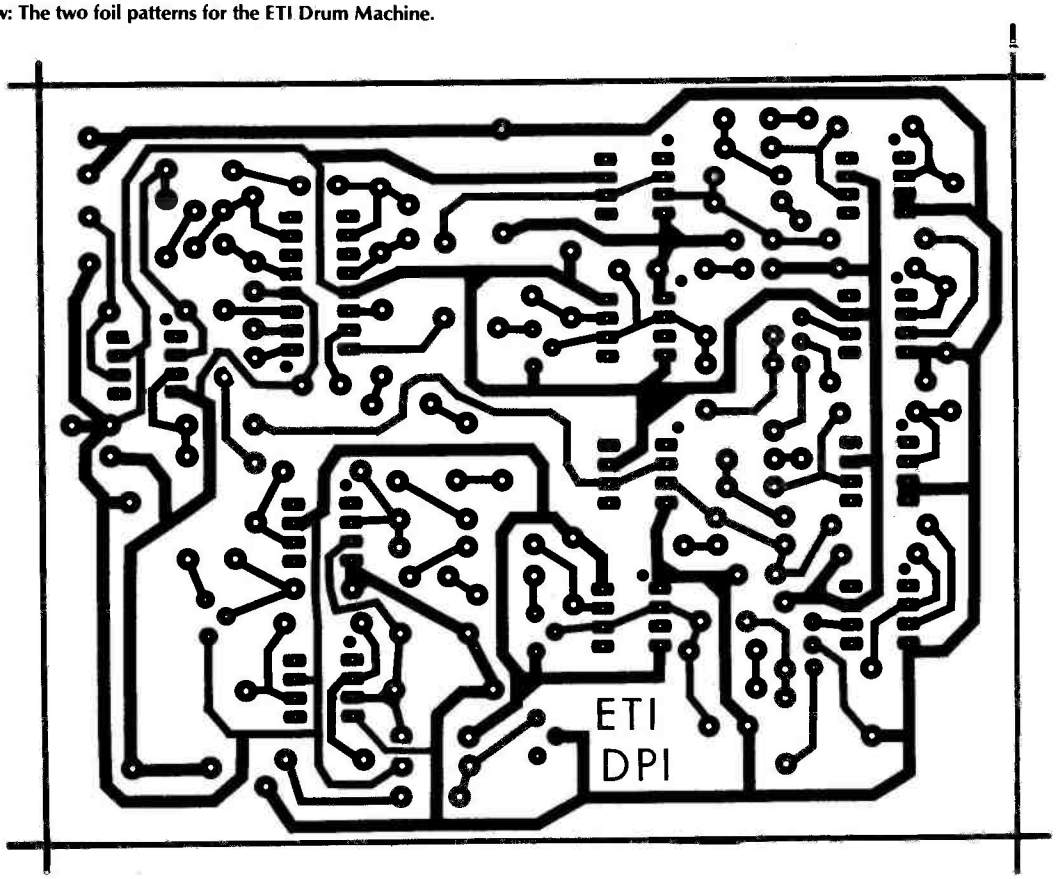Above and below: The two foil patterns for the ETI Drum Machine.



HAMEG

OSCILLOSCOPES

Top Performance In Every Range



HM 307

HM 312 **£220**
Y: Bandwidth DC-20MHz (-3dB) • Sensitivity 5mV-20V/cm (±3%)
X: Timebase 0.2s-40ns/cm incl. x5 Magn. • Trig. 3Hz-30MHz (4mm)
Dual trace • X-Y Operation • Calibrator • Screen 8x10cm • 2kV

HM 412 **£350**
Y: Bandwidth DC-20MHz (-3dB) • Sensitivity 2mV-20V/cm (±3%)
X: Timebase 2s-40ns/cm incl. x5 Magn. • Trig. DC-40MHz (5mm)
Dual trace • Algebr. addition • X-Y Operation • Screen 8x10cm
Sweep delay • Overscan, Trigger, Delay indications • Trigger filter
Z-Modulation • Calibrator • Graticule illumination • 2kV

HM 512 **£580**
Y: Bandwidth DC-50MHz (-3dB) • Sensitivity 5mV-50V/cm (±3%)
X: Timebase 5s-20ns/cm incl. x5 Magn. • Trig. DC-70MHz (5mm)
Dual trace • Algebr. addition • X-Y Operation • Screen 8x10cm
Delay line • Sweep delay • After delay triggering • Trigger filter
Single shot + Reset • Overscan, Trigger, Ready, Delay indications
var. Hold-off • Z-Modulation • Graticule illumination • 12kV

HM 812 **£1,458**
Y: Bandwidth DC-50MHz (-3dB) • Sensitivity 5mV-50V/div. (±3%)
X: Timebase 5s-20ns/div. incl. x5 Magn. • Trig. DC-70MHz (0.5div.)
Dual trace analog storage with var. Persistence and Auto-Storage
Algebr. addition • X-Y Operation • Screen 8x10div. (7.2x9cm)
Delay line • Sweep delay • After delay triggering • Trigger filter
Single shot • Overscan, Trigger, Ready, Delay, AS indications
var. Hold-off • Z-Modulation • X-Guard circuit • Calibrator • 8.5kV



HM 812 Storage

For more information contact:

Prices U.K. List Ex. VAT

HAMEG LTD. 74-78 Collingdon Street LUTON
Bedfordshire LU1 1RX Telephone (0582) 413174 Telex 825484

Happy Memories

4116 200ns	**£2.25**	**2114** 200ns	**£2.95**
2114 450ns	**£2.20**	**2716** 5 volt	**£5.25**
2708 450ns	**£3.95**		

MEMOREX SOFT-SECTORED MINI-DISCS for PET, TRS-80, etc. Supplied in **Free Library Case** . . . . . **£19.95 per 10**

Low Profile I.C. Sockets by Texas
Pins 8 14 16 18 20 22 24 28 40
Pence 10 11 12 16 17 20 21 28 37

Memory Upgrade Kits for Apple, 2020, TRS-80, etc. . . . . **from £18** please phone


Quantity prices available on request. Government and Educational Orders welcome. Trade accounts opened.

ALL PRICES INCLUDE V.A.T. POSTAGE FREE ON ORDERS OVER £15, OTHERWISE ADD 30p

Access and Barclaycard Welcome


HAPPY MEMORIES
Dept. ETI
Gladestry, Kington
Herefordshire HR5 3NY
Telephone (054422) 618

OHIO SCIENTIFIC NEW SUPERBOARD 3

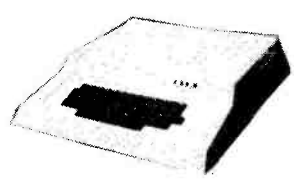

The special offer of the century (only Swanley could do it!): — for just **£159** we will supply Superboard 3 with a free power supply and modulator kit and our free guard band kit (a brilliant breakthrough in itself for this kit extends the display to 32 x 32, gives 1200 and 300 Baud tape speeds, increases the computing speed by 50% and converts the display to 50Hz for flicker free viewing). Guard band kit is also supplied separately for **£10.** 4K extra ram **£16.95.** Case **£27.** Cassette recorder **£17.** Cegmon improved monitor rom **£29.50.** Assembler/editor tape **£25.** Word processor program **£10.** Display expansion kit 30 lines x 54 characters. for Superboard 2 (Not 3) **£20.** Cheapo memory expansion offer:— Buy a 610 expansion board with 8K ram on board and space for another 16K for **£159** and get a free 5V 4A power kit and any extra ram you want for **£3**/K. Buy a minifloppy disc drive + case + power supply + OOS to **£275** and we will do the extra ram for **£2**/K (max. 16K).
New Series 2 Challenger C1P: — cheapo 4K version **£202.** Ohio 8K version (illustrated) **£259.**

PRINTERS

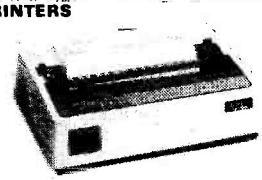

Buy any of the below and get a free interface kit and word processor programme for UK101 or Superboard 2:— OKI Microline 80 (illustrated) **£329.** Base 2 800MST **£299.** Seikosha GP80 **£225.**

MEMORY CHIPS
2114 450ns **£2.15.** 4116 200ns **£2.83.** 4027 **£1.30.** All low current.

★ SINCLAIR PRODUCTS
Sinclair products only are all post free. SC110 Oscilloscope **£139.** Adapter **£4.** Rechargeable batteries **£7.95.** X1 probe **£8.05.** X10 probe **£8.80.** Carry case **£8.80.** PFM200 **£54.50.** Adapter **£4.** Case **£1.73.** connector kit **£11.27.** PDM 35 **£32.95.** adapter **£4.** case **£1.73.** DM235 **£56.50.** DM350 **£78.50.** DM450 **£107.95.** adapter **£4.** case **£8.80.** rechargeable batts **£7.95.** Microvision TV **£69.** adaptor **£6.88.**

★ BATTERY ELIMINATORS
3-way type 6/7½/9V 300ma **£3.50.** 100ma radio types with press studs 9v **£4.95.** 9+9V **£6.26.** Car convertor 12v input, output 3/4½/6/7½/9v 800ma **£3.04.**

★ BATTERY ELIMINATOR KITS
100ma radio types with press-studs 9v **£1.79.** 9+9v **£2.50.** Stabilized 8-way types 3/4½/6/7½/9/12/15/18v 100ma **£3.12.** 1 Amp **£8.30.** Stabilized power kits 2-18v 100ma **£3.12.** 1-30v 1A **£8.60.** 1-30v 2A **£15.30.** TTL and computer supplies 5V stabilized 1½A **£9.** 3A **£12.** 6A **£20.** 12v car convertors 6/7½/9v 1A **£1.62.**

★ TV GAMES
Stunt cycle chip + kit **£20.95.** AY-3-8600 + kit **£12.98,** AY-3-8550 + kit **£9.26.**

★ PRINTED CIRCUIT MATERIALS
PC etching kit: economy **£3.42,** standard **£5.76.** 40 sq ins pcb **50p.** 1 lb FeC1 **£2.20.** Etch resist pens: economy **50p,** dalo **90p.** Drill bits 1/32" or 1mm **35p.** Etching dish **92p.** Laminate cutter **£1.30.**

★ BI-PAK AUDIO MODULES
AL30A **£4.53.** PA12 **£9.31.** PS12 **£1.75.** T538 **£2.90.** S450 **£27.90.** AL60 **£6.62.** PA100 **£19.24.** SPM80 **£5.26.** BMT80 **£8.36.** Stereo 30 **£24.14.** AL80 **£8.56.**

★ COMPONENTS
1N4148 **1.5p.** 1N4002 **3.7p.** NE555 8 dil **26p.** 7418 dil **20p.** bc182, bc184, bc212, bc214, bc547, bc549 **8.1p.** Resistors 5% ¼W E12 10R to 10M **1.5p.** 0.8p for 50+ of one value. Polyester capacitors 160v .015, .068mf **2.9p,** .047, .1mf **4.4p,** .01mf **3.3p,** .022, .033mf **3.7p,** .15, .22, .33mf **5.4p,** .47mf **6.6p.** Polystyrene capacitors E12 63V 10 to 1000pf **4p,** 1n2 to 10n **5p.** Ceramic capacitors 50v E6 22pf to 47n **2.5p.** Electrolytic capacitors 50v .5, 1, 2mf **8p,** 25V 5, 10mf **6p,** 16v 22, 33mf **6p,** 47mf **5p,** 100mf **7p,** 330, 470mf **9p,** 100mf **11p.** Zeners 400mw E24 2v7 to 33v **7p.** Preset pots subminiature 0.1W horiz or vert 100 to 2M2 **8p.** ic sockets 8 dil **8.7p,** 14 dil **10.1p,** 16 dil **12p.**

SWANLEY ELECTRONICS
Dept. ETI, 32 Goldsel Rd, Swanley, Kent, BR8 8EZ
Telephone Swanley 64851. Please add 45p postage, except on Sinclair products. Add VAT except on sections marked with a ★ which already include it. Lists 27p post free. No VAT on overseas orders which are welcomed. Official orders welcome.

CHROMATHEQUE 5000 5 CHANNEL LIGHTING EFFECTS SYSTEM



Panel size 19.0" x 3.5".
Depth 7.3"

COMPLETE KIT ONLY £49.50 + VAT!

This versatile system featured as a constructional article in ELECTRONICS TODAY INTERNATIONAL has 5 frequency channels with individual level controls on each channel. Control of the lights is comprehensive to say the least. You can run the unit as a straightforward sound-to-light or have it strobe all the lights at a speed dependent upon music level or front panel control or use the internal digital circuitry which produces some superb random and sequencing effects. Each channel handles up to 500W and as the kit is a single board design wiring is minimal and construction very straightforward.

Kit includes fully finished metalwork, fibreglass PCB controls, wire, etc. — Complete right down to the last nut and bolt!

MPA 200 100 WATT (rms into 8Ω) MIXER/AMPLIFIER

COMPLETE KIT ONLY £49.90 + VAT!

MATCHES THE CHROMATHEQUE 5000 PERFECTLY!

Panel size 19" x 3.5". Depth 7.3"



Featured as a constructional article in ETI, the MPA 200 is an exceptionally low priced — but professionally finished — general purpose high power amplifier. It features an adaptable input mixer which accepts a wide range of sources such as a microphone, guitar, etc. There are wide range tone controls and a master volume control. Mechanically the MPA 200 is simplicity itself with minimal wiring needed making construction very straightforward.
The kit includes fully finished metalwork, fibreglass PCBs, controls, wire, etc. — complete down to the last nut and bolt.

SP2-200 2-CHANNEL 100W AMPLIFIER



Panel size 19.0" x 3.5". Depth 7.3"

NEW!

COMPLETE KIT ONLY £64.90 + VAT!

The power amplifier section of the MPA 200 has proved not only very economical but very rugged and reliable too. This new design uses two of these amplifier sections powered by separate power supplies fed from a common toroidal transformer. Input sensitivity is 775mV.
Power output is 100 rms into 8 ohms from both channels simultaneously. The kit includes fully finished metalwork, fibreglass PCBs, controls, wire, etc. — complete down to the last nut and bolt!

POWERTRAN

SYNTHESIZER KITS ON PAGE 8. MORE KITS AND ORDERING INFORMATION ON INSIDE FRONT COVER.



DE LUXE EASY TO BUILD LINSLEY HOOD 75W STEREO AMPLIFIER £85.00 + VAT

This easy to build version of our world-wide acclaimed 75W amplifier kit based upon circuit boards interconnected with gold plated contacts resulting in minimal wiring and construction delightfully straightforward. The design was published in Hi-Fi News and Record Review and features include rumble filter, variable scratch filter, versatile tone controls and tape monitoring while distortion is less than 0.01%.

All kits also available as separate packs (e.g. PCB, component sets, hardware sets, etc.). Prices in our FREE CATALOGUE.



T20 + 20 20W STEREO AMPLIFIER £33.10 + VAT

This kit, based upon a design published in Practical Wireless, uses a single printed circuit board and offers at very low cost, ease of construction and all the normal facilities found on quality amplifiers. A 30 watt version of this kit (T30 + 30) is also available for £38.40 + VAT. MATCHING TUNERS — See our FREE CATALOGUE!

Above 2 kits are supplied with fully finished metalwork, ready assembled high quality teak veneer cabinet, cable, nuts, bolts, etc. and full instructions — in fact everything!


BLACK HOLE CHORALIZER

The BLACK HOLE designed by Tim Orr, is a powerful new musical effects device for processing both natural and electronic instruments, offering genuine VIBRATO (pitch modulation) and a CHORUS mode which gives a "spacey" feel to the sound achieved by delaying the input signal and mixing it back with the original. Notches (HOLES), introduced in the frequency response, move up and down as the time delay is modulated by the chorus sweep generator. An optional double chorus mode allows exciting antiphase effects to be added. The device is floor standing with foot switch controls, LED effect selection indicators, has variable sensitivity, has high signal/noise ratio obtained by an audio compander and is mains powered — no batteries to change! Like all our kits everything is provided including a highly superior, rugged steel, beautifully finished enclosure.

COMPLETE KIT ONLY £49.80 +VAT (single delay line system)

De Luxe version (dual delay line system) also available for **£59.80** +VAT

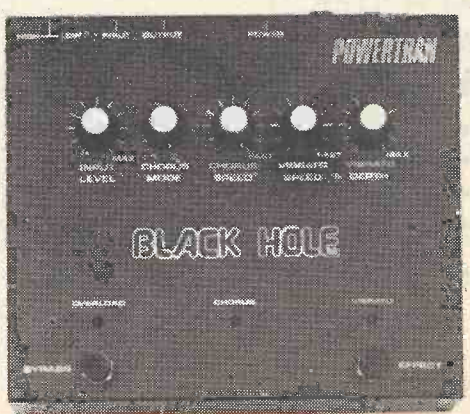
Cabinet size 10.0" x 8.5" x 2.5" (rear) 1.8" (front)



HIGH POWER MODULE KITS

125 WATT MODEL £10.50 plus £1.15 p&p (Illustrated)

200 WATT MODEL £14.95 plus £1.15 p&p

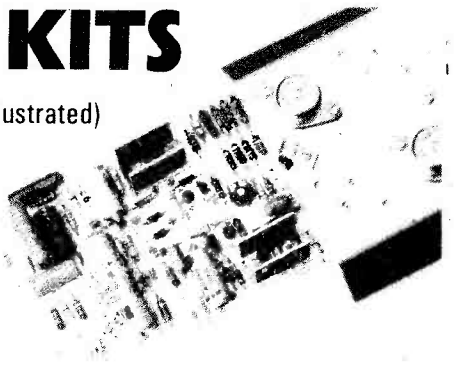

SPECIFICATIONS

Max. Output power	125 watt RMS
Operating voltage (DC)	50-80 Max.
Loads	4-16 ohms
Frequency response measured at 100 watts	25Hz-20KHz
Sensitivity for 100 watts	400mV @ 47K
Typical T.H.D. @ 50 watts 4 ohms load	0.1%
Dimensions	205 x 90 and 190 x 36 mm

The P.E. power amp kit is a module for high power applications—disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC Board is backprinted, etched and ready to drill for ease of construction, and the aluminium chasis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

ACCESSORIES


Suitable LS coupling electrolytic for 125W model **£1.00** plus 25p p&p.

Suitable LS coupling electrolytic for 200W model **£1.25** plus 25p p&p.


Suitable Mains Power Supply Unit for 125W model **£7.50** plus £3.15 p&p

Suitable Twin Transformer Power Supply for 200W model **£13.95** plus £4.00 p&p

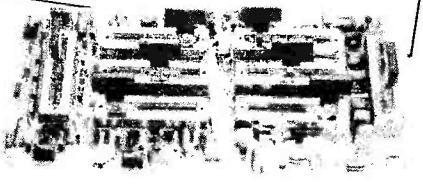MULLARD LP1183 STEREO PREAMP FREE! Original listed price over £5.00. Suitable for ceramic and auxiliary inputs, when you purchase 2 power module kits.



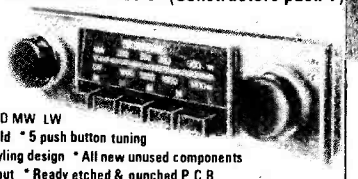PRACTICAL ELECTRONICS CAR RADIO KIT (Constructors pack 7)



2 WAVE BAND MW LW
*** Easy to build * 5 push button tuning**
*** Modern styling design * All new unused components**
*** 6 watt output * Ready etched & punched P.C.B.**
*** Incorporates suppression circuits * Now with tape input socket**

All the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March issue. Features: Pre-set tuning with five push button options, black illuminated tuning scale, with matching rotary control knobs, one, combining on/off volume and tone control, the other for manual tuning, each set on wood simulated fascia.
The P.E. Traveller has a 6 watts output, neg ground and incorporates an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit. The radio fits easily in or under dashboards.
Complete with instructions. **£10.50** plus £2.00 p&p

CONSTRUCTORS PACK 7A Suitable stainless steel fully retractable locking aerial and speaker (approx. 6" x 4") is available as a kit complete **£1.95** per pack, p&p £1.15



30 + 30 WATT STEREO AMPLIFIER BUILT AND TESTED


Viscount IV unit in teak simulate cabinet silver finished rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape and auxiliary. Rear panel features fuse holder. DIN speaker and input socket 30 + 30 watts. RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers. Size 14¾" x 10" approx.

READY TO PLAY £32.90 plus £3.80 p&p

HI FI STEREO AMPLIFIER MODULES



- Mullard LP1183 built preamplifier suitable for ceramic and auxiliary inputs. **£1.95** plus 70p p&p.
- Mullard LP1184 built preamplifier suitable for magnetic/ceramic and auxiliary inputs. **£4.95** plus 80p p&p
- Matching I.C. 10 + 10 Stereo Power amplifier kit. **£3.95** plus £1.15 p&p
- Matching power supply kit with transformer. **£3.00** plus £1.96 p&p
- Matching set of 4 slider controls complete with knobs for bass, treble and volumes. **£1.70** plus 80p p&p.
- Complete with application notes.

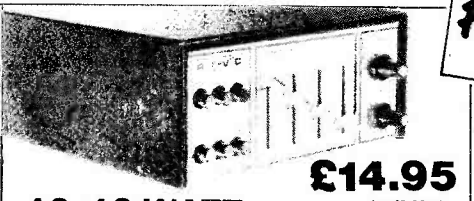

£14.95 plus £2.90 p&p

10+10 WATT STEREO AMPLIFIER KIT

- Featuring latest SGS/ATES TDA 2006 10 watt output I.C.'s with in-built thermal and short circuit protection.
- Mullard Stereo Preamplifier module.
- Attractive black vinyl finish cabinet. Size 9" x 8⅜" x 3⅜" approx.
- Converts to a 20 watt Disco amplifier.

To complete you just supply connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 20 watt mono disc amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus power amplifier assembly kit and mains power supply. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs and contrasting ready made black vinyl finish cabinet and ready made metal work. For further information instructions are available price 50p. Free with kit.

SPECIFICATIONS

Suitable for 4 to 8 ohms speakers	
Frequency response	40Hz — 20KHz
Input Sensitivity	P.U. 150mV Aux. 200mV Mic. 1.5mV
Tone controls	Bass ± 12db @ 60Hz
	Treble ± 12db @ 10KHz
Distortion	·1% typically @ 4 watts
Mains supply	220-250 volts 50Hz

BSR chassis record deck with manual set down and return, complete with stereo ceramic cartridge. **£8.50** plus £3.15 p&p when purchased with amplifier.
Available separately **£10.50** plus £3.16 p&p.


8" SPEAKER KIT 2 8" approx. twin cone domestic use speakers. **£4.75** per stereo pair plus £1.70 p&p when purchased with amplifier. Available separately **£6.75** plus £1.70 p&p.

STEREO MAGNETIC PRE-AMP CONVERSION KIT. All components including P.C.B. to convert your ceramic input on the 10+10 amp. to magnetic. **£2.00** when purchased with kit featured above. **£4.00** separately inc. p&p.

STEREO DISCO PREAMPLIFIER

matching above modules, suitable for twin deck mixing with P.F.L. output and Mic/Tape input.
Ready built, ready to play with circuit diagram and application notes to suit our power module kits. **£21.95** plus £1.72 p&p

100 WATT MONO DISCO AMPLIFIER

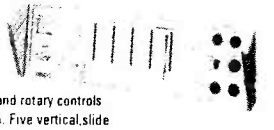

Brushed aluminium fascia and rotary controls
Size approx 14" x 4" x 10¼. Five vertical slide controls, master volume, tape level, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level controls (PRL) lets YOU hear next disc before fading it in. VU meter monitors output level.
Output 100 watts RMS 200 watts peak. **£76.00** plus £4.60 p&p


50 WATT MONO DISCO AMPLIFIER

Size appox 13⅜" x 5¼" x 6¾". 50 watts rms, 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume



£30.60 plus £3.68 p&p

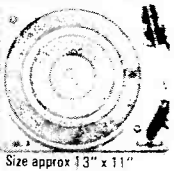BSR Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 rpm spindle adaptor ideally suited for home or disco use.



£12.25 OUR PRICE plus £3.16 p&p Size approx 13" x 11"

PHILLIPS RECORD PLAYER DECK GC037

Size approx 15¼" x 12¼"



Hi Fi record player deck, 2 speed damped cueing, auto shut-off, belt drive with floating sub chassis to minimise acoustic feedback. Complete with GP401 stereo magnetic cartridge—*LIMITED STOCK.*
UNBEATABLE OFFER AT
£27.50 complete plus £3.16 p&p

R T V C

323 EDGWARE ROAD, LONDON W2
21E HIGH STREET, ACTON W3 6NG
ACTON: Mail Order only. No callers

ALL PRICES INCLUDE VAT AT 15%
All items subject to availability. Price correct at 5.2.81 and subject to change without notice.
For further information send for instructions 20p plus stamped addressed envelope.
NOTE: Goods despatched to mainland and N. Ireland only.
Persons under 16 years not served without parent's authorisation.
R TVC LTD. reserve the right to alter, update or improve their products without notice.

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Closed all day Thursday. ACTON: Mail Order only. No callers. GOODS DESPATCHED TO MAINLAND AND N IRELAND ONLY

NEXT MONTH. NEXT MONTH. NEXT MONTH. NEXT MON

Hobby Electronics

Look for the April issue.
You can't afford to miss it!

Anatomy Of The Space-Shuttle

A special HE report on the forthcoming NASA Space-Shuttle launch. We investigate what the technical problems have been, why it's overdue, and give you a timetable running up to the launch and beyond

Tremolo

Just the effect you want for your guitar to complement the Fuzzbox in the March issue,although it will work with any electronic musical instrument. Simple-to-build, even simpler-to-use yet it won't burn a hole in your pocket

Russian Roulette

A novelty game designed to eliminate the players — without any mess whatsoever

---- STOP PRESS ---- STOP PRESS---- STOP PRESS ---- STOP PRESS ----
- COMPETITION - STOP - NEXT MONTH'S ISSUE OF HOBBY ELECTRONICS
- STOP - PROMOTING THE UNITED NATION'S INTERNATIONAL YEAR OF
THE HANDICAPPED PERSON - STOP - QUERY - DO YOU THINK YOU CAN
DESIGN AN ELECTRONIC AID TO HELP A HANDICAPPED PERSON - STOP -
ANY ELECTRONIC AID - SOLID-STATE, COMPUTER PROGRAM, EVEN VALVE
- ANY ELECTRONIC AID - STOP - ANY HANDICAP - STOP - PRIZES TO
WIN - STOP
---- STOP PRESS ---- STOP PRESS---- STOP PRESS ---- STOP PRESS ----

High Fidelity Comes To HE

Announcing a special audio project for HE: a hi-fi, high-power amplifier system which you can tailor according to your budget by making use of our special-offer kits. We start with the pre-amplifier in the April issue. This pre-amp requires *no wiring* except for the leads to the power supply! You can use it with your own amplifier too

Windscreen Washer Alarm

For the motorist who's fed up with cleaning his windscreen by hand because his washer bottle has run dry. As soon as the fluid drops below a predetermined level a 're-fill me' alarm is displayed

Plus:

News, views and info on CB, circuits, recent developments in electronics — everything for the electronics enthusiast and hobbyist — things you can't afford to miss. Get It!

Items mentioned here are those planned, but unforeseen circumstances may affect the actual contents



Vegas

The Winter Consumer Electronic Show keeps breaking its own records, and this year's event will be no exception. The Show organisers said that more than 850 exhibitors are showing off their new products at the Las Vegas Convention Centre, up from 757 at last year's Winter Show.

By the end of the year, it seems improbable that anyone will not have heard of the Video Disc. The long wait for the disc to become a functioning reality is over, and by next Winter's CES, close to 25 manufacturers will have a system on the market. The most carefully orchestrated and the most expensive promotion, advertising, and distribution programmes ever seen for an electronic product will forcefeed the video disc message to the American consumers in 1981.

Much of the attention is still focused on the competition between the Philips-made optical laser disc format and the RCA-patented CED Disc system. Matshushita's VHD system, which will be a later entry into the field, can be expected to buck the other two, benefitting from the publicity about discs created by the optical — CED dogfight.

Another Atari first is their new remote control console which combines sleek, futuristic styling and advanced technology and simply makes the game more enjoyable. Two quick-action remote controllers allow the players to move around the room freely without clumsy controller wires interfering with game action. Now the players can select, play and reset games on this new system without ever having to get up. Fingertip touch controls and LED signals are built into the hand-held remote controllers for game select and game reset options and the combination joystick and pedal controllers respond quickly and easily to the players' touch. Activision also showed some new cartridges they have lined up which are compatible with the Atari system. One is Centrecourt Tennis, which offers everything from lightning-quick serves to breathtaking back-hand cross-court returns. Charging players can rush the net or lay back and play the baseline. Laserblast casts you as the commander of a fleet of spacecraft; you come upon some very unfriendly alien types — just get them before they get you but remember the bad guys don't miss very often.


Finally, Studer/Revox enter the cassette equipment market with their model No. B710, utilising the same professionalism inherent in the company's other audio products. It is aimed to achieve the same high level of acceptance and respect by consumers that has been accorded to previous Studer/Revox audio equipment. Two peak reading LED bar displays are used for level indication and feature a resolution of 1 dB from −10 to +6 dB, with 2 dB intervals between −20 and −10 dB. A 0 dB indication represents "Dolby level". Stylistically, the B710 matches the other components in the Revox line.

Gerald Chevin



Versatile Video

Supplies of the new Ferguson Videostar VHS Portable video cassette recorder, model 3V24, are soon to become available. The 3V24 is expected to be the most lightweight recorder on the market, weighing in at 5.2 kg. The 3V24 has a microprocessor-assisted, fully electronic logic control cassette deck which can be operated either directly or by the full remote control unit supplied. The recorder incorporates a new Edit Start Control system for minimising picture break-up between recordings, as well as a picture scan facility which operates at 10 times normal speed, both forward and reverse. Other facilities include still frame, single frame advance and variable slow motion. A new quick-change power pack is supplied giving full recharge in 1½ hours, and there is a choice of two AC power supply/battery charger units available for use with the 3V24. The anticipated price of the Ferguson Videostar 3V24 is around £550.

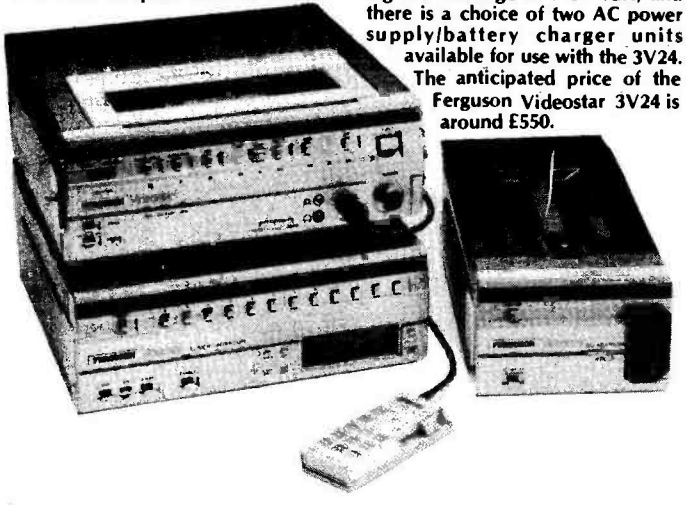

Telly Type

Delpa Systems have just announced their new Video telex which is capable of overcoming many of the inherent problems of ordinary telex machines. The Video telex uses a VDU and so the typing of messages takes half the normal time. The machine offers full correction and editing facilities, including the correction of spelling mistakes and the deletion of lines or paragraphs. It also provides full tabulation which means more attractive layouts, particularly useful in reports and orders. On existing machines where punch tapes are used, error correcting is extremely awkward and any incoming calls will interrupt the process, but the Video telex does not punch the message until it is 100% correct. The machine can either be used in the telex room or by other staff throughout the office building. Each station costs around £900 and further details can be obtained from Delpa Systems (UK) Ltd, Data Transfer Division, 56 Chiswick High Road, London W4 1SZ.

IMPORTANT NOTICE

Readers have recently confused Electronics Today Limited as being associated with the ownership of our magazine, Electronics Today International. Our magazine is owned by Modmags Limited, part of the Argus Press Holdings Limited Group of Companies.

Electronics Today Limited has advertised in our magazine, as "Metac", but so as to prevent any further confusion we wish to make it clear that Electronics Today Limited is not owned or managed by any member of the Argus Press Holdings Limited Group of Companies.

CLASSIFIEDS

RATES
1-3 insertions £7 per scc
4-11 insertions £6.50 per scc
12 insertions £6 per scc
24p per word (min. 15 words)
Box No. of application

All advertisements in this section must be pre-paid
Closing Date:- 1st Fri. month preceding publication

Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request).

SEND TO:- ETI CLASSIFIED, 145, CHARING CROSS ROAD, LONDON WC2H 0EE. TEL: 01-437 1002



CIRCUIT DESIGN, Prototype construction, Analogue or Digital, Single Circuits or Complete Instruments/Systems. Write A. J. ATTWOOD, C.Eng., MIERE, Heathercote, Heatherton Park, Taunton, Somerset, TA4 1ET or Phone Bradford-on-Tone (082-346) 536.

PARAPHYSICS JOURNAL. Russian/Czech translations. Autogenics (self-training) improves vitality. Psychotronic Generators, UFOs, contacting extraterrestrials, Kirlianography, telelinesis, levitation, gravity lasers. S.A.E. 4x9". Paralab, Downton, Wilts.

ZX80 £75. Mk14 £37. ATCM £99. Occasionally available secondhand. Tel: Redditch Electronics (0527) 61240 evenings.

PANELS

Give your project the professional finish it deserves. Blend in with existing equipment with these tough 2mm thick anodised aluminium fascia panels, matt black or brushed silver finish. Stock sizes: 44 × 16 cm **£4.75,** 35 × 15 cm **£4.25,** 30 × 12 cm **£3.90.** Other sizes available in quantity to order. Prices incl. c.w.o.

PROJECT FINISHERS
P.O. Box 2, Buntingford, Herts.

CITIZEN BAND RADIO and accessories. — Phone 0527 43169 or s.a.e. with enquiries to P.O. Box 13, Redditch B98 8NS.

TRS-80 or ZX80. 4 games on cassette. TRS-80, £3.50; ZX80, £3. S.A.E. Details/list. — Bobker, 29 Chadderton Drive, Unsworth, Bury, Lancs.

TELEPHONE ANSWERING MACHINES, Super Phones, Radio Phones, etc. Ring C.W.A.S. 0274 682674.

BURGLAR ALARM Component Catalogue out now. Ring: C.W.A.S. 0274 682674.

ZX80, ATOM, Mk 14 wanted. Tel: Redditch Electronics (0527) 61240 evenings.

SUPERBOARD II

STILL the best value in Home Computers. Just compare the features:

★ 8K floating point BASIC in ROM
★ Full ASC11 keyboard
★ Standard cassette/TV interface
★ RS232 printer interface
★ 4K user RAM
★ Expandable to 32K & dual mini floppy

AVAILABLE **NOW** from:
C.T.S.
31/33 Church Street
Littleborough
Lancs.

Please ring or write for latest prices
Tel: Littleborough (0706) 74342 any time

CENTURION ALARMS

BURGLAR ALARM EQUIPMENT AT UNBEATABLE VALUE
JUST LOOK!

Order No
100 ALARM TRIGGER MODULE. 100% Solid State. Battery operation. Pos. & Neg. Rings. N/C for 4-wire contacts. N/O for Mats, etc. One Amp Switching Capacity. Only **£9.95**
210 Quality White Flush fitting 4-wire **MAGNETIC REED CONTACT** + matching magnet **£1.10**
220 Surface 4-wire **MAGNETIC REED CONTACT** . . . **£1.50**
240 PRESSURE MAT, Standard size 4-wire 30"x15" . . **£2.20**
250 PRESSURE MAT. Stair size 4-wire 23"x6½" . . . **£1.73**
355 NEW PASSIVE MULTI-BEAM. Infra-red Detector, 8 metre range **£55.00**
360 SIX INCH UNDER DOME BELL £9.95
390 BEST QUALITY BELL HOUSING. PVC coated metal, not to be confused with the cheaper decoy covers . Fully signwritten with our Centurion Insignia **£9.50**
400 DECOY P.V.C. BELL COVER £6.60
NEW TWO-TONE U.S.A. POLICE SOUNDERS, complete with weatherproof horn **£14.50**
SOUNDER PCB Module, only **£4.95**
WEATHERPROOF Louspeaker, 8 ohm horn, only **£9.55**
Note: All equipment operates on 12 Volts DC.
Terms: Add 15% VAT to Prices + 60p Postage & Packing.



We welcome Access

No Minimum Order. Access telephone orders welcome on 0484-35527 or send S.A.E. for Full List to:
CENTURION ALARMS & ELECTRONIC SALES, Dept. ETI, 265 Wakefield Road, Huddersfield, W. Yorks HD5 9BE.

MEMORY BARGAINS. Low-price guaranteed devices. Eprom Programming Service. S.A.E. information and discounts. — T.D.S., 57 Westmead, Woking, Surrey, GU21 3BS.

TELEPHONE ANSWERING MACHINES from £75; flipcaller £25, watches from £5.75; car radio, cassettes, boosters, speakers, walkie-talkies. S.A.E. for details. — H.P. Supplies, Dept. ETI, 162 London Road, Wembley, Middx.

Acorn Atom SOFTWARE

ON HIGH QUALITY C12 CASSETTE

Note: figures refer to TOTAL memory required

Atom Invaders! ★★ GRAPHICS MODE 4 12K

A fantastic machine code program utilising the high-resolution graphics capability of the Atom and sound output. All the usual features. £12.00

ATOM BREAKOUT Another highly entertaining machine code program with sound output. Requires 4K memory. £5.00

sinclair ZX80 SOFTWARE

.ZX80 PROGRAMMING COURSE

This consists of a book and a cassette of programs, which together cover those aspects of ZX80 programming likely to cause difficulty. Many useful programing examples are included, dealing with PEEK & POKE, arrays, USR etc.

Also includes sections on flowcharts, and the Z80 microprocessor. ONLY £8.95

NEW DIGITAL CLOCK (1K) for **ZX80 only £4.50**

CONTINUOUSLY CHANGING GRAPHICS – NO FLICKER!!

MANY MORE PROGRAMS AVAILABLE FOR ZX80 AND ATOM – SEND S.A.E. FOR DETAILS

BUG-BYTE DEPT. ETI
251 HENLEY ROAD, COVENTRY

PC WHOLESALE

1 THORNHILL, ROMSEY ROAD
WHITEPARISH, SALISBURY SP5 2SD

All good new full spec — prices are for minimum 100 any one type. Minimum Order £10 + 50p post. No VAT. SAE for full list.

AC126	.14	IC's		1N4002	.032
AC176	.14	4001B	.10	1k	.024
AD161/2	.45	4011B	.10	10k	.029
BC107	.07	4013BF	.30	1N4003	.034
BC108	.08	4017A	.35	1N0	.025
BC108C	.08	4025A	.12	10k	.021
BC114	.05	4029A	.50	1N4006	.046
BC147/8/9	.05	4040A	.25	1k	.024
BC171/2	.05	4068B	.00	10k	.029
BC177	.07	4069B	.12		
BC182B	.045	4511B	.80	CAPACITORS cropped lead PCB mntg.	
BC182L	.04	4081B	.50	0.47/50	.022
BC212B	.045	2114B-L	1.50	1/50	.024
BC237/8/9	.05	2708 450ns	2.80	2.2/50	.024
BC308B	.05	741	.12	4.7/25	.022
BC328	.07	555	.17	10/16	.021
BC327/8	.07			10/40	.023
BC441	.10			22/25	.023
BC461	.20	LED's		47/16	.024
BC557/8/9	.06	3mm red	.055	47/40	.028
BD246	.30	yellow	.080	100/16	.022
BD433	.32	green	.080	100/25	.025
BF181	.15	5mm red	.080	100/40	.027
BF258	.20	yellow	.080	220/63	.037
BFY50	.15	green	.080	1000/16	.060
BFY51/2	.13	Clips	.02	2200/40	.320
PNP100	.05				
PN100	.05				
TIP2955	.46	Zeners, 400mW			
TIP3055	.45	2V4 3V6 4V7 5V6 6V2			
ZN1132	.16	6V8 7V5 8V2 9V1 11V			
ZN1711	.16	12V 14V 18V 24V. All at			
ZN2369	.12	.03.			
ZN2646	.34				
ZN2926G	.045				
ZN3053	.15	DIODES			
ZN3055	.30	1N4148	.02		
ZN3702/8	.045	1k	.012		
ZN3819	.14	10k	.008		
ZN5401	.17	Quad 1k	.013		
40673	.45	Quad 10k	.009		


£1 BARGAIN PACKS

All packs £1 each; any 12 for £10. Post 25p. All top-grade new components — no rubbish.

PC1 12 BC107	PC9 10 TO3 sockets
PC2 14 BC108	PC10 15 0.1/35V tants
PC3 12BBC109	PC11 14 3mm red LEDs
PC4 3 2N3055	PC12 12 5mm red LEDs
PC5 7 BFY51	PC13 8 741
PC6 16 BC182	PC14 6 555
PC7 60 1N4148	PC15 15 12V zeners
PC8 25 1N4003	PC16 100 1k ¼W 5% Rs

Send S.A.E. for 8-page list/enquiries. Mail only.
PC ELECTRONICS, 1 Thornhill, Romsey Road Whiteparish, Salisbury, SP5 2SD

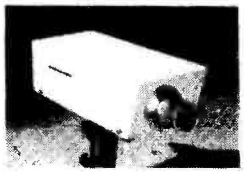AMAZING ELECTRONICS PLANS. Lazers; Super-powered cutting rifle, pistol, light show, ultra-sonic force fields, pocket defence weaponry, giant tesla, satellite T.V. Pyrotechnics, 150 more projects. Catalogue 75p. From: Plancentre, St. John's Street, Bridgenorth, Shropshire.



CCTV CAMERA

£126.50 + P&P £3.45 (inc. VAT) Total £129.95

BEST OFFER EVER
Camera Kit, Lens, Vidicon & Modulator

CROFTON

Tel: 01-891 1923 For full details

SHARP MZ-80K

and PC1211 Computers at LOWEST PRICES!!
With lots of FREE PROGRAMS

KING PIN COMPUTERS
PO Box 40, Stevenage, Herts.
SG2 7NF
Tel. Stev. (0438) 59677, up to 9 p.m.

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive lacquer – now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric Chloride 55p. Clear acetate sheet for master 14p. Copper-clad fibreglass board, approx. 1mm thick £1.75 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

BURGLAR ALARM EQUIPMENT. Wide selection at competitive prices. Sae for price list. A. Barton (ETI), 27 Gunville Road, Newport, I.o.W.

GOULD OS253 OSCILLOSCOPE. 18 months old £300. Phone Sheffield (0742) 339073 after 6.30 weekdays.

GOLD UNDER YOUR FEET? Special purchase C-Scope VLF/TR750 Metal Detectors. Normal price £84.90, 2 year guarantee. £59.90 including carriage. (0634) 250625.

AN UNBEATABLE KLIFCO OFFER. Quality Stereoamplifier chassis + Free Stereo Magnetic Pick-up. P.C.B. + Data £10.50. 60+60 watt (RMS) protected; 3Ω min 0.03% THD; 12-50V working, din sockets + controls; selector, V/C etc. Tested. 1 Regent Road, Ilkley LS29 9EA.

PRINTED CIRCUITS
and
HARDWARE

Comprehensive range Constructors' Hardware and accessories.

Selected range of popular components
Full range of HE printed circuit boards normally ex-stock, same day despatch at competitive prices
P.C. Boards to individual designs
Resist-coated epoxy glass laminate for the d.i.y. man with full processing instructions (no unusual chemicals required)

Alfac range of etch resist transfers, and other drawing materials for p.c. boards

Send 15p for catalogue.

RAMAR CONSTRUCTOR SERVICES
MASONS ROAD
STRATFORD-ON-AVON
WARWICKS. Tel. 4879

COLOUR MODULATOR

- R.G.B. inputs, PAL/UHF output
- Unlimited colour combinations
- TTL etc. interface details supplied
- 1000's already in use!



KIT: only **£12** Built & Tested: only **£18**

— please add VAT at 15% to all prices
— Barclay/Access orders accepted by telephone

WILLIAM STUART SYSTEMS Ltd
Dower House, Billericay Road, Herongate, Brentwood, Essex CM13 3SD
Telephone: Brentwood (0277) 810244

C.B.S.

If you are in Business and considering an application of a Minicomputer or Microprocessor based System and are a little confused why not attend one of our courses.

A. Microcomputer Application — BUSINESS
B. Microcomputer Application — ENGINEERING AND CONTROL
C. Programming in BASIC — INTRODUCTION
D. Programming in BASIC — ADVANCED

We are an independent consultative organisation specialising in business and engineering application, prepared to recommend systems when required and provide full software and programming support.

Courses are available for individual or group instruction, and may be arranged to suit your specific applications.

For full details and dates available write or phone:


CLEVELAND BUSINESS SERVICES
Cleveland House
Routh, Near Beverley
North Humberside HU17 9SR
Tel: Leven 0401-43139

SHARP POCKET COMPUTERS

PC 1211 Pocket Computer with CE121 Cassette Interface **£105.95**
Printer Cassette Interface CE122 ..... **£59.95**
The CE122 combines the functions of printer and cassette interface.
PC 1211, complete with CE122 Printer/Cassette Interface **£152.00**
Free Papermate Pen with all orders. All prices include 15% VAT and U.K. delivery
ELKAN ELECTRONICS, 28 Bury New Road Prestwich, Manchester, M25 8LD

ZX80 'LIVE ACTION' SOFTWARE. Top quality games at unbeatable prices: BREAKOUT (1K) £4; SPACE INTRUDERS (2K) £4. Also MOVIES (2K plus), 7x8 character pictures displayed in rapid rotation giving animation effect £3 — No hardware modification whatsoever. Written in machine code without loss of T.V. synchronisation. SOUNDS INCREDIBLE? — YES, but it's true. Reviews say the ZX80 can't be used for continuous live action ARCADE type games — WELL IT CAN — WE'VE DONE IT — SEEING IS BELIEVING — Send cheques or P.O.'s for program listing (or S.A.E. for list of all software) to: MACRONICS (K. Macdonald), 26 Spiers Close, Knowle, Solihull, B93 9ES.

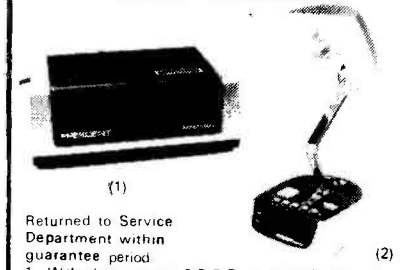BARGAINS FOR THE ELECTRONIC HANDYMAN BRANDED L.E.D. DIGITAL ALARM CLOCKS



(1) (2)

Returned to Service Department within guarantee period.

1. With alarm repeat. S.R.S.P. of £17.00. Offered at **£3.95**, inc. VAT, or 3 for **£9.95**, inc. VAT.
2. With luxury lamp and repeat alarm. S.P.S.P. £31.00. Offered at **£7.95** inc. VAT each, or 3 for **£19.95** inc. VAT.

These will be sold as received from our customers with the existing fault(s) and without guarantee.
U.K. only
Discounts available on large bulk purchase.

PRESCOTT CLOCK & WATCH CO. LTD.
PRESCOTT HOUSE, HUMBER ROAD, LONDON NW2 6ER

SPEED — VERSATILITY — ECONOMY

Road Runner

Designed originally for logic wiring applications, it is now accepted and used extensively throughout industry, education and research. ROADRUNNER is used by hobbyists, students, technicians, designers and engineers, to carry out work on:— *P.C.B. REPAIRS *ANALOGUE BREADBOARDING *SIMPLE LOGIC WIRING *COMPLEX INTERCONNECTING OF MICROS AND MEMORIES.

EURO INTROKIT **£16.70.** PORJECT KIT **£8.18.** MINIKIT (A) **£7.** PENCIL WITH LOADED 'QSE' BOBBIN **£2.81** WITH T.C.W. BOBBIN **£2.76.** STRIPS: GLUE FIX 20/PKT. 6" LONG **£3.20.** HIGH DENSITY GLUEFIX 20/PKT. 6" LONG **£3.20.** PRESS FIX 20/PKT. **£3.20.** SINGLE HIGH DENSITY D-SIDED EUROCARD **£5.18.** SINGLE SIDED **£3.80.** DOUBLE HIGH DENSITY D-SIDED EUROCARD **£8.60.** PROJECT CARD **£2.50.** BOBBINS. BLUE 4/PKT. **£2.12.** GREEN 4/PKT **£2.12.** GOLD 4/PKT. **£2.12.** PINK 4/PKT. **£2.12.** 1 OF EACH COLOUR **£2.20.** TINNED COPPER 2/PKT **£0.96.** ADHESIVE **£0.41.** SOLDERING IRON 420° C **£5.52.** REPLACEMENT WELLER TIPS — PTAA8 430 C **£1.40.** PTAA9 480 C **£1.40.**

Please add 40p for P&P + VAT to all orders

FOR FURTHER INFORMATION ON ROADRUNNER PRODUCTS SEND LARGE S.A.E. TO:

T. J. BRINE ASSOCIATES
FREEPOST, Haslemere, Surrey GU27 3BL

DIGITAL WATCH BATTERY REPLACEMENT KIT



These watches all require battery (power cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screwdriver, case knife and screwback case opener. Also one doz. assort. push-pieces, full instructions and battery identification chart. We then supply replacement batteries — you fit them. Begin now. Send **£9** for complete kit and get into a fast-growing business. Prompt despatch.

BOLSTER INSTRUMENT CO. (ET23)
11 Percy Avenue, Ashford, Middx. TW15 2PB

PRE-WAR ONWARD VALVES, wireless (S.W.s included). S.A.E. 100 transistors £5. Bargains list 15p. — Sole Electronics, ETI, 37 Stanley Street, Ormskirk, Lancs.

FM MINI TRANSMITTERS 88-108 MHz, 150 yard range. Money back (before/after assembly). Guaranteed. Kit £2.65 + 25p P&P. P. Faherty, 37 College Drive, Ruislip, Middx.

SN76477 sound generator plus data	**160p**
XR2206 tone decoder plus data	**270p**
MM57160 STAC timer	**500p**
ZN425E D to A converter	**380p**
NE555 timer	**18p**
2708 450nS EPROM	**300p**
TBA800 5W audio amplifier	**70p**
NE567 tone decoder	**100p**
LM13600 dual transconductance amp	**120p**
LM387 low noise preamp plus data	**130p**
LM386 power amplifier	**80p**
LM377 dual 2w. amplifier	**160p**
LF351 operational amplifier	**40p**
LF353 dual LF351	**80p**
TDA1022 delay line	**500p**
7805 or 7812 TO220 regulator	**50p**
7905 or 7912 TO220 regulator	**60p**
Metal film ¼w. 1% resistors 51Ω to 300K. E24 series	**4p**
Siemens polyester capacitors 0.01, 0.022, 0.047, 0.1	**9p**
Pack 50 each 6BA nuts, washers, ½" screws	**50p**
Pack 50 each 4BA nuts, washers, ½" screws	**70p**
Connecting cable single strand, 1 metre of eight different colours; total 8 metres	**30p**
As above but 5 metres each colour; total 40m.	**140p**
Light duty stranded 10/0.1mm, 8 colours	**4p** metre
Extra flex. 55/0.1, red or black	**12p** metre
Twin cable, speaker type	**10p** metre
Single screened cable	**15p** metre
Twin individually screened	**20p** metre
Min. 3-core mains cable, 2.5A	**22p** metre

All prices exclude V.A.T. Please add 40p carriage. All brand new components.

J. NELSON **203 HIGH STREET LONDON, S.E.13**

MICROTYPE



READY CUT CASE FOR SUPERBOARD, UK101, NASCOM 2
(ALSO AVAILABLE WITH BLANK KEYBOARD FOR HOMEBREW, NASCOM 1, ETC.)

PRODUCED IN BLACK ABS PLASTIC, COMPLETE WITH SCREWS AND INSTRUCTIONS. SPACE FOR EXPANSION, FORCE FEED FAN, NUMERIC PAD AND ADDITIONAL KEYS. ONLY £24.50 + £1.50 P&P + VAT.
SEND CHEQUES OR P.O.'S FOR £28.90 TO:
MICROTYPE, P.O. BOX 104, HEMEL HEMPSTEAD, HERTS. HP2 7QZ
SAE FOR DETAILS. DEALER & OEM ENQUIRIES WELCOME.

B.U.F.O.R.I.N. BUFORIN UFO Research Network urgently need Investigators in all parts of Britain. For more details, send 10p and s.a.e. to — The BUFORIN, Upper Grange Farm, Old Dalby, Melton Mowbray, Leicestershire.

SYNTHESISER 4600 for sale. Full constructional data, professionally built. Calibrated, tuned and tested. Excellent finish, beautiful condition, £750 ono. Tel: Letchworth 04626 76951 after 6pm.

POWER SUPPLIES, new, guaranteed. Many types cased and uncased. Write Petron Electronics, 1 Courtlands Road, Newton Abbot, Devon.

BUILD A 12 into 2 mixer for £100. Details £3.50. P.O. to Mr J. A. Lovatt, Flat 5, 36 William Ave., Margate, Kent.

POWERTRAN D.P.X. Polyphonic Synthesiser fully built and tested, perfect working order, £350 ono. Phone Leeds 450586/8. Ext. 38. (Flat F3).

CB SPARES

Japanese original transistors and integrated circuits.

Largest selection in Britain at very low prices.

Write or phone for free list.

McLaughlin Electronics
44 Carlisle Road
Londonderry
N. Ireland BT48 6JW

Tel: (0504) 65002

ADAM HALL

Cabinet & Flightcase Fittings, [illegible] handles, castors etc. Jacks & sockets. Gain cells. Bulgins reverb trays. Tendar compression drivers. ASG mics. Celestion speakers. ASS glassfibre horns.

Send 30p. postal order for illustrated catalogues to:
ADAM HALL (E T SUPPLIES)
Unit B, Charlton Court
Grainger Road, Southend-on-Sea
Essex SS2 5BZ

EXACT TIME?

MSF CLOCK is ALWAYS CORRECT — never gains or loses, self setting at switch-on, 8 digits show Date, Hours, Minutes and Seconds, auto GMT/BST and leap year, also parallel BCD output and audio to record and show time on playback, receives Rugby 60kHz atomic time signals, built-in antenna, 1000Km range, ABSOLUTE TIME, £54.80.
V.L.F.7 EXPLORE 10-150KHz, Receiver £13.70.
60KHZ RUGBY RECEIVER, as in MSF Clock, serial data output, built-in antenna, £15.70.

Each fun-to-build kit includes all parts, printed circuit, case, instructions, postage etc, money back assurance so GET your NOW.

CAMBRIDGE KITS
45 (TR) Old School Lane, Milton, Cambridge

MK 14 KITS. Keyboard £12.80. ½" display £12.80. 4K memory board, fitted 1K £20.82. Ditto fitted 4K £43.47. 16 bit LED board £11.41. Mother board £9.34. Cassette interface £8.21. 5v, 1.5A power supply, less transformer £7.55. Super VDU interface £39. New monitor £14.95. VDU monitor PROM (5v) £14.95. Plco-2 basic PROM (5v) £14.95. Mk 14 book £5.95. Secondhand Mk 14 £37. Catalogue 80p. Full price list — send SAE. Post 80p. Redditch Electronics, 21 Ferney Hill Ave., Redditch, Worcs. B97 4RU. Tel: (0527) 61240 evenings.

TELEPHONE ANSWERING MACHINE. Build your own for under £10 plus any cassette recorder. Send £3 for circuit and plans. S. D. Cross, 24 Thorney Road, Streetly, Sutton Coldfield, West Midlands.

DOUBLE SIDED COPPER CLAD Fibreglass Board. ½p/sq. inch. Please state size. Maximum size 12" x 12". Minimum order £1. P&P 60p. Also complete P.C.B. service. H.C.R. (Chelmsford), 1 Bankside, off New Street, Chelmsford.

FORMANT SYNTH, integral case, reverb, phaser, etc. Less one VCO, all working. £450. Tel: (0670) 513567.

100 IN4148 £1, 150 Resistors £1, 100 Capacitors £1. P&P 25p. S.A.E. lists. Dept. T, D.B. Products, P.O. Box 8, York YO1 1FT.

Mail Order Protection Scheme

If you order goods from mail order advertisers in this magazine and pay by post in advance of delivery, this publication *Electronics Today International* will consider you for compensation if the advertiser should become insolvent or bankrupt, provided

1. You have not received the goods or had your money returned; and
2. You write to the publisher of this publication *Electronics Today International* explaining the position not earlier than 28 days from the day you sent your order and not later than 2 months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the advertiser has been declared bankrupt or insolvent to a limit of £1800 per annum for any one advertiser so affected and up to £5400 p.a. in respect of all insolvent advertisers. Claims may be paid for higher amounts, or when the above procedures has not been complied with, at the discretion of this publication *Electronics Today International;* but we do not guarantee to do so in view of the need to set some limit to this commitment and to learn quickly of readers' difficulties.

This guarantee covers only advance payment sent in *direct* response to an advertisement in this magazine (not, for example, payments made in response to catalogues, etc., received as a result of answering such advertisements). Classified advertisements are excluded.

BUDGET MICRO BITS:

1K Extra Memory Kit for Mk. 14's..... £8.54
Decoding logic kit for Mk. 14 address to full 16 lines £2.81
4k Static Memory block kit..... £30.95
Address and Data buffers with memory control logic kit..... £18.70

TREMORRAN DATA SYSTEMS
Tors Park, Infracombe, N. Devon

WANTED. Electronic components and test equipment. Good prices given. Q Services, 29 Lawford Crescent, Yately (0252) 871048, Camberley, Surrey.

VIDEO MUSIC



The amazing **Videograph**, as featured recently in Electronics Today International, links your Hi-Fi with any Colour TV to produce a Fantasia of hypnotic visual effects. The system displays stereo music as brilliantly coloured waveforms against an ever changing background. For the technically-minded, a square-wave signal generator is built-in, permitting advanced demonstrations of transient response etc. Truly the ultimate accessory for any Hi-Fi system!

DIY KIT ONLY £33.95
Case & Controls £15.95
or READY BUILT £69.95

All prices include VAT and postage

WILLIAM STUART SYSTEMS Ltd
Dower House, Billericay Road, Herongate, Brentwood, Essex CM13 3SD.
Telephone: Brentwood (0277) 810244

PROGRAMMING, UV. Eproms, most types, 1 & 3 rail. £3/1K. Dept. E, Petron Electronics, 1 Courtlands Road, Newton Abbot, Devon.

WANTED

Test equipment, valves, tubes and scrap electronics.

Reasonable prices paid. Distance no object (UK mainland only).

FRG General Supplies
Unit 3, Longhill Industrial Estate
March, Cambridgeshire
PT15 8NQ

Tel: March (03542) 56614
or 01-404 5011
Telex: 24224 Quote Ref. 3165

DIGITAL VOLTMETER MODULE



Fully built and tested, ONLY **£11.95**+VAT

- ★ Reads positive and negative voltages with a sensitivity of 0 - +999mV and 0 - -99mV
- ★ Requires only single supply between 7 & 12 volts (220mA)
- ★ High accuracy +0.1% +1 digit
- ★ Large bright 0.43" high efficiency displays
- ★ 4 readings per second sampling rate
- ★ Size only 41 x 95 x 10mm.
- ★ Supplied with full data & applications information

This quality module manufactured by Autona Limited (one of the U.K's largest module manufacturers) means you can build accurate test equipment, multimeters, thermometers, etc., easily and at a fraction of the cost of ready-made equipment. Full details are provided showing how to measure A.C. voltage, current, resistance and temperature.

Send your cheque or P.O. (£11.95 + £1.79 V.A.T. + 50p p. & p. = £14.24) now to:

Dept. ET14, RISCOMP LIMITED
21 Duke Street, Princes Risborough
Bucks. HP17 0AT
Telephone (084-44) 6326

Retail shop callers welcome

Buy it with Access

EX-STOCK DELIVERY

Buy it with Access

ADVERT INDEX

Acorn Computers....53
Altek Instruments....74
Ambit International....43
Audio Electronics....14 & 90
Bi-Pak Semiconductors....54
BK Electronics....16 & 94
BNRS....18
Butterworths....101
Calculator Sales & Service....94
Cambridge Learning....57
Campbell Clark Cabinets....86
Castle Electronics....98
Chiltmead....81
Chordgate Ltd....63
Chromasonics....48 & 49
Clef Products....85
Comp Comp Comp....114 & 115
Crimson Elektrik....97
Crofton Electronics....103
Delta Tech & Co....93
Display Electronics....65 & 80
Doram Electronics....69
Drallim Davis Electronics....42
Electronize Design....85
Electro Supplies....42
Electrovalue....103
GMT Electronics....74
Greenbank....99
Greenweld....94
G.S.C....19 & 62
Hameg Ltd....106
Happy Memories....106
Henry's Radio....64, 86 & 93
I.C.S....7
I.L.P....32, 33 & 64
Keelmore....49
Kode Services....70
Langstone Electronics....34
LB Electronics....86
L & B Electronics....70
LEM Services....74
Linsac....93
Manor Supplies....86
Maplin....116
Marshalls....90
Micro Circuits....87
Microdigital....80
Midwich Computers....103
Mitrad....73
NIC Models....70
Parndon Electronics....52
T. Powell....52
Powertran....2, 8 & 107
Rapid Electronics....34
J. W. Rimmer....52
R.T.V.C....108
Safgan Electronics....80
Saxon Entertainments....98
Science of Cambridge....4 & 5
Silica Shop....42
Swanley Electronics....106
Tangerine....38 & 39
Technomatic....12
Teleradio....52
Tempus....20
Timedata....64
TK Electronics....58
Transam Components....26
Vero Electronics....34
Videotone Ltd....89
Watford Electronics....6 & 7
Wilmslow Audio....64
Yale Security....98

ELECTRIFY YOUR SALES! • CLASSIFIED ADVERTISEMENT

1	2	3
4	5	6
7	8	9
10	11	12
13	14	15

Please place my advert in: Electronics Today International
(Delete as applicable) Hobby Electronics

Advertise nationally in Electronics Today International/Hobby Electronics. Simply print your advertisement in the coupon here (left), indicating which magazine you require.
Or telephone for more information.

Name .....
Address .....
.....
.....
Tel. No. (Day) .....

Send, together with your cheque to:
Jenny Naraine, ETI/HE,
145 Charing Cross Rd., London WC2H 0EE.
Tel: 01-437 1002 Ext. 50.

NEW REDUCED PRICES

8K £399
16K £449
32K £499
} VAT

RRP £795 for 32K



The PEDIGREE PETS

Very popular for home & business use. 8K Microsoft Basic in ROM. 8K Pet 32K & 16K with new improved keyboard. All with green screen.

Cassette Deck **£55** extra. Full range of software available.

Interface PET IEEE — Centronics Parallel
Decoded **£77.00** + VAT

We give a full one year's warranty on all our products.

SPECIAL SCOOP — GET YOURSELF A PRINTER FOR YOUR PET AND SAVE A FORTUNE

only **£299** + VAT



Interface Cards for Apple, Pet, TRS80, Nascom and Compukit — **£49** + VAT

Full Pet Graphics including cables. Ready to go. **EX-STOCK.**

NASCOM 2 DISC DRIVES

Add a powerful, double density, mini floppy disc to your Nascom system.

- Disc Controller Card (includes Nasbus 6 S100 interface
- Will control 4 Drives.
- CPM operating system.
- Extended Disc Basic Compiler.
- Power supply included



One Disc System — **£499** + VAT
Additional Disc Unit — **£299** + VAT

NASCOM 2 GAMES TAPE

featuring Space Invaders and Android Nim, Re-numbering program and other goodies!


£7.50 + VAT

NEC SPINWRITER

only **£1350** + VAT



NEC's high quality printer uses a print "thimble" that has less diameter and inertia than a daisy wheel, giving a quieter, faster, more reliable printer that can cope with plotting and printing (128 ASCII characters) with up to five copies, friction or tractor fed. The ribbon and thimble can be changed in seconds. 55 characters per second bidirectional printing — with red/black, bold, subscript, superscript, proportional spacing, tabbing, and much, much more.

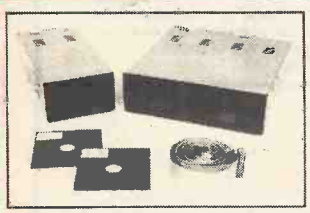

TEAC DISK DRIVES

- TEAC FD-50A has 40 tracks giving 125K Bytes unformatted single density capacity.
- The FD-50A can be used in double density recording mode.
- The FD-50A is Shugart SA400 interface compatible.
- Directly compatible with Tandy TRS80 expansion interface.
- Also interfaces with Video Genie, SWTP, Heathkit, North Star Horizon, Superbrain, Nascom, etc, etc.
- Address selection for Daisy chaining up to 4 Disks.
- Disks plus power supply housed in an attractive grey case.

Single Disk Drive **£225** + VAT
Double Disk Drive **£389** + VAT

COMP POCKET COMPUTER GREATEST BREAKTHROUGH YET



£99.90 + VAT

COMPUTER POWER THAT ONCE FILLED A ROOM CAN NOW BE CARRIED IN YOUR POCKET!

- **Programs in BASIC**
- **"QWERTY" Alphabetic Keyboard**
- **1.9K Random Access Memory**
- **Long Battery Life.**

Computer power that once filled a room can now be carried in your pocket! It's easy to load with ready-to-run software from cassette tape (interface and recorder optional) or program it yourself in easy-to-learn BASIC. 24-character liquid crystal readout displays one line at a time. Special feature is advanced non-volatile memory allows you to power on and off without losing the contents of memory. Note: Memory must be transferred to tape before changing batteries. Automatic statement compaction squeezes every ounce of memory space. Features power-off retention of programs and data. Powerful resident BASIC language includes multiple statements, math functions, editing, strings, arrays and much more. Multiple program loading capability subject to RAM availability. Carrying case and batteries included.

FANTASTIC FOR FILE HANDLING

ACULAB FLOPPY TAPE

The tape that behaves like a disc, for TRS-80 LEVEL 2.




only **£169** + VAT

The Aculab Floppy Tape for the TRS-80 and Video Genie is a highly reliable digital storage system that provides many of the advantages of floppy disks at less cost. Automatic debounce routine for the Level 2 keyboard.
Connects directly to TRS-80 Level 2 Keyboard. Operating and file handling software in ROM. 8 commands add 12 powerful functions to Level 2 BASIC.

THE VIDEO GENIE SYSTEM

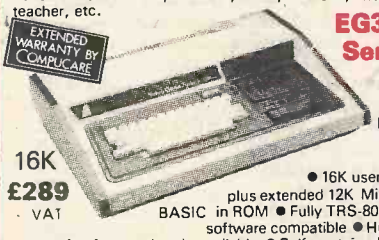Ideal for small businesses, schools, colleges, homes, etc. Suitable for the experienced, inexperienced, hobbyist, teacher, etc.



EG3000 Series

WITH NEW EXTRA KEYS!

16K **£289** + VAT

- 16K user RAM plus extended 12K Microsoft BASIC in ROM
- Fully TRS-80 Level II software compatible
- Huge range of software already available
- Self contained, PSU, UHF modulator, and cassette
- Simply plugs into video monitor or UHF TV
- Full expansion to disks and printer
- Absolutely complete — just fit into mains plug.

The Video Genie is a complete computer system, requiring only connection to a domestic 625 line TV set to be fully operational; or if required a video monitor can be connected to provide the best quality display. 51 key typewriter style keyboard, which features a 10 key rollover. Supplied with the following accessories:- ● BASIC demonstration tape; ● Video lead; ● Second cassetee lead; ● Users manual. ● BASIC manual; ● Beginners programming manual. Write useful programs in the BASIC computer language yourself.

VIDEO GENIE EXPANSION BOX NOW IN SHOP

only **£325** + VAT



TRS80 LEVEL 2 16K

Fully converted to UK T.V. Standard. Comes complete with easy to follow manuals. UK Power Supply – Cassette Leads – Sample tapes. Special box to enable you to plug into your own T.V. Recommended for first time-buyers. Just plug in and go. Full Range of Software Available.

Interface to Centronics Parallel for TRS80 **£75.00** + VAT

only **£295** + VAT

TRS80 EXPANSION INTERFACE

Expand your TRS80 by 32K
32K Memory on board
Centronics parallel port
Disk controller card. Real time clock. Requires Level II Basic. Interface for 2 cassette decks complete with power supply




YOU NEED NEVER MISS AN IMPORTANT CALL AGAIN TWO CORDLESS TELEPHONE SYSTEMS — DIRECT FROM USA



THE ALCOM

only **£147** + VAT

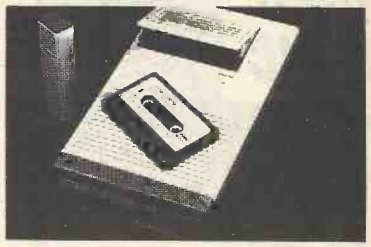Base station connects to your telephone line. Remote handset clips to your belt and gives you push-button dialling — Bleeps when call arriving — Nicad rechargeable batteries. Charger in base unit.



LOW COST TELEPHONE ANSWERING MACHINE

only **£99.95** + VAT

Microprocessor controlled answering machine. Plug into your phone line. Records any phone call messages. Remote bleeper enables you to listen to your messages from anywhere in the world. Uses standard cassettes. Comes complete with mains adaptor, microphone, remote bleeper, base unit, cassette with 30 sample pre-recorded messages.

COMMERCIAL EXPANDABLE ● COMPLETE TRS 80 · MODEL II



64K
1-Disk
Model II

£1995.00 + VAT


RRP £2250.00

The Model III is now in our showroom

This new unit from the world's most successful micro company is now available immediately with software.
The basic unit comes complete with 64 thousand characters (bytes) of Memory. The built in 8" Floppy disc adds another ½ million extra characters including the disc operating system. More disc expansion is now available.
The Model II is a complete unit with a full keyboard including a numeric pad and 12" screen which gives 24 lines of 80 characters. The computer is supplied with both the disc operating system and the Level III Basic.
A full self test routine is written into the power up procedure to eliminate incorrect operation. Both serial and parallel expansion sockets are standard. A printer is a plug-in operation.
Both hardware and software necessary to talk to a mainframe are included. Terminal usage is very possible. With the addition of CPM2 you can operate with COBOL, FORTRAN, MBASIC, CBASIC in which languages are many other applications packages i.e. accounting, payroll stock etc.

CP/M2	**£95.00**	M BASIC	**£155.00**
CIS COBOL	**£400.00**	FORTRAN	**£220.00**
C BASIC	**£75.00**	WORDSTAR	**£255.00**

COMP PRO MIXER

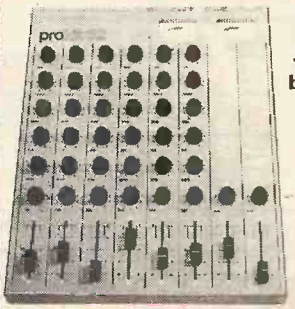


Professional audio mixer that you can build yourself and save over £100.

Only **£99.90** plus VAT for **complete** kit. Plus **FREE** power supply valued at £25.00

FULL RANGE OF ACCESSIT AUDIO ADD-ONS

Learn more about our products - Send £1 & S.A.E. for 1981 Spring Catalogue

RRP £540

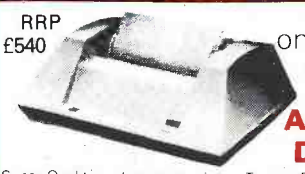

only **£399** + VAT


EXTENDED WARRANTY BY COMPUCARE

ANADEX DP8000

Super Quality — Low cost printer. Tractor Feed with full 96 ASCII character set. Accepts RS232C at band rates between 100 and 9600 and Parallel Bit data.
Attaches either directly or through interfaces to Pet, Apple, TRS80, Sorcerer, Nascom, Compukit etc.

EXTENDED WARRANTY BY COMPUCARE

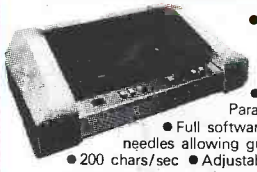THE NEW ANADEX DP9500 and DP9501 A PROFESSIONAL PRINTER



- Bi-directional printing
- Up to 220 chars/line with 4 print densities
- 500 char buffer
- RS232C and Centronics Parallel interface built in
- Full software control of matrix needles allowing graphics capability
- 200 chars/sec
- Adjustable width tractor feed.

DP9500 — ONLY **£795** + VAT
DP9501 — ONLY **£845** + VAT

THE ATARI VIDEO COMPUTER GAMES SYSTEM



£83.00 + VAT

EXTENDED WARRANTY BY COMPUCARE

Atari's Video Computer System now offers more than 1300 different game variations and options in twenty Game Program™ cartridges!

Most Cartriages only £13.90 + VAT
Prices may vary with special editions Basic Maths, Airsea Battle, Black Jack, Breakout, Surround, Spacewar, Video Olympics, Outlaw, Basketball, Hunt & Score*, Space War, Sky Diver, Air Sea Battle, Codebreaker*, Miniature Golf.

Extra Paddle Controllers — **£14.90** + VAT
*Keyboard Controllers — **£16.90** + VAT

SPACE INVADERS NOW IN STOCK £25



EUROPE'S FASTEST SELLING ONE BOARD COMPUTER

COMPUKIT UK101

★ 6502 based system — best value for money on the market. ★ Powerful 8K Basic — Fastest around ★ Full Qwerty Keyboard ★ 4K RAM Expandable to 8K on board. ★ Power supply and RF Modulator on board. ★ No Extras needed — Plug-in and go. ★ Kansas City Tape Interface on board. ★ Free Sampler Tape including powerful Dissassembler and Monitor with each Kit. ★ If you want to learn about Micros, but didn't know which machine to buy then **this is the machine for you.**

40 pin Expansion Jumper Cable for Compukit expansion **£8.50** + VAT

Build, Understand and Program your own Computer for only a small outlay.

KIT ONLY **£179** + VAT
NO EXTRAS NEEDED

Available ready assembled, tested & ready to go **£229** + VAT

NEW MONITOR FOR COMPUKIT UK101
● In 2K Eprom 2716 ● Allows screen editing ● Saves data on tape ● Flashing cursor ● Text scrolls down **£22.00** + VAT
Special Bonus SAVE £22. New Super Monitor inc. in each kit or sold separately for **£22** + VAT.

FOR THE COMPUKIT

Assembler/Editor	**£14.90**
Screen Editor Tape	**£5.90**

All Prices exclusive VAT

Game Packs

1. Four Games	**£5.00**
2. Four Games	**£5.00**
3. Three Games 8K only	**£5.00**
Super Space Invaders (8K)	**£6.50**
Space Invaders	**£5.00**
Chequers	**£3.00**
Real Time Clock	**£3.00**
Case for Compukit	**£29.50**

EXTENDED WARRANTY BY COMPUCARE



HITACHI PROFESSIONAL MONITORS

9" — ~~£129~~ **£99.95**
12" — ~~£199~~ **£149**

● **Reliability** Solid state circuitry using an IC and silicon transistors ensures high reliability. ● **500 lines horizontal resolution** Horizontal resolution in excess of 500 lines is achieved in picture center. ● **Stable picture** Even played back pictures of VTR can be displayed without jittering. ● **Looping video input** Video input can be looped through with built-in termination switch. ● **External sync operation** (available as option for U and C types) ● **Compact construction** Two monitors are mountable side by side in a standard 19-inch rack.

EXTENDED WARRANTY BY COMPUCARE

ENGLISH COLOUR TV/ AMERICAN NTSC COLOUR MONITOR

Suitable for Apple, Atari and Texas 99/4 **£295** +VAT


8MHz Super Quality Modulators	**£4.90**
6MHz Standard Modulators	**£2.90**
C12 Computer Grade Cassettes	10 for **£4.00**
Anadex Printer Paper — 2000 sheets	**£25.00**
Floppy Discs 5¼" Hard and Soft Sectored	**£3.50**
Floppy Disc Library Case 5¼"	**£3.50**
Verocases for Nascom 1 & 2 etc.	**£24.90**
Keyboard Cases	**£9.90**

MEMORY UPGRADES

16K (8 x 4116) **£29.90** +VAT
4K Compukit (8 x 2114) **£29.90** +VAT

SPECIAL OFFER

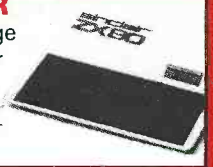
We will part exchange your Sinclair ZX80 for any of our products.



Refurbished ZX80's — fully guaranteed **£69.90** + VAT
Refurbished MicroAces —
(Supply dependant upon stocks).

NEW

TV GAME BREAK OUT

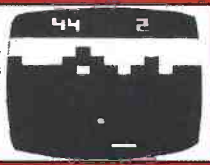

Has got to be one of the world's greatest TV games. You really get hooked. As featured in ETI. Has also 4 other pinball games and lots of options. Good kit for up-grading old amusement games.
MINI KIT — PCB, sound & vision modulator, memory chip and de-code chip. Very simple to construct. **£14.90** + VAT
OR PCB **£2.90** MAIN LSI **£8.50** Both plus VAT

We have one of the largest collections of Computer Books under one roof, along with racks of software for the PET and TRS80.
Come and see for yourself.

WE ARE NOW STOCKING THE APPLE II AT REDUCED PRICES



EXTENDED WARRANTY BY COMPUCARE

16K **£599**
32K **£649**
48K **£659**
} + VAT

Getting Started APPLE II is faster, smaller, and more powerful than its predecessors. And it's more fun to use too because of built-in features like:
● BASIC — The Language that Makes Programming Fun. ● High-Resolution Graphics (in a 54,000-Point Array) for Finely-Detailed Displays. ● Sound Capability that Brings Programs to Life. ● Hand Controls for Games and Other Human-Input Applications. ● Internal Memory Capacity of 48K Bytes of RAM, 12K Bytes of ROM; for Big-System Performance in a Small Package. ● Eight Accessory Expansion Slots to let the System Grow With Your Needs.
You don't need to be an expert to enjoy APPLE II. It is a complete, ready-to-run computer. Just connect it to a video display and start using programs (or writing your own) the first day. You'll find that its tutorial manuals help you make it your own personal problem solver.

NOW OPEN

OUR NEW SHOWROOM & SALES CENTRE AT

311 Edgware Road,
London W2.
Telephone: 01-262 0387

APPLE DISC II



Disc with Controller **£349** + VAT

EXTENDED WARRANTY BY COMPUCARE

Additional Drives **£299** + VAT

● Powerful Disk Operating Software Supports up to 6 drives ● Name Access to Files for Ease of Use ● BASIC Program Chaining to Link Software Together ● Random or Sequential File Access to Simplify Programming ● Dynamic Disk Space Allocation for Efficient Storage ● Individual File Write-Protection Eliminates Accidental File Alterations ● Loads an 8K Byte Binary Image in 6.5 sec. (1.2 sec. in Pascal) ● Storage Capacity of 116 Kilobytes (143K Bytes with Pascal) on Standard 5¼" Diskettes ● Powered Directly From the APPLE (Up to 6 Drives) for Convenience and High Reliability ● Packaged in Heavy-Duty, Colour-Coordinated Steel Cabinet

A SELECTION OF APPLE INTERFACES ARE NOW AVAILABLE AT OUR NEW SHOWROOM.

COMP SHOP LTD

"Europes Largest Discount Personal Computer Stores"

Delivery is added at cost. Please make cheques and postal orders payable to **COMPSHOP LTD.**, or phone your order quoting **BARCLAYCARD, ACCESS, DINERS CLUB** or **AMERICAN EXPRESS** number.

CREDIT FACILITIES ARRANGED — send S.A.E. for application form.

MAIL ORDER AND SHOP:
14 Station Road, New Barnet, Hertfordshire, EN5 1QW *(Close to New Barnet BR Station — Moorgate Line).*
Telephone: 01-441 2922 (Sales) 01-449 6596 Telex: 298755 TELCOM G
OPEN (BARNET) — 10am - 7pm — Monday to Saturday


NEW WEST END SHOWROOM:
311 Edgware Road, London W2. Telephone: 01-262 0387
OPEN (LONDON) — 10am - 6pm — Monday to Saturday

- **IRELAND:** 80 Marlborough Street, Dublin 1. Telephone: Dublin 749933
- **COMPSHOP USA,** 1348 East Edinger, Santa Ana, California, Zip Code 92705. Telephone: 0101 714 5472526

BARCLAYCARD VISA · AMERICAN EXPRESS · DINERS CLUB INTERNATIONAL · Access We welcome Access

COMP COMPUTER COMPONENTS
(Part of the Compshop Ltd. Group)

Make it for a Song!

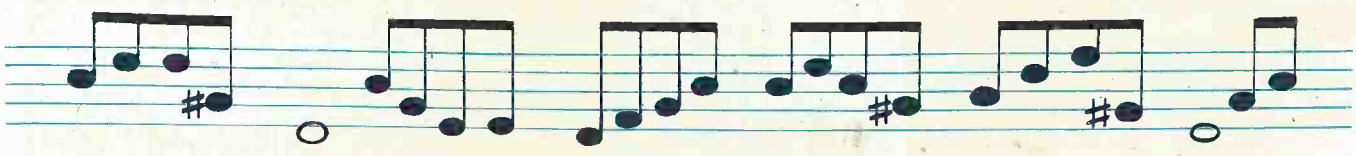

The New Maplin in Matinée

Amazing Value For Only **£299.95** + £99.50 for cabinet if required.

Easy to build. Latest technology — means less cost, less components and 80% less wiring. Comparable with organs selling for up to £1,000.00. Two 49-note manuals. 13-note pedalboard. All organ voices on drawbars. Preset voices: Banjo, Accordion, Harpsichord, Piano, Percussion. Piano sustain Sustain on both manuals, and pedalboard. Electronic rotor, fast and slow. Vibrato and Delayed vibrato. Reverb. Manual and Auto-Wah. Glide (Hawaiian Guitar Sound). Single finger chording plus memory. 30 Rhythms! 8-instrument voicing. Major, Minor and Seventh chords. Unique walking bass lines with each rhythm. Unique countermelody line with each rhythm. Truly amazing value for money. Full construction details in Electronics & Music Maker magazine.





The complete buyers' guide to electronic components. With over 300 pages, it's a comprehensive guide to electronic components with thousands of photographs and illustrations and page after page of invaluable data. Get a copy now — it's the one catalogue you can't afford to be without.

Post this coupon now for your copy of our 1981 catalogue price £1.
Please send me a copy of your 320 page catalogue. I enclose £1 (Plus 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the UK send £1.68 or 12 International Reply Coupons.
I enclose £1.25.

Name _____

Address _____

_____

ETI481

MAPLIN

Maplin Electronic Supplies Ltd.
All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR
Telephone: Southend (0702) 554155. Sales (0702) 552911.

Shops:
159-161 King Street, Hammersmith, London W6. Telephone: (01) 748 0926.
284 London Road, Westcliff-on-Sea, Essex. Telephone: Southend (0702) 554000.
Both shops closed Mondays.

Catalogue now on sale in all branches of WHSMITH Price £1.00

TTLs by TEXAS

7400	11p	74293	150p	4020	100p
74S00	60p	74298	200p	4022	100p
7401	12p	74365	100p	4023	27p
7402	12p	74366	100p	4024	50p
7403	14p	74367	100p	4025	20p
7404	14p	74368	100p	4026	130p
7405	18p	74390	200p	4027	50p
7406	36p	74393	200p	4028	84p
7407	38p	74490	225p	4029	100p
7408	17p	**74LS SERIES**		4030	55p
7409	19p	74LS00	14p	4031	200p
7410	15p	74LS02	16p	4034	200p
7411	24p	74LS03	18p	4035	110p
7412	20p	74LS04	16p	4036	295p
7413	30p	74LS05	25p	4039	295p
7414	40p	74LS08	22p	4040	100p
74C14	90p	74LS09	21p	4041	80p
7416	27p	74LS10	20p	4042	80p
7417	27p	74LS11	40p	4043	90p
7420	17p	74LS13	40p	4044	90p
7421	40p	74LS14	50p	4046	110p
7422	22p	74LS20	20p	4047	100p
7423	34p	74LS21	40p	4048	55p
7425	30p	74LS27	38p	4049	45p
7426	40p	74LS30	20p	4050	45p
7427	34p	74LS32	27p	4051	80p
7428	36p	74LS37	30p	4052	80p
7430	17p	74LS38	38p	4053	80p
7432	30p	74LS42	70p	4054	150p
7433	40p	74LS47	75p	4055	125p
7437	35p	74LS51	24p	4056	135p
7438	35p	74LS55	30p	4059	600p
7440	17p	74LS73	50p	4060	115p
7441	70p	74LS74	27p	4063	120p
7442A	60p	74LS75	38p	4066	50p
7443	112p	74LS76	45p	4067	450p
7444	112p	74LS83	70p	4068	27p
7445	100p	74LS85	80p	4069	20p
7446A	93p	74LS86	40p	4070	30p
7447A	75p	74LS90	40p	4071	25p
7448	80p	74LS92	70p	4072	25p
7450	17p	74LS93	50p	4073	25p
7451	17p	74LS96	110p	4075	25p
7453	17p	74LS107	45p	4076	107p
7454	17p	74LS109	80p	4081	27p
7460	17p	74LS112	40p	4082	27p
7470	36p	74LS113	90p	4086	72p
7472	30p	74LS114	46p	4089	150p
7473	34p	74LS122	80p	4093	70p
7474	30p	74LS123	60p	4094	250p
7475	38p	74LS124	180p	4095	95p
7476	32p	74LS125	50p	4096	95p
7480	50p	74LS126	50p	4097	340p
7481	100p	74LS132	60p	4098	120p
7482	84p	74LS133	30p	4099	200p
7483a	90p	74LS136	55p	40100	220p
7484	100p	74LS138	65p	40101	132p
7485	110p	74LS139	75p	40102	180p
7486	34p	74LS145	120p	40103	180p
7489	210p	74LS147	220p	40104	99p
7490A	30p	74LS148	175p	40105	120p
7491	80p	74LS151	80p	40106	90p
7492A	46p	74LS153	60p	40107	60p
7493A	36p	74LS154	200p	40108	470p
7494	84p	74LS155	80p	40109	100p
7495A	70p	74LS156	90p	40110	300p
7496	65p	74LS157	60p	40114	250p
7497	180p	74LS158	60p	4502	120p
74100	130p	74LS160	90p	4503	70p
74107	34p	74LS161	75p	4507	55p
74109	55p	74LS162	140p	4508	290p
74116	200p	74LS163	100p	4510	99p
74118	130p	74LS164	90p	4511	120p
74119	210p	74LS165	140p	4512	80p
74120	110p	74LS166	180p	4514	250p
74121	34p	74LS173	110p	4515	300p
74122	48p	74LS174	100p	4516	110p
74123	60p	74LS175	100p	4518	100p
74125	75p	74LS181	320p	4520	100p
74126	60p	74LS190	100p	4521	250p
74128	75p	74LS191	100p	4526	108p
74132	75p	74LS192	100p	4527	150p
74136	75p	74LS193	100p	4528	100p
74137	50p	74LS195	140p	4532	140p
74141	50p	74LS196	120p	4534	550p
74142	200p	74LS197	90p	4536	375p
74145	90p	74LS221	120p	4538	120p
74147	190p	74LS240	175p	4543	180p
74148	150p	74LS241	175p	4553	320p
74150	130p	74LS242	170p	4556	72p
74151A	70p	74LS243	170p	4560	200p
74153	70p	74LS244	150p	4569	250p
74154	120p	74LS245	250p	4572	40p
74155	90p	74LS247	140p	4583	110p
74156	90p	74LS251	140p	4584	90p
74157	70p	74LS253	90p	4585	150p
74159	190p	74LS257	90p	4724	250p
74160	100p	74LS258	160p	40097	90p
74161	100p	74LS259	160p	14411	1100p
74162	100p	74LS266	100p	14412	1100p
74163	100p	74LS273	170p	14433	1100p
74164	120p	74LS279	90p	14500	700p
74165	130p	74LS283	90p	14599	290p
74166	120p	74LS298	160p	**INTERFACE ICs**	
74167	200p	74LS323	400p	AD536A	£13
74170	240p	74LS324	200p	AD561J	1400p
74172	450p	74LS348	200p	AD7524	600p
74173	120p	74LS365	48p	DM8123	175p
74174	90p	74LS367	70p	DM8131	375p
74175	85p	74LS368	100p	DP8304	450p
74176	90p	74LS373	150p	DS8835	250p
74177	90p	74LS374	150p	DS8836	150p
74178	160p	74LS375	120p	DS8838	225p
74180	93p	74LS377	160p	MC1488	75p
74181	160p	74LS378	140p	MC1489	75p
74182	90p	74LS390	120p	MC3446	300p
74184A	150p	74LS393	120p	25S10	350p
74185	150p	74LS399	200p	75107	160p
74186	500p	74LS445	140p	75110	325p
74188	325p	74LS670	400p	75150	175p
74190	120p	**4000 SERIES**		75154	175p
74191	120p	4000	15p	75182	230p
74192	100p	4001	22p	75322	300p
74193	100p	4002	20p	75324	375p
74194	120p	4006	95p	75361	300p
74195	95p	4007	20p	75363	400p
74196	95p	4008	80p	75365	200p
74197	80p	4009	40p	75451/2	72p
74198	150p	4010	50p	75491/2	70p
74199	150p	4011	20p	8T26	160p
74221	160p	4012	25p	8T28	250p
74251	140p	4013	50p	8T95	180p
74259	250p	4014	84p	8T97	180p
74278	290p	4015	84p	81LS95	120p
74279	110p	4016	45p	81LS96	140p
74283	140p	4017	70p	81LS97	120p
74284	360p	4018	89p	81LS98	140p
74285	360p	4019	45p	9602	220p

93 SERIES

9301	160p
9302	175p
9308	316p
9310	275p
9311	275p
9312	160p
9314	165p
9316	225p
9321	225p
9322	150p
9334	360p
9368	250p
9370	300p
9374	200p

74S SERIES

74S00	60p	74S114	120p
74S04	60p	74S124	300p
74S05	75p	74S132	160p
74S08	75p	74S133	75p
74S10	60p	74S138	225p
74S20	60p	74S139	225p
74S30	60p	74S157	250p
74S32	90p	74S174	250p
74S37	90p	74S175	320p
74S64	60p	74S194	350p
74S74	90p	74S241	450p
74S85	300p	74S260	70p
74S86	180p	74S373	500p
74S112	120p	74S374	500p

LINEAR ICs

AY1-0212	600p	LM13600	125p
AY1-1313	668p	MB3712	150p
AY1-1320	320p	MC1310P	150p
AY1-5050	140p	MC1458	48p
AY3-1270	840p	MC1495L	350p
AY3-8912	650p	MC1496	70p
AY5-1224A	240p	MC3340P	120p
AY5-1315	600p	MK50398	750p
AY5-1317A	775p	ML920	775p
AY5-4007D	520p	MM57160	620p
CA3019	80p	NE531	150p
CA3046	70p	NE555	20p
CA3048	225p	NE556	70p
CA3080E	72p	NE562B	425p
CA3086	48p	NE564	420p
CA3089E	225p	NE565	130p
CA3090AQ	375p	NE566	165p
CA3130E	90p	NE567	140p
CA3140E	50p	NE571	425p
CA3160E	100p	NE5534A	250p
CA3161E	140p	RC4136	80p
CA3162E	450p	S566B	270p
CA3189E	300p	SAD1024A	1250p
CA3280	160p	SFF96364	1100p
DAC1408-8	200p	SL490	400p
FX209	750p	SN76477	180p
HA1388	280p	SP8515	750p
ICL7106	850p	TA7205	140p
ICL8038	300p	TAA621	275p
ICM7555	80p	TBA641B11	300p
LF13331	310p	TBA651	200p
LF351	48p	TBA800	90p
LF356P	95p	TBA810	100p
LM10C	425p	TBA820	80p
LM301A	27p	TBA950	300p
LM311	70p	TCA220	350p
LM318	200p	TCA940	175p
LM319	225p	TDA1004	300p
LM324	45p	TDA1008	320p
LM339	75p	TDA1010	225p
LM348	95p	TDA1022	570p
LM358P	50p	TDA1024	120p
LM377	175p	TDA1034B	250p
LM380	75p	TDA1170	300p
LM381AN	180p	TOA2002V	325p
LM386	95p	TDA2020	320p
LM393	100p	TL071/81	45p
LM709	36p	TL072/82	75p
LM710	50p	TL074	130p
LM725	350p	TL084	110p
LM733	100p	TL170	50p
LM741	18p	UAA170	175p
LM747	70p	UDN6118	320p
LM748	35p	UDN6184	320p
LM2917	250p	ULN2003	100p
LM3302	140p	XR2206	300p
LM3900	70p	ZN414	90p
LM3909	70p	ZN419C	225p
LM3911	130p	ZN424E	135p
LM3914	225p	ZN425E	400p
LM3915	225p	ZN427E	750p
		ZN1034	200p

VOLTAGE REGULATORS

Fixed Plastic TO-220

	+ve		-ve	
1A				
5V	7805	60p	7905	65p
12V	7812	60p	7912	65p
15V	7815	60p	7915	70p
18V	7818	60p	7918	70p
24V	7824	60p	7924	70p
100mA	TO 92			
5V	78L05	30p	79L05	70p
12V	78L12	30p	79L12	70p
15V	78L15	30p	79L15	70p

OTHER REGULATORS

LM309K	135p	78HGKC	600p
LM317T	200p	78HO5KC	550p
LM323K	500p	78MGT2C	135p
LM723	37p	79HGKC	600p
		TL497	300p

OPTO-ELECTRONICS

2N5777	45p	ORP60	120p
OCP71	90p	ORP61	120p
ORP12	120p	TIL78	55p

OPTO-ISOLATORS

ILD74	130p	TIL111	90p
MCT26	100p	TIL112	90p
MCS2400	190p	TIL116	90p

LEDS

0.125"		0.2"	
TIL32	55p	TIL220 Red	16p
TIL209 Red	13p	TIL222 Gr	18p
TIL211 Gr	20p	TIL228 Red	22p
TIL212 Ye	25p	Rectangular	
TIL216 Red	18p	LEDs (R, G, Y)	30p
		NSB5881	570p
		TIL311	600p
DISPLAYS		TIL312/3	110p
3015F	200p	TIL321/2	130p
DL704	140p	TIL330	140p
DL707 Red	140p	7750/60	200p
FND357	120p	**DRIVERS**	
FND500	110p	9368	250p
FND507	110p	9370	300p
MAN3640	175p	UDN611B	320p
MAN4640	200p	UDN6184	320p

TRANSISTORS

AC126	25p	BFR40	25p	TIP30A	48p	2N3055	48p
AC127/8	20p	BFR41	25p	TIP30C	60p	2N3442	140p
AC176	25p	BFR79	25p	TIP31A	58p	2N3553	240p
AC187/8	25p	BFR80	25p	TIP31C	62p	2N3565	30p
AF116	50p	BFR81	25p	TIP32A	68p	2N3584	250p
AD149	70p	BFX29	40p	TIP32C	82p	2N3643/4	48p
AD161/2	45p	BFX30	34p	TIP33A	90p	2N3702/3	12p
AU107	200p	BFX84/5	40p	TIP33C	114p	2N3704/5	12p
BC107/8	11p	BFX86/7	30p	TIP34A	115p	2N3706/7	14p
BC109	11p	BFX88	30p	TIP34C	160p	2N3708/9	12p
BC117	20p	BFW10	90p	TIP35A	225p	2N3773	300p
BC147/8	9p	BFY50	30p	TIP35C	290p	2N3819	25p
BC149	10p	BFY51/2	30p	TIP36A	270p	2N3820	50p
BC157/8	10p	BFY56	33p	TIP36C	340p	2N3823	70p
BC159	11p	BFY90	90p	TIP41A	65p	2N3866	90p
BC169C	12p	BRY39	45p	TIP41C	78p	2N3902	700p
BC172	12p	BSX19/20	20p	TIP42A	70p	2N3903/4	18p
BC177/8	17p	BU104	225p	TIP42C	82p	2N3905/6	20p
BC179	18p	BU105	190p	TIP54	160p	2N4037	65p
BC182/3	10p	BU108	250p	TIP120	120p	2N4058/9	12p
BC184	11p	BU109	225p	TIP122	130p	2N4060	12p
BC187	30p	BU126	150p	TIP142	130p	2N4061/2	18p
BC212/3	11p	BU180A	120p	TIP147	130p	2N4123/4	27p
BC214	12p	BU205	200p	TIP2955	78p	2N4125/6	27p
BC237	15p	BU208	200p	TIP4055	70p	2N4401/3	27p
BC327	16p	BU406	145p	TIS43	45p	2N4427	90p
BC337	16p	E300	50p	TIS93	30p	2N4871	60p
BC338	16p	E308	50p	ZTX108	12p	2N5087	27p
BC461	36p	E310	50p	ZTX300	13p	2N5089	27p
BC477/8	30p	MJ2501	225p	ZTX500	15p	2N5172	27p
BC516/7	40p	MJ2955	90p	ZTX502	18p	2N5179	90p
BC5478	16p	MJ3001	225p	ZTX504	30p	2N5191	90p
BC548C	9p	MJE340	50p	2N457A	250p	2N5194	90p
BC549C	18p	MJE2955	100p	2N696	35p	2N5245	40p
BC557B	16p	MJE3055	70p	2N697	25p	2N5296	55p
BC559C	18p	MPF102	45p	2N698	45p	2N5401	50p
BCY70	18p	MPF103/4	40p	2N706A	30p	2N5457/8	40p
BCY71/2	22p	MPF105/6	40p	2N708	30p	2N5459	40p
BD131/2	50p	MPS6531	50p	2N918	45p	2N5460	60p
BD135/6	54p	MPS6534	50p	2N930	18p	2N5485	44p
BD139	56p	MPSA06	50p	2N1131/2	36p	2N5875	250p
BD140	60p	MPSA12	50p	2N1613	25p	2N6027	48p
BD189	60p	MPSA13	50p	2N1711	25p	2N6041	160p
BD232	95p	MPSA20	50p	2N2102	70p	2N6044	160p
BD233	75p	MPSA42	50p	2N2160	350p	2N6052	300p
BD235	85p	MPSA43	50p	2N2219A	30p	2N6059	325p
BD241	70p	MPSA56	32p	2N2222A	30p	2N6107	65p
BD242	70p	MPSA70	50p	2N2369A	25p	2N6247	190p
BDY56	200p	MPSU06	63p	2N2484	30p	2N6254	130p
BF200	32p	MPSU45	90p	2N2904/5	30p	2N6290	65p
BF244B	35p	MPSU65	78p	2N2906A	30p	2N6292	65p
BF256B	70p	OC28	130p	2N2907A	30p	2SC1172	150p
BF257/8	32p	OC35	130p	2N2926	9p	3N128	120p
BF259	36p	TIP29A	40p	2N3053	30p	3N140	120p
BFR39	25p	TIP29C	55p	2N3054	65p	3N141	110p
						3N201	110p

MEMORIES

2101-4L	400p
2102-2L	120p
21078	800p
2111-2	280p
2112-2	300p
2114	300p
2114-2L	800p
4027-3	375p
4044	900p
4116	400p
4118-4	£10
5101	400p
6514-45	£5
6810	325p
74S201	400p
82516	325p

ROM/PROMs

71301	700p
74S188	225p
74S287	350p
74S470	650p
74S471	650p
74S571	650p

CPUs

1600	1200p
1802CE	750p
2650A	£16
6502	600p
6800	550p
6802	950p
6809	£16
8080A	450p
8085A	1100p
INS8060	1000p
TM59980A	£20
Z80	600p
Z80A	800p

EPROMs

1702A	800p
2708	450p
2716 (+5V)	£7
2532	£12
2732	£12

SUPPORT DEVICES

3242	800p
3245	480p
6522	600p
6532	825p
6820	375p
6821	340p
6845	£16
6850	300p
6852	370p
8155	1100p
8205	320p
8212	200p
8216	200p
8224	275p
8226	250p
8228	525p
8251	475p
8253	1000p
8255	450p
8257	900p
8259	950p

TMS9918	POA
Z80P10	800p
Z80AP10	700p
Z80CTC	800p
Z80ACTC	700p
Z80ADART	£15
Z80S10-1	£24
MC1441L	1100p

UART

AY-3-1015P	450p
AY-5-1013A	400p
IM6402	480p

CHARACTER GENERATORS

3257ADC	990p
RO-3-2513 UC	600p
RO-3 2513 LC	700p
SN74S262AN	£10

KEYBOARD ENCODER

AY-5-2376	700p
74C922	600p

CRYSTALS

32.768KHz	250p
100KHz	300p
200KHz	370p
1.0MHz	320p
1.008MHz	350p
1.8432MHz	325p
2.00MHz	325p
2.457600MHz	325p
3.276MHz	300p
3.579MHz	175p
4.00MHz	290p
4.194MHz	POA
4.43MHz	125p
5.0MHz	325p
6.0MHz	300p
6.144MHz	300p
7.0MHz	300p
7.168MHz	300p
8.00MHz	300p
8.867MHz	300p
10.00MHz	310p
10.7MHz	300p
12.0MHz	350p
16.00MHz	350p
18.00MHz	300p
18.432	350p
19.968MHz	390p
26.690MHz	350p
27.145MHz	325p
38.6667MHz	350p
48.0MHz	300p
55.5MHz	400p
116.0MHz	350p

3N204	120p
40290	250p
40360	40p
40361/2	75p
40364	120p
40408	90p
40409	100p
40410	100p
40411	300p
40594	120p
40595	120p
40673	75p
40841	90p
40871/2	100p

DIODES

BY127	12p
BYX36-300	20p
OA47	9p
OA81	15p
OA85	15p
OA90	9p
OA91	9p
OA95	9p
OA200	9p
OA202	10p
1N914	4p
1N916	7p
1N4148	4p
1N4001/2	5p
1N4003/4	6p
1N4005	8p
1N4006/7	7p
1N5401/3	14p
1N5404/7	19p
IS920	9p

HEAT SINKS

For TO220 Voltage Regs and Transistors 22p
For TO5 12p

BRIDGE RECTIFIERS

1A 50V	19p
1A 100V	20p
1A 400V	25p
1A 600V	30p
2A 50V	30p
2A 100V	35p
2A 400V	45p
3A 200V	60p
3A 600V	72p
4A 100V	95p
4A 400V	100p

6A 50V	80p
6A 100V	100p
6A 400V	120p
10A 400V	200p
25A 400V	400p

ZENERS

2.7V-33V	
400mW	9p
1W	15p

TRIACS PLASTIC

3A 400V	60p
6A 400V	70p
6A 500V	88p
8A 400V	75p
8A 500V	95p
12A 400V	85p
12A 500V	105p
16A 400V	110p
16A 500V	130p
T2800D	130p

THYRISTORS

1A 50V	70p
1A 400V	90p
3A 400V	100p
8A 400V	140p
12A 400V	160p
16A 100V	160p
16A 400V	180p
BT106	110p
C106D	45p
MCR101	36p
TIC44	27p
2N3525	130p
2N4444	140p
2N5060	34p
2N5064	40p

LOUDSPEAKERS

Size		
2½"	64R	80p
2½"	8R	80p
2"	8R	90p
1½"	8R	100p

MODULATORS

6MHz UHF	375p
8MHz UHF	480p

LOW PROFILE DIL SOCKETS BY TEXAS

8 pin	9p	18 pin	18p	24 pin	24p
14 pin	10p	20 pin	20p	28 pin	30p
16 pin	11p	22 pin	22p	40 pin	40p

WIRE WRAP SOCKETS BY TEXAS

8 pin	28p	18 pin	50p	24 pin	70p
14 pin	35p	20 pin	60p	28 pin	80p
16 pin	40p	22 pin	65p	40 pin	100p

ZERO INSERTION FORCE SKT

24 pin £7

HEADER PLUGS

14 pin	50p
16 pin	60p
24 pin	100p
40 pin	275p

SOFTY: Ideal Software/Hardware Development tool. Using SOFTY you can develop your Programmes, Debug/Verify and then commit them to EPROM
KIT £100 BUILT AND TESTED £125
Also available Expansion Board for Programming single rail (+5v) EPROMS. **Ready built £40**

MINI FLOPPY DISC DRIVE MECHANISM: Teac Type FD-50A 40 track 5¼" Double/Single Density drives **£140**
FLOPPY DISC CONTROLLER: FD1771 **£24**, FD1791 **£36**, FD1691 **£15**, 2143 **£5.50**.
EPROM ERASERS: Type UV140. Will erase up to 14 EPROMS in approx. 20 mins. Has slide-in tray for safe use. MAINS and ERASE Indicators **£61.50**

NANOCOMP MICROPROCESSOR TRAINER. As described in WW, January 1981. A complete kit of parts available (excluding PCB and the case). The kit includes pre-programmed 2716, sockets for all ICs and PSU parts as well. Price £64 inc. VAT and P&P.

VEROBOARDS 0.1 (copper clad)

2.5×3.75"	65p
2.5×5"	75p
3.75×3.75"	75p
3.75×5"	88p
3.75×17"	340p
4.75×17.9"	420p
Pkt of 100 pins	50p
Spot face cutter	88p
Pin insertion tool	118p
Vero Wiring Pen	

ANTEX SOLDERING IRONS

C-15W	415p
CX-17W	425p
CCN-15W	425p
X25	440p

SPARE BITS

C/CX/CCN	60p
X25	50p

SPARE ELEMENTS

C/CX/X25	180p
CCN	200p

COUNTERS

74C925	550p	MC4024	325p
74C928	600p	MC4044	325p
ICM7216B	2000p	10116	700p
ICM7217A	850p	10231	350p
ZN1040E	700p		

TTL & ECL

★SPECIAL OFFERS★

	1-24	25-99	100
2114-4L (450ns)	1.75	1.60	1.50
2708	3.90	3.75	3.50
2716 (+5V)	4.00	3.75	3.50
4116-2L (200ns)	1.75	1.60	1.50

BOOKS by TEXAS INSTRUMENTS

TTL Data Book (700 pages)	£6.80
Power Semiconductor Data Book (600 pages)	£4.50
Linear Control Data Book (368 pages)	£3.00
Software Design for Microprocessors (400 pages)	£11.00
The Great Int'l Maths on Keys (208 pages)	£3.50
Understanding Microprocessors (240 pages)	£3.50
Understanding Solid State Electronics (240 pages)	£3.50
Understanding Digital Electronics (240 pages)	£3.50
Understanding Communications Systems	P.O.A.
Others: TTL Cook Book	£7.25
CMOS Cook Book	£7.75
Microprocessor Interfacing Techniques	£9.95

Please add 70p P&P on each book (NO VAT)

BREADBOARDS

EXP300	£575p
EXP350	315p
EXP600	630p
EXP650	360p
PB6	920p
PB100	1180p
PB102	2295p
PB103	3445p

THANDOR TEST EQUIPMENT

DM235 Digital Multimeter	£50
DM350 Digital Multimeter	£69
TM352 Hand Held DMM	£48
TF200 Frequency Meter	£145
TG105 Pulse Generator	£81

P&P £2.50 per item + VAT

We carry a large stock of 74 and 74LS TTLs, CMOS, Linears, Memories, etc. and can normally offer ex-stock deliveries. We welcome inquiries for volume quantities both from local and overseas buyers.

NEW RETAIL SHOP
367 Edgware Road, W2
Open: 9.30—5.30

Please add 30p P&P & VAT 15%.
Government, Colleges, etc. Orders accepted.
CALLERS WELCOME
Mon-Fri 9.30-5.30
Saturday 10.30-4.30

TECHNOMATIC LTD.

17 BURNLEY ROAD, LONDON NW10
(2 minutes Dollis Hill tube station) (ample street parking)
Tel: 01-452 1500/01-450 6597 Telex: 922800



Hidden Security

A new system from STC Electronic Security Systems (STC-ESS) protects itself while it is protecting the customer. The ITT Access Control System, now marketed by STC has no visible mechanism to vandalise or attack at the point of entry. It operates by proximity. A hidden sensor reads a credit-card-size command key and transmits signals to a unit which controls and records access. Conventional keys, key holes or card slots are not used. The command key can even be used while it is still inside a wallet, pocket or bag or is being used as a lapel badge.

The system is modularly expandable and can be integrated into existing or planned security and environmental systems requiring control of multiple access locations. More information on Access Control Systems and other STC security products is available by contacting STC-ESS, 313 Ballards Lane, London N12.

Wire Cutting

If you've ever had an electrical fault in your Rolls, you're only too well aware of the jungle of wires that lurk beneath your bonnet, the colour coding cleverly hidden under years of crud. Ripault of Enfield in collaboration with Liverpool University's Dept. of Electrical Engineering and Electronics have addressed themselves to the sticky problem of cutting down the wiring harness to something a little more manageable.


The prototype has already been installed in a Maxi. It uses 10 m of twin core cable instead of 100 m of 130 separate leads used in the conventional Leyland harness. The wire links a number of electronic control boxes, one core carrying power and the other digital control signals for the black boxes. Not only does this method cut down enormously the amount and complexity of the vehicle's wiring, but it also eliminates the use of high current electromechanical relays which are subject to contact wear.

The system is designed to meet a BL specification. Amongst the requirements are that the system should operate under the hostile environment of the engine compartment. That means surviving a temperature range of -40°C to +120°C.

Benefits of the new system include low power consumption, quick and convenient fault diagnosis and easier servicing. A security system could also be built-in.

IC Survival


Winslow Component Systems has introduced a new range of IC sockets designed to be virtually indestructable. The heart of the socket is a new contact featuring an inverted leaf design. This double-sided inverted leaf allows for a certain degree of careless handling when inserting an IC, which also facilitates the use of automatic insertion equipment. It is available in two versions — the W3200 series, which has tin plated contacts, for the lower cost consumer type applications and the W3300, aimed at the industrial and professional market incorporating tin and gold plated contacts which are totally insulated from surface tracks on double sided PCBs. The W3300 is also 100% anti-wicking. Both versions come in the complete range of contact configurations from 8-40 pins, they are only 0.15" high and are moulded in UL approved glass reinforced polyester.

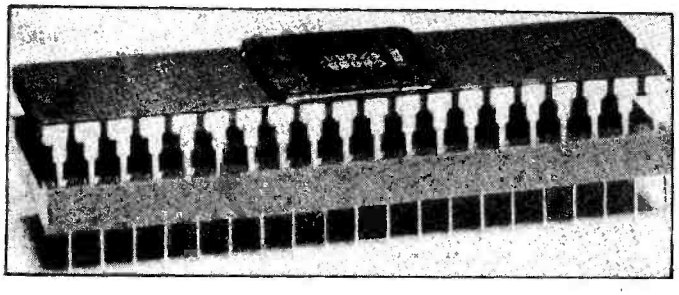

Teach Yourself Video

Have you invested in a video recorder, but haven't yet discovered its full potential? If the sole function of your recorder is to commit 'Crossroads' to tape, a new publication from 'those awfully nice Sony people' might widen your horizons. Their 48 page full colour handbook 'How To Video' is on sale at their 134 Regent Street showroom in London for 60p (also by post for 90p).

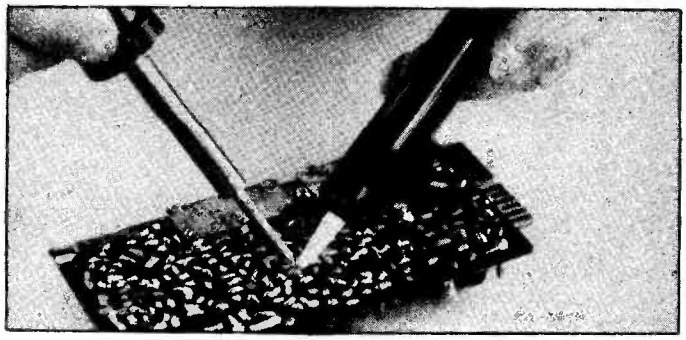Video recorders are very complex electronic devices, but are nevertheless simple to operate. 'How To Video' uses simple, non-technical language and ample illustrations to explain what your recorder is capable of, how to make home movies, the use of sound and lighting and even the creation of professional style, special effects and titling.



Suck It And See

New from OK Machine & Tool (UK) Ltd is the DSP-1 desolder pump. OK claim that it features industrial performance at an economy price. For about £6.00 you can arm your toolkit with this all-metal device, with an easy-to-replace Teflon tip — self-cleaning on each stroke.

The DSP-1 desolder pump is supplied by OK Machine & Tool (UK) Ltd, Dutton Lane, Eastleigh, Hants SO5 4AA.

April Fair

Keep April 14th to 16th of 1981 free in your diary for the gathering of the clans in the Polytechnic of North London Theatre when the Association of London Computer Clubs hold their second London Computer Fair. For only 75p you can spend a day in North London in the company of everyone who is anyone in personal computing. In addition to retail stands you can visit seminars, workshops and club stands. There's even a bring and buy sale. If you're within reach of a tube station, you're half way there. The venue, the Polytechnic of North London, is opposite Holloway Road tube station.

- ORDER BY POST OR TELEPHONE WITH BARCLAYCARD/ACCESS
- ELECTRONIC TEST EQUIPMENT SPECIALISTS
- CALL IN AND SEE FOR YOURSELF


AUDIO ELECTRONICS

- ALL MODELS ON DISPLAY
- RETAIL – MAIL ORDER EXPORT – INDUSTRIAL
- OPEN SIX DAYS A WEEK

ALL PRICES INCLUDE VAT

SCOPES

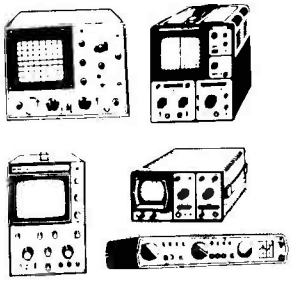A range of Scopes in stock from 5mHZ Single Trace to 50mHZ Dualtrace. Mains and Battery/Mains Portables. Many on demonstration.



SINGLE TRACE (UK c/p etc £2.50)

Hm 307-3 10mHZ. 5mV, 6 x 7 cm display plus component test **£158.78**
CO1303D 5mHZ, 10mHZ, 7 x 7cm display **£109.25**
SC110 10mHZ battery portable, 10mV 3.2 x 2.6cm display (Optional case **£8.86**. Nicads **£8.63**. Mains unit **£4**) **£158.95**
***LBO512A** 10mHZ 10mV. 5" display **£195.00**
CS1559A 10mHZ 10mV. 5" display **£190.50**
***V151** 15mHZ 1mV 5" display **£241.50**

OPTIONAL PROBES (ALL MODELS)

XI **£6.50**, X10 **£8.50**, X100 **£12.95**, X1-X10 **£10.95**

*PRICE INCLUDES FREE PROBE(S)


DUAL TRACE (UK c/p etc £3.50)

CS1562A 10mHZ, 10mV 5" display **£267.00**
CS1575 5mHZ 1mV 5" display **£284.00**
Hm 312-8 20mHZ. 5mV 8 x 10cm display **£253.00**
CS1566A 20mHZ, 5mV, 5" display **£339.00**
***LBO 3085** 70mHZ, 2mV, 5 x 6.3cm display. Battery/mains. Portable built-in Nicads **£482.00**
HM412-4 20mHZ, 5mV, 8 x 10cm display plus Sweep Delay **£399.50**
CS1577A 35mHZ, 2mV, 5" display **£478.00**
CS1830 30mHZ, 2mV. 5" display plus sweep delay and delay line — new model **£569.00**
Hm512-8 50mHZ, 5mV, 10 x 8cm display. Delay Sweep **£667.00**
***LBO514** 10mHZ, 1mV, (5mV) 5" display **£294.00**
***V152** 15mHZ, 1mV, 5" display **£326.00**
***V302** 30mHZ, 1mV, 5" display **£447.35**
***V550** 50mHZ, 1mV, 10 x 8cm Delay sweep + 3 channel display **£799.25**

HAMEG ● TRIO ● LEADER ● SINCLAIR ● HITACHI

GENERATORS

(UK c/p **£1.75**)

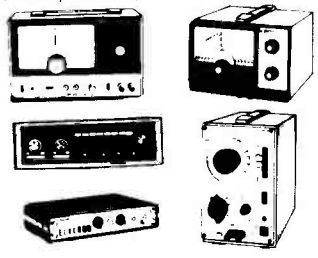

TRIO ● LEADER ● CSC SINCLAIR ● LEVELL

RF

SG402 100 KHZ-30mHZ with AM modulation **£68.00**
LSG16 100KHZ-100mHZ (300mHZ on Harmonics) **£63.25**
SG2030 250KHZ-100mHZ low cost range **£46.95**
ARF 300 18HZ-200mHZ low cost range audio and RF **£76.95**

PULSE

2001 1HZ-100KHZ (function) **£89.70**
TG105 5HZ-5mHZ **£92.50**
4001 0.5HZ-5mHZ **£109.25**
TT100 (function 10KHz) **£90.85**

AUDIO (All sine/square)

AG202A 20HZ— 200KHZ **£69.00**
LAG26 20HZ— 200KHZ **£73.60**
AG203 10HZ— 1mHZ sine/sq **£126.75**
LAG120A 10HZ— 1mHZ **£146.00**

LOGIC PROBES/MONITORS

Logic probes indicating high/low, etc., states that scopes can miss. All circuit powered for all ICs.

LP3 50 mHZ logic probe **£55.95**
LP1 10 mHZ logic probe **£35.50**
LP2 1½ mHZ logic probe **£19.95**
LM1 Logic monitor **£33.00**
LDP 50 MHz logic probe with case **£51.00**
Also in stock range of Protoboard kits and breadboards.

'PRO' MULTIMETERS

M1200 100K/Volt 30 ranges plus AC/DC 15 amp **£67.00**
K1400 20K/Volt 23 range large scale **£79.95**
M1500 20K/Volt 42 range plus AC/DC 10 amp **£53.50**
(UK c/p **£1.20**)
K200 38 range FET 10m ohm input 20Hz to 30MHz multimeter **£95.00**
(UK c/p **£1.50**)

SWR/FS AND POWER METERS




Range in stock covering up to 150mHZ and up to 1K watt power PL259 sockets. Also 250 UHZ Grid Dipmeter.
SWR9 SWR/S 3-150mHZ £9.50
SWR50 SWR/Power meter. 3½-150mHZ 0-1000 watts £13.95
110 SWR/Power 1½-144mHZ 0/10/100 watts £11.50
171 As 110 Twin meter plus F/S £14.50
Plus large range of BNC/PL259/etc leads / plugs / adaptors / connectors always in stock.
176 SWR/Power/FS 1½-144mHZ 5-50 watt £16.68
KDM6 Gnd Dip 1½-250mHZ £38.50

DIGITAL MULTIMETERS

KAISE ● SINCLAIR ● LASCAR ● THURLBY

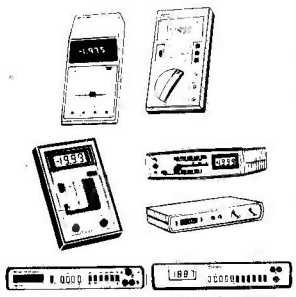A range of LED and LCD Bench and Hand DMM's battery operated with optional Mains Adaptors some with optional Nicads. All supplied with batteries and leads.



HAND HELD (UK post etc 85p)


TM352 3½ Digit LCD plus 10 ADC and Hfe checker **£54.95**
TM354 3½ Digit LCD 2A AC/DC **£45.94**
ME502 3½ Digit LED plus 10A DC and Hfe checker **£43.95**
LM2001 3½ Digit LCD 2 amp AC/DC 0.1 % **£51.70**
6200 3½ Digit LCD 0.2A AC/DC. Auto range **£45.95**
6220 As 6200 plus 10A AC/DC **£55.95**
6100 As 6200 plus Cont. test/range hold **£69.95**
6110 As 6100 plus 10A AC/DC **£85.95**
GL35C 3½ Digit LCD 1A AC/DC with case **£37.50**

BENCH PORTABLES

(UK c/p £1)

DM235 3½ Digit LED 21 ranges, 0.5% AC/DC 2A **£60.38**
DM350 3½ Digit LED 34 ranges AC/DC 10A **£87.38**
TM353 3½ Digit LCD AC/DC 2 amp **£96.60**
TM351 3½ Digit LCD AC/DC 10 amp **£113.85**
LM100 3½ Digit LCD AC/DC2 amp **£86.50**
DM450 4½ Digit LED 34 ranges AC/DC 10 amp **£113.85**
(DM series options. Carry case £8.86 Nicads £8.63 Mains adaptor £4)


MULTIMETERS (UK post etc 75p)

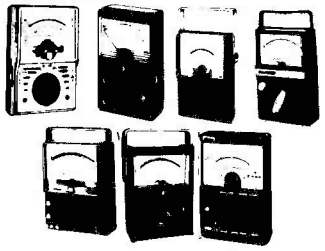

KRT101 1K/Volt 10 range pocket **£4.60**
ATM1/LT1 1K/Volt 12 range pocket **£5.98**
NH55 2K/Volt 10 range pocket **£6.50**
ATI 2K/Volt 12 range pocket de luxe **£7.75**
NH56 20K/Volt 22 range pocket **£11.95**
YN360TR 20K/Volt 19 range pocket plus hfe test **£13.50**
AT1020 20K/Volt 19 range de luxe plus hfe test **£16.95**
7081 50K/Volt 36 range plus 10 amp DC **£20.80**
TR303TR 20K/Volt + 12A DC + Hfe test **£15.95**
AT20 20K/Volt 21 range de luxe plus 10A DC and 5KV DC **£21.95**
AT205 50K/Volt 21 range de luxe plus 10A DC **£24.95**
7080 20K/Volt 26 range large scale, 10A DC plus 5KV AC/DC **£26.95**
AT2050 50K/Volt 18 range de luxe plus hfe test **£28.50**
AT210 100K/Volt 21 range de luxe 12A AC/DC **£29.95**
360TR 100K/Volt 23 range plus hfe cvker and AC/DC 10 amps **£34.95**

FREQUENCY COUNTERS

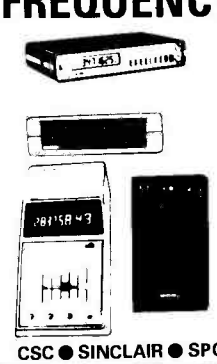Portable and Bench LCD and LED Counters up to 600mHZ. Prices include batteries and leads.



HAND HELD (UK post etc 85p)

PFM200 20HZ to 200mHZ 8 Digit LED **£52.27**
MAX50 100HZ to 50mHZ 6 Digit LED **£61.00**
MAX550 30KHZ to 550mHZ 6 Digit LED **£106.00**

BENCH PORTABLES (UK c/p £1)

MAX100 8 digit LED 5HZ to 100mHZ **£89.00**
TF200 8 Digit LCD 10HZ to 200mHZ **£166.75**
7010A 9 Digit LED 10HZ to 600mHZ **£169.00**
200SPC 6 Digit 100mHZ LED built into 5.5mHZ Pulse Generator 0.002HZ to **£437.00**
TP600 600mHZ Pre-Scaler for TF200 **£43.13**
TF040 8 Digit LCD 60MHz **£126.50**

CSC ● SINCLAIR ● SPC ● OPTO ELECTRONICS

SOLDERLESS BREADBOARD AND KITS

EXP350 **£3.45.** EXP650 **£3.95.**
EXP300 **£5.95.** EXP600 **£6.50.**
KITS
PB6 **£9.95.** PB100 **£12.95**
PB101 **£17.95.**

(UK c/p EXPs **30p.** Kits 55p)

MINI DRILLS AND KITS

(9–12 Volt 1/8" chucks)

Small Drill plus 3 collets **£7.25**
Medium Drill plus 3 collets **£10.50**
Small Drill plus 20 tools **£14.95**
Medium Drill plus 20 tools **£17.95**
Mains Drill **£13.95**
Mains Drill plus 20 tools **£21.50**

CHOOSE FROM UK's LARGEST SELECTION

Stockists of electronic equipment, speakers/kits, PA equipment plus huge range of accessories ● UK carriage/packing as indicated ● Export — prices on request
● All prices correct at **1.2.81** E & OE ● All prices include VAT


AUDIO ELECTRONICS Cubegate Limited
301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TELEPHONE 01-724 3564

OPEN SIX DAYS A WEEK

FREE CATALOGUE!
Send large SAE (17½p UK) Schools, Companies, etc. free on request.

NEXT MONTH

electronics today INTERNATIONAL

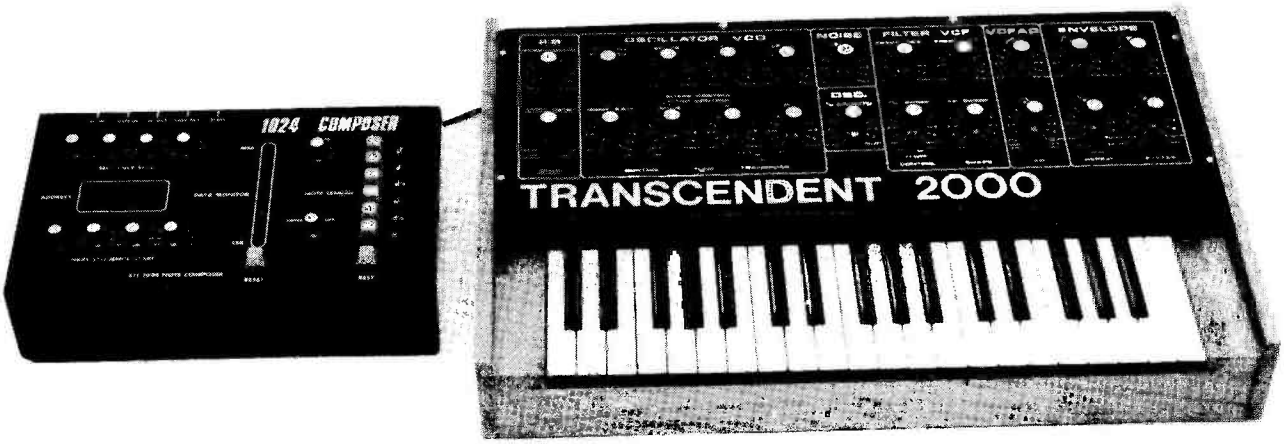

1024 COMPOSER

This machine will plug into the back of your synthesiser and allow sequences of up to 1024 notes to be played automatically. This Powertran design provides complete control of the starting and finishing points of the sequence, so several shorter tunes may be stored in the memory simultaneously. Both pitch and note length are fully programmable and rests may also be entered.

IR REMOTE CONTROL

As promised last month, we present a five-channel infra-red remote control system which will interface with last month's Noiseless Power Switch. The unit has three latching channels (ie push-on, push-off), two non-latching channels, and a range of up to 30 feet. Full constructional details of both the transmitter and receiver will be given.

SOLDERING IRON

A DIY design for a thermostatically-controlled soldering iron that is a must for any serious constructor. If you've ever cursed your unwieldy welding device, you'll be glad to know that with our tiny version your fingers are only 1½" from the bit for precision control. The iron runs from a switched-mode power supply at only 3 V, so it's completely safe for soldering CMOS — with a continuous temperature range up to 500°C, built-in light, interchangeable tips and a price one-fifth of a commercial equivalent, you can't afford *not* to build one.

TOUCH DIMMER

This project makes light work of lamp dimming. Based on the S566B IC, it provides touch control of brightness and a memory that turns the light on at a pre-determined level. The big difference with this design is that it can be used with the IR remote control and still retain all the normal functions. The remote control unit can operate two of these dimmers.

POWER SWITCH


For those of you who don't need the low noise and high current capability of the Noiseless Power Switch, we're publishing a cheap power switch that will handle a current of 5 A and interface with the IR remote control. Up to three of these switches can be controlled by the IR transmitter.

SONIC HOLOGRAPHY

Surround-sound in your living room! No, your eyes don't deceive you — the speakers are in front of you. No, your ears don't deceive you — sounds to the left of you, to the right, behind and above you. Find out more in next month's ETI.

Articles described here are in an advanced state of preparation. However, circumstances may dictate changes to the final contents.

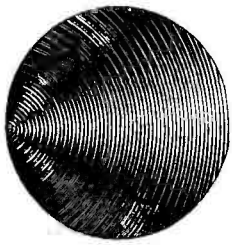LOOK OUT FOR THE MAY ISSUE ON SALE APRIL 3rd




B.K. ELECTRONICS

thandar STOCKIST

thandar STOCKIST


A SOUND CHOICE

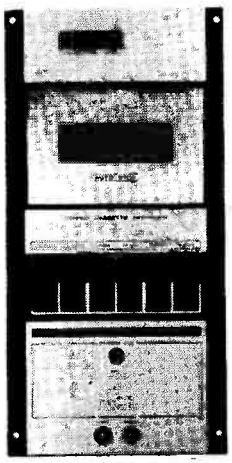★ PROMPT DELIVERY ★ PRICES INCLUDE V.A.T. ★ AMPLE STOCKS
A PERSONAL SERVICE FROM A SMALL EXPANDING COMPANY




6 piano type keys

STEREO CASSETTE TAPE DECK MODULE. Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.
Features: Three digit tape counter. Auto-stop. Six piano type keys, record,rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. **Input sensitivity:** 100mV to 2V. **Input Impedance:** 68K. **Output level:** 400mV to both left and right hand channels. **Output Impedance:** 10K. **Signal to noise ratio:** 45dB. **Wow and flutter:** 0.1%. **Power Supply requirements:** 18V DC at 300mA. **Connections:** The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). **Dimensions:** Top panel 5½in x 11¼in. Clearance required under top panel 2¼in. Supplied complete with circuit diagram and connecting diagram.
Price £25.70 + £2.50 postage and packing. Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) **£3.00.**

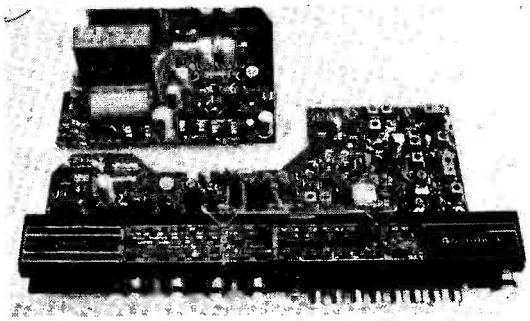

GEC AM/FM STEREO TUNER AMPLIFIER CHASSIS. Originally designed for installation into a music centre. Supplied as two separate built and tested units which are easily wired together. **Note:** Circuit diagram and interconnecting wiring diagrams supplied. **Rotary Controls:** Tuning, on/off volume, balance, treble, bass. **Push-button controls:** Mono, Tape, Disc., AFC, FM (VHF), LW, MW, SW. **Power Output:** 7 watts RMS per channel, at better than 2% THD into 8 ohms. 10 watts speech and music. **Frequency Response:** 60Hz-20kHz within ±3dB. **Tape Sensitivity:** Output — typically 150 mV. Input — 300 mV for rated output. **Disc Sensitivity:** 100mV (ceramic cartridge). **Radio:** FM (VHF), 87.5MHz — 108MHz. Long wave 145kHz — 108kHz. Medium wave. 520kHz — 1620kHz. Short wave. 5.8MHz — 16MHz. **Size:** Tuner — 2¾in x 15in x 7½ in approx. Power amplifier — 2in x 7½in x 4½in approx. 240V AC operation. Supplied complete with fuses, knobs and pushbuttons, and LED stereo beacon indicator. **Price £23.50** plus £2.50 postage and packing.

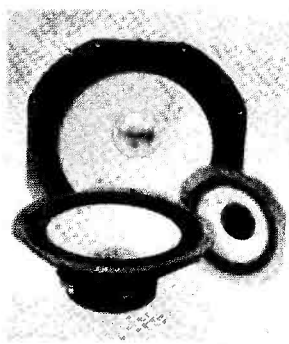


NEW RANGE QUALITY POWER LOUDSPEAKERS (15", 12" and 8"). These loudspeakers are ideal for both hi-fi and disco applications. Both the 12" and 15" units have heavy duty die-cast chassis and aluminium centre domes. All three units have white speaker cones and are fitted with attractive cast aluminium (ground finish) fixing escutcheons.
Specification and Price:—


15" 100 watt. Impedance 8ohm 59 oz. magnet, 2" aluminium voice coil. Resonant Frequency 20Hz. Frequency Response to 2.5KHz. Sensitivity 97dB. **Price £32 each.** £2.50 Packing and Carriage each.

12" 100 watt. Impedance 8 ohm. 50 oz. magnet. 2" aluminium voice coil. Resonant Frequency 25Hz. Frequency Response to 4KHz. Sensitivity 95dB. **Price £23.70 each.** £2.50 Packing and Carriage each.

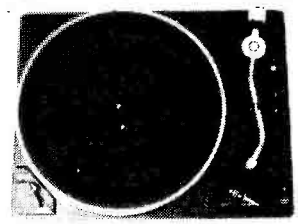8" 50 watt. Impedance 8 ohm. 20 oz. magnet. 1" aluminium voice coil. Resonant Frequency 40Hz. Frequency Response to 6KHz. Sensitivity 92dB. **Price £8.90 each.** £1.25 Packing and Carriage each.



JVC TURNTABLE. JVC Turntable supplied complete with an Audio Technica AT10 stereo magnetic cartridge.
★ 'S' shaped tone arm.
★ Belt driven.
★ Full size 12in platter.
★ Precision calibrated counterbalance weight (0-3 grms.)
★ Anti-skate (bias) device. Nylon thread weight.
★ Damped cueing lever.
★ 240V AC operation, (50Hz).
★ Cut-out template supplied.
Size — 12¾in x 15¾in (approx).
Price £28.50 plus £2.50 postage and packing.

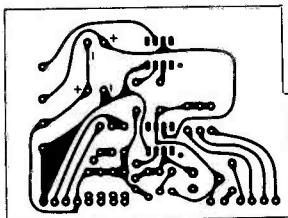


COPPER LAMINATED PRINTED CIRCUIT BOARD (single sided). Paxoline based type. Size 15½" x 12¼". Brand new. Still shiny and bright. **£1.25** per sheet. Post free.


PIEZO ELECTRIC TWEETERS — MOTOROLA
Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover **is not** required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



Type 'A'

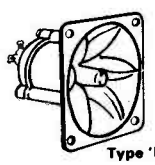

Type 'B'

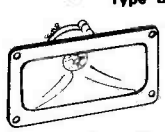


Type 'C' Type 'D'

Type 'A' 3in round with removable wire mesh. Ideal for bookshelf hi-fi speakers. **Price** (Type 'A') **£3.45 each.**
Type 'B' 3½in super horn. For general purpose speakers disco and PA systems, etc. **Price £4.35 each.**
Type 'C' 2in x 5in wide dispersion horn. For hi-fi systems and quality disco etc. **Price £5.45 each.**
Type 'D' 2in x 6in wide dispersion horn. Frequency response extending down to mid-range (2000 c/s) suitable for hi-fi systems and quality disco. **Price £6.90 each.**
Post and Packing, all types, 15p each (or SAE for Piezo leaflets).

FIRE ALARM CENTRAL CONTROL UNIT (S.T.C.)
Ideal for Fire or Burglar Alarm Systems

★ Responds to normally open or closed switches (or smoke detectors etc.)
★ Complete with an internal EXIDE lead acid accumulator (dry charged) as a back-up for mains failure. This is trickle charged
★ 6v-2 amp output for Fire/Burglar alarm, etc.
★ Re-set button for silencing Fire/Burglar alarm.
★ Internal buzzer which sounds if re-set button if pressed until initiating switch is cleared.
★ Wall mounting, complete with red case, approx. 11" x 7½" x 4".
★ 240v AC operation.
Price £18.50 + £3 postage and packing.

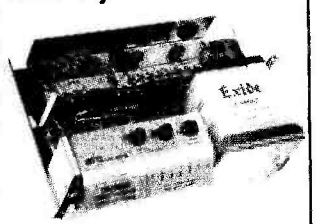

LOUDSPEAKER
High quality full range 8" loudspeaker. 15 watts RMS 8 ohm. Rolled surround with aluminium centre dome.
Price £3.75 each + £1. Postage and Packing each.



B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by **prior** appointment, please phone 0702-527572.

VISA

KIT REVIEW

There are many adverts about for build-it-yourself electronic kits — everything from door chimes to hi-fi. But do they represent value for money? This new series finds out for you.



This is the first in a new series of articles, designed to look in detail at some of the DIY kits available on the market, particularly those which yield a useful item for the home or car when completed.


We will be paying close attention to ease of construction — which includes a consideration of the clarity of the instruction leaflets provided. Anyone reading this who produces a kit which they feel might be suitable, is asked to ring the editor at our office number and we'll take if from there.

Taking A Dim View!


For our first month we're having a look at TK Electronic's remote controlled light dimmer, which sells for around £20. The kit comprises two separate units, a touch operated light switch and an IR (infra-red) control box. The dimmer can be constructed initially with straightforward touch operation, and the IR option added later.

The dimmer itself uses the 566 IC, which allows for a neat little circuit with 'memory' capability. Turn on the light by touching the plate and it will assume the level of brightness you last set it at. Holding a finger on the plate will cause the level to cycle between maximum and minimum brightness.

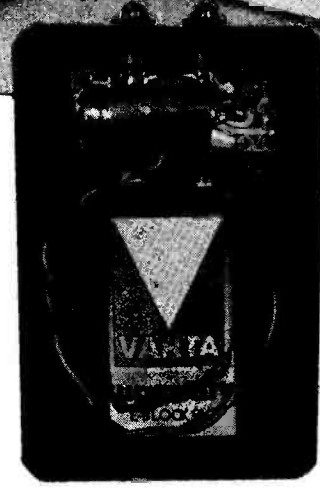
To add the IR facility an external photodiode is fitted to the mounting plate (see photo). This then produces full operation from the hand-held unit. The latter is little more than a multivibrator and two IR LEDs. A neat little black plastic box is provided, predrilled, for mounting the controls.



How to connect photodiode D8 to P.C.B.

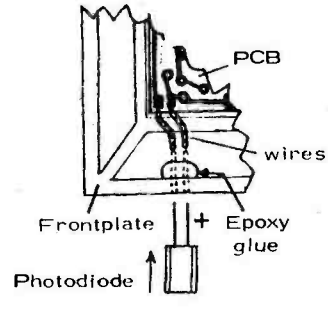

P.C.B. LAYOUT

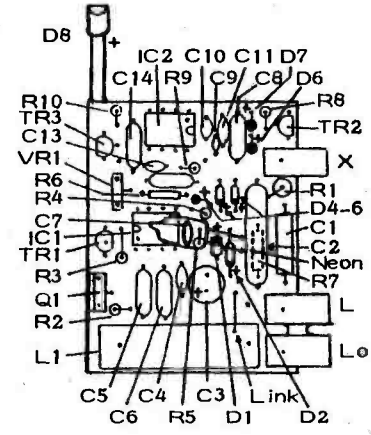

Above left: the assembled transmitter. Note the shaky PCB fittings. Above and right: examples from the well-explained notes. Diagrams are basic, but well thought out. Instructions are generally adequate for the constructor with a little experience.

Constructive Thinking

The instructions provided with the kit are well explained, but could be better presented. A separate sheet is included with details of different types of electronic components and some helpful hints on soldering.

These serve as a general construction guide, the detailed building notes for a specific project being pretty sparse. This, together with the very high component density found on the PCB, makes me think that an absolute beginner would find the dimmer a difficult task. As this is a mains circuit, best make a start in electronics elsewhere.

Having said that, anyone who has built a few magazine projects would find the kit *relatively* simple to put together, although care will still be needed in soldering up the PCB, however experienced you may be!

Assembly of the hand controller is very simple indeed, as there are only some eight components involved! The push button is PCB mounted, as are the LEDs. One point about the controller that I did not like was the fact that the LED leads are used to secure the PCB into the box. This means that every time the push button is operated, the leads are stressed unnecessarily. Also the box is a fraction too narrow to admit a PP3 with a battery clip fitted. Thus, it has to be laid along the case which means in turn that it is effectively jammed against the PCB — again putting stress upon the LED leads!

Built And Working

Assembly took about two hours, including the time required to sort out the components initially. No "sillies" manifested themselves from the instructions and the kit was complete as supplied.

Once built the unit functioned first time and the notes provided on installation and use were clear and concise. Take some care with the choice of wiring box you use for mounting the kit, though, as it is fairly deep and will protrude some 35 mm behind the front plate when fitted.

In use the dimmer functioned perfectly at all times, with the photodiode having a good wide acceptance angle. Range is about 30 ft — more than most living rooms I would have thought.

Conclusions


Overall a good design. The circuit is neat and well thought out and the PCB design quite a feat of miniaturisation! However, this does tend to mean that the kit is best suited to someone with some previous constructional experience.


The unit represents reasonable value for money and can be confidently recommended.

RON HARRIS

BUYLINES

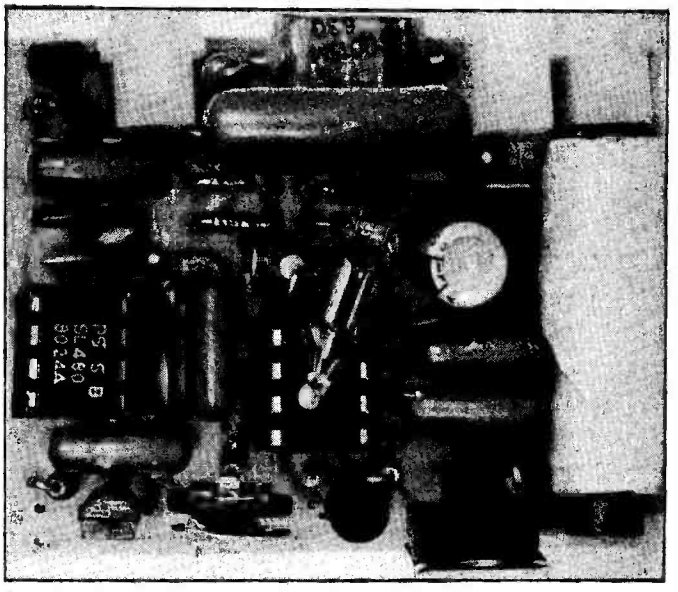TDR300K Touch Dimmer Kit £14.30 + VAT (+ 40p P&P per order), MK6 Infra-red Transmitter £4.20 + VAT. TK Electronics, 11 Boston Road, London W7 3SJ. Tel: 01-579 9794.



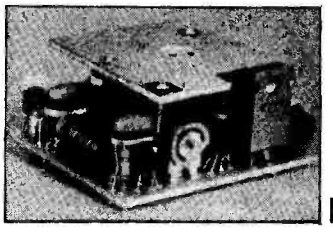

Above: the main PCB assembled — note the bulb fitting. This is to ensure that it lines up with the hole in the touch plate, shown fitted (right photo). The board is somewhat crowded in places and care needs to be exercised when soldering.

ETI

Conquer the chip.

Be it a career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.

MASTER ELECTRONICS

LEARN THE PRACTICAL WAY BY SEEING AND DOING

- Building an oscilloscope. ● Recognition of components.
- Understanding circuit diagrams. ● Handling all types Solid State 'Chips'.
- Carry out over 40 experiments on basic circuits and on digital electronics.
- Testing and servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.



MASTER COMPUTERS

LEARN HOW TO REALLY UNDERSTAND COMPUTERS, HOW THEY WORK – THEIR 'LANGUAGE' AND HOW TO DO PROGRAMS.

- Complete Home Study library. ● Special educational Mini-Computer supplied ready for use. ● Self Test program exercise.
- Services of skilled tutor available.

MASTER THE REST

- Radio Amateurs Licence. ● Logic/Digital techniques.
- Examination courses (City & Guilds etc.) in electronics.
- Semi-conductor technology.
- Kits for Signal Generators – Digital Meters etc.

FREE

Please send your FREE brochure without obligation to:

Name .....

Address .....

.....

BLOCK CAPS PLEASE

I am interested in –

PRACTICAL ELECTRONICS .....

COMPUTER TECHNOLOGY .....

OTHER SUBJECTS .....
(please state your interest)

.....


.....

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL


4 CLEVELAND ROAD, JERSEY, CHANNEL ISLANDS. ETI 4/813

You can't beat The System.

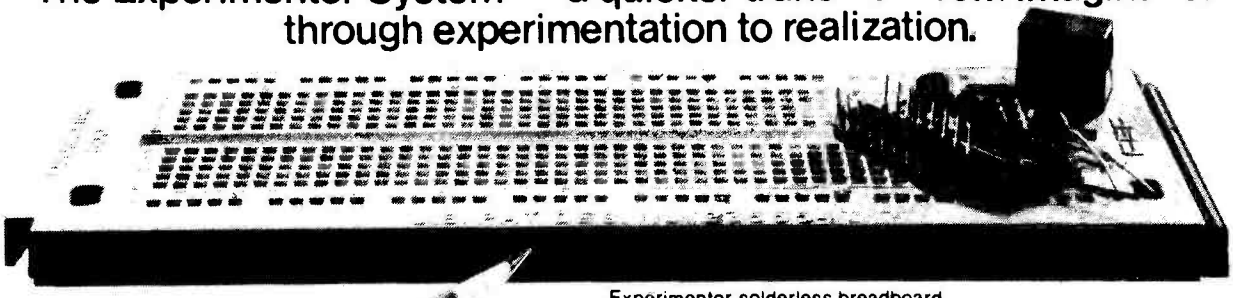
The Experimentor System™ — a quicker transition from imagination through experimentation to realization.



Experimentor solderless breadboard.

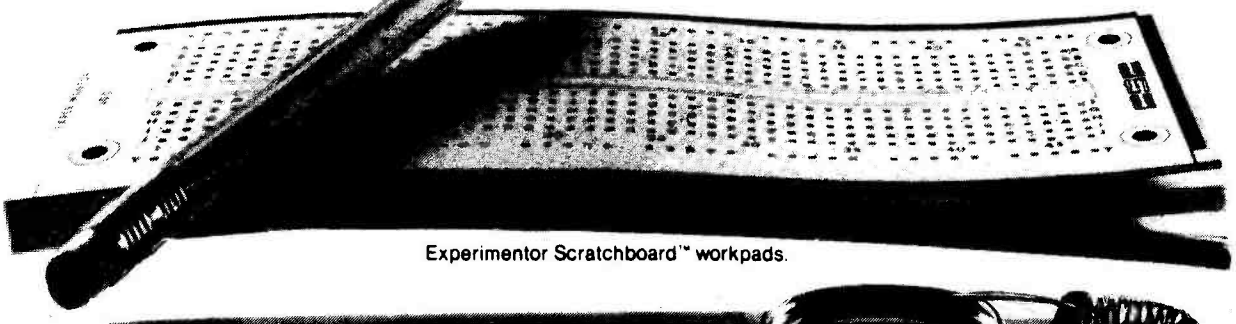

Experimentor Scratchboard™ workpads.

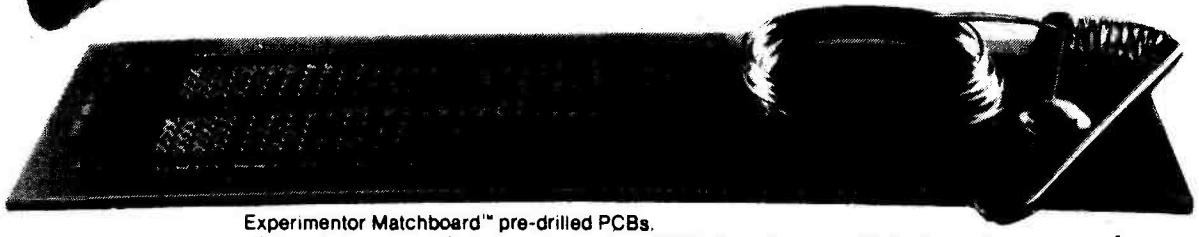

Experimentor Matchboard™ pre-drilled PCBs.

When you have a circuit idea that you want to make happen, we have a system to make it happen quicker and easier than ever before: The Experimentor System.

You already know how big a help our Experimentor solderless breadboards can be. Now we've taken our good idea two steps further.

We've added Experimentor Scratchboard workpads, with our breadboard hole-and-connection pattern printed in light blue ink. To let you sketch up a layout you already have working so you can reproduce it later.

With Experimentor Matchboard you can go from breadboard to the finished product nonstop! We've matched our breadboard pattern again, this time on a printed circuit board, finished and ready to build on. All for about £1.32.

There's even a letter-and-number index for each hole, so you can move from breadboard (where they're moulded) to Scratchboard™ (where they're printed) to Matchboard™ (where they're silkscreened onto the component side) and always know where you are.

When you want to save time and energy, you can't beat The Experimentor System.

1. EXP-300PC, which includes one item: A Matchboard pre-drilled PCB **£1.20**	**2.** EXP-302, which includes three items: Three 50-sheet Scratchboard workpads **£1.50**	**3.** EXP-303, which includes three items: Two Matchboards and an EXP-300 solderless breadboard **£7.60**	**4.** EXP-304, which includes four items: Two Matchboards, an EXP-300 breadboard and a Scratchboard workpad **£8.70**

GLOBAL SPECIALTIES CORPORATION

GSC

G.S.C. (UK) Limited
Dept. 9W Unit 1, Shire Hill Industrial Estate
Saffron Walden, Essex CB11 3AQ
Telephone: Saffron Walden (0799) 21682
Telex: 817477

GLOBAL SPECIALTIES CORPORATION, DEPT. 9W
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex.

Name _____

Address _____

Inc P&P and 15% VAT

1.EXP 300PC **£2.25**	Qnty Reqd.	2.EXP 302 **£2.58**	Qnty Reqd.
3. EXP 303 **£9.90**	Qnty Reqd.	4. EXP 304 **£11.15**	Qnty Reqd.

FREE Catalogue tick box☐
I enclose cheque/ PO for
£ _____

Phone your order with Access, Barclaycard or American Express

Card No. _____ Expiry date _____

New from Casio, world leaders in creative technology combined with high quality and reliability

JOIN THE KEYBOARD REVOLUTION!

For everyone music has its own meaning. It is to capture the true values of music that Casio have spent years of research and development efforts. They bring to life beautiful sound experiences never before available. A new generation of tone-true electronic sounds of vivid realism — the composition of a fresh musical system.

By closely analyzing the natural sound variations in the waves and pitches of different instruments, Casio have been able to trace the characteristics peculiar to each traditional instrument. Pitch, timbre and harmonics have been measured, digitalised and stored in electronic chip memory for faithful and exciting reproduction of the clarity and beauty of the originals.

CASIOTONE 401



RRP £345

ONLY £295*


Full polyphonic 8-note playing of **14 instruments and sounds** over 4 octaves.
Rhythm accompaniment. 16 different rhythms with full-in **auto-rhythm.**
Casio Auto Chord. Allows one finger accompaniment. Just press a key with a single finger and play major, minor and seventh chords, with bass accompaniment, automatically. Combines with auto-rhythm for professional sounds.
Vibrato, Delayed vibrato, sustain and hold are incorporated in the at-a-glance, simple to use operational panel. Pitch control makes group tuning easy. Compact 4⅝ × 31⅜ × 12⅞ inches with integral amplifier and speaker. The light weight (28.2lb) allows playing anywhere there is an A.C. socket. **Stand £39.**

CASIOTONE 301

The same size and basic specification as the 401 above, the 301 does not have Casio Auto Chord or built-in sustain and hold facilities. There are 8 rhythm voices with a variation on each. Weight 27lbs.

£245*

CASIOTONE MT-30

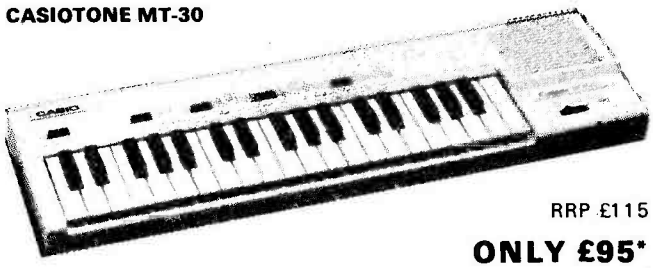

RRP £115

ONLY £95*


Full polyphonic playing of **22 instruments and sounds** over 3 octaves. 4-position **sound memory** lets you switch between pre-selected sounds without pause. Built-in **vibrato and sustain functions** greatly enhance the overall musical effect. **Compact** 2⅜ × 22¾ × 6½ inches, with built-in amplifier and loudspeaker. Battery/mains power source and light weight (6lb) allows playing anywhere.

CASIOTONE 201 and M-10

Please telephone for availability.
201. Mains version of the MT-30. 29 instruments over 4 octaves **£245***

M-10. 4 instruments over 2½ octaves. Battery/mains. **£69***

CASIO BQ-1100 BIOLATOR/ WATCH

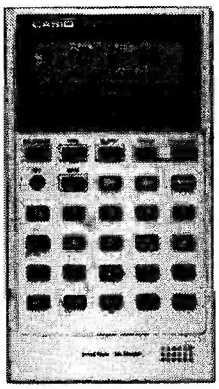

Clock, calendar, 2 alarms, countdown alarm stopwatch, time memory, three date memories, biorhythm and date calculations, calculator
Clock. Hours, minutes, seconds, am/pm. Day/date.
Universal calendar. Pre-programmed 1901 to 2099. Day, date, month and year display.
Alarm. Two separate alarms. 24-hour system.
Countdown alarm. 1/10 second to 24 hours, or
Stopwatch 1/10 second to 24 hours. Net times, or
Time memory. Dual time facility. 24-hour system.
Calculator. 8 digits. Full memory. Sq roots, %. Date calculations. Any monthly calendar from 1901 to 2099 can be displayed and utilised.
Biorhythm calculations. Forecast your physical, emotional and intellectual performance potential. Chart your peak, ebb and critical days and reschedule to avoid mistakes. Two silver oxide batteries last approx 1 year.
Dims: ¼ x 2.7/16 x 4⅜ inches. Leatherette wallet.

ALL THIS FOR ONLY £14.95*


MG-880 SPACE GAME/CALCULATOR

Our best selling calculator. Thousands sold! An action packed speed game that will give you hours of skilful entertainment and chair-gripping excitement. Also an 11-note melody calculator with full memory, %.

KEEP A DATE WITH CASIO

You always wanted a musical calculator with date memories and date/time alarms — HERE IT IS!


UC-365 UNIVERSAL CALENDAR

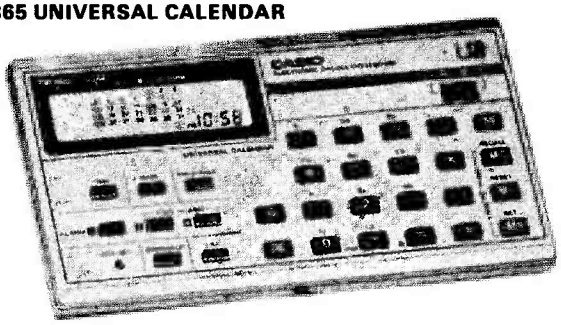

Clock, universal calendar, date memories, daily alarm, 2 daily or date/time alarms, hourly chimes, stopwatch, countdown alarm, time memory, calculator.
Clock display: Hours, minutes, seconds, am/pm, or hours, minutes, full calendar.
Calendar: Pre-programmed from 1901 to 2099. Full month display.
Date memories: Any day or days pre-settable within 12-month period. (Birthdays, etc.)
Alarms: Alarm 1 — Daily alarm. Alarm 2 & 3 — Daily alarms or time alarms on pre-set dates. (Pre-programmed melodies or electronic buzzer.)
Stopwatch: 1/10 second to 24 hours; net, lap and first and second place. Or
Countdown alarm: 1/10 second steps, settable in minutes up to 24 hours. Or
Time memory: 24 hour system. The time of any other zone can be stored.
Calculator: Optional musical keys, full memory and percentage.
Two silver oxide batteries last approx. 1 year. RRP £22.95
¼ × 4½ × 2½ inches. Leatherette wallet with window **£19.95***

UC-360. Card sized version of above. 7/32 × 3⅜ × 2⅜ inches **£19.95***
UC-3000. Office desk version. Angled display. 1¾ × 4 × 6¼ inches **£27.95***

CASIO'S AMAZING NEW FX-3500P

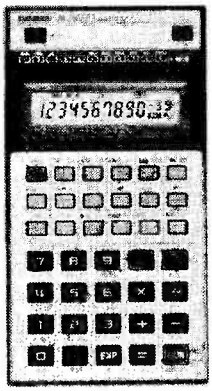

Programmable. Non-volatile memories and stores. Statistical regression and integrals.

38 functional (non-volatile) steps. 2 programme storage capability. Unconditional and conditional jumps. 7 (non-volatile) memories; one independent, 6 constant memories. 18 pairs of parentheses, nestable in 6 levels.

61 built-in functions, including: Integrals (Simpson's rule). Linear regression, logarithmic regression, exponential regression and power regression.

Hyperbolics, sexagesimal and co-ordinates conversions. 10 digit mantissa or 10+2 exponent. Two silver oxide batteries give approximately 1,000 hours continuous use with power-saving automatic cut-off, with data and memory protection.

Dims: 9/32 x 2⅞ x 5¼ inches. Supplied with leatherette wallet.

ALL THIS FOR ONLY £22.95*

FX-180P. Hand held version without hyperbolics. 2 x AA batteries. ¾ × 3 × 5⅞ **£19.95***
FX-2700P. As FX3500P but 8+2, without integrals, regression. 1 programme **£19.95***
FX-8100. Scientific with clock, calendar, alarm, chimes, stopwatch, etc. **£24.95***

CASIO'S BEST SELLING WATCHES



AA81



M1200



W150B

LCS ANALOGUE/DIGITAL ALARM CHRONOGRAPH with countdown alarm.
AA-81 chrome, s/s bracelet **£29.95. AA-81G.** Gold plated **£49.95. AA-82.** All s/s **£39.95.**
12 MELODY ALARM CHRONOGRAPHS with countdown alarm. **M-12** resin case/strap **£24.95. M1200** all stainless steel **£29.95.**
100 METRE WATER RESISTANT Alarm chronographs with countdown alarm. **W100.** Resin case/strap **£19.95. W150C** Stainless steel case/resin strap **£25.95. W150B** Stainless steel case/bracelet **£32.50.**

Send 20p (postage) for our illustrated catalogue of Casio and Seiko.

***PRICES** We will beat any lower advertised price by 5% providing we still make a profit! Just send details and your remittance for the lower amount. **Prices include VAT and P&P.**

Price includes VAT, P&P. Send your company order, cheque, P.O. or phone your ACCESS or BARCLAYCARD number to:

TEMPUS

Dept. ETI, FREEPOST, 164-167 East Road, Cambridge CB1 1DB. Tel: 0223 312866

VISUAL COMPLEX SOUND ANALYSER

This unusual unit continuously analyses the amplitude/frequency content of complex audio signals and presents the results on a multi- colour 60-LED display. Design by Ray Marston. Development by Steve Ramsahadeo.



This very unusual project makes an excellent multi-colour visual display accessory for use with any audio-output system. The unit continuously analyses the complex sound content of the audio signal and presents the results of the analysis, in three colours, on six 10-LED bar displays arranged as a diamond with a diagonal. Naturally, in the presence of music, etc., the displays bounce and sway in sympathy with the analysed contents of the audio signal and present an attractive moving display.

The Visual Complex Sound Analyser display unit is mains powered and receives its audio input signal from the output (speaker) of the system under test. The audio signal is actually analysed in the form of three overlapping audio bands, having nominal 3 dB points of 20 Hz — 120 Hz (red display), 250 Hz — 2 kHz (yellow display), and 2 kHz — 7 kHz (green display). The upper three 10-LED bars each move in 3 dB steps and display the instantaneous signal amplitudes of the three audio bands. The lower three 10-LED bars move in linear steps and display the instantaneous dominant frequencies of the three bands.

The Display

This is a project where the skilled constructor might like to experiment with alternative display-pattern layouts. Our development prototype unit was originally built up on Veroboard and had a display in which the six 10-LED bars were arranged as three parallel 20-LED lines, each representing a specific colour-coded frequency band, with the upper half of the display showing amplitude and the lower half showing instantaneous dominant frequencies. On this unit, the central 'reference' bar (four LEDs) of the display represents zero amplitude/frequency, so that each of the three display lines appears to expand and contract from its central point.

On the final PCB version of the unit we've changed the display to the form shown in the photographs. Here, the display is again in the form of three 20-LED lines, each representing a specific colour-coded frequency band, with the upper half of the display showing amplitudes and the lower half showing dominant frequencies, but in this case the two outer lines of the display are angled to form a diamond shape. The major difference of this display is that the individual 10-LED bars are so arranged that the entire display appears to rotate left or right in sympathy with the music, rather than simply expand or contract. Thus, on the low-frequency (red) band the two 10-LED bars expand downwards with increasing amplitude/frequency, whereas on the high-frequency (green) band the two 10-LED bars expand upwards under the same condition; the central (yellow) band expands in a downwards direction. If you've got any better ideas, feel free to do your own thing.

Construction

The entire circuit, with the exception of mains transformer T1 and pot RV1, is built up on a single large (12 x 8 inches) PCB. On our prototype we've coated the entire top surface of the PCB with navy-blue flock paper, to enhance the visual appeal of the unit: if you wish to do the same, proceed as follows.

(1). The PCB uses a fairly large number of bridging links on the top side of the PCB, as well as several long links on the underside; these underside links are facilitated by Veropins (marked on the overlay as A, B, C, etc) pushed through the board from the top side. The underside links are completed by joining A to A, B to B, etc. To start the construction, drill all holes to accommodate the wire links and the Veropins, then insert the links and pins from the component (upper) side of the PCB and solder into place.

(2). Now coat the entire upper surface of the PCB and the lower side of the flock paper with cow gum, allow ten minutes to set and then press the paper evenly into place and trim the outer edges.

(3). Next, drill all remaining holes in the PCB and then proceed with the construction in the normal way, taking extra care to observe the polarities of all semiconductor devices (particularly IC17 and IC18) and electrolytic capacitors. Take special care to check the functioning/polarity of all LEDs before soldering them into place and note that the LEDs *must* be of the colours

shown in the circuit diagram. Don't forget to connect the (several) links on the underside of the PCB.

When the construction is complete, double-check all wiring, connect the unit to RV1 and T1 and then switch on. Initially, only the central 4-LED 'bar' should illuminate. Now connect the unit to an audio (music) source and check that the unit is functioning by adjusting RV1 to give a display that behaves in the manner already described.

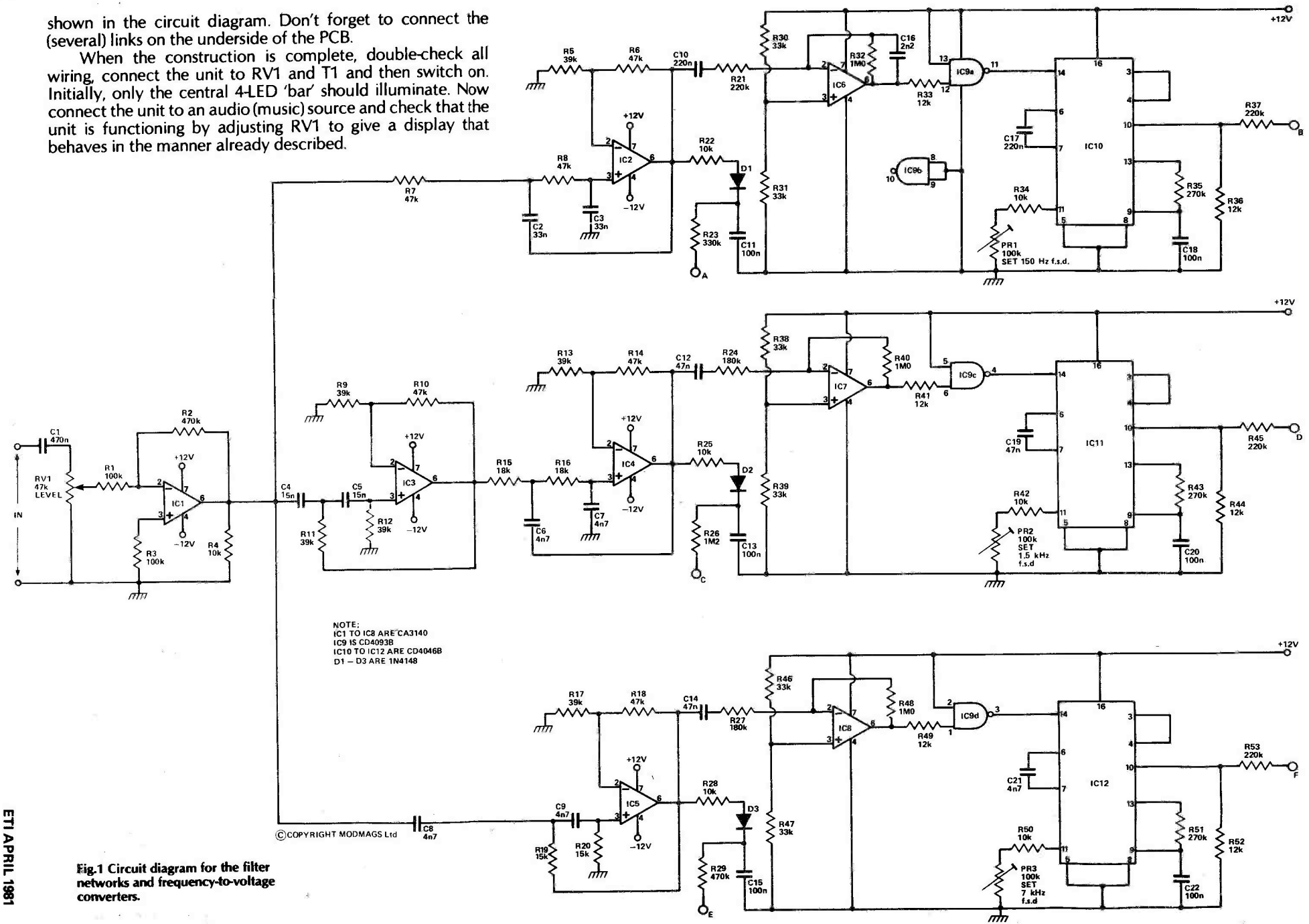


Fig.1 Circuit diagram for the filter networks and frequency-to-voltage converters.

HOW IT WORKS

The audio input signal is fed, after a simple 'level control' (RV1-IC1), to a multiple filter network, which divides the complex input signal into three distinct (but overlapping) bands. The lowest band has an upper 3 dB cut-off frequency of 120 Hz and operates in the low-pass mode (IC2). The middle band operates in the band-pass mode (using high-pass filter IC3 and low-pass filter IC4) and has lower and upper cut-off points of 250 Hz and 2 kHz respectively. The upper band operates in the high-pass mode (IC5) and has a lower cut-off point of 2 kHz.

The output of each filter is peak-detected and filtered by a rapid-charge slow-discharge network (R22-D1-C11-R23-R56, etc) and passes to the input of a 10-LED 'amplitude indication' display. These displays are based on LM3915 dot/bar drivers and give a log display in 10 3 dB steps: they are set, via pins 6-7, to read full scale at 1.2 V. The outputs of the rectifier networks are fed to the inputs of the LM3915 drivers via fixed potential divider networks (R23-R56, R26-R60, and R29-R64), the values of which have been calculated to compensate for differences in the gains of the three sets of filters.

Note that in the LM3915 circuits the ICs are powered from a 12 V supply, but the LED chains are driven from a 24 V supply. The ICs are wired to operate in the 'dot' mode (via pins 9 and 11), but the 10 LEDs in each chain are wired in series; consequently, the LEDs produce a 'bar' display with the LEDs that are on passing a common current. Thus, the LED current consumption is constant, irrespective of whether one or 10 LEDs are turned on.

The low-frequency level indicator (IC13) uses red LEDs, the mid-band indicator (IC15) uses yellow LEDs and the upper indicator (IC17) uses green LEDs. To give an equal brightness to all three colours, the LED drive current of each LM3915 is weighted by the resistor connected to pins 6-7. The red LEDs pass approximately 8 mA, the yellow pass 18 mA and the green pass 25 mA.

The output of each of the three audio filters is also fed to a frequency-to-voltage converter network, and the instantaneous frequency is subsequently displayed on another line of 10 LEDs by LM3914 linear drivers. These drivers are again operated in the dot mode with a bar display and are current-weighted.

Each frequency-to-voltage converter operates as follows. The output of each audio filter is amplified (by IC6, etc) and converted to a square wave by one of the IC9 Schmitt gates. The resulting square wave signal is fed to the input of a phase-locked loop (PLL) circuit (IC10, etc) and compared with an externally set reference frequency (set by C17-R34-PR2, etc). The PLL incorporates a phase comparator and a voltage-controlled oscillator (VCO). The output of the comparator is coupled to the input of the VCO via a simple filter network (R35-C18) and the VCO input voltage is made available, via an internal buffer, at pin 10. As the PLL tries to track the rapidly-shifting input signal, it generates a signal at pin 10 that is proportional to the instantaneous frequency of the input signal (0 V at zero frequency, 12 V at the reference frequency, etc). The output signal of each PLL circuit is fed to the input of its respective LM3914 display driver via a simple potential divider network (R37-R57, etc).

The total of six 10-LED displays are arranged in three pairs, each of a different colour and each displaying the instantaneous amplitude (upper LEDs) and frequency (lower LEDs) of a specified audio band. A bar of four red LEDs is mounted horizontally across the centre of the display, to enable the amplitude and frequency areas of each band to be readily distinguished.

The complete unit uses +24 V, +12 V and −12 V supply rails, each regulated by an IC.

The unit incorporates only three preset controls (PR1, PR2, PR3), which are used to set the full-scale reading of each frequency display (150 Hz, 1.5 kHz and 7 kHz). Figure 5 shows a simple circuit which can be used to generate suitable reference signals when initially calibrating the unit. The circuit is a basic astable, with its frequency determined by the C1-R2-R3-R4 values; the circuit can be easily built on a spare piece of Veroboard.

Fig.2 Block diagram of the complete circuit.


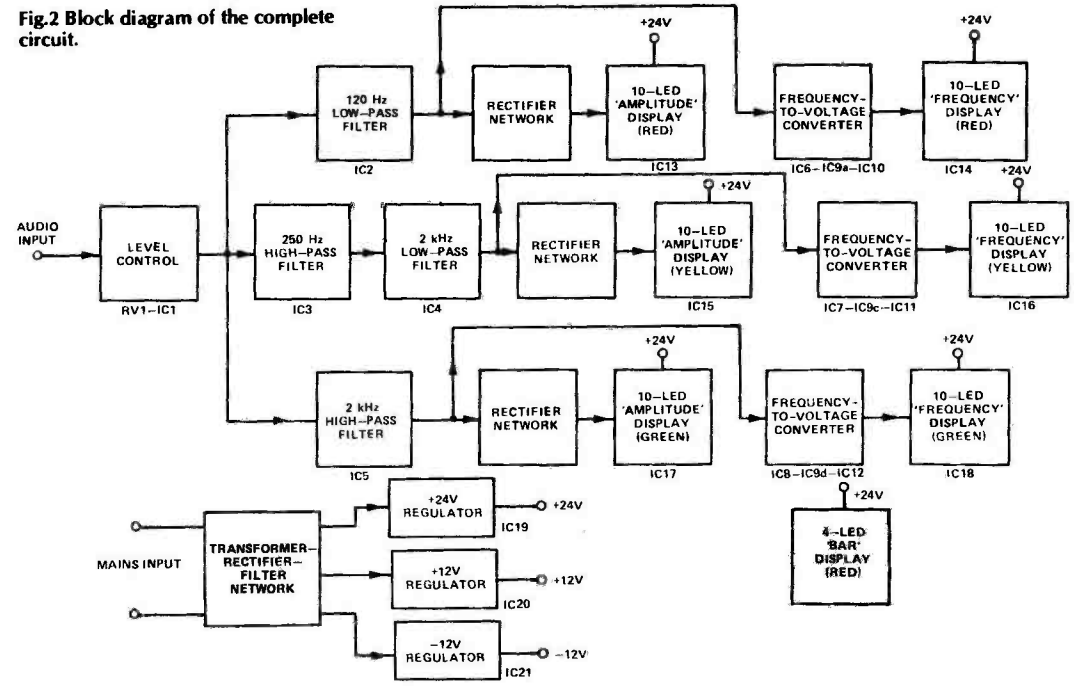


Fig.3 Circuit diagram of the power supply section.

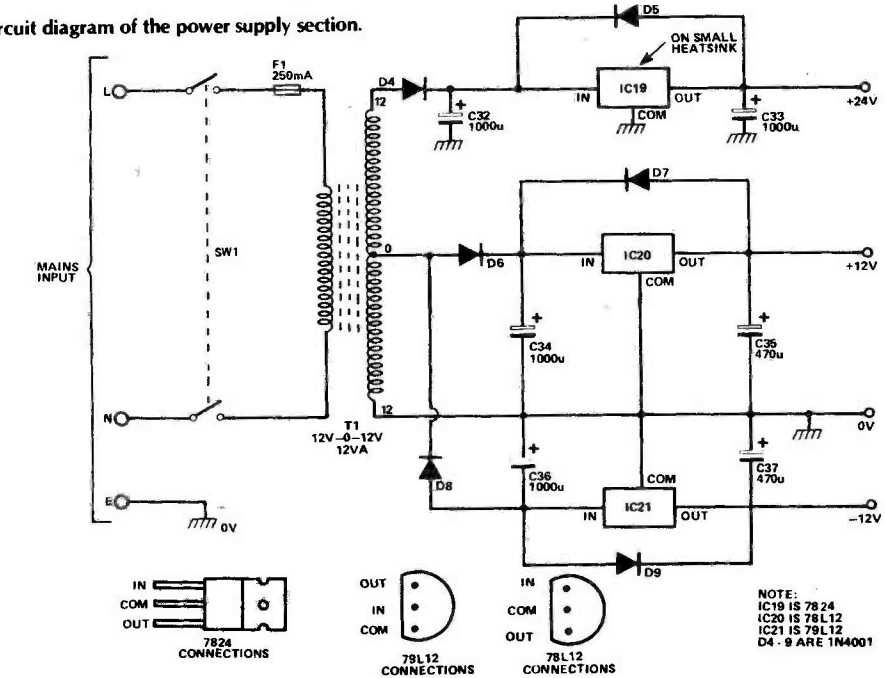

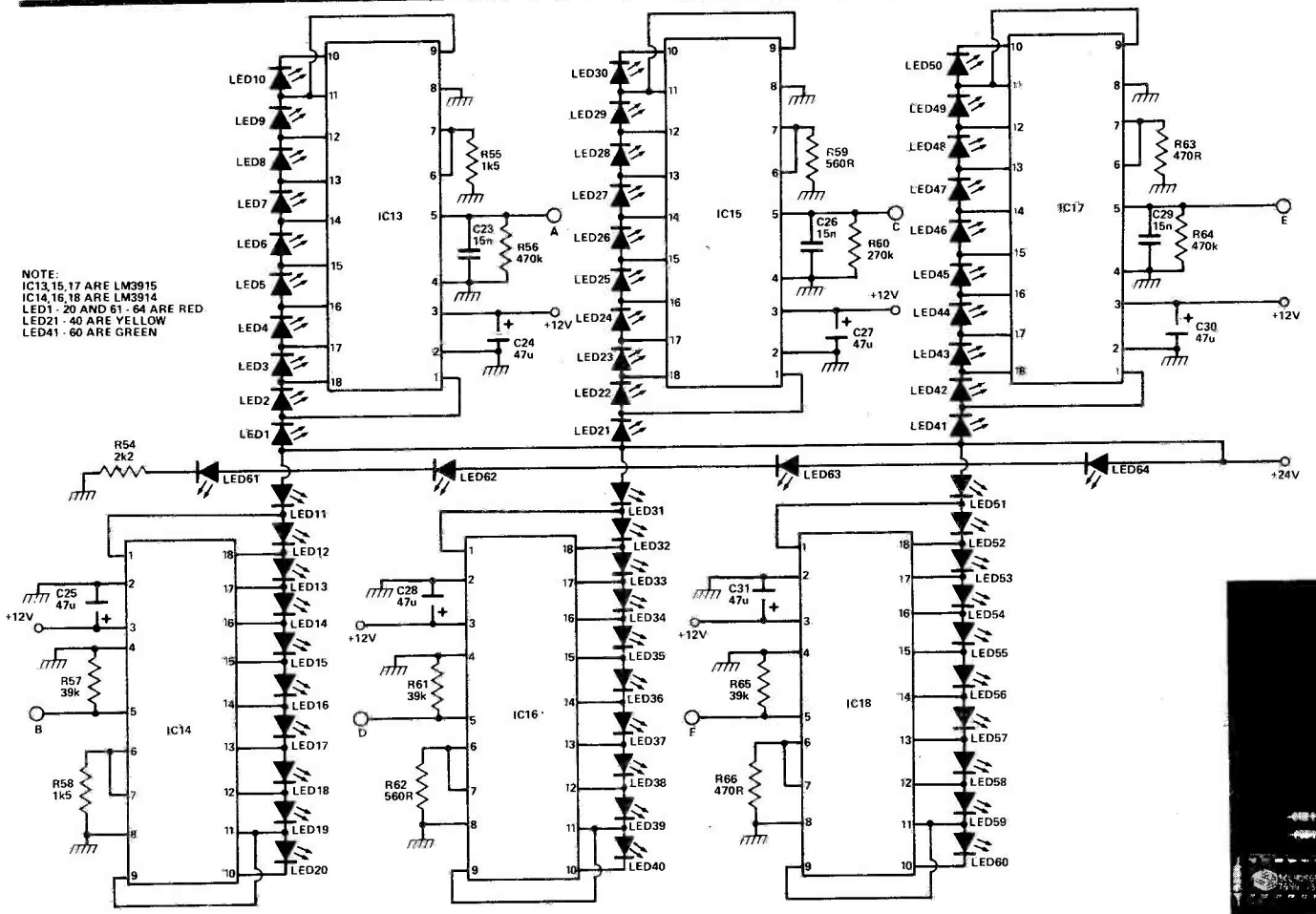


Fig.4 Circuit diagram of the display circuitry. The three sections at the top display the amplitude, and those below display the dominant frequency, in each of the three bands.

© COPYRIGHT MODMAGS Ltd

Finally, to correctly calibrate the frequency response of the completed unit, build the simple calibration oscillator (see Fig. 5) on a piece of Veroboard and then use it to set up the full-scale frequency levels of the three frequency bars with PR1, PR2 and PR3.


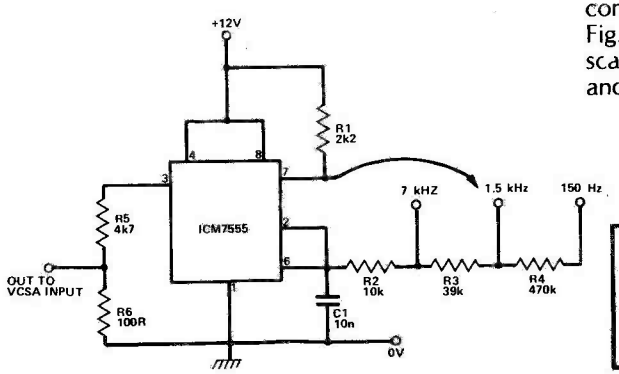


Fig.5 (left) This simple circuit will generate the three frequencies required to calibrate the frequency display.

BUYLINES

All components used in the V.C.S.A. are easily available. In case of difficulty the LM3914 and LM3915 can be purchased from advertisers in this issue. Should you decide to enhance the appearance of your PCB with flock paper then Paperchase Products Ltd., 213 Tottenham Court Road, London W1P 9AF offer a selection of colours.

Close-up of the filter circuitry (below).

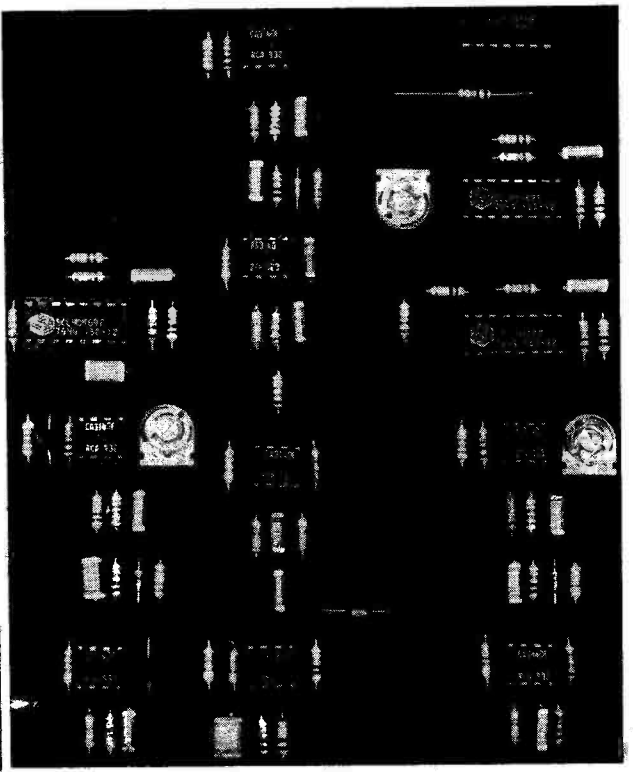

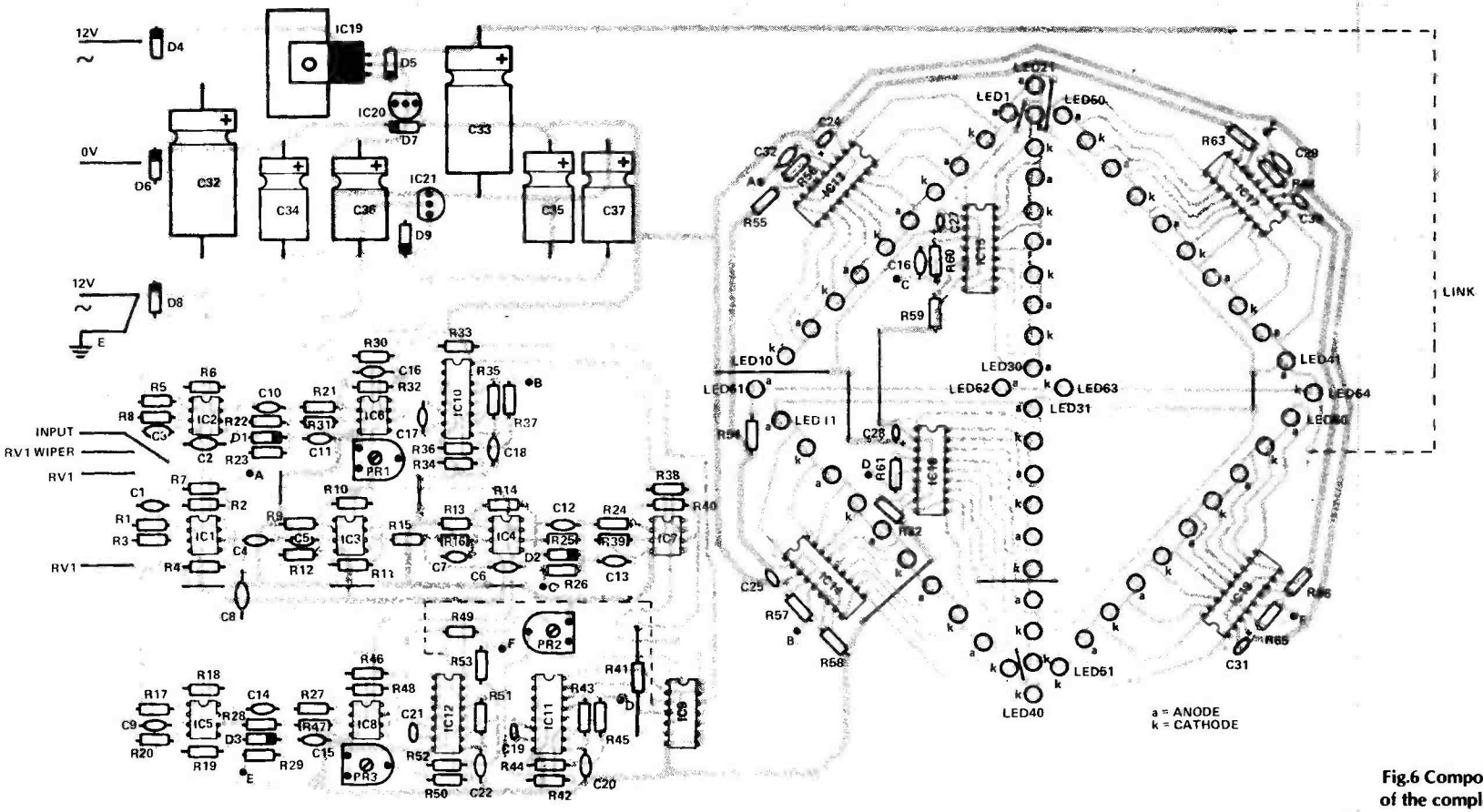


Fig.6 Component overlay of the complete VCSA.

PARTS LIST


Resistors (All ¼W 10%)		R63, 66	470R	C35, 37	470u 16 V electrolytic
R1, 3	100k			**Semiconductors**	
R2, 29, 56, 64	470k	**Potentiometers**		IC1-8	CA3140
R4, 22, 25, 28, 34, 42, 50	10k	RV1	47k linear	IC9	4093B
R5, 9, 11, 12, 13, 17, 57, 61, 65	39k	PR1, 2, 3	100k minature horizontal preset	IC10, 11, 12	4046B
				IC13, 15, 17	LM3915
R6, 7, 8, 10, 14, 18	47k	**Capacitors**		IC14, 16, 18	LM3914
R15, 16	18k	C1	470n polycarbonate	IC19	7824
R19, 20	15k	C2	33n ceramic	IC20	78L12
R21, 37, 45, 53	220k	C3	33n polycarbonate	IC21	79L12
R23	330k	C4, 5, 23, 26, 29	15n polycarbonate	D1-3	1N4148
R24, 27	180k	C6, 7, 8, 9, 21	4n7 polycarbonate	D4-9	1N4001
R26	1M2	C10, 17	220n polycarbonate	LED1-20, 61-64	0.125" Red
R30, 31, 38, 39, 46, 47	33k	C11, 13, 15, 18, 20, 22	100n polycarbonate	LED21-40	0.125" Yellow
R32, 40, 48	1M0	C12, 14	47n polycarbonate	LED41-60	0.125" Green
R33, 36, 41, 44, 49, 52	12k	C16	2n2 ceramic		
R35, 43, 51, 60	270k	C19	47n ceramic	**Miscellaneous**	
R54	2k2	C24, 25, 27, 28, 30, 31	47u 16 V tantalum	T1	12-0-12, 12 VA
R55, 58	1k5	C32, 33	1000u 63 V electrolytic	SW1	DPDT miniature toggle
R59, 62	560R	C34, 36	1000u 25 V electrolytic	F1	250 mA fuse and holder

WE HAVE MOVED

TO OUR NEW CENTRAL LONDON SHOWROOM

59/61 THEOBALDS RD, WC1 TUBE HOLBORN.

MICROS

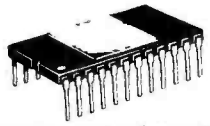

Micros, memory and support

MC1489	95	74S287	2.50
MC1488	95	74S288	2.50
MC14411	11.95	74S471	4.95
MC14412	11.95	74S472	11.95
1702	6.95	74S474	11.95
2101	2.99	8T26	1.80
2102	99	8T28	1.80
2111	2.32	8T95	1.80
2112	2.32	8T97	1.80
2114	3.45	8T98	1.80
2114L	3.75	SC/MP2	9.95
2142	10.40	8080	5.49
2376	11.50	8085	11.95
2513	6.50	8086	89.00
2516(5v)	13.95	8154	11.50
2532	29.00	8155	12.50
2708	6.50	81LS95	1.30
4027	2.95	81LS96	1.30
4116	4.95	81LS97	1.30
4118	14.95	81LS98	1.30
5204	7.95	8212	2.45
57109	12.43	8216	2.50
57161	9.95	8224	2.50
6011	4.95	8228	4.20
6402	4.95	8251	4.95
6502	7.95	8253	10.95
6520	4.50	8255	4.95
6522	7.95	8257	10.95
6532	8.50	8259	11.95
6545	17.50	8678	12.95
6576	14.95	8602	2.20
6800	7.95	96364	10.95
6802	12.49	Z80-2mHz	7.50
6809	19.95	Z80-PIO	6.95
6810	3.95	Z80-CTC	6.95
6821	4.50	Z80-4mHz	8.95
6845	19.50	Z80-PIO	7.50
6850	3.95	Z80-CTC	7.50
6852	5.95	Z8000	120.00
74S00	69	ADC0817	14.47
74S04	65	DG300	3.80
74S201	3.95	F8	9.95
74S188	2.50	F8SMI	9.95
74S262	9.95		

SOFTWARE

CP/M® DISK WITH / MAN MANUAL

Available on 8" IBM format & 5¼ for TUSCAN & TRITON

TCL SOFTWARE

TCL Disc Basic	£55/£9
TCL Pascal	£120/£9

MICROSOFT

Basic-80	£155/£15
Basic Compiler	£195/£15
Fortran-80	£205/£15
Cobol-80	£325/£15
Edit 80	£45/£10
Macro 80	£75/£10

MICROPRO

Word Star	£255/£15
Word-Star/Mail-Merge	£315/£15
Data Star	£195/£25
Word-Master	£75/£15

DIGITAL RESEARCH

CP/M 1-4	£75/£18
CP/M 2-2	£95/£18
MAC	£55/£10
SID	£45/£10

OTHERS

KISS	£190/£15
SUPER SORT I	£125/£15
C BASIC 2	£75/£10
Z80 Dev Pack	£50/£12
ZSID	£60/£7
POSTMASTER	£85/£10

MEDIA

5¼ S/Sided D/D	£3.50
" per 10	£29.50
8" S/Sided D/D	£4.50
" per 10	£35.00
C12 Data Cassettes	50p

MAIL ORDER

TEL & MAIL ORDERS ACCEPTED

BARCLAYCARD VISA ACCESS

74LS00

LS00	13	LS366	65
LS01	13	LS367	65
LS02	15	LS368	65
LS03	15	LS373	180
LS04	20	LS374	180
LS05	23	LS375	150
LS08	23	LS377	199
LS09	23	LS378	185
LS10	20	LS379	215
LS11	32	LS386	85
LS12	32	LS390	140
LS13	40	LS393	140
LS14	75	LS395	210
LS15	40	LS396	199
LS20	24	LS398	275
LS21	32	LS399	230
LS22	40	LS445	140
LS26	48	LS447	195
LS27	45	LS490	150
LS28	48	LS668	105
LS30	24	LS669	105
LS32	30	LS670	270
LS33	39		
LS37	39		
LS38	39		
LS40	28		
LS42	80		
LS47	85		
LS48	120		
LS49	120		
LS51	25		
LS54	30		
LS55	70		
LS63	150		
LS73	40		
LS74	40		
LS75	48		
LS76	45		
LS78	45		
LS83	105		
LS85	105		
LS86	45		
LS90	50		
LS91	125		
LS93	75		
LS95	115		
LS96	180		
LS107	45		
LS109	75		
LS112	60		
LS113	65		
LS114	49		
LS122	70		
LS123	95		
LS124	180		
LS125	60		
LS126	60		
LS132	95		
LS133	30		
LS136	55		
LS138	70		
LS139	90		
LS145	120		
LS148	175		
LS151	95		
LS153	85		
LS155	95		
LS156	95		
LS157	75		
LS158	85		
LS160	120		
LS161	98		
LS162	110		
LS163	100		
LS164	115		
LS165	155		
LS166	175		
LS168	210		
LS169	210		
LS170	285		
LS173	105		
LS174	147		
LS175	110		
LS181	295		
LS190	120		
LS191	120		
LS192	125		
LS193	125		
LS194	125		
LS195	125		
LS196	120		
LS202	345		
LS221	120		
LS240	225		
LS241	225		
LS242	232		
LS243	232		
LS244	225		
LS245	360		
LS247	135		
LS248	135		
LS249	135		
LS251	130		
LS253	130		
LS257	115		
LS258	120		
LS259	160		
LS261	450		
LS266	75		
LS273	160		
LS275	320		
LS279	85		
LS280	260		
LS283	190		
LS290	130		
LS293	130		
LS295	215		
LS298	215		
LS299	420		
LS324	200		
LS325	320		
LS326	330		
LS327	315		
LS352	185		
LS353	185		
LS365	65		

CMOS

4000	18
4001	18
4002	24
4006	92
4007	22
4008	82
4009	40
4010	48
4011	24
4012	24
4013	45
4014	85
4015	85
4016	42
4017	82
4018	28
4019	48
4020	89
4021	105
4022	85
4023	25
4024	75
4025	25
4026	180
4027	48
4028	82
4029	105
4030	60
4033	175
4034	210
4035	125
4040	105
4041	80
4042	80
4043	85
4044	85
4046	130
4047	98
4049	45
4050	48
4051	80
4052	80
4053	80
4054	130
4055	135
4068	28
4069	28
4070	30
4071	25
4072	25
4073	25
4075	25
4075	99
4078	30
4081	28
4093	89
4502	125
4507	80
4508	325
4510	98
4511	150
4512	85
4514	195
4515	250
4516	120
4518	105
4519	70
4520	115
4521	250
4522	150
4526	150
4527	180
4528	120


REGS

T03	+ve
7805	145
7812	145
7815	145
7818	145
-ve	
7905	220
7912	220
T0220	plast
7805	80
7812	80
7815	80
7818	80
7824	80
7905	85
7912	85
7915	85
7918	85

74XX
74CXX
LINEARS

Many other types in stock. Tel for details

FLOPPY DISK DRIVES

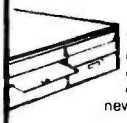

We sell all you need cased or uncased. Cables & connectors. Brand new fully guaranteed.

	Price
Single 5¼ Drive	£195
Single 8" SA800	£395
Dual 5¼ PSU	£59
Dual 8" PSU	£76
Dual Cabinet & PSU 1x8"	£565
Dual 8" Drive Unit	£945
Dual 5¼ Drive Unit	£440

VIDEO TERMINAL



24x80 display Pentland Video Terminal full features professional terminal. Full details on request

Price **£595**

S100 CARDS



NEW LOW PRICES

	KIT	ASSM
16K STATIC		
with no RAM(2114)	£ 62	£ 82
" 8K RAM "	£109	£130
" 16K RAM "	£157	£178
8K static (16x2114 chips)		£ 48
64K DYNAMIC (4116)		
with 16K RAM	£149	£165
with 32K RAM	£189	£205
with 48K RAM	£229	£245
with 64K RAM	£269	£285
16K upgrade 8x4116		£ 40

16/32K EPROM CARD

Without EPROMs

2708/2516 £63 £ 89

FDC DOUBLE DENSITY

Double Density for 5¼ or 8" Drives £ – £195

VAT

ALL OUR PRICES EXCLUDE VAT & P/P

CENTRONICS 737 PRINTER

LETTER QUALITY FOR £425



Uses any paper roll, fanfold, single sheets, 96 character ASCII, 7 x 7 dot matrix, 50 CPS, RS232 or parallel I/O.

OK TOOLS

Full range of wire wrapping accessories & boards & dip jumpers etc. Visit our showroom or send for our catalogue.

VERO

S100 prototyping boards and full range of accessories.

BOOKS


Complete range of microcomputer books and magazines on sale in our showroom.

CATALOGUE AVAILABLE

Catalogue available. Send 50p & S.A.E. (A4 size).

TUSCAN S100

A Z80 based S100 Computer

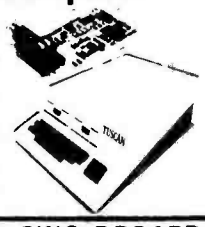

Single board will hold up to 8K RAM, 8K ROM, Video interface Z80 processor – I/O and cassette interface. 5 spare S100 expansion sockets for memory/disc expansion. System monitor, resident BASIC or CP/M system option. All components available separately or ready-built

NEW LOW PRICES

TUSCAN MAIN BOARD KIT ONLY £235 + VAT SAE FOR DETAILS

TRITON

SINGLE BOARD PERSONAL COMPUTER

8080 BASED SINGLE BOARD system with EUROCARD EXPANSION


Complete Kit incl. PSU/Case/Keybd	£286
Expansion Motherboard Kit	£ 50
8K (2114) RAM Card Kit	£ 97
8K (2708) ROM Card Kit	£ 97

Expandable up to CP/M Disc System. SAE for details.



TCL PASCAL

FOR PET & CP/M systems

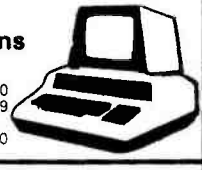

Put Pascal on your PET now	
Pascal conversion ROM	£ 20
Pascal manual	£ 9
Complete package including compiler	£120

Edge £4.00

Connectors S100



DIP Switches

4 way	£1.20
7 way	£1.75
8 way	£1.80

DIP Plugs

14 DIL	£ 65
24 DIL	£2.20
40 DIL	£3.60

DIL SOCKETS (TEXAS)

	Low Prof	Wire Wrap
8pin	10p	26p
14pin	12p	35p
16pin	13p	42p
18pin	16p	60p
20pin	22p	90p
22pin	25p	–
24pin	30p	65p
28pin	35p	90p
40pin	40p	1.10p

Zero Insertion Force Sockets

16 way	£4.95
24 way	£6.00
40 way	£9.50

D-Types

25W Male	£2.80
25W Female	£3.80
25W Cover	£1.80

Edge Connectors

	1	156
2x 6 way	–	1.75
2x12 way	–	3.00
2x10 way	–	2.00
2x15 way	–	3.20
2x18 way	–	3.50
2x22 way	3.20	3.65
2x25 way	3.60	–
2x30 way	4.15	–
2x36 way	4.75	3.90
2x40 way	5.00	–
2x43 way	5.50	4.60

Insulation/Piercing Ribbon/Cables

I/OHEADER	PLUG
10 way £2.20	10 way £1.60
20 way £3.40	20 way £2.30
26 way £4.00	26 way £2.70
34 way £4.80	34 way £3.30
40 way £5.40	40 way £3.75
50 way £6.00	50 way £4.60
60 way £6.50	60 way £6.00

Insulation Piercing Edge Connectors

20 way £3.60	40 way £5.30
26 way £4.00	50 way £6.00
34 way £4.60	

Insulation Piercing DIP Plugs

14 way DIP Plug	£1.30
16 way DIP Plug	£1.50
24 way DIP Plug	£2.80

Ribbon Cable

PRICE/M

	Grey	Coloured
10	.65	10 .90
14	.90	14 1.20
16	1.20	16 1.40
20	1.40	20 1.60
26	1.60	26 2.40
34	2.40	34 2.80
40	2.80	40 3.30
50	3.30	50 4.00
60	4.00	60 5.50

CRYSTALS FOR MICROS

32.768KHz	3.00	4.00MHz	2.70	10.00MHz	2.70
100KHz	3.00	4.43MHz	1.00	10.7MHz	2.70
200KHz	3.70	5.0MHz	2.70	16.00MHz	2.90
1.0MHz	3.60	6.0MHz	2.70	18.00MHz	2.90
1.008MHz	3.50	6.144MHz	2.70	18.432	2.90
1.8432MHz	3.00	7.0MHz	2.70	36MHz	2.90
2.00MHz	1.50	7.168MHz	2.50	48.0MHz	2.70
2.45760MHz	3.05	8.00MHz	2.70	100MHz	2.90
3.276MHz	2.70				

TRANSAM

59/61 THEOBALDS RD
LONDON WC1
TEL: 405 5240/2113
TELEX 444198.

TRANSAM

electronics today international BOOK SERVICE

How to order; Make cheques payable to ETI Book Service. Payment in sterling only please. Orders should be sent to: ETI Book Service, Modmags Sales Office, 145 Charing Cross Road, London WC2. All prices include P&P. Prices may be subject to change without notice.

BEGINNERS

Beginners Guide to Electronics Squires **£4.25**
Beginners Guide to Transistors Reddihough **£4.25**
Beginners Guide to Integrated Circuits Sinclair **£4.25**
Understanding Electronic Circuits Sinclair **£5.10**
Understanding Electronic Components Sinclair **£5.10**
Beginners Guide to Radio King **£4.25**
Beginners Guide to Audio Sinclair **£4.25**
Understanding Electronics, Warring **£4.90**

COOKBOOKS

TV Typewriters Cookbook £7.75
CMOS Cookbook £8.20
Active Filters £11.30
IC Timer Cookbook £7.65
IC Op-Amp Cookbook £10.00
Video Cookbook £8.50
ITL Cookbook £7.55
The Basic Cook £4.00
IC Converter Cookbook £9.50
Master IC Cookbook Hallmark **£7.45**

APPLICATIONS

Fire and Theft Security Systems B. Weis **£2.15**
How To Build Electronic Kits Chapel **£3.25**
110 Electronic Alarm Projects R.M. Marston **£4.95**
110 Semiconductor Projects for the Home Constructor R. M. Marston **£4.95**
110 Integrated Circuit Projects for the Home Constructor R. M. Marston **£4.95**
110 Thyristor Projectors Using SCRs R. M Marston **£4.95**
110 Wave Form Generator Projects R. M. Marston **£4.95**

COMPUTING & MICROPROCESSORS

What is a Mircroprocessor? 2 cassette tapes plus a 72-page book **£10.00**
Beginners Guide to Computers and Microprocessors with Projects C. Adams **£8.05**
BASIC Computer Games Ahl **£6.05**
BASIC for Home Computers A self-teaching guide B. Albrecht **£6.80**
Illustrating BASIC D. Alcock **£4.25**
Troubleshooting to Microprocessors and Digital Logic Goodman **£5.90**
Z-80 Microcomputer Handbook W. Barden **£7.75**
How to Program Microcomputers W. Barden **£7.25**
Introduction to Microcomputers and Microprocessors A. Barna **£9.50**
Microprocessors in Instruments and Control R. J. Bibbero **£13.10**
Basic BASIC J. S. Coan **£7.40**
Advanced BASIC J. S. Coan **£8.40**
Getting Acquainted with Microprocessors L. Frenzel **£7.25**
Beginners Guide to Microprocessors C. M. Gilmore **£4.90**
1001 Things to do with Your Personal Computer Sawusch **£6.00**
Beginning BASIC R. E. Gosling **£4.75**
Microprocessor Programming for Computer Hobbyists N. Graham **£7.15**
Miniprocessors from Calculators to Computers Heiserman **£5.35**
Microcomputers, Microprocessors, Hardware, Software and Applications J. L. Hilburn **£17.40**
BASIC Programming J. G. Kemeny **£8.20**
Microprocessor Systems Design E. Klingman **£17.65**
Intro to Microprocessors Leventhal **£11.00**
Microprocessor – Technology, Architecture & Applications D. R. McGlynn **£11.30**
Interactive Computing with BASIC Monro **£4.35**
BASIC with Style P. Nagin **£4.60**
Software Design for Microcomputers Ogdin **£8.85**
Microcomputer Design Ogdin **£7.45**
Microcomputer Base Design Peatman **£6.10**
Hands on BASIC with a PET Peckham **£10.50**
Complete Microcomputer Systems Handbook £8.75
6800 Software Gourmet Guide and Cookbook Scelbi **£9.20**
8080 Software Gourmet Guide and Cookbook £9.20
The 8080A Bugbook: Microcomputer Interfacing & Programming P. H. Rony **£8.35**
8080/8085 Software Design Titus **£7.60**
57 Pratical Programs & Games in BASIC Tracton **£6.65**
How to Design, Build and Program Your own Working Computer System £7.10
Your Own Computer Waite **£2.25**
Microprocessor/Microprogramming Handbook Ward **£6.20**

LOGIC

Logic Design Projects Using Standard ICs J. Wakerly **£7.25**
Pratical Digital Design Using ICs J. Greenfield **£16.00**
Designing With TTL Integrated Circuits Texas Instruments **£9.60**
How To Use IC Circuit Logic Elements J. Streater **£4.85**
110 COSMOS Digital IC Projects for the Home Constructor R. M. Marston **£4.95**
Understanding CMOS Integrated Circuits R. Melen **£4.60**
MOS Digital ICs G. Flynn **£5.25**

TEST INSTRUMENTS

The Oscilloscope In Use Sinclair **£4.00**
Working with the Oscilloscope A. Saunders **£4.60**
Servicing with the Oscilloscope A. King **£7.50**
Radio Television and Audio Test Instruments King **£8.30**

OP-AMPS

Applications of Operational Amplifiers Graeme (Burr Brown) **£8.45**
110 Operational Amplifier Projects for the Home Constructor R. M. Marston **£4.95**
Designing With Operational Amplifiers Burr Brown **£19.65**
Operational Amplifiers Design and Applications G. Tobery (Burr Brown) **£7.80**

COMMUNICATIONS

Communication Systems Intro To Signals & Noise B. Carison **£7.85**
Digital Signal Processing Theory & Applications L. R. Rabiner **£24.40**
Electronic Communication Systems G. Kennedy **£8.75**
Frequency Synthesis. Theory & Design Mannassewitsch **£25.00**
Principles of Communication Systems H. Taub **£8.40**

THEORY

Introduction to Digital Filtering Bogner **£10.60**
Transistor Circuit Design Texas Instruments **£10.00**
Foundations of Wireless Electronics M. G. Scroggie **£6.10**
Electronic Circuit Design Handbook 4th Edition **£16.75**
Master Guide to Electronic Circuits Adams **£9.25**

REFERENCE


Electronic Engineers Reference Book (Ed. 4) L. W. Turner **£38.00**
Electronic Components M. A. Colwell **£3.40**
Electronic Diagrams M. A. Colwell **£3.40**
International Transistor Selctor T. D. Towers New update **£10.70**
International FET Selector T. D. Towers New update **£4.60**
International Op-Amp Linear IC Selector Towers **£8.00**
International Microprocessor Selector (NEW) Towers **£16.00**
Radio, TV and Audio Technical Reference Amos **£37.00**

MISCELLANEOUS

Electronic Fault Diagnosis Sinclair **£4.00**
Integrated Electronics J. Milman **£8.20**
Practical Solid State DC Supplies T. D. Towers **£6.50**
Practical Triac/SCR Projects for the Experimenter R. Fox **£2.35**
Printed Circuit Assembly Hughes & Colwell **£3.40**

Fallen behind recent advances?
Just starting out?
Need a decent reference book?
ETI Book Service provides an easy way of getting your hands on the right title.


ELECTRONICS IN BOATS

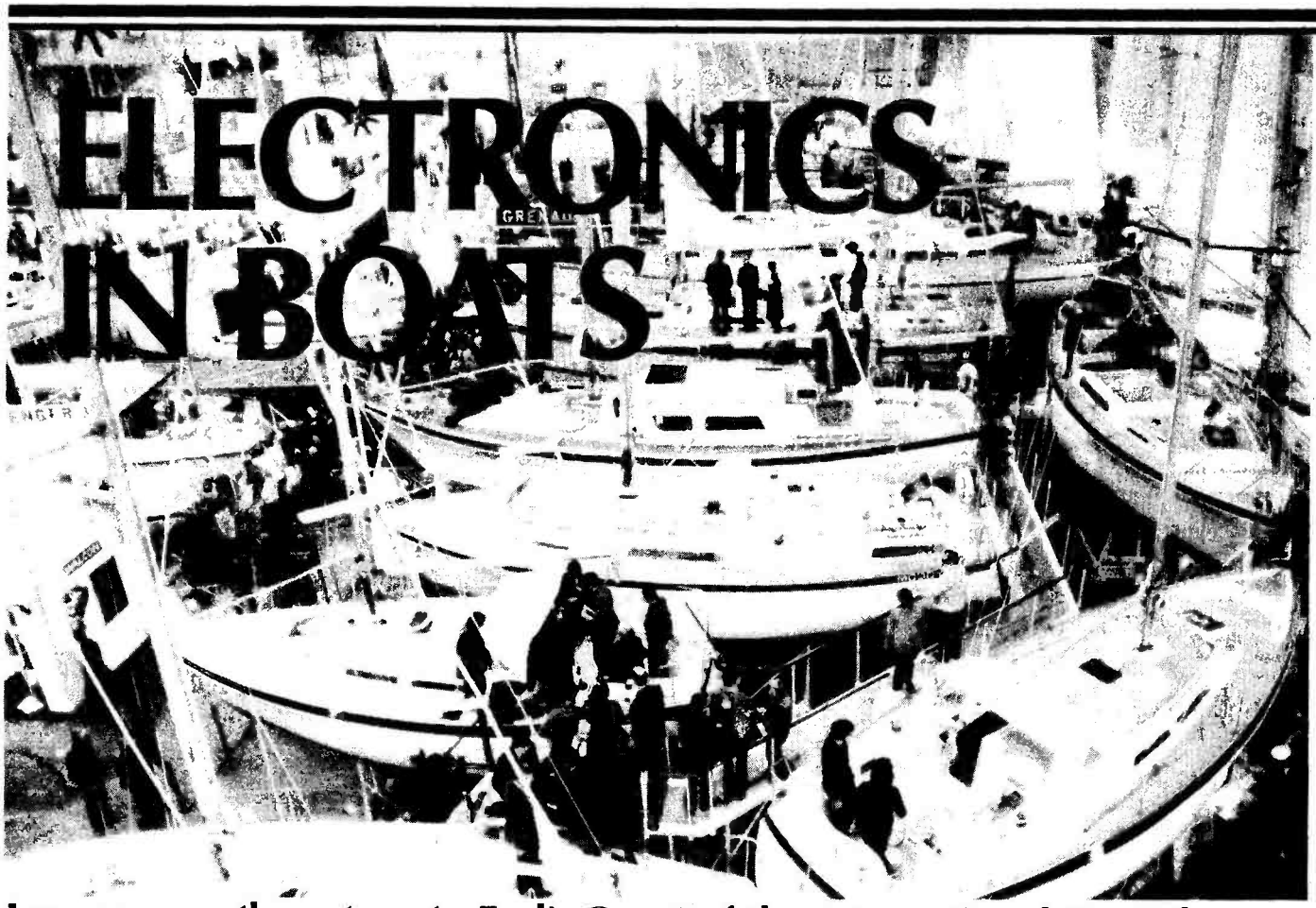

January saw the return to Earl's Court of the International Boat Show. Tina Boylan, (ETI's very own Tiller Girl) and Peter Green went along to see what part electronics plays in boating.

The 27th London International Boat Show brought a brief glimpse of the sunny Caribbean to a frost-bitten and land-locked crowd this January at Earl's Court. It was filled to the gunwales with land-lubbers and sea-goers alike, for the show is not merely aimed at the enthusiast or those of us with money to burn. There are plenty of attractions; gadgets to puzzle over and pleasure craft of every conceivable shape and size fill the huge halls as far as the eye (no offence, Nelson) can see. The whole experience is geared towards sun-baked fantasies and the epitome of luxury.

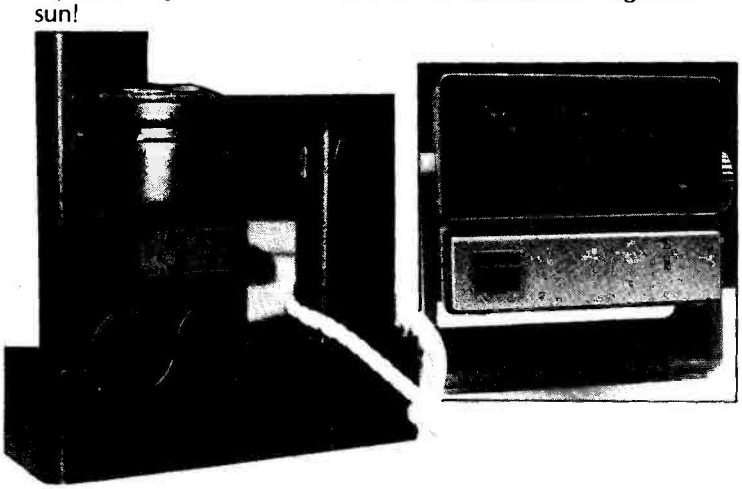
As you leave the lower halls, however, you find stands with some of the more down-to-earth(?) elements of boating on offer. Waterproof gear, life jackets and a million different types of rope. Proving that there's a lot more to boats than basking in the sun!



Messing About In Boats

Practically a whole floor was given to what interests ETI most — electronic devices. Electronics now plays an extremely important part in sailing the seven seas; the aid it gives to navigation and safety is immeasurable. For although men have successfully managed to sail over quite long distances for thousands of years with little more than the stars to guide them, electronics enables them to navigate far more accurately and has saved hundreds of lives.

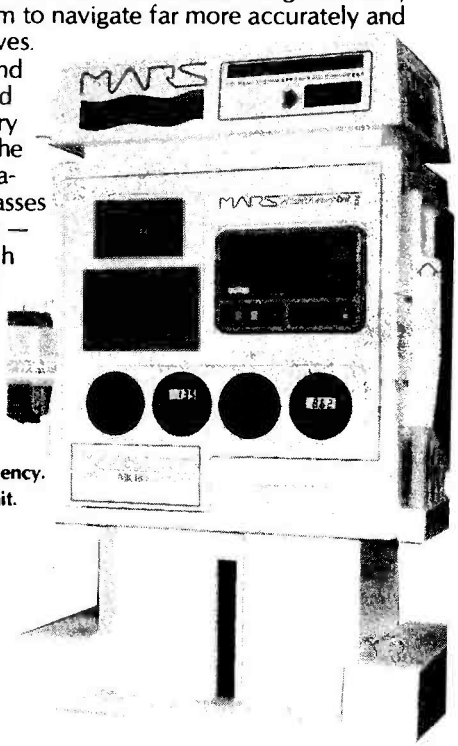Direction finding and measurement of speed are the most rudimentary necessities for sailing. The earliest form of navigation used charts, compasses and the first instrument — the log (literally!), which was a log tied to a rope knotted at equal intervals and dropped over the stern of the boat, the rope being paid



Far left: A small radio direction finder with digital readout of the selected frequency.

Left: A satellite navigation unit.

Right: A demonstration console for various navigational aids.

out for a known length of time and the knots counted. Calculations would then be made using these three ingredients. The result was always an approximation, as time keeping was not very accurate. In order to solve this problem, during the 17th century the British Admiralty offered a prize of ten thousand pounds for the development of an accurate chronometer. This huge sum was clearly an indication of the importance of such a device. In 1762 horologist John Harrison collected the prize for his design which kept an accuracy of better than two minutes over a six week period — a considerable achievement for the time(groan)!

Today electronic time keeping and calculation are accepted as being both accurate and simple. But electronics in navigation has come a long way from this simple level. Any mechanical instrument can be used in conjunction with electronics and in the case of navigation it is used in three main ways.


Which Way Now?

The first simple method is mainly an offshore aid and is called Radio Direction Finding (RDF). To use this system you must know your approximate position and from your (still indispensable) charts, you then choose three or more transmitting aircraft or marine radio beacons which are in the vicinity of your approximate position. The simplest RDF receivers are operated by manually turning a loop of ferrite antenna until the chosen beacon is heard at minimum strength. Beacon direction is then read off a calibrated scale. A separate sensing antenna must be incorporated to tell whether the beacon is in front of the boat or behind it. Some of the hand-held RDFs, of which there were many at the show, have a built-in compass. Using this it is possible to obtain a fix quickly and the skipper is able to use this on deck, therefore avoiding interference from rigging etc. Headphones are provided on many models for aural identification of very weak signals. When you have read off the bearing of each beacon you plot them on the chart and where the lines cross — X marks the spot, your position has been found! The bearings taken from these fixed stations give a resultant bearing which is usually accurate to within 2°.

The second method of navigation is an essential for any water-going vessel and is the aforementioned log, only somewhat changed in design! The log indicates speed and nautical mileage using a sensor. The simplest form of this is a small impellor monitoring water flow which is mounted through the hull, or over the stern of small boats. As it rotates it pulses a reed or similar switch to provide a suitable signal for subsequent analogue or digital processing and display. This type of sensor is unfortunately liable to clogging by seaweed or flotsam or may be inaccurate due to protrusions from the hull of the boat.

A way round this is to use one of two other electronic systems which have no moving parts. The first of these transmits ultrasonic pulses through the hull into the water and then listens for reflections caused by bubbles or other moving particles under the boat. The frequency of the received signal will differ from the transmitted one because of the Doppler shift and this is proportional to the speed of the water flow. The instrument displays the frequency difference as units of speed. Incorporated circuitry compensates for variations in the speed of sound in water at different temperatures and salinities.

The second and more common device is a hull-mounted electromagnet which creates a magnetic field at right-angles to the motion of the boat, with the lines of flux passing vertically through the hull. Since seawater is conductive, a voltage is induced in the water proportional to the velocity at which the water cuts through the field. There are two small metal studs which protrude through the hull and pick up the voltage — and

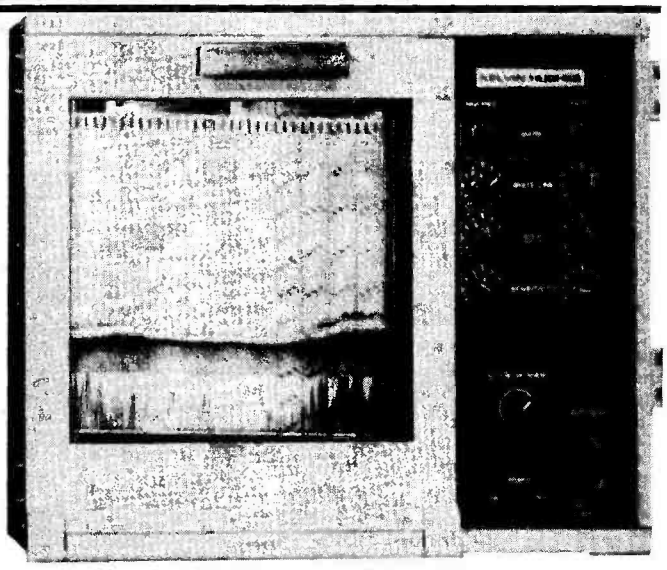

Above: A depth sounder with pen recorder.
Bottom: Another satellite navigation console.


that's all there is to it! With the log to calculate speed and mileage and bearings taken from a compass, this method can be used for dead reckoning navigation out at sea.

Seeing Stars

Satellite navigation is the last and most accurate means of position finding at present. This method is used mostly in large boats and ships as it can be rather expensive to install. As each satellite orbits the earth it transmits a signal on 150 and 400 MHz every two minutes. These signals give its exact orbital parameters, which are frequently updated with information based on observations made by land-based dedicated tracking stations. The satellites can provide information 19 or 20 times in every 24 hours, and, although their passes are not evenly spaced the worst delays are not normally longer than 2½ to 3 hours. Using the most sophisticated type of on-board dual frequency receivers, a positional accuracy of a few metres can be achieved anywhere in the world. Current satellite navigation receivers often incorporate extra features which are capable of predicting the next satellite pass, and have the ability to perform dead reckoning navigation *between* passes as well as ringing an alarm when the predicted destination is reached.

Sounds Fishy

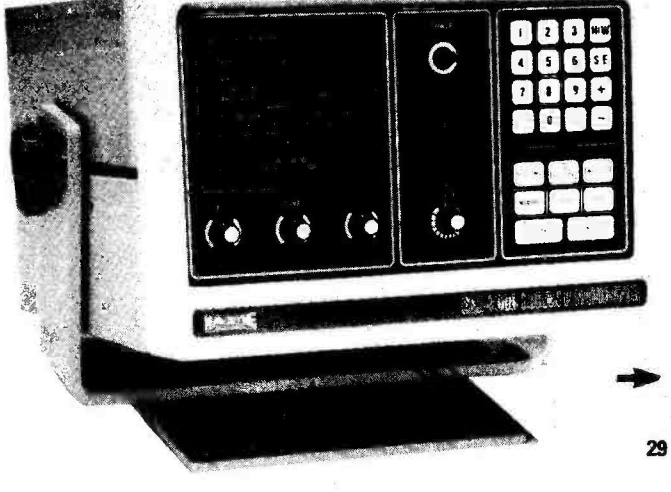So now your direction is pretty clear, but there is more information which must be found because you *really* need to know what's around you as well, and particularly what's under you. The open sea is not a swimming pool with a constant depth everywhere, and rivers are not like canals; they have sandbanks and shallows. So next on the list of electronic aids is a depth sounder.



These work by transmitting an impulse and measuring how long it takes to return. Ultrasonic energy is used for this; all types of depth sounder use this principle and only vary in the type of display, output power and frequency.


The display is usually an LED type, and when the acoustic pulse is sent out an LED flashes at the zero mark. When the echo returns another LED flashes on the dial at an angle proportional to the time since the transmit pulse was sent, thus indicating the depth of water below the hull. Apart from indicating the distance of the sea bed, the depth sounder will also pick up the position of shoals of fish, making it a useful aid for fishermen. Many depth sounders incorporate a pen recorder which enables them to return to a particularly good area where shoals have been found before. The depth sounder also makes landing less hazardous in bad weather conditions.

So now you know exactly where you're going. Great. But with the waterways of the world crowded with many different types of vessel, it's rather important that you know where *they're* going to, otherwise — oops! A collision, and that happens all too frequently!


On The Rebound

As far as hitting other vessels at sea goes, radar is the most effective safeguard available, even for the smallest craft. Radar not only enables you to see other vessels, but can also be used as a navigational aid because coastlines are also visible on it. Most radar sets consist of two main units — a console containing the display circuitry and controls, and a transceiver/scanner unit containing the RF electronics and the rotary antenna. Efficient radar does depend largely upon the height of elevation of the antenna since radar waves are transmitted on a line-of-sight principle. In bad weather this can mean that high waves will deflect the radar signal from a small boat making readings inaccurate. A small boat can also be easily mistaken for a wave by a radar operator on a large vessel, and this point brings us neatly to an associated safety device which is used with radar.

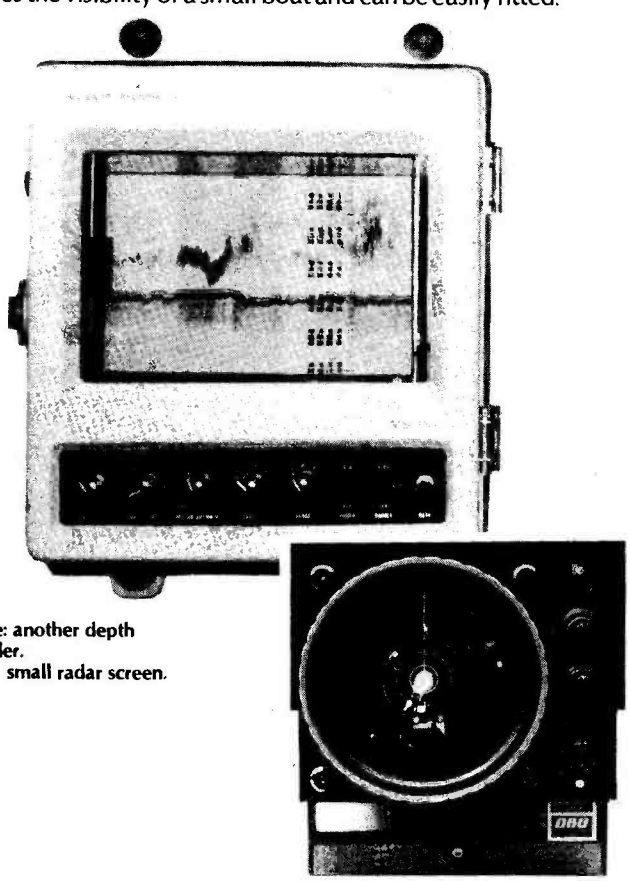A small boat, particularly if it is built of fibreglass or wood, does not reflect radar waves as well as a large vessel or one made of steel or aluminium, which leaves it little hope of being spotted on radar. Luckily there is a device which greatly improves the visibility of a small boat and can be easily fitted.



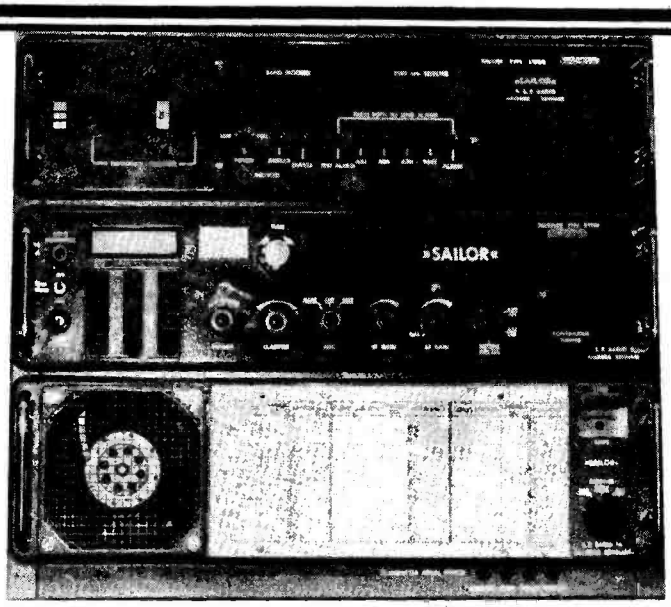Above: another depth recorder.
Right: small radar screen.



Above and left: Two reasons for choosing a small VHF radio telephone. These HF units are fairly bulky and would only suit large craft travelling far out to sea.

The metal radar reflector is masthead mounted and its shape and material make it an effective reflector of radar beams, giving a clear indication of the presence of a small boat on a radar monitor. These do have to be carefully fitted or they can be practically useless.

Steering A Straight Course


Electronics can also be used for steering your course once it is chosen. An 'autopilot' can be used for either power boats or sailing boats. Basically an autopilot is a straightforward servomechanism; the actual heading is compared to the desired course and the error signal is used to drive a servomotor, thus correcting the rudder. A disadvantage with this system is that the swell of waves can affect the autopilot and cause it to continually try to correct the movements of the rudder, however insignificant they may be, so many autopilots have a built-in override mechanism which can be adjusted to compensate for varying sea conditions.

On a sailing boat, steering is far more dependent on wind direction, so an autopilot of the type used in power boats would be next to useless; it would keep a heading regardless of wind change leaving the sails set wrongly, which, at best, would cause the boat to lose speed and at worst could put it into a dangerous situation. So most sailboat autopilots keep the boat on the right heading relative to the wind; these units offer a choice of compass or wind vane to generate the control signal.

Come In Number 44

Even boats equipped with all of the safety features so far mentioned can find themselves running into trouble and in need of communication with rescue services. Or maybe you want to contact someone you wish to speak to (you're half-way across the North Sea when you realise that it's Aunt Maud's birthday and you forgot to send a card . . .).

British Telecom International, the new telecommunications branch of the Post Office, now operates 12 coastal radio stations in Britain; 11 of these are for medium/short range use, one is for long range. In addition, there is a continually growing network of remotely controlled VHF stations. The coastal stations will deal with any type of message, from ship-to-shore social calls to distress signals — the latter naturally receiving priority at all times — and also broadcast routine weather reports, gale warnings and details of navigational hazards.

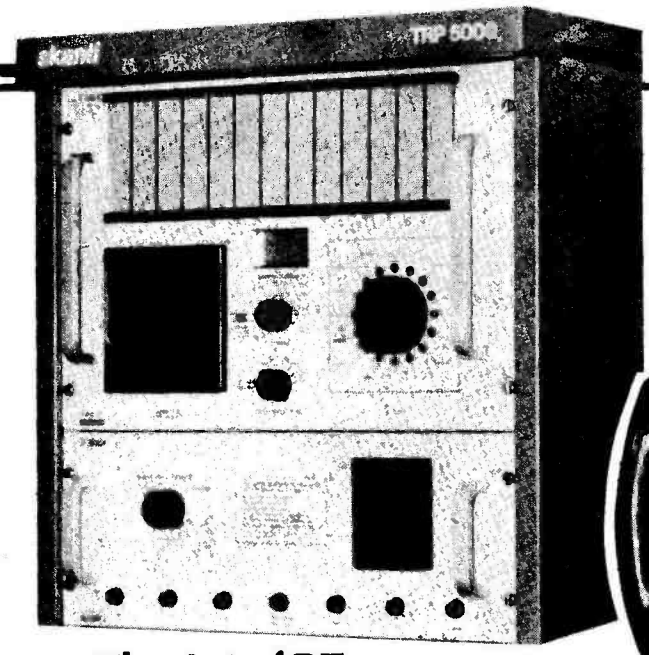



Left: This VHF radio telephone features more facilities than the basic models but is still quite compact.

The Art of RT

The VHF radio telephone solves many of the problems that prevent small boat owners from fitting HF equipment and as such is an invaluable aid to safety for pleasure boats. HF radios are generally large and draw a lot of power, sometimes necessitating extra batteries. They are more complex, more prone to interference, more expensive and more difficult to install (aerials are generally loaded whips which require a ground plane). A typical VHF unit, though, is only slightly bigger than a car radio/cassette player and is just as easy to install. Mounting brackets for vertical or horizontal fitting are usually provided, and some types have a mounting flange that allows flush installation in a bulkhead, car dashboard style. After that you simply fit a mast-top aerial, plug into the boat's 12 V supply and you're ready to go.

Models generally offer similar facilities and these are limited to the essentials — on/off switch, volume, squelch and channel selector switch. The VHF frequencies allocated are from 156 MHz to 162 MHz and generally the transceivers will have a selection of a dozen channels in this range. Some models use a frequency synthesiser, so you can only transmit on the frequencies pre-selected by the manufacturer. Others have individual crystals fitted for each channel, and by changing crystals you can pick any set of frequencies that are convenient. *All* radio telephones should be capable of transmitting on channel 16 — this is the VHF international distress frequency.

Output power ranges from about 10 W to 25 W and often a control is provided to reduce the power output when speaking to a station at close quarters. This may either be in the form of a high/low switch or a continuously variable pot, and prevents unnecessary interference to more distant users.

Simply Simplex

Although there are some duplex channels in the VHF band (ie you may transmit and receive simultaneously, as with a telephone), only simplex transceivers were in evidence at the Show. These require the use of a press-to-talk button on the microphone, a feature well-known to those "good buddies" who have the *other* sort of radio fitted in their cars!

The qualification "in-shore and coastal" is due to the one disadvantage of VHF compared to HF: lack of range. VHF frequencies are not subject to 'skip' via the ionosphere and while this provides immunity from unwanted signals, it does mean that only line-of-sight communication is possible. Even with a mast-top aerial, range is limited to about 20 nautical miles.

A few VHF radio telephones have an optional version which allows completely portable use: the set has a battery pack (rechargeable from the ship's 12 V supply), a telephone handset and a small helical aerial. In an emergency the set can be removed from its installation and used as a walkie-talkie; an obvious advantage if your cockpit is on fire, you've lost your mast and the main aerial with it, or you're sitting in a small rubber dinghy about 20 fathoms above the remains of your yacht! However, in this mode your range will be reduced still further, especially at sea level.

Hand-Held Help

For absolute assurance that an accident at sea will not be compounded by your inability to summon help, a portable distress radio telephone is essential. These units are complete, self-contained HF radio telephones, pre-tuned to one frequency only, the international maritime distress frequency (2182 kHz). Unlike the VHF band, this frequency is not subject to line-of-sight restrictions and is insensitive to aerial height. Typical 'worst-case' transmitting ranges exceed 40 miles; under favourable conditions this can be greatly extended.

A typical distress radio telephone is shock-resistant, waterproof and self-buoyant (radio overboard?!). The controls are kept to an absolute minimum and are designed to be easy to operate even with numbed fingers. Instructions are clearly and concisely printed on the case for the benefit of untrained people. To use the unit, the earth-wire with its lead sinker is thrown into the sea, the telescopic aerial extended fully, and the alarm button pressed for abut 20-30 S. This causes a two-tone signal to be transmitted which overrides all other traffic on the 2182 kHz frequency and automatically activates the watch-keeping receivers used by coastguards, rescue services, merchant ships and trawlers. Once you've attracted everyone's attention you can make speech contact with your rescuers.

These units may also be used for 'urgency' calls (without using the alarm button), for direct contact with coastguards and commercial ships in order to obtain medical, meteorological or navigational advice, or to report any less serious damage to your vessel such as engine failure.

It should be pointed out that, especially in the case of VHF sets, there is little point in fitting a radio telephone unless *everyone* who is aboard the boat has been told where the set is and how to use it. Help is going to be a long time coming if the only man who can use the radio is the one who has just suffered a heart attack, or food poisoning, or been washed irretrievably overboard. For similar reasons, try to get a VHF set with duplex operation. Then anyone unfamiliar with radio procedure is unable to cause, at least, confusion and at worst, fatal delay, by forgetting to press the push-to-talk button.


Be Prepared

So that more or less sums up the wide range of electronic gadgets you will need for your boat, whatever size it may be. Of course, there are still many developments being made in nautical electronics because, unfortunately accidents *do* still happen. One thing visiting the Boat Show can teach you is how important having the right equipment is, and, if you visit next year's Show you too may become hooked on boats for life! **ETI**

SIMPLY AHEAD and staying there

The range grows bigger...better...

New Profile Amplifiers - Two New Series

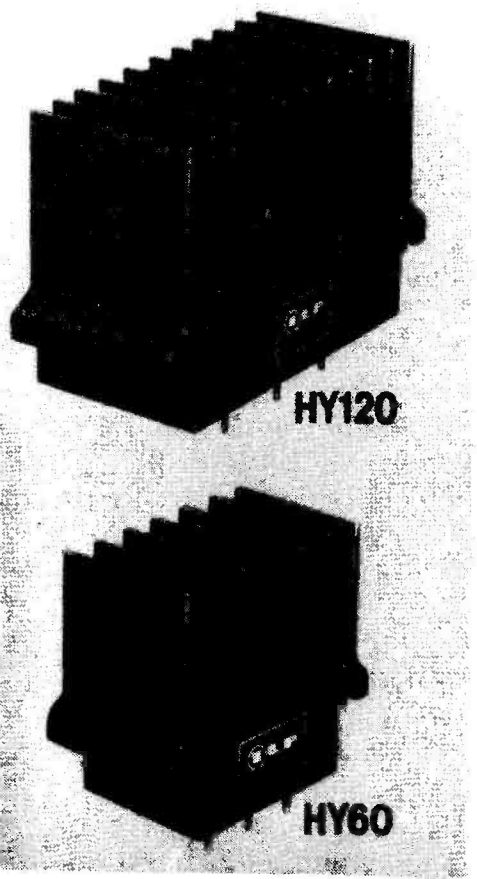

MOSFET

CHOOSE AN I.L.P MOSFET POWER AMP when it is advantageous to have a faster slew rate, lower distortion at higher frequencies, enhanced thermal stability, the ability to work with complex loads without difficulty and complete absence of cross-over distortion. I.L.P's exclusive encapsulation technique within fully adequate heatsinks has been taken a stage further with specially developed computer-verified 'New Profile' extrusions. These ensure optimum operating efficiency from our new MOSFETS, and are easier to mount. Connection is via five pins on the underside. **I.L.P MOSFETS ARE IDENTICAL IN PERFORMANCE TO THE COSTLIEST AMPLIFIERS IN THIS EXCITING NEW CATEGORY BUT ARE ONLY A FRACTION OF PRICES CHARGED ELSEWHERE.**


Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
MOS120	60W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£25.88 + £3.88
MOS200	120W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£33.46 + £5.02


BIPOLAR

(Standard O-P Transistors)

CHOOSE AN I.L.P BIPOLAR POWER AMP where power and price are first consideration while maintaining optimum performance with hi-fi quality and wide choice of models. From domestic hi-fi to disco and P.A., for instrument amplification, there is an I.L.P Bipolar to fill the bill, and as with our new Mosfets, we have encapsulated Bipolars within our New Profile extrusions with their computer-verified thermal efficiency and improved mounting shoulders. Connections are simple, via five pins on the underside and with our newest pre-amps and power supply units, it becomes easier than ever to have a system layout housed the way you want it.


Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
HY30	15W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£7.29 + £1.09
HY60	30W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£8.33 + £1.25
HY120	60W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£17.48 + £2.62
HY200	120W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£21.21 + £3.18
HY400	240W into 4Ω	0.01%	15V/μs	5μs	100dB	£31.83 + £4.77

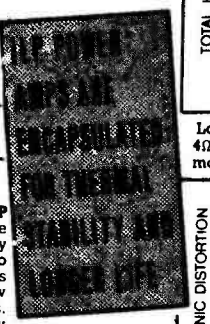

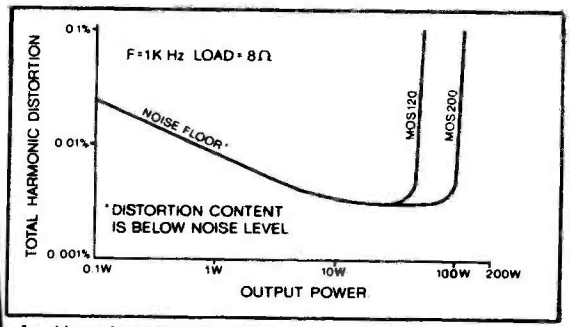

Load impedance both models 4Ω-∞ Input sensitivity both models 500mV

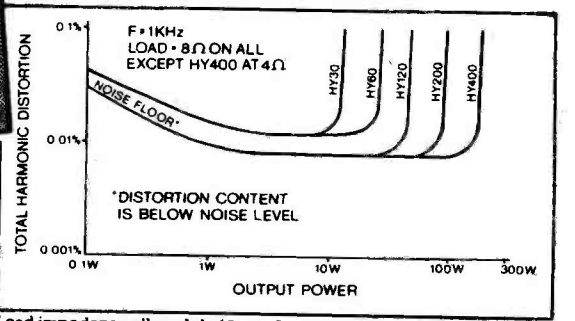Input impedance both models 100KΩ Frequency response both models 15Hz-100KHz-3dB




Load impedance all models 4Ω-∞ Input sensitivity all models 500mV


Input impedance all models 100KΩ Frequency response all models 15Hz-50KHz-3dB



THE NEW PROFILE EXTRUSIONS

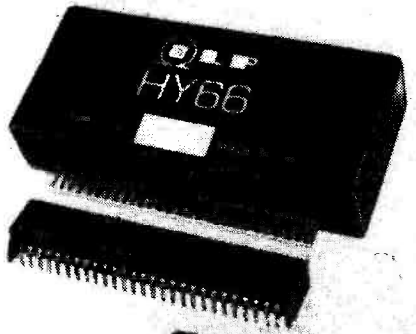The introduction of standard heatsink extrusion for all I.L.P. power amplifiers achieves many advantages:— Research shows they provide optimum thermal dissipation and stability. Slotted shoulders allow easy mounting; standardisation enables us to keep our prices competitive. Surfaces are matt black, anodised for higher thermal conductivity. Extrusions vary in size according to module number.



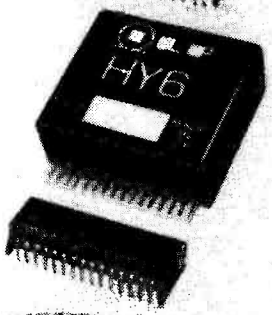



PSU

NO QUIBBLE 5 YEAR GUARANTEE
7-DAY DESPATCH ON ALL ORDERS
BRITISH DESIGN AND MANUFACTURE
FREEPOST SERVICE


NEW PRE-AMPS

COMPATIBLE WITH ALL I.L.P MODULES

HY6 (mono) and **HY66** (stereo) are new to I.L.P's range of advanced audio modules. Their improved characteristics and styling ensure their being compatible with all I.L.P power-amps both MOSFET and BIPOLAR, giving you chance to get the best possible reproduction from your equipment. HY6 and HY66 pre-amps are protected against short circuit and wrong polarity. Full assembly instructions are provided. Mounting boards are available as below.
Sizes – **HY6** – 45×20×40 mm. **HY66** – 90×20×40 mm. Active Tone Control circuits provide ±12dB cut and boost. **Inputs Sensitivity** – Mag. PU. –3mV: Mic – selectable 1-12mV: All others 100mV. **Tape O/P** – 100mV: **Main O/P** – 500mV: **Frequency response** – D.C. to 100KHz – 3dB.

HY6 mono £6.44 + 97p VAT Connectors included
HY66 stereo £12.19 + £1.83 VAT Connectors included

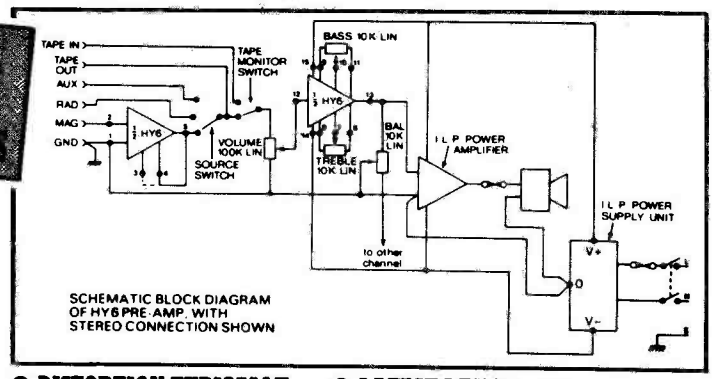B6 Mounting Board for one HY6 78p + 12p VAT
B66 Mounting Board for one HY66 99p + 15p VAT



SCHEMATIC BLOCK DIAGRAM OF HY6 PRE-AMP. WITH STEREO CONNECTION SHOWN

- **DISTORTION TYPICALLY 0.005%**
- **S/N RATIO – 90dB (Mag. P.U. – 68 dB)**
- **38 dB overload margin on Mag. P.U.**
- **LATEST DESIGN HIGH QUALITY CONNECTORS**
- **ONLY POTS, SWITCHES AND PLUGS/SOCKETS NEED ADDING**
- **NEEDS ONLY UNREGULATED POWER SUPPLY ±15 to ±60v**

NEW POWER SUPPLY UNITS

IN A RANGE OF 11 MODELS USING LATEST TOROIDAL TRANSFORMERS

Of the eleven power supply units which comprise our current range, nine have toroidal transformers made in our own factory. Thus these I.L.P power supply units are space-saving, more efficient and their better overall design helps enormously when assembly building. All models in the range are compatible with all I.L.P amps and pre-amps with types to match whatever I.L.P power amps you choose.

PSU30 ± 15V at 100mA to drive up to 12 x HY6 or 6 x HY66 **£4.50** + 0.68p VAT
• *THE FOLLOWING WILL ALSO DRIVE I.L.P PRE-AMPS*
PSU36 for use with 1 or 2 HY30's **£8.10** + £1.22 VAT
• *ALL THE FOLLOWING USE TOROIDAL TRANSFORMERS*
PSU50 for use with 1 or 2 HY60's **£10.94** + £1.64 VAT
PSU60 for use with 1 HY120 **£13.04** + £1.96 VAT
PSU65 for use with 1 MOS120 **£13.32** + £2.00 VAT
PSU70 for use with 1 or 2 HY120's **£15.92** + £2.39 VAT
PSU75 for use with 1 or 2 **MOS120** **£16.20** + £2.43 VAT
PSU90 for use with 1 HY200 **£16.20** + £2.43 VAT
PSU95 for use with 1 **MOS200** **£16.32** + £2.45 VAT
PSU180 for use with 1 HY400 or 2 HY200 **£21.34** + £3.20 VAT
PSU185 for use with 1 or 2 **MOS200** **£21.46** + £3.22 VAT

1971-1980
TEN YEARS OF PLANNED PROGRESS

When, in 1971, Ian L. Potts founded his now world-famous company, he saw the need for a different and more rational approach to exploiting to the full, the potential that lay in modular construction. New thinking was badly needed. The result was a range of modules revolutionary in concept. The rightness of this new thinking is shown by the size of the company today, its new factory, its vast exports, its acceptance by constructors as *the* modules to build with. The range grows bigger and better. Exciting new lines (in no way conflicting with existing ones) are well past drawing board stage. This is why I.L.P are simply ahead and staying there.

★ **Freepost facility**
When ordering or writing about I.L.P products, you do not need to stamp the envelope. Mark it FREEPOST plus the code shown in the address below. We pay the postage for you.

★ **TO ORDER** Send cheque or money order payable to I.L.P Electronics Ltd and crossed. Or pay by ACCESS or BARCLAYCARD. Cash payments must be in registered envelope; if C.O.D. payment is wanted, please add £1.00 to TOTAL value of order.

BRITAIN'S FOREMOST QUALITY MODULE SUPPLIERS

To: I.L.P ELECTRONICS LTD. CANTERBURY CT2 7EP

Please supply .....

..... Total purchase price £.....

I enclose Cheque ☐ Postal Orders ☐ International Money Order ☐

Please debit my Access/Barclaycard Account No. .....

.....

NAME .....

ADDRESS .....

.....

Signature .....

ALL U.K. ORDERS DESPATCHED POST FREE

I.L.P ELECTRONICS LTD.

FREEPOST 4 Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP.
Telephone (0227) 54778 (Technical (0227) 64723) Telex 965780

Available also from MARSHALLS, WATFORD ELECTRONICS and certain other selected retailers

Rapid Electronics

Pack No.		
A10	10 PP3 battery leads	50p
A72	10 3.5mm jack plugs	80p
A73	10 3.5mm jack sockets	80p
A74A	5 Standard jack plugs	80p
A75A	5 Std. jack sockets	90p
A84A	5 5 pin 180 DIN plugs	70p
A85A	5 5 pin 180 DIN sockets	55p
C21	5 Min. slide switches	75p
C28	5 Push to make switches	70p
C29	5 Push to break switches	90p
C50	20 8 pin DIL sockets	170p
C51	20 14 pin DIL sockets	200p
C52	20 16 pin DIL sockets	220p
E10	Resistor kit. 650 resistors ¼W 10 ea value 4.7 to 1M	480p
–	Single potentiometers 5K-1M log in lin	35p
–	Slide potentiometers. 60mm travel. 5K-500K log or lin	65p
E26	10 100K min. presets	70p
E31	10 1u 63V electrolytics	50p
E33	10 4u7 63V radial elec.	50p
E34	10 10u 25V radial elec.	50p
E37	10 100u 25V radial elec.	75p
E44	10 1u 35V bead tants.	100p
E50	10 0.01 C280 polyester	50p
E54	10 0.01 C280 polyester	50p
E10	10 BC107 transistors	90p
F11	10 BC108 transistors	90p
F12	10 BC109 transistors	90p
F17	10 BC214L transistors	90p
F27A	5 2N3819 transistors	100p
F311	1 BD131 transistor	45p
F312	1 BD132 transistor	45p

Pack No.		
F331	1 BD139 transistor	45p
F421	1 MJ2955 transistor	110p
F43	5 78L05 regulators	180p
F46A	1 7805 regulator	70p
F47A	1 7812 regulator	70p
F49A	1 7905 regulator	75p
F53	1 LM317T variable reg.	200p
F54	LM323K 3A 5V reg.	500p
H11	20 1N4002 diodes	75p
H30	2 W005 bridge rectifiers	45p
H60	100 1N4148 diodes	180p
H73	2 C106D thyristors	90p
J5	10 0.2in red LEDs	100p
J25	10 0.2in green LEDs	150p
J45	10 0.2in yellow LEDs	150p
J70	20 0.2in LED clips	60p
J7	10 0.125in red LEDs	100p
J27	10 0.125in green LEDs	150p
J47	10 0.125in yellow LEDs	150p
J72	20 0.125in LED clips	60p
J75	1 FND500 CC display	100p
K5	5 741 op amps.	90p
K20	5 CA3140 op amps.	225p
K30	5 LM301A op amps.	140p
K40	1 LM324 op amps.	50p
K50	1 LM380 2W amp.	70p
K75	1 LM3914 LED bar graph	320p
K85	5 NE555 timers	110p
K90	1 NE556 timer	50p
K100	5 TL081 op amps.	175p
L8	5 4011 CMOS	130p
L9	1 4013 CMOS	40p
L11	1 4017 CMOS	75p
L22	1 4049 CMOS	45p

All prices include VAT. Please add 50p postage and packing. Send s.a.e. for our complete catalogue.

Rapid Electronics Limited
Hillcroft House, Station Road, Eynsford, Kent

LANGSTONE ELECTRONICS

38 OUTRAM ROAD, SOUTHSEA, HANTS. PO5 1QZ

TRANSISTORS

ACY18/19	29p
BC107/8/9	12p
BC177/8/9	15p
BC182/3/4	9p
BC212/3/4	11p
BCW91/2	30p
BCY70/1/2	17p
BD135/6	40p
BDY56	200p
BF257/8	29p
BFY50/1/2	23p
BU126	150p
BU208	200p
BUX48	500p
ME0404	13p
ME1001	10p
MEF3819	23p
MEU11/12	30p
MEU21/2	36p
2N404A	25p
2N914	17p
2N2218/9	23p
2N2221/2	23p
2N2369A	17p
2N2484	30p
2N2646	45p
2N2904/5	24p
2N2906/7	24p
2N3055	48p
2N3702/3	11p
2N3704/11	10p
2N3819	23p
2N4058-62	11p
2N5308	29p

DIODES

AA143/4	10p
OA91/5	10p
1N914	4p
1N4001/2	5p
1N4003/5	6p
1N4006/7	7p
1N4148	4p
1N5401/2	14p
1N5404/5	19p
1N5406/7	19p
Diac	25p

ZENERS

0.5W	8p
1.3W	12p

THYRISTORS

0.8A/100V	37p
1.6A/400V	39p
4A/400V	47p
10A/400V	140p
25A/400V	520p

TRIACS

1.6A/400V	47p
6A/400V	70p
10A/400V	115p
25A/700V	500p
40A/700V	600p

74 TTL

7400	12p
7401/2	14p
7404/5	16p
7406/7	28p
7413	26p
7447	79p
7450/4	15p
7473/4	23p
8481/3	89p
7485	110p
7489	190p
7491	65p
7493	38p
74121	33p
74123	62p
74145	79p
74155/6	69p
74164/5	105p
74182	99p
74192/3	95p

LINEARS

355/6/7	80p
358	60p
301A	39p
324	65p
741	25p
1458	45p
309K	120p
7805/12	85p
7905/12	92p
555	25p

CMOS

4000/1/2	18p
4008	79p
4011/2	18p
4016	39p
4017/8	79p
4023/5	18p
4040	90p
4046	120p
4049/50	45p
4093	79p
4402/12	38p
4502	99p
4510	110p
4514	240p
4516/8	99p
4528/31	99p
4581	185p
4582	125p
4584	69p
4585	99p

CONSUMER

SAJ180	196p
SAK115	123p
TAA930	180p
TBA800	196p
TCA910	95p
ESM1601	165p
TDA1067	190p
TDE2608	280p
ULN2136	120p
ULN2244	250p

MPUs

6800	440p
6802	660p
6809	1790p
6821	230p
6840	680p
6850	230p
6852	270p
6862	820p
6875	480p
6880	130p
6882	270p
6888	95p
6889	130p
9364	1150p

MEMORIES

6810	170p
2114	340p
4116	370p
2708	510p
2716	840p

PLUS:
Resistors
Capacitors
Veroboards
Veroboxes
Connectors
Knobs
Potentiometers
Solder Eqpt.
Wire & Cable

NOTE: ALL OUR PRICES INCLUDE VAT

PLEASE RUSH ME YOUR CATALOGUE — FREE!


Name: .....

Address: .....

.....

.....


THE NEW AND UNIQUE VEROBLOC

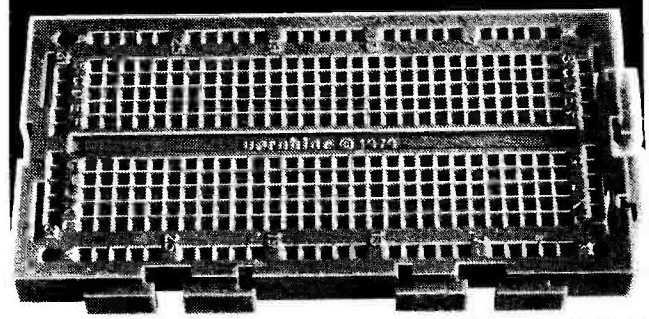

ADDS TO YOUR CAPABILITY

Already used in industry, this solderless breadboard is now available to the hobbyist. Unique because of its universal interlocking facility meaning you no longer need lots of different boards.

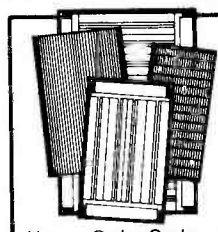Send now for the unique Verobloc.
Order code 200-21092G. £4.16p inclusive.



AND VERO HAVE ADDED TO THEIR TRADITIONAL RANGE OF HIGH QUALITY BOARDS, ALSO EX-STOCK.

No.	Order Code	Description	Size (mm)	Price
1)	10-2845B	Microboard	160 x 100	5.66
2)	10-2846H	Microboard	160 x 233.4	12.41
3)	200-21084E	V-Q Board	147.83 x 73.66	1.65
4)	09-2196L	Veroboard	160 x 100	1.63

Carriage & VAT included.

Vero Electronics Limited, Retail Dept., Industrial Estate, Chandler's Ford, Hampshire SO5 3ZR. Tel (04215) 62829

State quantity and order codes required .....

Name .....

Address .....

ETI4


I enclose Cheque/PO for £ ..... or debit my Barclay Card/

Access No .....

Exp. date .....

vero

TECH TIPS

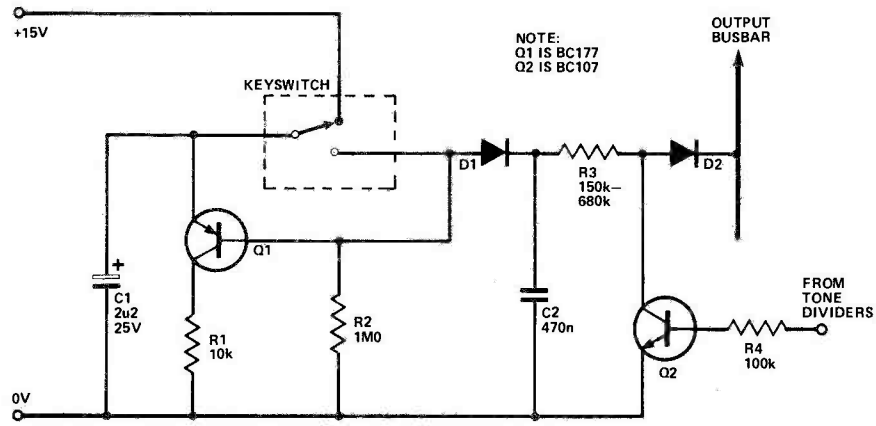

Touch-Sensitive Piano Keying

J. Cozens, York

The circuit is operated by a single-pole change-over key switch. When the key is in the fully released position C1 is held charged from the 15 V rail. Q1 is turned on by the bias current supplied by R2. When the key is depressed C1 is disconnected from the 15 V rail and starts to discharge through Q1 and R1. When the key is fully depressed Q1 is turned off and the remaining voltage on C1 then charges up C2 via D1. Both capacitors then discharge via R3. The envelope produced by this decaying voltage is chopped by Q2, driven directly from the tone dividers. Upon the release of the key, C1 is disconnected from the chopper circuit and C2 discharges rapidly via R3, simulating the action of the dampers. D1 is included to prevent C2 discharging through R2 when the key is released and D2 prevents interaction with other keying circuits.

As the voltage remaining on C1 at the completion of a keystroke depends on the key velocity, a degree of touch-sensitivity is obtained with this circuit.

Tuning Fork Mods.


M.L. Duncan, Greenford.

With a few slight modifications to the ETI Tuning Fork it is possible to use the very cheap and plentiful TV colour crystal tuned to 4.43361875 MHz.

The oscillator circuit output is divided by 2519 giving a frequency of 1760 accurate to one part in 250,000. The division is done by a 4040 in place of the 4020 and the switching giving an alternate 'A' at 445 Hz is eliminated.


A 4013 dual flip-flop is added before the output buffer to give further division by two and four. These outputs are switched before the buffer to give a choice of 'A's at 880 and 440 Hz respectively. The extra cost of the 4013 is offset by eliminating one of the 4011s.

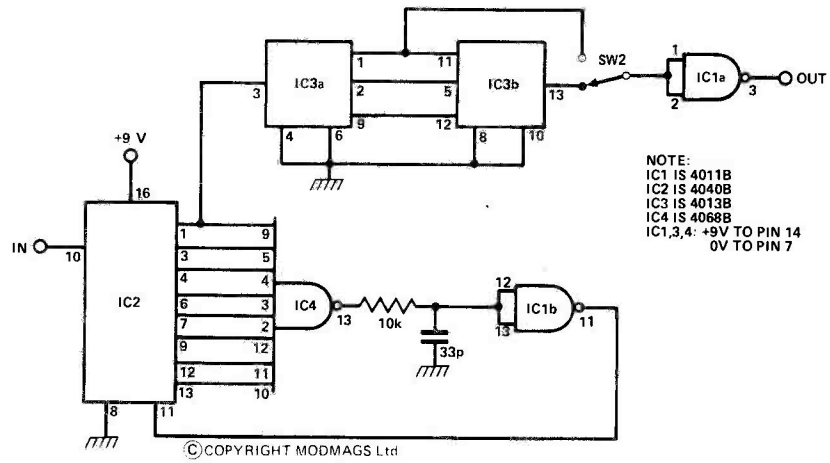The diagram shows the altered parts of the circuit. The oscillator is retained, using the changed crystal, as is the output circuit from R4 onwards.



©COPYRIGHT MODMAGS Ltd

Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items. ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to ETI TECH-TIPS, Electronics Today International, 145 Charing Cross Road, London WC2H 0EE.

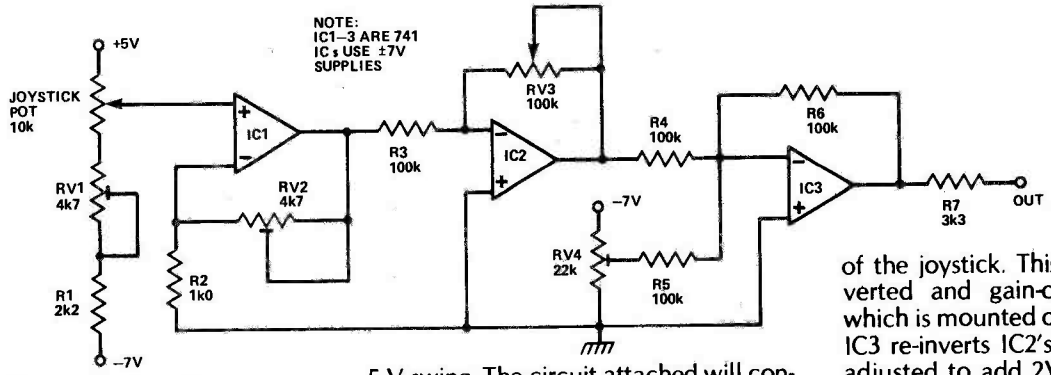

Joystick Control

M. Swale, Cardiff

Having recently built the ETI 4600 synthesiser, I found, to my dismay, that most joystick pots only vary by about 30° at maximum deflection. Consequently, the original circuit for the joystick control, which assumes complete rotation of the joystick pot, will not give the required 5 V swing. The circuit attached will convert a small DC voltage change provided by the joystick into 0-5 V at the output.

Circuit function and setting up is as follows:- RV1 is adjusted so that there is 0 V at the joystick pot wiper. (Note that RV1 and R1 may need to be on the + 5 V side of the joystick pot, depending on the actual pots used in the joystick).

RV2 is then adjusted to give ±2V5 swing at IC1 output with full deflection of the joystick. This voltage is then inverted and gain-controlled by RV3, which is mounted on the joystick plate. IC3 re-inverts IC2's output and RV4 is adjusted to add 2V5 to the output of IC3. The output then becomes a 0-5 V swing, with 2V5 at the centre point.

This control voltage swing is ideal for use in the 4600 synthesiser since 2V5 into the keyboard modulation input gives no variation in pitch, ie the keyboard pitch can be shifted up and down by an amount dependent on RV3. The power for the circuit can be taken directly from the 4600 PSU.

Improved Speaker Overload Indicator

J. Harrold, Bristol


This circuit is based on a design by J. P. Macaulay, which appeared in Electronics Digest Vol. 1. This one offers an improvement in performance, which is low cost and does not introduce an external DC power supply.

Peaks in music can be very short and may be too fast (or dim) to be seen clearly on a LED if held for their duration only. This circuit uses a monostable to hold a LED on for a set time after triggering by a peak in music.

The voltage at the speaker output terminals is rectified and then passed to potential divider R2, R3. ZD1 provides 'last ditch' protection for Q1 and IC1 (this method is not suitable if indication of overloads of greater than 50 W is required). Q1 is used as a voltage variable resistor and with ZD2, series pass transistor Q2 and C1, provides a regulated supply. This supply improves the stability of the 3V9 reference potential at the inverting input of IC1 and also provides a stable supply for IC2 and its timing components R8, C2. C1 cannot be placed between 0 V and the collector of Q2 as this would have an adverse filtering effect on high frequency signals. When the voltage across R2 is less than 3V9, the output from comparator IC1 is low (≃1V5) and this voltage is dropped across forward biased red LED 1 (or alternatively any three silicon diodes in series). Q3 is off and the trigger (pin 2) of IC2 is high. When the voltage across R2 exceeds 3V9, IC1 output goes high and Q3 is turned on, lowering the voltage at IC2 pin 2, triggering the monostable and lighting LED 2 for a period dependent on R8, C2 (about 100 mS with given values). C2 must be a low leakage type (not ceramic). Decoupling of the control voltage (pin 5) by C3 was not necessary in the prototype. R1 protects the amplifier from possible bridge failure. Q1 may be replaced by a fixed resistor appropriate to the input voltage with slight degradation of performance. The value of R3 is given by:

$$R3 = (\sqrt{2PR} - 3.9)\ \text{kilohms},$$

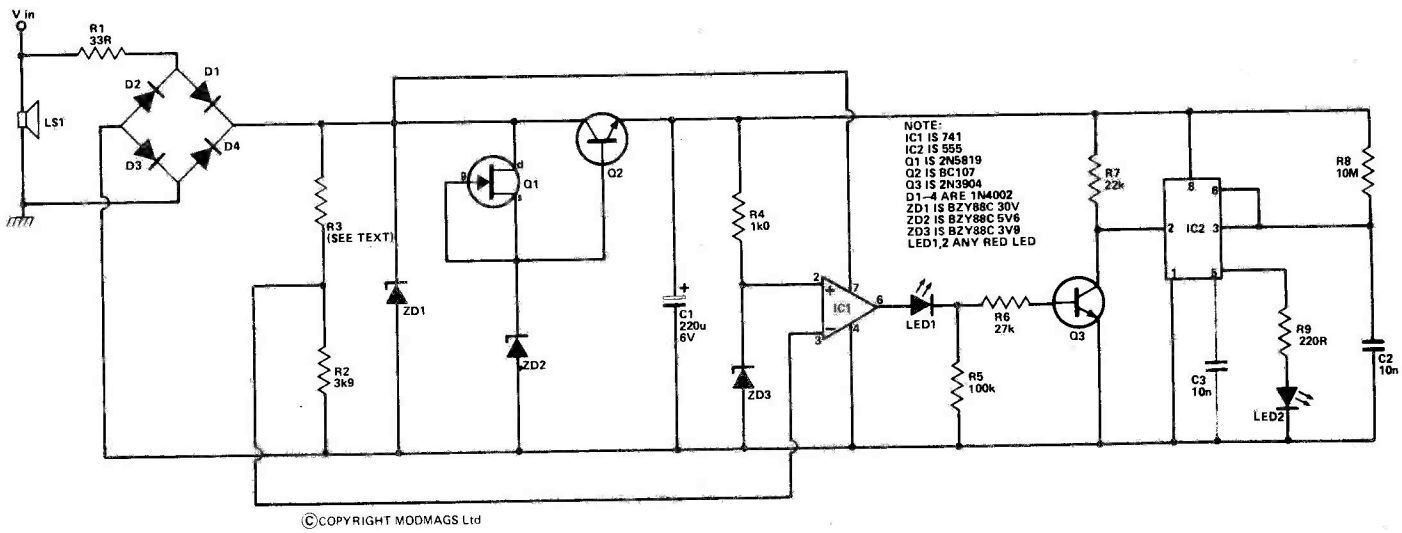where P is the power output and R is the speaker impedance.



©COPYRIGHT MODMAGS Ltd

'Zener-less' Battery Eliminator


P.J. Hunt, Wimborne

Designed as a variable-voltage battery eliminator, this circuit provides a stabilised output without Zener diodes as the reference source. Instead, a V_{be}-multiplier is employed, so that the output voltage may be continuously varied by PR1 over the range 6-10 V.

The V_{be}-multiplier is shown schematically in the inset. Provided that V_{cc} is high enough, the potential across R1 will be about 600 mV for a silicon transistor. The current through R1 can thus be adjusted so that the base current of the transistor may be ignored for practical purposes. In this case, the current through R1 will equal the current through R2. The potential at point A is thus given by:


$$V = V_{be} \times \frac{(R1 + R2)}{R1}$$

— hence the name V_{be}-multiplier.

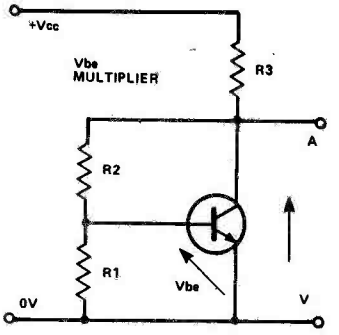


R3 limits the current through the parallel combination of the transistor and R1/R2. Suppose as an example that V_{cc} tries to rise. The potential divider formed by the three resistors will try to raise the voltage across R1. This will tend to increase the collector current and thus increase the potential drop across R3, leading to a stabilising effect at point A. This is a case of voltage-derived series feedback.

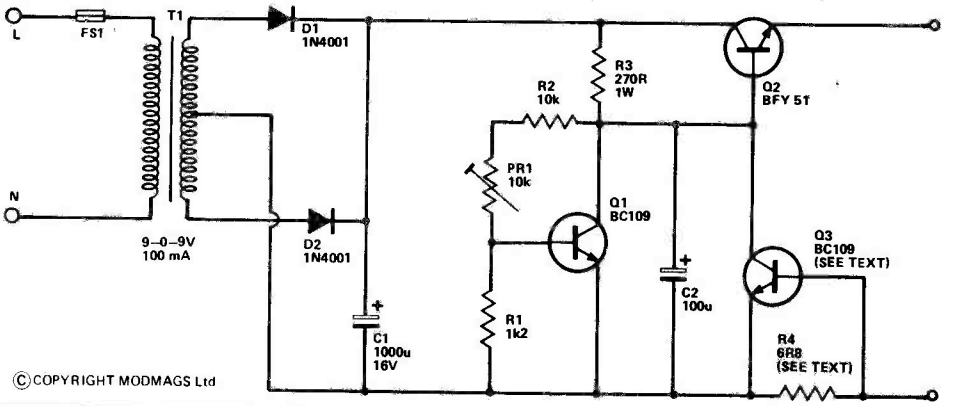In the practical circuit, R3 also provides base current for the series transistor Q2. Q3 and R4 form a current limiter. If the output current exceeds approximately 100 mA, Q3 starts to turn on, reducing the output voltage. If desired, Q3 and R4 may be omitted, in which case R3 may be de-rated to ½ W. The whole unit fits easily inside a PP9 battery case.



©COPYRIGHT MODMAGS Ltd

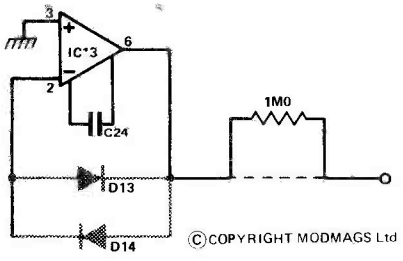


©COPYRIGHT MODMAGS Ltd

Transcendent Pulse Wave Improvement

J.F. Jordan, Cambridge

The pulse wave on the original Transcendent 2000 suffers from a slow falling edge, making LFO modulation of pulse width less effective for chorus sounds and removing the characteristic hollow tone of the square wave.

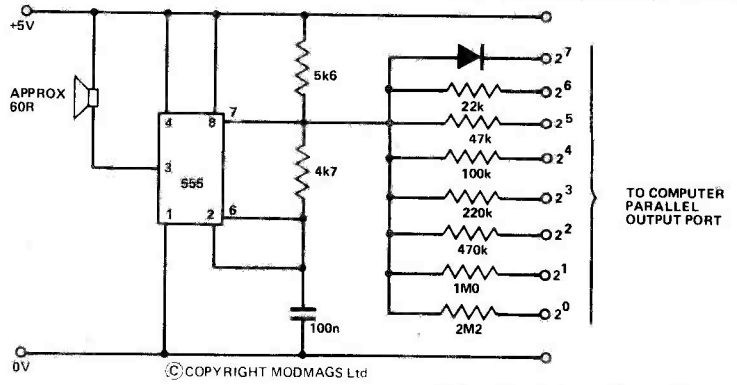This problem can be solved by removing D13 and D14 and inserting a 1M0 resistor across a break in the track from the output of IC13 to SW4. The comparator then operates in open loop mode giving much improved waveform edges.



©COPYRIGHT MODMAGS Ltd

Cheap Micro Music Box

T.M. Tobin, Birmingham


This circuit may be connected to the output port of any micro to generate musical notes over a range of about 1½ octaves. On/off control is provided by the most significant bit and the resistors provide seven bit resolution. Alternative on/off control methods can be used to give eight bit resolution, eg by using the handshake lines, if available.

If the diode is replaced by a resistor, say 10k, it will be found that below a certain output value the voltage at pin 7 is insufficient to charge the capacitor. Thus the sound can be switched off.

The resolution is sufficient to enable values to be found corresponding to tones and semitones throughout the frequency range. Current consumption depends largely on the loudspeaker impedance and is generally low enough for power to be taken directly from the computer. Most constructors will have all the parts required which in any case will cost less than £1.

£395
incl.VAT& P&P

micron

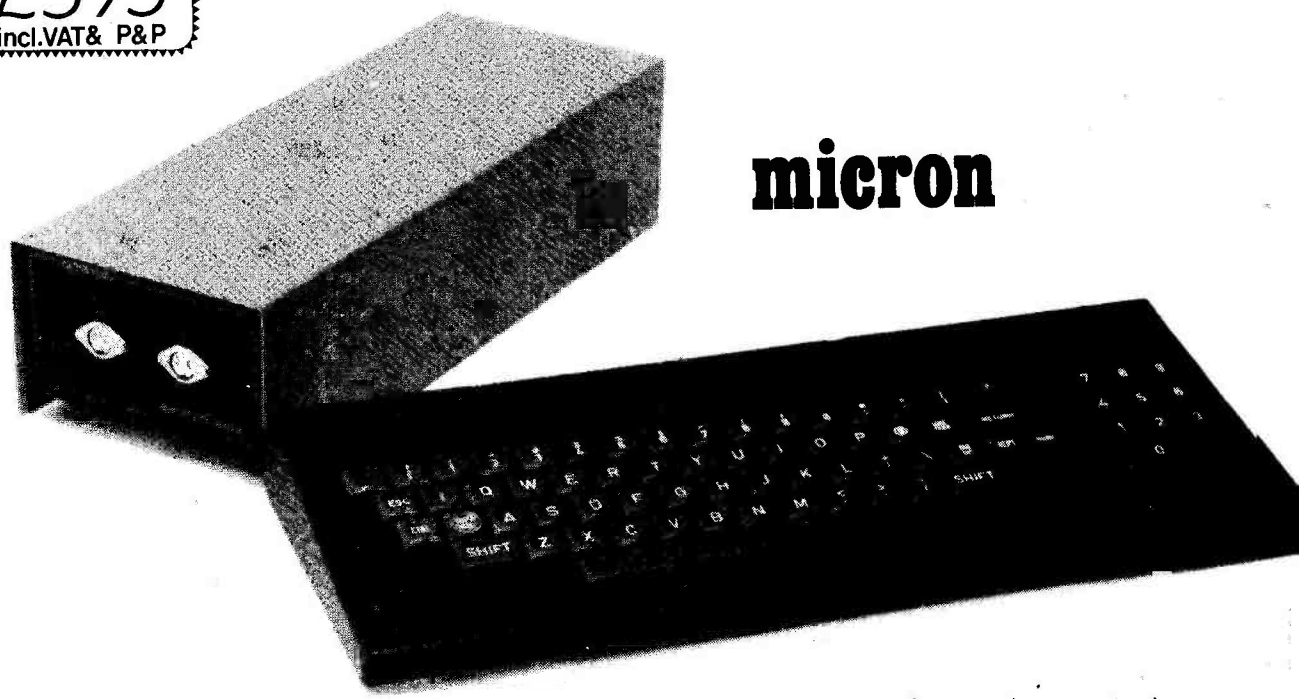

'MICRON' may sound small - but we all know that it's much larger than an atom!

The un-beatable features of Microtan 65 and Tanex have been brought together to give you **Micr** a ready built and tested computer of outstanding value. Fully supported by comprehensive documentati **Micron** represents an ideal starting point in personal computing. We've taken a full O.E.M. lice for Microsoft Basic, which means that you'll have the support of the most popular Basic availab (as used on PET, APPLE, TANDY etc.). If you want to expand **Micron** there's no problem, just move i the system rack and choose from the range of Microtan modules. Read the information, study what magazines have to say about us and compare what we have to offer with other systems, then we f sure that you'll be convinced that we've produced an excellent product.

- FULLY BUILT, TESTED AND CASED.
- 6502 BASED MICROCOMPUTER.
- VDU ALPHA NUMERIC DISPLAY.
- 8K RAM.
- 32 PARALLEL I/O LINES.
- 2 TTL SERIAL I/O LINES.
- 1 SERIAL I/O PORT WITH RS232/20mA LOOP, AND 16 PROGRAMMABLE BAUD RATES.
- 300 / 2400 BAUD FILENAMED CASS. INTERFACE.
- DATA BUS BUFFERING.
- MEMORY MAPPING CONTROL.
- 71 KEY ASCII KEYBOARD, INCLUDING NUMERIC KEYPAD.
- POWER SUPPLY INCLUDED.


SOFTWARE

- 10K EXTENDED MICROSOFT BASIC.
- ALL THE USUAL BASIC COMMANDS.
- INTEGER AND REAL NUMBERS.
- INTEGER AND REAL ARRAYS.
- INTRINSIC FUNCTIONS: ABS, INT, RI SGN, SIN, SQR, TAB, USR, ATN, CO EXP, LOG, TAN.
- USER DEFINED FUNCTIONS.
- READ AND DATA STATEMENTS.
- DUMP AND LOAD PROGRAMS.
- PROGRAM EDITING COMMAND.
- STRING FUNCTION FOR TEXT I/O.
- BASIC CAN CALL MACHINE CODE SUB-ROUTINE.
- USER MACHINE CODE INTERRUPT HAND LER INTERFACES WITH BASIC.
- XBUG.
- DATA CASSETTE FILE HANDLING IN BA

TANGERINE
COMPUTER SYSTEMS LIMITED

Forehill Works
Forehill Ely Cambs England **Tel: (0353)3633**

microtan 65

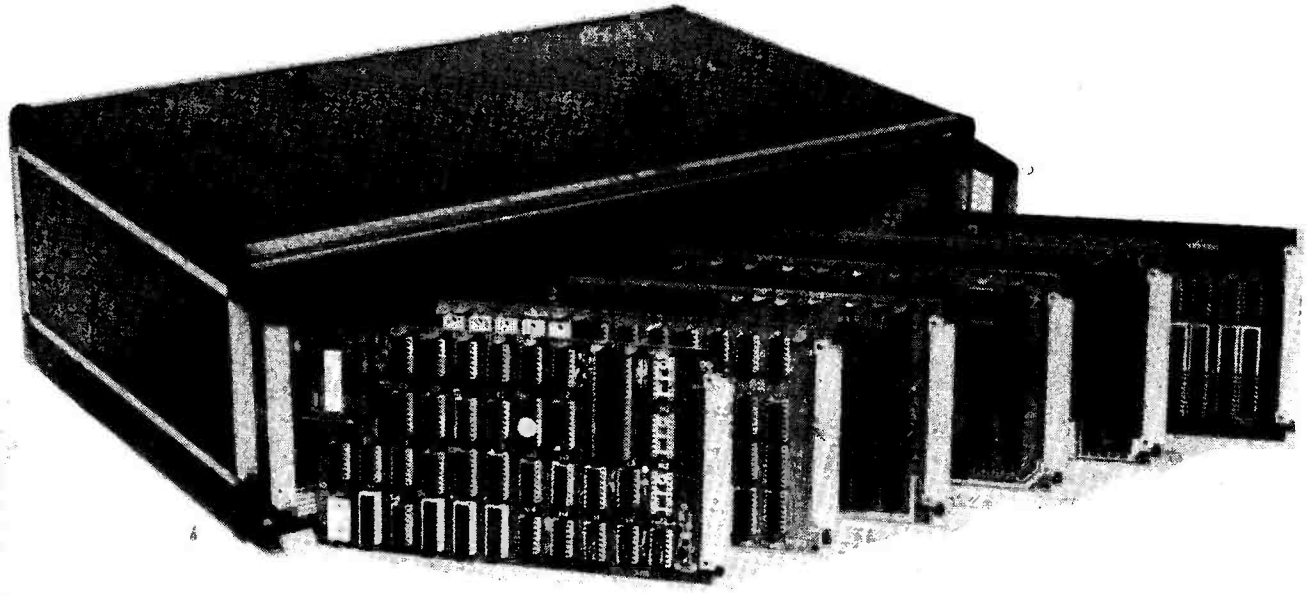

he **Microtan** system is rapidly becoming accepted as the ultimate approach to personal computing. Start ith **Microtan 65**, a 6502 based single board computer, and expand to a powerful system in simple and -expensive stages. The **Microtan** system is a concept and not an afterthought, this means expansion s easy and very efficient! Unlike many other systems, you'll find it difficult to outgrow **Microtan**, nd you won't be wasting your money on a product that will only last you a few months! When you are eady to expand, **Tanex** is waiting. The features offered by **Tanex** are tremendous, and you can start into hem for just £49.45! Cassette interface, 16 I/O lines, two 16 bit counter timers, data bus buffering, emory mapping and a further 1K of RAM are standard. From thereon expansion is simple, just plug in xtra integrated circuits to get yourself 8K of RAM, a further 16 I/O lines and two more counter timers serial I/O line with RS232/20mA loop and full modem control, **XBUG** - a firmware package containing assette file handling routines, plus a line-by-line assembler (translator) and dis-assembler, **PLUS OK EXTENDED MICROSOFT BASIC**, a suped-up version of the Basic as used by major manufacturers such as pple, Tandy and Nascom, **NO OTHER LOW COST MICROCOMPUTER OFFERS YOU THIS SUPERB PACKAGE**. O.K. so you ant more memory, try **Tanram** for size! Upto 40K bytes on one board starting for as little as £50.60. AM freaks will be pleased to hear that our system mother board offers page memory logic which will upport 277K Bytes, satisfied? To house these beautiful modules you can choose between our mini-rack as used on **Micron**), which accepts **Microtan** and **Tanex**, or our system rack pictured above. The system ack will support 12 modules. What are these extra modules? Well for starters there's a couple of I/O odules, parallel and serial offering upto 128 I/O lines organised as 16 8 bit ports and 8 serial I/O orts respectively. Shortly we'll be introducing high definition (256x256) colour graphics, A to D nd D to A modules, IEEE 488 Bus interface, a PROM programmer, disc controller and **TANDOS** - a 6502 CPM ystem. So there's plenty to keep you busy. Send for more details, and find out how you can get started or just £79.35!

ALL PRICES QUOTED INCLUDE V.A.T.

IM 65, KIM 1, SIM 1 USERS- READ ON!

e have produced a T.V. interface module which simply onnects to the expansion socket of your computer and roduces a display of 16 rows by 40 characters! Of even ore interest will be our Buffer module, which allows ou to expand into our system rack, giving you access o the full range of Microtan modules.

Please underline the information required.

AIM T.V. INTERFACE. MICROTAN SYSTEM.


NAME: _____

ADDRESS: _____

_____

PLEASE ENCLOSE 12p STAMP. THANK YOU.

LOW-OHM METER

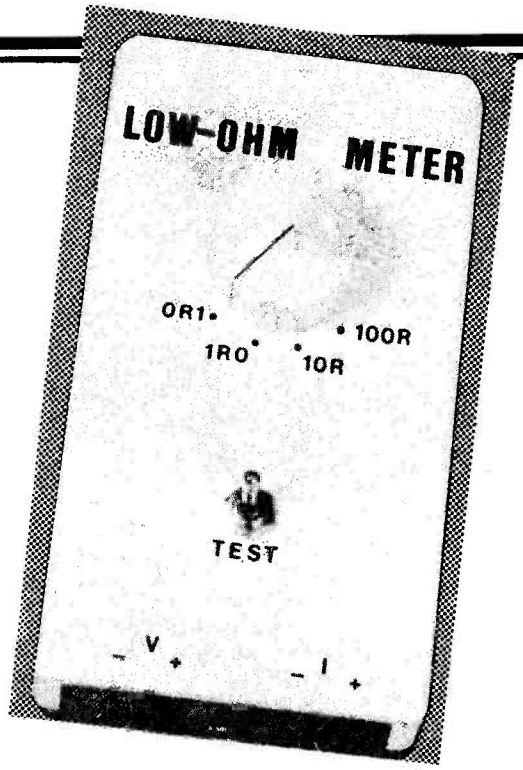


Measure resistances from a hundred ohms down to a few milliohms with this accurate four-range meter. It can be built as a self-contained unit or as an adaptor for use with an existing multimeter. Design and development by Ray Marston.

Ever wanted to measure the resistance of a transformer winding or a suspect solder joint, but found that your trusty multimeter wasn't sensitive enough to do the job? If so, our Low-Ohm Meter will solve your problems. It accurately measures resistances from a hundred ohms down to a few milliohms, in four decade ranges, using a precision four-terminal measuring technique that eliminates the effect of connecting leads, etc, from the readings.

Our Low-Ohm Meter contains two fully independent (and independently powered) circuits, these being a multi-range constant-current generator and a DC millivoltmeter with a full-scale sensitivity of 10 mV. The generator is used to apply a fixed test current to the resistor that is being measured, and the voltmeter is used to measure the resultant voltage that is developed directly across the resistor, indicating the true value of the resistor and ignoring the effects of the test leads. This four terminal measurement technique is widely used in precision calibration laboratories.

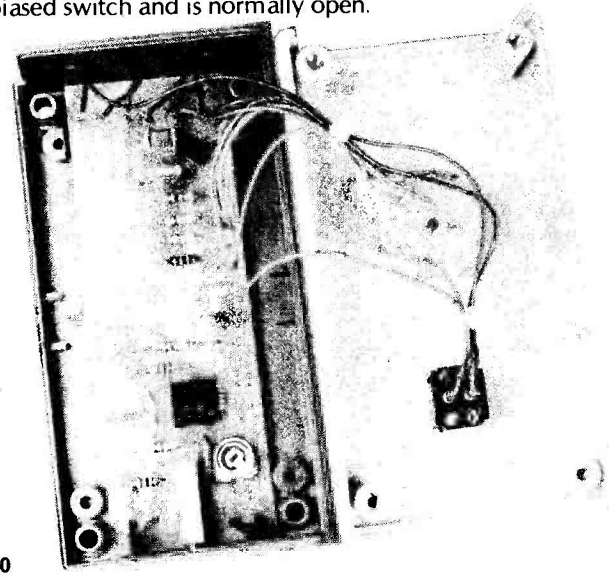The Low-Ohm Meter indicates 100 milliohms (0R1) on its most sensitive range, using a test current of 100 mA. Supply battery B1 must be capable of supplying this current without excessive voltage drop; a PP9 type is recommended. The unit consumes power only when TEST switch SW1 is closed. SW1 is a biased switch and is normally open.



The PCB is mounted so that the cermet preset can be adjusted through a hole in the case.

Construction

The Low-Ohm Meter can be built as either a self-contained unit, with built-in supply batteries and moving coil meter, or as an adaptor unit for use with an existing multimeter. In this latter instance, use a meter set to its 1 V DC range.


Start the construction by assembling the components on the PCB, as shown on the overlay. If your meter or multimeter has a sensitivity of 100 uA (10k/V) or better, give R9 a value of 10k. If the sensitivity is 1 mA (1k0/V) or better, reduce the R9 value to twice the ohms-per-volt value of the meter.

When assembling the components, note that PR2 is a multi-turn 3/4 inch cermet trimmer and that its adjuster spindle overhangs the edge of the PCB; we'll refer to this end of the PCB as the 'front'. Solder four flexible leads to the indicated points at the front of the PCB. Solder Veropins to the other terminal points. Now test-fit the PCB in your chosen case. Drill a small hole in the front of the case, in line with PR2, to accept PR2's spindle and facilitate external 'set zero' adjustments. Drill two additional holes in the case front, to allow passage of the two pairs of 'I' and 'V' leads. You might consider taking the 'I' leads to a pair of quick-connection terminals (push-button loudspeaker type), for easy insertion of the resistor under test. Now drill the top of the case to accept SW1 and SW2 and fit these components into place. Finally, fix the PCB into the case and complete the interwiring to the switches.

Test And Use

When construction is complete, connect the two 9 V batteries to the unit, noting that B1 must be capable of supplying 100 mA, and connect the 'M' terminals to a 1 V DC meter or multimeter. Now short the two 'V' terminals together, close the test switch, and adjust PR2 to obtain a zero reading on the meter.

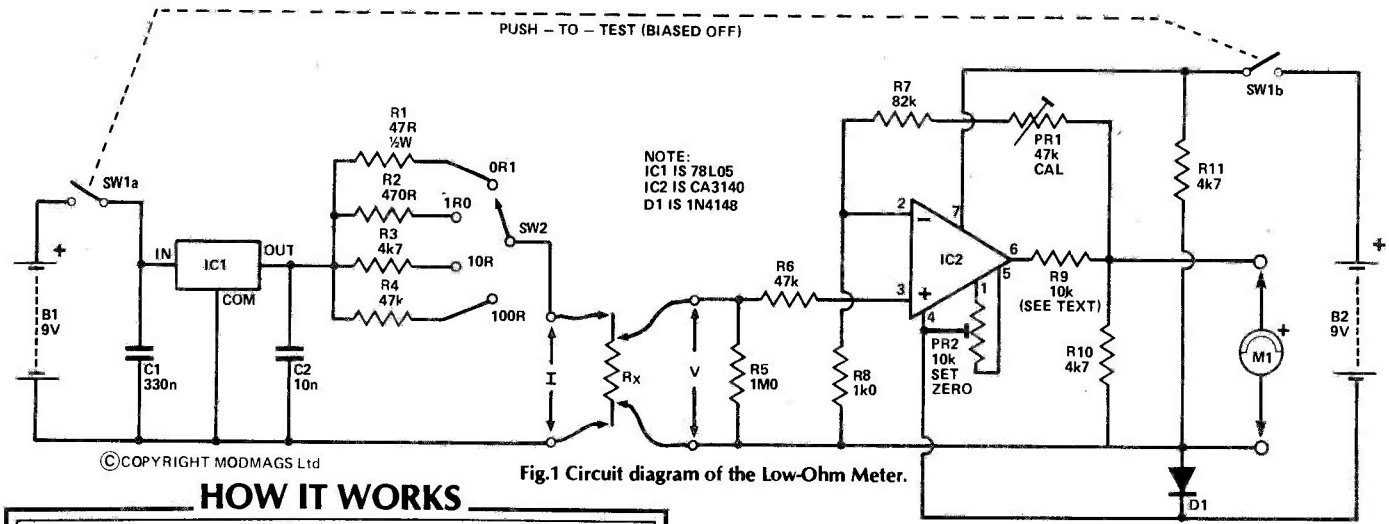Next, turn SW1 to the 100R range and connect a 100R resistor (5% or better) accross the 'I' terminals. Now connect the 'V' terminals across the test resistor (on the resistor side of the 'I' leads), with like polarities to like (+ to +, etc), close the test switch, and adjust PR1 to obtain a full scale reading on the meter. The unit is now calibrated and ready for use.



©COPYRIGHT MODMAGS Ltd

Fig.1 Circuit diagram of the Low-Ohm Meter.

HOW IT WORKS

The constant generator circuit is very simple. IC1 is a 5 V regulator and the output test current (I) is determined by resistor R1 to R4. On each range, the value of the test resistor (Rx) is very low relative to the current-limiting resistor, and the full scale test voltage (10 mV) is very small relative to the 5 volts of the regulator. Consequently, on each range, the test current is virtually independent of the effects of lead resistances, etc: on the most sensitive (100 milliohms) range (I = 100 mA), one ohm of lead resistance will introduce a maximum full-scale error of 2%. A similar lead resistance will introduce an error of only .002% on the 100R (I = 100 uA) range. In practice, therefore, the reading errors are primarily determined by the accuracies of R1 to R4.

The DC millivoltmeter (designed around IC2) is a fairly conventional design. It is based on a CA3140 op-amp, which can respond to DC inputs down to zero volts. To enable the output to go slightly negative (for zero-setting purposes), a −600 mV supply rail is generated by R11 and D1. Resistor R9 is used to limit the maximum voltage to the meter to about 2 V, to eliminate the possibility of meter damage if the unit is incorrectly ranged. The sensitivity of the meter is variable over a limited range by PR1, for calibration purposes (to compensate for test-current errors).

PARTS LIST

Resistors (¼ W 5%, unless otherwise stated)	
R1	47R ½W
R2	470R
R3, 10, 11	4k7
R4,6	47k
R5	1M0
R7	82k
R8	1k0
R9	10k
Potentiometers	
PR1	47k miniature horizontal preset
PR2	10k ¾ inch cermet multiturn preset
Capacitors	
C1	330n polycarbonate
C2	10n polycarbonate
Semiconductors	
IC1	78L05
IC2	CA3140
D1	1N4148
Miscellaneous	
SW1	Miniature 2-pole biased toggle (normally off)
SW2	1-pole 4-way rotary switch
M1	Moving coil meter, 1 V FSD, sensitivity 100 uA or better.
Case, quick-connection terminals.	

BUYLINES

Absolutely no problems here: all components are readily available

When using the unit, note that the 'I' terminals supply a test current to the resistor being measured, and that the 'V' terminals indicate the voltage developed directly across the resistor. The 'V' terminals must therefore always be connected to the resistor 'inside' the 'I' leads, as indicated by the circuit diagram. When using the meter on its most sensitive (0R1) range, the 'I' leads should be kept as short as possible: on this range, 1R0 of lead resistance will introduce a maximum reading error of 2% on a 100 milliohm test resistance.

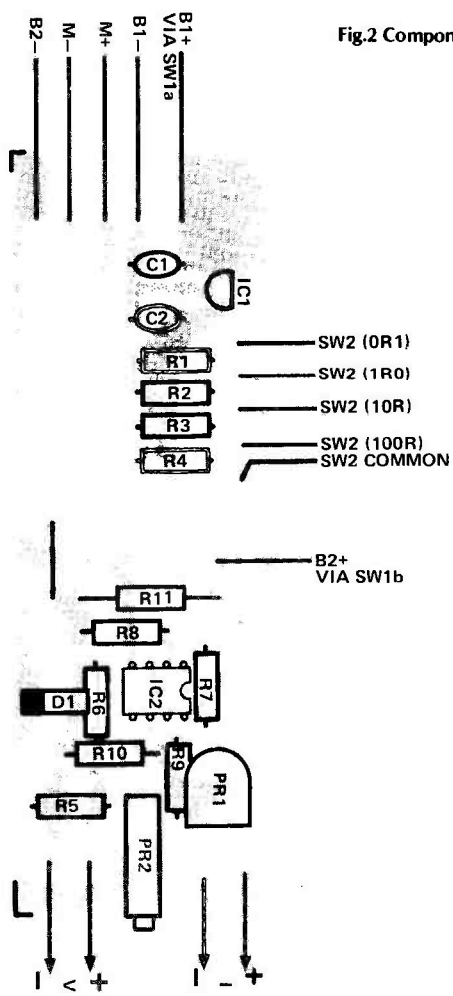


Fig.2 Component overlay.

ETI

ELECTRO SUPPLIES

TRANSISTORS

BC107	10p	BC237	12p	BF194	12p	BF595	30p	2N3055	45p
BC108	10p	BC337	15p	BF195	12p	BFR40	25p	2N3583	60p
BC109	10p	BC547	10p	BF197	14p	BFY90	50p	2N3702	10p
BC125B	8p	BD238	40p	BF245	30p	BUW81A	200p	2N3705	10p
BC149	10p	BD239	40p	BF256A	40p	MJE340AT	50p	2N3710	10p
BC154	12p	BD371A	30p	BF324	30p	MPF131	25p	2N4061	15p
BC159	9p	BDX94	65p	BF469	65p	MPF132	25p	2N4123	10p
BC171	10p	BDY92	120p	BF495	20p	MPU131	25p	2N4125	12p

LINEAR ICs

CA3012	45p	MC1349	90p	TAA320	40p	TDA0470			
CA3080	50p	MC1350	90p	TBA120S	60p	TDA1010	150p	SPECIAL OFFER	
LM324	60p	MC1558	100p	TBA651	100p	TDA1170	75p	AY-5-3507 DVM	
LM741	15p	NE535T	50p	TBA661B	125p	TDA1190	200p	CHIP (with data)	
LM1458	40p	NE555	22p	TBA800	70p	TDA2524	150p	£2.75p (limited	
LM3900	60p	SAJ110A		TBAB10S	80p	TDA2541	150p	quantity).	
MC1307	75p	SAS560	100p	TBA920	150p	TDA2560	150p		
MC1310	100p	SAS590	100p	TCA270S	90p	TDA2581	175p		

LOW PROFILE IC SOCKETS

14 pin — 12 ..... **100** (150 **£10**)
16 pin — 10 ..... **100** (130 **£10**)
22 pin — 7 ..... **100** (100 **£10**)
24 pin — 6 ..... **100** (70 **£10**)
40 pin — 3 ..... **100** (40 **£10**)

For larger quantities please phone for prices

35-amp 50-volt Stud Diodes, c/w mounting kit **4 £1**

Semi-conductor Packs. Diodes/Transistors/SCRs/ICs, over 100 items (no rejects) ..... **£1.50** each, two for **£2**

SPECIAL OFFERS

LM1101N (DOLBY B I/C)..... **£2.50**
TDA2020 (20 watt amp)..... **£2.50**
MM57105 (PAL colour TV game I/C)..... **£2.00**
MM53100N (TV clock timer) **£2.00**
AY-5-1013 (UART)..... **£2.00**

Prices include VAT, please add 50p P&P

MAIL ORDER DEPT.
(Callers please phone first)
BOWNESS MILL, SHAWCLOUGH RD
WATERFOOT, ROSSENDALE, LANCS
TEL: ROSSENDALE 5556

RETAIL SHOP
(Open 6 days)
6A TODD ST
MANCHESTER
(next to Victoria Stn.)
TEL: 061-834 1185

Counter Intelligence



Only £129-95 plus VAT

High precision, performance, reliability at a very low price. The HFC 60 high frequency counter is based on the very latest LSI technology.

- Bright 8 digit 0.5" LED display.
- Mains input for normal use.
- DC power input, 9–16 volts, for mobile use.
- Tough anodised metal case, neat tilt legs.
- Model HFC 60 – £129.95 plus VAT (60 Mhz).
- Model HFC 600 with high gain X10 UHF pre-scaler extends operation to full 600 Mhz – £159.95 plus VAT.
- Proportional temperature controlled crystal oven available for both models. Supplied fitted or as easy 'add on' £30 extra plus VAT.

Get full details on these and our other models now. Why pay more?

DRALLIM

DRALLIM DAVIS ELECTRONICS LTD
Brett Drive, Bexhill-on-Sea, East Sussex TN40 2JR Telephone (0424) 216611 Telex 95285
Agency enquiries invited.

ELECTRONIC GAMES

ATARI



SPECIAL PRICE

£86 + VAT

INTELLIVISION MATTEL



This is the most advanced TV game in the world. Expandable this year into a full microcomputer. COLOUR CATALOGUE AVAILABLE WITH DETAILS ON ALL THE CARTRIDGES

£173.87 + VAT

CHESS COMPUTERS



NEW RANGE AVAILABLE AUGUST 1980
We specialise in computer chess machines & stock over 13 different models from £20 to £300

Send for further details.

TELETEXT



RADOFIN TELETEXT Add on Adaptor

£173 + VAT

BRIDGE COMPUTER



- ★ Plays 1/2/3 or 4 Hands
- ★ Problem Mode
- ★ Audio Feedback
- ★ Instant Response
- ★ Auto scorekeeping

BACKGAMMON COMPUTERS



OMAR 1
OMAR 2
CHALLENGER
GAMMONMASTER

From £38 to £108. Send for further details.

SPACE INVADERS




HAND HELDS + CARTRIDGES
ATARI · ACETRONIC
PRINZTRONIC
RADOFIN · DATABASE etc.

We keep a full range!
Send for cartridge lists stating which machine you own.

24-TUNE DOOR BELL £13.65 + VAT



DRAUGHTS COMPUTER

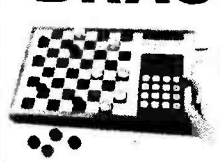

- ★ Solves Problems
- ★ Rejects illegal moves

2 level machine
£43 + VAT
4 level machine
£77.78 + VAT

LEISURE

- ★ CHEAP TV GAMES
- ★ TELEPHONE ANSWERING MACHINES
- ★ AUTO DIALLERS
- ★ CALCULATORS
- ★ DIGITAL WATCHES
- ★ PRESTEL
- ★ HAND HELD GAMES

FREE CATALOGUE
For a free copy of our 32 page catalogue, send a 12p stamp to Silica Shop Ltd or Telephone 01-301 1111

MAIL ORDER SERVICE – Free postage & Packing
TELEPHONE & MAIL ORDERS - accepted on:
Access ★ Barclaycard ★ American Express ★ Diners Club
CALLERS WELCOME – at our shop in Sidcup – Demonstrations daily
Open from 9am-5pm Mon -Sat. (9am-1pm Wed.)
GUARANTEE – Full 12 months + After Sales Support!

SILICA SHOP
SILICA SHOP LTD., Dept. ETI 4
1-4 The Mews, Hatherley Road
Sidcup, Kent, DA14 4DX
Tel: 01-301 1111

We have comprehensive brochures on all products. Please let us know what you are interested in and we will send you detailed brochures AND our over 32 page catalogue covering most games on the market.

AND THERE'S MORE WHERE THIS CAME FROM

It's a long time since one of our adverts was presented in 'list' form - but simply because we do not try to squeeze this lot in every time doesn't mean that it's not available. Our new style price list (now some 40 pages long) includes all this and more, including quantity prices and a brief description. The kits, modules and specialized RF components - such as TOKO coils, filters etc. are covered in the general price list - so send now for a free copy (with an SAE please). Part 4 of the catalogue is due out now (incorporating a revised version of pt.1).

LINEAR ICs - NUMERIC LISTINGS

TBA120S	1.00	KB4413	1.95
L200	1.95	KB4417	1.80
U237B	1.28	TDA4420	2.25
U247B	1.28	KB4420B	1.09
U257B	1.28	KB4423	2.30
U267B	1.28	KB4424	1.65
LM301H	0.67	KB4431	1.95
LM301N	0.30	KB4432	1.95
LM308H	0.96	KB4433	1.52
LM308N	0.65	KB4436	2.53
LM339N	0.66	KB4437	1.75
LM348N	1.86	KB4438	2.22
LF351N	0.38	KB4441	1.35
LF353N	0.76	KB4445	1.29
LM374N	3.75	KB4446	2.75
LM380N-14	1.00	KB4448	1.65
LM380N-8	1.00	NE5044N	2.26
LM381N	1.81	NE5532N	1.85
ZN419CE	1.95	SD6000	3.75
NE544N	1.80	SL6270	2.03
NE555N	0.30	SL6310	2.03
NE556N	0.50	SL6600	3.75
NE560N	3.50	SL6640	2.75
NE562N	4.05	SL6690	3.20
NE564N	4.29	SL6700	2.35
NE565N	1.00	ICL8038CC	4.50
NE566N	1.60	MSL9362	1.75
NE570N	3.85	MSL9363	1.75
SL624	3.28	HAI1211	1.95
TBA651	1.81	HAI1223	2.15
uA709HC	0.64	HAI1225	1.45
uA709PC	0.36	HAI2002	1.45
uA710HC	0.65	HAI2017	0.80
uA710PC	0.59	HAI2402	1.95
uA741CH	0.66	HAI2411	1.20
uA741CN	0.27	HAI2412	1.55
uA747CN	0.70	LF13741	0.33
uA748CN	0.36	SN76660N	0.80
uA753	2.44		
uA758	2.35		
TBA810AS	1.09		
TBA820M	0.75		
TCA940E	1.80		
TDA1028	2.11		
TDA1029	2.11		
TDA1054	1.45		
TDA1062	1.95		
TDA1072	2.69		
TDA1074A	5.04		
TDA1083	1.95		
TDA1090	3.05		
HAI137	1.20		
HAI196	2.00		
HAI197	1.00		
TDA1220	1.40		
LM1303	0.99		
LM1307	1.55		
MC1310P	1.90		
MC1330	1.20		
MC1350	1.20		
HAI370	1.90		
HAI388	2.75		
TDA1490	1.86		
MC1496P	1.25		
SLI610P	1.60		
SLI611P	1.60		
SLI612P	1.60		
SLI613P	1.89		
SLI620P	2.17		
SLI621P	2.17		
SLI623P	2.24		
SL624C	3.28		
SLI625P	2.17		
SLI626P	2.44		
SLI630P	1.62		
SLI640P	1.89		
SLI641P	1.89		
TDA2002	1.25		
TDA2020	3.00		
ULN2242A	3.05		
ULN2283B	1.00		
CA3080E	0.70		
CA3089E	1.84		
CA3090AQ	3.35		
CA3123E	1.40		
CA3130E	0.80		
CA3130T	0.90		
CA3140E	0.46		
CA3189E	2.20		
MC3357P	2.35		
LM3900N	0.60		
LM3909N	0.68		
LM3914N	2.80		
LM3915N	2.80		
KB4400	0.80		
KB4406	0.60		
KB4412	1.95		

FREQUENCY DISPLAY & SYNTHESISER ICs

SAA1056	3.75
SAA1058	3.35
SAA1059	3.35
11C90DC	14.00
LN1232	19.00
LN1242	19.00
MSL2318	3.84
MSM5523	11.30
MSM5524	11.30
MSM5525	7.85
MSM5526	7.85
MSM5527	9.75
MSM55271	9.75
ICM7106CP	9.55
ICM7107CP	9.55
ICM7216B	19.25
ICM7217A	9.50
SP8629	3.85
SP8647	6.00
95H90PC	6.00
HD10551	2.45
HD44015	4.45
HD12009	6.00
HD44752	8.00

CMOS 4000 SERIES

4001	0.17
4000	0.17
4002	0.23
4008	0.80
4009	0.58
4010B	0.58
4011AE	0.20
4011B	0.20
4012	0.55
4013	0.55
4015	0.95
4016	0.52
4017	0.80
4019	0.60
4020B	0.93
4021	0.82
4022	0.90
4023	0.17
4024	0.76
4025	0.17
4026	1.80
4028	0.72
4029	1.00
4030	0.58
4035	1.20
4040	0.83
4042	0.85

TTL N and LSN

7400N	0.13	7443N	1.15	74LS112	0.38	74LS169	2.00
74LS00	0.20	7444N	1.12	74LS113	0.38	74170N	2.30
74LS01	0.20	7445N	0.94	74LS114	0.38	74LS170	2.00
74LS02	0.20	7446N	0.94	74118N	0.83	74LS174	1.20
7403N	0.14	74LS47	0.89	74120N	1.15	74175N	0.87
74LS03	0.20	7448N	0.56	74121N	0.42	74LS175	1.10
7404N	0.14	74LS48	0.99	74122N	0.46	74176N	0.75
74LS04	0.24	74LS49	0.99	74123N	0.73	74177N	0.78
7405N	0.18	74LS54	0.24	74LS124	1.75	74181N	1.65
74LS05	0.26	74LS55	0.24	74125N	0.38	74LS181	3.50
7406N	0.28	7460N	0.17	74LS125	0.44	74LS183	2.10
7407N	0.38	74LS63	1.24	74126N	0.57	74184N	1.35
7408N	0.17	7470N	0.28	74LS126	0.44	74185N	1.34
74LS08	0.24	7472N	0.28	74128N	0.74	74LS190	0.92
7409N	0.17	7473N	0.32	74132N	0.73	74192N	1.05
74LS09	0.24	74LS73	0.38	74LS132	0.78	74LS192	1.80
7410N	0.15	7474N	0.27	74LS136	0.40	74193N	1.05
74LS10	0.24	74LS74	0.28	74LS138	0.60	74LS193	1.80
7411N	0.20	7475N	0.38	74141N	0.56	74194N	1.05
74LS11	0.24	7476N	0.37	74142N	2.65	74196N	0.99
7412N	0.17	74LS76	0.38	74143N	3.12	74LS196	1.10
7413N	0.30	74LS78	0.38	74144N	3.12	74LS197	1.10
7414N	0.51	7480N	0.48	74LS145	0.97	74198N	1.50
74LS15	0.24	7481N	0.86	74147N	1.75	74199N	1.60
7416N	0.30	7482N	0.69	74148N	1.09	74LS247	0.93
7417N	0.30	7485N	1.04	74LS148	1.19	74LS257	1.08
7420N	0.16	74LS85	0.99	74150N	0.99	74LS260	1.53
74LS20	0.24	74LS86	0.40	74151N	0.55	74LS279	0.52
7421N	0.29	7489N	2.05	74LS151	0.84	74LS283	1.20
74LS21	0.24	7490N	0.33	74153N	0.64	74LS293	0.95
7423N	0.27	74LS90	0.90	74LS153	0.54	74LS365	0.49
7425N	0.27	7491N	0.76	74154N	0.96	74LS366	0.49
7427N	0.27	74LS91	1.10	74155N	0.54	74LS367	0.43
74LS27	0.44	7492N	0.38	74LS155	1.10	74LS368	0.49
7428N	0.35	74LS92	0.78	74156N	0.80	74LS374	1.80
74LS28	0.32	7493N	0.32	74157N	0.67	74LS377	1.95
7430N	0.17	74LS93	0.99	74LS157	0.55	74LS379	1.30
74LS30	0.24	7494N	0.78	74LS158	0.60	74LS393	1.40
7432N	0.25	7495N	0.65	74159N	2.10		
74LS32	0.24	74LS95	1.14	74160N	0.82		
7437N	0.40	7496N	0.58	74LS160	1.30		
7438N	0.33	74LS96	1.20	74161N	0.92		
74LS38	0.24	7497N	1.85	74LS161	0.78		
7440N	0.17	74LS107	0.38	74LS162	1.30		
74LS40	0.24	74109N	0.63	7416 3N	0.92		
7441N	0.74	74LS109	0.70	74LS163	0.78		
7442N	0.70	74110N	0.54	74164N	1.04		
74LS42	0.99	74111N	0.68	74LS164	1.30		
				74165N	1.05		
				74LS165	1.04		
				74167N	2.50		

4043	0.85
4044	0.80
4046	1.30
4047	0.99
4049	0.52
4050	0.55
4051	0.65
4052	0.65
4053	0.65
4063	1.09
4066	0.56
4068	0.25
4069	0.20
4070	0.20
4071	0.20
4072	0.20
4073	0.20
4075	0.20
4076	0.90
4077	0.20
4078	0.20
4082	0.20
4093	0.78
4175	0.95
4503	0.69
4506	0.51
4510	0.99
4511	1.49
4512	0.98
4514	2.55
4518	1.03
4520	1.09
4521	2.36
4522	1.49
4529	1.41
4539	1.10
4549	3.50
4554	1.53
4560	2.18
4566	1.59
4568	2.18
4569	3.03
4572	0.30
4585	1.10

VOLTAGE REGULATORS

78series	0.95
79series	1.00
78Mseries	0.65
78Lseries	0.35
79L05	0.85
78MGT2C	1.75
79MGT2C	1.75
723CN	0.65
L200	1.95
TDA1412	0.75
NE5553N	1.25
LM317MP	1.48
LM337MP	1.48

MICROMARKET

8080A/2	7.50
8212	2.30
8214	3.50
8216	1.95
8224	3.50
8251	6.25
8255	5.40
6800P	7.50
6810	5.95
6820	7.45
6850	4.90
6852	4.85
MC2708	7.50
2114	6.50
4027	5.78
2102	1.70
2112	3.40
2513	7.54
HM4716	4.50
81LS97	1.25

CRYSTAL FILTER PRODUCTS

10.7MHz 2 POLE TYPES:	
10M15A 15KHz BW	2.49
10.7MHz 8 POLE TYPES:	
10M4B1 15kHz BW	14.50
H4402 7.5KHz BW	15.50
10M22D 2.4KHz SSB	17.20
HF FIRST FILTER:	
B34F8A 34.5MHz HF	32.00

RADIO CONTROL CRYSTALS

(No splits available)

AM TX:-	
3rd OT 30pF HC25U	1.65
AM/FM RX:-	
3rd OT 30pF HC25U	1.65
FM TX :-	
Fund 20pF HC25U	1.85
Pairs FM	3.25
Pairs AM	3.10

CRYSTALS

32.768 kHz	2.70
100kHz	3.85
455kHz	5.00
1.0MHz	3.00
3.2768MHz	2.70
4.000MHz	2.00
4.19439MHz	2.30
6.5536MHz	2.10
10.0MHz	2.50
10.6985MHz	2.50
10.7015MHz	2.50
10.245MHz	2.50
10.7MHz	3.00
11.52MHz	2.50
100MHz	3.00

TOKO COILS AND FILTERS

SEE THE EXTENSIVE SECTION IN OUR NEW PRICE LISTS AND CATALOGUE

LF/HF FIXED INDUCTORS - FULL E12 RANGE

7BA series 1uH-1mH	0.16
8RB series 100uH-33mH	0.19
10RB series 33mH-120mH	0.33
10RBH series 120mH-1.5H	0.55
PIEZO SOUNDER PB2720	0.44

LEDs

5MM RED	0.12
3MM RED CLEAR	0.15
3MM RED	0.15
2.5 X 5MM RED	0.17
5MM GREEN	0.15
3MM GN CLEAR	0.16
3MM GREEN	0.16
2.5 X 5MM GN	0.20
5MM YELLOW	0.15
3MM YELLOW CL	0.16
3MM YELLOW	0.18
2.5 X 5MM YE	0.20
5MM ORANGERED	0.20
5MM ORA CL	0.29
3MM ORANGERED	0.19
2.5 X 5MM ORA	0.24
5MM INFRA RED	0.56
BPW41 IR DET	1.51
IR OPT CPLR	1.44
5MM CLIP	0.04

LCDs

3.5 digit	9.45
4 digit	8.95
5 digit	8.95

SCHOTTKY DIODE BAL MIXERS (SBL1=MD108)

SBL1 1-500MHz	4.25
SBL1-8 .1-200MHz	4.55
SBL1-X 10-1000MHz	5.75
SRA1 .5-500MHz	8.45
SRA1-1 .1-500MHz	9.25
SRA1H .5-500MHz	13.35
SRA3 .025-200MHz	10.25

VARICAP TUNING DIODES

BA102	0.30
BA121	0.30
ITT210	0.30
BB204B	0.36
BB105B	0.36
BB109	0.27
MVM125	1.05
BB212	1.95
KV1210	2.45
KV1211	1.75
KV1226	1.95
KV1225	2.75
KV1215	2.55
KV1225	2.75

SWITCHING AND PIN DIODES

SHOTTKY DIODES

1N6263	0.62
BA182	0.19
BA244	0.17
BA379	0.35
TDA1061	0.95

SIGNAL DIODES & RECTIFIERS

1N4148	0.06
1N4001	0.06
1N4002	0.07
1N5402	0.15
OA91	0.07
AA112	0.25
BRIDGES:	
1A/50V	0.35
6A/200V	0.75

TRANSISTORS AUDIO DEVICES

BC237	0.08
BC238	0.08
BC239	0.08
BC307	0.08
BC308	0.08
BC309	0.08
BC413	0.10
BC414	0.11
BC415	0.07
BC416	0.08
BC546	0.12
BC556	0.12
BC550	0.12
BC560	0.12
BC639	0.22
BC640	0.23
2SC1775	0.18
2SA872A	0.14
2SD666A	0.30
2SB646A	0.30
2SD668A	0.40
2SB648A	0.40
2SD760	0.45
2SB720	0.45
2SC2546	0.19
2SA1084	0.20
2SC2547	0.19
2SA1085	0.20

AUDIO POWER DEVICES

2SB753	2.34
2SB723	2.34
2SK133	3.00
2SJ 48	3.00
2SK134	3.10
2SK135	3.75
2SJ 50	3.75
BD535	0.52
BD536	0.52
BD377	0.33
BD378	0.33
BD165	0.30
BD166	0.31

SMALL SIGNAL RF DEVICES

BF194	0.18
BF195	0.18
BF224	0.22
BF241	0.18
BF274	0.18
BF440	0.21
BF441	0.21
BF362	0.49
BF395	0.18
BF479	0.66
BF679S	0.55
BFR91	1.33
BFW92	0.60
BFT95	0.99
BFY90	0.90
40238	0.85

RF POWER DEVICES

VN66AF	0.95
2N3866	0.85

SMALL SIGNAL RF FET/MOSFET

BF256	0.38
2SK55	0.28
2SK168	0.35
J310	0.69
J176	0.65
40823	0.65
40673	3SK51
3SK45	0.49
3SK51	0.54
3SK60	0.58
MEM680	0.75
BF961	0.70
BF960	1.24
3SK48	1.64

LCD Module

CM161. Miniature clock, 12/24 hr., alarm, day, date, backlight. All for.....9.95

CAPACITORS

All 5mm or less spacing

CERAMIC 50v
2P2, 3P3, 4P7, 6P8
8P2, 10P, 15P, 18P..0.04
22P, 27P, 33P, 47P
56P, 68P, 82P, 100P..0.05
150P, 220P, 270P
330P, 390P, 470P...0.055
1N0, 2N2, 3N3, 4N7..0.06
10N (0.01uF).....0.05
22N, 47N.....0.06
100N, 220N.....0.09

MONOLITHIC CERAMIC
10N, 100N.....0.16

FEEDTHRU
1N0 SOLDER IN....0.09

POLYESTER (SIEMENS)
10mm LEAD SPACING
10N, 22N, 33N.....0.17
47N, 68N, 100N.....0.19
220N, 470N.....0.22
1uF.....0.29

POLYESTER (GENERAL)
10mm LEAD SPACING
10N, 15N, 22N, 33N..0.06
47N, 68N, 100N.....0.08
220N.....0.11
20mm LEAD SPACING
220N, 330N, 470N...0.18

MYLAR
5mm LEAD SPACING
1N0, 10N, 22N, 33N..0.08
100N.....0.09
20mm LEAD SPACING
220N, 470N..... 0.17

POLYSTYRENE
10P, 15P, 18P, 22P,
27P, 47P, 56P, 68P..0.08
100P, 180P, 220P,
270P, 330P, 390P...0.09
470P, 680P, 820P...0.10
1N0, 1N2, 1N5, 1N8..0.11
2N2, 2N7, 3N3, 3N9..0.12
4N7, 5N6, 6N8, 10N..0.13

TANTALUM BEAD CAPS
16v: 0.22, 0.33,
0.68, 1.0.....0.18
16v: 2.2, 4.7, 10..0.19
6v3: 22, 47.....0.30
10v: 22, 100.....0.35

ALUMIN ELECTROLYTICS RADIAL (VERT. MOUNT)

(uF/voltage)
1/63, 2.2/50, 4.7/35
10/16, 15/16, 22/10
33/6.3.....0.08
22/16, 33/10,
47/10.....0.09
10/63, 22/50, 33/50,
47/16, 100/16.....0.10
47/63, 100/25, 220/16
470/6.3.....0.12
100/63, 470/16,
1000/10.....0.18
1000/16, 470/63...0.23
1000/63, 2200/16..0.30
3300/25.....0.69
1000/100.....0.88
10000/70.....3.00

AXIAL (HORIZ. MOUNT)
1/25, 4.7/16, 6.4/25
10/16.....0.08
4.7/63, 22/10, 22/16
33/16.....0.09
47/25, 100/16.....0.10
100/25.....0.11
1000/16.....0.25
2200/16, 1000/25..0.36
1000/35, 4700/16..0.45
1000/50.....0.58

RESISTORS

0.25W, 5% E12 CARBON
1ohm-10M.....0.02
0.25W 1% E12 METAL FILM
1.1ohm-1M.....0.05

HORIZ CARBON PRESETS
10mm TYPE
100ohms-2M5.....0.12

HORIZ CERMET PRESETS
1k, 10k.....0.27

Please send an SAE with all enquiries. Access/Barclaycd (min £5 please) Callers welcome

PRICES EXCLUDE VAT - PLEASE ADD 15%* Postage 35p per order. CWO please. (*UK only)

CWO PLEASE : Commercial MA terms on application Goods are offered subject to availability, prices subject to change - so please phone and check if in doubt.

CATALOGUES 2 & 3....60p ea 4.....75p (4 inc. rev. of part 1)


ALL PARTS : .....£1.75.....

ambit INTERNATIONAL

200 North Service Road, Brentwood, Essex

TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

PICKUP PRINCIPLES

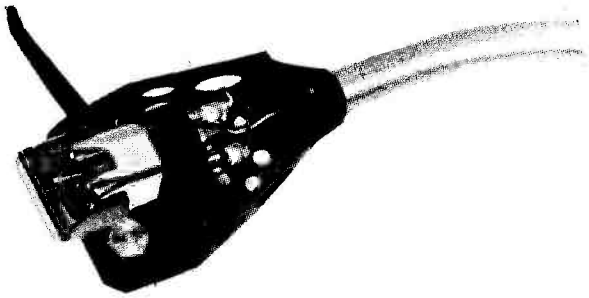



There have been many features on hi-fi in ETI. We have pondered preamplifiers. We have looked at loudspeakers. We have tested turntables. And now — Ron Harris gives you the needle!

The pickup cartridge is the smallest and most oft overlooked component in the hi-fi chain. Much debate has taken place of late as to the what, which and how of turntables and amplifiers. Speakers have also had their day in the centre of the stage, but cartridges — apart from the resurgence of the moving coil a few years back — have simply and quietly gone from strength to strength. Companies such as Goldring, Shure, Ortofon and Empire have continued to add more art to the science of music reproduction without always receiving due attention or accolade.

There have been many variations on the pickup theme. Such divergences as the electret/capacitive cartridge and the almost universal (cheap and cheerful!) piezo-electric are still for sale in most emporiums, but are of little importance to the main hi-fi market. Two main systems dominate; moving magnet and moving coil.

Both are based upon Faraday's laws of electromagnetic induction, which can be briefly, if a little impolitely, summed up as stating that if you move a magnet around anywhere near a coil of wire, you will cause a voltage to appear across that coil. The voltage will bear a direct relationship to the movement.

Elements Of Generation

Before moving on to a consideration of the important parameters and how they affect performance, let's take a look at how each of the systems work:-

1/ Moving Magnet And Induced Magnet

Figure 1 shows a very generalised view of a moving magnet cartridge. Figure 1a shows the relationship of magnet to record groove and the position of the pole pieces. Axis A allows the two drawings to be related.

As the stylus follows the groove wall the magnet transcribes a similar path, parallel to PR and at varying distance from PL. A voltage is thus generated in the coil which is directly related to the groove information.

All cartridges must be well shielded from external fields generated by such as mains transformers, as the flux changes are minute and such a field can induce an output comparable to the wanted signal. (Hence that all-too-familiar mains hum.)

The most oft employed variation upon this theme replaces the moving magnets with a single high permeability armature (usually iron). The magnets are fixed within the body, with a resulting drop in mass attached to stylus. A voltage is induced into the coils by the movement of the iron armature within the magnetic field. For this reason the technique is called 'induced magnet' or 'moving iron' and excellent examples are marketed by Ortofon and Empire amongst others.

Output levels are generally around 2-3 mV.

2/ Moving Coil

It may come as a surprise to some of the newer converts to the black arts of hi-fi to know that moving coil cartridges have a longer history than the ubiquitous moving magnet. Originally

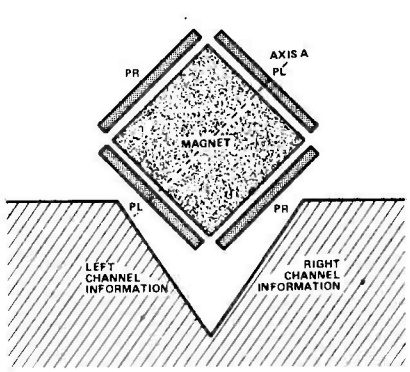


Fig. 1a The mechanical relationship between the pole pieces (which are fixed to the cartridge body), the magnet (which is attached to the stylus), and the record groove wall.

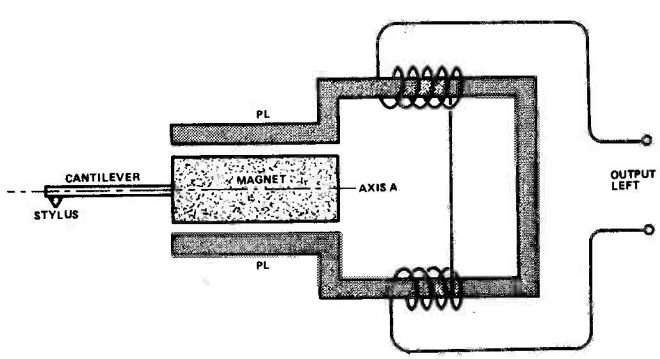


Fig. 1b Axis A can be referred to Fig. 1a to show the positioning of the generator within a moving magnet cartridge.



Strange looking things, but every home should have one. This particular point is a close-up Van der Hul stylus as employed in the Goldring G900IGC.

developed by Ortofon, their tracking-ability weaknesses and requirement for a step-up device led to their practical extinction a few years ago. However, the birth of the 'esoteric' hi-fi market and the subsequent interest of the Japanese audiophiles, has led to their virtues being prized over their vices once more.

The principle is extremely simple, and is illustrated in very general terms in Fig.2. The magnets are held in a fixed position within the cartridge body and the coils are mechanically linked to the stylus assembly. As the stylus follows the groove modulations the coils move relative to the magnets, thus generating the required signal voltages.

Output is generally lower, of the order of 0.2 mV and an extra amplification stage (step-up device) is required. However, a new generation of cartridges has arisen which utilise a far greater number of windings on the coils and more powerful magnets to generate a higher voltage level, comparable to moving magnet designs. The need for a step-up device is thus eliminated.

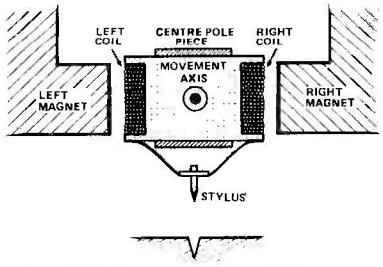


Fig. 2 Moving coil cartridge basics. As the stylus moves the coils, a current is generated within them by the magnetic field from the fixed magnets.

Two By Two

Considering the cartridge to be composed of two separate systems allows the different parameters of each to be evaluated correctly. The two systems are (i) dynamic components:- i.e. stylus, cantilever, pivot and moving generator (ii) static components:- i.e. body, fixed generator elements, electrical connections. If we define the task of the pickup as that of translating the mechanical movements produced at the stylus, by the LP, into an electrical signal for transmission to an amplifier, then we can consider the design requirements for each stage of that translation in turn.

Before proceeding, it should be noted that the pickup cartridge is an integral part of the record playing system as a whole. Many of the design parameters for the cartridge are correctly chosen to optimise the complete system under dynamic condition. In this article we cannot fully explore these interactions, but merely highlight them where they impinge upon the cartridge design directly.

Putting On The Stylus

In order to correctly interpret the record groove, a stylus must remain in contact with the groove wall, and be able to follow each and every modulation. The earliest stylus shape employed was a spherical one, simply because it was easiest to make and required least alignment. This suffered from the disadvantage of an inability to follow the highest frequencies recorded on a disc, because it will get "squeezed out" of the groove once the modulations become shorter than the length of the stylus, measured along the groove.

Elliptical stylii were introduced to overcome this by reducing that length and yet maintaining as large an area of contact with the groove wall as possible. Tracking weights had to be lower to prevent record wear increasing significantly, but the modulation tracing (tracking) deficiency of the spherical tip was overcome. Many companies have since attempted to refine this stylus configuration, with varying degrees of success. Only the Shure hyper-elliptical appears to offer any real advantage over the basic design, having an increased tracking ability and better high frequency definition.

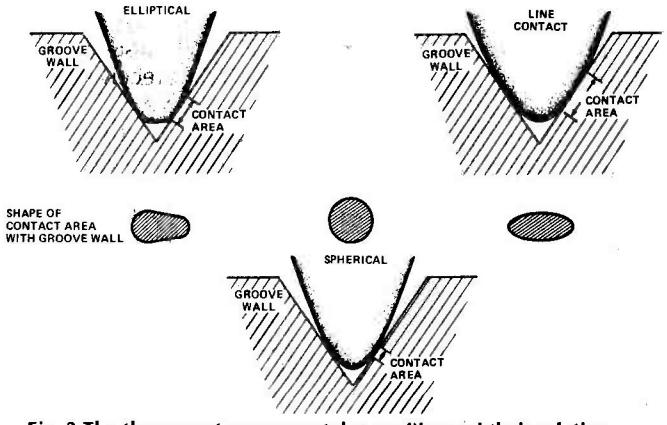


Fig. 3 The three most common stylus profiles and their relative parameters. Note that whilst the elliptical offers a greater tracking ability, its area of contact will generate increased record wear.

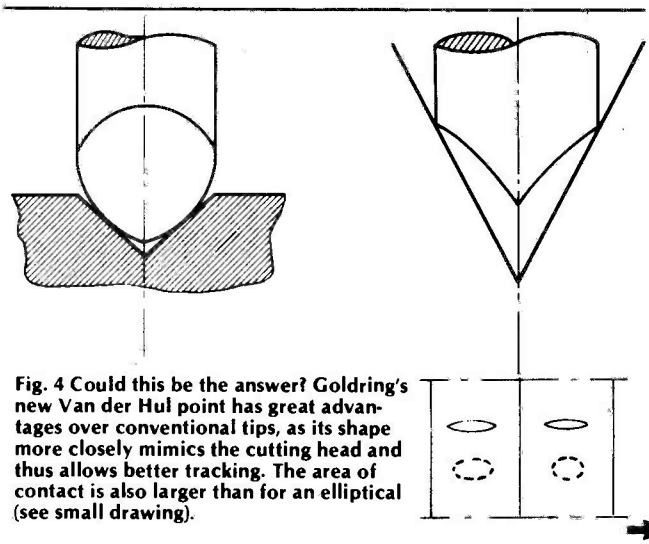


Fig. 4 Could this be the answer? Goldring's new Van der Hul point has great advantages over conventional tips, as its shape more closely mimics the cutting head and thus allows better tracking. The area of contact is also larger than for an elliptical (see small drawing).


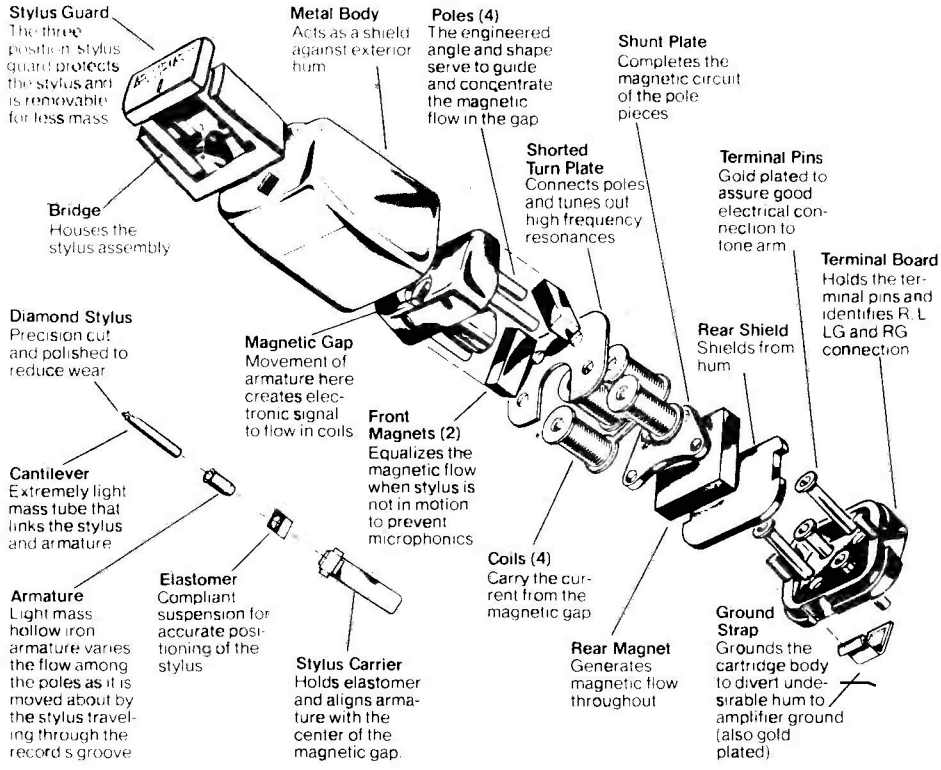


Fig. 5 This exploded view of an Empire induced magnet design gives an indication of the lengths that top manufacturers will go to in order to beat reasonances and colourations.

A still later development has been the line-contact stylus, (Shibata) which has attempted to get closer to the shape of the cutter head used in the initial production of the disc — this would obviously allow it to follow the groove more closely than anything else. Contact area would also be increased, with a resultant reduction in record wear. This type has reached its zenith with the introduction of the Goldring G900IGC cartridge and its Van der Hul stylus. It dramatically improved the performance of the G900 series and would seem, at the moment, to be closer to The Answer than anything else.

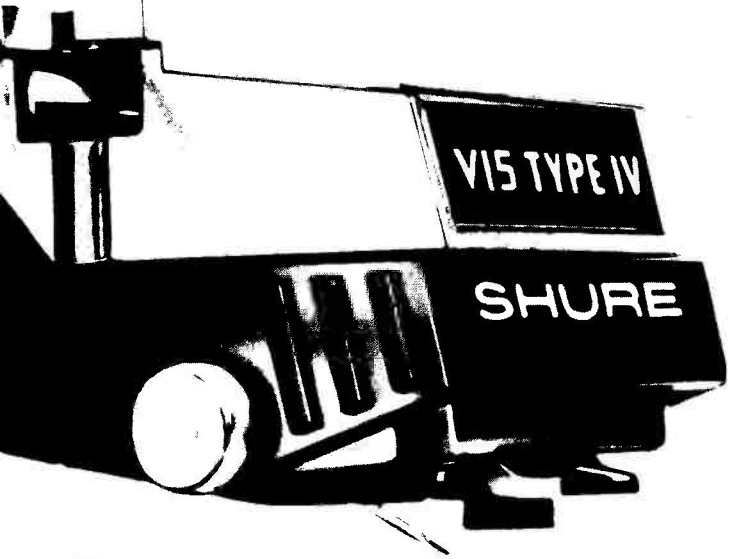

This V15IV attempts to optimise its own working conditions by using a damped, static-conducting 'rider' brush, operating ahead of the stylus. Warp effects are drastically reduced.

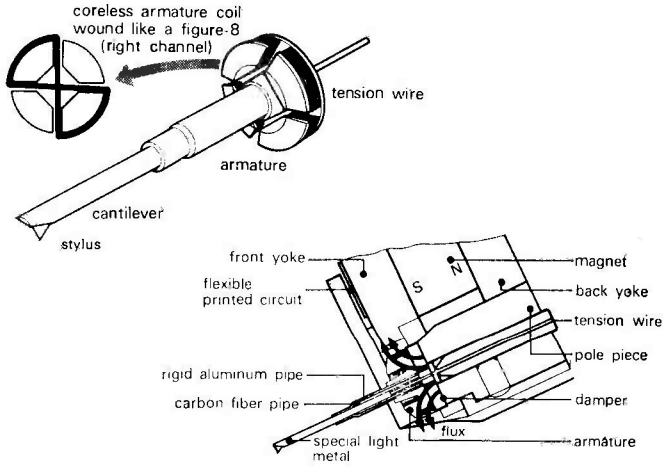


Fig. 6. A cross-section of a Sony moving coil pickup, showing how the coils are miniaturised to decrease the mass of the moving element, thus improving transient behaviour.

Cantilever Leavings

The stylus is joined to the generating element, be it coils or magnetic material, by the cantilever. It should be so attached that it tracks the disc at 20° to the vertical, (vertical tracking angle), since this is the cutting head angle and any deviation from this will be yet another source of distortion. (20° is, in fact, not yet a totally standard figure, but is the most used and best compromise figure we have).

If the cantilever were a totally rigid coupling then the pickup would be just as totally unable to produce a signal from the record, since the stylus would be prevented from moving with the groove. If it were too compliant, then the slightest warp or variation in surface would destroy the unit, with the arm mass inertia bending the cantilever out of shape.

Compliance is thus an important compromise parameter. The higher the compliance the lower must be the arm mass for the correct operation. This is because, like any mechanical system, the two working together will possess a resonant frequency — i.e. they will move easier at one frequency than any other, producing a non-linear response. Since the usable audio band extends approximately from 20 Hz-20 kHz and disc warps generally produce a signal somewhere around 6 Hz the ideal compromise is to place the system resonance between the two.

Combinations of compliance and arm mass are chosen to achieve this aim. Low mass pickup arms score a few points here as mass is easily added to these to 'tune' the resonance to an ideal frequency. If an arm is too heavy for a particular cartridge then there is little that can help — short of a hacksaw! For that reason alone, I tend to favour the SME Series III for all but a couple of cartridges — and those are low compliance, low output, moving coil designs, for which there exist specially designed carriers.

Compliance is normally measured in Compliance Units or CU where 1 CU = 1×10^{-6} cm/dyne.

Damping For All

All cartridge cantilevers are 'damped' to some extent, to control the resonances of the system. Some companies eg Ortofon (in the MC30) employ a complex mechanical linkage to overcome both the low frequency resonance and that at around 18 kHz — way at the other end of the spectrum — excited by the interaction between the record itself and the stylus. It is this resonace, and how successfully it is controlled which, more than any other single factor, determines how well a cartridge will audition.

A large number of factors are involved here; the mass of the stylus tip itself, the length of cantilever, compliance, damping of the pivot and the mass seen by the stylus reflected back from the arm through the cantilever, ie the effective mass of the system. It is an unfortunate fact that the better solutions to the problem are all expensive, which is why cartridges continue to cost a comparable amount of money, per ounce, to precious metals.

Generators

In the case of moving magnet designs the requirement for the fixed coils is fairly straightforward. The vast majority of amplifiers carry a 47k input, which is designed to accept these units. This makes electrical matching a fairly simple affair. The greatest source of contention will be the level of capacitance that the cartridge will be subjected to as a load. Too high a value will act as an HF filter and 'dull' the cartridge sound significantly. Too little will subjectively boost the treble, giving increased noise and a harsh brittle sound. Manufacturers always specify a capacitance value at which their unit performs best and this should be rigidly adhered to. Add about 150pF, for arm leads, to the input value of the amplifier and adjust by adding capacitors if necessary — ±15% will generally be close enough.

Some units, such as Grado are uncritical to a great extent, whilst others, eg Goldring, will have their subjective performance jeopardised if the value is not adjusted properly.

Moving coils present a more involved problem. The output here is too low to be connected directly to a conventional pickup, and so too is the impedance, so the step-up device must act as a buffer stage as well as providing the gain needed to allow normal usage. Impedance levels are of the order of 10-40R and as the device is essentially a current generator, noise will be a problem if matching is not precise. Again the easiest way around this is to stick with the manufacturer's recommendations as to which unit performs best with his cartridge.

High-Outputs

The latest generation of moving coil cartridges employ a generator technique which obtains outputs of around 2 mV, allowing their direct connection to a standard input. The coils in these models are generally wound with many more turns of wire to produce a higher voltage from the same magnetic field strength. The impedance is also 'padded' by this technique to improve matching. However, the resultant unit 'gain' has led some companies into problems with hum induction and electrical matching difficulties, despite their precautions.

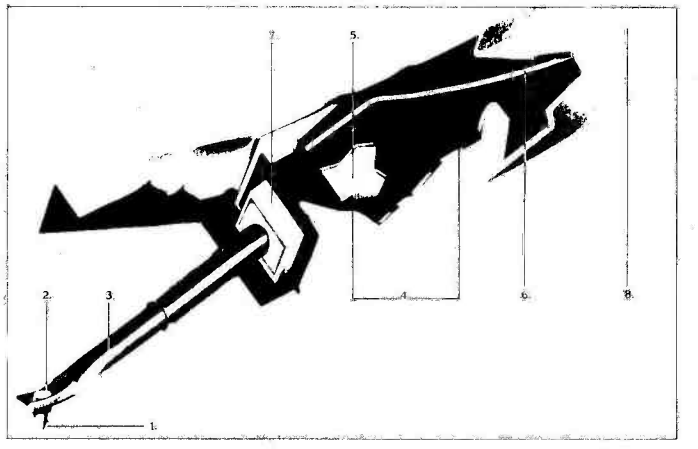


Fig. 7. So you thought cantilevers were simple? Take a look as this Shure version:- 1. Full diamond stone, meticulously shaped and polished, then assembled into an accurately machined mounting. Hyperelliptical in the V15 Type IV; hyperbolic in the M24H; biradial (elliptical) in the V15 Type III, and spherical in the V15 IV-G. 2. Doubly secure mounting — aligned, the diamond is first fitted into its socket, then high-temperature cemented to ensure permanent geometric orientation. 3. Ultra-thin-wall stylus shank — telescoped structure in V15 Type IV for low mass. Beryllium interior control lever in V15 Type III, M24H, M95 Series, M75 Type 2, and M91 Series for rigidity where needed to prevent tracking errors. 4. Viscoelastic suspension block — the efficient "heart" of the bearing which defines the pivot point of the stylus. In the V15 Type IV and M24H, a two-function bearing system separately optimized for high frequencies and for low frequencies. 5. High-energy magnet with electromachined aperture for exact positioning of stylus shank. Pivot location ensures minimal contribution to effective mass of moving system. 6. Precisely adjusted, resonance-free support wire. 7. Pivot control — correct location and function of bearing and support wire ensured. 8. Stylus assembly carrier — placement of stylus assembly relative to pickup coils within cartridge body is optimised. Not so straightforward really, is it?

Ultimo produce perhaps the best known examples of high-output moving coils and they are also renowned for requiring very high capacitive loading, well in excess of the levels normally found in amplifier circuits. *Correctly* loaded, though they possess a very high sound quality and avoid the need (and expense) of a step-up device altogether.

Conclusions

Summarising briefly then, a cartridge has to extract the mechanical information from the record groove without passing on any appreciable vibration to the pickup arm if possible, and translate this into as faithful an electrical signal as possible; it must not be affected by warps or distortions in the vinyl surface; it must be impervious to electrical fields produced by motors, transformers etc and, ideally should be totally insensitive as to which pickup arm it is used in.

Any cartridge which met those requirements could be safely described as perfect, and whilst we are unlikely ever to have such a unit offered for sale, some of the approximations we do have are really incredible engineering achievements when you consider the difficulties involved, — whether you happen to like the sound of them, or not! **ETI**

CHROMASONIC electronics


48 JUNCTION ROAD, ARCHWAY, LONDON N19 5RD — 100 yards from Archway Station & 9 Bus Routes
TELEPHONE: 01-263 9493/01-263 9495


YOUR SOUNDEST CONNECTION IN THE WORLD OF COMPONENTS AND COMPUTERS

PETS & SYSTEMS

8N 8K RAM — £399
16N 16K RAM — £499
32N 32K RAM £599
CASSETTE DECK — £55

343K Twin Floppy Disk
£695

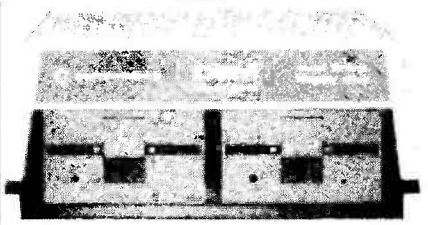

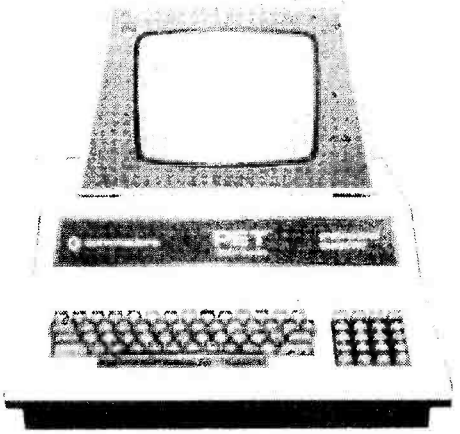


COMPLETE 32K SYSTEM £1789

NEW 32K with 80 col Screen Twin Disk Drive 950K **£825 £895**

All with new keyboard and green screen

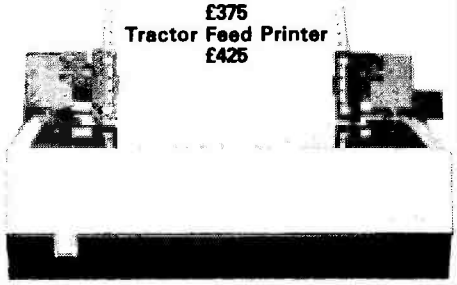FRICTION FEED PRINTER
£375
Tractor Feed Printer
£425




MEMORY EXPANSION KIT

Suitable for UK101, Superboard expansion using 2114's each board has 16K ram capacity kit contains:

- ★ On board power supply
- ★ 4K Eprom expansion
- ★ Fully buffered for easy expansion via 40 pin socket
- ★ 8K kit **£79.95**
- ★ 16K kit **£106.95**
- ★ Printed Circuit Board **£29.95**
- ★ 40 pin-40 pin header plug **£8.50**

NEW SHOP

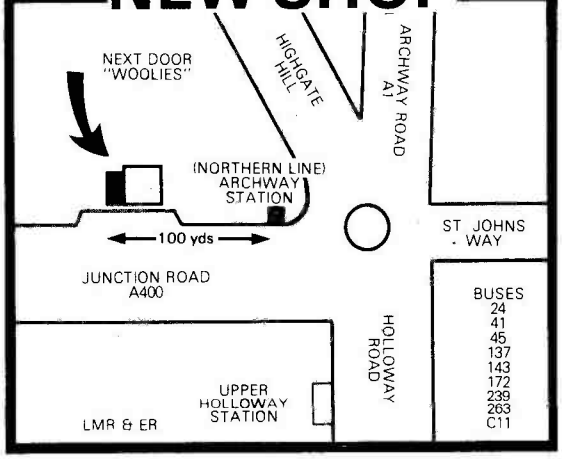

VIDEO GENIE

VIDEO GENIE based on TRS80



Utilises Z80, 12k level II Basic, Integral Cassette Deck, UHF O/P 16k RAM, all TRS80 features

£289

CASES


Available for UK101, Superboard, Nascom. Appx. DIM 17" x 15" 435 x 384 mm

PRICE £24.50
Post & Packing £1.50

UK101 P.P.I

Built & tested. Interfaces TX80 Printer direct. Can be programmed to operate relays, motors, various other peripherals "CENTRONICS COMPATABLE" Plugs into IC socket. LED binary display fully documented. **£29.95**

PRINTERS

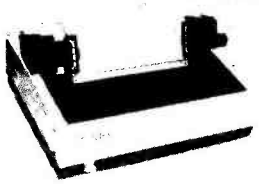

EPSON MX80 £359
EPSON TX80 £295

Dot-matrix printer with Pet graphics interface: Centronics parallel and serial: Pet and Apple compatible.

U K 1 0 1



£179 IN KIT FORM
£229 READY BUILT & TESTED
£255 COMPLETE IN CASE

4K Expansion (8x2114)
NOW ONLY £14.00

No extras required
- ★ Free sampler tape
- ★ Full Qwerty keyboard
- ★ 8K basic
- ★ Ram expandable to 8K on board (4K inc)
- ★ Kansas City tape interface
- ★ NEW MONITOR ALLOWS FULL EDITING & CURSOR CONTROL **£22.00**

BARCLAYCARD VISA

Please add VAT 15% to all prices. Postage on computers, printers and cassette decks charged at cost, all other items P&P 30p. Place your order using your Access or Barclaycard (Min tel order £5). Trade and export enquiries welcome. credit facilities arranged

We welcome Access

CHROMASONIC electronics

NEW SHOP & SHOWROOM NOW OPEN

Telephone: 01-263 9493/01-263 9495

UK101 SOUND

Sound Generator and combined parallel in out port kit, containing P.C.B., AY-3-8910, 6820 PIA. Fully documented and demo tape. **£29.95.**
AY-3-8910 £8.50.

UK101 SOFTWARE

	£
Space Invaders	6.50
Real Time Clock	3.00
Chequers	3.00
Othello	4.00
Game Pack I	5.00
Game Pack II	5.00
Game Pack III	5.00
Screen Monitor	4.00
Assembler Editor	14.90
10xC12 Blank Tapes	4.00

Z80 2.5Meg	7.95
Z80A 4Meg	9.95
6502	6.95
6800	6.50
8080	4.75
9900	25.95

SUPPORT CHIPS

Z80 CTC	5.95
Z80A CTC	6.95
Z80 P10	5.95
Z80A P10	6.95
6520	3.95
6522	6.85
6532	8.50
6821	4.25
6850	3.60
6852	4.35
8212	1.95
8216	1.95
9224	2.75
8228	
8251	4.95
8253	9.75
8255	4.50
TMS9901	13.16
TMS9902	11.18
TMS9904 (74LS362)	8.40

I.C. SOCKETS

	D.I.L.	W/W
8 pin	.09	.25
14 pin	.11	.35
16 pin	.12	.42
18 pin	.16	.50
20 pin	.20	.62
22 pin	.22	.65
24 pin	.24	.70
28 pin	.30	.80
36 pin	—	.99
40 pin	.40	1.10

MEMORY

D.RAMS	£ p
4027	2.75
4050 (350NS)	2.35
4060 (300NS)	2.39
4116	3.95
S.RAMS	
2102A	1.30
2102A2	1.69
2112A	2.75
2114/4045	2.75
4035	1.07
4044-5257	6.93
6810	3.50
BULK PURCHASE	
8x2114	14.00
8x4116	18.00
16x2114	26.00

EPROMs

2708	4.25
2716 (5v)	6.95
2532	29.95

ROM

2513 (UC)	5.95

BUFFERS

81LS95	1.25
81LS96	1.25
81LS97	1.25
81LS98	1.25
SN74365	.52
SN74366	.52
SN74367	.52
SN74368	.52
8T26	1.50
8T28	1.50
8T95	1.50
8T96	1.50
8T97	1.50
8T98	1.50

BAUD RATE GENS

MC14411	8.75
MM5307	8.75

UARTS

AY-5-1013	3.95
AY-3-1015	4.75
MM5303	4.75
TMS6011	3.55

SEND S.A.E. FOR COMPLETE PRICE LIST OR PHONE 01-263 9493

KEELMOOR


Quality... at Keener Prices

LADIES WATCHES
5 function — Hours, mins, secs day, date, back light, auto calendar. Only 6mm thick. Elegant matching metal bracelet.
Dress £8.95 Day £5.95


QUARTZ LCD Slim Chronograph. 11 function. hours, mins, secs, 6 digit-month, date, day of week. 1/100 sec stop watch split and lap modes, backlight.
ONLY £7.95

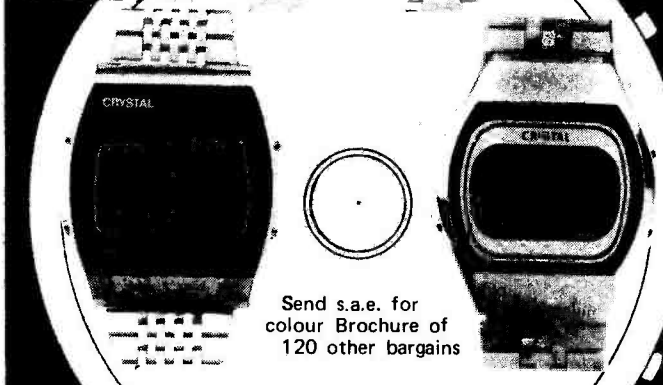QUARTZ LCD ALARM. 6 digit hours, mins, secs, day,date.24-hour alarm with on/off indicator.
ONLY £8.95





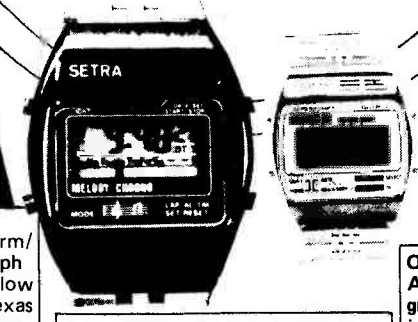Send s.a.e. for colour Brochure of 120 other bargains



MELODY LCD, Alarm/chronograph plays Yellow Rose of Texas date, stopwatch, dual time.
ONLY £14.95

QUARTZ LCD Alarm / Chronograph. 22 functions. Hours,mins, secs, day, date, month,1/10 sec stopwatch,split & lap modes, 12 & 24 hour modes, 24 hour alarm.
ONLY £12.95

ALL WATCHES CARRY A 1 YEAR GUARANTEE. They come complete with fully adjustable, matching, stainless steel straps and demonstration battery fitted (this battery is not guaranteed). Please add 60p for each spare battery required. Send cheques/P.O.'s, quoting watch/watches required to


KEELMOOR LTD

78 CASTLE STREET, MELBOURNE, DERBY, DE7 1DY

Please add50p&p per order.

MUSICAL BOX

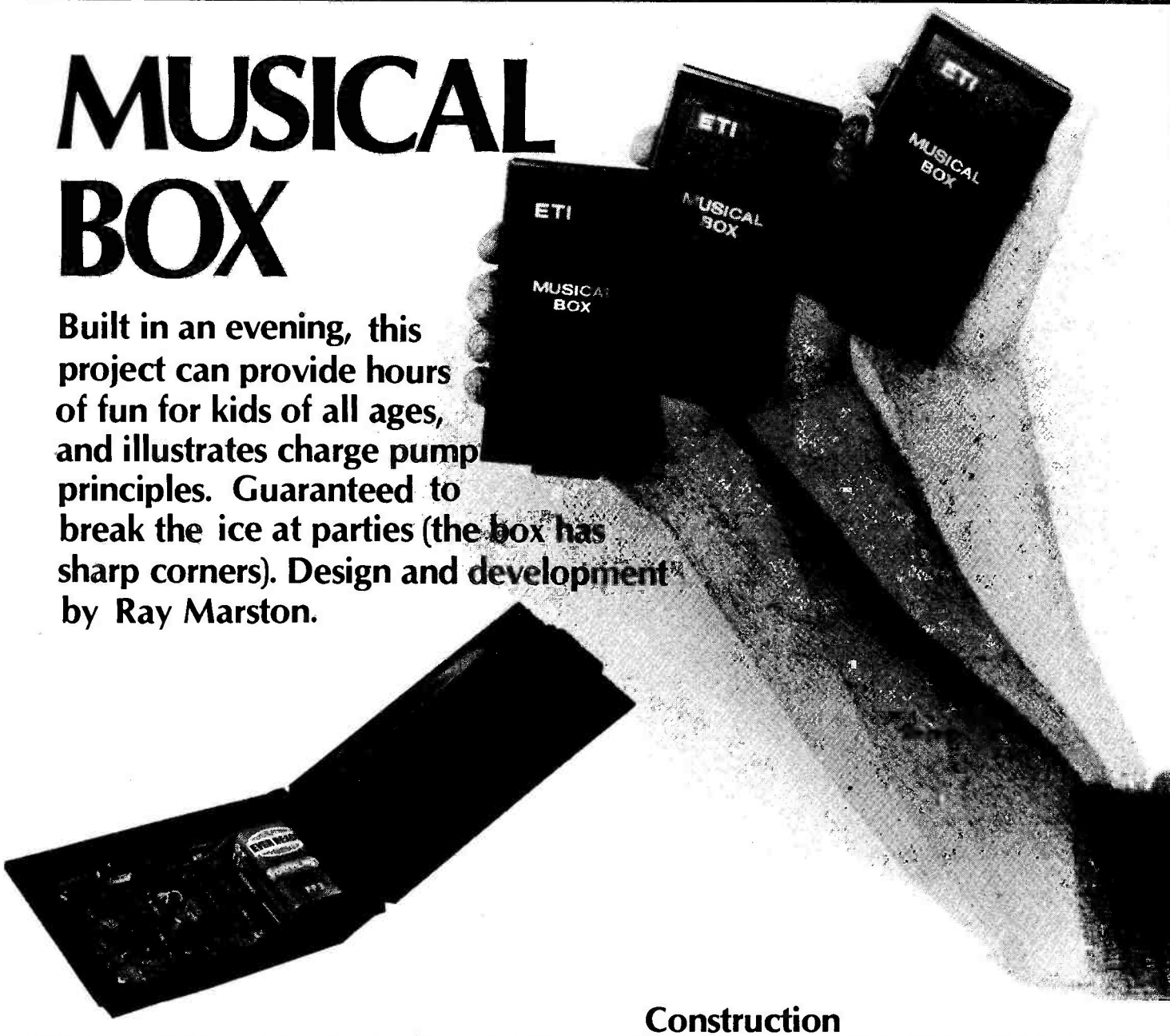Built in an evening, this project can provide hours of fun for kids of all ages, and illustrates charge pump principles. Guaranteed to break the ice at parties (the box has sharp corners). Design and development by Ray Marston.



This neat little novelty project contains a variable-frequency master tone generator and a variable-rate gate oscillator, both activated by a single built-in mercury tilt switch. The output of the tone generator is fed directly to a miniature acoustic transducer (sound generator); the frequency of this generator slowly rises when the tilt switch is open or slowly falls when it is closed. The gate oscillator is used to pulse the master tone generator on and off. Its operating rate is proportional to the switching rate of the tilt switch; the rate decays slowly towards zero when the tilt switch takes up a stable state.

Thus, if the unit is gently tilted downwards, a rising tone is generated; tilt the unit upwards, and a falling tone is produced. Give the unit a gentle shake and the tone will be pulsed on and off at a slow rate. Shake the unit vigorously and the pulse rate will rise to a high value. In all cases, the tone can be increased or decreased by suitably tilting the unit. A whole range of sounds can be produced by shaking and/or tilting the unit.

The unit is housed in a pocket-sized 'flip-top' black case. The unit's on/off switch is mounted directly on the PCB, access to the switch being gained by flipping open the case top. The unit is powered by a single PP3 battery.


Construction

This is a very easy project to build, since all of the circuit's components (including the battery and the acoustic transducer) are mounted directly on a single PCB. The PCB is designed to fit into the Verobox mentioned in the list of components.

When building the unit, note that the two CMOS ICs should be mounted in suitable sockets. Other points to note are that two bridging links are used on the board and that the mercury tilt switch is fixed by soldering it to Veropins (see photograph). On/off switch SW2 is a sub-miniature PCB-mounting type, soldered directly to the board. Don't solder the transducer leads yet.

When construction is complete, fix the acoustic transducer (Tx) to the underside of the PCB (below the large unetched copper area) with double-sided sticky pads. Now pass the transducer leads through the hole near the centre of the board and solder them in place. Fix the PP3 battery in place on the PCB, again using sticky pads. Now fix the completed PCB into the specified case, after first drilling a large hole in the case below the position of the acoustic transducer. Finally, switch the unit on, snap the lid shut, give it a shake, and sit back and enjoy the sounds.

Fig.1 Circuit diagram.

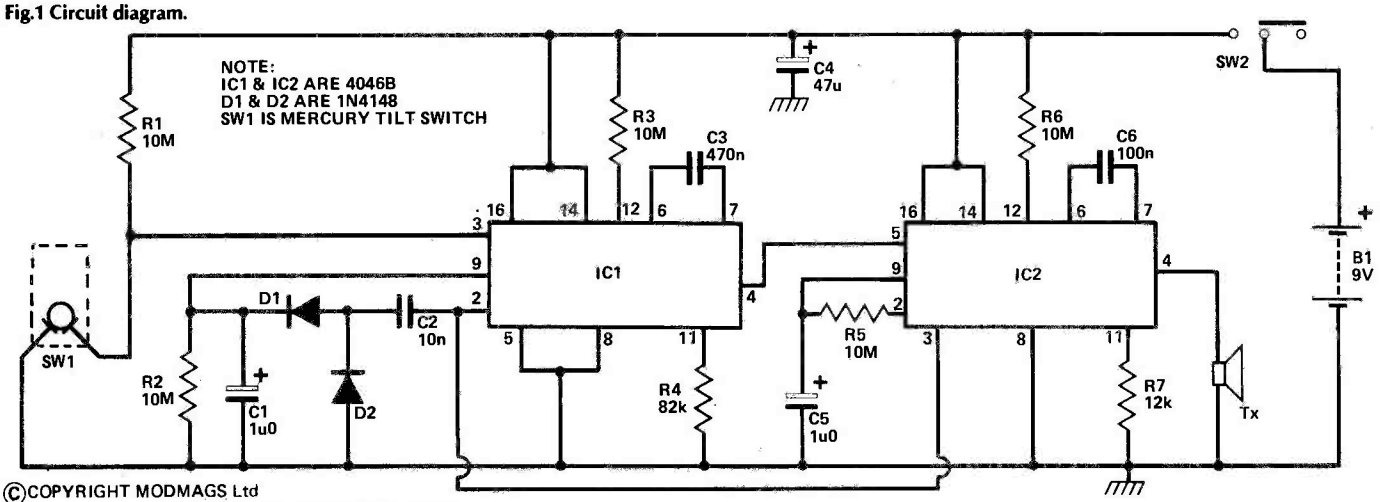

©COPYRIGHT MODMAGS Ltd

HOW IT WORKS

The circuit contains two wide-range voltage-controlled oscillators (VCOs), each built around a 4046B IC, together with a mercury tilt switch and some switch-conditioning circuitry. The two oscillators are basically similar, their frequencies being determined by the input voltage on pin 9 (of the 4046B ICs) and by the values of the capacitors/resistors connected to pins 6, 7, 11 and 12.

The 4046B ICs contain a variety of elements in addition to the VCOs. In our circuit, the most important of these is an EX-OR gate which, in our application, is wired as a simple pulse inverter with its input at pin 3 and its output at pin 2. We use these inverters as part of the switch-conditioning circuitry.

The mercury tilt switch is wired to the input of the built-in inverter (pin 3) of IC1: the output of this inverter (pin 2) is connected to the input of the inverter of IC2. If the tilt switch is opened, these two inverters cause the pin 2 voltage of IC2 to switch to a high value, so C5 starts to charge up via R5, thereby causing the VCO in IC2 to generate a rising tone signal in the acoustic transducer. When the tilt switch closes, pin 2 of IC2 switches low, causing C5 to discharge via R5 and so generating a falling tone.

The inverted switch output of IC1 (pin 2) is also fed to a charge pump circuit (designed around C2-D1-D2-C1-R2), which causes a small amount of charge to be fed to C1 each time that the tilt switch activates. This charge leaks away slowly via R2, so that the mean voltage of C1 is proportional to the rate at which the tilt switch is operated or shaken. The C1 voltage is used to control the VCO frequency of IC1, and the output (pin 4) of this IC is used to gate the VCO of IC2 on and off via pin 5.

Thus, the operating frequency of IC2 is controlled by tilting the mercury tilt switch and the pulse rate is controlled by shaking the switch.

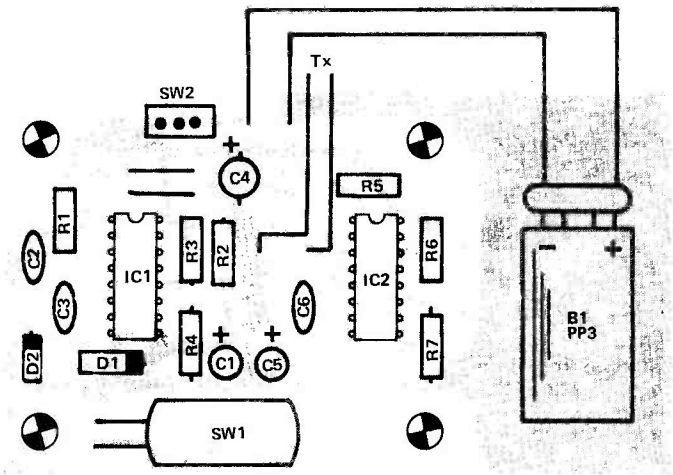


Fig.2 Component overlay for the Musical Box.

PARTS LIST


Resistors (all ¼ W 5%)	
R1,2,3,5,6	10M
R4	82k
R7	12k
Capacitors	
C1,5	1u0, 16 V electrolytic (PCB-mounting)
C2	10n polyester
C3	470n polyester
C4	47u, 16 V electrolytic (PCB-mounting)
C6	100n polyester
Semiconductors	
IC1,2	4046B
D1,2	1N4148
Miscellaneous	
SW1	mercury tilt switch
SW2	sub-miniature PCB-mounting slide switch
Tx	PB-2720 transducer

Verocase, order no. 202-21317

BUYLINES

The only unusual components here are the mercury tilt switch and the acoustic transducer. The transducer is available from Ambit International.

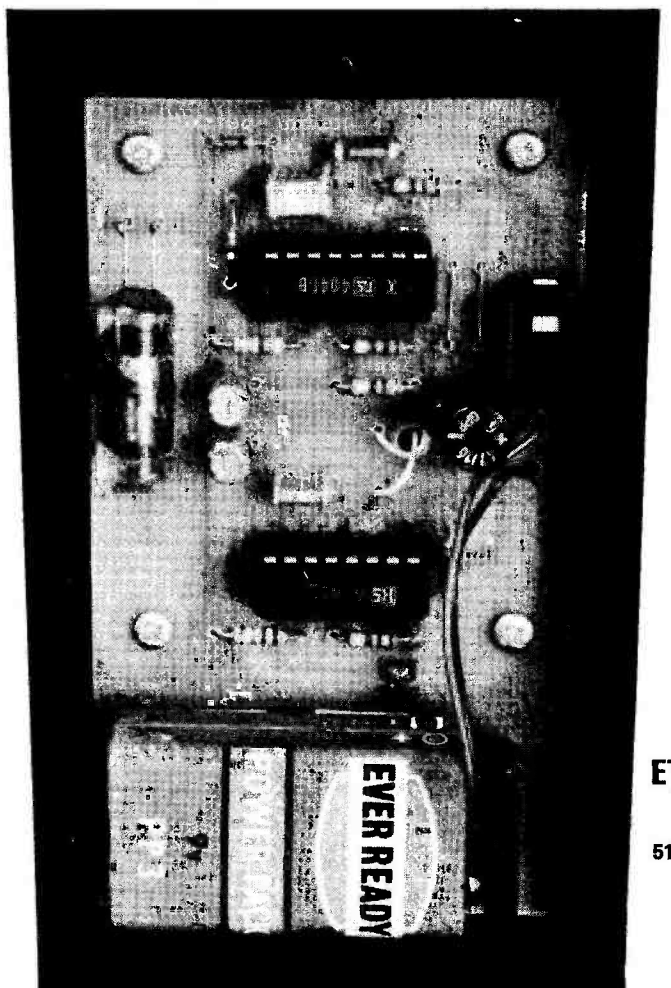The tilt switch used in our prototype is available, to order, from Watford Electronics.



PARNDON ELECTRONICS LTD.

Dept. No. 23, 44 Paddock Mead, Harlow, Essex CM18 7RR. Tel. 0279 32700

RESISTORS: ¼ Watt Carbon Film E24 range ± 5% tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Bandoliered and colour coded.
£1·00 per hundred mixed. (Min 10 per value)
£8·50 per thousand mixed. (Min 50 per value)
Special stock pack. 60 values. 10 off each **£5·50**



DIODES: IN4148 3p each. Min order quantity – 15 items
£1·60 per hundred

DIL SWITCHES: Gold plated contact in fully sealed base – solve those programming problems
4 Way **86p** each. 6 Way **£1·00** each. 8 Way **£1·20** each.



DIL SOCKETS: High quality, low profile sockets
8 pin – **10p**. 14 pin – **13p**. 16 pin – **15p**. 18 pin – **19p**. 20 pin – **25p**.
22 pin – **29p**. 24 pin – **35p**. 28 pin – **39p**. 40 pin – **57p**.

ALL PRICES INCLUDE V.A.T. & POST & PACKING — NO EXTRAS
MIN. ORDER – U.K. £1·00. OVERSEAS £5 · CASH WITH ORDER PLEASE

LATEST ADDITION TO OUR RANGE OF AUDIO SIGNAL GENERATORS



MODEL AO 150
Very low distortion unit with frequency meter.

£53 (+ UK VAT). P&P £2.50

Earlier models still available **(from £23).** Send SAE for full lists plus Function Generator. Millivoltmeter, Distortion Analyser, R.F. Signal Generator, etc.

TELERADIO

325 FORE STREET, LONDON N9 0PE
01-807 3719 Closed Thursdays

IONISER KIT

This negative ion generator gives you power to saturate your home or office with millions of refreshing ions. Without fans or moving parts it puts out a pleasant breeze. A pure flow of ions pours out like water from a fountain, filling your room. The result? Your air feels like fresh ocean air, pure crisp and wonderfully refreshing.

All parts P.C.B. and full instructions **£10.** A suitable case including front panel, neon switch, etc. **Available at £8** extra.

H.E. KITS

Car Booster ZD50 £18; Multi Option Siren ZD36 £10.50; Car Equaliser ZD52 £13.30; Envelope Generator ZD20 £11.79; R/C Speed Controller ZD3 £9.60; White Noise Effects Unit ZD18 £16.85; Track Cleaner ZD12 £7.75; Drill Speed Controller ZD21 £7.

All Hobby Kits supplied cases except ZD3. All kits contain components as specified plus Texas I.C. sockets where required. Also connecting wire. Special introductory offer to E.T.I. readers, a pack of nuts, bolts, washers, self-cutting, self-tapping screws supplied with each kit.

SPECIAL OFFERS

Texas/I.T.T. 1N4148, 100 for £1.50.
Fairchild FLV ISO Red '2 LEDs 10 for £1; 100 for £7.50.

Mullard Computer Electrolytics S/T 21,000 U.F. 40V	**£3.50**
Daly Electrolytic Capacitors 2000μF, 100V	**£1.50**
I.T.T. BCY 72 Transistors leads pre-formed	10 for **50p**
Varicap Tuners ELC1042	**£6.00**
Varicap Tuner ELC1043	**£6.00**
Philips Scope Tube 5" CV2191/DG-13-2	**£10.00**
Thorn-Sylvannia Scope Tube 5" SE5J	**£17.50** (Callers only)
Toshiba 12" TV Tube 310GAB4	**£12.50** (Callers only)

If you do not have the issue of H.E. which contains the Project, we can supply a reprint at 40p extra orders. Please add 30p post and packing. Add 15% VAT to total order.

Callers please ring to check availability of Kits.

T. POWELL

306 ST. PAUL'S ROAD
HIGHBURY CORNER, LONDON, N.1.
TELEPHONE: 01-226 1489

Access/Visa accepted
Shop hours: Mon. to Fri. 9-5.30. Sat. 9-4.30

POWERFET AMPLIFIERS AND COMPONENTS



PFA120

PFA80/120

The PFA is perhaps the perfect realisation of the classic powerful amp design. The superb P.C.B. allows the use of either one or two pairs of output services, providing easy expandability for those starting with the smaller system. (The extra output pair of the PFA120 results in lower distortion and improved efficiency, particularly into low impedance loads.)

The components used in the PFA have been chosen with extreme care. The lowest noise input devices and lowest distortion gain stage devices were selected regardless of cost. 140V powerfets were chosen against the more usual 120V to give improved safety margins.

Specification	PFA80	PFA120
Bandwidth	10Hz—	100KHz± 1dB
Output power RMS into 8Ω	80W (Vs=± 50V)	120W (Vs=± 55V)
T.H.D. from 1w to rated output at all audio frequencies	⩽0.008%	⩽0.005%
SNR	120dB	120dB
Slew Rate	20V/μs	20V/μs
Gain	X22	X22
Rin	30K	30K
Vs max.	± 70V	± 70V
Cost		
(built)	**£15.95**	**£22.85**
(kit)	**£13.95**	**£20.85**

Simple modification for bridge mode

POWERFETS

	CHAN	VDS * max V	ID max A	PDISS max W	Price
BD512	P	60	1.5	10	**90**
BD522	N	60	1.5	10	**85**
VMP4	N	60	2.0	25	**1250**
VN10KM	*N	60	0.5	1.0	**60**
VN64GA	N	60	12.5	80	**750**
VN67AF	*N	60	2.0	15	**80**
2SJ49	P	140	7.0	100	**340**
2SK134	N	140	7.0	100	**340**

* L/p protected. † our selection. VN/VM 120-page Design Cat. **45p.** Heat clips/sink TO202 **12p**, TO92 **8p.** TO3 **35p.**

COMPONENTS

CA3045	**70p**	NE555	**25p**	40163	**40p**
CA3080E	**70p**	SAD 1024	**1050p**	4069	**17p**
CA3086	**55p**	TL081	**29p**	709	**15p**
CA3140E	**45p**	TL082	**55p**	710	**25p**
DAC08EN	**250p**	2102	**80p**	733	**50p**
DM2502	**585p**	2114	**340p**	741	**18p**
HA12017	**80p**	40018	**17p**	78L06	**29p**
HA1397	**195p**	4007	**17p**	78L12	**29p**
LM3900	**43p**	40118	**17p**	78M05	**39p**
MC3401	**30p**	40138	**40p**	78M12	**39p**
NE529	**145p**				

SCOPE TRACE DOUBLER P.C.B.

Built C/W shift, chan select, choprate controls and instructions. Useful display from DC to 10MHz. Runs from 9v battery. **£9.95.**

2μS ADC chip set (DAC08, DM2502, NE529) with data £9. HA1388 (Bridge amp, 18w from car battery). With data **105p.**

Heatsink for HA1388/1397 **40p.**

See next month's issue for more on the PFAs or send SAE for details.

Pre-amp PAN 20 (Available March '81)

Taking advantage of Hitachi's ultra-low noise bipolar technology, J. W. RIMMER have produced a state-of-the-art pre-amp board to complement their power amplifiers.

The design is unique. Equalisation is applied after a flat gain stage, resulting in one of the best noise performances available. Superb overload figures are ensured by a front end incorporating a special gain/attenuator control (volume control to you!). The inputs are uncommitted and can be used with any combination of signal sources in the 1mV to 10V range. RIAA equalisation is provided for mag. PUs, and space on the board is available for different equalisations. (Tone control + filter circuits available shortly on separate board.)

Specification	
B.W.	20Hz-30KHz ± 1dB
THD at rated o/p	0.003% type
SNR	85dB (ref. 5mV RIAA) 105dB (ref. 100mV flat)
Vs	± 20V
Output	1V (clips at +20dB)
Cost	
(built board less controls)	**£4.75,** 2 needed for stereo

Power Amp PAN 1397 (Available March '81)

A high quality 20W power amp board based on the HA1397. Easily modified for bridge operation, providing high powers from low supply voltages.

Specification	
Output power RMS	20W into 8Ω at ± 22V
THD	20W into 4Ω at ± 19V
SNR	0.02% at 1KHz. 1W to 12W
Input	90dB 100mV into 50K
Cost	
(Built)	**£5.80**

Power supply components for 1397. Trans. (16-0-16V, 50VA) **£3.95.**
Supply board. ± 22V with above, and anti-thump circuitry. Drives 2 x 1397 **£3.95.**

P&P 75p with PFAs or transformers, otherwise 40p. VAT inc. prices.

FROM THE POWERFET SPECIALISTS J. W. RIMMER

Mail order only to — **148 QUARRY STREET, LIVERPOOL L25 6HQ. Tel: 051 428 2651**
Technical enquiries **367 Green Lanes, London N4 1DY 01-800 6667**

Unique in concept - the home computer that grows as you do!

-The Acorn Atom

NEW! Colour Encoder for full colour graphics **£21.50**



Also available ready-built **£150** plus VAT and p&p


£120 plus VAT and p&p. An outstanding personal computer kit

The ATOM – a definitive personal computer. Simple-to-build, simple-to-operate. But a really powerful full-facility computer. And designed on an expandable basis. You can buy a superb expanded package now – tailored to your needs. Or, you can buy just the standard Atom kit, and, as you grow in confidence and knowledge, add more chips. No need to replace your equipment. No need to worry that your investment will be overtaken by new technology. As you need more power, more facilities, you can add them!

*The picture shown demonstrates mixed graphics and characters in three shades of grey provided by the Standard Atom.

The standard ATOM kit includes:

●Full sized QWERTY keyboard ●Rugged polystyrene case ●Fibreglass PCB ●2K RAM ●8K ROM ●23 integrated circuits ●Full assembly instructions including tests for fault-finding. (Once built, connect it to any domestic TV and power source) ●Power requirement: 8V at 800 M A. ATOM power unit available. See coupon. PLUS FREE MANUAL written in two sections – teach yourself BASIC and machine code for those with no knowledge of computers, and a reference section giving a complete description of the ATOM's facilities. All sections are fully illustrated with example programs.

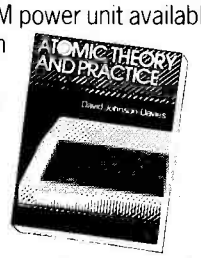

The ATOM concept

Adding chips into sockets on the PCB allows you to progress in affordable steps to large-scale expansion. You can see from the specifications that the RAM can be increased to 12K allowing high resolution (256 x 192) graphics. Two further ROM chips, e.g. maths functions, can be added directly to the board giving a 16K capacity. In addition to 5 I/O lines partly used by the cassette interface, an optional VIA device can provide varied I/O and timer functions and via a buffer device allow direct printer drive. An optional module provides red, green and blue signals for colour. An in-board connector strip takes the ATOM communications loop interface. Any number of ATOMs may be linked to each other – or to a master system with mass storage/ hard copy facility. Interface with other ACORN cards is simplicity itself. Any one ACORN card may be fitted internally.

So you can see there are a vast number of modular options and additions available, expanding with your ability and your budget.

The ATOM hardware includes:

●Memory from 2K to 12K RAM on board (up to 35K in case) ●8K to 16K ROM (two 4K additions) ●6502 processor ●Video Display allows high resolution (256 x 192) graphics and red, green and blue output ●Cassette Interface – CUTS 300 baud ●Loudspeaker allows tone generation of any frequency ●Channel 36 UHF Modulator Output ●Bus output includes internal connections for Acorn Eurocard.

The ATOM software includes:

●32-bit arithmetic (±2,000,000,000) ●High speed execution ●43 standard/extended BASIC commands ●Variable length strings (up to 256 characters) ●String manipulation functions ●27 32-bit integer variables ●27 additional arrays ●random number function ●PUT and GET byte ●WAIT command for timing ●DO-UNTIL construction ●Logical operators (AND, OR, EX-OR) ●LINK to machine-code routines ● PLOT DRAW and MOVE.

ACORN COMPUTER **4a Market Hill, CAMBRIDGE CB2 3NJ**

Your ACORN ATOM may qualify as a business expense. To order complete the coupon below and post to Acorn Computer for delivery within 28 days. Return as received within 14 days for full money refund if not completely satisfied. **All components are guaranteed with full service/repair facility available.**

Quantity	Item	Item price inc VAT+p&p	TOTALS
	ATOM KIT – 8K ROM + 2K RAM (MIN)	@ £140.00	
	ATOM ASSEMBLED – 8K ROM + 2K RAM (MIN)	@ £174.50	
	ATOM KIT – 12K ROM + 12K RAM (MAX)	@ £255.00	
	ATOM ASSEMBLED – 12K ROM + 12K RAM (MAX)	@ £289.50	
	1K RAM SETS	@ £11.22	
	4K FLOATING POINT ROM (inc. in 12K Version)	@ £23.30	
	PRINTER DRIVE 6522 VIA	@ £10.35	
	(inc. in 12K version) LS244 Buffer	@ £3.17	
	COLOUR ENCODER	@ £21.50	
	MAINS POWER SUPPLY (1.3 amps)	@ £10.20	
		TOTAL	

To: Acorn Computer Ltd., 4a Market Hill, CAMBRIDGE CB2 3NJ

I enclose cheque/postal order for £

Please debit my Access/Barclaycard No.

Signature

Name (Please print)

Address

Telephone No.

Registered No: 1403810. VAT No: 215 400 220

ETI 4/81

THE BI-PAK OPTO SHOW

LEDs

1501	**£0.10**	TIL209 Red LED .125"
1502	**£0.16**	TIL211 Green LED .125"
1503	**£0.16**	TIL213 Yellow LED .125"
1504	**£0.10**	FLV117 Red LED .2"
1505	**£0.16**	FLV310 Green LED .2"
1506	**£0.16**	FLV410 Yellow LED .2"
1507	**£0.80**	2nd Grade LED pack 10 assorted
1522	**£0.12**	MIL32 Clear illuminating Red LED .125"
1523	**£0.12**	FLV111 Clear illuminating Red LED .2"
1524	**£0.65**	CQX21 Red Flashing LED
1525	**£0.75**	CQX95 two colour LED

OPTO-ISOLATORS

1515	**£0.55**	Opto-isolator IL74 Single
1516	**£1.16**	Opto-isolator ILD74 Dual
1517	**£2.10**	Opto-isolator ILQ74 Quad

7 SEGMENT LED DISPLAYS

1508	**£0.80**	BDL307 7 segment LED display .3"
1509	**£1.80**	BDL527 dual 7 segment LED display .5"
1510	**£0.98**	BDL707 7 segment LED display .3"
1511	**£1.75**	BLD747 7 segment LED display .6"
1512	**£1.90**	BDL727 dual 7 segment LED display .5"

MISCELLANEOUS

1514	**£0.60**	ORP12 Light Dependent Resistor
1518	**£0.60**	Photo transistor P20 NPN
1519	**£0.26**	Photo Darlington MEL11 NPN
1520	**£0.40**	Photo transistor OCP71 PNP
1526	**£0.38**	FPE100 Infra Red Emitter
1527	**£0.38**	CQY89 Infra Red LED

BEGINNER'S PAK NO. 1 — 100 TRANSISTORS

A pack of well-known transistors, as used in many popular projects. A must for beginners (and very useful to experienced constructors too).

10	BC107/8	TO18	Metal	NPN
10	BC237	TO92	Plastic	NPN
5	BC177/8	TO18	Metal	PNP
5	BC251	TO92	Plastic	PNP
10	BFY51/BC141	TO39	Metal	NPN
5	BC160	TO39	Metal	PNP
5	2N3055	TO3	Metal	NPN
2	BD312/MJ2955	TO3	Metal	PNP
5	TIP29-31	TO220	Plastic	NPN
2	TIP30-32	TO220	Plastic	PNP
10	OC71-76	Germanium		PNP
5	AC128-188	Germanium	Metal	PNP
5	AC127-187-188	Germanium	Metal	NPN
5	OC44-45	Germanium		PNP
5	TIS43-UT46	Unijunction	Plastic	
5	2N3819	FET		
2	MEL11	Photo Transistor	Plastic	
2	BD131	TO126	Plastic	NPN
2	BD132	TO126	Plastic	PNP
100	TOTAL			

ALL devices — brand new and full spec as per device coding. Data and lead out details included in pak.
Normal Retail Value £23
Our Special Offer Price **£15**

BEGINNER'S PAK NO. 2 — 100 RECTIFIERS, SCRs, TRIACS, DIODES

20	IN4001 IN4007	1amp Silicon Rectifier
20	IN5401-IN5407	3amp Silicon Rectifier
20	IN4148	Fast switch diodes Silicon
10	OA200 BAX13-16	General Purpose Diode Silicon
5	C106D	Thyristor 400v TO202 Case
2	10amp Triacs 400v	TO220 Case Isolated Tab
2	4amp Triacs 400v	TO220 Case Non-isolated Tab
10	Assorted 3amp Case	Thyristors 50-600 volts TO64-TO66
5	Assorted 1amp	Thyristors 50-600 volts TO39 Case
6	OA81 91	General Purpose Germanium Diodes
100	TOTAL	

ALL devices brand new and full spec. Data and lead out details included.
Normal Retail Value £17
Our Special Offer Price **£11**

UNTESTED SEMICONDUCTOR PAKS

U1	150 germ Gold Bonded Diodes OA47	**£1.00**
U2	150 germ Point contact diodes OA81	**£1.00**
U3	150 Silicon G.P. 200mA Diodes OA200	**£1.00**
U4	150 Silicon Fast Switch Diodes IN4148	**£1.00**
U5	25 Stud type Silicon Rectifiers up to 10A	**£1.00**
U6	10 SCRs 5amp TO66	**£1.00**
U7	40 Sil Trans NPN TO18 Case BC107/8/9	**£1.00**
U8	40 Sil Trans PNP TO18 Case BC177/8/9	**£1.00**
U9	40 Sil Trans NPN TO18 Case 2N706/8	**£1.00**
U10	40 Sil Trans NPN TO5/39 2N697/2N1711	**£1.00**
U11	40 Sil Trans PNP TO5, 39 2N2905/1132	**£1.00**
U12	30 Sil Trans NPN TO39 BFY51-BC141	**£1.00**
U13	30 Sil Trans PNP TO39 BC160-161 etc	**£1.00**
U14	10 Sil Trans NPN TO3 2N3055	**£1.00**
U15	10 Sil Trans NPN TO220 TIP29-31-33	**£1.00**
U16	10 Sil Trans PNP TO220 TIP30-32-34	**£1.00**
U17	30 Sil Trans NPN TO39 High Vlts BF258, 115	**£1.00**
U18	40 Sil Trans TO92 BC237/8	**£1.00**
U19	40 Sil Trans TO92 BC251	**£1.00**
U20	40 Sil Trans NPN TO92 BC183/4	**£1.00**
U21	40 Sil Trans PNP TO92 BC257 BC212L	**£1.00**


Code Nos mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

ELECTROLYTIC PAKS

A range of paks each containing 25 first quality mixed value miniature electrolytics

EC1	Values from .47mFD-10mFD	**£1.00**
EC2	Values from 10mFD-100mFD	**£1.00**
EC3	Values from 100mFD-1000mFD	**£1.00**

NEW SHAPE LEDs

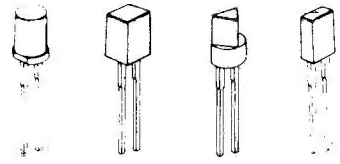

1561	**£0.26**	3mm Cylindrical LED Red
1562	**£0.26**	3mm Square LED Red
1563	**£0.26**	3mm Triangular LED Red
1564	**£0.26**	5mm Rectangular LED Red
1565	**£0.26**	5mm Cylindrical LED Red
1566	**£0.26**	5mm Square LED Red
1567	**£0.26**	5mm Triangular LED Red
1568	**£0.28**	3mm Cylindrical LED Green
1569	**£0.28**	3mm Square LED Green
1570	**£0.28**	3mm Triangular LED Green
1571	**£0.28**	5mm Rectangular LED Green
1572	**£0.28**	5mm Cylindrical LED Green
1573	**£0.28**	5mm Square LED Green
1574	**£0.28**	5mm Triangular LED Green
1575	**£0.28**	3mm Cylindrical LED Yellow
1576	**£0.28**	3mm Square LED Yellow
1577	**£0.28**	3mm Triangular LED Yellow
1578	**£0.28**	5mm Rectangular LED Yellow
1579	**£0.28**	5mm Cylindrical LED Yellow
1580	**£0.28**	5mm Square LED Yellow
1581	**£0.28**	5mm Triangular LED Yellow

CERAMIC PAKS

Containing a range of first quality miniature ceramic capacitors

MC1 40 miniature ceramic capacitors: 5 of each value
22pf, 27pf, 33pf, 39pf, 47pf, 56pf, 68pf, 82pf — **£1.00**

MC2 40 miniature ceramic capacitors: 5 of each value
100pf, 120pf, 150pf, 180pf, 220pf, 270pf, 330pf, 390pf — **£1.00**

MC3 40 miniature ceramic capcitors: 5 of each value:
470pf, 560pf, 680pf, 820pf, 1000pf, 1500pf, 2200pf, 3300pf — **£1.00**

MC4 35 miniature ceramic capacitors: 5 of each value:
4700pf, 6800pf, .01uf, .015uf, .022uf, .033uf, .047uf — **£1.00**

SPEAKERS AND CROSSOVERS

1901	Dome Tweeter 3½" 8ohms 50w	**£3.20**
1902	Dome Tweeter 3" 8ohms 20w	**£2.60**
1903	Flared Horn Tweeter 8ohms 30w	**£3.80**
1904	2 way crossover 15w 8ohms	**£1.24**
1905	2 way crossover 40w 8ohms	**£2.70**
1906	3 way crossover 60w 8ohms	**£3.50**
1907	Piezo Tweeter	**£5.20**
1914	70mm 80ohm speaker	**£1.20**
1915	70mm 8ohm speaker	**£0.95**
1916	56mm 8ohm speaker	**£0.85**
1917	2½" 8ohm speaker	**£0.75**
1918	2½" 64ohm speaker	**£0.82**
1919	5½" whoofer 4ohms 10w	**£3.90**
1920	5½" whoofer 8ohms 10w	**£3.90**
1921	5¼" Dual cone wide range 8ohms	**£5.80**
1922	8" Dual cone long throw 8ohms 15w	**£4.84**
1923	8" whoofer dual 4 + 8ohms rubber edge 20w	**£7.80**

DIL SOCKETS


1601	8 Pin	**0.09**	1606	22 Pin	**0.24**
1602	14 Pin	**0.11**	1607	24 Pin	**0.28**
1603	16 Pin	**0.12**	1608	28 Pin	**0.32**
1604	18 Pin	**0.18**	1609	40 Pin	**0.36**
1605	20 Pin	**0.20**			

LATE ADDITIONS — HIGH CURRENT AMPS AND SWITCHES

		VCEO	VCBO	I.C. Max
BFT32	**£0.60**	60	80	3A
BFT33	**£0.62**	80	100	3A
BFT34	**£0.65**	100	120	3A
BFT37	**£0.95**	100	120	3A

RPY76A Infra Red Detector **£0.65**

LED CLIPS AND HOUSINGS

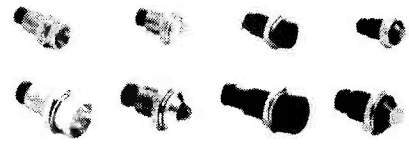

1548	**£0.15**	LED Plastic clips .125"
1549	**£0.18**	LED Plastic clips .2"
1550	**£0.28**	LED Housing (nickel plated) .125" A
1551	**£0.22**	LED Housing (nickel plated) .125" B
1552	**£0.37**	LED Housing (matt black) .125" C
1553	**£0.31**	LED Housing (matt black) .125" D
1554	**£0.34**	LED Housing (nickel plated) .2" E
1555	**£0.28**	LED Housing (nickel plated) .2" F
1556	**£0.44**	LED Housing (matt black) .2" G
1557	**£0.36**	LED Housing (matt black) .2" H

BULBS AND NEONS

1534	**£0.24**	LES Bulb 6v 0.36w
1535	**£0.24**	LES Bulb 6.5v 1w
1536	**£0.24**	LES Bulb 14v 0.75w
1538	**£0.24**	MES Bulb Round 6v .04A
1539	**£0.20**	MES Bulb Round 6.5v .15A
1540	**£0.20**	MES Bulb Round 6.5v .3A
1541	**£0.20**	MES Bulb Round 12.0v .1A
1542	**£0.20**	MES Bulb Round 12.0v 2.2w
1543	**£0.34**	Neon Red Round 240v
1544	**£0.34**	Neon Red Rectangular 240v
1545	**£0.34**	Neon Orange Rectangular 240v
1546	**£0.34**	Neon Green Rectangular 240v
1547	**£0.18**	MES Batten Holder

CARBON FILM RESISTOR PAKS

These paks contain a range of Carbon Film Resistors, assorted into the following groups:

R1	80 Mixed ¼w 100ohms-820ohms	**£1.00**
R2	80 Mixed ¼w 1Kohms-8.2Kohms	**£1.00**
R3	80 Mixed ¼w 10Kohms-82Kohms	**£1.00**
R4	80 Mixed ¼w 100Kohms-1M	**£1.00**
R5	60 Mixed ½w 100Kohms-820ohms	**£1.00**
R6	60 Mixed ½w 1Kohms-8.2Kohms	**£1.00**
R7	60 Mixed ½w 10Kohms-82Kohms	**£1.00**
R8	60 Mixed ½w 100Kohms-1M	**£1.00**

TANTALUM BEAD CAPACITORS

401	0.1uF 16v	**0.11**	414	47.0uF 16v	**0.55**
402	0.22uF 16v	**0.11**	415	100.0uF 10v	**0.55**
403	0.33uF 16v	**0.11**	416	.1uF 35v	**0.12**
404	0.47uF 16v	**0.11**	417	.22uF 35v	**0.12**
405	0.68uF 16v	**0.11**	418	.33uF 35v	**0.12**
406	1.0uF 16v	**0.11**	419	47uF 35v	**0.12**
407	2.2uF 16v	**0.12**	420	68uF 35v	**0.12**
408	3.3uF 16v	**0.13**	421	1.0uF 35v	**0.12**
409	4.7uF 16v	**0.14**	422	2.2uF 35v	**0.13**
410	6.8uF 16v	**0.15**	423	3.3uF 35v	**0.15**
411	10.0uF 16v	**0.16**	424	4.7uF 35v	**0.18**
412	22.0uF 16v	**0.28**	425	6.8uF 35v	**0.30**
413	33.0uF 16v	**0.50**	426	10.0uF 35v	**0.38**

FAIRCHILD/DARLINGTONS

Type	Pol	VCEO	VCBO	I.C.	HFE	Case	£.p
2N6052	PNP	-100v	-100v	12A	750-18K	TO3	**1.50**
2N6282	NPN	60v	60v	20A	750-18K	TO3	**1.25**
MJ3000	NPN	60v	60v	10A	1KMN	TO3	**1.00**
SE9300	NPN	60v	60v	10A	1000	TO220	**0.80**
SE9031	NPN	80v	80v	10A	1000	TO220	**0.85**
SE9304	NPN	80v	80v	10A	1000	TO3	**0.85**
SE9305	NPN	100v	100v	10A	1000	TO3	**1.00**
SE9401	PNP	-80v	-80v	10A	1000	TO220	**1.10**
TIP115	PNP	-60v	-60v	2A	1K	TO220	**0.40**
TIP117	PNP	-100v	-100v	2A	1K	TO220	**0.50**
TIP120	NPN	60v	60v	5A	1K	TO220	**0.60**
TIP121	NPN	80v	80v	5A	1K	TO220	**0.65**
TIP122	NPN	100v	100v	5A	1K	TO220	**0.68**
TIP126	PNP	-80v	-80v	5A	1K	TO220	**0.70**
TIP127	PNP	100v	-100v	5A	1K	TO220	**0.72**

POWER SUPPLIES

137	AC-DC Adaptor 6, 7½, 9 & 12 volts	**3.50**
138	DC-DC Adaptor 6, 7½, 9 volts	**2.70**

CABINETS

139	Teak 30 Case	**7.00**
140	Teak 60 Case	**9.50**

Access and Barclaycards accepted — just telephone our Orderline — Ware (STD 0920) 3182.
All prices exclude V.A.T., add 50p postage per order. Terms: C.W.O., cheques, Postal Orders payable to Bi-Pak at address below.

BI-PAK

SEMICONDUCTORS

Dept. E.T.I. 4, P.O. BOX 6, WARE, HERTS.
Tel: Ware (STD 0920) 3442. Telex: 817861.
Giro No. 3887006.
Visit our shop at: 3 Baldock St, Ware, Herts.

BARCLAYCARD VISA

Access — Buy it with Access

MICROBASICS

Having dealt with the hardware, Microbasics now takes a look at its use. Programmers aren't born, they're. . . . programmed? A.P. Stephenson explains how.

Programming entails far more than the mechanical mastery of the BASIC language. However cunning you are with the IF/THENs, however nifty with the FOR loops, however subtle with ON GOTOs and however flashy your attack on the keyboard, you can remain in a time-wasting rut unless all this brilliance is tempered with self-discipline.

The media in general and the American TV slush programs in particular would have us believe that programmers have an IQ of three figures and walk about with glazed eyes and swollen brains. This is absolute codswallop. The primary attribute required of a programmer is patience. The secondary attribute is a strong sense of method.

A programmer must also have compassion. Consideration for the poor wretch who must use the program afterwards is not always taken as seriously as it should be. Rather paradoxically, this compassion should also be directed inward. A month or so can elapse between the start and finishing date of even moderately sized programs, at the end of which the details of the structure seem to be indelibly printed in the mind. . . a dangerous and often entirely false assumption. A year after writing it, scrutiny of the listing may fail not only in recalling to mind how the thing works but in many cases may not even be recognised as one's own work! Superficially, this would appear to be unimportant. It worked when I wrote it so why the hell does it matter if I can't understand it now? This is a comforting philosophy if the program was perfect, complete, covered all possible variations and was immune to constructive criticism. The probability of this is about as remote as finding a farmer who confesses to making a profit. In truth, any program will eventually reveal annoying deficiencies or omissions with the result that modifications are reluctantly forced upon the original masterpiece. It is at this time that the programmer may wish a little more care had been taken in the original version. A few more REMarks, perhaps, or a few less purposeless GOTOs all over the place. . . in short, a little more compassion.

A programmer must also be willing to learn from others. To put it more bluntly, you must not be afraid to cheat a little by indulging in controlled plagiarism. Programs in magazines should be studied for novel twists, clever little short cuts or elegant new solutions to old problems. Most 'inventions' are ninety-nine percent other peoples' ideas, plus perhaps a few additions or rearrangements. The same applies to programs.

For example, the well known trick used in the PRESS ANY KEY TO CONTINUE situation:

```
200 GET K$ : IF K$ = "" THEN 200
```

must have been invented by somebody and yet we all use it at times. But this is obvious you might say. So is the safety pin *now*, but the 'inventor' is alleged to have made a fortune. There is of course a respectable middle of the road approach between blatent stealing of an entire program (perhaps with a few pathetic attempts at disguise by changing the names of a few variables) and complete avoidance of all previous ideas.

A programmer should be familiar with the programming language. This should be self-evident but surprisingly is not always the case. It is easy to become hooked on a small subset of the language and neglect some of the keywords because they are difficult to understand. The string handling keywords LEFT$, RIGHT$, MID$ AND STR$ are particularly neglected in BASIC and even subscripted variables are sometimes shunned. Before embarking on any ambitious project, any weaknesses in this area should be patched up by re-reading the manual and practising at the keyboard. Learning to program is like learning to play the piano. You practice difficult exercises even if they sound boring.

Last but certainly not least, a programmer must be dedicated. Once a program has been started, whatever difficulties arise, it must be finished. Shelving a program because it becomes difficult is disgraceful, pretending it was due to the usual 'lack of time' is worse. Unfortunately, it takes some time before you acquire an instinct for assessing the 'complexity potential' of a given programming project. However dedicated, it is no good carrying on if the project turns out to be beyond your capabilities. There is a balanced midway approach between dedication and pigheadedness which can only come with experience.

Before Sitting At The Keyboard

Serious works on programming have traditionally sneered at the thought of 'writing' a program at the keyboard. The correct approach, we are told, is to first draw the flowchart and then the coding on paper. . . only then should we sit at the keyboard. Whilst agreeing with the general principle, it is a little hard to stick rigidly to such idealistic advice. In the days when the main (or usually the only) peripheral was the printer and the keyboard was operated under time-sharing disciplines it was too expensive on paper and computer time to monopolise the keyboard for trial-and-error programming techniques. In the modern era of the personal computer the situation is easier and the advice can be taken less literally. However, it is advisable to scribble out a rough flowchart outlining the strategy to be employed before the bout of keyboard bashing.

Regarding flowcharts in general, there appears to be a growing doubt as to their usefulness in some quarters. It has even been suggested that most programmers write the program *first* and the flowchart *afterwards* just to please the academic Establishment. In other words the flowchart is used to explain how the program *was* designed rather than as a prelude to the actual design. The structure of a flowchart is beginning to show basic changes. A new idea entirely is superseding the old scheme. Thus, the flow in the new flowchart is from left to right with progressively more detailed levels of 'explanation' beneath. If you are experienced, the first left — right level is sufficient without assistance from lower levels. An idea of the difference between the old and the new can be gained by examining Fig.1 and Fig.2.

Deeper levels of even greater detail can be shown if desired. This leads on to the idea of structured programming which is a set of rules and regulations which advanced programmers are now expected to use when they are part of a team. Anyone interested should buy a book on the subject if they want to get with it! ➔

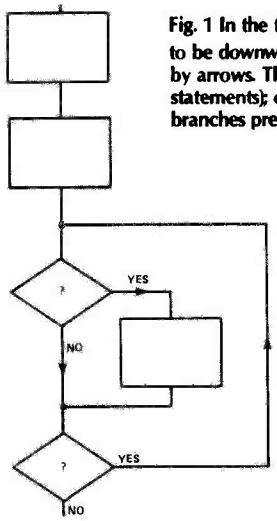


Fig. 1 In the traditional flowchart, data flow is assumed to be downwards or the right unless otherwise indicated by arrows. The diamonds are decision elements (IF/THEN statements); complex programs with many decision branches present a rather confusing appearance.

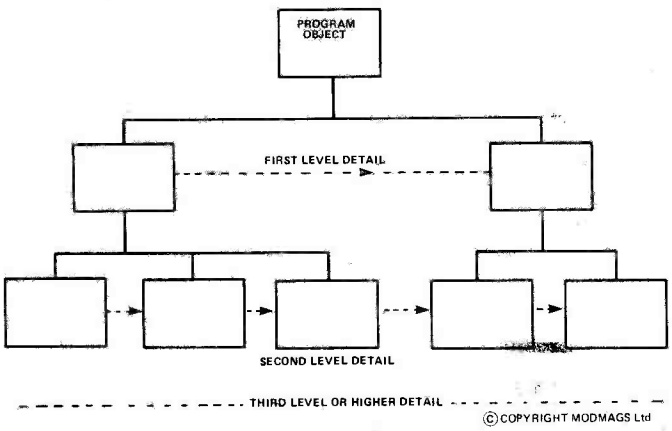


Fig. 2 In the modern flowchart, flow is only from left to right (the arrows shown are normally omitted). The different levels of detail simply 'explain' how the level above is programmed. If you are clever, the crude first level is sufficient to understand the program structure; the second level merely explains more fully how the first level works.

Back to earth again. Get hold of a folder, preferably a loose leaf ring binder, and collect vital pieces of information such as POKE numbers and codes, hex to decimal conversion tables, an abridged BASIC keyword list, the memory map (and in particular, the screen memory map), cuttings from magazine articles etc. etc. But watch the Parkinson syndrome. The binder can get fatter and fatter and particular information more and more difficult to locate as the collection grows. Be ruthless and periodically spit out the muck which, in this sense, means anything you now KNOW.

One final piece of advice . . . have some scrap paper and a pencil by the side of you. Once you get locked-on to a computer keyboard, it becomes an effort of will to get up and search for a pencil. Consequently you will try to memorise GOTO line numbers and almost certainly forget them once the listing scrolls back.

Starting At The Keyboard

Rule 1. Always have a blank (or rubbish) tape in the cassette, fully rewound, and another by the side. As soon as a reasonable segment of the program has been entered and roughly proved, get it onto tape and rewind it again. Then place the other tape in the cassette and continue with another segment and then tape it. The reason for this advice is based on the following possible hazards:

a. another member of the household or workshop, unacquainted with the volatile properties of RAM may suddenly decide to unplug the PET in order to use the iron!

b. the current segment you are working on has been the subject of an improvement . . . but a bug shows up and you get lost. Frantic efforts to remember the pre-modified version to get back to safety often fail miserably.

Under these conditions the advantage of a "fall-back" tape is obvious. By continually swopping the tapes as the program progresses, each one being a proven update of the last, much frustration can be avoided without the expensive assistance of the psychiatrist.

Rule 2. Risking the charge of advertising, PET owners should save up and get the PROGRAMMER'S TOOLKIT. This is without doubt the most useful aid to programming the PET you are ever likely to meet. Once you have used it, it appears to be indispensable. No more ragged line number sequences. No more endless searches to discover which variables have been used and which haven't. The ability to append subroutines to programs on tape is a joy to behold and operate. All this at seemingly lightening speed and idiot-proof in operation. (This should bring me a crate of whisky at Christmas).

One word of advice regarding the RENUMBERING facility. Avoid renumbering too many times during program development. This is not due to any technical reason but to the erasure of previously memorised GOTO line numbers. The TOOLKIT changes all the GOTO and THENs accordingly but it doesn't change your memory with it! As far as possible, renumber *after* the last bug has been hurled out of the system.

Developing The Program

There are no rules . . . just keep pegging away until you have 'finished'. To finish a program is perhaps the most elusive of all the arts. The elusive nature is seldom due to unexpected difficulties in the actual programming. It is a self-inflicted elusiveness resulting from, on the one hand a growing confidence, and on the other a dissatisfaction with the original terms of reference. The original moderate aim gathers momentum and the 'end' is pushed further and further away, the number of lines grow and grow, the number of variables increase, the facilities offered are increased until the bomb bursts with a polite but spine chilling message . . . "OUT OF MEMORY ERROR IN LINE 2.597E25".

The moral from all this can be summed up in one sentence: Decide the aim, stick to it, write it, debug it, test it, save it and switch off.

Testing The Program

After the crude bugs have been cleared and the programmer is satisfied with it, the real testing should now begin. It is necessary to enlist the aid of an independent guinea pig with no prior knowledge of computer keyboards. The luckless individual should be persuaded (or forced) to sit down and operate the program. Signs of consternation should be noted and the offending message from the screen should be earmarked for amendment. It is an astounding law of nature that if the message . . . "PRESS ANY KEY TO CONTINUE" meets the eye of certain guinea pigs, their diabolical little finger will jab at the STOP or the SHIFT LOCK keys; this in spite of there being about seventy other keys to assault. If you subsequently change this to PRESS SPACE BAR, the very size of the thing seems to make it transparent to the gaze and the eyes will be seen to oscillate wildly as they search for a key marked "SPACE BAR". The air usually becomes charged with emotion, sarcasm is freely interchanged between programmer and guinea pig, at times even escalating to full scale military activity. It is all very disappointing and sad for anyone trying to become a programmer. But don't let that discourage you. **ETI**

Self Instruction Courses from Cambridge Learning

They're faster and more thorough than classroom learning: you pace yourself and answer questions on each new aspect as you go. This gives rare satisfaction — you know that you are learning and without mindless drudgery. With a good self-instruction course you become the world's best teacher.

MICROCOMPUTERS ARE COMING— RIDE THE WAVE! LEARN TO PROGRAM!

MILLIONS OF JOBS ARE THREATENED, BUT MILLIONS MORE WILL BE CREATED

LEARN BASIC

The language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency with a unique style of graded hints. In 60 straightforward lessons you will learn the five essentials of programming: problem definition, flow-charting, coding the program, debugging, clear documentation. Harder problems are provided with a series of hints so you never sit glassy-eyed with your mind a blank. You soon learn to tackle really tough tasks such as programs for graphs, cost estimates, compound interest, and computer games.



COMPUTER PROGRAMMING IN BASIC (CPB) 4 Vols. £10.00

Book 1 Computers and what they do well; READ, DATA, PRINT, powers, brackets, variable names; LET; errors; coding simple programs.
Book 2 High- and low-level languages; flowcharting; functions; REM and documentation; INPUT, IF....THEN, GO TO; limitations of computers, problem definition.
Book3 Compilers and interpreters; loops, FOR....NEXT, RESTORE; debugging; arrays; bubble sorting; TAB.
Book 4 Advanced BASIC; subroutines; string variables; files; complex programming; examples; glossary.

THE BASIC HANDBOOK (BHB) £11.50

This best-selling American title usefully supplements our BASIC course with an alphabetical guide to the many variations that occur in BASIC terminology. The dozens of BASIC 'dialects' in use today mean programmers often need to translate instructions so that they can be RUN on their system. The BASIC Handbook is clear, easy to use and should save hours of your time and computer time. A must for all users of BASIC throughout the world.

A.N.S. COBOL (ANS) £5.90

The indispensable guide to the world's No. 1 business language. After 25 hours with this course, one beginner took a consulting job, documenting oil company programs and did invaluable work from the first day. Need we say more?

Flow Charts and Algorithms

are the essential logical procedures used in all computer programming and mastering them is the key to success here, as well as being a priceless tool in all administrative areas - presenting safety regulations, government legislation, office procedures etc.


THE ALGORITHM WRITER'S GUIDE (AWG) £4.00

explains how to define questions, put them in the best order and draw the flow chart, with numerous examples.

JOIN THE DIGITAL REVOLUTION!

DESIGN OF DIGITAL SYSTEMS (DDS) 6 Vols. £13.50

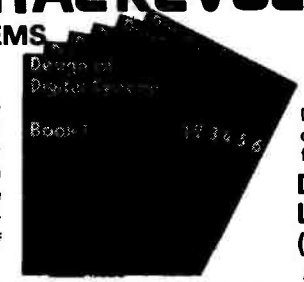Written for the student or enthusiast, this course is packed with information, diagrams, and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters, and simple arithmetic circuits; and finally to an understanding of the design and operation of calculators and computers




BOOK 1 *Decimal, Octal,* hexadecimal, *and binary number systems and conversion between number systems;* negative numbers; complementary systems. **BOOK 2** *OR and AND functions; multiple-input gates; truth tables; De Morgan's Laws;* canonical forms; logic conventions; Karnaugh mapping; three-state and *wired logic.* **BOOK 3** *Half,* full, serial, and parallel *adders;* subtraction; processors and ALU's; multiplication and division. **BOOK 4** *flip flops; shift registers; asynchronous,* synchronous, *ring,* Johnson, and exclusive-OR feedback *counters; ROMS and RAMS.* **BOOK 5** Structure of calculators; keyboard encoding; decoding display-data; register systems; control unit; PROM; address de-coding. **BOOK 6** CPU; memory organisation; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems.

Digital calculators and watches came in during the 1970's. Soon you will see digital cash cards, telephones, car instruments, and TV messages from your friends.

DIGITAL COMPUTER LOGIC AND ELECTRONICS (DCL) 4 Vols. £7.50

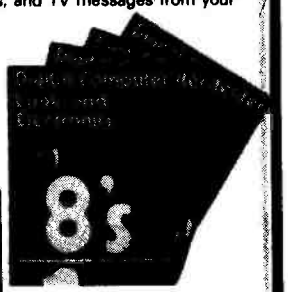A course covering the material in *italics* on the left, but at a slower pace. (4 vols)



GUARANTEE — No risk to you. If you are not completely satisfied your money will be refunded without question, on return of the books in good condition within 28 days. Our free booklist is sent with each order.

CAMBRIDGE LEARNING LTD. (Registered in England No. 1328762)

Unit 11, Rivermill Site, FREEPOST, St. Ives, HUNTINGDON, Cambs PE17 4BR. Phone 0480 67446

Order Form

To: Cambridge Learning Ltd., Unit 11, Rivermill Site, Freepost, St. Ives, Huntingdon, Cambs. PE17 4BR

PLEASE SEND: Quantity

CPB	(£10.00)	
BHB	(£11.50)	
ANS	(£5.90)	
AWG	(£4.00)	
DDS	(£13.50)	
DCL	(£7.50)	

THESE PRICES COVER THE COST OF SURFACE MAIL WORLDWIDE, AIRMAIL: Europe, North Africa, Middle East, add ½ to price of books. Japan, Australia, New Zealand, Pacific Islands add ⅔. Elsewhere add ½.

U.K. Delivery: up to 28 days (or send 50p per course for 1st class post.)

Name .....

Address .....

.....

.....

.....

FOUR WAYS TO PAY:
1) A U.K. cheque or a U.K. postal order (Not Eire)
2) A bank draft, in sterling on a London bank (available at any major bank)
3) Please charge my Access/American Express/Barclaycard/Diners Visa/Mastercharge/Trustcard


Card No .....

Expiry Date .....

Signed .....

Or phone us with these credit card details on 0480 67446 (24 hour ansafone service)

SPRING IS HERE

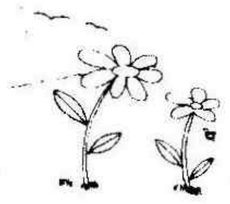


AND MEN'S THOUGHTS TURN TO . . . OUR AMAZINGLY LOW PRICED SPECIAL OFFERS!?!

Closing date 31.4.81 — Don't forget P&P and V.A.T. to your order

6 x 555	£1.00	LEDs 0.2"		15 x BC182	£1.00
6 x 741	90p	10 each red, green, yellow	£2.50	15 x BC212	£1.00
IC Sockets		LM3915 + 10-element LED display	£3.20	4 x C106D	£1.00
15 x 8 pin	£1.00	Liquid Crystal Display, 3½ 0.5" digits, d.p.i.	£4.00	6 x CD4011 C MOS	£1.00
12 x 14 pin	£1.00	2 x TIC226D 8A/400V Triacs	£1.00	Voltage Regulators	
10 x 16 pin	£1.00	2 x TIC236D 12A/400V Triacs	£1.35	2 x 7805	£1.00
8 x 18 pin	£1.00			2 x 7812	£1.00
6 x 22 pin	£1.00			2 x 7815	£1.00

★ **BONUS** ★ Further 5% discount if you buy the lot **(£24.75 + VAT)**

REMOTE CONTROL COMPONENTS AND KITS

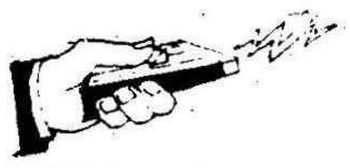



LD271 IR Emitting diode	.36	ML926 16-channel receiver 4 momentary binary outputs	1.40
SFH205 Photodiode Detector	.90	ML928 16-channel receiver, 4 latched binary outputs	1.40
SL480 IC Pulse Amp.	1.70	ML929 16-channel receiver, 4 latched binary outputs	1.40
SL490 32 Command Encoder/transmitter	2.40	Clip-on Plastic Reflector for IR LEDs, increases range	.20
ML922 10-channel receiver + 3 analogue outputs	4.20		

NEW ML925. A decoder designed for model/toy control, providing a 2-speed drive motor and three position latched steering system or a vehicle with momentary action steering and a third motor, eg. gun turret, winch, etc. Outputs also available for other facilities such as horn, turn indicators, headlights, etc. **2.10**

To make things EVEN EASIER, we have designed several new kits: —

MK6 — Simple Infra Red TRANSMITTER. A Pulsed infra red source which comes complete with a hand held plastic box. Requires a 9V battery. **4.20**

MK7 — Infra Red RECEIVER. Single channel, range approximately 20 ft. Mains powered with a triac output to switch loads up to 500W at 240Vac, but can be modified for use with 5 to 15V dc supplies and transistor or relay outputs. **9.00**

* Special Price * MK6 and MK7 together. Order as RC500K. **12.50**

MK8 — Coded Infra Red TRANSMITTER. Based on the SL490, the kit includes 2 IR LEDs, measures only 8x2x1.3 cms. and requires a 9V (PP3) battery. **5.90**

MK9 — 4 Way KEYBOARD. For use with the MK8 kit, to make a 4-channel remote control transmitter. **1.90**

MK10 — 16-Way KEYBOARD. For use with the MK8 kit, to generate 16 different codes for decoding by the ML928 or ML926 receiver (MK12) Kit **5.40**

MK11 — 10 On-Off Channel IR RECEIVER with 3 analogue outputs (0-10V) for controlling such functions as lamp brightness, volume, tone, etc. Other functions include an on/standby output and a toggle output, which may be used for sound muting. Based on ML922 decoder IC. Includes its own mains supply **12.00**

MK12 — 16 Channel IR RECEIVER. For use with the MK8 kit with 16 on/off outputs which with further interface circuitry, such as relays or triacs, will switch up to 16 items of equipment on or off remotely. Outputs may be latched or momentary, depending on whether the ML926 or ML928 is specified. Includes its own mains supply. **11.95**

MK13 — 11-Way KEYBOARD. For use with MK8 and MK11 kits. Transmits programme step + and —, analogue + and — (3), mute, normalise analogue outputs, and on/standby **4.35**



24HR. CLOCK/APP. TIMER KIT



Switches any appliance up to 1KW on and off at preset times once per day. Kit contains AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac, PCBs & full instructions

CT1000K Basic Kit **£14.90**

CT1000KB with white box (56/131 x 71mm) **£17.40**

Ready Built **£22.50**

LIGHTING CONTROL KITS

Directly replace conventional light switch and control up to 300W of lighting. No mains rewiring. Insulated touchplates. Easy to follow instructions.

TD300K TOUCHDIMMER. Single touchplate with alternate action. Brief touch switches lamp on and off, longer touch dims or brightens lamp. Neon lamp helps find the switch in the dark **£6.50**

TDE/K Extension kit for TD300K for 2-way switching, etc. **£2.00**


TSA300K TIMEDELAY TOUCHSWITCH. Delay variable from 2 secs to 3½ mins. **£4.30**

LD300K Conventional LIGHTDIMMER **£3.20**

DISCO LIGHTING KITS

Each unit has 4 channels (rated at 1KW at 240V per channel) which switch lamps to provide sequencing effects, controlled manually or by an optional opto isolated audio input.

DL 1000K

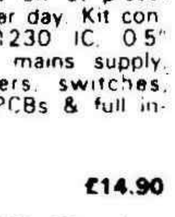

This kit features a bi-directional sequence, speed of sequence and frequency of direction change being variable by means of potentiometers. Incorporates master dimming control. **£14.60**


DLZ1000K



A lower cost version of the above, featuring undirectional channel sequence with speed variable by means of a preset pot. Outputs switched only at mains zero crossing points to reduce radio interference to minimum. **£8.00**

Optional Opto Input DLA1 **60p**

DIGITAL VOLTMETER/ THERMOMETER KIT

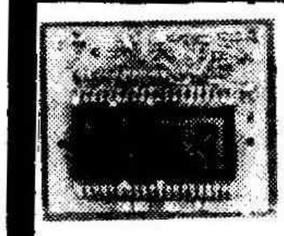

Based on the ICL 7106. This kit contains a PCB, resistors, presets, capacitors, diodes, IC and 0.5" liquid crystal display. Components are also included to enable the basic DVM kit to be modified to a Digital Thermometer using a single diode as the sensor. Requires a 3mA 9V supply (PP3 battery). **£19.50**

MINI KITS

These kits form useful subsystems which may be incorporated into larger designs or used alone. Kits include PCB, short instructions and all components

MK1 TEMPERATURE CONTROLLER/ THERMOSTAT
Uses LM3911 IC to sense temperature (80°C max) and triac to switch heater. 1KW **£4.**

MK2 SOLID STATE RELAY
Ideal for switching motors, lights, heaters, etc from logic. Opto-isolated with zero voltage switching. Supplied without triac. Select the required triac from our range **£2.60**


MK3 BAR/DOT DISPLAY
Displays an analogue voltage on a linear 10-element LED display as a bar or single dot. Ideal for thermometers, level indicators, etc. May be stacked to obtain 20 to 100 element displays. Requires 5-20V supply **£4.75**

MK4 PROPORTIONAL TEMPERATURE CONTROLLER
Based on the TDA1024 Zero voltage switch, this kit may be wired to form a "burst fire" power controller or a "proportional temperature" controller enabling the temperature of an enclosure to be maintained to within 0.5°C.
3KW **£5.55**

MK5 MAINS TIMER
Based on the ZN1034E Timer IC this kit will switch a mains load on (or off) for a preset time from 20 minutes to 35 hours. Longer or shorter periods may be realised by minor component changes. Maximum load 1KW **£4.50**

TRIACS


400V Plastic Case (Texas)

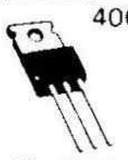


3A TIC206D	49p
8A TIC226D	58p
12A TIC236D	85p
16A TIC246D	95p
25A TIC263D	190p
6A with trigger Q4006LT	80p
8A isolated tab TXAL226B	65p
Diac	18p

ARE YOU SITTING COMFORTABLY?

Our new TDR300K Touch Dimmer Kit will ensure that you are. Based on our highly successful TD300K touch controlled dimmer kit, the TDR300K incorporates an infra red receiver, enabling the lamp brightness to be varied and switched on or off by touch or remotely by means of a small hand held transmitter. The complete kit, which includes easy to follow instructions, will fit into a plaster depth box and the plastic front plate has no metal pads to touch, ensuring complete safety. Even a neon is included to help you locate the switch in the dark.

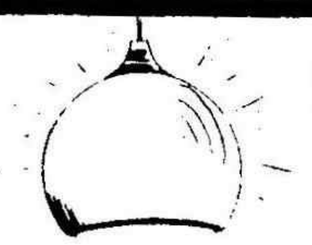

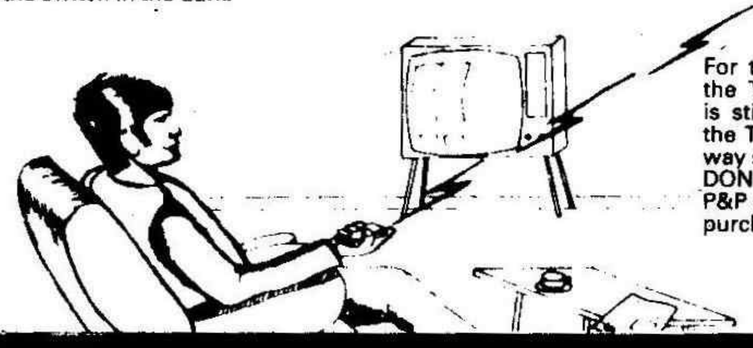In years to come everyone will be selling remote control dimmers, but you can have your TDR300K kit now for ONLY £14.30 for the dimmer unit and £4.20 for the transmitter.



For the more athletic of you, the TD300K Touchdimmer kit is still available at £6.50 and the TDE/K Extension kit, for 2-way switching etc., is £2.
DON'T FORGET to add 50p P&P and 15% VAT to your total purchase.


INTEGRATED CIRCUITS



555 Timer	21p
741 Op. Amp	19p
AY-5-1224 Clock	£2.60
AY-5-1230/2 Clock/Timer	£4.50
AY-3-1270 Thermometer	£8.20
ICL7106 DVM (LCD drive)	£7.00
LM377 Dual 2 W Amp	£1.45
LM379S Dual 6W Amp	£3.50
LM380 2W Audio Amp	80p
LM382 Dual/low noise Preamp	£1.00
LM386 250mW low voltage Amp	75p
LM1830 Fluid Level Detector	£1.50
LM2907 f-v Converter (8 pin)	£1.40
LM2917 f-v Converter (14 pin)	£1.60
LM3909 LED Flasher/Oscillator	80p
LM3911 Thermometer	£1.20
LM3814 Dot/Bar Driver (Lin)	£2.10
LM3915 Dot/Bar Driver (log)	£2.20
MM74C911 4 digit display controller	£6.50
MM74C915 7 segment-BCD converter	98p
MM74C926 4 digit counter with 7 seg o/p	£4.50
S566B Touchdimmer	£2.50
SL440 AC powered control	£1.75
SN76477 Complex Sound Generator	£2.52
TBA800 5W Audio Amp.	88p
TBA810AS 7W Audio Amp.	£1.00
TDA1024 Zero Voltage Switch	£1.20
TDA2020 20W Audio Amp.	£2.85
ZN1034E Timer	£1.80

All ICs supplied with data sheets
Data Sheets only 10p each device.


MINI TRANSFORMERS

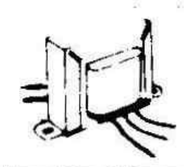

Standard mains primaries 240V a.c.
100mA secondaries
6-0-6V 80p
9-0-9V 85p
12-0-12V 90p

Opto Isolated **TRIAC**
MOC 3020 400v **£1.10**

LEDs

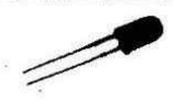

0.1" Red	9p
0.1" Green	12p
0.1" Yellow	12p
0.2" Red	9p
0.2" Green	12p
0.2" Yellow	12p
0.2" clips	3p
Rectangular Red	16p
Rectangular Green	17p
Rectangular Yellow	17p
Flat Face Rectangular, Triangular, Arrowhead, Square	
Red	17p
Green	20p
Rec. Yellow	20p

DISPLAYS



DL304 Red 0.3" c.c. pin compatible with DL704 **75p**
DL307 Red 0.3" c.a. pin compatible with DL707 **75p**
DL727 Dual 0.5" c.a. Red **£1.50**
MP463 0.5" c.c. Red, four digit multiplexed **£2.20**

CMOS

4000	17p	4019	42p	4069	19p
4001	18p	4023	22p	4070	19p
4002	18p	4025	21p	4071	18p
4007	17p	4026	£1.30	4077	26p
4011	19p	4027	40p	4081	20p
4012	17p	4028	50p	4093	54p
4013	38p	4040	80p	4501	24p
4015	75p	4049	38p	4511	90p
4016	35p	4050	40p	4514	£1.80
4017	70p	4060	£1.08	4516	£1.80

D.I.L. I.C. SOCKETS

8 pin	8p	18 pin	17p
14 pin	12p	28 pin	24p
16 pin	14p	40 pin	38p
Soldercon Pins			50p/100

CAPACITORS

Polyester 250V

0.01	6p	0.22	12p
0.002	6p	0.33	12p
0.033	7p	0.47	15p
0.047	7p	0.68	18p
0.068	7p	1.0	24p
0.1	7p	1.5	27p
0.15	12p	2.2	31p

Electrolytics A Axial R Radial

63V	1.0	R	5p	16V	10	R	5p
	2.2	R	5p		22	R	5p
	4.7	R	6p		33	R	5p
	10	R	7p		47	R	6p
	47	R	12p		100	R	8p
25V	22	A	8p		220	R	11p
	47	A	10p		470	R	14p
	100	A	14p		1000	R	20p
	110	A	15p	10V	47	A	8p
	470	A	24p		100	A	8p
	1000	A	34p		220	A	12p

Tantalum (bead)


35V	0.1	9p	10V	22	20p
	0.22	9p	6.3V	33	20p
	0.47	9p		47	27p
	1.0	9p	3V	100	27p
25V	2.2	10p			
	4.7	14p			
	10	20p			

Ceramic 50V			
100pF	4p	1,000pF	4p
220pF	4p	2,200pF	4p
470pF	4p	4,700pF	5p
		10,000pF	5p

BOXES

Moulded in high impact ABS. Supplied with lids and screws. Black.

B1 75x6x35mm	65p
B2 95x71x35mm	85p
B3 115x95x37mm	95p

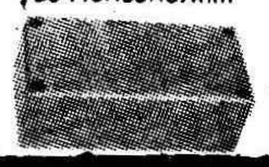


ZENER DIODES

400mW 3.3V-30V	8p
1.3W 7.5-27V	15p

RESISTORS

¼W 10 ohm-10M, E12 series
Pack of 10 (one value) 10p
10 Packs (10 values) 80p

VOLTAGE REGULATORS

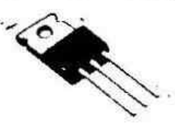

Available in 5V, 12V & 15V versions.
78L series 100mA pos. **26p**
79L series 100mA neg. **60p**
78 series 1A pos. **52p**

LM317T adjustable 1.2V-37V 1.5A **£1.80**

RECTIFIERS

1N4001 1A/50V	4p
1N4004 1A/400V	6p
1N5401 3A/50V	8p
1N5404 3A/400V	10p
1A 50V Bridge	19p
1A 400V Bridge	22p
3A 50V Bridge	48p
3A 400V Bridge	58p

(Bridge rectifiers are miniature PCB mounting types)

VMOS POWER FETS

VN10KM 0.5A/60V (TO92)	52p
VN66AF 2A/60V (TO220)	88p

TRANSISTORS

BC108	8p	BFY50	20p
BC182	8p	TIP31A	40p
BC182L	8p	TIP32A	40p
BC212	9p	2N3055	45p
BC212L	9p	2N3442	90p
BC337	16p	2N3819	20p

ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION. ADD 50p P&P and 15% VAT TO TOTAL. OVERSEAS CUSTOMERS ADD £1.50 (Europe), £4 (elsewhere) for P&P. Send sae for price list and with all enquiries. Callers welcome 9.30-5.00 (Mon-Fri) 10.00-4.00 (Sat).

TK Electronics

(ETI), 11 BOSTON ROAD
LONDON W7 3SJ. 01-579 9794



58

NOISE GENERATOR

Despite what the average audiophile will tell you, noise can be useful. This noise generator with sample and hold facility is the basic building block for Project 80 sound effects. Design and development by Charles Blakey.



Noise sources are essential for the synthesis of many sounds. These range from musical instruments, such as pipe organ and percussive devices, to natural sounds like wind, rain and surf, and to man-made sounds such as steam engines, explosions and gunfire. The 80-12 module provides white noise, which has the characteristic hissing sound, pink noise, which is deeper in intensity, and a low frequency noise (sometimes referred to as red noise). The low frequency noise may also be used as a random modulating source.

A sample and hold circuit, also incorporated, allows external sound sources to be sampled and converted into control voltages for, say operating a VCO. The sample and hold unit, therefore, provides a means by which the synthesiser can play itself.

Noisy Networks

In this design white noise is produced by reverse biasing an NPN transistor, since this method produces a wide bandwidth. The main problem with this technique is the low amplitude of the noise and often the need to try several transistors to attain the desired amplitude. This has been largely overcome by using a two stage amplifier, IC1a and IC1b, which allows the overall gain to be varied between about 100 to 5700 times. As an additional safeguard the transistor is mounted in a socket to facilitate trying other devices, should the amplitude prove insufficient. White noise is defined as having equal energy per cycle and pink noise equal energy per octave. To derive the latter requires the white noise to be filtered at — 3 dB/octave and, since filters usually have slopes of 6 dB/octave, a 3 dB type has to be approximated. Note that other variations in noise colouration may be obtained by filtering the white or pink noise with Project 80 filters 80-6 or 80-7. The low frequency noise is obtained by low pass filtering the pink noise using a 6 dB/octave filter with a cut-off frequency of about 16 Hz (constructed around IC1d). The white and pink noise outputs will be in the range 5-10 V p-p while the low frequency noise is 10 V p-p.

The sample and hold circuit uses the principle of gating a FET, Q2, on and off and storing the sampled voltage on C16, which is buffered by voltage follower IC5b. FET gating is achieved using a CA3140E, configured as a comparator such that a positive clock pulse will cause it to go high (about 13 V) and allow the signal through to be stored on C16. When the clock pulse is near zero, IC4 will swing to about -14 V and gate the FET off. If the signal being sampled is varying rapidly in amplitude, it is essential that the clock pulse be short otherwise the output will not be in discrete steps but will follow the variations in signal amplitude while the clock pulse is high.

The internal clock in the 80-12 uses a CMOS 555 timer whose sampling rate may be varied from about 1 cycle per 4.5 S to 25 Hz. The pulse width is adjustable and the output from the clock, buffered by IC3, is available for use as, say, a synchronising trigger on an ADSR. Provision is made for using an external clock and the pulse output from the 80-2 VCO or 80-3 VCLFO is suitable.

Achieving the desired results depends on the clock rate and the amplitude of the signal being sampled. The latter may be attenuated by RV2. Additionally, when using a VCO as the clock, the pulse width is another variable for special effects.

PROJECT 80 NEWSFLASH: Due to considerations of space and time, the final Project 80 module, a combined effects unit (containing an external Input Interface and Dual Ring Modulator), the system keyboard and the keyboard controller will now be available in a booklet at the end of February. To get your copy send a cheque or postal order for £2.95 (including postage and packing) to: ETI/Project 80, 145 Charing Cross Road, London WC2H 0EE.


Construction And Setting Up


Setting up the noise generator is simply achieved by adjusting PR1 to obtain the desired amplitude. This may be done in three ways: (a) using a DMM on the white noise output and adjusting PR1 until a reading of about 1V8 to 3V2 is obtained on the AC range; (b) using an oscilloscope and observing the white noise output while adjusting PR1 to obtain a peak to peak output of 5-10 V; or (c) connecting the output of the low frequency noise at R16 to a DC voltmeter and adjusting PR1 until occasional readings of about - 7 V are obtained when observed over a period of a few minutes. With most analogue meters the above readings will be approximately halved. With some transistors it may be possible to obtain the correct amplitude of the white and pink noise by increasing the gain with PR1, but the amplitude of the low frequency noise will be too high. In the latter circumstances the best approach is to try another NPN transistor rather than alter the value of R14.

Only one adjustment is required in the sample and hold section, namely, to adjust PR2 to obtain a short pulse output from the internal clock based on IC2. This adjustment should be made in the following sequence:-

a) Connect the low frequency noise output to the signal input of the sample and hold with RV2 fully clockwise. ➔

b) Connect the output of the sample and hold to a VCO with the coarse frequency control set to mid position and one of the waveforms connected to an amplifier.
c) Set RV1 (clock rate) to about 75% rotation which should give a sampling rate of about 2-3 Hz.
d) Turn PR2 fully anti-clockwise and switch power on.
e) After a few seconds delay slowly turn PR2 clockwise until the VCO output starts changing frequency in a step-wise manner.
f) Finally check that the VCO continues to change step-wise over the full range of the internal clock (RV1) and if necessary turn PR2 further clockwise until this is achieved.

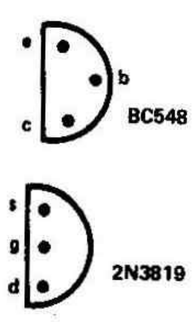

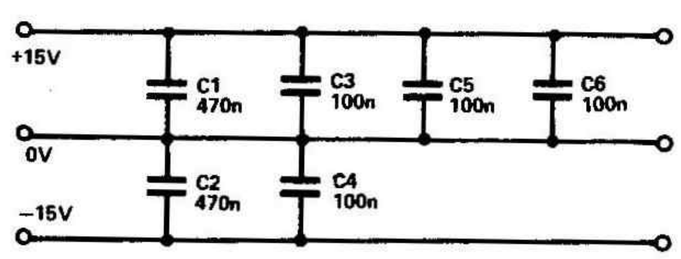

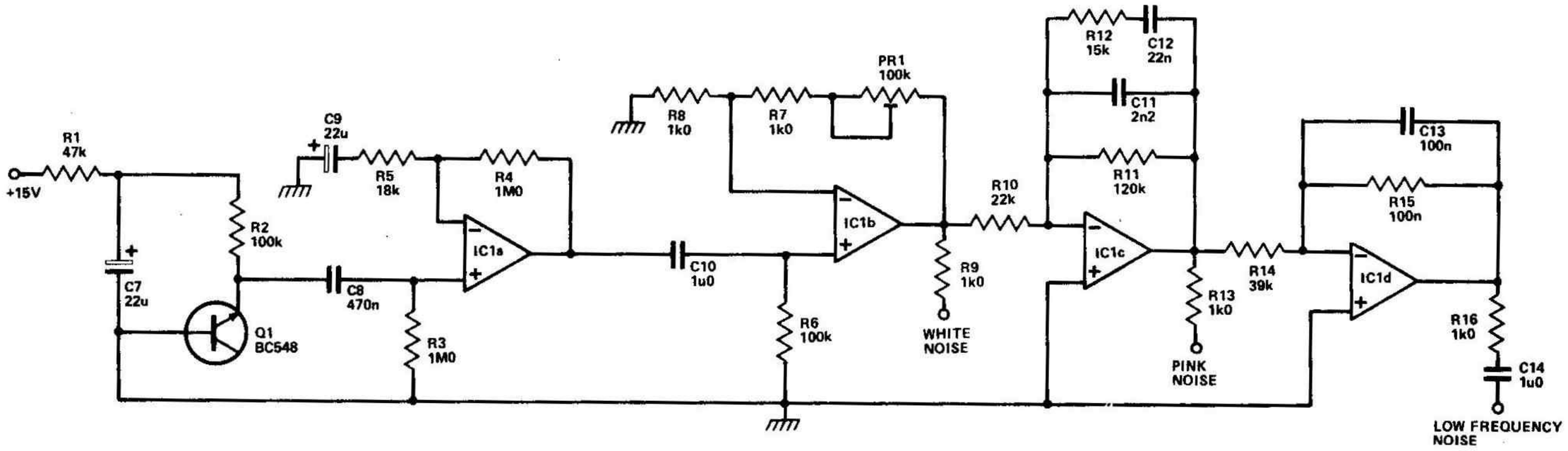


Fig.1 Circuit diagram.

HOW IT WORKS

Reverse biasing the NPN transistor, Q1, will generate noise at its base-emitter junction. The few millivolts of noise at the output of Q1 has to be amplified to the levels required for the synthesiser and this is achieved with two AC coupled non-inverting amplifiers configured around IC1a and IC1b. The gain of IC1a is fixed at about 56 while the gain of the IC1b amplifier may be adjusted from 2 to 102 by means of PR1. The overall gain of the amplifier section may, therefore, be varied from 113 to 5760 times. The amplified white noise is available via R9.

To obtain pink noise it is necessary to filter the white noise by - 3 dB/octave and a close approximation over the audio range is obtained with the active filter built around IC1c. R11 and C11 form a first order low pass filter with a cut off frequency of 663 Hz, while R12 and C12 are an augmenting integrator which has an output proportional to the input signal added to an output proportional to the time integral of the input signal. The frequency response of the latter is relatively flat above about 1 kHz and below this frequency the incoming signal is attenuated at a rate of 6 dB/octave. The combination of R11/C11 with R12/C12 achieves the - 3 dB/octave response and the pink noise output is available at R13. The low frequency noise is obtained by using a first order low pass filter with a cut off frequency of about 16 Hz and this is obtained with IC1d, R15 and C13 with the output being available via R16 and C14.

In the sample and hold network a signal is applied to the source of FET, Q2, via IC5a configured as a voltage follower and whose signal input may be attenuated by RV2. When Q2's gate is positive, the signal passes through and the voltage present at the signal input will change the voltage on C16 accordingly. If Q2 is gated off the last voltage on C16 is held, since leakage is kept low by buffering it with a voltage follower based on IC5b. By sampling the input for only very short durations, the voltage on C16, available at R27, will be a series of discrete steps which may in turn be used to control voltage controlled modules. The negative to positive voltage transition for gating Q2 on for sampling is obtained with IC4 configured as a comparator. With a near zero voltage at the non-inverting input of IC4 its output will be close to the negative rail voltage of - 15 V and Q2 will be off. When a positive pulse is applied to the non-inverting input then IC4 goes positive (about + 13 V) and turns on Q2 so that a sample of the signal voltage can be taken and stored on C16. The internal clock used to turn Q2 on and off via IC4 is based on CMOS 555 timer, IC2. The pin configuration and operational features are the same as a bipolar 555 but the CMOS version has advantages in terms of power consumption and absence of crowbarring the power supply during the output transition. A conventional astable configuration is used and, while D1 allows a wide range of duty cycle, the main adjustment for the latter is the application of a positive voltage to its control voltage input, pin 5, via PR2. The output of the timer is buffered by IC3 so that it may be used for external synchronisation purposes. The output also goes via an SPDT switch, SW1, to comparator IC4. The switch allows external clock sources to be used.

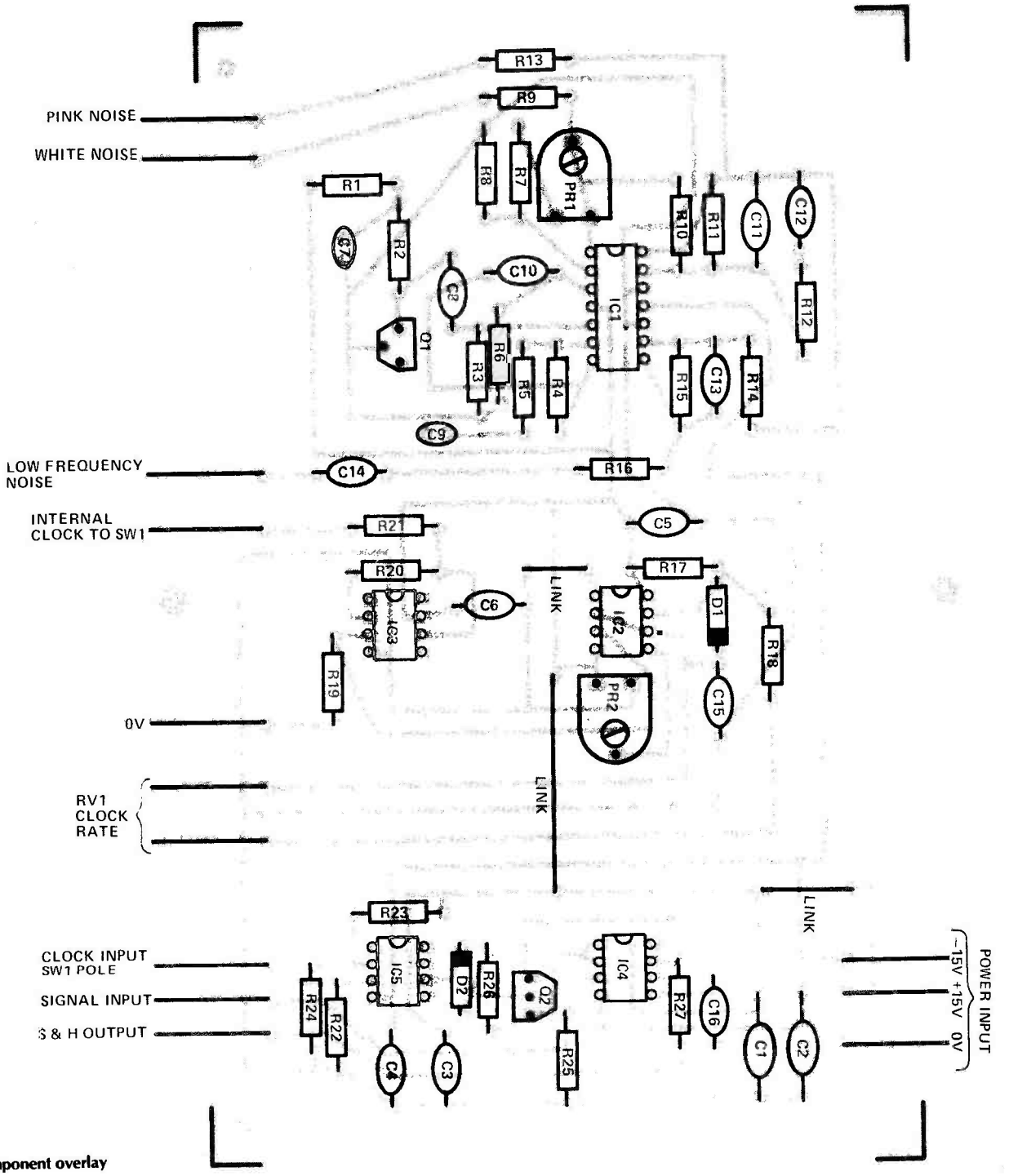


Fig.2 Component overlay

PARTS LIST

Resistors ¼ W 5% carbon

R1,18	47k
R2,6,15,19,22,23,25	100k
R3,4,26	1M0
R5	18k
R7,8,9,13,16,27	1k0
R10	22k
R11	120k
R12	15k
R14	39k
R17	8k2
R20	3k9
R21,24	10k

Capacitors

C1,2	470n polyester
C3,4,5,6,13	100n polyester
C7,9	22u 25V PCB electolytic
C8	470n MKH polyester
C10,14,15	1u0 MKH polyester
C11	2n2 polystyrene
C12	22n polycarbonate
C16	220n MKH polyester

Potentiometers/Trimmers

RV1	4M7 linear
RV2	100k linear
PR1	100k carbon
PR2	470k carbon


Semiconductors


IC1	LM348N
IC2	ICM7555 IPA
IC3,4	CA3140E
IC5	TL082 CP
D1, 2	1N4148
Q1	BC548
Q2	2N3819

Miscellaneous

SW1	SPDT miniature toggle
Transistor holder	

PROJECT : Noise Generator

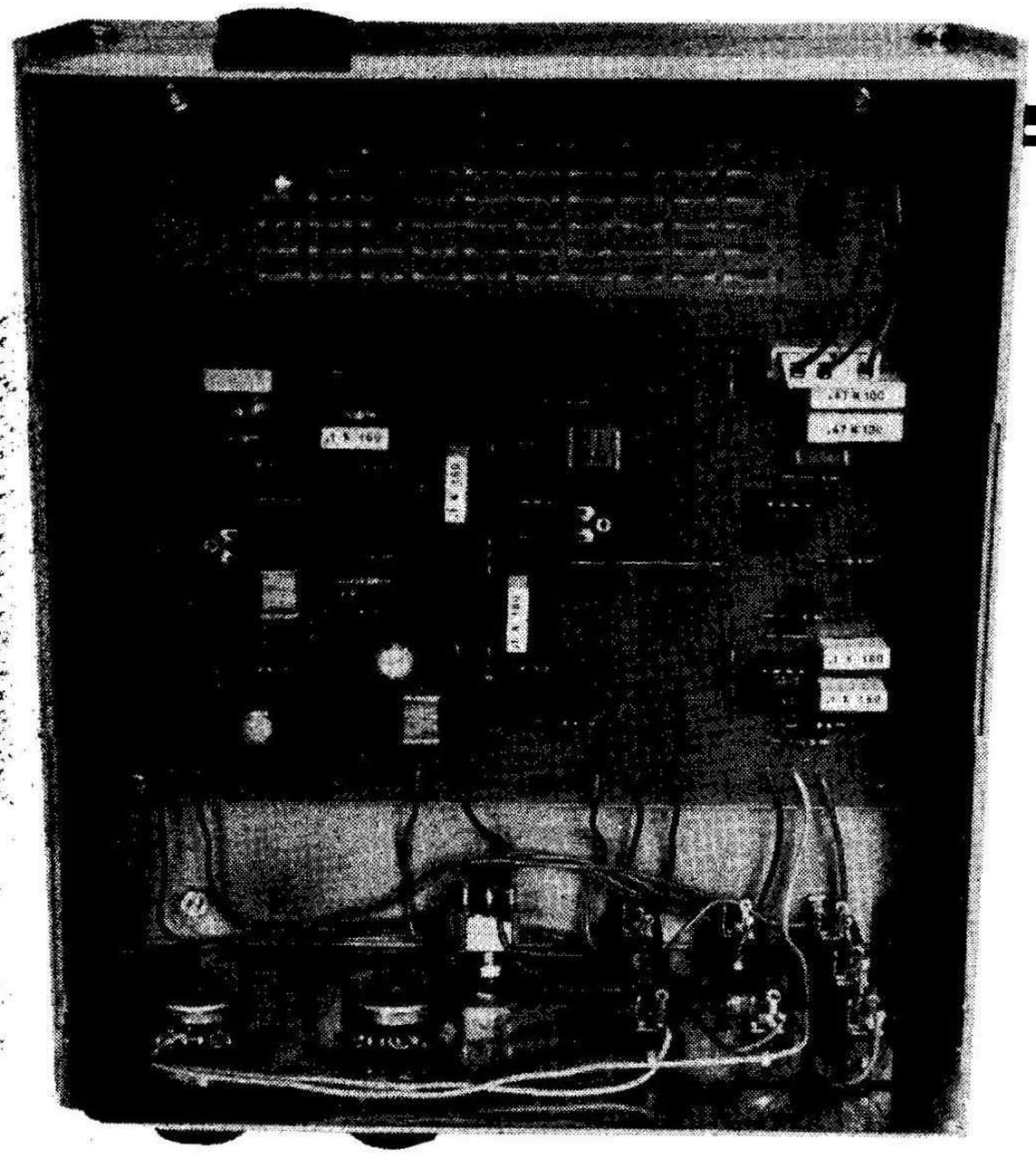

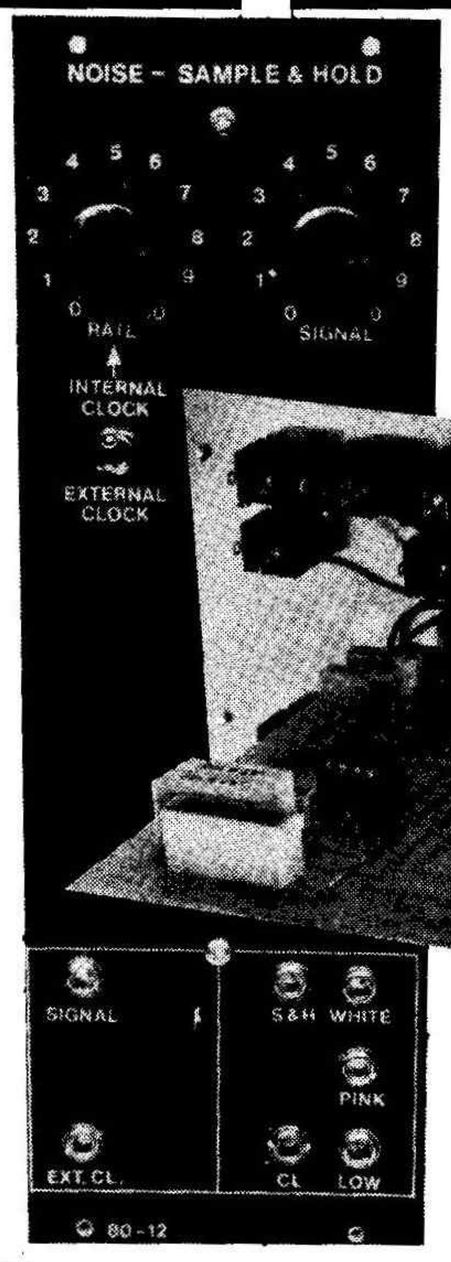

Each Project 80 module can be housed in a West Hyde Developments' Teko Alba A23G case (far left) or on a front panel only (left).


All the modules can be mounted on front panels (above) and cased together in one cabinet.

BUYLINES

The 80-12 Noise Generator — Sample & Hold module is available as a kit with PCB and all listed components for £13.17, inclusive of postage and VAT, from Digisound Limited, 13 The Brooklands, Wrea Green, Preston, Lancs. PR4 2NQ.

ETI

The 2001 sweeps the board at only £78*

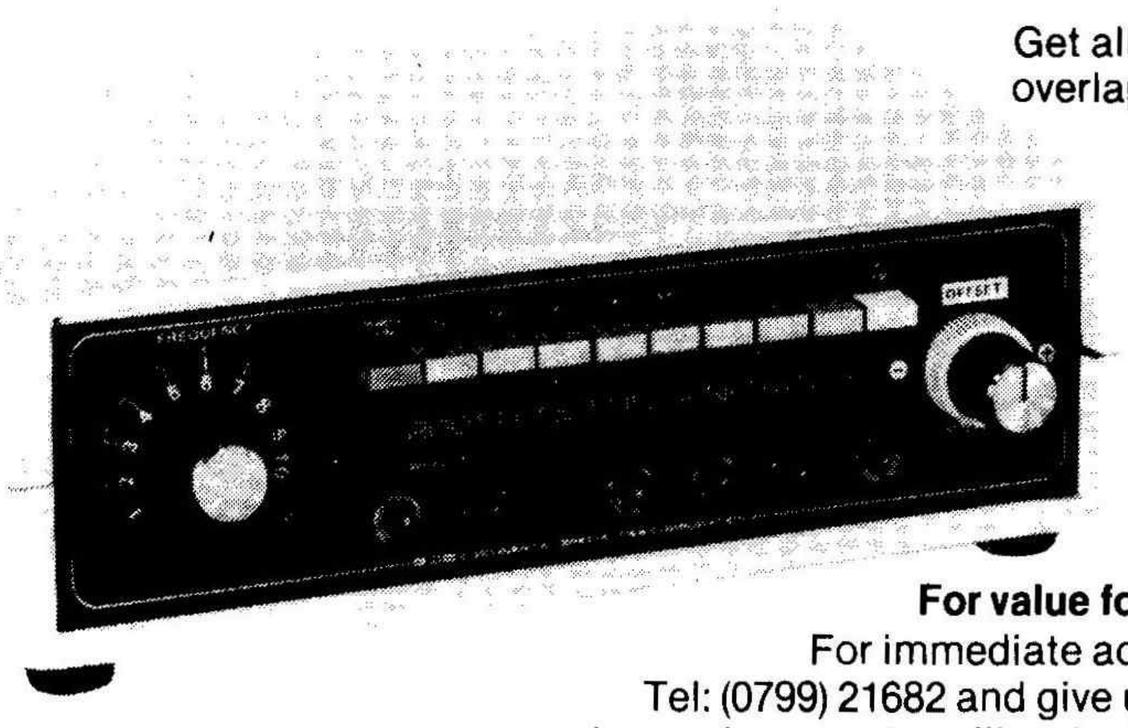

Get all the waveforms you need – 1 Hz to ·1 MHz in five overlapping ranges: stable, low-distortion sine waves, fast rise/fall-time square waves, high linearity triangle waves — even a separate TTL square wave output. Plus high- and low-level main outputs.
An applied DC Voltage at the Sweep input can shift the 2001's frequency: or sweep up to 100: 1 with an AC signal.
A pushbutton activates the DC Offset control, which shifts the output waveform up or down on command.

For value for money the 2001 sweeps the rest off the board.

For immediate action — The G.S.C. 24 hour, 5 day a week service Tel: (0799) 21682 and give us your Access, American Express, Barclaycard number and your order will be in the post immediately or just clip out the coupon.

*price excluding P&P and 15% VAT

GLOBAL SPECIALTIES CORPORATION

GSC

G.S.C. (UK) Limited
Dept. 9HH Unit 1, Shire Hill Industrial Estate
Saffron Walden, Essex CB11 3AQ
Tel: Saffron Walden (0799) 21682 Telex 817477

Global Specialties Corporation (UK) Limited
Dept 9HH Unit 1, Shire Hall Industrial Estate, Saffron Walden, Essex CB11 3AQ

Model 2001 Sweepable Function Generator	**£91.43** (inc. P&P and 15% VAT)	Qnty Reqd.		For FREE catalogue tick box [

Name ..... Address .....

.....

I enclose PO/Cheque for £..... or debit my Barclaycard/Access/American Express No ..... exp date .....

SUBSCRIPTIONS



This year we present a new twelve-part, non-fiction series — ETI 1981. . . . . available from your newsagent every month.

Forget to buy it this month, or is your newsagent sold out?

Why worry when ETI gets to the shop? Sit back and wait for it to come to you. Take out an ETI Subscription. For only £11.00 we'll send you twelve issues of ETI.

To claim your years' supply of ETI, send your PO or cheque direct to :

ETI Subscriptions,
Modmags Ltd,
145 Charing Cross Road,
London WC2H 0EE

It's easy to complain about advertisements.

The Advertising Standards Authority.
If an advertisement is wrong, we're here to put it right.
A.S.A. Ltd., Brook House, Torrington Place, London WC1E 7HN.

MIGHTY NINETY PACKS

SUPER VALUE PACKS ALL AT 90p EACH
POSTAGE 15p PER PACK UP TO FOUR PACKS
FIVE OR MORE POST FREE
BUY SIX PACKS AND GET A SEVENTH PACK FREE!

MN1. 300 ¼-watt Resistors pre-formed for P&C Mtg.
MN2. 200 ¼ & ½-watt Resistors.
MN3. 100 1 & 2-watt Resistors.
MN4. 50 Wirewound Resistors.
MN5. 100 metal oxide Resistors. 1%, 2% and 5%.
MN6. 12 asstd. potentiometers.
MN7. 25 asstd. skeleton pre-set Resistors.
MN8. 50 asstd. Electrolytic Capacitors.
MN9. 100 asstd. Ceramic Capacitors. Plte, disc, tub and monolythic etc.
MN10. 100 mixed capacitors. Polyester, Polystyrene, Metallised, Radial and Axial types.
MN11. 20 asstd. Silver Mica Capacitors.
MN12. 8 Tantalum Bead Capacitors (useful values).
MN13. 20 asstd. Transistors. BC, 2N Series + Power etc.
MN14. 40 IN4148 Diodes.
MN15. 5 Light Sensitive Devices.
MN16. 20 min. wire-ended Neons.
MN17. 2 12-volt Relays. Ex nearly new equip.
MN18. 3 Encapsulated Reed Relays. 9-12v. coil, d.-pole and t.-pole.
MN19. 2 24-volt Relays. Ex nearly new equip.
MN20. 1 240-110 to 12-volt, 100ma Transformer.
MN21. 1 240-110 to 24-volt 100ma Transformer.
MN22. 8 .2" Led s with clips, 4 red, 2 yellow, 2 green.
MN23. 116 asstd. screws, nuts, washers, self-tappers etc.
MN24. 100 asstd. small springs.
MN25. 50 asstd. pop rivets.
MN26. 50 asstd. insulated crimps.
MN27. 200 items, grommets, spacers, cable markers, plastic screws, sleeving, tie wraps etc.
MN28. 20 asstd. fuses. 1¼" 20mm etc.
MN29. 75mts equipment wire, asstd. colours and sizes.
MN30. 3 x 2m length. 3 core, mains cable.
MN31. 12 asstd. trimmer capacitors, compression film. Air-spaced etc.
MN32. 15 30pF Beehive trimmers.
MN33. 20 coil formers, ceramic, plastic, reed relay etc.
MN34. 25 min. glass reed switch.
MN35. 10 asstd. switches, toggle, slide, micro etc.
MN36. 10 ex equipment panel lamps (no rubbish).
MN37. 10 asstd. audio connectors. 0in phono etc.
MN38. 1 PCB with triac control IC data inc.
MN39. 1 oscillator PCB loads of components. (no data).
MN40. 50 Polystyrene capacitors.
MN41. 10 asstd. T.T.L. I/Cs.
MN42. 10 BC107 Transistors.
MN43. 10 BC108 Transistors.
MN44. 10 Screwfix S.P.C.O. min. slide switches.

CHORDGATE LTD.

75 FARINGDON ROAD, SWINDON, WILTS
TEL: SWINDON (0793) 33877
RETAIL SHOP AT ABOVE ADDRESS

PLEASE QUOTE NO. OF PACKS WHEN ORDERING

ILP Toroidal

TRANSFORMERS IN A RANGE OF 76 TYPES



We use advanced winding technology to make our toroidal transformers. They have only half the weight and height of their laminated equivalents and are appreciably more efficient. Our toroidals cost virtually the same as the older types which they are rapidly replacing. Induced hum is reduced by a factor of ten.
Supplied with rigid mounting kit with centre bolt, steel and neoprene washers.

30VA *70mm dia. x 30mm Weight 0.45 Kg* **£4.71** *(+£1.20 p.p. +0.89 VAT)*

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
1X010	6+6	2.50
1X011	9+9	1.66
1X012	12+12	1.25
1X013	15+15	1.00
1X014	18+18	0.83
1X015	22+22	0.68
1X016	25+25	0.60
1X017	30+30	0.50

50VA *80mm dia. x 35mm Weight 0.9 Kg* **£5.19** *(+£1.30 p.p. +0.97 VAT)*

2X010	6+6	4.16
2X011	9+9	2.77
2X012	12+12	2.08
2X013	15+15	1.66
2X014	18+18	1.38
2X015	22+22	1.13
2X016	25+25	1.00
2X017	30+30	0.83
2X028	110	0.45
2X029	220	0.22
2X030	240	0.20

80VA *90mm dia. x 30mm Weight 1 Kg* **£5.76** *(+£1.50 p.p. +£1.09 VAT)*

3X010	6+6	6.64
3X011	9+9	4.44
3X012	12+12	3.33
3X013	15+15	2.66
3X014	18+18	2.22
3X015	22+22	1.81
3X016	25+25	1.60
3X017	30+30	1.33
3X028	110	0.72
3X029	220	0.36
3X030	240	0.33

120VA *90mm dia. x 40mm Weight 1.2 Kg* **£6.72** *(+£1.60 p.p. +£1.25 VAT)*

4X010	6+6	10.00
4X011	9+9	6.66
4X012	12+12	5.00
4X013	15+15	4.00
4X014	18+18	3.33
4X015	22+22	2.72
4X016	25+25	2.40
4X017	30+30	2.00
4X028	110	1.09
4X029	220	0.54
4X030	240	0.50

160VA *110mm dia. x 40mm Weight 1.8 Kg* **£8.88** *(+£1.80 p.p. +£1.60 VAT)*

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
5X012	12+12	6.66
5X013	15+15	5.33
5X014	18+18	4.44
5X015	22+22	3.63
5X016	25+25	3.20
5X017	30+30	2.66
5X018	35+35	2.28
5X028	110	1.45
5X029	220	0.72
5X030	240	0.66

225VA *110mm dia. x 45mm Weight 2.2 Kg* **£10.59** *(+£1.90 p.p. +£1.87 VAT)*

6X014	18+18	6.25
6X015	22+22	5.11
6X016	25+25	4.50
6X017	30+30	3.75
6X018	35+35	3.21
6X026	40+40	2.81
6X028	110	2.04
6X029	220	1.02
6X030	240	0.93

300VA *110mm dia. x 50mm Weight 2.6 Kg* **£12.27** *(+£2.00 p.p. +£2.14 VAT)*

7X016	25+25	6.00
7X017	30+30	5.00
7X018	35+35	4.28
7X026	40+40	3.75
7X025	45+45	3.33
7X028	110	2.72
7X029	220	1.36
7X030	240	1.25

500VA *140mm dia. x 60mm Weight 4 Kg* **£16.35** *(£2.10 p.p. +£2.77 VAT)*

8X017	30+30	8.33
8X018	35+35	7.14
8X026	40+40	6.25
8X025	45+45	5.55
8X033	50+50	5.00
8X028	110	4.54
8X029	220	2.27
8X030	240	2.08

• I.L.P. TOROIDAL TRANSFORMERS ARE GUARANTEED FOR 5 YEARS

CHOICE OF 3 PRIMARY INPUTS

I.L.P. Toroidal Transformers are available in choice of 110V, 220V, 240V, coded as follows: (Secondaries can be connected in series or parallel)

For 110V Primary insert 0 in place of "X" in type number.
For 220V Primary (Europe) insert 1 in place of "X" in type number.
For 240V Primary (U.K.) insert 2 in place of "X" in type number.

Example – 120VA 240V 15+15V. 4A = 42013.


★ CUSTOMER DESIGN ENQUIRIES INVITED.
QUANTITY PRICE LIST AVAILABLE.

FREEPOST facility. (U.K. only).

Simply address envelope to **FREEPOST** to address below. NO STAMP REQUIRED.

TO ORDER *Enclose cheque/Postal Order/Money Order payable to I.L.P. Electronics Ltd or quote your ACCESS or BARCLAYCARD account No. To pay C.O.D. add £1 extra to TOTAL value of order.*
Also available from ELECTROVALUE and MARSHALLS.

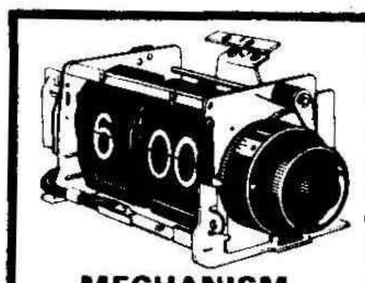ILP TRANSFORMERS
A division of I.L.P. ELECTRONICS LTD.
FREEPOST T4 GRAHAM BELL HOUSE ROPER CLOSE CANTERBURY CT2 7EP
Phone (0227) 54778 Technical (0227) 64723 Telex 965 780



MECHANISM WITH ALARM



Assemble it in an evening!
MECHANISM & CASE
Inc. assembly instructions

DIGITAL 24 HOUR CLOCK

- SILENT RUNNING
- LARGE ILLUMINATED NUMERALS

AS USED IN BRAUN DIGITAL CLOCKS

£5.00 THREE FOR £13.50

£6.99 MECHANISMS 10 FOR £39. 100 FOR £300

- AC MAINS
- SIZE 6⅜ x 2⅜ x 2¾

Your receipt is a 2-year guarantee

HALF PRICE OFFER

HENRY'S Radio

HENRY'S RADIO
404 EDGWARE ROAD,
LONDON W2 1ED
EXPORT ENQUIRIES INVITED
01-723 1008

BARCLAYCARD · Buy it with Access · DELIVERY FROM STOCK

THE ZX80 MAGIC BOOK £4.75

20 plus programs including one which allows you to make music with your ZX80, and games such as Moon Lander, Hammurabi, Othello and Hexpawn. Also sections on How it Works, Plotting, Using USR, Converting Programs Written in Other BASICs, and hardware notes including circuits for static and dynamic RAM and I/O.

THE ATOM MAGIC BOOK £5.50

Programs to run on your ATOM, including Brickout, Hexpawn, Othello and Space Battle. Also Programming Tips and Hardware Notes.


ASCII CODED KEYBOARD £35 inc. VAT & 9p

Brand new, assembled and tested. 60 keys in stepped rows. Auto repeat. S.a.e. for details.

ALL PRICES INCLUDE UK DELIVERY & VAT

TIMEDATA LTD.

57 Swallowdale, Basildon, Essex

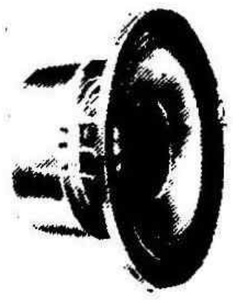

Wilmslow Audio

THE firm for speakers!

SEND 50P FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC, AND DISCOUNT PRICE LIST.

AUDAX - AUDIOMASTER - BAKER - BOWERS & WILKINS
CASTLE - CELESTION - CHARTWELL - COLES - DALESFORD
DECCA - EAGLE - ELAC - EMI - FANE - GAUSS - GOODMANS
HARBETH - ISOPHON - I.M.F. - JORDON - JORDAN WATTS
KEF - LOWTHER - McKENZIE - MISSION - MONITOR AUDIO
MOTOROLA - PEERLESS - RADFORD - RAM - ROGERS
RICHARD ALLAN - SEAS - SHACKMAN - STAG - TANNOY
VIDEOTONE - WHARFEDALE.

WILMSLOW AUDIO

35/39 CHURCH STREET
WILMSLOW, CHESHIRE SK9 1AS

Tel. 0625-529599 FOR MAIL ORDER AND EXPORT OF DRIVE UNITS, KITS, ETC.

Tel. 0625-526213 SWIFT OF WILMSLOW)
5 SWAN STREET, WILMSLOW, CHESHIRE SK9 1HF)
FOR HI-FI AND COMPLETE SPEAKERS

COMPUTER WAREHOUSE

NOW OPEN
MONDAY-SATURDAY
9.30-5.30


RAM AND EPROM NEW LOW VAT INCLUSIVE PRICES

2716 5v Rail	£9-50	4116	200NS 16KX1 DYN.	8 for	£19-95
2716 3 Rail	£8-50	2114L-3	300NS 1KX4 ST.	8 for	£22-50
2708 450NS	£4-50	2102L-3	650NS 1KX1 ST.	8 for	£ 5-50
2708 Ex Equip	£2-25	TMS4030JL	300NS 4KX1 DYN	8 for	£ 9-95

All devices full spec. and guaranteed. Bulk enquiries welcome.

In stock now test equipment, microprocessors, teletypes, transformers, power supplies, scopes, sig. gen's, motors, peripheral equipment, I.C.'s, tools, components, variacs, keyboards, transistors, microswitches, V.D.U's sub-assemblies + thousands of other stock lines. Just a mere fraction of our vast range, is displayed below: 100's of bargains for callers.


TELETYPE ASR33 I/O TERMINALS

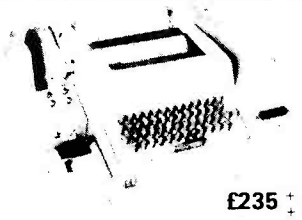

£235 + CAR + VAT

Fully fledged industry standard ASR33 data terminal. Many features including: ASCII keyboard and printer for data I/O, auto data detect circuitry, RS232 serial interface, 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order.
Options: Floor stand **£12.50 + VAT**
Sound proof enclosure **£25.00 + VAT**


ICL TERMIPRINTER 300 BAUD TERMINALS

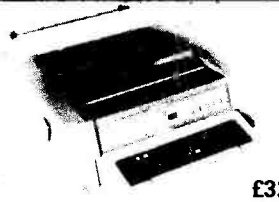

£325 + CAR + VAT

Made under licence from the world famous GE Co. The ICL Termiprinter is a small attractive unit with so many features it is impossible to list them in the space available! Brief spec. as follows; RS232 serial interface, switchable baud rates 110, 150, 300, (30 cps), upper and lower case correspondence type face, standard paper, almost silent running, form feed, electronic tab settings, suited for word processor applications plus many more features. Supplied in good condition and in working order. Limited quantity.

SCOOP PURCHASE 12" VIDEO MONITORS

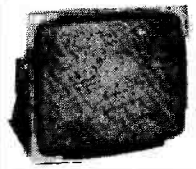

CONNECT DIRECT TO YOUR MICRO

Made by the "BALL MIRATEL" CORPORATION USA the CD12 is a self contained, mains powered chassis professional monitor. All controls are inbuilt on a single PCB with exception of the brightness control which can be brought out for external use. Many features such as composite video, quoted bandwidth of 19 Mhz, superb linearity and definition make this a must for any MICRO/CCTV application.
Brand new and boxed only + carriage **£7.50 + VAT.** **£97.50 + VAT**
Input harness, brightness pot and connector **£2.50 + VAT.** Dimensions 9"H × 11"D × 11½"W
HURRY WHILE STOCKS LAST

EX STOCK SOFTY


EPROM BLOWER

Software development system invaluable tool for designers, hobbyists, etc. Enables open heart surgery on 2716, 2708 etc. Blows, copies, reads EPROMS or emulates EPROM/ROM/RAM in situ whilst displaying contents on domestic TV receiver. Many other features. **£115 + carr. + VAT.** Optional 2716, 2716 Function Card **£40 + VAT.** PSU **£20 + £1.50 carr. + VAT.**
Write or phone for more details.

3K × 8 STATIC RAM CARDS

BRAND NEW PCB organised as a 3K × 8 page memory with 24 socketed 2102-L 650ns Rams, 4 Eprom Sockets and 16 TTL Chips for decoding. All IC's guaranteed.
Complete with circuit only
£24.50 + £1.75 P.P.
Dimensions 264 × 195mm.
0.1" connector.

EQUIPMENT CASES

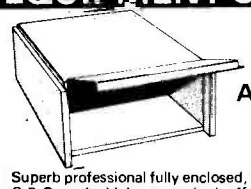

GIVE YOUR M.P.U. A HOME ONLY
£9.95 + 1.85 pp

Superb professional fully enclosed, made for the G.P.O. to the highest standard, offered at a fraction of their original cost they feature aluminium sides, hinged removable front panel, which can be secured by 2 screws to prevent prying fingers. All are finished in two tone G.P.O. grey and although believed brand.new may have minor scuff marks/scratches due to bad storage.
Dimensions 16"D × 6½"H × 14¾"W

NATIONAL MA1012 LED CLOCK MODULE



★ 12 HOUR
★ ALARM
★ 50/60 HZ

The same module as used in most ALARM/CLOCK radios today, the only difference is our price! All electronics are mounted on a PCB measuring only 3" × 1½" and by addition of a few switches and 5/16 volts AC you have a multi function alarm clock at a fraction of cost. Other features include snooze timer, am pm, alarm set, power fail indicator, flashing seconds cursor, modulated alarm output etc. Supplied brand new with full data only
Suitable transformer £1.75. **£5.25**

SEMICONDUCTOR 'GRAB BAGS'

Amazing value mixed semiconductors, include transistors, digital, linear I.C 's, triacs, diodes, bridge recs. etc. etc. All devices guaranteed brand new, full spec. with manufacturers markings, fully guaranteed.
50 + BAG **£2.95** 100 + BAGS **£5.15**

MUFFIN FANS

Keep your equipment Cool and Reliable with our tested ex-equipment "Muffin Fans" almost silent running and easily mounted. Available in two voltages. **110 V.A.C. £5.05 + pp 90p OR 240v A.C. £6.15 + pp 90p DIMENSIONS** 4¼" x 4¼" x 1½".

ELECTRONIC COMPONENTS & EQUIPMENT 66% DISCOUNT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistors, Relays, Cap's., P.C.B.'s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads., we are packing all these items into the "**BARGAIN PARCEL OF A LIFETIME**" Thousands of components at giveaway prices! Guaranteed to be worth at least *3 times* what you pay plus we always include something from our ads for unbeatable value!! Sold by weight

2.5kds £ 4.75 + pp £1.25 **5kds £ 6.75 + pp £1.80**
10kds £11.75 + pp £2.25 **20kds £19.99 + pp £4.75**

OP PRESS – STOP PRESS – STOP PRESS – ST

STEP INTO THE 80's EX STOCK

WITH TOMORROW'S WORLD TECHNOLOGY TODAY
The "TANTEL" Post Office approved

PRESTEL – VIEWDATA ADAPTOR

At last this amazing piece of micro technology is available at a price you can afford. Just connect to the aerial socket of any colour or black and white domestic TV receiver and to your Post Office installed jack socket and you are into the exciting world of **PRESTEL**. Via simple push button use you are able to view a staggering 170,000 pages of up to the minute information on many services and utilities, order goods from companies, even play games!! All this and more without ever leaving your armchair!


ONLY £170 + £1.75 carr + VAT **Send £197.50p**

Note: When ordering please give the address and telephone number where the Tantel adaptor is to be used, we will arrange all details with the Post Office for installation of the jack socket (normally within 7 days).

WE'VE BOUGHT ANOTHER SHIPMENT! SAVE OVER £1300!!

DZM 180 CPS HIGH SPEED
MATRIX PRINTERS

NOW ONLY **£499** + Carr + VAT

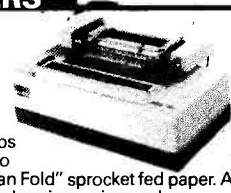

This must be one of our greatest bulk deals, this fabulous printer is listed at over £1800 and judging by the construction we are not surprised. Made under license from the LOGABAX Co. the DMZ180 is an exceptionally sturdy high speed 180 cps matrix printer, capable of printing up to 132 characters per line on standard "Fan Fold" sprocket fed paper. A precision 7 × 7 matrix head using ruby bearings, gives a clear concise type font. Many other features include internal buffer for high throughput, standard ink ribbon, software controllable form and tab functions, standard "CENTRONICS" ASCII parallel interface etc. etc.
Optional extras **Floor Stand £30.00 + VAT, Paper Stand £18.00 + VAT**

DIABLO S30 2.5MB HARD DISK DRIVES


Limited quantity of these ultra high speed access hard disk drives type Diablo 30. They accept interchangeable 200 TP1 disk packs and require only a + and −15v DC supply. Fully DEC RK05 compatible, supplied second hand and in excellent condition.
Only £425 + carr + VAT
Dimensions 7"H × 17½"W × 22¾"D

"THE MULTIVOLT PSU"

The PSU to end *all* your MPU/LAB requirements, made by "Weir" Electronics at over £200.00. The supply features full regulation, current limit, and overvoltage protection on all 7 outputs, just look at the spec.
+5v @ 12 amps, +5v @ 4.5 amps, +5v @ 4 amps, +30v @ 2 amps, +12v @ 2.5 amps, −12v @ 2.5 amps and −9v @ 1 amp.
A superb unit supplied in two grades, complete with data.

Brand New, Fully Tested	**£59.99**
Used and Untested	**£39.99**
Carriage and Insurance	**£7.50**

RCA FULLY CASED ASCII CODED KEYBOARDS

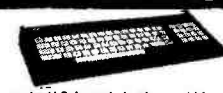

Straight from the U.S.A. made by the world famous R.C.A. Co., the VP600 Series of cased freestanding keyboards meet all requirements of the most exacting user, right down to the price! Utilising the latest in switch technology. Guaranteed in excess of 5 million operations. The keyboard has a host of other features including full **ASCII** 128 character set, user definable keys, upper/lower case, rollover protection, single 5V rail, keyboard impervious to liquids and dust, TTL or CMOS outputs, even an on-board tone generator for keypress feedback, and a 1 year full R.C.A. backed guarantee.

VP601 7 bit fully coded output with delayed strobe, etc.	**£43.95**
VP611 Same as VP601 with numeric pad.	**£54.95**
VP606 Serial, RS232, 20MA and TTL output, with 6 selectable Baud Rates.	**£60.95**
VP616 Same as VP606, with numeric pad,	**£72.50**
Post, Packing and Insurance.	**£1.95**

ORDER NOW OR SEND FOR DETAILS.

5v D.C. POWER SUPPLIES

Following the recent "SELL OUT" demand for our 5v 3 amp P.S.U. we have managed to secure a large quantity of ex-computer systems P.S.U.'s with the following spec.: 240 or 110v A.C. input. Outputs of 5v @ 3·4 amps, 7.2v @ 3 amps and 6.5v @ 1 amp. The 5v and 7.2v outputs are fully regulated and adjustable with variable current limiting on the 5v supply. Unit is self contained on a P.C.B. measuring only 12" x 5" x 3". The 7.2v output is ideal for feeding "on board" regulators or a further 3 amp LM323K regulator to give an effective 5v @ 7 amp supply.
Supplied complete with circuit at only **£10.95 + £1.75pp.** Believed working but untested, unguaranteed.

ELECTRONICS

Dept. E.T.I. 64-66 Melfort Rd., Thornton Heath, Croydon, Surrey. Tel: 01-689 7702 or 01-689 6800

MAIL ORDER INFORMATION

Unless otherwise stated all prices inclusive of V.A.T. Cash with order. Minimum order value £2.00. Prices and Postage quoted for UK only. Where post and packing not indicated please add 50p per order. Bona Fida account orders minimum £10.00. Export and trade enquiries welcome. Orders despatched same day where possible. Access and Barclaycard Visa welcome.

DESIGNER'S NOTEBOOK

Certain elementary safety precautions must be taken when handling CMOS ICs or designing CMOS circuits. Ray Marston explains all in this month's 'Notebook'.

Early CMOS ICs earned a reputation for being easily damaged by static electricity, either when being handled or when being soldered into circuit boards, etc. Subsequently, manufacturers tried to overcome this 'fragility' problem by providing the ICs with extensive built-in input and output protection on each gate in each package. These protection networks do a fairly satisfactory job, but provide the design engineer with a few extra problems when designing CMOS circuits. This month's Notebook takes an in-depth look at the subject.

CMOS Protection Networks

CMOS ICs are, by definition, Metal-Oxide Semiconductor devices, in which the input signal is applied to the near-infinite impedance (about 10^{12} ohms) of the metal-oxide gate. Typically, the gate oxide has a breakdown voltage of about 80 V: if a gate oxide break-down does occur, the resultant damage to the device is catastrophic and irreversible. To protect the CMOS against excessive input voltages (particularly arising from static energy), all modern CMOS ICs are provided with extensive built-in protection on all inputs and outputs.

Figure 1 shows the standard protection network that is used on the vast majority of B-series CMOS devices. Here, all diodes marked as 'D1' are used to prevent the input or output from swinging more than 600 mV below the V_{SS} (0 V) rail, and all diodes marked as 'D2' are used to prevent the input or output from swinging more than 600 mV above the V_{DD} (supply positive) rail. D3 is intended to prevent the V_{DD} terminal from swinging negative to the V_{SS} pin (electrostatically) when the device is being handled.

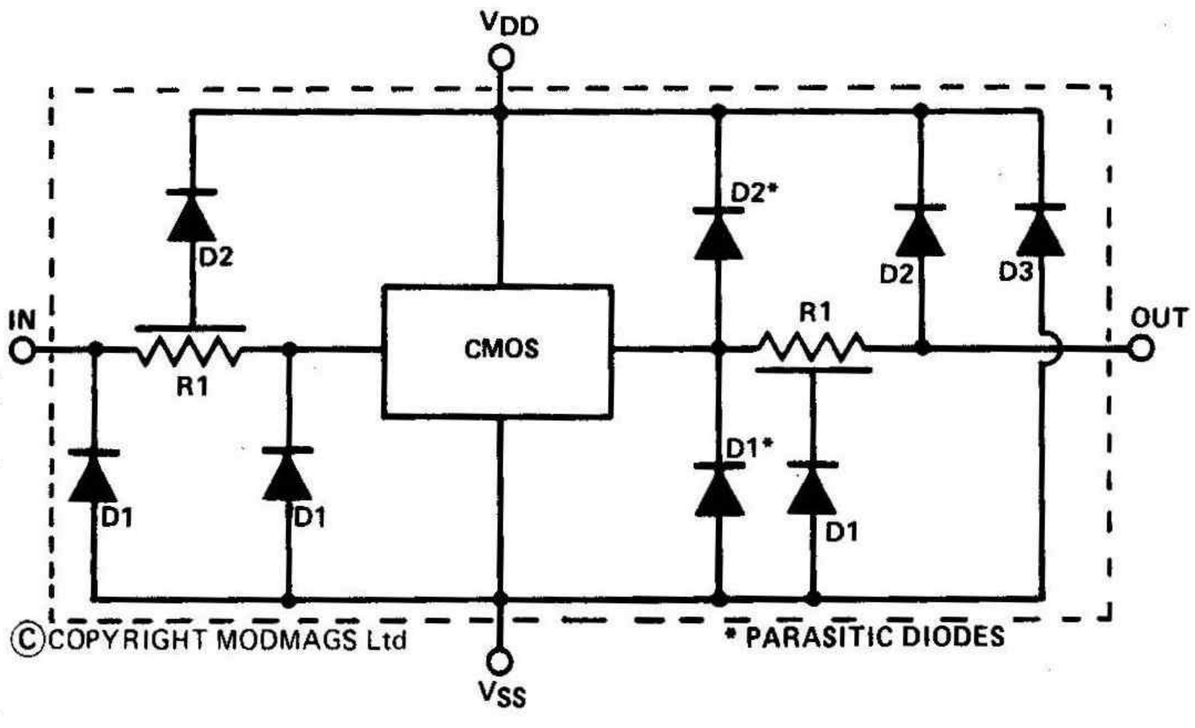


Fig. 1 These are the standard electrostatic-discharge protection networks used on most B-series CMOS ICs. The two diodes associated with the resistors are distributed across the entire resistance, as shown.

There are a couple of minor exceptions to the standard version of the protection network. One of these is the type used on the 4049B and 4050B series of hex buffer/converters which, as shown in Fig. 2, have their inputs free to swing well above the V_{DD} rail. These particular ICs are specifically intended for use in logic-level conversion applications, in which (for example) the input may come from a 12 V CMOS network but the output and the IC supply rail are matched to a 5 V TTL network.



Fig. 2 This protection network is used on the 4049B and 4050B hex buffers. Note that the input is free to swing above the positive supply (V_{DD}) rail.

Another exception is the 4066B type of transmission gate or bilateral switch, and its equivalents. These devices comprise a bilateral electronic switch and a switch-control network. In these circuits, all switch-control networks have the type of input protection shown in Fig. 1, but the switches themselves have the simple protection network shown in Fig. 3.

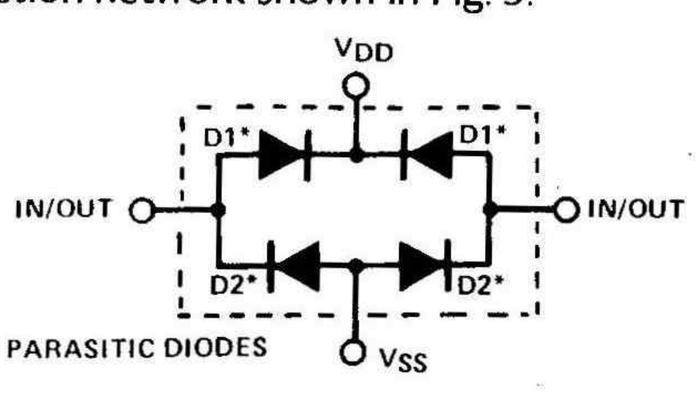


Fig. 3 The 4066B quad bilateral switch has standard B-series protection on its gate control input terminals, but has this simplified form of protection on its 'switch' elements.

Note in Figs. 1-3 that all diodes marked with asterisks are 'parasitic' devices, which just happen to occur fortuitously as an inherent part of the CMOS manufacturing process, while all other diodes are specifically designed into the circuits. Also note that the networks are intended only to give protection

against 'normal' electrostatic discharge voltages. When the networks are subjected to ordinary DC signals, the diodes are liable to burn out if their forward currents exceed 10 mA or so, thereby causing possible catastrophic damage to the IC substrate.

Major CMOS manufacturers such as RCA reckon that an electrostatically charged human body can be approximated by the circuit of Fig. 4, in which the 'body' has an effective capacitance of 100pF and a source resistance of 560R. The manufacturers have carried out extensive tests with this model by charging the 'body' to various voltages and then discharging it (via the 560R series resistor) into different terminal combinations (input, output, V_{SS}, V_{DD}) of CMOS devices to establish worst-case capability figures for the three types of electrostatic-discharge protection networks. It should be noted in these tests that the 560R series resistor acts as a current-limiting voltage dropper, so the voltage actually reaching the CMOS device is far lower than the initial electrostatic voltage.

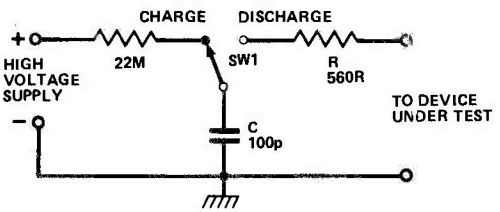


Fig. 4 Manufacturers use this equivalent-body discharge network when evaluating the capabilities of their CMOS protection networks.

The results of the manufacturer's protection capability tests are shown in Fig. 5. As you can see, the standard protection network can withstand a 4 kV electrostatic discharge. A quick calculation shows, however, that this represents a peak protection-diode current of several amps, yet we've already seen that these diodes can withstand DC currents of only 10 mA or so. Puzzled?

PROTECTION NETWORK	WORST – CASE CAPABILITY
STANDARD B–SERIES 4049B AND 4050B 4066B BILATERAL SWITCH	4 kV 1 kV TO 2 kV < 800 V

©COPYRIGHT MODMAGS Ltd

Fig. 5 These are the worst-case capabilities of the three different CMOS protection networks, when tested with the network of Fig. 4.

Up The Junction

Just about the only way of destroying a diode is to literally vaporise its junction, and this can only be done by applying an adequate amount of power for sufficient time for the melting process to take place. Since a junction must inevitably be formed on a substrate, which has a finite mass, all junctions inevitably have a certain amount of thermal inertia and are, in fact, destroyed by energy overloads (power-time product), rather than by simple power overloads.

Consequently, it is quite normal to find that a diode rated at 1 A (for example) can, in fact, withstand brief current surges up to several hundred amps. Similarly, CMOS protection diodes, which have very low DC current ratings (10 mA), can withstand very high levels of surge current (several amps), provided that the surge current duration is very brief. Figure 6 shows the typical surge current capabilities of these protection diodes. Remembering that the 100p — 560R 'human body' equivalent circuit has a time constant of a mere 56 nS, it no longer comes as a surprise to note that these diodes can withstand several amps of peak current from a 4 kV discharge!


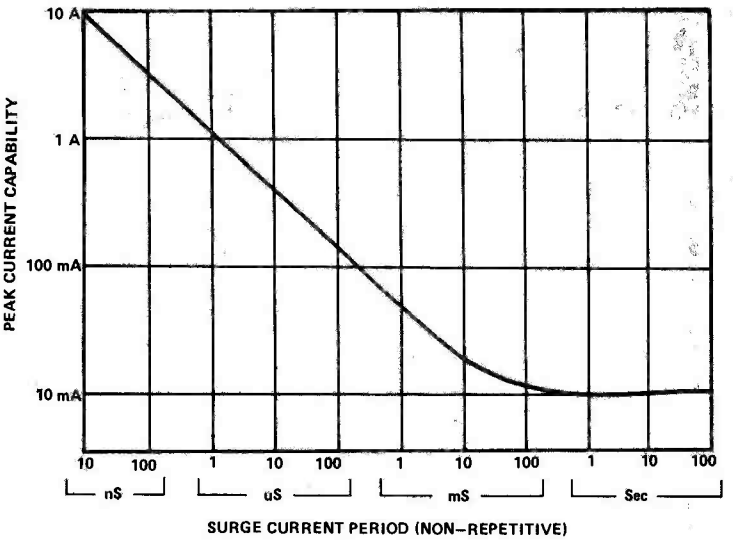


Fig. 6 Typical surge-current capabilities of CMOS protection diodes.

CMOS Circuit Design

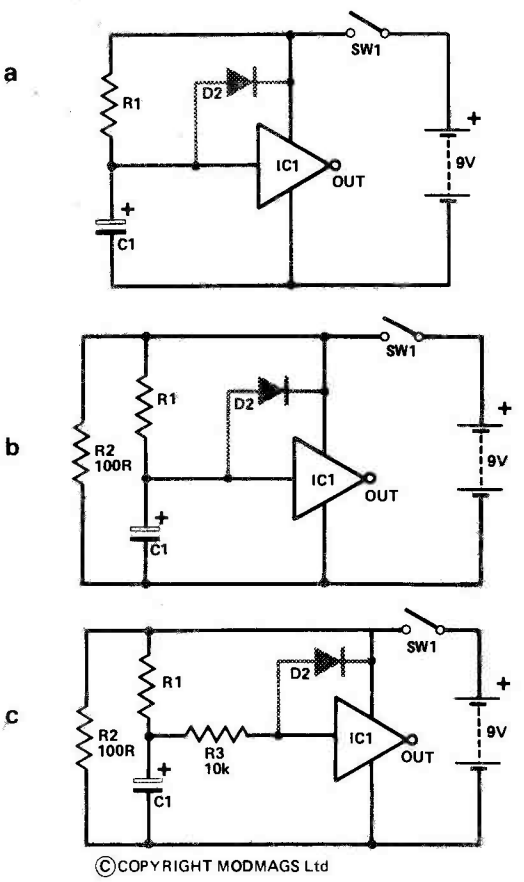By now you will have gathered that you can effectively destroy a CMOS device by simply blowing one or more of its 'protection' diodes with a DC current as low as 10 mA. Consequently, when designing CMOS circuits, precautions must be taken to ensure that excessive diode current cannot flow in the CMOS chips.



©COPYRIGHT MODMAGS Ltd

Fig. 7 Circuits (a) and (c) are safe, but circuit (b) will almost certainly cause a front-end 'blow'. See text for explanation.

CMOS ICs can be 'blown' by excessive signals applied to either the input or the output terminals. If several CMOS stages are cascaded, empirical experience shows that a front-end blow will usually destroy only a single device (because low energy levels are normally involved), but a rear-end (output) 'blow' will often have a ripple effect (because high energy levels are involved) and cause the destruction of all ICs in the chain.

The most common cause of front-end 'blow', and its cure, are illustrated in Fig. 7. Here, a capacitor is connected directly between the IC gate and the 0 V line: when SW1 is closed, the capacitor charges up via R1 and eventually attains the full positive supply potential. When SW1 is opened (to switch the circuit off), C1 tries to discharge via D2, the 'upper' input protection diode of the gate.

In the Fig. 7a circuit, the only discharge path for C1 is via D2 and the IC's supply terminals; consequently the discharge currents will be quite low and the IC will probably suffer no damage. In Fig. 7b, on the other hand, a 100R resistor is connected across the supply terminals, so C1 will try to discharge to ground via D2 and R2, and the resulting 90 mA peak current will almost certainly result in the destruction of the chip. In practice, R2 may well take the form of various resistors and semiconductor devices distributed throughout the total circuit.

Figure 7c shows the cure for the Fig. 7b design problem, a 10k resistor wired in series with the gate to limit the C1 discharge currents to a safe value. Whenever you design CMOS circuits and have to connect a capacitor between a gate and the 0 V rail, always make sure that the capacitor discharge current is limited to a safe value, either by a series gate resistor or by some other factor.

Back-end Blowing

The most common cause of back-end blowing is unexpected back-EMFs (from inductive loads) reaching the CMOS output by breaking through from power-driving circuitry.

Inductive loads, such as relays, can generate surprisingly large back EMFs as their fields collapse at switch-off, as can be proved by connecting a relay in the 'buzzer' mode shown in Fig. 9. Typically, a 12 V relay will generate a back-EMF of about 300 V! If you ever use CMOS to switch a relay or other highly inductive load using a transistor driver, always protect the transistor with a pair of 1N4001 diodes connected as shown in Fig. 10a. If you want to be really safe, you can use another pair of similarly-connected diodes to directly protect the output of the CMOS stage, as shown in Fig. 10b.

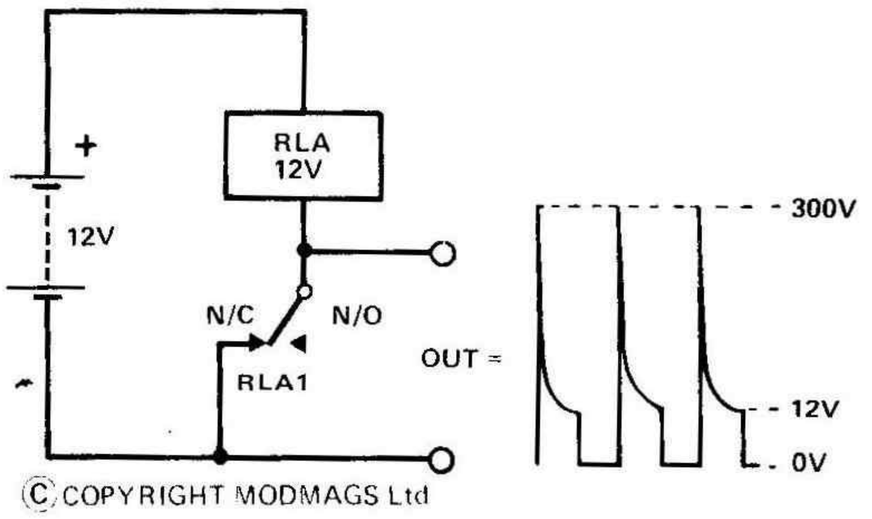


Fig. 9 This 'buzzer' circuit can be used to check the magnitude of the back-EMF from a relay. 300 V is typical!

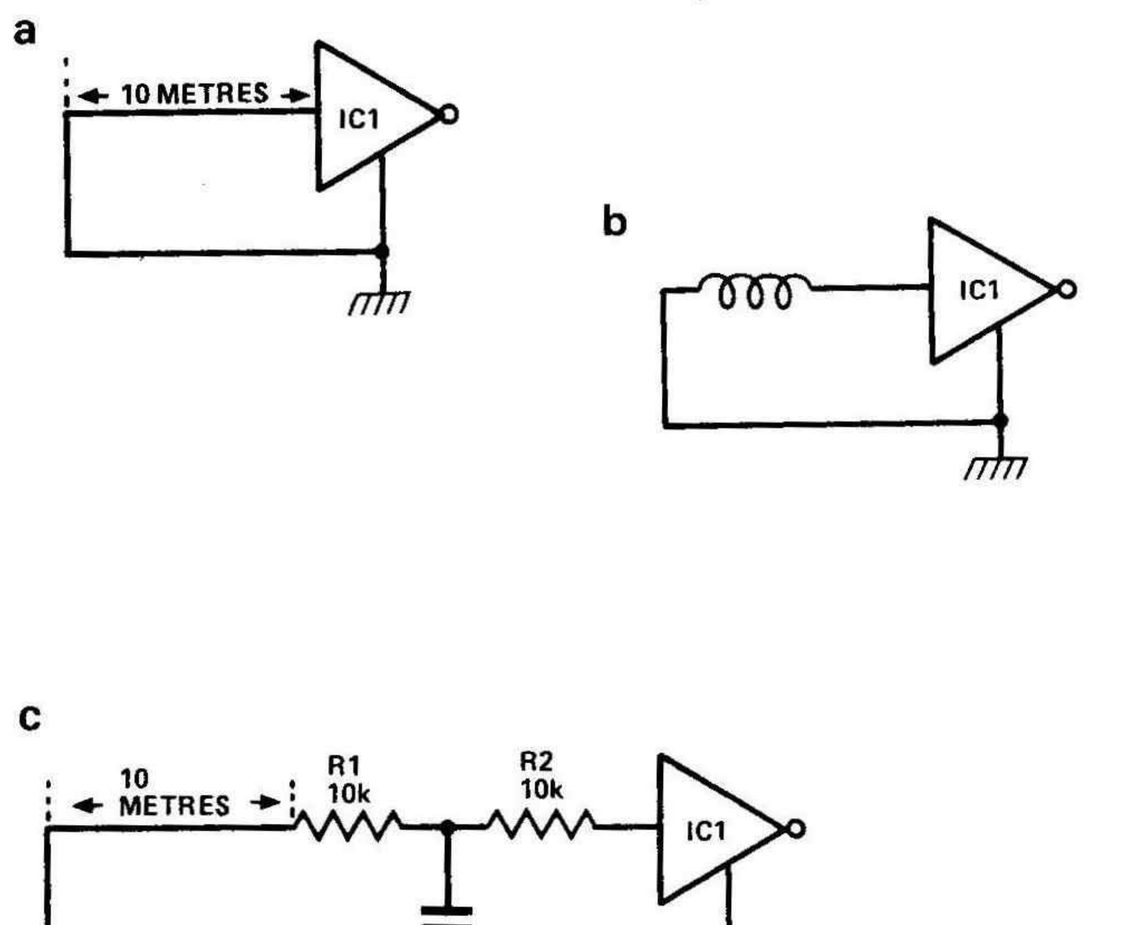


Fig. 8 Long input cables, as in (a), can be equivalent to an inductor (b), and present another front-end blowing hazard. The cure is simple (c).

Figure 8 illustrates another possible cause of front-end 'blowing', and its cure. In Fig. 8a, it seems that the IC's input is safely grounded by the 10 m of input cable (in practice, this cable may go to a low impedance sensor, etc), but in actual fact (Fig. 8b) this cable will inevitably be inductive and can easily pick up unwanted radiation and possibly feed destructive signals to the IC input. Figure 8c shows that the circuit can be rendered safe with a simple filter (R1-C1) and a series gate resistor (R2).

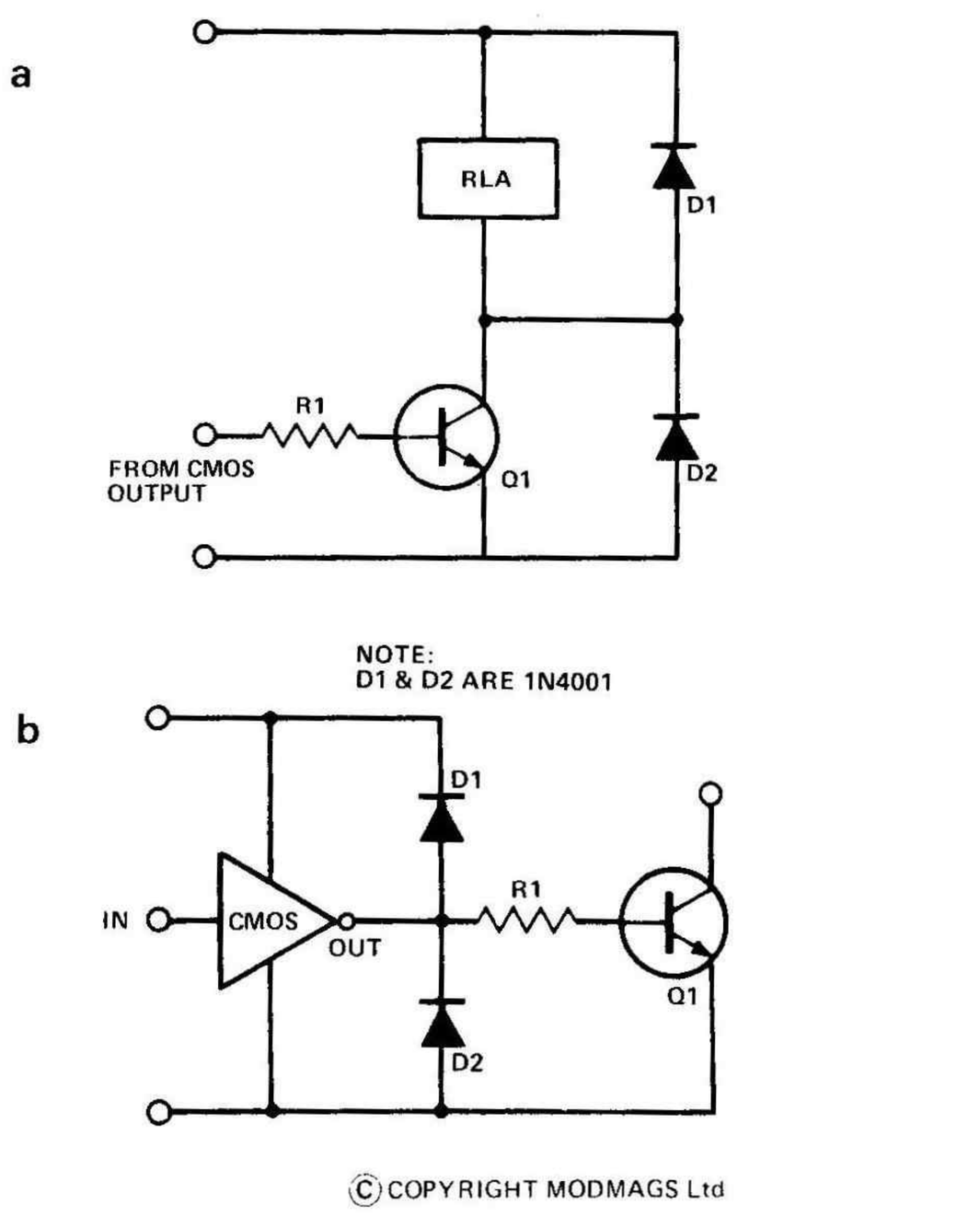


Fig. 10 (a) A transistor relay-driver can be protected with a pair of diodes. (b) The output of a CMOS stage can be given added protection with a similar arrangement.

ETI

DORAM

DORAM ELECTRONICS LTD

Fitzroy House, Market Place,
Swaffham, Norfolk, PE37 7QH.

TEL: (0760) 21627 TELEX: 817912
VAT Reg: 324 5604 75

PROJECT PACKS

Projects for beginners

LCD Converter (80117) Simple to construct display for FM and AM Bands **£41.20**
Pools predictor (79053) An analogue computer that may win you a fortune **£8.15**
Talk Funny (80052) A ring modulator circuit that produces very strange results when fed with a human voice **£9.60**
Pest Pester (80130) An electronic insect repellant **£2.35**
Steam train sound effects (80019) Simulates the sound of steam and whistle **£6.50**
Electronic Nuisance (80016) Makes an annoying noise, but only in the dark! **£3.85**
Cackling Eggtimer (9985) An eggtimer with a difference, it clucks like a hen **£7.20**

New projects

200w Disco Power Amplifier (81082) **£20.85**
Swinging Poster (81073) Animated poster **£15.20**
Minimixer (81068) High quality 5 channel stereo mixer **£37.50**
Process Timer (81101) Photographic darkroom timer **£18.20**
High Com (81117-1) Telefunken noise reduction system **£49.55**

Audio projects

Top-preamp (80031) Mini, all IC preamplifier for use with most power amplifiers **£34.40**
Topamp (80031) Hybrid audio power amplifier uses Philips modules for high fidelity performance. Two power levels:
OM931 (output 30 watt) **£18.50**
OM961 (output 60 watt) **£33.40**
Parametric Equalizer (9897) A modular system of construction to suit your equalisation requirements. Filter section (9897-1) **£6.45**
Tone section (9897-2) **£5.20**
Elektornado (9897) A single board design that can be used as either a single 100 Watt amplifier or two 50 Watt amplifiers **£19.50**
UAA180 LED meter (9817) A two channel voltage display unit **£13.00**
Peak Programme Meter (9860) To be used with UAA180 LED meter to give PPM display **£3.70**
Audio Analyser (9932) An analyser that can pinpoint the deficiencies in an audio chain **£14.80**
Stereo dynamic Preamp (80532) A low noise high quality disc preamplifier **£5.20**
STAMP (80543) Super tiny amplifier up to 1 Watt output **£3.75**
Melody Maker (80502) An electronic musical box that can play up to 27 tunes **£23.50**

Car projects

Car Battery Charger (79517) Reliable and safe charger for all types of lead-acid batteries **£21.70**
Transistor Ignition (80082) The most significant advantages of other systems combined in one **£20.45**
Dipstick Probe (80102) Direct warning of high oil temperature. State long or short dipstick required **£11.25**
Intelligent Wiper Delay (80086) Can be set to produce delayed wipes at any predetermined interval **£15.85**
Battery Protection (80109) Automatically switches off the headlamps of a parked car **£5.15**
Battery Voltage Indicator (80101) LEDs indicate the condition of your battery **£6.85**
Active Car Aeriel (80081) Improves the sensitivity of AM and FM radio reception in your car **£13.85**

Music projects

Chorosynth (80060) A cheap mini synthesizer. Send for details **£57.90**
Elektor Vocoder (80060) The first Vocoder designed to be built in kit form. 10 Channel modular construction **£162.50**
Analogue Reverberation Unit (9973) Uses a SAD 1024 which can produce a delay up to 100mS **£27.70**
Guitar Preamp (77020) With three tone controls **£6.50**

Projects for the home

Touch Dimmer (78065) Room lighting controlled by a single touch **£6.80**
Programmable Slide Fader (81002) Mixes audio signals on tape with operation of two slide projectors **£46.50**
Fridge Alarm (81024) Audible warning if fridge door is left open **£5.55**
Loudspeaking telephone amplifier (9987) Amplifies without direct connection **£11.50**
Proximity Detector (9974) Detects by electric field change movement in a room **£9.80**

Our Project Packs include the electronic components, the PCB, sockets and solder together with assembly instructions. Cases, knobs etc can be supplied as extra items if required. This is only part of our wide range of projects. See our catalogue for details of other projects that we can supply. You can also ring our number between 12.30 and 1.30 p.m. any weekday for a recorded announcement of any new items we have available.

HOW TO ORDER
Send a cheque or postal order to DORAM ELECTRONICS LTD or write or ring with your Access account number. All our prices include VAT. Overseas customers please deduct 15%. Please add 40p to your order for postage and packing. An answering service is available to take your orders outside our normal office hours. Mail Order service only.

a de boer company

Buy it with Access


NAME _____

ADDRESS _____

_____

3 CHANNEL SOUND/LIGHT CHASER


LB31000SLC **£32.70**

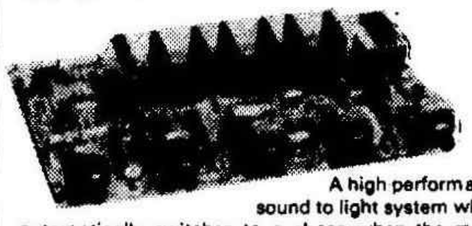

A high performance sound to light system which automatically switches to a chase when the music ceases. Super sensitive with an anti interference circuit, the unit will operate from practically any amp and control up to 1,000W/channel, 5Hz to 70K. Controls: bass/mid/treble/master sensitivity/chase speed.

3 CHANNEL SOUND/LIGHT

LB31000SL

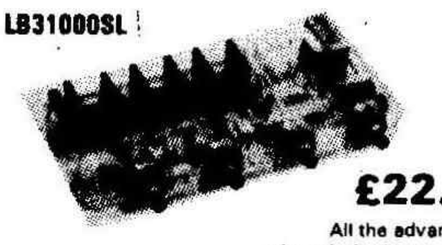


£22.70

All the advantages of the SLC without chase.
Controls: bass/mid/treble/master sensitivity.

2/4/8 CHANNEL CHASER

LB81000LC

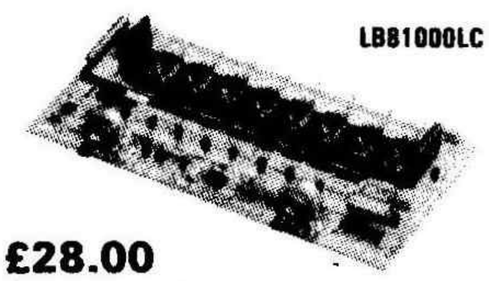


£28.00

An all logic chaser system for use with up to 8 channels at 1,000 watts each. Facilities include footswitch trigger and module cascading (16, 24, 32 channel, etc.), chase speed and re-cycle delay.

4 CHANNEL SEQUENCER

LB41000LS

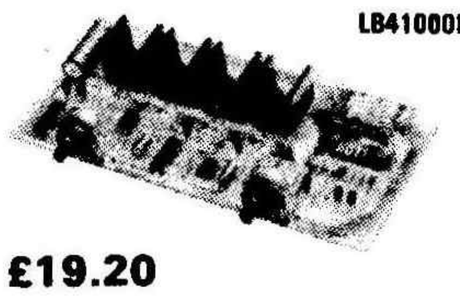


£19.20

A 4 channel sequence generator for banks of lamps up to 1,000W per channel. Two speed controls, cross effect to provide settings between seconds and rapid burst.

1 AND 3 CHANNEL DIMMERS

LB31000LD

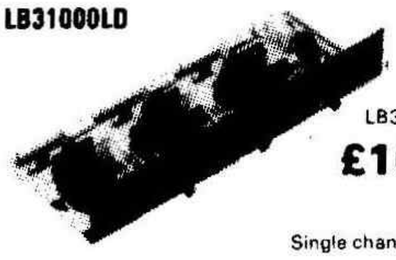

LB31000LD **£16.20**

Single channel version LB11000LD **£7.20**


Power dimmer units for theatre/stage applications up to 1,000W per channel, with on board suppressing. The unit is also available without rotary pots for use with sliders —

LB31000LD (no pots) **£15.00** Sliders **75p** each.

ROPE LIGHTS/DRIVER

LB41000LC-S

£24.20

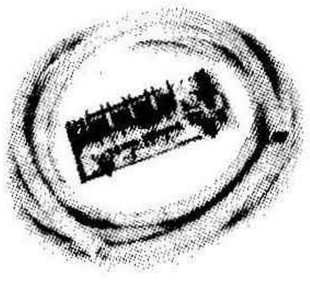

24 feet ropes
Red/Yellow
Blue/Green


ROPE LIGHTS

£45.40

A four channel chaser up to 1,000W per channel, with a sound trigger facility. The music input signal modulates the speed of the chase giving an excellent sound/light effect. The unit will control up to 10 ropes with chase speed and trigger level control.

STEREO DISCO MIXER/PREAMP

LBPA3
M – Magnetic
C – Ceramic

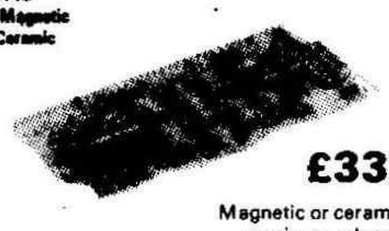

£33.70

Magnetic or ceramic deck versions – please state

All the requirements of a stereo disco preamp on one board, left and right deck mixers/tone controls/mic. mixer/tones/mic. auto fade over decks/and P.F.L. The unit can be used with either LB100/150/250

Full set of pots — **£8.63**

LBPA2 **£17.20**

A four channel mixer and tone stage for mics, guitars, etc. Can be used with any LB amps. Set of pots **£2.74.**

LBPA1 **£19.50**

A stereo hi-fi preamp and tone stage for mag. p.u./tape/tuner, etc. Set of pots **£3.27.**

3-WAY ACTIVE CROSSOVER

LBACO1

£17.90



LBPSU1

£7.20



Bass/mid/treble active crossover with stage booster! Available with crossover points of 200 or 300Hz, and 2K or 3KHz (please specify) LBPSU1 supply for LBACO1 (1 or 2).

POWER AMPLIFIERS

Tough dealing power amps for use in sound systems. Open/short circuit protection and fused. Heavy gauge heatsinks and rugged o/p devices (all operate down to 4 ohms).

25W R.M.S.	100W R.M.S.	150W R.M.S.	250W R.M.S.
20Hz to 60K	5Hz to 25K	5Hz to 25K	5Hz to 25K
0.07% THD	0.1% THD	0.1% THD	0.1% THD
96DB S/N	110DB S/N	110DB S/N	110DB S/N
LB25	LB100	LB150	LB250
£11.20	**£19.70**	**£29.20**	**£43.50**

Note all models are available with either 500mV or 775mV sensitivity. Please state when ordering.



LBRLD1

£6.20

A de-thump unit for use with any LB power amps.

POWER AMP POWER SUPPLIES

LB25PS	LB100PS	LB150PS	LB250PS
£11.20	**£16.20**	**£19.00**	**£26.50**
P/P £1.20	P/P £1.40	P/P £1.40	P/P £1.70

FOR GUITAR, P.A. AND DISCO

PIEZO HORNS

£5.75
P/P 50p



CELESTION LOUDSPEAKERS

(All standard cone 8 ohms)

G12-65 (12 inch 65W)		G12-100 (12 inch 100W)		G10-50 (10 inch 50W)	
£20.70	P/P £1.70	**£26.45**	P/P £1.70	**£14.70**	P/P £1.70

NEW – MINI MODULES – NEW

Ingeniously designed mini pre-amplifier 'building blocks' for use in music and P.A. applications. You choose the type and number of units you require for your particular system and mount each module via its control direct onto your panel.

LBMM1 Pre-amp for mics, guitars etc.
LBMM2 Mixer for up to 6 LBMM1/2/3/4/5
LBMM3 Bass/boost/cut for either LBMM1/2/3/4/5
LBMM4 Mid-boost/cut for either LBMM1/2/3/4/5
LBMM5 Treble boost/cut for either LBMM1/2/3/4/5
LBPSU1 ± 15V supply for up to 12 modules
LBPSU ± 15V regulated for up to 50 modules
MM1 £4.50; MM2 £5.20; MM3 £5.70; MM4 £5.70; MM5 £5.70; PSU1 £7.20; RPSU £14.50.
Mini Module Discount. Any types between 10 and 24 (quantity)—20%. 25+—30%.

L & B
ELECTRONIC MODULES
PROFESSIONAL ENGINEERING BY PROFESSIONALS
45 Wortley Road, West Croydon, Surrey CR0 3EB. Tel. 01-689 4138


Each module is manufactured from the highest quality components, fully tested, supplied with a connection and circuit diagram and guaranteed for twelve months.

All prices shown are VAT inclusive. Please include 50p post/packing except where individually stated. To mail order, send cheque/P.O./registered cash or Access number. C.O.D. service £1 extra. For the new Autumn catalogue send 50p (Full spec. shown).

Please note: This company has no connection with LB Electronics of Hillingdon.

NEW

TRS 80 MODEL III

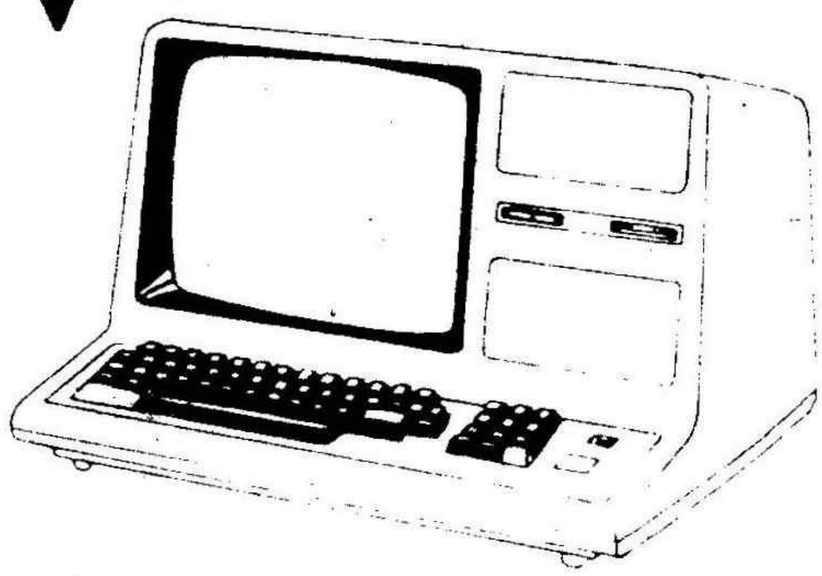

The Model III has arrived in the U.K.
★ NEW FEATURES AVAILABLE ★

★ Upper and Lower Case characters (standard) ★ Real Time Clock ★ 500 or 1500 Band Cassette ★ Parallel Printer Interface (standard) ★ Auto Repeat keys ★ Flashing Cursor ★ New Characters, Greek, Japanese Kana ★ Numeric Keypad ★ 16, 32 or 48K ★ Room for two D.D. Disc Drives & Interface ★ 12" VDU ★ All in stylish cabinet.

16K **£649** INCLUSIVE

S.a.e. Enquiries. Delivery 4-6 weeks

N.I.C
Unit 5 61 Broad Lane, London N15
Daytime: 808 0377; evenings: 889 9736

QUESTION?

1. Is your hobby home computing or electronics?
2. Do you understand the application of IC's, Transistors, Diodes, etc?
3. Have you used or applied analogue or digital techniques?
4. Are you applying TTL Logic to your home computer?
5. Are you programming your home computer using simple software techniques?

If the answer is YES to any of these questions then why not consider turning your hobby into a career — applying your knowledge to servicing electronic equipment ranging from basic terminals and data processing machines through to advanced micro-processor systems.


We will train you through to advanced technology at the company training school, fitting the individual in at their own level.

We have vacancies over the whole of the U.K. especially in the London area, with the successful applicants working from home, usually in a radius of no more than 60-70 miles.

We supply all tools and test equipment, plus a company car which is available for private use.

If you are interested, then why not contact **Mr. C. Marklew on 0249 813771** to discuss your own career opportunities in confidence, or write to:

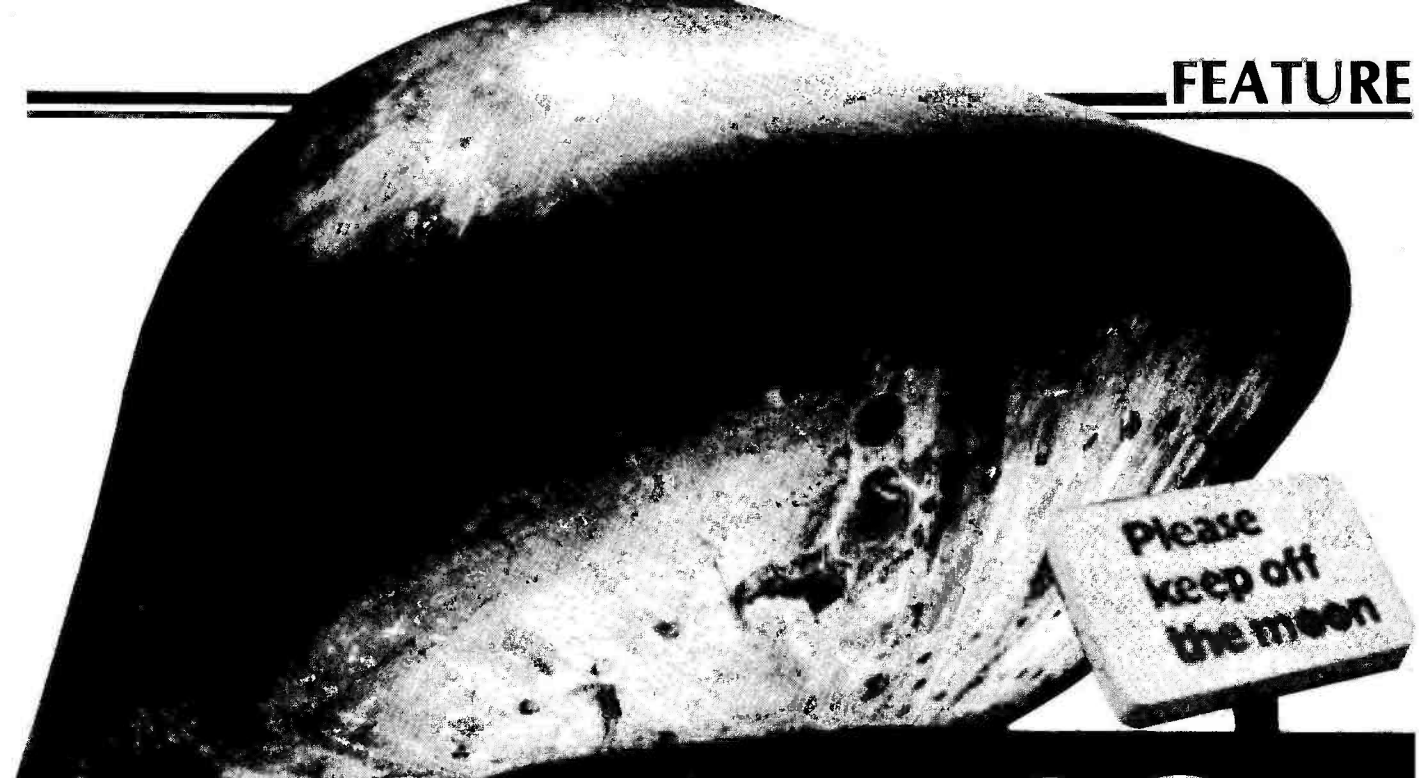KODE SERVICES LIMITED
Station Road, Calne, Wiltshire



ASTROLOGUE

Ian Graham looks at NASA's aeronautical research and answers a common Astrologue inquiry.

Say NASA and most people think of rockets and moon-shots. One side of NASA's activities that doesn't hit the headlines is its aeronautical research. The work falls into four categories:

Proof of concept — flying hardware to prove a theory eg the X-series of research aircraft.

Extension of the art — building upon the contemporary state of the art.

Future needs — meeting broad and far-reaching research goals.

Problem solving — trouble-shooting design problems.

The research reaches into almost every aspect of aviation — fluid physics, propulsion, materials, structures, electronics and human factors, all of which came together to support the development of safer, environmentally compatible (quieter and pollution-free), fuel-efficient aircraft.

Flying Circus

Testing out the drawing board ideas has brought some weird machinery into existence. The Bell Tilt Rotor Research Aircraft can, as the name implies, tilt its engines vertically and take off like a helicopter. Once off the ground, the rotors tilt forward into the horizontal attitude and, together with the fixed wing, generate lift in the normal way. This programme is aimed at developing more advanced vertical and short take-off and landing aircraft for use in difficult airport areas where long runways and shallow glide paths are impossible. They could also be a regular feature of future 'bus-stop' airports close to city centres.

Pivoting Wings

We naturally expect aircraft to be symmetrical vehicles. The port wing is always swept back at the same angle as the starboard wing. An aircraft with one wing swept forward and one swept back wouldn't fly. Wrong! Several decades ago, NASA's Robert T. Jones tested the idea in a wind tunnel and it worked. Scepticism and insufficiently advanced technology meant that the aircraft has not been built until now. It even has advantages over conventional first generation supersonic transports, producing a substantially quieter sonic boom. At low speed, the wing is kept at right angles to the fuselage. At high speed, the whole wing pivots up to 60° to reduce drag. In this configuration, the aircraft looks rather like a pair of flying scissors.

HiMAT

Inevitably, NASA is involved in a great deal of military aircraft research. The next generation of fighters must combine very high speeds and manoeuvrability, but remain within the g-forces that a pilot can withstand. To this end NASA has flight tested a scaled down remotely piloted airframe called HiMAT (Highly Manoeuvrable Aircraft Technology). The futuristic airframe is dropped from a modified B-52. The HiMAT pilot stays on the ground and flies the aircraft from the Dryden Flight Research Centre in front of typical flighter cockpit displays. If ground control is lost, an airborne pilot can take over. If both fail, HiMAT automatically flies in circles until control is regained (or its fuel runs out). I hope to look at HiMAT in detail in a future Astrologue.

Windy Caverns

The traditional image of aero research at this level is of a cavernous wind tunnel containing a full-size mock-up of the aircraft. This certainly still goes on, but much more advanced techniques can provide a means of 'flying' the aircraft before it is built. Computer dynamic analysis is still used to predict the behaviour of the new design in flight. A tethered scale model can be 'flown' in a wind tunnel to study the aircraft's behaviour at the limits of its performance. All the data from these studies can be used to program a simulator computer to give crewmen experience in handling the aircraft in potentially dangerous situations before they get off the ground in the real thing. →

Computer analysis, model testing and simulator flights all contribute to the designers' and pilots' understanding of the behaviour of the aircraft in the air. The fourth stage is the acid test — a NASA research pilot must actually strap the strange new machine to his seat and probe the limits of the flight envelope for himself.

Where Can I Get.....


The most common inquiry I receive in the Astrologue mail is, 'Where can I get slides, posters, photos, etc of astronauts, spacecraft, rockets, the planets.....?' I can answer you all by saying Space Frontiers. They will gladly supply sets of slides, postcards, charts, posters, mission badges, T-shirts, video tapes, movies, sound cassettes and replica plaques.

The slide sets cover Mercury, Gemini, Apollo, Skylab, Apollo-Soyuz, Space Shuttle, Mariner, Viking, Pioneers 10 and 11, Voyagers 1 and 2, stars and planets, rockets, storms and weather, space centres, 21st century space colonies and UFOs. They come in everything from five-slide sets at £1.75 to mammoth 80-slide sets at £16. A general set called 'Image of Space' (15 slides), showing an Apollo launch, the Earth from space, Earth-rise over the Moon, Buzz Aldrin on the Moon, UV activity in the Sun, a Skylab spacewalker, etc is available for £5 all inclusive. Quality and presentation are first class.

Science Museum

If you're in London, you can come by a set of Space Frontiers postcards at the Science Museum (nearest tube — South Kensington). 'Men in Space', a six-card set, and 'Man On The Moon', a 12-card set from the Hansen Planetarium in Salt Lake City, are available from the Museum shop.

While you're there it's worth popping into the ground floor 'Exploration' display. The theme is 'the extension of mankind's faculties by artificial means.' This special area is regularly brought up to date. In addition to the third floor space exploration and rocketry display, 'Exploration' features the Apollo 10 Command Module (not a replica — it's the real thing) and a full-size copy of the Apollo 11 Lunar Module.

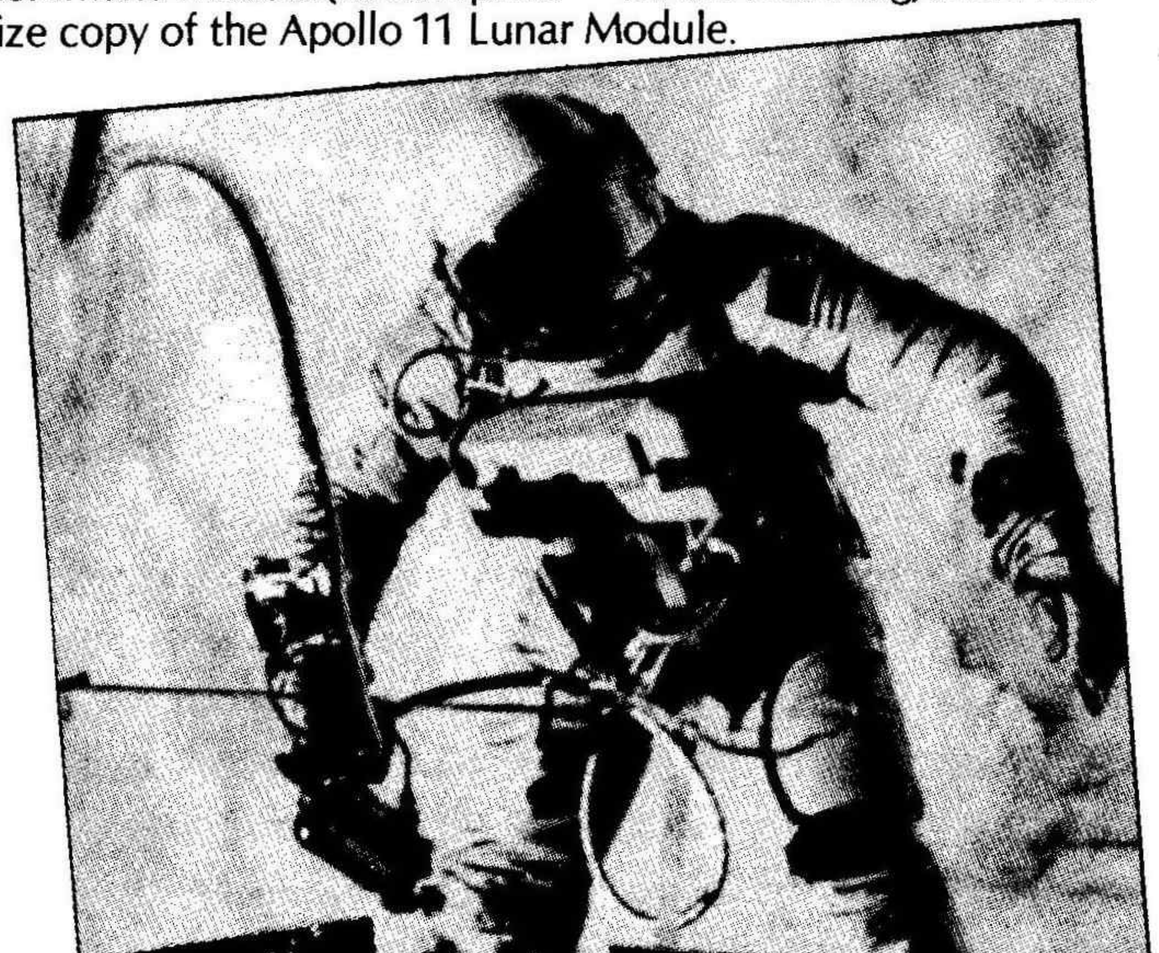



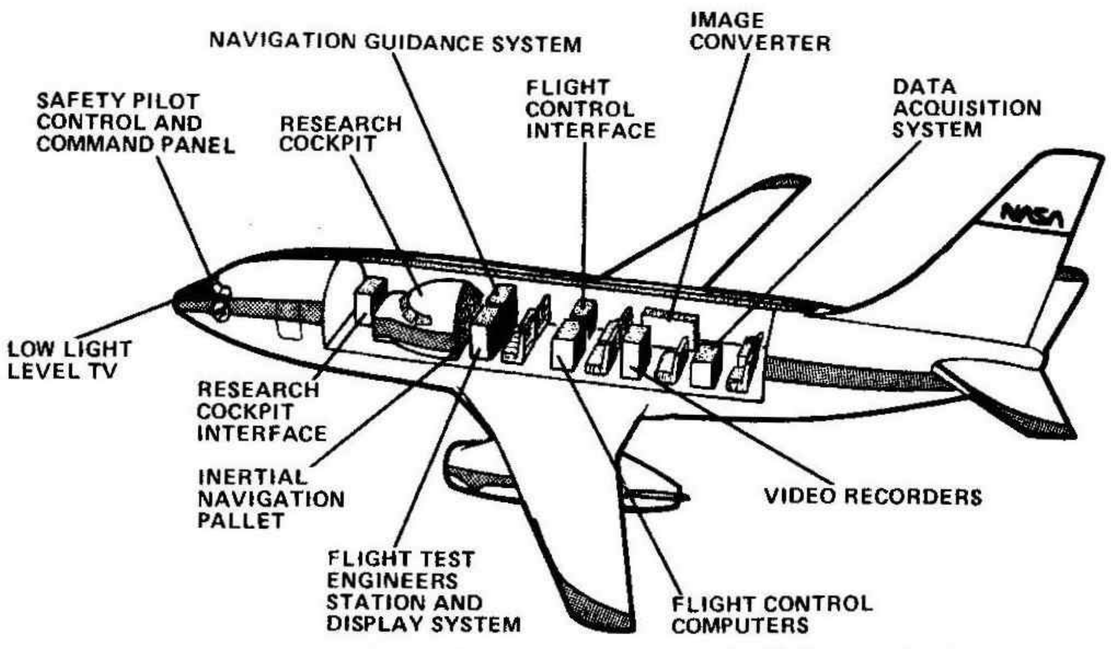


Fig.1 This modified Boeing 737 was used to study flying and take-off/landing routines in bad weather and the use of 'smart' avionics to assist in air traffic control. The Terminal-Configured Vehicle (TCV) can be flown from the research cockpit with the conventional cockpit crew providing a safety back-up. The aim of the programme is to reduce hold-ups at airports due to bad weather, reduce the separation of aircraft on take-off and landing and save fuel by using the most fuel-efficient landing programs. The end result — airlines and airports can substantially cut their losses.

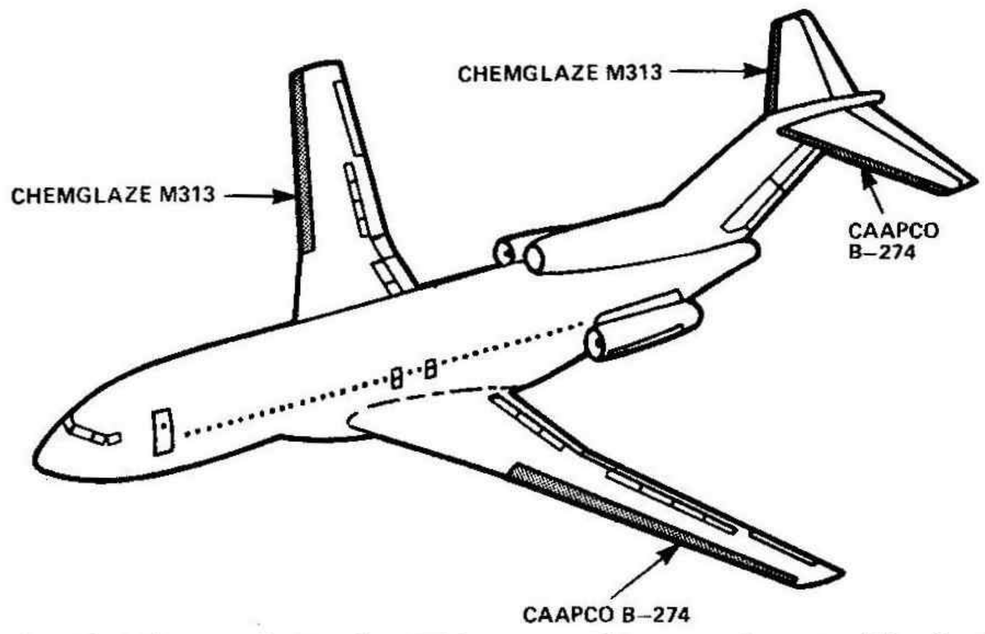


Fig.2 An Air Micronesia Boeing 727 was used to experiment with plastic coatings to reduce skin friction drag on wing and tail surfaces in a tropical environment. Two types of coatings — Chemglaze M313 and CAAPCO B-274 — are being investigated. The location and extent of the coatings on the 727 are shown above. Potential fuel savings from small drag reductions are substantial.

SHORTS

The Arianespace consortium has signed a $150 million contract with the Columbian government to launch two telecommunications sateliites, Satcol 1 and 2, into geostationary orbit in 1984.

The Mark II version of the Skyflash medium range, air-to-air missile has fallen prey to the latest defence cuts. The Mk. II version would have incorporated an improved homing head and electronic counter measures. The Mk I will have to be improved if it is to be a worthwhile weapon in service until the late 1980s.

BUYLINES

All manner of spaceflight memorabilia are available from Space Frontiers Ltd, 30 Fifth Avenue, Havant, Hampshire PO9 2PL. Tel:0705 475313. Send for details, price lists, etc.

Ed White floats in space, the solar wind experiment rises on the moon and supermen exercise in Skylab. Space Frontiers will supply these and many, many more in full colour.

Our lead photograph is the Apollo 10 Command Module, now on display in the Exploration section of the Science Museum, South Kensington.

ETI

The watches everyone wants at prices everyone can afford.

SENSATIONAL SEIKO OFFER



Three genuine Seiko quartz masterpieces – the world's most wanted watches – at the sort of incredible prices only Mitrad's purchasing power makes possible. (Check at any jewellers and see how much you save).

SEIKO QUARTZ DIGITAL ALARM CHRONOGRAPH/TIMER

Seiko prestige and precision in an elegant gentleman's watch. Exceptionally clear and uncluttered digital presentation give a continuous readout in hours, minutes, seconds, day and date, and with month, day and date calendar. Alarm, with AM/PM indication, sounds twice a second for 10 seconds, then four times a second for 10 seconds. Hourly time signals. 12 hour stopwatch records elapsed time and lap times to 1/100 second. Countdown timer sounds a continuous tone at the end of the selected time. Pushbuttom illumination. Water resistant. Hardlex glass. Stainless steel case with black panel. Adjustable stainless steel strap. In presentation box with operating instructions.

SPECIAL OFFER PRICE

ONLY £34.95

plus £1.25 p&p
Trade £26. Add 15% VAT + £1.50 p&p per order. *(Minimum order 5 watches, one style or mix of styles)*

SEIKO QUARTZ ANALOGUE WATCH

A beautiful, classically styled, ladies watch that combines elegance with the incredible accuracy of Seiko quartz technology. Gold plated case with stainless steel back. Gilt face with clear gold markings. Hardlex glass. Most attractive strap that has the appearance of the fashionable bangle strap, but is so flexible and adjustable that it will fit virtually any wrist – even a small child's. Gold safety chain. In presentation box with setting and care instructions.

SPECIAL OFFER PRICE

ONLY £49.95

plus £1.25 p&p
Trade £41. Add 15% VAT + £1.50 p&p per order. *(Minimum order 5 watches, one style or mix of styles)*

☎ Credit card holders may telephone (0536) 522024 24 hours a day stating card number for immediate attention.

NB. Please do not use the coupon for trade orders.

SEIKO QUARTZ MEMORY BANK CALENDAR WATCH

Inimitable Seiko styling in a gentleman's precision watch. Clear digital presentation provides continuous display of hours, minutes, seconds, month, day and date for optional 12/24 hour cycle. Optional monthly calendar display of month, year and dates for designated month (any month, January 1930 to December 2009). Sunday indication and Sunday dates flashing. Memory bank stores up to 11 dates, displays 'MEMO' and flashes on designated dates. Display flashes as battery life nears end. Pushbutton illumination. Water resistant. Hardlex glass. Stainless steel case with black panel. Adjustable stainless steel strap. In presentation box with operating instructions.

SPECIAL OFFER PRICE

ONLY £27.95

plus £1.25 p&p
Trade £20. Add 15% VAT + £1.50 p&p per order. *(Minimum order 5 watches, one style or mix of styles)*

MITRAD

MITRAD 68/70 High Street, Kettering, Northants, NN16 8SY.
Telephone (0536) 522024

The premier mail order house specialising in quality products and superior after-sales care.

To Mitrad 68/70 High Street, Kettering, Northants.
Please send me

- ☐ Seiko Quartz Digital Alarm Chrono. at £36.20 (incl. p&p)
- ☐ Seiko Quartz Memory Bank Calendar Watch at £29.20 (incl. p&p)
- ☐ Seiko Quartz Analogue Watch at £51.20 (incl. p&p)

Total value of my order £ _____

I enclose cheque/PO made payable to Mitrad

Or debit my Access/Barclaycard No. _____

Signature _____

Name _____

Address _____

_____

(BLOCK LETTERS PLEASE)

Allow up to 28 days for delivery. Full refund if not completely satisfied. Registered in England No. 2554356.

ETI 4/01

GMT ELECTRONICS

Freepost A
Birmingham
B19 1BR
021·233·2400

- FREEPOST ON ORDERS
- VAT INCLUSIVE PRICES
- ADD 30p P&P
- 24 HR PHONE ANSWERING SERVICE
- ACCESS
- VISA
- CASH
- CHEQUE

ALL PRICES IN PENCE EACH UNLESS OTHERWISE STATED

C·MOS (BUFFERED)

HEF4000	22	HEF4044	105	HEF4512	138	CA3046	84	IN914	5	BC182L	12
HEF4001	22	HEF4046	133	HEF4516	127	CA3080E	77	IN4001	5	BC184	11
HEF4002	22	HEF4047	109	HEF4517	478	CA3130E	99	IN4002	5	BC184L	12
HEF4006	119	HEF4049	57	HEF4518	118	CA3140E	48	IN4004	7	BC212	11
HEF4007	22	HEF4050	57	HEF4519	69	CA3189E	293	IN4007	9	BC212L	12
HEF4008	100	HEF4051	87	HEF4520	118	LM301AN	34	IN4148	4	BC214	11
HEF4011	22	HEF4052	90	HEF4521	235	LM339N	78	IN5402	15	BC214L	12
HEF4012	22	HEF4053	90	HEF4528	124	LM380N	104	2N2369	21	BC547	13
HEF4013	57	HEF4066	62	HEF4532	150	LM381AN	198	2N2646	46	BC548	11
HEF4014	105	HEF4067	475	HEF4534	638	LM3900N	75	2N2926G	13	BC549	12
HEF4015	100	HEF4068	22	HEF4539	138	MC3403P	156	2N3053	19	BC557	15
HEF4016	57	HEF4069	22	HEF4585	122	NE531	131	2N3054	55	BC558	15
HEF4017	100	HEF4070	22	HEF4724	214	NE536T	259	2N3055	55	BCY70	15
HEF4018	100	HEF4071	23	HEF40097	113	NE555N	28	2N3702	9	BCY71	15
HEF4019	58	HEF4072	23	HEF40098	92	NE556N	66	2N3704	9	BD131	39
HEF4020	112	HEF4073	23	HEF40106	78	NE566N	171	2N3705	10	BD132	39
HEF4021	107	HEF4075	23	HEF40160	149	NE570N	485	2N3773	297	BD139	39
HEF4022	103	HEF4076	130	HEF40192	149	NE571N	505	2N3819	22	BD140	39
HEF4023	22	HEF4077	22			RC4136	146	2N3820	39	BFR90	333
HEF4024	78	HEF4078	23	**Voltage Regulators**		T8A120S	88	2N3904	9	BFX85	29
HEF4025	22	HEF4081	23			TDA1022	713	2N5457	39	BFY50	17
HEF4026	244	HEF4082	23			TDA1034B	239	2N5459	35	BFY51	17
HEF4027	57	HEF4085	80	LM309DA(K)	119	TL081CP	84	40673	88	BRY39	50
HEF4028	89	HEF4086	80	UA723CN	42	TL084CN	156	BC107	14	BSX20	21
HEF4029	113	HEF4093	63	UA7805CU	78	UA741CN	20	BC108	14	CL8960	2850
HEF4030	58	HEF4094	219	UA7812CU	78	UA741CT	47	BC108C	18	TIP31	48
HEF4031	250	HEF4104	208	UA7815CU	78			BC109	14	TIP32	54
HEF4035	138	HEF4502	114	UA7912CU	97	**Zener Diodes**		BC109B	19	TIP41C	76
HEF4040	107	HEF4505	714	UA7915CU	97			BC109C	20	TIP42C	76
HEF4041	94	HEF4508	230	UA78L06CS	38	400mW C4V7-C33		BC148	10	TIP2955	75
HEF4042	83	HEF4510	135	UA78L12CS	38	BZY88/BZX79		BC158	10	TIP3055	60
HEF4043	100	HEF4511	157	UA78L15CS	38	+ Voltage	9	BC177	17	TIS43	36

CAPACITORS

Electrolytic Axial — −10% to +50% Tol. — Order Code Cap 018 + µF

µF	V	16	25	40	63
1.0					9
1.5					9
2.2					9
3.3					9
4.7					9
6.8			9		10
10			8		10
15		8		9	11
22			8		13
33		8		9	
47			8	11	13
68		9			
100			9	13	
150		9	10		31
220		13		26	36
330				30	40
470			23	32	47
680		21	30	39	54
1000		25	30	59	
1500		35	39		
2200		42			

Polyester Radial Leads — Order Code Cap 352 / Cap 360 + Value

Dipped Type, C280/352 Style
Moulded Type, 10.2mm Pitch

µF	352	360	µF	352	360
.001		7	.1	7	9
.0015		7	.15	8	10
.0022	6	7	.22	9	11
.0033	6	7	.33	11	
.0047	6	7	.47	14	
.0068	6	7	.68	17	
.01	6	8	1.0	21	
.015	6	8	1.5	30	
.022	6	8	2.2	35	
.033	6	8			
.047	6	8			
.068	7	8			

Electrolytic Radial Leads — −10% to +50% Tol. — Order Code Cap 034 + µF

µF	V	10	16	25	35	40	50	63
.47								7
.68								7
1.0								7
1.5								7
2.2								7
3.3								7
4.7						7		8
6.8				7			8	9
10			7			8		9
15			7	8			9	11
22		7	8			9	11	
33			8	9		11		
47		8	9		11			
68			9	11				
100		9						
150		11						

D.I.L. Sockets

8 Pin Low Profile Socket Tin	12	DIL SKT 8
14 Pin Low Profile Socket Tin	14	DIL SKT 14
16 Pin Low Profile Socket Tin	16	DIL SKT 16

P.C.B. Components

Dalo Pen, Blue Ink, Slow Drying	89

RESISTORS

		Order Code
Carbon Film, Fixed		
0.25W, E24 Values IRO-10M, 5% Tol. 100/100 (Mult 10/Value)	2 each	Res RD¼
0.5W, E12 Values IRO-4M7, 10% Tol.	3 each + Value	Res RD½
Metal Film, Fixed		
0.5W, E24 Values, SRI-1M, 2% Tol.	8 each	Res MR30
2.5W, E12 Values, 10R-27K, 5% Tol.	18 each + Value	Res PR52
Metal Glaze, Fixed		
0.5W, E24 Values, 1M-33M, 5% Tol.	16 each + Value	Res VR37

Skeleton Presets, Miniature

		Order Code
0.1W, E3 Values, 100R-1M, Lin. Vertical Mounting	8	Min. Preset V
0.1W, E3 Values, 100R-1M, Lin. Horizontal Mount	8	Min. Preset H + Value
Skeleton Presets, Standard		
0.3W, E3 Values, 100R-4M7, Lin. Vertical Mounting	11	Std. Preset V
0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mount	11	Std. Preset H + Value
Potentiometer, Rotary		
0.5W, E3 Values, 1K-2M2 Lin.	39	Ro Pot Lin
0.25W, E3 Values, 4K7-2M2 Log.	39	Ro Pot Log + Value
Potentiometer, Slider		
0.5W, E3 Values, 2K2-470 . Lin.	45	Sl Pot Lin
0.25W, E3 Values, 1K0 - 1M0 Log.	45	Sl Pot Log + Value

MAINS TRANSFORMERS — Order Code

Secondaries may be connected in series or parallel to give wide voltage range
Primaries 0-220, 240V

6VA – Clamp Type Construction — 235 each

Approx. 18% Regulation F.C. 54, H36, W35

0-4.5V, 0-4.5V Secondaries — Trans 6VA
0-6V, 0-6V
0-12V, 0-12V
0-15V, 0-15V
0-20V, 0-20V

20VA – Clamp Type Construction — 360 each

Approx. 16% Regulation F.C. 70, H48, W46

0-4.5V, 0-4.5V Secondaries — Trans 20VA
0-6V, 0-6V
0-12V, 0-12V
0-15V, 0-15V
0-17.5V, 0-17.5V
0-20V, 0-20V

VERO ELECTRONICS PRODUCTS

2.5" x 5" .1" pitch Veroboard	71	200-21069J
3.75" x 5" .1" pitch Veroboard	79	200-21072D
2.5" x 1" .1" pitch Veroboard (5)	85/Pack	200-21076C
3.75" x 5" .1" pitch Plain Board	68	200-21078H
5.82" x 2.9" .1" pitch V-Q DIP Board	135	200-21084E
Spot Face Cutter	107	203-21013A
Pin Insertion Tool for .040 type pin	147	203-21015F
DS Pins .040 (100)	44/Pack	200-21087G
SS Pins .040 (100)	44/Pack	200-21017B
Verowire Kit (1-pen, 2-wire, 25-comb)	454/Kit	200-21341D
Verowire Combs (25)	109/Pack	200-21339F
Verowire Wire (2)	109/Pack	200-21340G

Plastic Boxes – Boss Industrial Mouldings
Moulded Box and Close Fitting Flanged Lid
ABS Box, C/W Brass Bushes, and Lid In Orange

		Order Code
L112 W82 D31	99	Case BIM2003 OR
L150 W80 D50	131	Case BIM2005 OR
L190 W110 D60	223	Case BIM2006 OR

Plastic Boxes with Metal Lids
Recessed Top Box
ABS Base, C/W Brass Bushes, In Orange
1mm Aluminium Top Panel Finished Grey

		Order Code
L85 W56 D29	112	Case BIM4003 OR
L111 W71 D42	150	Case BIM4004 OR
L161 W96 D53	208	Case BIM4005 OR

Diecast Boxes
Diecast Box and Flanged Lid
Aluminium Box and Lid in Natural Finish

		Order Code
L113 W83 D31	124	Case BIM5003 NA
L152 W82 D50	215	Case BIM5005 NA
L192 W113 D61	334	Case BIM5006 NA


SWITCHES

			Order Code
Miniature Toggle – Honeywell			
SPDT		67	SW 8A1011
SPDT	C/Off	81	SW 8A1021
SPDT	Double Bias To Centre	90	SW 8A1041
DPDT		99	SW 8A2011
DPDT	C/Off	111	SW 8A2021
Miniature Push – C & K			
SP	Push To Make, Momentary	62	SW 8531
SP	Push To Break, Momentary	62	SW 8533

GMT ELECTRONICS PROJECTS	KIT	BUILT UP
FREE-STANDING COMPLETE TELETEXT UNIT - FULL SPEC	£199-90	£275-00
TELETEXT DECODER BOARD + REMOTE HAND CONTROL	£135-90	£160-00
TELETEXT COMPATIBLE TUNER AND P.S.U.	£ 46-90	£ 57-00
TELETEXT COMPATIBLE PAL ENCODER + MODULATOR	£ 22-90	£ 35-00
F.E.T. OUTPUT 100W MONO POWER AMPLIFIER MODULE	£ 27-50	£ 35-00
X-BAND DOPPLER RADAR ALARM MODULE - MARK II	£ 35-90	£ 44-00
ONE AMP P.S.U. MODULE (SPECIFY 5 OR 12 VOLTS)	£ 7-50	£ 10-00
SIMULATED INERTIA MODEL TRAIN CONTROLLER	£ 22-50	£ 35-00
SIMULATED INERTIA SLOT RACER CONTROLLER	£ 27-50	£ 40-00
MODEL TRAIN STEAM SOUND SIMULATOR MODULE	£ N/A	£ 5-00

LOW-COST, RUGGED TEMPERATURE CONTROL

HIGH QUALITY

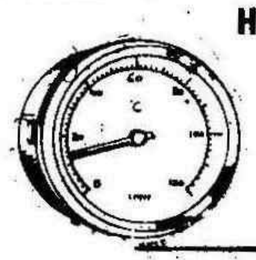

TEMP. GAUGE 0° -120° C
Remote sensor on 38" capillary, panel mounting dial 55mm. dia.
ONLY £1.85
(Incl. P&P)

16A 240V RANCO THERMOSTAT
Wide control range (low room temp. to over boiling point) Sensor on 22" capilliary. **£2.30,** including control knob.

RANCO THERMAL CUT-OUT 100° C
15A 240V. Sensing coil on 41" capillary. Panel mounting with reset button.

BUY ONE EACH OF ABOVE FOR £4.85

LIGHT DEPENDENT RESISTORS in plastic housing with window, 18" heavy duty lead. Two types — A similar to ORP61. B Similar to ORP12. You normally pay well over double for Resistor alone. Either type **30p** each or **£2.35** for 10 (any mix).

DOUBLE ENDED SMITHS BLOWERS
2 output apertures, 53 x 103 mm. Large flange. **Only £5.50.**

SMALL INDUCTION MOTOR (shaded pole), double ended with ¼" x 3½" shafts, 240V. **£3.25.**

BULGIN STRAIN RELIEF SLEEVE 10 FOR 30p

USEFUL RUBBER GROMMETS. Fit ¾" hole. **10 for 20p.**

20WATT RESISTOR. 410Ω 5% wire ended. **Only 50p.**


L.E.M. SERVICES
239 RUGBY ROAD
LEAMINGTON SPA CV32 6DY
WARWICKSHIRE



RELAYS BY KEYSWITCH
10A 2-Pole C/O 240V Coil.
ONLY 80p
2 for **£1.50**
5 for **£3.50**

Panel M.E.S. Bulb Holder. High quality. Red lens. **30p**

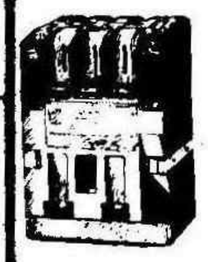BULGIN GLASS FUSES
20 mm 1A Quick Blow
10 for 40p
1" (same size as 13A plug fuse but not to BS1362). Will fit most 1¼" chassis mount fuse holders, 10A quick blow 5A anti-surge, 3A quick blow.
10 (any mix) 40p
100 for £3



GEC CONTACTOR
3 heavy duty normally open contacts 600V 35A. 240V coil.
ONLY £4.50.

TOP QUALITY CHROME TOGGLE SWITCHES
2 pole C/O centre off 10A 240V, **80p, 2 for £1.50, 5 for £3.50.**
2 Pole make, biased off 2A 240V.
30p. 4 for £1

CAPACITOR, 800V AC, RMS, 0.01 MFD.
30p each

ADD 50p P&P
ORDERS OVER
£2.50 post free

BUILD YOUR OWN METAL DETECTOR
VLF/TR VCO/TR IB/TR BFO . . .

Pre-aligned search heads — test equipment not required. Literature available in return for SAE. Manuals and parts sold separately: write or phone for price. Export welcome: write for quote.



Shadow VLF/TR. Full specification discriminator, not just ferrous/nonferrous indication. It works by measuring the conductivity of the target; now you can reject nails bottle caps even aluminium foil and ring pull tabs! Full ground effect exclusion over normal or high permeability soils.
The head is thermally and capacitively shielded.
4 modes: deepseeking VLF plus 3 TR discriminating ranges.
Push button "memory" tuning. Performance equals commercial detectors costing £200! As described in ETI.
Complete kit now only £87.67 inc. VAT & post!!

Shadow TR/1B

Individual parts: Search head **£21.33** PCB £6.80 Case £5.33 Adjustable shaft assy. £5.10. LM393 £1.12. Manual (gives more info. than ETI article — and extra function) £1.12. **All inc. VAT & post!** (Other parts also available separately)

Shadow TR/1B (illustrated). A true transmit receive/induction balance detector at a budget price for anyone who doesn't need discrimination. Waterproof and thermally insulated search head. Good sensitivity. Built-in speaker and headset jack. **Complete kit £33.60** inc. VAT and Post.

Shadow TR/VCO. An advanced version of the TR/IB. Use as a sensitive 1B machine or switch to VCO mode when the sound changes to a varying pitch, allowing easier use over mineralised ground and enabling detection of negative, high permability anomalies. **Kit price £38.67** inc VAT and Post.

Matching stereo headphones for all Shadow models £5.85 inc. VAT and Post.

Shell Kit. Consists of the (hard to find) hardware items, for detectors of your own design. Fully adjustable shaft with handle, search head mouldings (int. diam. 185mm) with hinge assembly, special clips to mount your own control housing (any box is suitable). Completely non-metallic and undrilled. With assembly instructions **£14.45** inc. VAT and Post.

ALTEK
(ETI), 1 Green Lane
Walton-on-Thames Surrey

Order by post or phone (24 hours). Access & Visa Cards quote number. Callers by appointment only please.
Phone (093 22) 44110 anytime!

DRUM MACHINE




Drums, cymbals, snares and bongos. You can simulate these instruments with this 'double percussion' project. The instruments can be played either manually or automatically using a built-in sequencer. Design by Ray Marston. Project development by Steve Ramsahadeo.

This attractive little musical instrument has two 'percussion simulator' channels. Channel 1 can be used to simulate the sounds of normal drums only: channel 2 can be used to simulate the sounds of all types of drums, including snares, plus metallic percussion sounds such as cymbals, etc. On each channel, the envelope decay times and the basic musical tones, etc., are fully variable using the manual controls, to enable a wide range of percussion sounds to be simulated. The outputs of the two channels are mixed internally and can be fed to an external power amplifier from a single output socket. The complete instrument is powered from a 12 V battery pack.

Play It, Sam

The instrument can either be played manually, automatically, or by a combination of the two methods. In the manual mode, each channel can be played using a small speaker, connected to the channel input: the speaker acts as a 'drum head' transducer and triggers a percussion sound when the cone is tapped with a finger or stick.

The instrument can be played automatically using the built-in eight-step double sequencer. Each channel of the sequencer is used to control one of the channels of the percussion instrument, and can be programmed with a DIL package of eight SPST switches to generate any one of a variety of rhythms. The sequencer can be used in the fully automatic mode, in which it continuously cycles through the eight-step sequence, or can be used in a triggered, or manual initiate, mode in which it runs through a single eight-step sequence each time that an external switch is momentarily closed. The manual initiate facility enables the internally-generated rhythm to be manually synchronised to an external beat (with a foot switch, etc), or to be introduced into the music only in those parts where it is required.

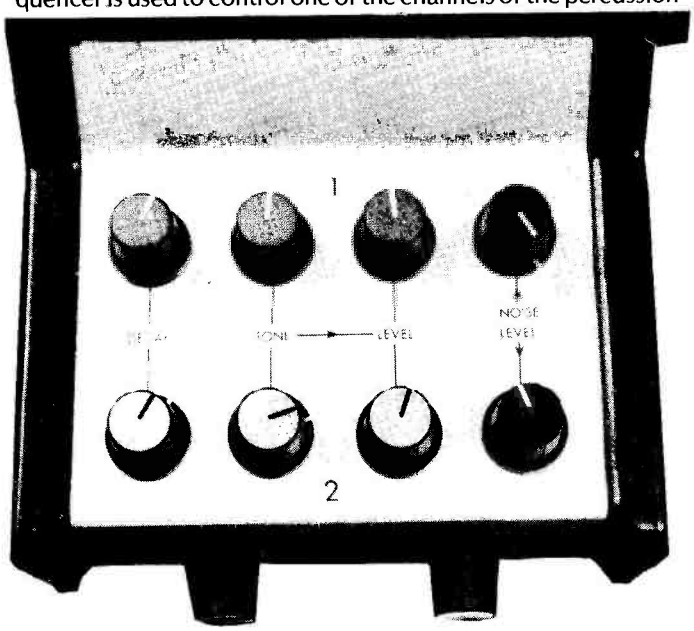


The manual and automatic playing methods operate in the OR mode. In other words, manually-initiated percussion sounds can be played at the same time as the automatically initiated sounds. A particularly attractive way of using the instrument is to play it mainly in the manual mode, but to occasionally bring in a few bars of automatic sequencing with a foot switch, using the manual initiate facility. The unit thus acts as a highly versatile musical instrument.

Construction

The circuitry is built up on two PCBs, a single large board being used to hold all of the components (except the pots and switches) of the main double percussion instrument, and a smaller board being used for the components of the sequencer circuit. The unit uses a good deal of interwiring between the PCB and the total of eleven control pots, etc., so some care is required in the construction.

Start the construction by building up the main PCB, taking the usual care over the component polarities. Use Veropins to facilitate the connections from the PCB to the ten control pots.

When construction of the main PCB is complete, give it a functional check by temporarily connecting the ten pots to the unit, wire a couple of small speakers (impedance not important) to the two input terminals, connect the unit to a 12 V supply and take the output to an external power amplifier. Check that plain drum sounds can be manually generated on channel 1, and all types of percussion sounds from channel 2. Note on channel 2 that Q5 is used as a white noise source (for generating cymbal

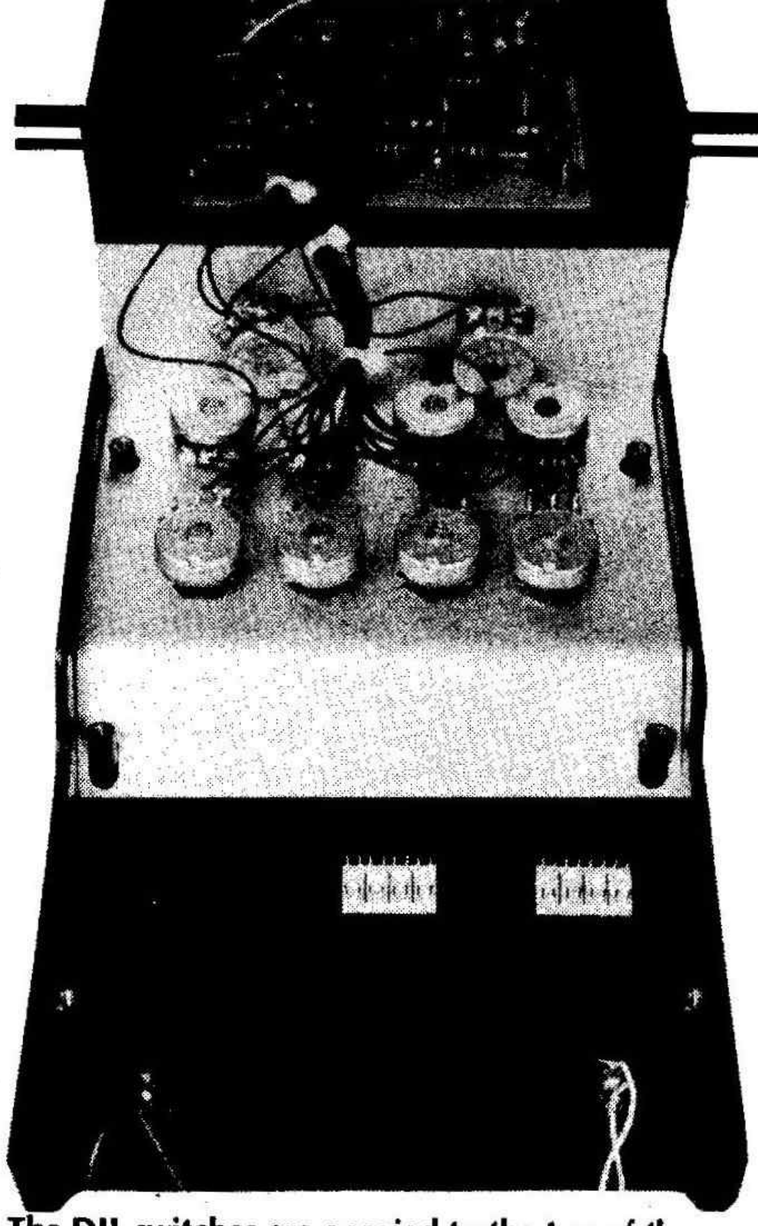

The DIL switches are epoxied to the top of the case as shown here. The sequencer board can then be secured by plugging the DIL sockets onto the exposed pins.

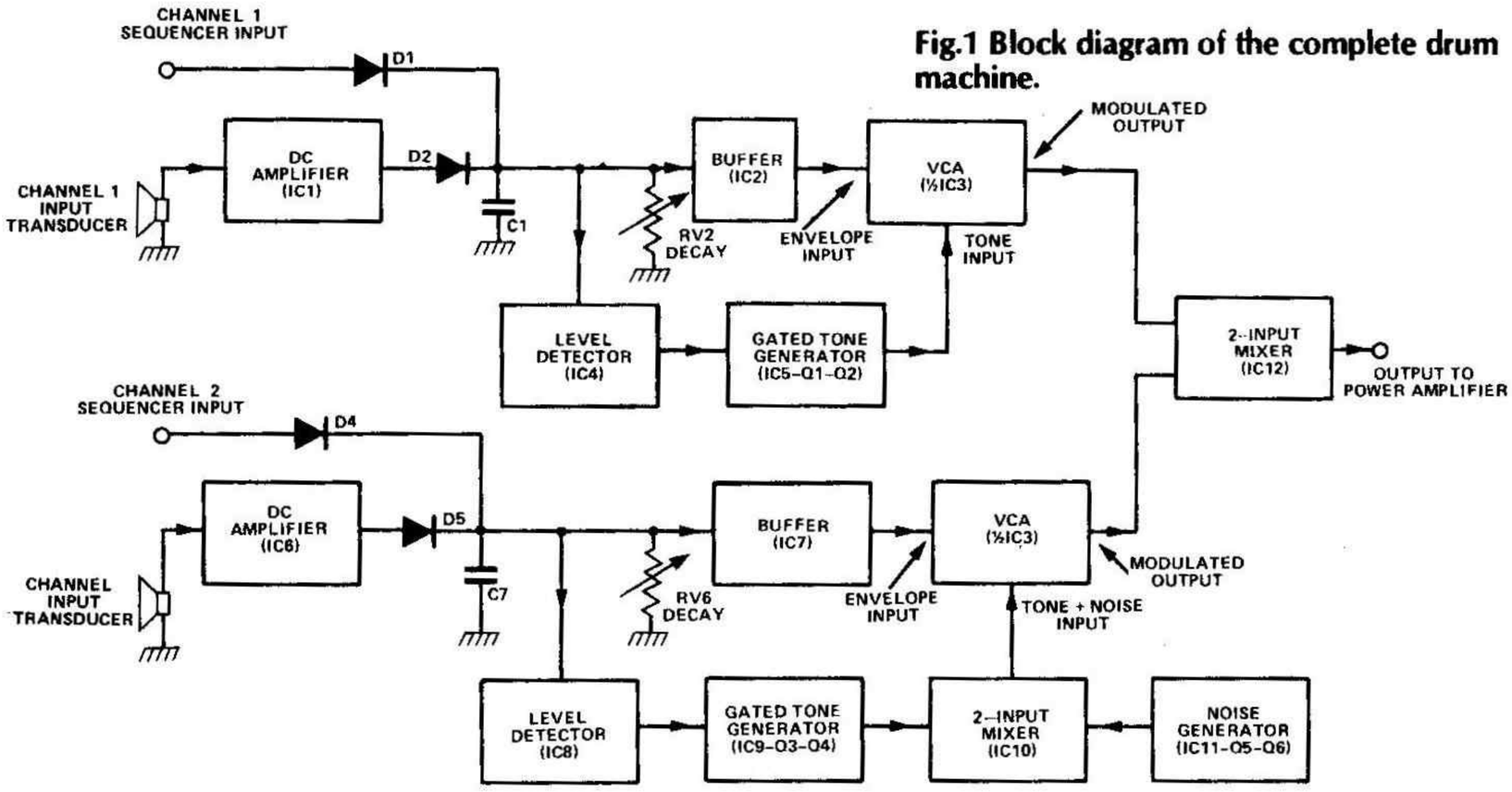



Fig.1 Block diagram of the complete drum machine.

BUYLINES

No unusual components are used in this project, your local emporium should meet your requirements. However, if you experience difficulty in obtaining the NE570, Watford Electronics are stockists of this device.

Collet knobs are available from Electrovalue Ltd. and the case from West Hyde Developments, order as BOC668.

Fig.2 Circuit diagram of both channels of the drum sound generator.

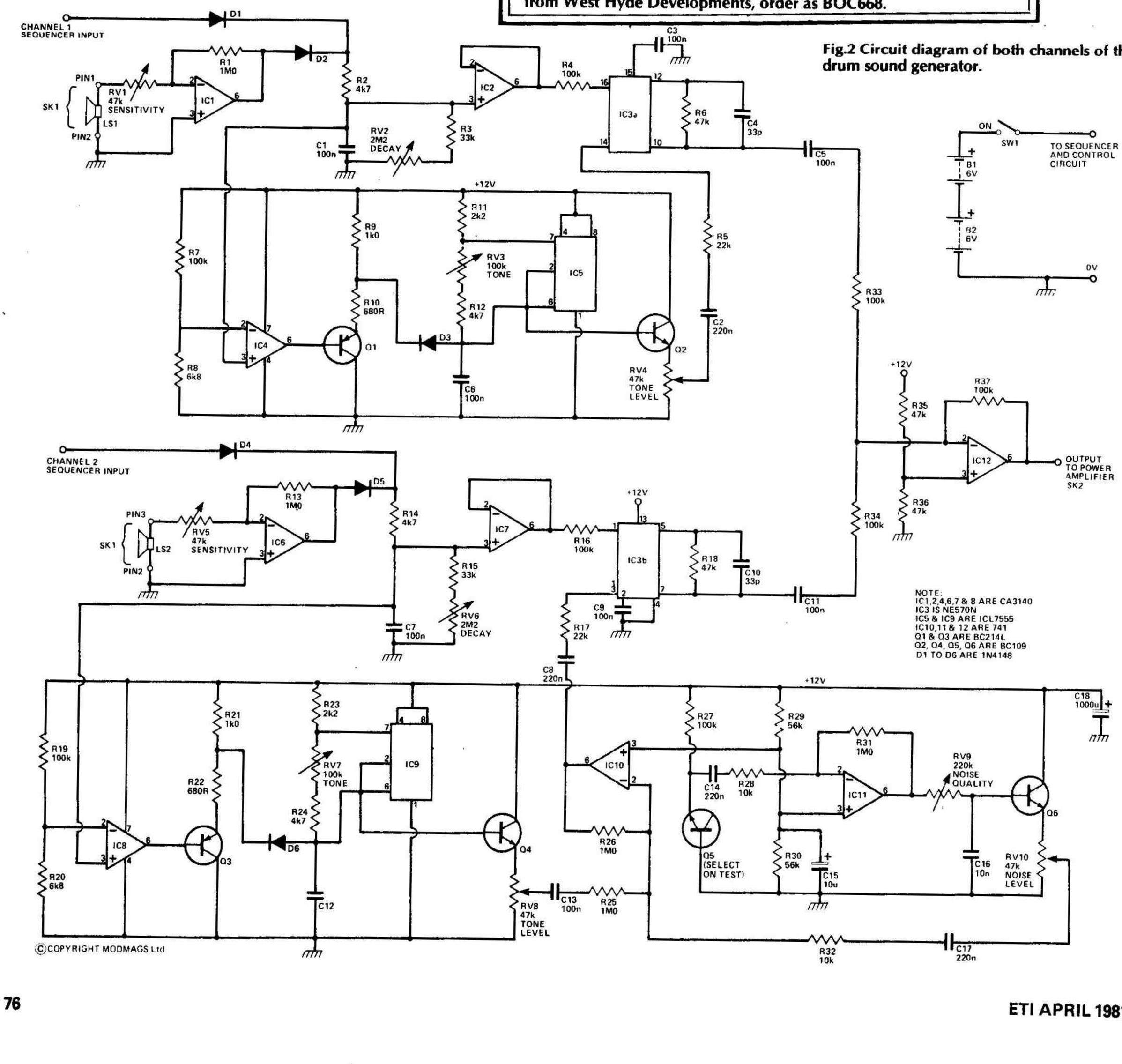

HOW IT WORKS

The basic instrument contains two essentially similar channels (see block diagram), each comprising a voltage-controlled amplifier (VCA), a gated tone generator and an envelope generator. The envelope generator produces the characteristic fast-attack/slow-decay modulation waveform of a percussion instrument and can be activated by either an external transducer (a speaker) or the pulse input of an automatic sequencer unit.

The outputs of the two channels are added in a two-input mixer and are made available at a phono socket, where they can be fed to a power amplifier. The channel 1 circuitry produces modulated tone signals only, and can be used to generate a range of simple drum sounds. The channel 2 circuitry incorporates a noise generator and a two-input mixer as well as a tone-generator, and can be used to reproduce all of the sounds of channel 1 plus snare drums, cymbals, etc.

The two channels of the instrument are basically similar, so let's start off with a detailed description of channel 1. When used in the manual mode the instrument is played using an external transducer such as a speaker (LS1), which is connected to the input of high-gain DC amplifier IC1. Each time that the transducer is tapped, the output of IC1 jumps abruptly positive and rapidly charges C1 via D2-R2: C1 then discharges exponentially via R3-RV2, to produce the characteristic fast-attack/slow decay modulation waveform of a percussion instrument. The waveform is then fed to one half of dual VCA IC3 via unity-gain buffer IC2, where it is used to control the gain of the VCA.

Note that the C1 modulation generator can be activated by either the transducer or by a pulse signal fed to C1 via D1-R1 from the independent sequencer circuit (auto mode). The C1 voltage is monitored by comparator IC4, which gates on astable IC5 whenever the C1 voltage exceeds a few hundred millivolts. The astable generates a symmetrical ramp waveform, which is buffered by Q1 and fed to the 'tone' input of VCA via level control RV4. The tone of the astable can be varied over the range 83 Hz to 1.4 kHz with RV3.

Thus, each time the channel is activated (by the transducer or by a sequencer) a modulation waveform is fed to one input of the VCA and a tone signal is fed to the other, to produce a modulated tone signal at output pin 10 of IC3. The signal is fed to one input of two-input mixer IC12. A wide variety of drum sounds can be simulated by suitable adjustment of RV2, RV3 and RV4.

Channel 2 is similar to channel 1, except that the output of the tone generator (from RV8) is fed to the VCA via a two-input mixer designed around IC10. The other input to this mixer is derived from a noise generator designed around Q5-IC11 and Q6. Here, the reverse-biased base-emitter junction of Q5 is used as a noise source and the noise signal is then amplified by IC11, filtered by RV9-C16 and made available via level control RV10.

The instrument is powered from a 12 V supply, derived from eight 1V5 cells. This supply is also used to power the Auto-Manual Eight-Step Sequencer unit.

The sequencer unit has two output channels, each of which produces a single or repeating sequence of up to eight 5 mS output pulses: the sequencing period can be varied over a wide range by a clock (or 'tempo') generator, and individual pulses can be programmed in or out on each channel with a dual-in-line package of eight SPST switches. The unit is designed to automatically sequence the double percussion instrument.


The unit comprises a clock generator (IC1), a 4017 counter (IC2) and two sets of switch-programmable clock/decoder coincidence detectors (IC1 and D3 to D18). The clock generator is designed around a 555 astable and generates a series of 5mS pulses, with the inter-pulse period variable over a wide range by RV1. The pulses are used to clock IC2.

IC2 is a 4017 counter with ten decoded outputs. These outputs sequentially go high on the arrival of each new clock pulse, with only one output being high at any moment in time. On each channel the decoded 4017 outputs that are required are fed to one side of a two-input AND gate (IC3a-IC3b or IC3c-IC3d) via a bank of diodes and switches, while the 5mS clock pulse is fed to the other side of the AND gate. The programmed sequence of 5 mS pulses are thus generated at the output of each AND gate.


When the unit is operated in the manual mode, the 4017 sequences automatically for the first eight clock pulses and then stops as its '9' output goes high and activates the inhibit pin: the single automatic sequence can be re-initiated by momentarily closing PB1 and thus resetting the 4017, so that the '1' output goes high on the arrival of the next clock pulse. The manual facility enables the sequencer to be manually synchronised to an external beat.

When the unit is operated in the auto mode the reset and inhibit pins of IC2 are shorted together by SW3. This configuration effectively causes the 4017 to see a double clock pulse as the '9' output goes momentarily high, thereby causing the '0' output to go high as the IC resets but then causing the '1' output to go high almost immediately. The net effect of all this is that the sequence repeats continuously when SW3 is set to the auto mode.

Fig.3 Circuit diagram of the eight-step sequencer unit.

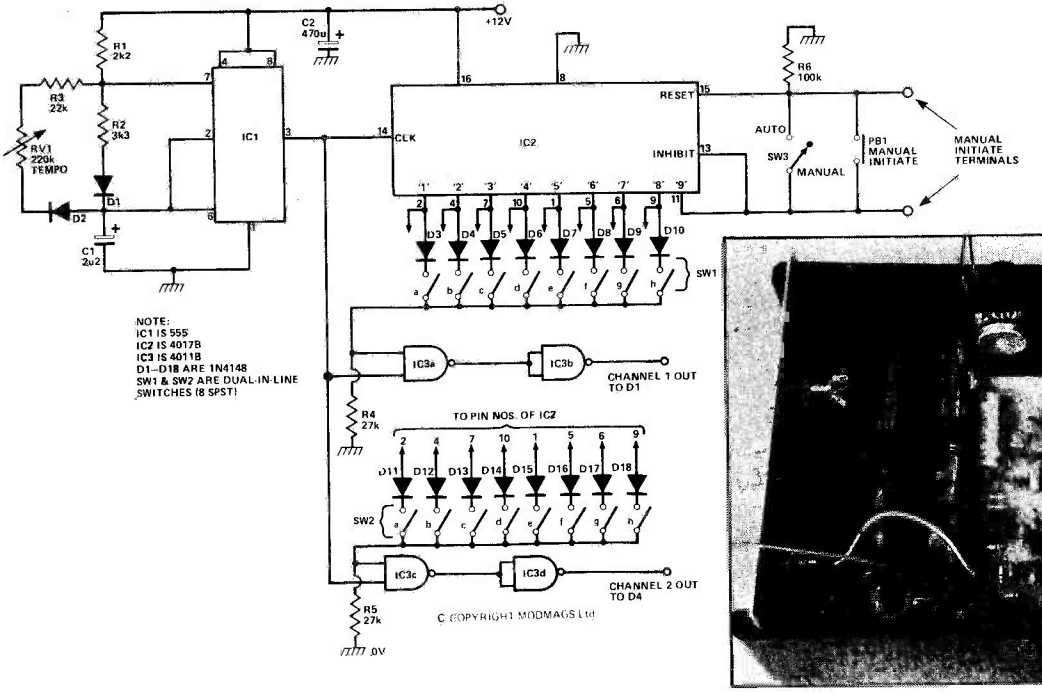

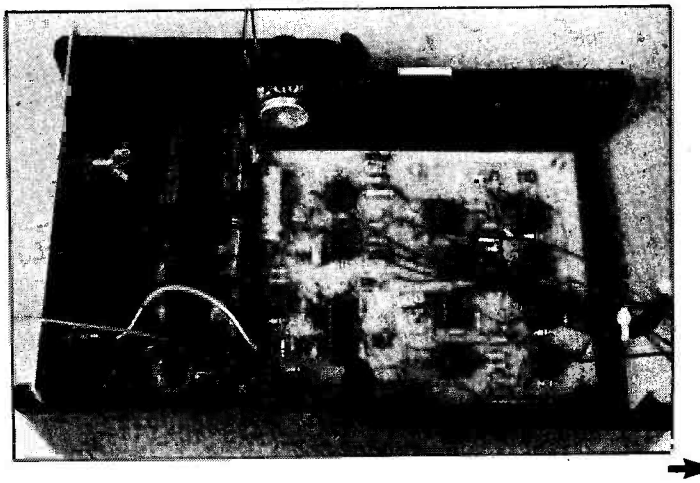Below: the sound generator board and batteries are mounted in the lower half of the case. RV1 (tempo control) can be seen mounted on the side — all other pots are situated on the front panel.



sounds, etc), and may have to be selected on test to produce an adequate noise level.

Proceed next with the construction of the sequencer circuit on the smaller PCB. Note that the two sets of DIL switches MUST be mounted in sockets, and that capacitor C2 is mounted on the *underside* of the PCB.

You can now proceed with the assembly of the two boards and all other components in the specified case. Note the following points. The large PCB is secured to the base of the case with stand-off pillars: leave sufficient space at the rear of the case to accommodate the battery pack (eight 1V5 cells). The ten percussion-control pots are mounted on the front section of the top half of the case.

The sequencer board is secured to the rear half of the top section of the case by the board's DIL switches, which are epoxied to the case. Proceed as follows.

First, hold the board in position below the case top and very carefully mark out the precise outlines of the two switches. Now cut two holes in the case top, to allow the switches to pass through the case. Next, remove the switches from their PCB sockets, push them into the holes so that the top faces are flush with the case top and then fix the two switches into place with epoxy or super-glue. When the glue has set, fit the PCB to the switches (and thus the case) by carefully inserting the DIL switches in the sockets. Tempo control RV1 is mounted on the right hand side of the lower half of the case.

Finally, to complete the construction, fit all the remaining switches and sockets into place and complete the interwiring. We recommend that you use jack sockets to connect the two 'drum head' speakers to the unit, configured so that the input pins short out if the speakers are removed.

When using the completed unit, note that, if the 'drum head' speakers are not used, they must be replaced by short circuits, to eliminate the possibility of circuit instability.



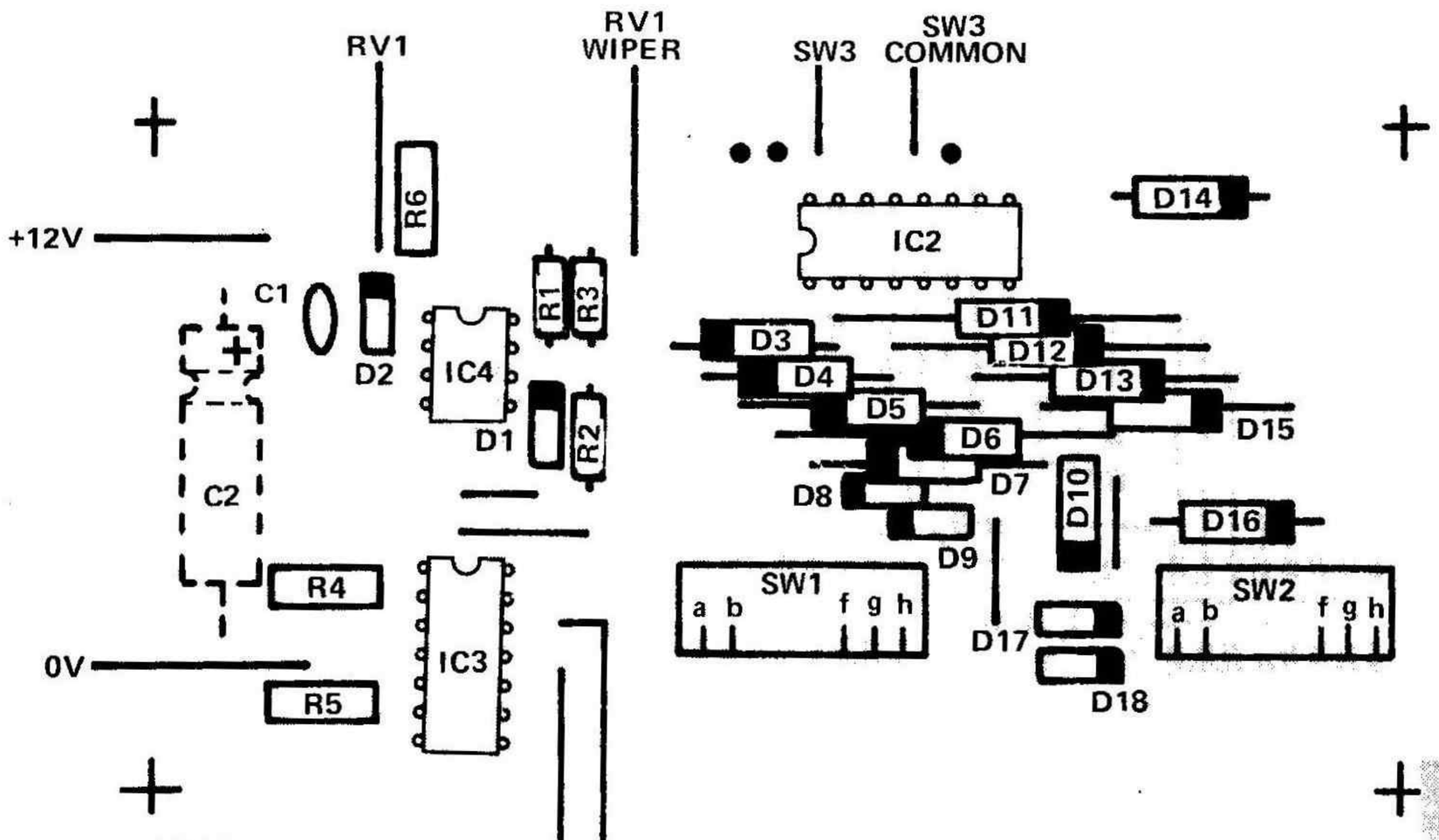


Fig.4 Component overlay for the sequencer board. Note that C2 is soldered underneath the PCB, and an insulated link should be soldered between IC2 pin 8 and the 0 V rail.

Below left: with the case open you can see how the boards and controls are interwired. The sequencer board (below) is secured to the top of the case by pressing the empty sockets onto the pins of the DIL switches.

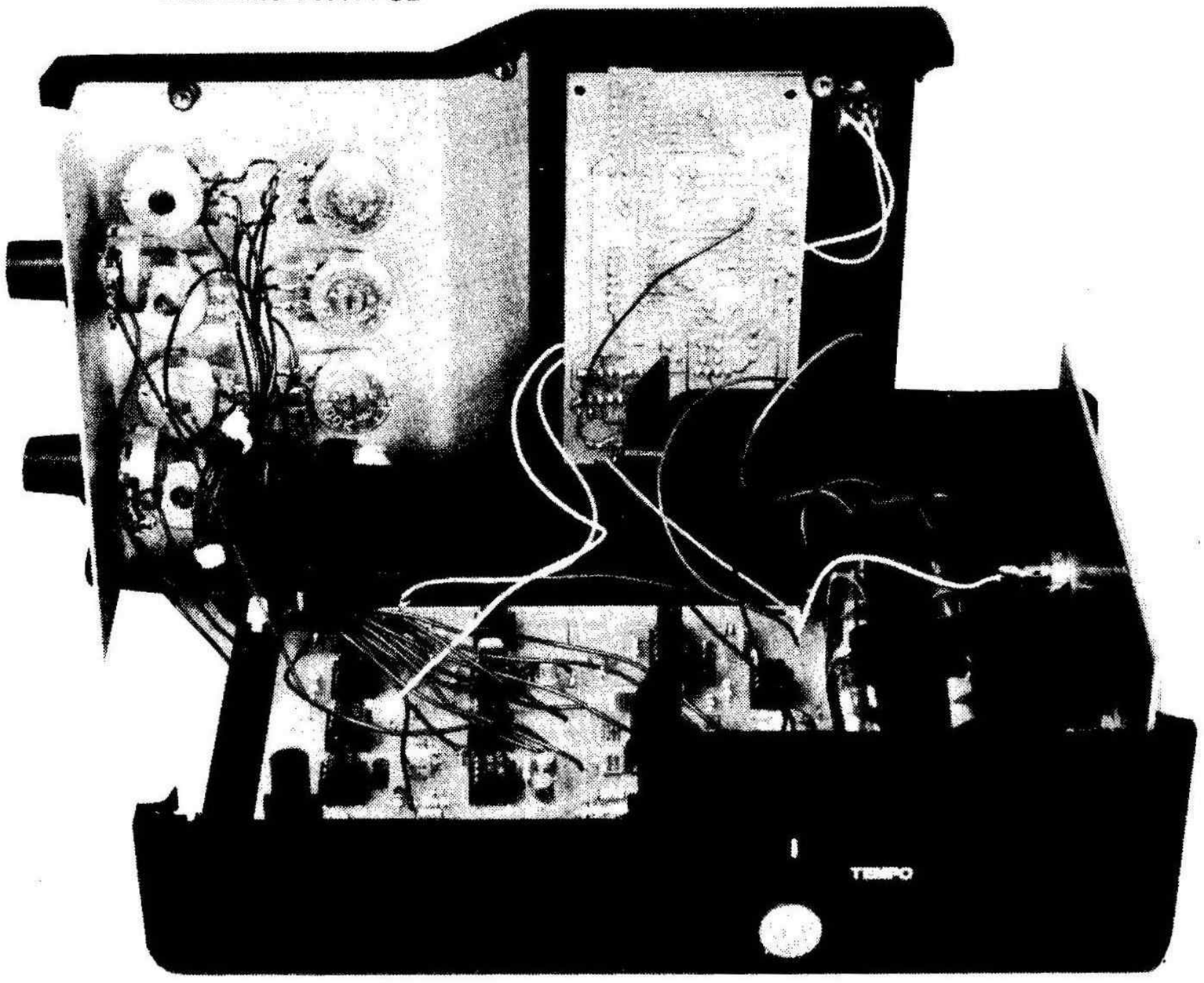

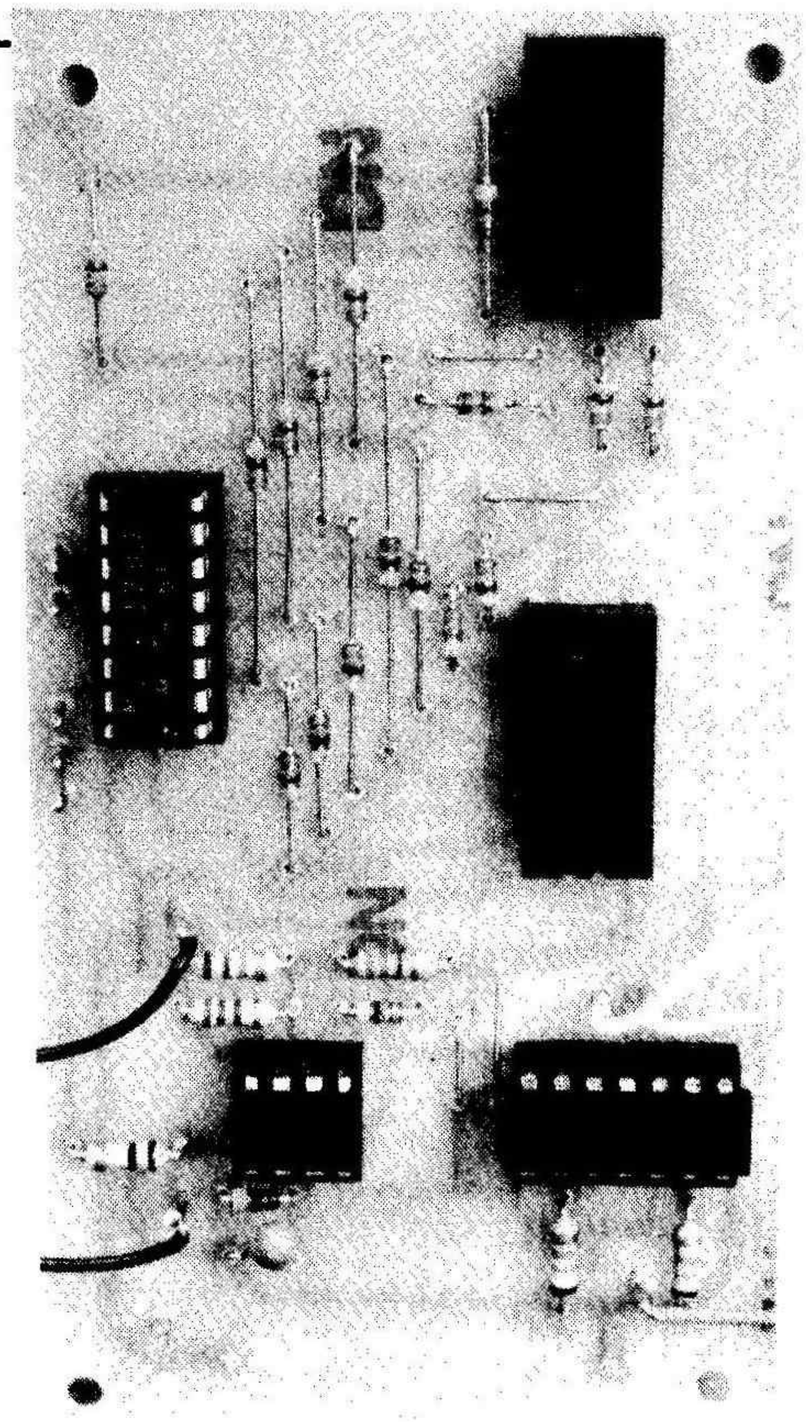

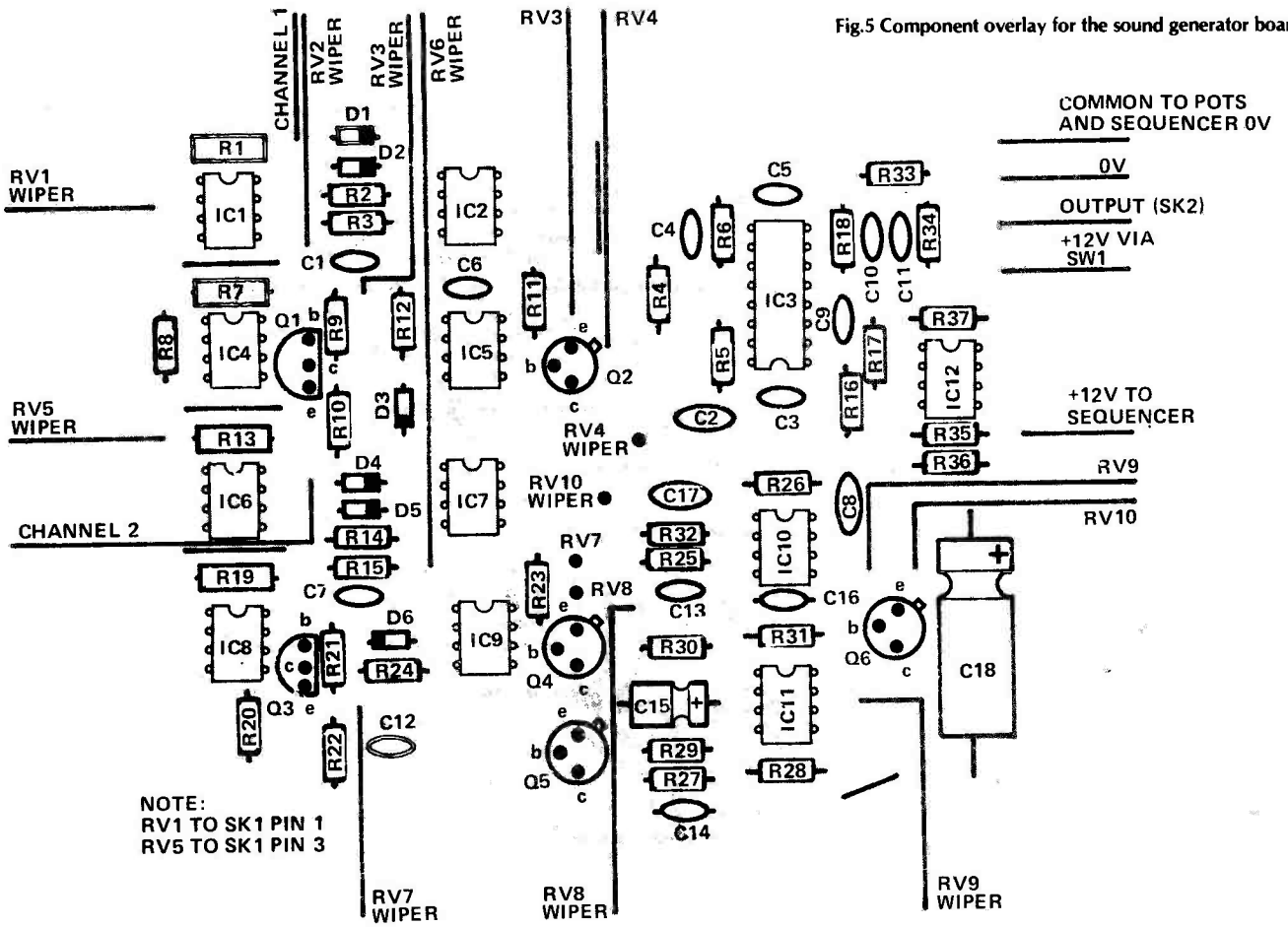


Fig.5 Component overlay for the sound generator board.

PARTS LIST

CONTROL CIRCUIT

Resistors (all ¼W, 5%)

R1,13,25,26,31	1M0
R2,12,14,24	4k7
R3,15	33k
R4,7,16,19,27,33,34,37	100k
R5,17	22k
R6,18,35,36	47k
R8,20	6k8
R9,21	1k0
R10,22	680R
R11,23	2k2
R28,32	10k
R29,30	56k

Potentiometers

RV1,4,5,8,10	47k linear
RV2,6	2M2 linear
RV3,7	100k linear
RV9	220k linear

Capacitors

C1,3,5,6,7,9,11,12,13	100n ceramic
C2,8,14,17	220n polycarbonate
C4,10	33p ceramic
C15	10u 25 V axial electrolytic
C16	10n ceramic
C18	1000u 16 V axial electrolytic

Semiconductors

IC1,2,4,6,7,8	CA3140
IC3	NE570N
IC5,9	7555
IC10,11,12	741
Q1,3	BC214L
Q2,4,5,6	BC109

Miscellaneous

SW1	SPST miniature toggle
SK1	3 pin DIN socket and plug
SK2	phono socket
LS1,2	50 mm loudspeaker

10 off collet knobs, caps and nut covers
Case (see Buylines)
2 off HP7- four section battery holders
8 off HP7 batteries

SEQUENCER

Resistors (all ¼W, 5%)

R1	2k2
R2	3k3
R3	22k
R4,5	27k
R6	100k

Potentiometers

RV1	220k linear

Capacitors

C1	2u2 35 V tantalum
C2	470u 25 V axial electrolytic

Semiconductors

IC1	555
IC2	4017B
IC3	4011B
D1-D18	1N4148


Miscellaneous

SW1,2	8-SPST dual-in-line lateral switches
SW3	SPST miniature toggle
PB1	momentary push button

1 off collet knob, cap and nut cover

SAFGAN DT-400 SERIES

DUAL TRACE OSCILLOSCOPES
NEW BRITISH PRODUCTS
FROM £169+VAT

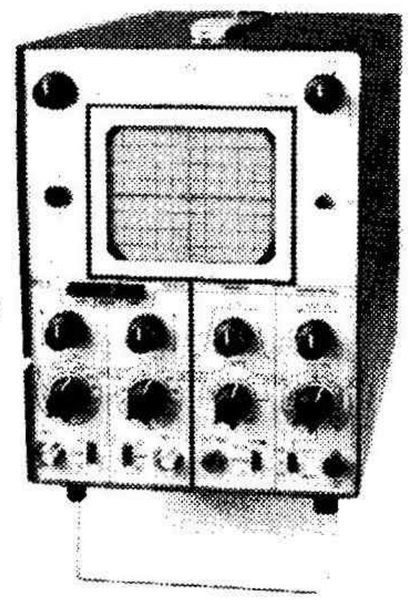
DT-400 SERIES

ALL MODELS

- DUAL TRACE
- 5mv/div
- 4'' CRT

MODELS

DT-410 10MHz £169+VAT
DT-412 12MHz £175+VAT
DT-415 15MHz £188+VAT

SPECIFICATION FOR ALL MODELS

- ★ CH1, CH2; 5mv div – 20V/div in 12 cal steps.
- ★ Bandwidth: 10MHz (DT-410), 12MHz (DT-412), 15MHz (DT-415).
- ★ Time Base; 0.5µs div – 200ms/div in 18 cal steps.
  x 5 expansion to 100ns/div.
  x 5 multiplier to 1s/div.
- ★ XY facility: matched x = CH1, Y=CH2.
- ★ Trigger: Level Control, ± slope selection.
- ★ Bright Line Auto, Normal, TV Triggering.
- ★ CH1, CH2 0.5div; 100mv External Source.
- ★ Z modulation.
- ★ CAL o/p for probe compensation.
- ★ Graticule blue ruled 8x10div (6.4x8 cm^2).
- ★ Size: H 215mm, W 165mm, D 280mm, Weight 4.5kg.

PROBE (X1 – REF – X10) £11.50+VAT

ORDERS TO SAFGAN ELECTRONICS LTD.
56 BISHOPS WOOD, ST. JOHN'S, WOKING
SURREY GU21 3QB. Tel: Woking
69560 or Woking 66836

GOODS + p&p £3.50 or parcel service £6.50 + 15%
LONDON STOCKIST: AUDIO ELECTRONICS. TEL: 01-724 3564
DT400s are designed and manufactured by SAFGAN in England

Lowest Prices Yet!

Memory Chips

Guaranteed quality – Any faulty chips should be returned to us within 12 months of purchase with proof of purchase for replacement by return of post.

4116 and 2114 chips at the same price

4116 dynamic memory chips guaranteed to 200 nanoseconds full cycle time. Suitable for Apple, TRS 80, Nascom, Exidy Sorceror, Sharp MZ 80K etc (8 chips give 16k bytes of memory).

2114 static memory chips guaranteed to 300 nanoseconds full cycle time. Low power, suitable for Superboard Compukit, Atom, ZX 80 etc. (2 chips give 1K byte of memory).

Prices No. of Chips	Unit Price	Total Price Nett	Vat	Total
2	1.80	3.60	.54	4.14
8	1.70	13.60	2.04	15.64
24	1.60	38.40	5.76	44.16
100	1.40	140.00	21.00	161.00
500	1.30	650.00	97.50	747.50
1000	1.25	1250.00	187.50	1437.50

Official orders welcome. Post and Packing free.
24 Hr Telephone Credit Card Orders 051-236 0707

Mail orders to:
MICRODIGITAL LIMITED
FREEPOST (No stamp required)
LIVERPOOL L2 2AB

A LASKYS COMPANY

Retail Premises at:
25 BRUNSWICK STREET,
LIVERPOOL L2 0PJ.
Tel: 051-227 2535/6/7

MICRODIGITAL

A NEW ADVENTURE IN COOKING!
COMPONENTS AND CHIPS FROM DISPLAY ELECTRONICS

Fast Service — Low Prices — Great Menu

COMPUTER GRADE HIGH RIPPLE CAPS

MF	Volts	Dim mm	Price	pp
1500*	100	80 · 35	70p	
2200	40	50 · 25	150p	
3300	25	50 · 25	150p	
3300*	63	115 · 35	80p	
3300*	150	100 · 65	120p	
4700	75	115 · 35	190p	
11000	25	68 · 50	180p	
15000	16	80 · 35	180p	
15000	40	115 · 35	190p	
22000	16	80 · 50	220p	
22000	25	115 · 35	250p	
28000	25	105 · 70	270p	80p
34000	50	145 · 75	350p	80p
64000	40	115 · 75	590p	80p
68000	16	115 × 60	575p	80p
138,000	10	145 × 75	600p	80p
160,000	30	220 × 75	750p	120p

ALL TYPES HAVE SCREW TERMINALS.
*EX-EQUIPMENT, TESTED

P.C.B. EDGE CONNECTORS

Pitch	Ways	*	Price
0.1"	17	AC	60p
0.1"	36	BD	190p
0.1"	45	BC	245p
0.1"	54	AC	110p
0.1"	85	AC	200p
0.1"	85	BC	400p
0.15"	12	AC	75p
0.15"	25	BC	120p
0.15"	56	BC	325p
0.156"	12	PET	150p
0.156"	28	BC	190p
0.156"	36	BC	200p

*A SINGLE SIDED B DOUBLE SIDED
C SOLD TAG D WIRE WRAP
ALL GOLD PLATED EASILY CUT TO SIZE

VOLTAGE REGULATORS

Type	V	A	Case	Price
LM309K	5	1 2	TO3	110p
LM323K	5	3 0	TO3	599p
7805	5	1 0	TO220	50p
7815	5	1 2	TO3	110p
LM723	VAR	–	DIL	35p

TTL ICs

Type	N	LS	S
7400	10p	15p	25p
7401	12p	–	–
7402	12p	15p	14p
7403	14p	–	16p
7404	14p	15p	–
7405	18p	–	–
7406	32p	–	–
7407	32p	–	–
7408	17p	22p	–
7409	22p	–	–
7410	15p	19p	–
7411	–	38p	–
7413	30p	–	–
7414	50p	–	–
7416	27p	–	–
7417	28p	–	–
7420	17p	19p	18p
7423	30p	–	–
7427	34p	–	–
7428	35p	–	–
7430	17p	20p	–
7432	28p	30p	–
7437	35p	–	–
7438	30p	35p	–
7439	30p	–	–
7440	17p	19p	–
7441	65p	–	–
7442	55p	–	–
7445	120p	–	–
7447	45p	–	–
7450	17p	–	–
7451	–	22p	–
7454	17p	23p	–
7470	33p	–	–
7472	28p	–	–
7473	34p	–	–
7474	28p	32p	36p
7475	28p	–	–
7476	35p	–	–
7485	90p	–	–
7486	34p	35p	–
7489	200p	–	–
7490	28p	–	–
7492	50p	–	–
7493	28p	–	–
7495	65p	–	–
7496	60p	–	–
7497	175p	–	–
74100	130p	–	–
74104	45p	–	–

Type	N	LS	S
74107	32p	–	–
74109	50p	–	–
74111	50p	–	–
74112	–	–	90p
74114	–	–	45p
74116	195p	–	–
74118	75p	–	–
74121	28p	–	–
74122	41p	–	–
74123	45p	60p	–
74125	53p	–	–
74128	72p	–	–
74132	68p	–	–
74133	–	25p	–
74147	180p	–	–
74148	103p	–	–
74150	98p	–	–
74151	60p	100p	–
74153	65p	–	–
74154	98p	–	–
74155	60p	–	–
74157	60p	65p	–
74161	90p	–	–
74163	80p	–	–
74164	120p	110p	–
74166	120p	–	–
74170	235p	–	–
74172	445p	–	–
74173	110p	–	–
74174	85p	–	–
74175	80p	100p	–
74180	92p	–	–
74181	150p	–	–
74182	–	90p	–
74190	85p	–	–
74191	85p	–	–
74193	85p	95p	–
74194	85p	–	–
74197	75p	–	–
74198	140p	–	–
74241	150p	–	–
74266	–	95p	–
74273	265p	–	–
74279	80p	–	–
74283	155p	–	–
74284	400p	–	–
74285	400p	–	–
74298	180p	–	–
74366	95p	–	–
74387	90p	–	–
74390	–	140p	–
74393	195p	–	–

XTALS

Frequency	Case	Price
19.20 KHz	HC6U	300p
38.40 KHz	HC6U	400p
100.00 KHz	HC6U	300p
110.00 KHz	B7G	400p
1.00 MHz	HC6U	320p
2.00 MHz	HC6U	280p
4.00 MHz	HC18	280p
5.00 MHz	HC18	280p
6.00 MHz	HC18	280p
8.00 MHz	HC18	280p
10.00 MHz	HC18	280p
10.25 MHz	HC18	280p
11.20 MHz	HC18	280p
20.00 MHz	HC18	280p

DIL XTAL OSC 9.600 MHz 450p
5000 XTALS EX – STOCK
PHONE YOUR FREQUENCY

LINEAR

CA3011	60p
CA3028B	100p
CA3046	85p
GE424	110p
LM301	30p
LM324N	40p
LM3900	60p
MC1408L8	400p
MC1458R	45p
NE555	25p
NE556	60p
NE567	165p
TBA673	225p
TLO82	85p
741	15p

BRIDGE RECTIFIERS

A	V	Price
1.5	50	30p
1.5	200	50p
2.5	75	40p
5	100	60p
10	100	150p
12	400	190p

'D' RANGE CONNECTORS

Ways	Plug	Sock
9	103p	126p
15	117p	201p
25	172p	258p
37	235p	414p
50	290p	546p

25 WAY RIGHT ANGLE P.C.B PLUG 255p, SOCK 295p

RAMS

1103		50p
2101-4		410p
*2114L-3	300NS	350p
4006-4		95p
4027	375NS	350p
*4116	200NS	200p
5101L	450NS	495p
TMS3114 SH REG		140p
*4116 8 for		1995p
*2114 8 for		2250p

EPROMS

1702	375p
2708	495p
2716 5v	950p
! 2716 3 rail	850p

I.C. SOCKETS

Pins	Prices		
8	10p	28	30p
14	14p	40	44p
16	16p	Wire Wrap	
18	18p	14	30p
20	20p	16	38p
24	25p	24	40p

MPU DEVICES

4004	250p
8085A	999p
8155C	895p
8251	350p
8253	695p
8255	995p
8259A	475p
8755A	2400p
2652	2200p
6850P	375p
6011	400p
AY-5-1013	400p

TRANSISTORS

2N697	22p	AD162	40p	BC251A	15p
2N689	35p	BC108	10p	BC252	16p
2N706A	25p	BC109	10p	BC327	13p
2N1136A	25p	BC147	7p	BC337	13p
2N2646	45p	BC148	7p	BC338	14p
2N2904	23p	BC149	7p	BC348	15p
2N2906	23p	BC157	8p	BC547	12p
2N2926	7p	BC159	10p	BC548	8p
2N3053	25p	BC167	10p	BC549	9p
2N3055H	60p	BC170	10p	BCY33A	120p
2N3440	60p	BC170A	11p	BD242C	80p
2N3442	120p	BC170C	12p	BF258	35p
2N3702	8p	BC171	10p	BFT60	28p
2N3703	8p	BC171A	11p	BFW22	20p
2N3704	8p	BC172A	10p	BFY50	28p
2N3771	150p	BC172B	10p	MJ1000	95p
2N3906	15p	BC172C	10p	MJ4030	225p
2N4304	20p	BC172	10p	MPU131	25p
2N4351	50p	BC173C	10p	TIP29	40p
2N4352	50p	BC174B	10p	TIP29A	30p
2N5447	10p	BC182L	10p	TIP30A	42p
2N5449	12p	BC207B	15p	TIP31	26p
2N5943	55p	BC212L	8p	ZTX108	8p
2N6385	125p	BC213A	8p	ZTX314	20p
ACY19	75p	BC250A	12p		
AD161	40p	BC251	14p		

SPECIAL OFFERS

4116	2200 NS RAMS 8 for £19.95
2114L-3	300 NS RAMS 8 for £22.50
2102L-3	650 NS RAMS 8 for £5.50
40305L	300 NS RAMS 8 for £9.95

BULK ENQUIRIES MOST WELCOME

Electronic Components and Equipment purchased for cash

Buy it with Access — BARCLAYCARD VISA

DISPLAY ELECTRONICS 64-66 Melfort Road
Thornton Heath, Croydon, Surrey CR4 7RN
Telephone Orders: 01-689 7702/01-689 6800

Please add 50p Post and Packing

All Prices Include VAT

Bona Fide Account Orders Minimum £10.00 | Warehouse Open 10-5.30 Mon-Sat | 1,000's of Other Items

TEKTRONIX STORAGE OSCILLOSCOPE. Type 434, as new. 12 months' warranty **£1,950.**
TEKTRONIX OSCILLOSCOPE. Type 647, with 10A2 and 3B11. **£500**
TEKTRONIX STORAGE OSCILLOSCOPE. Type 564 with 3A6 and 3B4 **£360.**
TELEQUIPMENT STORAGE OSCILLOSCOPE. Type DM53A **£285.**
TELEQUIPMENT OSCILLOSCOPE. Type D32. Portable, mains/battery. **£275.**
HAMEG OSCILLOSCOPE. Type 512 DB, 50MHZ. **£350.**
TELEQUIPMENT OSCILLOSCOPE. Type S54A SB 10MHZ. **£190.**
SE LABS OSCILLOSCOPE. Type SM111 DB 20MHZ. **£325.**
ADVANCE OSCILLOSCOPE. Type OS1000 DB 15MHZ. **£250.**
TEKTRONIX OSCILLOSCOPE 547 with 1A1 plug-in Dual TB. 50MHZ. **£375.**
TEKTRONIX OSCILLOSCOPE. Type 561A with 3A1 and 2B67 10MHZ. **£300.**
TEKTRONIX OSCILLOSCOPE. Type 533A with CA. DB 24MHZ. **£140.**
HEWLETT PACKARD AC CONVERTOR. Type 3461A **£120.**
MARCONI FM SIG. GEN. Type TF1066B/6S. **£295.**
G. & E. BRADLEY LTD. R.F. MILLIVOLTMETER. Type 112 **£75**
ADVANCE A.C. VOLTMETER. Type VM77E **£80**
MARCONI WAVE ANALYSER. TF2330. Good condition. **£150**
AVO R.F. SIG. GEN. Model HF135. **£75**
MARCONI WIDE RANGE R.C. OSCILLATOR. TF1370. **£95.**
MARCONI AM/FM SIG. GEN. Type TF1066/1. **£225.**
MARCONI SENSITIVE VALVE VOLTMETER. TF2600. **£50.**
MARCONI SIG. GEN. MK2. TF995A/3/S (CT402) **£275.**
TEKTRONIX type 1L30 SPECTRUM ANALYSER PLUG-IN. (works, slight corrosion) **£325**
AIRMEC SIGNAL GENERATOR. Type 204 AM/FM 320MHZ **£150**
WAYNE KERR UNIVERSAL BRIDGE. Type B221 **£50**
ADVANCE R.F. Signal Generator E2 100KHZ-100MHZ **£40**
ADVANCE VHF MILLIVOLTMETER VM70 (No probe) **£50**
ADVANCE SIGNAL GENERATOR type B4B7 30KHZ-30MHZ **£25**
COSSOR NOISE LEVEL METER CT454 (Ex-Ministry) **£18**
S.T.C. ATTENUATOR 0-100DB 600ohm **£9**
S.T.C. ATTENUATOR 0-100DB 75 ohm **£6**
AVO VALVE CHARACTERISTIC METER £20
E.H.T. UNIT 230V 50cs 25VA 7.5V **£22.50**
BRANDENBURG HIGH VOLTAGE GENERATORS 10KV **£60**
BRANDENBURG HIGH VOLTAGE GENERATORS 30KV **£60**
VARIACS Ex-equipment. Good condition 8 amp **£25**
VARIACS Ex-equipment. Good condition 20 amp **£35**
CRC GENERATOR TBFG8660. Sine/square/Triangle. Very good **£60**
B&K AUTOMATIC VIBRATION EXCITER CONTROL. Type 1018 **£50**
B&K AUTOMATIC VIBRATION EXCITER CONTROL. Type 1019 **£50**
MARCONI UNIVERSAL BRIDGE. Type TF868B **£100**
SOLARTRON TRUE RMS VOLTMETER. Type VM1484 **£75**
TAYLOR VALVE TESTER. Type 450 **£65**
ADVANCE LF OSCILLATOR. Type H1E **£45**
ADVANCE SIGNAL GENERATOR S62B 150KHZ-220MHZ **£60**
MARCONI UNIVERSAL BRIDGE. Type TF868A **£50**
TAYLOR METER MODEL 128. £15
R&S SELEKTOMAT USWV BN 15221/2 **£100**
B&K LEVEL RECORDER. Type 2304 **£50**
RACAL HF SELECTIVE ANALYSER. Type 9056. **£375**
SCHLUMBERGER AUTO COUNTER. Type FB2602. **£150**
MARCONI F.E.T. MULTIMETER. Type TF2650 (new) **£95**
LEVELL MULTIMETER. Type TM11 **£50**
ICE MULTIMETER SUPERTESTER 680R £18
MARCONI SIGNAL GENERATOR. Type TF144H. **£225**
MARCONI SIGNAL GENERATOR. Type TF801D/1/S. **£195**
MARCONI UNIVERSAL BRIDGE. Type TF1313. **£250**
RACAL SIGNAL GENERATOR. Type 365A, 1 to 320MHZ AM/FM. **£175**
R&S Z-g DIAGRAPH BN3582 300-2400MHZ £85
R&S POLYSKOP 1 SWOB BN 4244/2/50 £350
WAYNE KERR COMPONENT BRIDGE. CT375 (B521) **£75**

R&S UNBALANCED STANDARD ATTENUATOR 500HM. BN18942/50 **£45**
STODDART AIRCRAFT Radio Interference and Field Intensity Meter, type NM-52A 375-100DMHZ (2 pieces) **£325**
MARCONI SIGNAL GENERATOR. Type TF801B **£85**
R&S DIRECT CAPACITANCE METER £50
B&K HETERODYNE VOLTMETER (RECEIVER) Type 2005 **£250**
MARCONI VARIABLE ATTENUATOR. TF1073A/2S **£40**
MARCONI DOUBLE PULSE GENERATOR. Type TF1400/S **£50**
RADIOMETER (COPENHAGEN) WAVE ANALYSER. Type FRA 2CT3a **£80**
SOLARTRON DIGITAL VOLTMETER. Type LM1B67 **£75**
HEWLETT PACKARD DIGITAL RECORDER. Type 5050B **£50**
HATFIELD PSOPHOMETER. Type DRG 657167A **£50**
ADVANCE DUAL STABILISED D.C. SUPPLY PP3. 0-30V 1A **£25**
PICTURE MONITOR MODEL PM-52T (5in screen) As new **£55**
HEWLETT PACKARD POWER SUPPLY 6214A. 0-12V; 0-1.2A, new, boxed. **£85.**
H.P. DC POWER SUPPLY 6209B. 0-320V, 0-0.1A, new boxed. **£140**
T.O.A. ELECTRONICS LTD Electronic Polyrecorder EPR-2T. Mains **£120**
THE JAMES KING COMPANY FS-1100T FREQUENCY STANDARD £50
MARCONI CARRIER DEVIATION METER. Type TF891D **£50**
SOLARTRON PULSE GENERATOR. Type GO1101.2 **£40**
MI SANDERS LEVELLING AMPLIFIER. Type 6587 **£175**
SCOPEX OSCILLOSCOPE. Type 4D10 DB 10MHZ **£170**
ADVANCE OSCILLOSCOPE. Type OS240 DB 10MHZ **£175**
COSSOR OSCILLOSCOPE. Type CDU150 DB 35MHZ **£225**
TELEQUIPMENT OSCILLOSCOPE. Type D61 DB 10MHZ **£195**
HEWLETT PACKARD OSCILLOSCOPE. Type 120B X-Y. **From £85**
FLUKE DIFFERENTIAL AC/DC VOLTMETER. Model B32A **£60**
ADVANCE AUDIO SIGNAL GENERATOR. Type H1, Sine/Square **£25**
R & S TUNABLE INDICATING AMP. BN 12121/2 45-600MHZ **£100**
MUIRHEAD WAVE ANALYSER 30-31HZ **£60**
HEWLETT PACKARD DIGITAL VOLTMETER. Type 3460B **£75**
WAYNE KERR THERMOMETER. Type LT100 with probe. **£50**
HATFIELD RADIO FREQUENCY BRIDGE. Type LE300A/1. **£50**
SOLARTRON OSCILLOSCOPE. Type CD1400. DB 15MHZ. **From £75**
HAMEG OSCILLOSCOPE. Type HM412. **£250**
KNIGHT RF SIG. GEN. KG686 with Sweep Marker Gen. KG687. **The Pair £100.**
H.P. MEMORY DISPLAY 5480B with 5486A Control TB and 5488A Y System. **£275**
H.P. MEMORY DISPLAY 5480A with 5486A Control TB and 5485A two channel input. **£225.**
R&S UHF TEST RECEIVER 0.9-2.7GHZ. BN1524 **£150**
EDDYSTONE RECEIVER. Type 990S 250-850MHZ. **£450**
R&S UHF TEST RECEIVER. BN1523 280-940 MHZ **£120**
KEITHLEY REGULATED HIGH VOLTAGE SUPPLY. Type 241. **£250**
HEWLETT PACKARD D.C. CURRENT SOURCE. Type 6181B **£175**
MARCONI XY MEMORY Type TK2214. **£140**
R&S UHF SIGNAL GENERATOR. BN41022 300-1000MHZ **£80**
GPO DATEL TESTER NO IC. £100
LEVELL BROADBAND VOLTMETER. Type TM6B. **£40.**
DAWE AF ANALYSER. Type 1461A. **£30**
R&S UHF/VHF FREQUENCY METER. BN442 30-3000MHZ. **£60**
R&S UHF MILLIVOLTMETER. BN1091. **£70**
GERROLD SWEEP FREQUENCY GENERATOR. Model 602. **£40**
TELONIC SWEEP GENERATOR. Type SD-3 450-900 MHZ. **£75.**
H.P. VHF SIGNAL GENERATOR. Type 608D. Case damaged hence **£50**
MARCONI VALVE VOLTMETER. Type TF1300. **£15**
SOLARTRON DIGITAL VOLTMETER. Type LM1420.2. **£30**
VIDEO CIRCUITS LTD TUBE TESTER. Type V33. **£30**
LABGEAR COLOURMATCH 625 PATTERN GENERATOR. Type CM6004-PG. **£30**
B & K BEAT FREQUENCY OSCILLATOR. Type 1014. **£175**
ADVANCE OSCILLOSCOPE. Type OS1000A. DB 20MHZ. **£300**
PLEASE CHECK AVAILABILITY BEFORE ORDERING.

FERRET A.T.E.
£650
Phone for details

EDDYSTONE RECEIVERS
Model 770R-AM/FM
£95 each
Model 770R Mk II
£150 each

INFRA RED IMAGE CONVERTER Type 9606 (CV 144)
1¾in diameter. Requires single low current 3KV to 6KV supply individually boxed. With data.
£12.50 each
Infra Red Lamps also advertised

VARIAN RUBIDIUM STANDARD
Model R20
5mhz, 1mhz, 0.1mhz
£600

EX-MINISTRY SOLID STATE 400 HZ INVERTOR
28 VDC input, 115V output. Size 7 x 2½ x 15in approx. Connection details supplied.
£18 each. P&P £2

TRANSISTOR INVERTOR
115V AC 1.7 Amp Input. Switching is at 20Khz. Output windings from Pot Core. Can be rewound to suit own purpose or unit can be broken for host of components. Circuits supplied.
£1.25 each. P&P £2.

CONVERT THIS UNIT TO A
SUPER BATTERY CHARGER
Attractive green ministry quality case with removable top and bottom plates — heavy duty power switches, high powered resistors to control current, good quality centre mounted amp meter, strip of wing nut terminals on front panel which can be used for connecting leads. All this for **£3.50.** P&P £2. Four units £12. Carriage £5.

STEPPING MOTORS
6/12 position with additional where the rotor is coils. Device can be used as a tacho. Diagram supplied. Will actually work on 5 volts. 12/24 recommended.
£1.50 each P&P 75p
or 5 for **£5** P&P £1.50.

STEPPING MOTORS
200 Steps. 20 oz/in. torque, 12/24 volt input 4-wire.
£12 each. P&P £1.50

KEYBOARD PAD
Size 3x2½x2" high with 12 Alma Reed Switches. Blue keys marked in green 0-9 and a star with one blank.
£4 each, P&P £1, or 5 for **£15** P&P £2.

MINIATURE KEYBOARD
Push contacts, marked 0-9 and A-F and 3 optional function keys. **£1.75 each.**

SOME TEKTRONIX 500 RANGE OSCILLOSCOPES
with Single Trace Plug-ins. Working.
From £100. Phone for details

DIODES
All new full spec. devices IN3063 BAX 13, 1S44, 1N4148; 1N3470; 1N4151.
100 off **£1.50,** 1,000 off **£10**

CRYSTALS Flat metal case — 19.2KHZ, 844.8KHZ, 87G — 10MHZ. **50p each.**

LOUDHAILERS. Transistorised hand-held, no leads. Standard internal batteries supplied. Howl Switch **£20 ea.** P&P £2
INFRA RED QUARTZ LAMPS. 230V 620 Watts. Size 13½" × ⅛" dia. **£1.50 ea.** 240V 1650 Watts. Size 22¼" x ½" dia. **£3 ea.**
BRIDGE RECTIFIER. 2 Amp **50p ea.**
PHOTODIODE DETECTOR 4" fly leads, **25p ea.**
AMPHENOL. 17-way chassis mount edge connectors 0.1 spacing, **15p ea.**
I.E.C. Standard **MAINS LEAD.** Moulded (3 vertical flat pins centre offset) **60p ea.**
FANS. 115V 13 Watts. Size 3¼ × 3¼ × 1½" BRAND NEW **£4.50 ea.** Secondhand **£2.50 ea.**
DELAY LINE. 50 nanosecs. 3 connections — ground-in-out Size 2 × 7/16 × 5/16" New **25p ea.**
MOTOR 12V DC with pulley and integral semiconductor Speed Control. New **£1 ea.**
LEDEX ROTARY SOLENOIDS. 115V DC. No switch assembly. **15p ea.**
DIAMOND H CONTROLS ROTARY SWITCH. Single pole 10-way. Printed Circuit Mount. New **10p ea.** 100 for **£7.50**
PULSE TRANSFORMER. Sub min. Size ½ × 5/16 × ¼" Secondary centre tapped. New **20p ea.**
REMO TV TYPE MULTIPLIER. Two high voltage outputs and focus, **£1 each.**
DON'T TAKE CHANCES. Use the proper EHT CABLE, **10p per metre** or **£7.50 per 100 metre/drum.** P&P £2.
PHOTOGRAPHIC LAMPS. Pearl 230V 500 watt. Screw cap **75p ea.** Box of 12 **£5.50.** P&P £1.50.
RAPID DISCHARGE capacitors 8mfd 4kV **£5 each.** P&P £2
MYSTERY IC PACK. Some 40 pin — good mixture — all new devices. **25 ICs for £1.** P&P 50p.
DECOUPLING CAPACITORS
0.05mfd 10V; 0.01mfd; 0.047mfd 250V; 33K, 330pf. All values 400 for **£1.50.**
E.H.T. Capacitor 500pf 8KV 20p each.
10-way MULTI COLOUR RIBBON CABLE. New 40p per metre. 10 metres for £3.
GEC UHF 4-button tuner **£1.50 each.**
CENTAUR 115V FANS 4½ × 4 × 1½" **£4.50 ea.**
EX-USED equipment, tested, **60p each.**
CONTACTORS. Heavy Duty 24V DC 5 make **£1 each.**
GEC UHF/VHF 6-button tuner **£2 each.**
931A PHOTO MULTIPLIER £2 each. P&P £1.
RANCO 250V 18A THERMOSTATS with Control knobs calibrated 50-200 degree C **£2.50 each.**
SOLID STATE UHF TUNERS. 30 acs **£1 each.**
BRAND REX blue wire wraps. 30 metres for **£1.** P&P 25p
SLIDER CONTROL 500K Log. Single track. Complete with knob. Length 3½" **25p each.**
TRANSFORMERS
AUTO 240V input 115 V, 1 Amp output **£1.25 each.** P&P £1.25
240V input. Soc. 6V 1.86A Size 2½ × 2 × 2". Good quality **£1.50 ea.** P&P £1.
240V input Boc. 12V 0.92A. Size 2½ × 2 × 2". Good quality, **£1.50 ea.** P&P £1.
240V input 12V 100MA. Size 60 × 40 × 42mm. **50p each.**
240V input. Soc. 12-0-12V 50MA. Size 53 × 45 × 40mm. **£1 ea.**
115V input. Soc. 5V 250MA. Size 1 11/6 × 1.5 × 1¼". **2 for 50p.**
115V input. Sec 10-0-10V1A. Size 2½ × 2 × 2". 2 for **£1.50.**
SEMICONDUCTORS
1N4005 — **5p;** 1N4002 — **3p.**
At 5p each:
BC147, BC148B, BC157, BC158, BC237, BF197, OA90, OA81, BA154, BA243.
At 25p each:
TIP31, TIP41A, 2N5296, AF139, 2TX341.
BY127 **10p.** BF181 **20p;** BD239 **49p;** BD241 **40p;** MA343AT **49p;** BD228 **50p;** BD233 & BD234 Comp Pair 25W — **80p per pr. at 50p each.**
REGULATOR TBA625 8to 20V in — 5V out 100MA TO5 Con **50p each** BF256C **20p.**
TV AMPLIFIER TBA 120 **20p each.**

Integrated Circuits

7453	5p	74H74	12p	75325	£1
7451	5p	74H51	7p	SN15862	4p
7402	12p	74538	10p	MC4028	69p
7476	20p	74502	12p	7417	14p
7495	35p	74154	70p	7441	40p
74122	12p	74C02	16p	74C86	50p
74C00	17p	74C04	18p	74C161	24p
		74C74	18p		

MOTOROLA DUAL in Line 6 pin Opto Coupler **30p each.** Gold plate tester version **50p each.**
EPROMS 2708 **£5.50 each.**
SMITHS encapsulated transistorised AUDIBLE WARNING DEVICES 4V-12V. Can be driven from TTL **65p each.**
ELECTROSTATIC VOLTMETER. 7.5KV **£8 ea.** P&P £1.50
Other ranges available — please enquire.
TRIMMERS. Sub min. 0.25 to 1.25 pf. 1 to 4.5 pf. 7 to 45 pf. **All at 5p each.**
HONEYWELL humidity controllers **50p each.**
THYRISTOR TIMER. Solid State. 15 secs adjustable (reset) in plastic relay case. Standard 7-pin base. Series delay **50p each.**
MINIATURE PC MOUNT SLIDE SWITCH. 2 pole 2 way **10p each.**
4 DIGIT 7 SEGMENT per digit plus a figure one to the left plus a centre minus sign to the left of the figure one with decimal places between digits. Good brilliance at 1.5V. 15 connections **£2.50 each.** Some E.H.T. Transformers and Capacigx available. Please enquire.
TELEPHONES 706 style black; grey or blue **£8.50 ea;** 746 style black or grey **£7.50.** Older style black **£2.50 each.** Discoloured grey 706 **£4 ea** P&P £1.50 per telephone.
DC SERVO MOTOR 110V 2.5Amp continuous. Double shaft. Brand new. 4 wire, 4 brush **£25 ea.** Plus carriage.
PC Mount POTS. Wire wound with knob 200 ohm & 10ohm. **10p ea.**
MIN. RELAY 24V. 2 pole c/o. Brand new. **75p each.**
TIME DELAY RELAY 0.1 to 10 secs, 115V AC. DPDT. **£5 each.**
CAPACITORS at **5p each.** 0.1uf 400V. Small rec. block PC Mount German class; 3300pf, 220nf250V; 0.01mfd 160V.
INSERT can be used as Microphone/Earpiece (Like used as insert in telephone but superior quality) Ex-Min. Brand new wrapped **75p** each, or 10 for **£6.**
TOROIDAL TRANSFORMERS. Input 0-120-240 Volts. Output 0-12V; 0-12V. 10VA per winding. Encapsulated — identical to R.S. Components at £8.90. OUR SPECIAL PRICE **£5 ea.** P&P £1.50.
TANTALUM CAPACITORS — All at 10p each — 100 off **£7.50.** 22mfd 6V; 39mfd 10V; 22mfd 35V; 1mfd 35V.
MINIATURE SLIDE SWITCHES. Single pole 2 way **10p** each, 10 off **90p**
HEAVY DUTY RHEOSTAT. 7.50hm 5.5Amp. Diameter 5". Standard ¼" shaft **£2.50 each.** P&P £1.50.

LARGE EX-MINISTRY SPEAKERS. OUTSIDE 15 ohm or 500 ohm. Tested. £25 each or 5 for £100


MINIMUM ORDER £3 VALUE OF GOODS. MINIMUM P&P £1.50 — where P&P not stated please use own discretion — excess refunded.
£5 CARRIAGE ON ALL UNITS. P&P or CARRIAGE and VAT at 15% on total MUST BE ADDED TO ALL ORDERS.
CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5pm Monday to Saturday inc.
BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome.

CHILTMEAD LTD

NORWOOD ROAD, READING **TELEPHONE NO. READING 669656**

(2nd turning left past Reading Technical College in King's Road then first right — look on right for door with "Spoked Wheel")

AUDIOPHILE

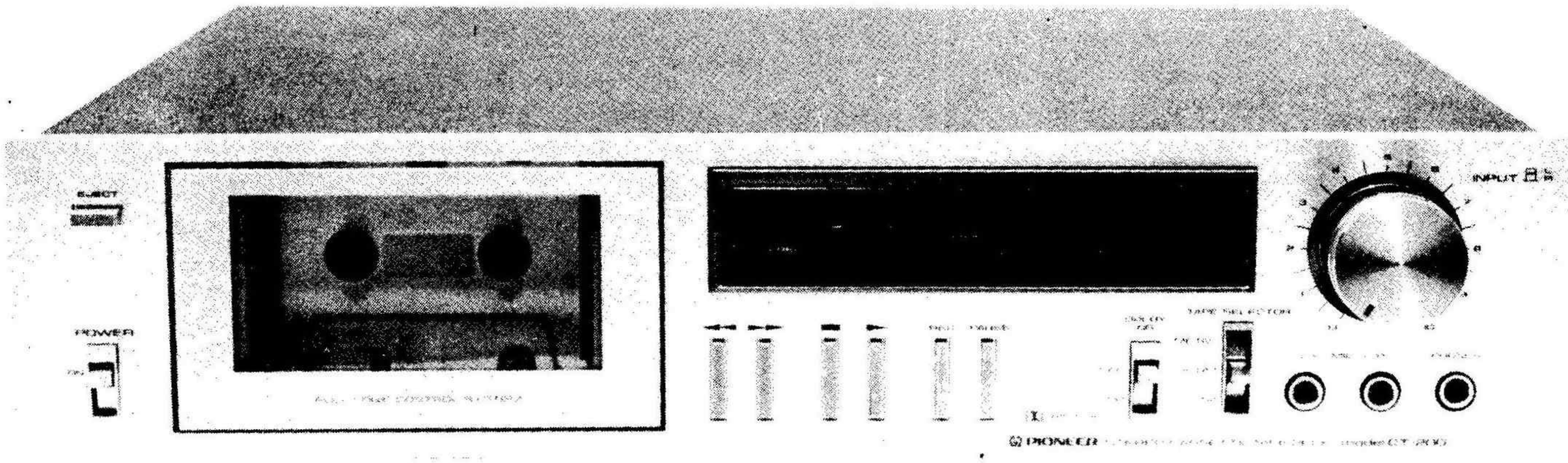

Yes, you read it right. . . Audiophile is back! Ron Harris takes pen in hand again to review a couple of Pioneer tape decks, and enthuses over some old friends.

Right. Put down the trannie radios, pack away the pine needles — Audiophile has returned! That man at the back with the yellow handbag who whispered "Oh gawd, not again" can leave now of his own accord, or be carried out later when the boys get round to landscape his anatomy.

To all my regulars who sorely missed these pages and who wept and wailed their grief to the dawn — thank you. To any tasteless cloth-eared ingrate who thinks I should have stayed away — read on, read on, there is yet hope and charity for such as ye in the halls of the righteous! (ie here. . .).

For my return trick, I'm taking a look at two tape machines from Pioneer's cassette deck range, one from each end: the CTF-1250, which is their flagship design, and the CT-200, an interesting new release at the budget end of the price scale. Thus we shall be all things to all men. . . I think.


Tape For All Seasons

The new CT-200 is a basic, no-nonsense machine intended mainly for the first time hi-fi man who doesn't wish to have to upgrade again in a hurry. It is compact and sports little in the way of excess controls. Normal VU meters are fitted, with no peak indicators. Logic control is employed for the tape transport mechanism and, strangely, Pioneer have opted for captive phono leads on the input/output connectors. Surely a yard of screened lead and a phono plug can't cost less than a plain ordinary panel socket?

Apart from this the CT-200 is distinguished only by its normality! There are no frills and no gimmicks at all. The controls worked impeccably at all times and the meters were fast enough to give reliable results when recording.



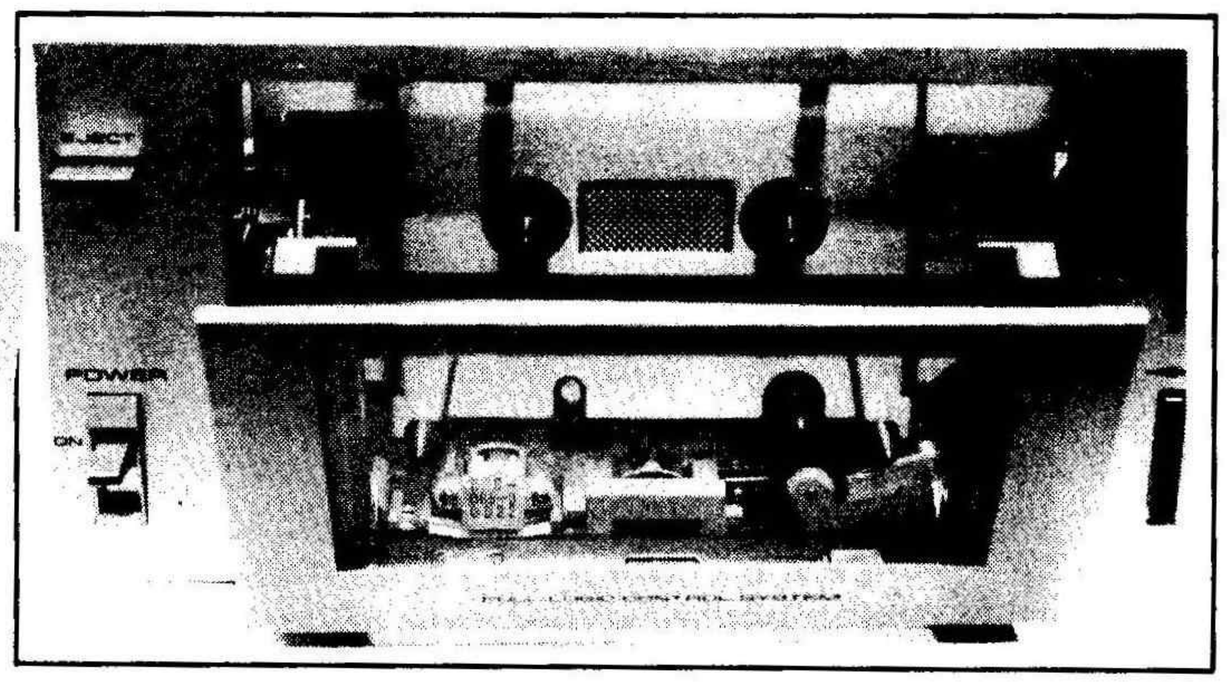As you can see from this detail of the control section of the CT-200, Pioneer have kept it simple. The meters are conventional VU, with no peak indicators, but this should not deter an intended purchase, as they are still pretty good at their jobs! Transport controls are solenoid operated, a plus point at the price.



Unusual is the way in which virtually a whole section of the front panel unhinges to accept a cassette. Can be a little un-nerving the first time, you think something somewhere has dropped off, if you'll pardon the expression!

The heads are easily accessed for cleaning.

The one minor annoyance was the switching 'thump' generated whenever the mains power was interrupted. A small thing, but one which Pioneer should attend to, ASAP.

Resulting Tests

The test bench brought forth no gremlins from the design and a scrutiny of the results will show that good figures were returned on all counts. The signal-to-noise and metal tape figures are particularly impressive for a machine in this price bracket.

Sensitivity was slightly below the spec., at about 80 mV, but this is still a very reasonable figure and one that, together with the input impedance of 90k, should ensure that the CT-200 will work happily with the majority of amplifiers.

Wow and flutter is very well controlled and proved unobtrusive in use. All in all the machine gave a surprisingly good account of itself under test and one which does it credit at the price.

Frequency response (−20 dB)	LH tape :-	25 Hz — 14 kHz ±4 dB
	CrO_2 :-	25 Hz — 17 kHz ±3 dB
	Metal :-	25 Hz — 18 kHz ±2 dB
	FeCr :-	25 Hz — 18 kHz ±3 dB
Signal-to-noise Ratio :- (best result, Dolby on)		−65 dB
Wow and Flutter :	DIN :-	±0.15%
	WRMS :-	±0.05%
Harmonic Distortion :-		1.2% (0 dB)
Line Sensitivity :-		80 mV
Input Impedance :-		90k

Table 1 — Test Results CT-200

Auditioning

Having duly done my duty with the meters and measures, it was down to the nice part of the job — settling back in a chair and listening to the deck playing coherent music as opposed to all those monotonous tones. Again the CT-200 provided a surprise — put simply, it sounded better than I suppose I'd expected. The sound was clean and sharp, with little trace of the old 'cassette sound' that was so immediately recognisable a couple of years back. The machine was always detectable against a reference, as would be expected for a £100 deck, but was never anything less than satisfying to listen to.

Overall it represents very good value for money and can be thoroughly recommended. It just goes to show how far budget hi-fi — and tape in particular — has come of late.

Battleship Engineering

The CTF-1250 is a massive machine which is some 16½ x 7½ x 14½ inches in size, and 26 lb in weight. Once more into the truss dear friends, or block up the living room with tape deck. . .

For all that, the front panel is tightly packed with controls, buttons and things that glow in the night. There is even a control to turn down the brightness of the fluorescent display, lest its brilliance offend thee.

Basically the machine is possessed of full tape optimisation facilities, a digital tape counter, full logic controls which can be operated from the counter, and peak reading meters which can be set to one of *three* modes.

Rather than waste an issue describing it all in a thousand words, take a look at the photo and diagram, the caption to which should explain the myriad machinations of the machine.


Results Of A Test

Table 2 gives a brief extract from the test results, in a form which can be compared to those for the CT-200. As you can see, there is not the difference you may expect, considering how many more bits of green paper are required to obtain the 1250. Those buttons cost money.


All results are given with the machine optimised for the tape in use. With the system employed here, such a set-up is easy and certainly yields improved results for relatively little effort. The figures are generally 'good' for a cassette deck but are nothing outstanding by any means. The CTF-1250 turned in solid, repeatable performance on all the important parameters.

Listening In

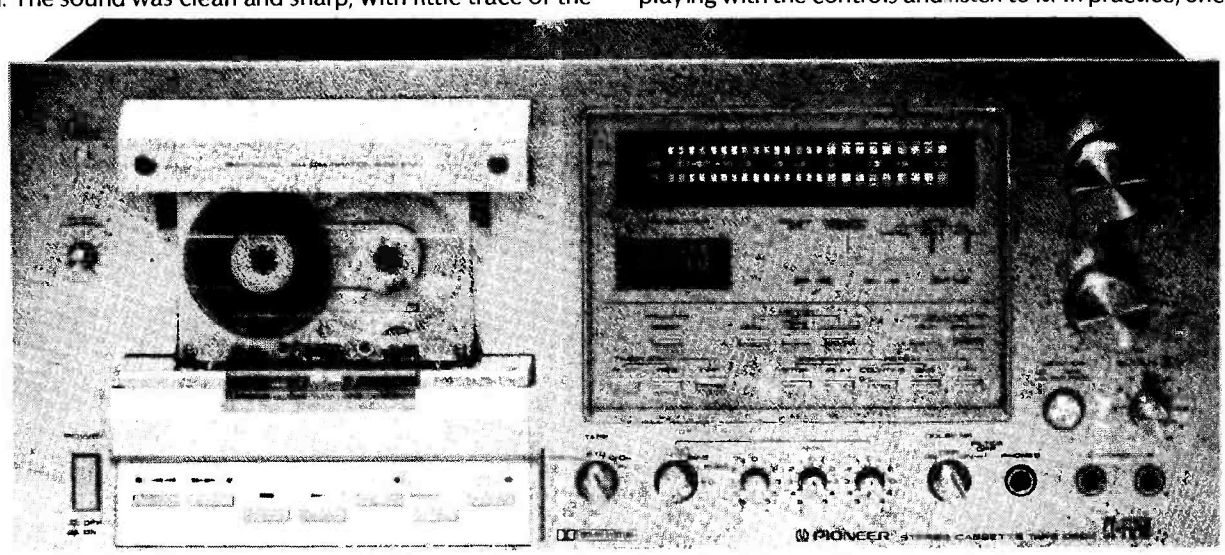Under audition the 1250 proved a difficult machine to live with. No insult intended, it was just well-nigh impossible to stop playing with the controls and *listen* to it! In practice, once a par-



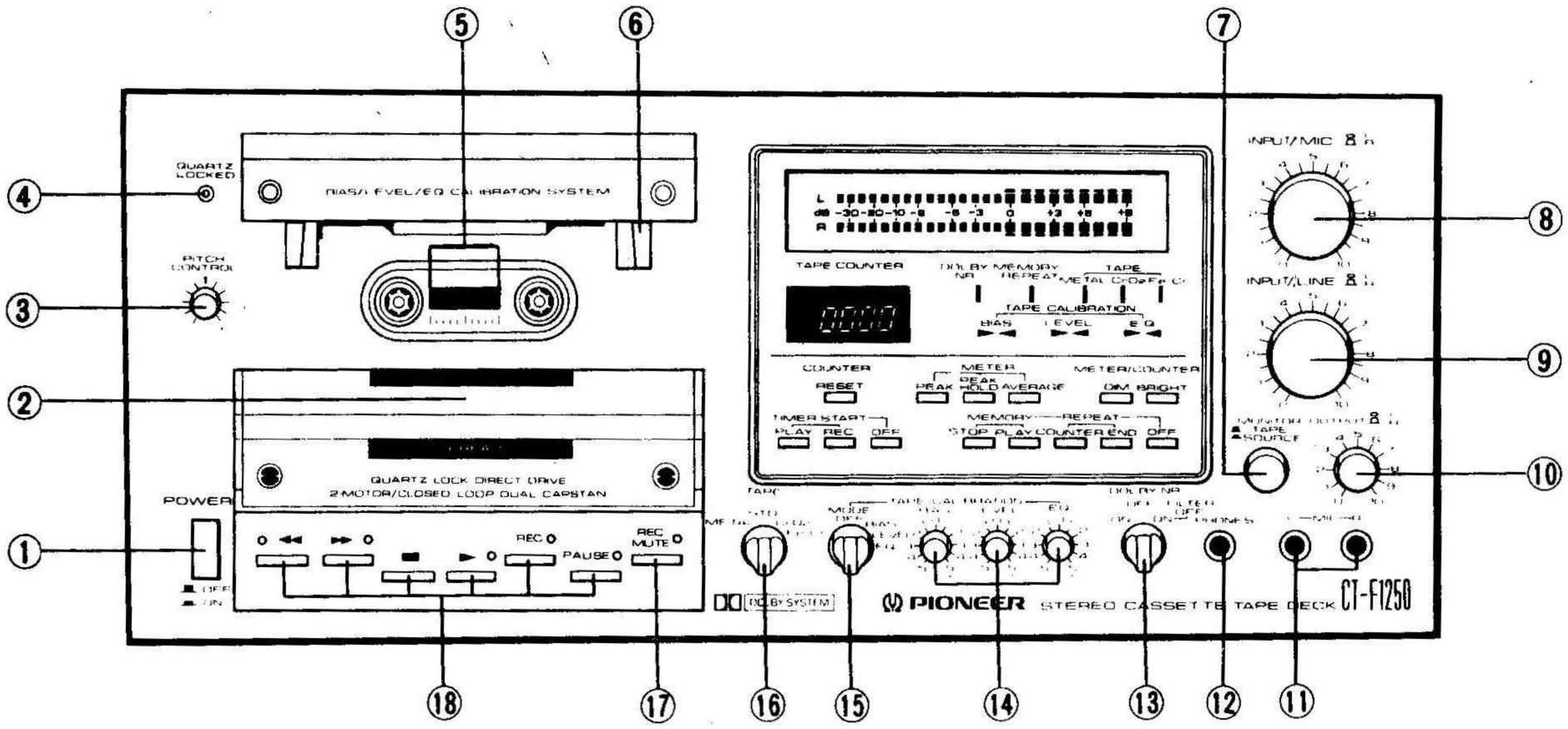The exact opposite of the CT-200 in every way! This is the daunting 1250, Pioneer's tape flagship. Those impressive meters have three modes of operation, peak reading or hold and average.



Rather than attempt to describe the 1250, I've taken the visual approach and stolen this illustration from the Pioneer handbook!
1) *Mains Power:* **One fault here is that it is not 'de-thumped'. 2)** *Dust Cover:* **fits over the heads which would otherwise be very vulnerable. A nice touch this. 3)** *Pitch Control:* **yes, that's right the speed is quartz locked and can be varied if required. 4)** *PLL Indicator:* **activates when speed is correctly set. 5)** *Remaining Tape Markers:* **just the usual backlight to show how much tape is left. 6)** *Tape Guide:* **accurately machined guide paths to make sure you put the cassette in straight. 7)** *Monitor:* **standard stuff for a 3-head design, chooses tape or source. 8)** *Mic Level:* **ganged input control for the front panel jacks. 9)** *Line Input:* **ditto for the two inputs on the rear panel. Friction linking is a little** *too* **strong! 10)** *Output Level:* **click stopped at 0 dB. 11)** *Mic Inputs:* **¼" jack sockets. 12)** *Headphone Output:* **provides a healthy output to drive a pair of dynamic phones. 13)** *Dolby/Filter:* **allows use of the NR with/without MPX filtering. 14)** *Tape Calibration:* **just set the Mode switch to required parameter and adjust the appropriate control until the calibration lights indicate purity. Simple and efficient. 15)** *Mode Control:* **used with 14. 16)** *Tape Selector:* **standard choice of four tape types. 17)** *Record Mute:* **useful for killing ads. when taping from radio etc. 18)** *Solenoid Controls:* **all transport controls are logic locked and virtually idiot-proof.**

ticular brand of tape has been settled on, and the control settings noted, there is little reason to fiddle around at all.

The metering is superb and about the most useful I've encountered anywhere. The sound quality is, again, good, but not as good as can be obtained elsewhere for £450. Some sacrifice has to be made if you want to buy all those lovely facilities.

Best results — regardless of optimisation, strangely enough — were obtained with Maxell tapes and in particular the UDX-II. Sony Metal came a close second, which although providing a cleaner result, showed some signs of treble lift whatever I did to the optimiser.

Frequency response : (−20 dB)	LH :-	25 Hz — 15 kHz ±3 dB
	CrO_2 :-	25 Hz — 17 kHz ±3 dB
	Metal :-	25 Hz — 19 kHz ±3 dB
	FeCr :-	25 Hz — 16 kHz ±3 dB
Signal-to-noise Ratio :- (best result, Dolby on)		−66 dB
Wow and Flutter :	DIN :-	0.1%
	WRMS :-	0.03%
Harmonic Distortion :-		0.9% (0 dB)
Line Sensitivity :-		60 mV
Input Impedance :-		50k

Table 2 — Test Results CTF-1250

Sum Summary

Adding it all up, the CTF-1250 comes out as a very crafty compromise; one that will appeal to many. Its sound is not of the ultimate quality, but its facilities and versatility are second to none.

The CT-200 is a well-conceived and well-executed budget deck that offers excellent value for money and an outstanding sound quality for the class.

Audio Updates


At present I'm working on a feature called 'Sonic Holography' for next month's ETI — and if you don't know what that is (S.H. not ETI!) then you're gonna have to buy our next issue, 'cos I ain't gonna tell you now — as part of which I've had the chance to renew my acquaintance with the Gale loudspeakers. I thought that since such opportunities occur but rarely, I'd drop the reader's letters and ramble on about them for a while instead.

Any Port In A Gale?

Few products, especially loudspeakers, can claim to have stood the ravages of time and changing tastes as successfully as the Gale GS401. It is now many years since Ian Gale first unleashed his chrome-end, unconventionally horizontal transducer upon the ears of the world and, if anything, its standing has risen with the passing of the summers.

Infinite baffle enclosure (330 x 605 x 270 mm)
Four unit design (2 x 200 mm; 1 x 100 mm; 1 x 19 mm dome)
Crossover frequency : 475 Hz and 5 kHz
Efficiency : 20 W produces 96 dB at 1 m
Power handling : 40 W — 200 W RMS per channel into 8R amplifiers recommended
Fuse-protected against overload

Table 3 — Specification of Gale GS401A

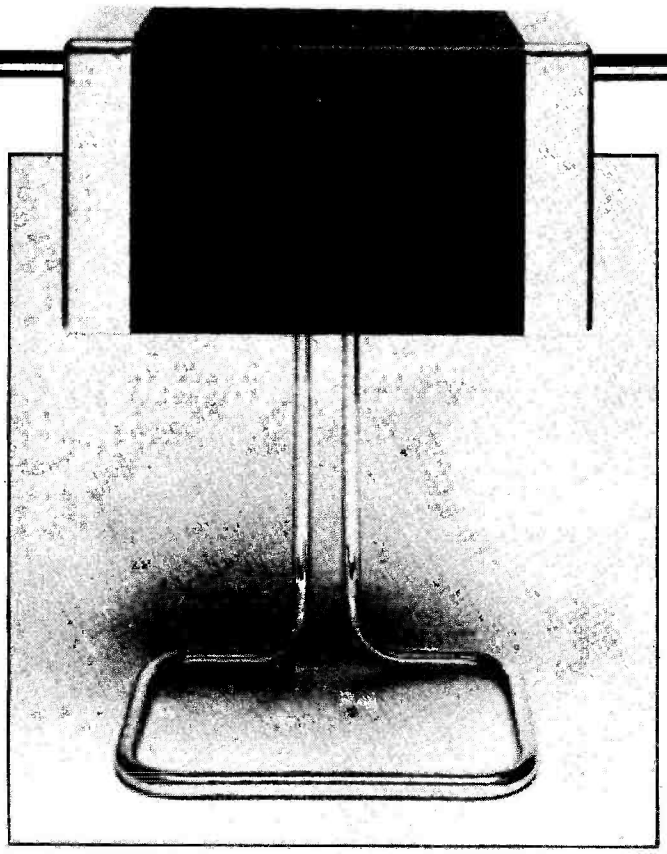

Above: the imposing Gale 401, in chrome livery. The stands are also available in a black finish and personally I prefer it that way!

It is basically a four unit, infinite baffle (sealed box) design of prodigious power handling and excellent imaging. Long before 'phase linearity' gathered unto itself the role of buzzword, the Gales were presenting an essentially phase stable performance, witnessed by the incredible square wave performance. This is one of the few loudspeakers through which such a signal may pass and emerge with some semblance of accuracy.

I had the Gales at home for a period of some weeks and grew to appreciate their virtues more with time. Comparing them to my usual reference — the KEF 105 II — they have a relatively similar approach to music. The 105 has a better defined bass register and a more transparent treble, but the Gales run them mighty close indeed — and at half the price!

Anyone who is about to spread over £400 on the counter for a pair of speakers would be well advised to hold onto the cash until he'd given the 401s a chance to show what they can do. They are more room dependent than most transducers in this league and less coloured than any when set up correctly. Still an outstanding design then, and a lasting credit to their designer.

Trailer

Next month it's back to pickups for a trio of moving coils from Mayware, Ultimo, and Ortofon. I'll also be putting down some words on a new Japanese speaker (shock horror. . .), the Mitshubishi DS-32B which has been specially designed for non-oriental ears.

ETI

— CLEF KITS —

MASTER RHYTHM

As published in Practical Electronics



FULLY PROGRAMMABLE TWENTY-FOUR PATTERNS

EIGHT PARALLEL TRACKS

TWELVE INSTRUMENTS

SEQUENCE OPERATION

Kit includes all components to build this comprehensive User Programmable Rhythm Generator in an attractive metal case with finished case, hardware and wire.

KIT. — £79. BUILT — £114

PIANOS

SPECIALISTS SINCE 1972 STAGE & DOMESTIC TYPES





SIX OCTAVES £207
7¼ OCTAVES £232

The most advanced form of Touch Sensitive action simulating piano keyinertia by patented technique.
Four mixable voices for serious tone variation plus electronic chorus and flanger effects.
See lists for Cabinets, P.A. & Manufacture.

STRINGS £169

Versatile String Synthesizer with split keyboard facility and impressive voices. 49 note organ diode keyswitch plus two-phase Chorus.

ROTOR-CHORUS £89

Two-speed Rotor simulation plus Three Phase Chorus on a single 8" x 5" p.c.b. Mains P.S.U. included.

KEYBOARDS

Square Front with two hole actuator—easily cut.

49 NOTE—£25; 73 NOTE— £39
88 NOTE—£47


OUR PRICES INCLUDE V.A.T., CARRIAGE AND INSURANCE

Please send s.a.e. for complete lists or use our telephone BARCLAYCARD service.
Very competitive EXPORT rates — in Australia please contact JAYCAR in Sydney.

ALL INSTRUMENTS MAY BE SEEN IN OUR SHOWROOM

CLEF PRODUCTS (ELECTRONICS) LIMITED (Dept. E.T.I.)
44A BRAMHALL LANE SOUTH, BRAMHALL,
STOCKPORT, CHESHIRE SK7 1AH. 061-439 3297

ELECTRONIC IGNITION SAVES PETROL

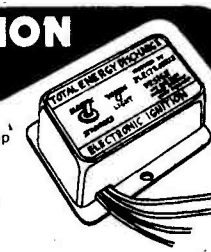

More and more new cars use elctronic ignition to give the best performance and economy. Bring YOUR CAR up to top specification by fitting the latest TOTAL ENERGY DISCHARGE electronic system.

TOTAL ENERGY DISCHARGE gives all the advantages of the best capacitive discharge ignitions;

★ Peak Performance—higher output voltage.
★ Improved Economy—consistent high ignition performance.
★ Better Starting—full spark power even with low battery.
★ Accurate Timing—prevents contact wear without 'contactless' errors.
★ Smooth Performance—immune to contact bounce effects.

PLUS

SUPER HIGH POWER SPARK—3½ times the energy of ordinary C.D. systems.

OPTIMUM SPARK DURATION—to get the very best performance and economy with today's lean carburettor settings.

DESIGNED IN RELIABILITY—with the 'ultimate insurance' of a changeover switch to revert instantly to standard ignition.

TECHNICAL DETAILS

HIGH EFFICIENCY INVERTER. A high-power, high efficiency, regulated inverter provides a 400-volt energy source—powerful enough to store twice the energy of other designs and regulated to provide full output even with the battery down to 4 volts.

SUPERB DISCHARGE CIRCUIT. A brand new technique prevents energy being reflected back to the storage capacitor, giving 3½ times the spark energy and 3 times the spark duration of ordinary C.D. systems, generating a spark powerful enough to cause rapid ignition of even the weakest fuel mixtures without the ignition delay associated with lower power 'long burn' inductive systems. In addition this circuit maintains the correct output polarity, thereby preventing unnecessary stress on the H.T. system.

SOPHISTICATED TRIGGER CIRCUIT. This circuit removes all unwanted signals caused by contact volt drop, contact shuffle, contact bounce, and external transients which, in many designs, can cause timing errors or damaging un-timed sparks. Only at the correct and precise contact opening is a spark produced. Contact wear is almost eliminated by reducing the contact breaker current to a low level — just sufficient to keep the contacts clean.


IN MONEY-SAVING KIT FORM at £14.85 Inc. V.A.T. and P. & P.

All you need is a small soldering iron and a few basic tools — everything else is supplied with easy-to-follow instructions.

FITS ALL 6/12-volt NEGATIVE EARTH cars

ELECTRONIZE DESIGN
2 Hillside Road, Four Oaks
Sutton Coldfield, West Midlands, B74 4DQ
Phone 021-308 5877

RADIATION DETECTORS

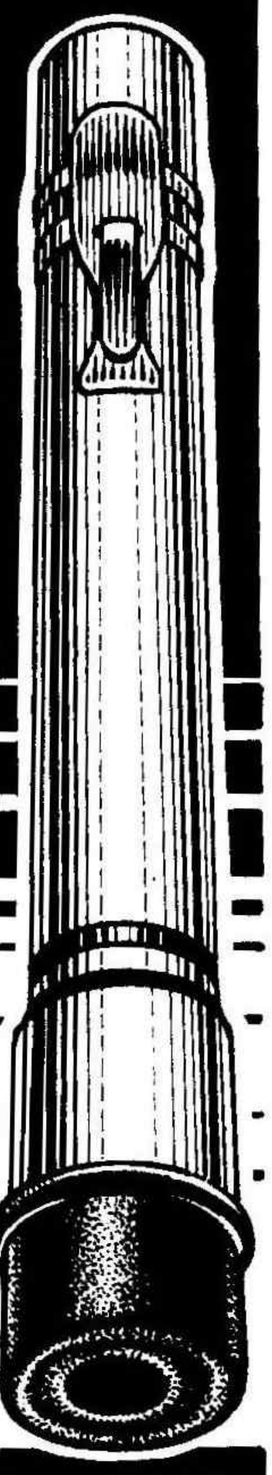

BE PREPARED WITH THIS DETECTOR

VIEW THRU LENS

R

Recommended for General use.
CIVIL DEFENCE ● FIRE SERVICES ● MEDICAL

- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS.
- UNIT IS SIZE OF FOUNTAIN PEN AND WILL CLIP IN TOP POCKET.
- PRECISION INSTRUMENT, METAL CASED, WEIGHT 2oz.
- CONTAINS 3 LENSES. ■ RUGGED CONSTRUCTION.
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH.

COMPLETE WITH DATA

British design and manufacture. Tested, calibrated and guaranteed. Ex-stock delivery by return.


Be prepared, buy whilst available.

Standard model
0-5 or 0-5OR ONLY
£6.95 inc.VAT
Post & Packing 60p

HENRY'S
404 EDGWARE ROAD, LONDON W2 1ED

Buy it with Access

VISA

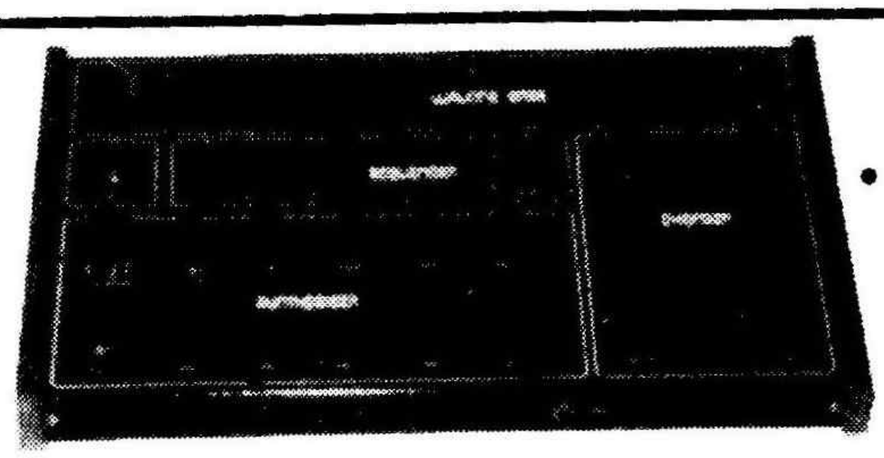

GUITAR
• •SYNTH• •
KIT.
£199·50

A stunning new concept. Play synthesiser from guitar or virtually any other instrument with no multicore lead problems. Chords, Walking Bass & Sequencer are all programmable by the instrument. Just send £3·60 Cheque or P.O. & we will return the complete description & plans, along with a £3·00 credit voucher to be used with any purchase over £20·00.

CAMPBELL CLARK CABINETS

2 ARDEN COURT, CHURCH ROAD, PERRY BARR, BIRMINGHAM. B42 2LF

TV SOUND TUNER
ETI SEP 80 PROJECT

All parts available / send for list

ALSO

No. 1 for Teletext Kits
TV Spare Parts and Components

Callers welcome at Shop Premises

MANOR SUPPLIES

172 WEST END LANE, LONDON NW6 1SD
TELEPHONE: 01-794 8751

Near West Hampstead Jubilee & British Rail Stations

TTL CMOS 74LS LEDS

LB ELECTRONICS

LINEAR RAMS EPROMS SURPLUS

TELEPHONE: UXBRIDGE 55399

SUPERSALE '81
All full spec. 2114 (450ns) **£1.85,** p&p 35p. 2708 **£2.00** p&p 35p. TEXAS INSTRUMENTS 2716 single rail, full spec. **£5.95.**

NEW FREEDOM PHONE
The completely portable telephone with intercom and bleep paging facility. Range 200 yards **£125** + VAT p&p £3.00. Leaflet available on request (not PO/HO certified).

MK 1002P (dual 128 bit Shift Reg) **35p.**
LM711CH (Voltage Comparator) **30p.**

(All Full Spec)
2526 Character Generator (64 × 9 × 9) **£2.95** + data & p&p 35p.
MM5240 AA/J Character Generator **£3.50** + data. p/p 35p.
LEAR SIEGLER dot matrix printhead. 7 needle. **£19.50** p/p 50p.
ZETTLER low profile PCB relay 30mm x 36mm 4.8/6.9v d.c. 2/2.5 amps a.c. contacts. **85p** p/p 35p.

D TYPE CONNECTORS
9 Way: sockets (solder) **55p.**
15 Way: wirewrap plugs only **75p.**
50 Way: skt (wirewrap) **£1.65.**
50 Way: skt **£1.45,** p&p 25p.
25 Way Male to Female with covers plus minimum 1 metre of cable (12 way) **£4.00 each** p/p 35p.
25 Way plug (soldercail). 25 Way socket **£1.20 each.**

COVERS
37 Way: **90p** (plastic), p&p 35p.
9 Way (metal) **60p,** 15 Way (metal) **75p,** 25 Way (plastic) **65p,** 37 Way reduced from 90p to **80p.**
50 Way (plastic) **90p.**

DISPLAYS
HP 5082 4 digit DIL display full spec **£1.50 each,** p&p 35p. Large quantities POA.
LED 3 Digit DIL **55p,** p&p 35p.
Bowmar 9 digit .1 in LED with red bezel. (As used in calculators). **£1.00** + 35p p&p.

SUPERSAVER 1
Ribbon Cable Headers 16 DIL Jermyn, gold plated, with cover **45p,** p&p 25p.
Ansley Header plugs. PCB mounting. 14 Way 75p, 16 Way 95p, 24 Way £1.80. (Insulation piercing type). p/p 35p.
Ansley I/O Header plugs. .1in 26 Way 65p, 26 Way (right-angled) 85p. 40 Way £1.00 p/p 35p.

SUPERSAVER 2
Tantalum Capacitors 25 volt. 4.7 uF, 14 for **£1.00,** p&p 35p.

SUPERSAVER 3
PRICE SMASH FND 500 .5in. LED displays, full spec **50p each,** p&p 35p, large quantities POA.

SUPERSAVER 5
Battery eliminator 6VDC 200MA 240V AC input ideal for calculators, radio, etc., give away price 95p each. Large quantities P.O.A. p&p 35p.

SUPERSAVER 6
EAO KEY SWITCH oblong fascia, 25mm x 18mm (approx. 18mm hole, fixing supplied, brand new with 2 keys. **£2.95** p&p 35p.

SUPERSAVER 7
SN74116 Dual 4 Bit letch **75p,** p&p 35p.
SN74118 Arithmetic Logic Unit, **80p,** p&p 35p.
SN74194 4 Bit Register, **50p** p&p 35p.
SN74198 8 Bit Shift Register, **75p** p&p 35p.

SUPERSAVER 8
ITT 4cx 250b brand new full spec £7.50 each p&p 35p.

SUPERSAVER 9
5 digit 7 segment DIL LED .11" displays 4 for **£1.50** p/p 35p.

SUPERSAVER 10
9 way male/female connector, ELCO 8129, 0.1 inch pitch, gold-plated PCB mounting, ideal for bussing two PCBs together. Superb value, **35p,** p&p 35p.

SUPERSAVER 11
74LS266 **50p.** 74LS245 **£2.40.** 74LS240 **£1.00.** 74S260 **35p.** P&P on all above 35p.

SUPERSAVER 12
TMS 3128NC Static shift register, **£1.50,** p&p 35p.

SUPERSAVER 14
Recording Designs Ltd digital cassette deck. 50-100 Baud RS232 240V input. A professional superb deck. **£48.00,** p&p £2.00.

SUPERSAVER 15
5K ¾" multiturn trimpots, PCB mounting, per box of 14 **£2.50,** p&p 35p.

SUPERSAVER 16
OPTRON OPTO SLOTTED SWITCH (Type OPB-814) **£1.00,** p&p 3 p.

LEDs (Full spec.)
TIL209, red **10p.** 0.2in, red **12p.** 0.2in. green **28p.** 0.2in, yellow **28p.**
RL54 red Axial lead. **15p.**
P&P on all above 35p.
VERNITRON Ceramic filters type FM4 10 yMHz **45p,** p&p 35p.
TRANSISTORS, BD236 **40p,** BC183L **10p,** BF195 **10p.**
TBA 810S, with data, **85p,** 4-way Dil switches, **75p.** MC1303 Dual Stereo preamp with data, **£1.25.** 7in. Nylon cable ties 100 for **£1.50.** All p&p 35p.
TMS 4030, 4096 x 1 dynamic RAM 2000 ns removed from PCBs. **£1.00 each.** 16 for **£25,** p&p 35p.
PCB KEYBOARD, 65mm × 82mm, 18 key Clickers less Key tops, ideal Hexadecimal use **35p,** p&p 35p.
CAPACITOR SCOOP. 1.600uF at 10v, 160uF at 25v. Axial lead. 2 dozen for **£1** + 35p p&p.
DON'T KILL YOUR EPROMS. Augat 24 Way low profile socket. Solid gold pins. A superb socket. Leave your eproms in them for programming or usage to prevent breaking off pins. Only **40p** each, p&p 35p.

GIVEAWAY
18 pin low profile dil socket 13p EACH or 8 for £1.00 p&p 35p

Just arrived. ITT 2082 Data Modem. Brand new and boxed, with manual. 600/1200 Baud. Data Modem to CC ITT. V24/RS232C. Channel centre frequencies 1300 and 1700Hz (600 Baud) or 1300 and 2100Hz (1200 Baud). Synchronous or asynchronous operation over 2 or 4 wire, switch or dedicated lines, built in self and lines test functions. Some of the best equipment we have ever obtained. £115.00 each, p&p £3.00. (Fraction of original cost).

IC HOLDERS (Low-profile)

8 Dil	**12p**	14 Dil	**15p**
16 Dil	**17p**	18 Dil	**20p**
22 Dil	**28p**	24 Dil	**35p**
28 Dil	**45p**	All p&p 35p	

WE STOCK a vast range of TTL, CMOS, some 74LS. MINIATURE TOGGLES, etc.
PSUs. We have a large stock of power supplies at very realistic prices (callers).

RELAYS
Banor resettable double pole changeover 12V **£1.** Both p&p 35p.

JUST ARRIVED — PCB 008 OSCILLATOR Containing 1 NPN transistor, 1 resistor, 1 transformer and PP3 battery connector. 30mm x 20mm (approx). **35p** each. **5 for £1.** p/p 35p. **PCB 009** 1 x CD4069, 1 x CD4011, 5 transistors, 7 capacitors, 12 resistors, 1 diode, 45mm x 55 mm (approx). **45p** each. p/p 35p.
CENTRONICS 101A Dot Matrix printer. Fully overhauled. 165 char/sec. £450.00 inc. VAT. Carriage at cost. As above dual headed 300 char/sec £650 inc. VAT.

C.P.U. TYPE 10660. These devices are brand new, supplied with data sheet for experimental use. **4 for £1.** p&p 35p.

ICL POWER SUPPLY (exchange units) 240V AC input. Output +24V at 2 amps DC, —24V at 2 amps DC (adjustable to 12V) +5V at 4 amps DC —100V DC and 6.3V AC. £10.50.
Terms cash with order (official orders welcomed from colleges, etc). All enquiries s.a.e. please. All prices inclusive of VAT, unless otherwise stated. **Postage** as shown per item.
FOR THE PROFESSIONAL USER. CP Clare Keyboard switches with buttons (blank) **65p** each p&p 35p.

BURROUGHS keyboard, 96 key station. On-board crystal and TTL. Brand new and boxed. 500mm x 190mm. At the time of advert no data. No keytops at all. Clare pender. Reed switches. Bargain £12.00 each, p&p £1.50.
PLEASE DO NOT ORDER GOODS FROM OLD ADVERTS. PHONE BEFORE ORDERING.

SURPLUS STOCKS PURCHASED FOR CASH

LB ELECTRONICS
11 HERCIES ROAD
HILLINGDON, MIDDLESEX
UB10 9LS, ENGLAND
All enquiries s.a.e. please
Telephone answering machine service out of business hours.

New retail premises, now open Mon, Tues, Thurs, Fri, and Sat, 9.30-6.00 Lunch 1-2.15 weekdays. Closed all day Wednesday. We are situated just off the A40 opposite Master Brewer.

ALL PRICES INCLUSIVE OF VAT

UXBRIDGE 55399

All components full spec.

MC Micro Circuits — Prime components~Low prices.

Dept. ETI 8, Unit 9/10, 1st Floor, East Block, 38 Mount Pleasant, London WC1X 0AP. Tel: 01-837 1165, 01-278 7369. Telex: 8953084 Maclin G.

All our microchips are at micro prices. Don't be fooled by low prices. We do not offer for sale surplus, sub-spec or rebranded devices. All our parts are guaranteed new, first quality, factory prime, full spec devices. It is also our policy to offer you the best of new devices that become available and these are featured regularly. Prices are exclusive of p&p and VAT – please refer to "Ordering information" before ordering. Official orders from schools, colleges, universities and Gov. authorities accepted.

NEW, LOW, LOW PRICES ON MEMORIES!!!

Compare *our* prices before you buy *elsewhere!* All devices are brand new, factory prime, full spec, and fully guaranteed! All prices exclude p&p and VAT. Please refer to Ordering Information before ordering. DON'T DELAY – BUY TODAY – SUCH LOW PRICES DON'T LAST FOR EVER!!

STATIC RAMS	1-24	25-99	100+
2114L 450 NS	195p	175p	150p
2114L 300 NS	225p	195p	175p
2114L 200 NS	250p	225p	195p
4118 250 NS 8K NEW!!	895p	795p	695p
HM61 16 16K (2K x 8) 150 NS 24-pin NEW!!	£19.95	£17.95	£15.95
DYNAMIC RAMS			
4116 200 NS Ceramic	195p	175p	150p
4116 150 NS	375p	350p	325p
HM4864 64K (65K x 1) 200 NS Single + 5V supply 16-pin NEW!!	£29.95	£24.95	£19.95
CMOS RAMS			
5101 1K (256 x 4) 450 NS	350p	325p	295p
4315 4K (4K x 1) 450 NS	995p		
TC5514P 4K (1K x 4) 450 NS	495p	450p	395p
HM6116 16K (2K x 8) 150 NS 24-pin NEW!!	£19.95	£17.95	£15.95
EPROMS			
2708 450 NS	350p	325p	295p
2716 Single 5V 450 NS	475p	450p	395p
2532 Single 5V 450 NS	£14.95	£12.95	£11.95
2732 Intel-type 450 NS	£14.95	£12.95	£11.95
2564 64K (8K x 8) 450 NS 28-pin	£99	£95	£90

Ordering Information. Unless otherwise stated for orders under £50 add 50p p&p. Add 15% VAT to total (no VAT on books). All devices are brand new, factory prime and full spec and subject to prior sales and availability. Prices subject to change without notice. Minimum telephone order using ACCESS, is £10. If ordering by post with ACCESS, include name, address and card no. written clearly. Please allow 4/6 weeks delivery on books.

DTL

830	55p
935	65p
937	55p
944	65p
946	55p
947	55p
962	55p
9099	90p

7400

7400	11p
7401	12p
7402	12p
7403	13p
7404	17p
7409	18p
7410	18p
7412	18p
7413	28p
7420	16p
7430	18p
7432	25p
7440	16p
7442	68p
7448	75p
7473	32p
7474	32p
7475	40p
7476	40p
7490	35p
7492	50p
7493	50p
7496	45p
74121	35p
74123	45p
74154	90p
74157	55p
74122	45p
74125	50p
74195	100p
74196	100p
74283	140p
74290	120p
74365	90p
74365	90p

74LS

74LS00	12p
74LS01	12p
74LS02	13p
74LS03	13p
74LS04	13p
74LS08	20p
74LS10	19p
74LS11	20p
74LS12	30p
74LS13	35p
74LS14	60p
74LS15	38p
74LS20	18p
74LS21	30p
74LS22	38p
74LS26	45p
74LS27	45p
74LS30	18p
74LS32	23p
74LS37	35p
74LS38	35p
74LS40	25p
74LS42	56p
74LS47	78p
74LS48	85p
74LS49	99p
74LS73	30p
74LS74	30p
74LS75	42p
74LS85	98p
74LS86	39p
74LS90	35p
74LS93	70p
74LS96	150p
74LS107	40p

74LS112	75p
74LS123	63p
74LS125	50p
74LS126	50p
74LS132	79p
74LS138	69p
74LS139	75p
74LS148	170p
74LS151	75p
74LS153	75p
74LS155	65p
74LS157	74p
74LS160	115p
74LS161	78p
74LS163	90p
74LS164	90p
74LS165	150p
74LS168	190p
74LS173	100p
74LS174	99p
74LS175	99p
74LS181	280p
74LS190	110p
74LS195	87p
74LS196	100p
74LS221	110p
74LS240	210p
74LS241	200p
74LS242	220p
74LS244	175p
74LS245	220p
74LS251	120p
74LS253	120p
74LS257	110p
74LS260	90p
74LS273	175p
74LS290	95p
74LS293	120p
74LS366	57p
74LS373	170p
74LS374	170p
74LS375	140p
74LS393	135p
74LS490	140p
74LS670	260p

CMOS

4001	19p
4002	19p
4006	75p
4007	19p
4008	80p
4009	35p
4010	45p
4011	24p
4012	24p
4013	38p
4014	70p
4015	75p
4016	35p
4017	75p
4018	76p
4019	42p
4020	88p
4021	100p
4022	88p
4023	22p
4024	50p
4025	20p
4026	130p
4027	45p
4028	75p
4029	80p
4030	50p
4031	195p
4033	145p
4035	104p
4036	290p
4037	105p
4038	110p
4039	290p
4040	99p
4041	75p

4042	73p
4043	86p
4044	88p
4045	160p
4047	99p
4048	56p
4049	38p
4050	40p
4051	69p
4052	75p
4053	73p
4054	111p
4055	121p
4056	121p
4059	560p
4060	112p
4063	112p
4066	56p
4067	422p
4068	19p
4069	19p
4070	28p
4071	25p
4072	25p
4078	425p
4075	20p
4076	88p
4077	23p
4078	29p
4081	23p
4082	25p
4085	86p
4086	68p
4089	130p
4093	68p
4094	225p
4095	99p
4096	325p
4098	110p
4099	180p
4501	25p
4502	112p
4503	68p
4507	52p
4508	288p
4510	76p
4511	125p
4512	75p
4514	250p
4515	290p
4516	109p
4518	99p
4520	99p
4521	230p
4526	105p
4527	130p
4528	99p
4529	140p
4531	150p
4532	125p
4538	150p
4543	160p
4556	70p
4560	225p
4569	240p
4572	46p
4584	79p
4585	125p

74C

74C20	30p
74C76	60p
74C85	145p
74C97	125p
74C98	125p
74C107	100p
74C160	110p
74C161	145p
74C162	145p
74C163	145p
74C192	175p
74C193	175p
74C194	175p
74C195	175p
74C903	45p

LOW PROFILE SOCKETS BY TEXAS

	SALE
8 pin	7p
14 pin	9p
16 pin	10p
18 pin	15p
20 pin	18p
22 pin	22p
24 pin	22p
28 pin	25p
40 pin	28p

MEMORIES

STATIC RAMS

2114L 450 NS	195p
2114L 300 NS	225p
2114L 200 NS	250p
4118 250 NS 8K NEW!!	£8.95
HM6116 16K (2K x 8) 150 NS 24-pin NEW!	£19.95

DYNAMIC RAMS

4116 200 NS Ceramic	175p
4116 150 NS	375p
HM4864 64K (65K x 1) 200 NS Single 5V supply, 16-pin NEW!	£29.95

KEYBOARD ENCODER

AY 52376	795p

SUPPORT DEVICES

6520	325p
6522	625p
6532	825p
6551	825p
6810	350p
6820	360p
6821	325p
6845	£23.50
6850	295p
6852	350p
8212	210p
8214	450p
8216	210p
8224	275p
8226	225p
8228	425p
8251	475p
8253	995p
8255	445p
8257	895p
8259	950p
MC144 12VL	797p
Z80 PIO	595p
Z80 CTC	595p
Z80A PIO	695p
Z80A CTC	695p
Z80 DMA	£19.95
Z80A DMA	£24.95
Z80 S10/1	£29.95
Z80A S10/0	£34.95
Z80 S10/1	£29.95
Z80A S10/1	£34.95
Z80 S10/2	£29.95
Z80A S10/2	£34.95

LINEAR IC s

INTERFACE LINEAR

AY 3 1350	795p
AY 3 8910	825p
709	30p
723	33p
741	18p
ICL7106	575p
ICL7107	695p
ICL8038	295p
ICM7216A	1875p
ICM7216B	1675p
ICM7555	80p
LM301AM	30p
LM311	50p
LM318	75p
LM324	45p
LM339	45p
LM380	65p
LM1496	65p
LM1871	550p
LM1872	550p
LM3900	50p
LM3914	225p
LM3915	225p
LM13600	125p
NE555	18p
NE556	50p
RC4136	85p
SN76477N	175p
TBA810DAS	85p
TL071	55p
TL074	130p
TL082	75p
TL084	110p
TL490	175p
XR2206	325p
XR2207	375p

VOLTAGE REGULATORS

7805/7812	50p
7905/7912	80p
78HO5SC	575p
78HGKC	625p

EPROMS

2708 450 NS	350p
2716 5V 450 NS	475p
2532 32K 450 NS	£14.95
2732 Intel-type 450 NS	£14.95
2564 NS (8K x 8) 450 NS 28-pin NEW!	9900p

UARTS

AY 3 1013A	325p
AY 3 1015D	398p
IM6402 1PL	325p

CPU'S

6502	625p
6504	750p
6505	750p
6800	645p
6802	925p
6809	£19
8080A	425p
8085A	£10.95
Z80	700p
Z80A	900p
Z8001	£125
Z8002	£95

BIPOLAR RAMS

27LS00	995p
93419DC	1125p

DIL SWITCHES

4 pole	99p
6 pole	115p
8 pole	140p
10 pole	175p
MC1488	90p
MC1489	90p
DM8123	125p
75150	125p
75154	125p
75182	195p
75322	250p
75324	325p
75325	325p
75361	350p
75365	295p
75451	50p
75491/2	75p
8T26	155p
8T28	175p
8T95	175p
8T97	155p

LEDs

TIL209	9p
TIL211	13p
TIL212	15p
TIL220	12p
TIL222	15p
TIL224	18p

DISPLAYS

FND500	80p
FND510	80p
FND567	125p
DL704	85p
DL707	85p
MV57164	225p

ISOLATORS

ILD74	120p
ILQ74	325p
MCT6	90p
TIL111	75p

CMOS RAMS

5101 1K (256 x 4) 450 NS	350p
4315 4K (4K x 1) 450 NS	995p
TC5514P 4K (1K x 4) 450 NS	495p
HM6116 16K (2K x 8) 150 NS 24-pin NEW!	£26.00

FLOPPY DISC CONTROLLERS

FD 1771 B-01 S/D Inverted Bus	£19.95
FD 1791 B-01 D/D Inverted Bus	£32.95

NOW LONDON-BASED FOR EVEN FASTER SERVICE!

See new address above

NEW SUPER MUSIC MACHINE KIT!

AT LAST – an affordable kit that can be PROGRAMMED TO PLAY ANY SONG OR GROUP OF SONGS! Instead of a nightmare of numerous ICs and special expensive Bipolar ROMs the SUPER MUSIC MACHINE uses a SPECIAL MASK PROGRAMMED COMPUTER CHIP one CMOS gate and the most popular erasable EPROM, the 2708/2716 series. BASIC KIT includes drilled, plated and screened PC board and ALL components except the EPROM and 12V transformer. The basic kit will play short renditions of 25 tunes through its 7 WATT AMPLIFIER SECTION. Add an optional ROM and any tune programmed will be played. If you have the equipment to program 2708 EPROMs, we supply full information on programming your own music!

FEATURES

- **Basic kit contains 25 short tunes in the main ICI.**
- **Will address external ROM for up to 1,000 MORE NOTES per ROM (ROM is not included).**
- **Operates on 12V AC or 12V DC at 500mA. (Using unit on 12V DC and with optional ROM requires 9V bias battery, not included).**
- **7 watts of audio power will drive 8 or 16 ohm speakers or horn speakers (not included).**
- **DIP switches not included.**
- **'NEXT TUNE' provision steps sequentially through all tunes.**
- **Tune address can be wire jumper selected or board is designed to take DIP switches.**
- **PITCH, VOLUME and TEMPO are all adjustable.**
- **SPECIAL 'CHIME' SEQUENCES can be activated regardless of tune address to provide for multiple doorbell applications.**
- **All tunes consist of electronic musical notes played one at a time. There are no chords or harmony sound to the music.**
- **STEP-BY-STEP ASSEMBLY INSTRUCTIONS provided.**
- **Large number of PREPROGRAMMED ROMS with popular and classical tunes readily available. Send SAE for list and prices.**

ONLY £16.75 for basic kit (plus p&p 60p).

SE 01 Sound Effects Kit

The SE 01 is a complete kit that contains all the parts to build a programmable effects generator. Designed around the new Texas Instruments SN 76477 Sound Chip, the board provides banks of MINI DIP switches and pots to program the various combinations of the SLF Oscillator VCO Noises, One Shot and Envelope Controls A Quad Op Amp IC is used to implement an Adjustable Pulse Generator Level Comparator and Multiplex Oscillator for even more versatility. The 3¼" × 3" PC Board features a prototype area to allow for user added circuitry. Easily programmed to duplicate Explosion, Phaser Guns, Steam Trains or almost an infinite number of other sounds. The unit has a multiple of applications. The low price includes all parts, assembly manual programming charts and detailed 76477 chip specifications. It runs on a 9V battery (not included). On board 100MV amp will drive a small speaker directly or the unit can be connected to your stereo with incredible results! (Speaker not included) **COMPLETE KIT ONLY £14.99** P&P 67p VAT

BIPOLAR PROMS

All are identical and equivalent types – we reserve the right to substitute any make

256 bit (32 × 8) 16-pin tri-state MB 7051/ 27S09/7603/5600/6331/74S288/82S123	395p
256 bit (32 × 8) 16-pin open collector MB 7056/27S08/7602/5600/6330/74S188/82S23	395p
1K (256 × 4) 16-pin tri-state MB7052/74S287/ TBP14S10/93427/82S129/7611/6301	395p
1K (256 × 4) 16-pin open collector MB7057/ 74S387/ TBP14SA10/93417/82S126/7610/6300	395p
2K (512 × 4) 16-pin tri state MB7053/93446/ 82S131/7621/6306	495p
2K (512 × 4) 16-pin open collector MB7058/93436/ 82S10/7620/6305	495p
4K (1024 × 4) 18-pin tri-state MB7122/74S476/ 93453/82S137/7643/6353/27S33/3625/5626	995p

BOOKS

Please order books by reference no. and title and add 50p post & packing for each book ordered

21168	Active Filter Cookbook	£10.95
21440	Aviation Electronics 3rd Ed	£6.75
21558	Audio IC Op Amp Applications 2nd Ed	£5.95
21524	The Cheap Video Cookbook	£4.50
21396	CMOS Cookbook	£7.75
21539	Design of Active Filters with Experiments	£5.95
21537	Design of Op Amp Circuits with Experiments	£5.95
21545	The Design of Phased Locked Loop Circuits with Experiments	£8.75
21686	Design of VMOS Circuits with Experiments NEW!	£5.95
21616	Electronic Telephone Projects	£4.95
21127	How to Read Schematic Diagrams 3rd Ed	£4.25
21613	How to Use Integrated Circuits Logic Elements 3rd Ed	£4.50
21627	IC Converter Cookbook	£10.50
21595	IC Op Amp Cookbook 2nd Ed	£11.25
21516	IC Timer Cookbook	£8.50
21601	Instrumentation Transducers and Applications	£8.95
21452	Learn Electronics Thru' Troubleshooting 2nd Ed	£8.25
21894	LCC Circuits	£4.46
21542	Logic and Memory Experiments Using TTL Integrated Circuits Book 1	£7.50
21543	Logic and Memory Experiments Using TTL Integrated Circuits Book 2	£7.50
21568	Linear IC Principles Experiments and Projects 2nd Ed	£7.50
21612	Oscilloscope Applications & Experiments	£6.75
21535	99 Practical Electronics Projects 2nd Ed	£3.75
21599	Practical Low Cost IC Projects 2nd Ed	£3.50
21557	Practical RF Communication Data for Engineers and Technicians	£6.75
21482	Regulated Power Supplies 2nd Ed	£7.50
21419	Security Electronics 2nd Ed	£4.50
21621	Solar Heating	£5.25
21036	TTL Cookbook	£7.25
21103	Troubleshooting with the Oscilloscope 3rd Ed	£4.50
21313	TV Typewriter Cookbook	£7.50
21339	Video Security Systems	£5.25
21521	Video Tape Recorders	£7.50

6809 S-100 SINGLE-BOARD COMPUTER

- Meets IEEE S-100 Standard!
- Uses Motorola's Powerful MC6809 CPU!
- 4K, 8K, 16K ROM!
- 2K RAM!
- ACIA, PIA, 8080 Simulated I/O!
- RS – 232 Handshake!
- Selectable BAUD Rates!
- Manual includes: 11" × 7" Schematic, Parts List, User Notes, Software Listings and MORE.
- ACIA, PIA, 8080 Simulated I/O! **Bareboard only £49!** (plus £1 p&p)

CPU (6809) £19.00! ADSMON, Monitor (2716) £25! **COMPLETE BOARD ASSEMBLED AND TESTED, ONLY £250!** (plus £2 p&p).

Autoranging, Auto Unit Diplay 3½-digit DMMs from ONLY £45.95 inc. VAT

6200, as itemised, ONLY £49.95 inc. VAT!
6220, as 6200, plus 10Amp AC/DC measurement ONLY £55.95 inc. VAT!
6100, with 10Amp AC/DC measurement AND Continuity Check! ONLY £85.95 inc. VAT!

Optional vinyl carry case £2.65 inc VAT

- **1mV, 100μA and 0.1Ω resolution!**
- **Measures AC voltage to 600V!**
- **Measures DC voltage to 1000V!**
- **Measures resistance to 2 Megohms!**
- **Low power Ohm ranges!**
- **Displays mV, V and mA!**
- **0.8% accuracy!**
- **Zero adjustment!**
- **3 other models too!**

NEW EXCITING ENTERTAINING SOFTWARE FOR THE APPLE II and APPLE II PLUS!! **ASTEROIDS IN SPACE!!!**

If you liked Invaders you'll love ASTEROIDS IN SPACE by Bruce Wallace! Your spaceship is travelling in the middle of a shower of asteroids. Blast the asteroids with lasers, but beware – BIG ASTEROIDS FRAGMENT INTO SMALL ASTEROIDS! The apple game paddles allow you to rotate your spaceship, fire its laser gun and give it thrust to propel it through endless space. From time to time, too, you'll encounter an alien spaceship whose mission is to DESTROY YOU, so you'd better destroy it first! High resolution graphics and sound effects add to the arcade-like excitement this program generates. RUNS ON ANY APPLE II WITH AT LEAST 32K AND ONE DISK DRIVE!

ON DISKETTE **ONLY £14.95**

UNIVERSAL SCR

C106D 400V/5A Sale 30p

THE NEW GI COMPUTER SOUND CHIP

The amazing AY-3-8910 is a fantastically powerful sound and music generator, perfect for use with any 8-bit micro processor. Contains 3 tone channels, noise generator, 3 channels of amplitude controls, 16 bit envelope period control, 2 parallel I/O, 3D/A converters plus much more. All in 40 pin DIP Super easy to interface to the S 100 or other Busses. ONLY £8.50 + VAT, including FREE reprint of BYTE 79 article! Also, add £2.25 for 60 page data manual. "Perhaps the next famous composer will not direct a 150 piece orchestra but rather a trio of microcomputers controlling a bank of AY-3-8910s." BYTE July '79.


SPOT DESIGNS

20 W MOSFET Amplifier

Although power MOSFETS were originally only used in super-fi amplifiers, they have fallen in price to the point where they can be given serious consideration for use in any amplifier where an output power of between about 20 W and 100 W RMS is required. This simple design gives good quality results with the level of total harmonic distortion well below 1% at all audio frequencies provided the maximum output power is not exceeded. The maximum output power is a little over 20 W RMS if a 50 V supply is used and approximately 30 W RMS if a 60 V supply is employed with the unit (both are loaded voltages).

The circuit is basically quite conventional with Q2,3 being used as a Darlington pair, common emitter driver stage. The main collector load for this is formed by a constant current generator circuit using Q1 and its associated components. This gives a current of about 6-7 mA in the driver stage. Such a low current is acceptable due to the very high current gain of the complementary source follower MOSFET output devices. PR2 is used to set the appropriate quiescent output current through the output stage and the slightly negative temperature coefficient of the output devices makes any thermal stabilisation here totally unnecessary. R2,3 and PR1 are used to bias the amplifier. No phase or frequency compensation components are needed due to the excellent high frequency performance of the two output transistors.

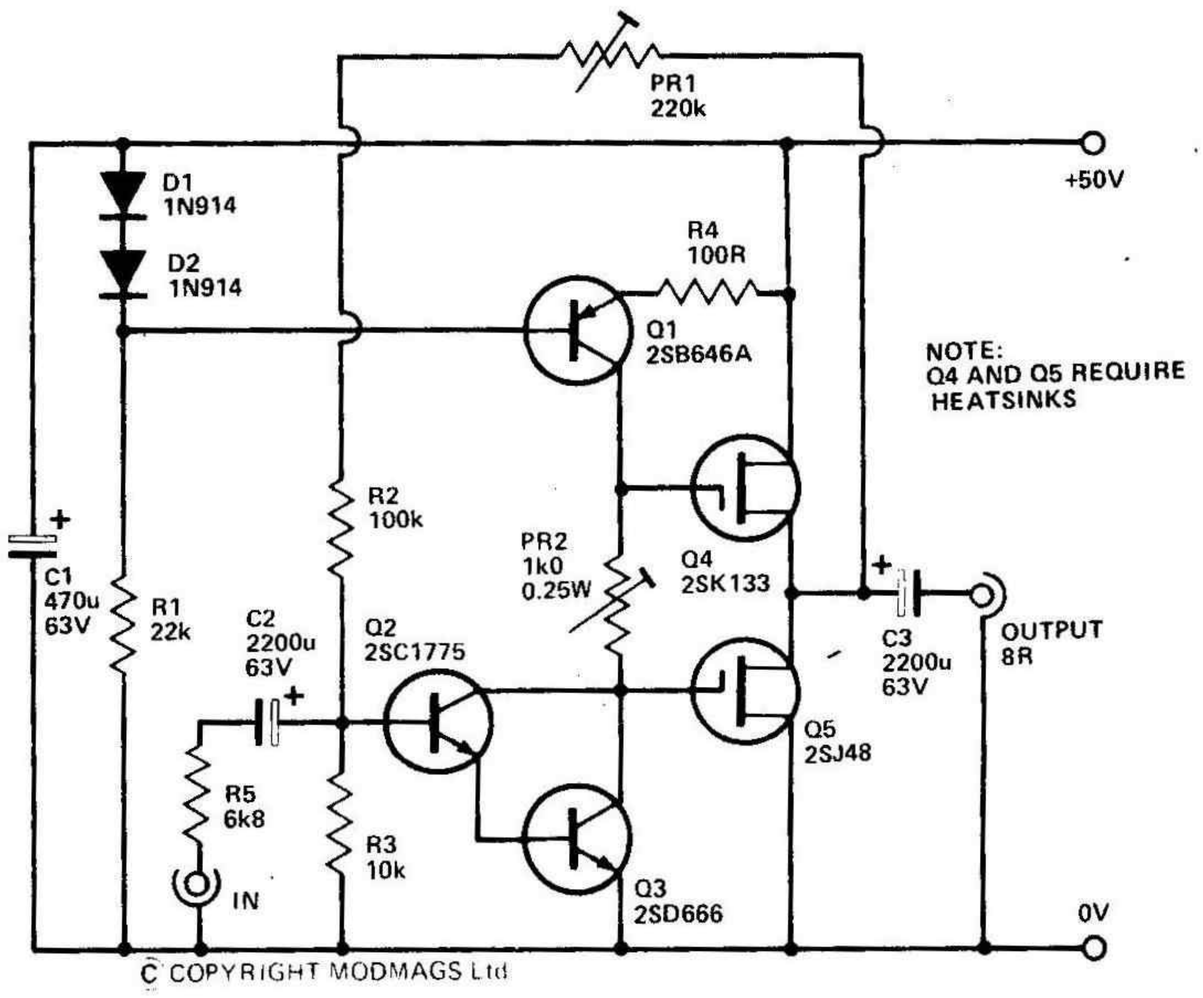Before initially connecting the supply to the circuit, set PR1 at about half maximum resistance. PR1 is then adjusted to give half the supply voltage at Q4 and Q5 source terminals and PR2 is advanced to give the circuit a quiescent current consumption of approximately 100 mA. The circuit has an input sensitivity of about 500 mV into 6k8



for full output. Current consumption is about 800 mA RMS at 20 W RMS output and almost 1 A with an output of 30 W RMS. The transistors are available from Ambit International.


Call Charge Reminder

The idea of this simple circuit is to give the user some idea of the number of units that are being accumulated while a telephone call is in progress. It is not intended to give a readout of the number of units, but instead gives a warning (clicking) sound each time an extra unit is accumulated. This enables a very simple and inexpensive circuit to be used and is effective in that it prevents the user from losing track of time.

A CMOS version of the 555 timer device (the ICM7555) is used as the basis of the unit. Using the CMOS version has the advantage of giving a much lower current consumption (about 100 uA). Before starting to dial the required number the unit is switched to the standby mode using SW1. This connects power to the circuit, but the 555 astable is blocked from operating properly by R1 which holds timing capacitor C2 into a charged state.

When the call is answered, SW1 is switched to the on position and R1 is then disconnected so that the unit is able to function normally. However, the astable cycle does not start at the normal point with C2 charging from zero. Instead, C2 is rapidly discharged to one third of the supply voltage through R11 and IC1 and then starts to charge again. This is important, since the initial cycle of the circuit would otherwise be significantly elongated (an effect that occurs with virtually all astable circuits).

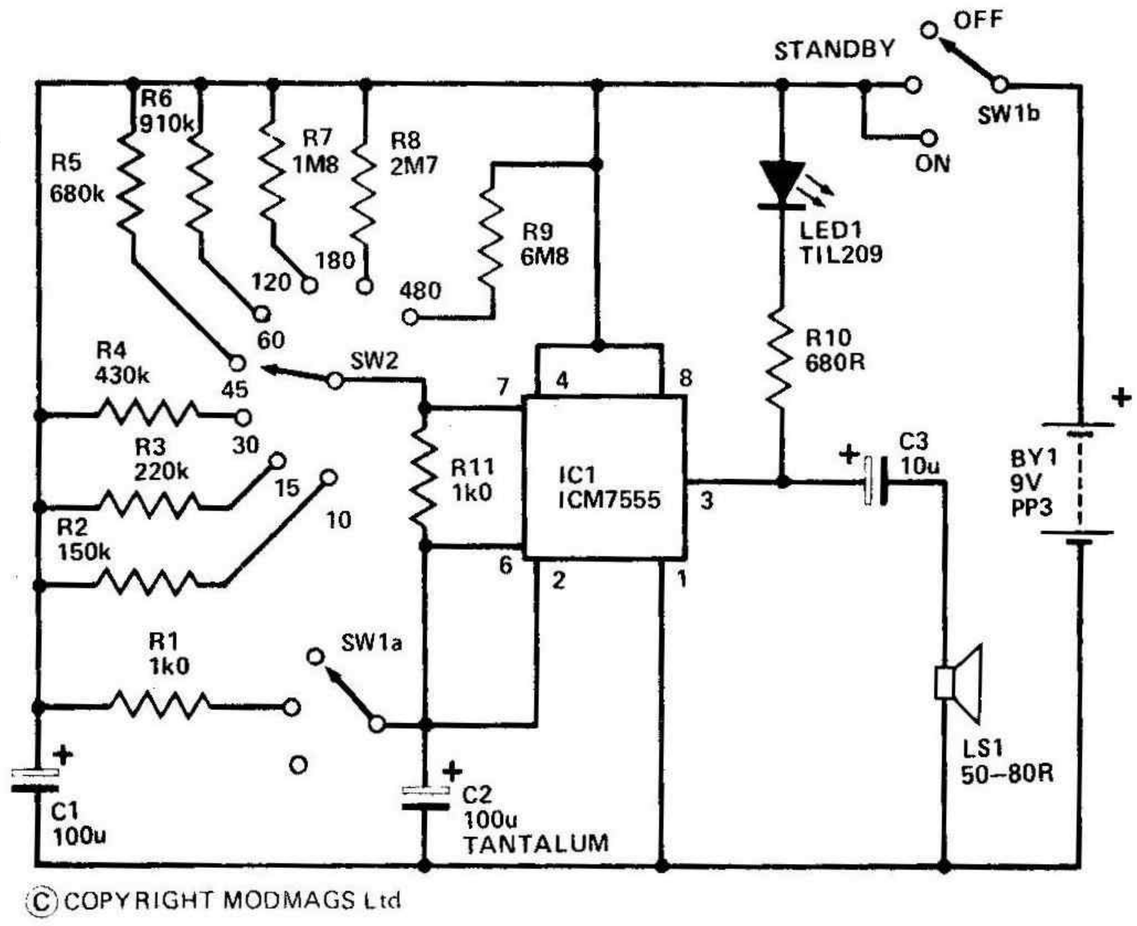
The operating frequency of the unit is controlled by SW2 and the series of timing resistors (R2-9). The telephone dialling instructions booklet should be consulted to ascertain the time per unit of the call you are about to make and SW2 is then set to the appropriate time. The output of IC1 is normally high, but at the end of each cycle it briefly



goes low, giving a clicking sound from LS1 and giving a brief flash from optional indicator LED 1. Each click, including the one that occurs as the unit is switched to the on position, indicates an extra unit has been accumulated.

VIDEOTONE

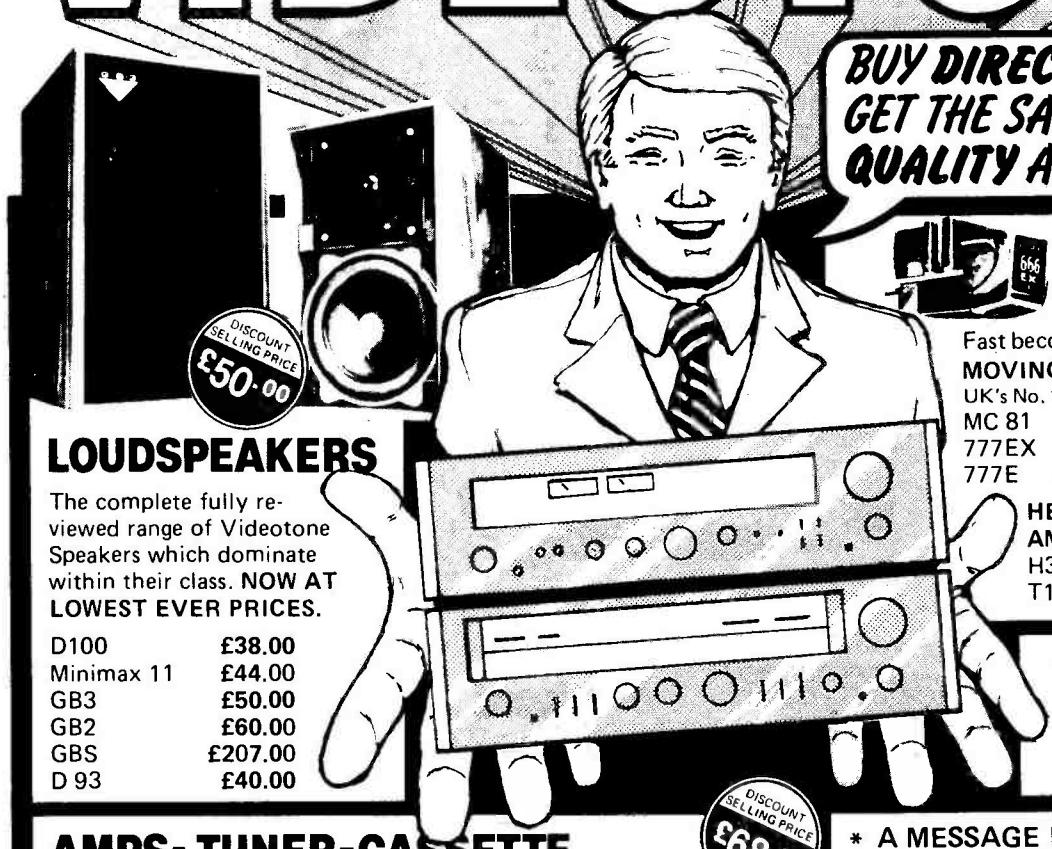BUY DIRECT FROM US AND GET THE SAME HIGH QUALITY AT LOW PRICES!



LOUDSPEAKERS

DISCOUNT SELLING PRICE £50.00

The complete fully reviewed range of Videotone Speakers which dominate within their class. **NOW AT LOWEST EVER PRICES.**

D100	£38.00
Minimax 11	£44.00
GB3	£50.00
GB2	£60.00
GBS	£207.00
D 93	£40.00

CORAL CARTRIDGES

Fast becoming one of the top names

MOVING COIL UK's No. 1 Cartridge		MOVING MAGNET	
MC 81	£48.87	555SX	£7.28
777EX	£35.00	555E	£14.22
777E	£25.00	666E	£32.48

HEAD AMP		HEADSHELLS	
H300	£51.75	S100	£6.00
T100	£24.75	S101	£7.00
		S200	£4.00

TURNTABLES

Sansui SR222 Mk2	£69.00
Sansui P50S	£69.00

AMPS- TUNER-CASSETTE

DISCOUNT SELLING PRICE £68.00


DISCOUNT SELLING PRICE £75.00

30 watt amp MC input SA4 130	£75.00
Stereo Tuner ST 4120	£68.00
Cassette full features SC 4200	£95.00
50 watt amplifier WA7700	£77.00
20 watt amplifier LA2020	£58.00

This new range of Electronics from Videotone redefines the words quality and value for money to a new high.

MICROPHONES

MU 105-22	£29.30
MU 105-12	£22.25
MU 25 C	£17.39

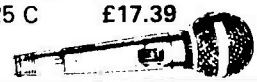

HEADPHONES

Superbly made with top flight performance

HP90	£12.65
HP80	£9.69



* A MESSAGE FROM VIDEOTONE *

Dear Customer

You will find that the products advertised on this page are the best possible value for money. They are only low in price because we have eliminated large amounts of selling costs that other brands have to suffer. These savings are passed directly onto you. We have full brochures on any specific item you may be interested in and a competent realistic staff of engineers at our London Showrooms to help you in your choice. Our consumer protection packages are comprehensive and we offer every form of financing you may require. We carry out our own servicing and are dedicated to giving **Value for Money.** We are confident our products are unbeatable. You may purchase with confidence because our Engineers have specially selected them from competitive sources throughout the world and we import them directly ourselves. **Remember, you have 21 days trial period on all products. That is the measure of our confidence.**

Cliff Hardcastle, Managing Director.



Quality plus value ~ always

VIDEOTONE

ALL PRICES INCLUDE VAT

ALL PRODUCTS ON DISPLAY & CONTINUOUS DEMONSTRATIONS

98 CROFTON PARK ROAD
LONDON SE4
TEL: 01-690 8511/2

SEND FOR OUR LATEST FREE BROCHURE
AND DETAIL LIST OF LOCAL SALES OUTLETS IN THE U.K.

NAME _____

ADDRESS _____

_____

ET

Get a great deal from Marshall's

CRIMSON ELEKTRIK HI FI MODULES		
CE 608	Power Amp	£20.09
CE 1004	Power Amp	£23.43
CE 1008	" "	£26.30
CE 1704	" "	£33.48
CE 1708	" "	£33.48
CPS 1	Power Unit	£19.52
CPS 3	" "	£23.52
CPS 6	" "	£30.00
CPR1	Pre Amp	£32.17
CPR1S	" "	£42.52

SINCLAIR INSTRUMENTS

Digital Multimeter
PDM35 £ 34.50
" " DM235 £ 52.50
" " DM350 £ 72.50
" " DM450 £ 99.00

Digital Frequency Meter
PFM200 £ 49.80

Low Power Oscilloscope
SC110 £139.00

TF200 Frequency Meter
£145.00

TGF105 Pulse Generator
NEW £ 85.00

LCD Multimeter
TM351 £99.00

LCD Multimeter
TM352 £49.95

Prescaler
TP600 £37.50

ILP HI FI MODULES

Power Amplifiers
HY30 £ 7.29
HY60 £ 8.33
HY120 £17.48
HY200 £21.21
HY400 £31.83

Pre Amplifiers
HY6 £ 6.44
HY66 £12.19

Power Supplies
PSU30 £ 4.50
PSU36 £ 8.10
PSU60 £13.04
PSU70 £13.04
PSU180 £21.34

MULTIPLEX NICKEL CADMIUM CELLS


Type S101 (HP4) £0.98
Type SubC (HP11) £1.75
Type SubD (HP2) £1.95
Friwo Chargers for above
Penlight 4: accommodates 1–4 size HP7 £5.50
Combibox FW611: accommodates HP7, HP11 £13.25

NOTE ALL PRICES NET. EXCLUDING VAT. POSTAGE/PACKING

New

Presensitised PC Boards, Developer. U.V. units.
Toyo miniature Fans 230v AC £9.95
Mini Metal Detector/Voltage Tester for locating cable under plaster £9.95
Flow/Speed Sensors for monitoring fuel consumption electronically in vehicles

Just one ot the exciting Leader range

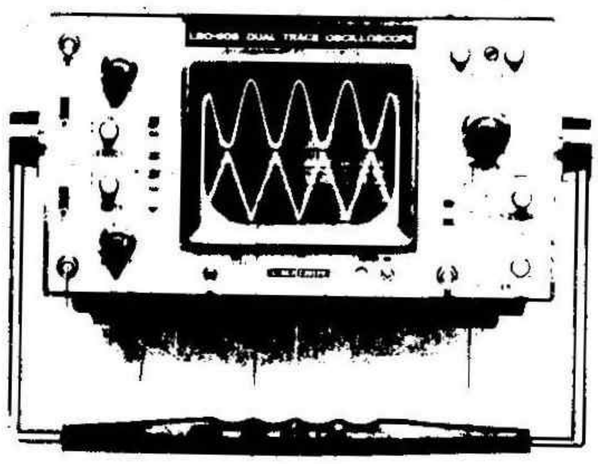

LB0508A OSCILLOSCOPE With 20MHz DC bandwidth and 10 mv input sensitivity on a 5" screen this universal oscilloscope is suitable for a wide range of applications.

£299 + VAT

Send SAE for details of full range.

Marshall's 80/81 catalogue is now available by post, UK 75p post paid Europe 95p post paid: Rest of world £1.35 post paid.


A. Marshall (London) Ltd., Kingsgate House,
Kingsgate Place, London NW6 4TA.
Industrial Sales: 01-328 1009
Mail Order: 01-624 8582 24hr service.

Also retail shops: 325 Edgware Road, London W2.
40 Cricklewood Broadway, London NW2. 85 West Regent St., Glasgow. 108A Stokes Croft, Bristol.

QUALITY DOES NOT HAVE TO COST VERY MUCH!

ALL PRICES INCLUDE VAT

BECKER Hi-Fi Speakers

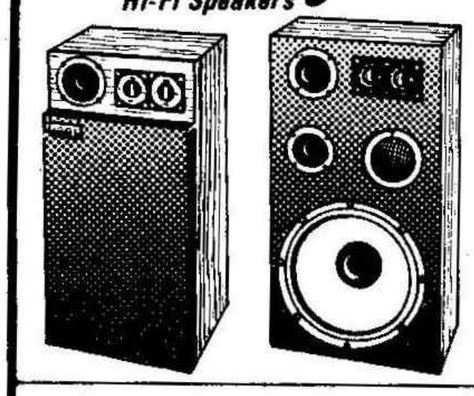


All models multi-speaker systems

With controls, attractive woodgrain finish. RMS ratings for 8 ohm.

12.60 12" 4 speaker system 60 watts 26½" × 14½ × 11" .... **£115.95** pair

15.90 15" 5 speaker system 90 watts 28" × 17½" × 11½" ..... **£135.95** pair
(UK c/p **£12.00** pair)

ON DEMONSTRATION TO CALLERS

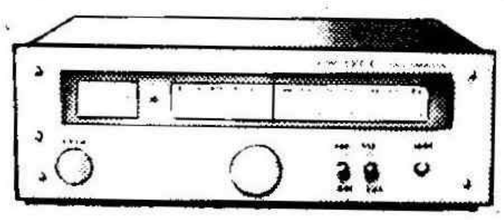

SCOTT T516 STEREO FM/AM TUNER

HIGH QUALITY STEREO FM/AM TUNER BY SCOTT OF USA.

Overall size 5" x 14½" x 12". Brand new and fully guaranteed at a special low price.
(C/P £1.55)

£38.95

On demonstration for callers.




JVC BELT DRIVE TURNTABLE

JVC TURNTABLE WITH FREE AUDIO TECHNICA AT100 STEREO CARTRIDGE.

- ★ 'S' shaped tone arm
- ★ Belt drive
- ★ 12" Platter ★ Calibrated counter-balance weight
- ★ Anti-static device

Size 12¾" x 15¾"
(C/P £1.55)

£29.95

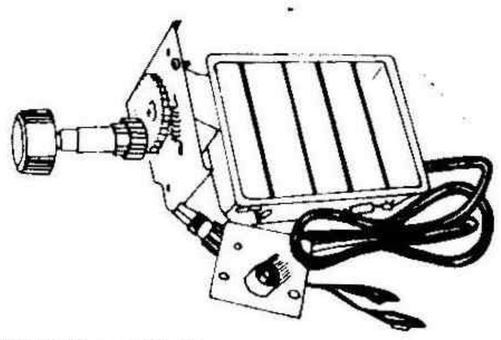

1000's SOLD

TV SOUND FROM YOUR HI-FI

High quality TV sound converter plugs into aerial socket of your FM tuner. 9 volt battery operated (battery not supplied). Nothing to look at . . . but just listen!

★ Fitted slow-motion drive

(UK Post etc. 65p)

On Demonstration for callers.


New model (appearance may differ from illustration)

£8.50



SEAS SPEAKER KITS

8 ohm

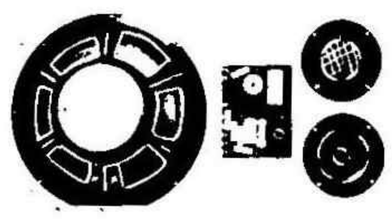

Professional sound hi-fi speaker kits with high sensitivity (89-92dB). Extended frequency response ('223' 50-20kHz, '253' 35-25kHz). Designed and made in Scandinavia to the highest quality. All supplied with complete cabinet plans, tweeters/crossovers/leads etc. ★ On Demonstration to callers.

- ★ **Hi-Fi 223.** 30/45 watt 3 speaker 8" system ..... **£43.50 pair**
- ★ **Hi-Fi 253.** 60/100 watt 3 speaker 8" system ..... **£34.50 each**
- ★ **Hi-Fi 403.** 60/100 watt 3 speaker 10" system ..... **£44.50 each**
- ★ **Hi-Fi 603.** 80/150 watt 3 speaker 12" system ..... **£64.50 each**

(UK C/P £2.50)

COMPLETE RANGE OF SEAS CHASSIS SPEAKERS ETC ALWAYS IN STOCK ALSO STOCKISTS FOR AUDAX, GOODMANS, KEF, PEERLESS ETC.

PIEZO TWEETERS



New low prices

Clean sound, very low distortion tweeters. No crossover required. Suitable up to 100 watts – more in series.

1 Mid-range horn for disco/pa/groups .. **£6.95**
2 Tweeter horn for hi-fi/disco/pa **£5.50**
3 Popular hi-fi and disco **£4.40**
4 Flat type hi-fi **£3.50**

On Demonstration to callers.
C/P 50p (up to 4 items)

STEREO ACCESSORIES

- ★ GE1305 Hi-Fi Frequency Equaliser .. **£62.95**
- ★ APM 200 Peak programme meter (twin scale) **£39.95**
- ★ MS3219 Twin Scale audio output meter **£12.95**
- ★ MC350 Tape echo chamber **£59.95**

FREE CATALOGUE

Large range of speakers/stereophones/microphones/mixers/PA equipment etc – and much more!
Plus huge range of test equipment.
ALL PRICES INCLUDE VAT
SEND LARGE 20p SAE

PRICES CORRECT AT 1.2.81.

AUDIO ELECTRONICS Cubegate Limited

301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND.
TELEPHONE 01-724 3564 **OPEN 9-6 Mon-Sat**

ORDER BY POST OR TELEPHONE WITH BARCLAYCARD/ACCESS
OR CALL IN AND SEE FOR YOURSELF

THE LEPTONS

No, not more aliens for Captain Kirk to deal with, but a family of subatomic particles. Lepton means 'light particle', but some of them aren't, and they may not be made up of quarks either. Confused? So are the particle physicists. A.S. Lipson explains.

Once upon a time, physics was simple (well, nearly. . .). Subatomic physics especially, seemed to be fairly clear cut. Around the turn of the century, J. J. Thomson had discovered the electron, which carried a negative electrical charge. A few years later, Max Planck had stated the existence of the photon, or 'particle of light'. There was one other particle; the proton, which was positively charged, and had a mass about 1836 times that of the electron. The proton and electron were known to exist within atoms. That was the entire list of subatomic particles, and it looked as though everyone would live happily ever after.

Then things got complicated. In the 1930s and 40s, more particles started turning up, and they have continued to do so to the present day. First there were the neutron and mu-meson. Then there were the pi-mesons, or pions (three different ones!), the Kaons, the positron, the anti-proton, the anti-neutron, the anti-muon, a few different particles called Sigmas, and no less than four variations on a type of particle known as a neutrino (of which we will see more later). . . . The list seemed endless.

Eventually, the physicists managed to start simplifying the situation. It became apparent that many particles — the proton and neutron, for example, might be made up of various combinations of a few even more basic particles — called quarks. Instead of having all those different particles, maybe everything could be explained in terms of just three or four quarks. There was a particular group of particles, however — collectively known as 'leptons' — which did not seem to be made up of quarks. It's these particles which concern us in this article.

Light Matter

The word lepton comes from the Greek word 'lepto', meaning light, since the earliest leptons discovered were particles with relatively little mass. It is now known that not all leptons are light, after all, but the name has stuck.

The first lepton to be discovered was the electron, which has a negative electric charge of 1.6×10^{-19} coulombs, and a mass of 9.1×10^{-31} kg. (It will be convenient for the purposes of this article to refer to particles as having a mass of so many times the mass of the electron, so for the moment we can say simply that an electron has mass 1. Using this scale, a hydrogen atom has a mass of nearly 2000). The next particle to enter our story is the neutron. The neutron is not a lepton, but its relationship with the electron leads us to the next important point — the neutrino.

The neutron is a fairly massive particle; on the electron's scale it has a mass of 1839. It carries no net electrical charge — hence its name. One important feature of the neutron is that, like many particles, it is unstable. An isolated neutron will tend, after an average time of 15 minutes or so, to disintegrate, producing a proton (mass 1836) and an electron. You will notice that, since the neutron carries no charge, when it turns into a positively charged proton, it is necessary that an equal and opposite charge — the electron — is created at the same time, so that the total charge remains zero. All well and good, then; sometimes a neutron spontaneously changes into a proton and an electron.

Particle	Mass (x electron mass)	Charge (in coulombs)	Lifetime	Lepton
Proton	1836	1.6×10^{-19}	Stable	No
Neutron	1839	Zero	About 15 min	No
Electron	1	-1.6×10^{-19}	Stable	Yes
Electron-neutrino	Very small	Zero	Stable	Yes
Muon	207	-1.6×10^{-19}	2.2×10^{-6} S	Yes
Muon-neutrino	Very small	Zero	Stable	Yes
Tau	About 3500	-1.6×10^{-19}	Less than 3×10^{-12} S	Yes
Tau-neutrino	Very small	Zero	Stable	Yes

Table 1. Particles discussed in the article (antiparticles left out for simplicity).

Think Of A Particle. . .

Unfortunately, it isn't quite that simple. You see, when this reaction was first observed to happen, physicists weren't too happy with it. It seemed that certain physical laws which had always held before weren't holding any more. But then it was spotted that all the laws *would* be holding, if only there was another particle taking part in the reaction. This particle, although it had never been observed, was christened the 'neutrino', from Italian words meaning 'little neutral one' — since the neutrino, if it existed, would have little or no mass and be electrically neutral. The fact that the neutrino had never been detected was easily explained — all the methods used to detect subatomic particles depended on their having measurable masses and charges. The neutrino had neither. In fact, neutrinos react with other matter very rarely. If a beam of neutrinos was aimed at a concrete slab a light-year thick, by far the majority would get through easily!

You may think it a little bit far-fetched that scientists would actually *invent* a new particle — one that had never been found — just to explain why some physical laws didn't seem to work. Why not just change the laws? Well, all through the history of science, it has invariably turned out that the simplest explanation of a set of events is the correct one. In this case, it was simpler to keep the old, simple set of laws and invent a new particle, than it would have been to invent a whole new set of more complicated laws. This, at least, was how the physicists reasoned, and as it happened, they were right! In 1956, twenty-five years after its original invention, the neutrino was discovered! In fact, it was found that the particle produced when a neutron

turned into a proton and an electron was not a neutrino, but its 'antiparticle', the antineutrino. This, however, was a small point, and the discovery of the actual existence of the neutrino is regarded as a major triumph for theoretical physics, which had predicted its existence all those years before.

So now our family of leptons contains two particles; the electron and the neutrino (and their antiparticles — the 'positron' and the 'antineutrino' respectively). This wasn't the case for long, though. In the late 1930s, another lepton was discovered in cosmic rays high up in the atmosphere. This particle was called the mu-meson, or muon for short. It was given the symbol μ , the Greek letter mu. There are only two real differences between the muon and the electron. Firstly, the muon has a much greater mass, about 207 times that of the electron; and secondly, the muon, like the neutron, is unstable, although on average it has a much shorter lifetime. Under normal conditions, a muon will disintegrate after only about one five hundred thousandth of a second, turning into an electron and producing two neutrinos. Apart from these two differences, however, the electron and muon are strikingly similar. For instance, both carry the same charge, -1.6×19^{-19} coulombs. The anti-muon carries a positive charge of the same magnitude, just as does the anti-electron, or positron. The similarity between the two particles has been puzzling physicists ever since the discovery of the muon. But there's one more thing puzzling them, too. . . .

Identical Twins?

It was found that many of the reactions involving electrons also involved neutrinos. Similarly, many reactions involving muons also involved neutrinos. The neutrinos that reacted along with electrons didn't seem to be the same as those which reacted along with muons. Apparently, there were two types of neutrinos. If you examined a neutrino from a reaction involving an electron, you would find that it could not be made to take part in a reaction involving a muon. Similarly, a neutrino from a muon reaction could not be made to react with an electron. Neutrinos, then, had to be divided into two groups; 'electron neutrinos' and 'muon neutrinos'. What is the difference between the two types of neutrino? The somewhat embarrassing answer (for a physicist) is that, even today, nobody really knows. They *are* different, but we don't know why. All we do know is that reactions involving electrons tend also to involve electron neutrinos, whereas reactions involving muons tend to involve muon neutrinos. When a reaction involves both electrons and muons, both types of neutrinos are involved. For instance, when a muon turns into an electron, a muon neutrino and an electron antineutrino are produced (see Fig.1b). The two types of neutrinos are like almost-identical twins — you can't tell the difference just by looking at them, but only by looking at the different ways they behave. And, of course, each of the two types of neutrino has its own anti-neutrino, as well.

Three's A Crowd. . . .

As if the situation wasn't already complicated enough, experiments conducted in the last five years or so indicate (wait for it) that there's yet another lepton. This one, called the tau particle (and given the symbol τ — the Greek letter tau) is, again, just like the electron and muon, but with a still greater mass (about 3500 times the mass of an electron — nearly as massive as a molecule of hydrogen! As far as subatomic particles go, this is well into the heavyweight league), and with a still shorter average lifetime before it distintegrates into other particles. As yet, experiments are not conclusive, but it seems that the tau particle also has its own pair of neutrinos — the tau neutrino and the tau antineutrino. Unsurprisingly, these neutrinos refuse to take part in electron or muon reactions, unless a tau particle is also involved.

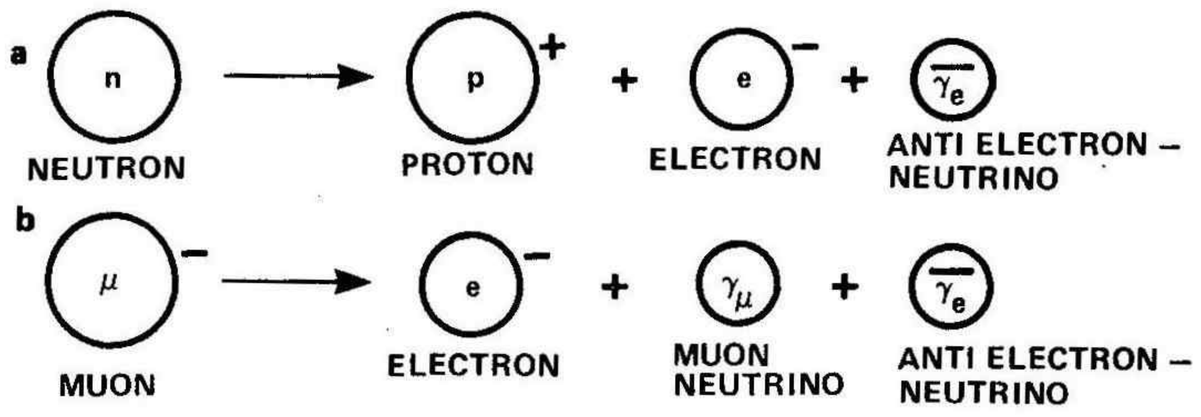


Fig. 1. (a) Neutron turning into proton and electron, giving off anti-neutrino. (b) Muon disintegrating to produce electron, muon-neutrino and anti electron-neutrino.

Any Answers?

So that is the situation at the moment. There are three known leptons which carry electric charge — the electron, the muon and the tau (each also having a positively charged antiparticle) and correspondingly, three sets of a pair of neutrinos — the electron-, muon- and tau-neutrinos, with their antiparticles. There are a lot of questions still to be answered. Are there any more leptons, like the electron, muon and tau, but with still greater masses, and shorter average lifetimes? If there are, do they also have their own neutrinos? And for that matter, what is it that makes, say, a muon neutrino different from a tau neutrino? There's one more major problem too. . . . .

A Massive Question

It has been known for several decades now that neutrinos have very little, or perhaps no mass at all. In fact, there has been a tendency among physicists to believe that the latter is the case — that the neutrino has no mass, although this has never been proved. Very recent experiments, however, make it look as though perhaps the neutrinos do have masses after all. If this is so, then physicists may have to rethink a lot of theories. Do neutrinos have mass? We shall just have to wait and see and maybe everyone *will* live happily ever after. . . . . **ETI**

CIRCUIT DIAGRAMS/OVERLAYS/ FLOWCHARTS!

Do you require professionally drawn Circuit diagrams, Overlays, Flowcharts etc. drawn from your own designs? MM Design & Print offer a quick, accurate and cheap Technical Illustration and lettering service to readers of ETI. We illustrate anything from a single chip amplifier to a colour television circuit design, with finished artwork supplied to your specification. For further details please ring Paul Edwards, on 01—437 1002/7 extension 29, or write to the address below.

Part of the Modmags Group.

145 Charing Cross Road,
WC2H 0EE

KNOW YOUR ZX80

With LINSAC products for the Sinclair ZX80



NOW ONLY £7.95

THE ZX80 COMPANION
(Second Edition)
Maunder, Logan and Trotter

ISBN 0 907211 00 3. Price £7.95 incl. UK postage.

This best selling manual on the Sinclair ZX80 covers ZX80 BASIC, hardware and programs and has a detailed explanation of the ZX80 Monitor, routines and entry points. A routine for generating moving displays is also included.

Ch.1 - Operating the ZX80.
Ch.2 - Theory of Computers
Ch.3 - ZX80 BASIC
Ch.4 - The ZX80 Monitor
Ch.5 - Construction and Hardware
Ch.6 - ZX80 Programs
App.1 - Comparison of Z-80 Opcodes and ZX80 Characters.
App.2 - The 8K ROM.

For a cassette of ten programs from the Companion add £4.95.

The ZX80 Monitor A complete assembly language listing of the ZX80's 4K Monitor, with annotations - Price £10.00 incl. UK postage.

Cassette Software

All LINSAC program packs are on single C12 cassettes with printed run instructions. All run on 1K ZX80's unless otherwise stated. Price £7.95 per pack incl. UK postage.

GAMES PACK 1	–	Three Towers, Number Guessing, Mastermind, Sketcher, Hurkle, Nim, Symbol Simon.
GAMES PACK 2	–	Nine Lives, The Maze Game, Plain Sailing, OXO, Chinese Puzzle, Tower of Hanoi, Battleships.
GAMES PACK 3	–	(2K+) – Fruit Machine, Four-in a line, Zombies
EDUCATION PACK 1	–	Maths Drill, Dot Recognition, Musical Notes, Spelling Quiz, Day Finder.
EDUCATION PACK 2	–	Graph Plotter, Prime Factors, Number Bases, Bar Charts, Statistics.
EDUCATION PACK 3	–	(2K+) – CAL Quiz Package with three sample data sets
UTILITY PACK 1	–	Memory Display, Hex Code Monitor, Renumber, Memory Search.

LINSAC 68 Barker Road, Linthorpe,
Middlesbrough, Co. Cleveland TS5 5ES

Professional ASCII Keyboards

ONLY £29.95 + VAT
ADD POST £1.50
SCOOP



The 'APPLE' Computer Keyboard

- 52 KEY 7 BIT ASCII CODED
- POSITIVE STROBE. +5V – 12V
- FULL ASCII CHARACTERS
- PARALLEL OUTPUT WITH STROBE
- POWER LIGHT ON CONTROL
- NATIONAL mm 5740 CHIP. TTL OUTPUT
- SUPERBLY MADE. SIZE 12x5.5x1.5ins
- BLACK KEYS WITH WHITE LEDGENS
- ESCAPE. SHIFT. RETURN & RESET KEYS

Complete with CIRCUIT & DATA
Ideal for use with TANGERINE
TRITON
Ex-Stock from HENRY'S TUSCAN
APPLE & most computers

This is definitely the **BEST BUY**
Supplied **Brand NEW** in manufacturers original jacking (ANTI-STATIC)
Just post remittance total £35.95 (incl. VAT & Post)

HENRY'S
Computer Kit Division
404 Edgware Road, London, W2, England
01-402 6822

MAIL ORDER ONLY

DELTA TECH & CO.

62 NAYLOR ROAD, LONDON, N20 0HN
Tel: 01-445 8224
Prices include VAT. Add 35p P&P
Minimum Access order £3

SWITCHES
SLIDE 1A/250V DPDT 12p
TOGGLE 3A/250V DPDT 35p
ROTARY 2A/250V DPST 35p
CERAMIC CAP (50V)
33 pF to 4700 pF 4p
POLYSTYRENE CAP (50V)
10 pF to 1000 pF 5p
POLYESTER CAP (100V)
1 nF to 68 nF **6p**; 100 nF 150 nF **8p**; 220 nF **9p**; 330 nF **10p**; 470 nF **11p**; 680 nF **7p**; 1uF **7p**; 1.5 uF **7p**; 2.2 uF **20p**; 3.3uF **15p★**; 4.7uF: **15p★**
ELECTROLYTIC CAP (uF/V)
1/25 to 47/25 **8p**; 68/25 **7p**; 100/35, 150/25 **8p**; 160/25: **5p★**; 200/12: **6p**; 250/12 **7p**; 220/25 **10p**; 470/25, 500/30 **12p**; 470/40 mini **15p**; 640/16: **8p**; 1000/10 **10p**; 1000/40 **24p**; 1500/25: **24p★**; 2200/6.3 **12p**
ZENER DIODES (400mW)
2V7 to 33V **8p**
VEROBOARDS (.1" copper)
2.5" x 5" 65p
3.75" x 5" 80p
RESISTORS (5% E12)
10 Ohms to 10Mohms 2p
PRESETS (.15W HORIZONTAL)
100 Ohms to 2 Mohms 7p
POTENTIOMETERS (¼W)
Linear & Log Scales
4K7 to 2M2 33p

LINEAR CIRCUITS

709-8	28p	LF351N	44p
710-14	35p	LF356N	85p
741-8	22p	LM301AN	30p
747-14	50p	LM30BN	★38p
748-8	35p	LM318N	120p
CA3018	70p	LM318H	120p
CA3028A	85p	LM324N	57p
CA3046	50p	LM339N	52p
CA3054N	40p	LM348N	90p
CA3080	78p	LM377N	175p
CA3090AQ	200p	LM380N	90p
CA3130E	95p	LM381N	★120p
CA3140E	48p	LM382N	120p
		LM1310N	115p
		LM1458N	★40p
		LM3900N	★50p
		LM3909N	75p
		MC1496P	80p
		NE531	120p
		NE555	26p
		NE556	★45p
		NE566	140p
		SN76023N	120p
		SN76115N	★80p
		TBA641B	200p
		TBA800	75p
		T8A 810S	110p
		ZN414	90p
		ZN1034E	220p

DIODES

OA47	8p
OA91	7p
OA200	5p
OA202	6p
1N916	4p
1N4148	4p
1N4001/2	4p
1N4003	5p
1N4004/5	6p
1N4006/7	8p
1N5400	11p
1N5401	12p
1N5402	13p
1N5404	14p

BRIDGE RECTIFIERS

WO2M	18p
WO6M	20p
1A/50V	20p
1A/200V	23p
1A/400V	28p
1A/600V	29p
1A5/75V	22p
2A/50V	30p
2A/100V	32p
3A/100V	60p
3A/600V	75p

THYRISTORS

4A/300V	20p
4A/400V	40p
12A/100V	30p
8A/400V	75p

TRIACS

3A/400Vp	58p
10A/600Vm	70p
30A/600Vm	80p

DIAC

ST2	24p

VOLTAGE REGULATORS

7805	70p
7812/15	70p
7818/24	70p
7905	80p
7912/15	80p
7918/24	80p

OPTO/ELECTRONIC

2N5777	40p
OCP71	65p
ORP12	80p
DL704	110p
DL707	110p

LEDs:

0.125" & 0.2"	
Red	12p
Green	16p
Yellow	16p
Rect. Green	25p
0.125" Clip	3p
0.2" Clip	3p

DIL SOCKETS

8 pin	★8p
14 pin	★9p
16 pin	★10p
18 pin	16p
22 pin	20p
24 pin	21p
28 pin	25p
40 pin	35p

CMOS AE

4000	16p
4001B	17p
4002	16p
4006B	75p
4007	★16p
4008	85p
4009	42p
4010	48p
4011B	20p
4012	25p
4013B	45p
4014/5B	80p
4016	44p
4017	70p
401B	85p
4019	50p
4020B	100p
4021/2	95p
4023	22p
4024B	55p
4025	20p
4027	50p
402B	70p
4029	90p
4030	55p
4035	110p
4041	85p
4042	80p
4043/4	99p
4047	105p
404B	60p
4049	50p
4050B	50p
4066	60p
4068/9	22p
4070B/1	22p
4072/3	22p
4081/2	26p
4086	80p
4510	100p
4511B	100p
4516/8	105p
4520/8	105p

TTL

7400/1	16p
7402/3	16p
7404/5	16p
7406	18p
7407	25p
7408	22p
7409	13p
7410	13p
7411/2	17p
7413	30p
7414	45p
7416	20p
7417	25p
7420	15p
7421	30p
7422	26p
7427	20p
7428	28p
7430	16p
7432	28p
7433	38p
7437	14p
743B	18p
7440	13p
7441	52p
7442	32p
7443	60p
7444	100p
7445	64p
7446	65p
7447A	50p
7448	52p
7450	10p
7451/3	13p
7454	10p
7460	13p
7470	20p
7472	19p
7473	★18p
7474	28p
7475	28p
7476	30p
7480	32p
7485	140p
7486	18p
7490	28p
7491	57p
7492/3	30p
7494	50p
7495	40p
7496	37p
7497	200p
74100	60p
74105	43p
74107	22p
74109	34p
74110	40p
74118	84p
74121	25p
74122	30p
74123	50p
74125/6	42p
74132	65p
74141/5	46p
74150	85p
74151	65p
74153	43p
74154	66p
74155	46p
74156	42p
74157	38p
74160	57p
74161	55p
74162/3	60p
74164/5	56p
74166	95p
74173	110p
74174/5	55p
74176/7	70p
74180	35p
74181	80p
74182	45p
74190	50p
74191	90p
74192/3	50p
74194	70p
74195	68p
74196	95p
74197	45p
74198	120p
74199	90p

TRANSISTORS

AC126/7	22p
AC128	20p
AC153	25p
AC176	22p
AC187/8	22p
AC187K	30p
AD149	40p
AD161/2	28p
AF114	30p
AF124	35p
AF125/6	35p
AF127	35p
BC107/8	10p
BC109	10p
BC140	20p
BC142/3	30p
BC147/8	10p
BC149	10p
BC157/8	12p
BC159	12p
BC169C	13p
BC171	10p
BC173	8p
BC177/8	16p
BC179	16p
BC182	10p
BC182L	★8p
BC183B	10p
BC184	10p
BC186	25p
BC187	15p
BC207/9	13p
BC212	10p
BC212L	★8p
BC213L	10p
BC214	10p
BC214L	★8p
BC238	18p
BC261B	23p
BC301/3	32p
BC328	17p
BC461	40p
BC477	35p
BC478	20p
BC479	23p
BC547/8	12p
BC549	12p
BC557/8	14p
BC559	14p
BCY70	18p
BCY71/2	18p
BD115	35p
BD121/3	50p
BD124	50p
BD131/2	40p
BD135 to 8D140	40p
BF179	19p
BF180	34p
BF181	8p
BF183	34p
BF184/5	25p
BF194/5	12p
BF196/7	12p
BF198	10p
BF200	23p
BF224B	14p
BF244B	★22p
BF258	28p
BF259	40p
BFR39	30p
BFR40	20p
BFR79	32p
BFR80	20p
BFX29	25p
BFXB4	25p
BFX85/6	20p
BFX87/B	25p
BFY50/1	20p
BFY52	22p
BRY39	50p
BSX19	12p
BSX20	22p
BU205	150p
BU208	210p
MJ2955	110p
MJE340	52p
MJE3055	80p
MPF102	45p
MPF104/5	40p
MPF106	45p
OC28/35	50p
TIP29	40p
TIP29B	42p
TIP30	40p
TIP30B	42p
TIP31	30p
TIP31A	31p
TIP32	40p
TIP33	65p
TIP33C	70p
TIP34A	75p
TIP35B	200p
TIP36A	200p
TIP36B	210p
TIP41A	60p
TIP42A	60p
TIP2955	70p
TIP3055	★30p
ZTX107/8	12p
ZTX109	12p
ZTX300/1	14p
ZTX302/3	18p
ZTX304	23p
ZTX500/1	15p
ZTX502	20p
ZTX504	24p
2N696/7	20p
2N698	20p
2N706	14p
2N914	20p
2N918	35p
2N1302/3	35p
2N1304	35p
2N1306	30p
2N1308	35p
2N1613	25p
2N1711	13p
2N1893	25p
2N2217	18p
2N2219	23p
2N2222A	23p
2N2369	17p
2N2484	25p
2N2646	46p
2N2904/5	21p
2N2906/7	21p
2N2926G	10p
2N3053	20p
2N3054	30p
2N3055	45p
2N3442	140p
2N3702 to 2N3711	11p
2N3772	★70p
2N3773	250p
2N3819	21p
2N3820	40p
2N3823	70p
2N3866	65p
2N3903/4	15p
2N3906	15p
2N4037	45p
2N4058	10p
2N4059	10p
2N4060	10p
2N4061	10p
2N5458	40p
2N5459	40p
2N6027	30p
3N128	50p

MINIMUM 25 PIECES EACH	4001B	15p	4016A	25p	7473	16p	1N4005	4.5p	ZD5V6	5p	BFY50	15p	CA3090AQ	70p	160 uF/25V	4p	WO6	19p
	4007A	13p	4017A	40p	7490	23p	1N4007	6p	ZD9V1	5p	TIP31A	22p	SN76115N	50p	640 uF/16V	4p	SO1	23p
	4011B	15p	7420	13p	OA91	5.5p	1N5404	10p	BF244C	14p	TIP3055	22p	33uF/40V	4p	WOO5	16p	**MANY MORE**	

GREENWELD

443A Millbrook Road Southampton SO1 0HX

All prices include VAT @ 15% — just add 40p post

THE SPECTACULAR 1981 GREENWELD Component Catalogue

Bigger and better than ever!!!

- ★ 60p discount vouchers
- ★ First Class reply paid envelope
- ★ Free Bargain List
- ★ Priority Order Form
- ★ VAT inclusive prices
- ★ Quantity prices for bulk buyers
- ★ Free Data Sheet

SEND 75p FOR YOUR COPY NOW!!

BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

ALL PACKS CONTAIN FULL SPEC. BRAND NEW MARKED DEVICES — SENT BY RETURN OF POST, VAT INCLUSIVE PRICES.

K001 50V ceramic plate capacitors. 5%, 10 of each value 22pF to 1,000pF, total 210. **£3.69.**
K002 Extended range 22pF to 0.1µF, 330 values **£5.53.**
K003 Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µ, 110 altogether for **£5.07.**
K004 Mylar capacitors, min 100V type 10 each all values from 1,000pF to 10,000pF. Total 130 for **£4.06.**
K007. Electrolytic capacitors 25V working small physical size. 10 each of these popular values 1, 2.2, 4.7, 10, 22, 47, 100µF. Total 70 for **£3.59.**
K008 Extended range, as above, also including 220, 470 and 1000µF. Total of 100 for **£5.05.**
K021 Miniature carbon film 5% resistors CR25 or similar. 10 of each value from 10R to 1M, E12 series. Total 610 resistors **£6.15.**
K022 Extended range. Total 850 resistors from 1R to 10M **£8.50.**
K041 Zener diodes 400mW 5% BZY88, etc. 10 of each value from 2.7V to 36V, E24 series. Total 280 for **£16.37.**
NEW K061 LEDs — 10 each red, green & yellow 3mm & 5mm, with clips. Total 60 LEDs for **£8.95**

BUZZERS, MOTORS & RELAYS

Z401 Powerful 6V DC buzzer, all metal construction. 50mm dia×20mm **85p.**
Z402 Miniature type buzzer, 6, 9 or 12V, only 22x15x16mm. Very neat **65p**
Z450 Miniature 6V DC motor, high quality type 32mm dia×25mm high, with 12mm spindle. Only **£1.**
A372 Audible Warning device — solid state circuit drives high efficiency transducer to give high output. Voltage reqd 4-18V. Can also be driven direct from TTL or CMOS. Module size 45×21×12mm. Comprehensive data supplied **£1.50**
W892 Heavy Duty 12V relay, ideal for car use — single 15A make contact. Coil 25R in sealed metal can with mounting bracket **85p.**
W890 DIL Reed relay SPCO 2.4-10V. 200R coil. Only **£2.20.**
FSRA60 Latching relay. 2 × 10A contacts, 1M, 1B. Coil is 250R, and rated 60V ac, but works on 12-24 DC. Solid Encapsulation with screw terminals makes it ideal for car use. **£1.20.**

REGULATED PSU PANEL

Exclusive Greenweld design — better spec. than anything on the market being offered at the price. Panel 110×82×33mm high contains all components including bridge rectifier and smoothing capacitor. Ready built and tested — just add a 30V 2A transformer and two pots for a fully variable voltage and current supply.

SPEC: Output voltage 0-28V
Output current 20mA-2A
Source Impedance OR1
Open circuit ripple 10mV

Send SAE for full details of the many ways this useful module can be used, together with price list of parts for various options. Only **£7.75**

1N4006 DIODES

Special purchase of 1A rects, Russian made. Packed in boxes of 300, **£8.50** per box; 4 boxes **£30.00;** 10 boxes **£75.00**

DISC CERAMICS

0.22uF 12V 9mm dia. Ideal for decoupling. 100 for **£2.75;** 1000 **£20.00.**
0.05uF 12V 15mm dia. 100 **£1.50;** 1000 **£12.00.** Pack of disc ceramics, assorted values and voltages — 200 for **£1.00**

TRANSFORMERS

Mains primary, 50V 20A sec. **£20.00.** Mains pri. 110V 15A sec **£30.00;** 20A **£40.00.**

SLIDER POT SCOOP!!!

Made by Piher, types PL40CP & PL60C. Silly prices for superb goods!!
PL40CP — 69×16×9mm, 40mm slide length. 220R, 2k2 or 10k lin only. Prices (any mix): 1-24 **20p;** 25-99 **17p;** 100+ **14p.**
PL60C — 84×10×7mm. 60mm slide length. 5k, log. only. Prices 1-24 **25p;** 25-99 **22p;** 100+ **17p.**

REGULATED PSU PANEL

Exclusive Greenweld design, fully variable 0-28V & 20mA-2A. Board contains all components except pots and transformer. Only **£7.75**. Suitable transformer and pots **£6.00**. Send SAE for fuller details.

CALC CHIPS 60p!!!

New full spec, supplied with data. Type MK50321 — full function inc. memory. **Only 60p**

£1 BARGAIN PACKS

Each pack £1; any 25 packs £22

K101	16	BC239B transistors
K102	15	BC349A transistors
K103	10	BC546B transistors
K104	18	BC182B transistors
K105	50	1N4148 diodes
K106	18	BC184L transistors
K107	18	BC213L transistors
K108	8	2N5060 thyristors, 30V 0.8A T092 case
K109	15	BC114 transistors
K110	4	BD131 transistors
K111	4	BD132 transistors
K112	12	3A 100V rects, wire ended
K113	30	DA002 rects 150V 0.5A
K114	15	XK6116 (BF241) transistors
K115	18	SP1218 (2N3702) transistors
K116	10	MPSL01 NPN 140V T092
K117	10	BF450 PNP TV IF amp transistor
K118	16	ME4101 NPN 60V AF low noise
K119	10	2N5401 NPN 160V T092
K120	6	prs 2SD96/2SB496 AF O/P sim to AC128/176
K121	20	7V5 400mW zeners
K122	10	VR525 5.25V 2.2W zener
K123	10	56V 1W zener
K124	50	.02µF disc ceramic
K125	200	1k 5% ¼W carbon film resistors
K126	100	300pF 63V polystyrene preformed caps
K127	25	47µF 25V axial lead caps
K128	25	15µF 40V do
K129	8	AA113 diodes
K130	25	470R V 0.1W presets
K131	10	VA1086 thermistor
K132	12	4.7µF 50V bead tants
K133	20	3 way 5A term blocks
K134	50	unmarked untested OC71 type transistors
K135	30	4.7µF 10V radial elecs
K136	4	AC187k transistors
K137	5	18µF 100V non-polarized caps
K138	30	¼" coil former with slug
K139	40	.025µF 50V mylar caps
K140	30	.05 do
K141	40	0.01µF 400V axial caps (C296)
K142	25	wire ended neons std size, 90V
K143	200	squares mica insulation 25mm sq.
K144	30	IR5 3W wirewound resistors
K145	10	1500µF 16V caps — radial PC mntg.
K146	25	330µF 4V axial caps
K147	3	150µF 350V caps—radial PC mntg.
K148	30	transformer former type X228
K149	12	Ferrite rod type X036
K150	10	switches type W430
K151	12	0.125" red LED's
K152	10	0.2" red LEDs
K153	30	T05 heat sinks, same as G104
K154	15	5 pin 180° Din socket, clip fix
K155	100	metres thin flex (10×2m lengths)
K156	15	1¼" chassis mntg fuseholder
K157	12	16 pin QIL-QIL IC sockets
K158	6	SPCO centre off white rocker switches
K159	20	0.3W presets 500k V with knurled knob
K161	20	0.3W presets 2k5 V
K162	20	0.3W presets 2M5 V with knurled knob
K163	400	15R ¼W 5% preformed vert mntg resistors
K164	50	22pF 2% silver mica caps
K165	20	Sub-min reed switch, body 20mm long
K166	100	3300pF 630V polyester PC mntg caps
K168	50	AA144 diode preformed as above
K169	30	8V2 400mW zener as K167
K171	25	11V do
K173	12	1.5µF 25V tant bead caps
K174	12	0.47µF 25V tant bead caps
K175	100	2000pF 2½% 125V p/s caps
K176	24	150R 0.1W vert presets
K177	24	470R 0.1W horiz presets
K178	24	470R 0.1W vert presets
K179	24	2k 0.1W horiz presets
K180	24	2k 0.1W vert presets
K181	24	2k2 0.1W horiz presets
K185	200	1R ½W CF preformed R's for horiz mntg, 15mm centres
K187	18	PE5030 NPN Si TO92 transistos. Vce 35V, Hfe 75
K188	18	F544 PNP Si TO92 transistors. Vce 20V, Hfe 300
K189	30	1N649 600V 0.4A diodes, preformed for H mntg.
K190	16	BZY85 8V2 250mW zener diodes
K191	8	BY300/600 'Top Hat' switching diode, 600V 6A
K192	25	RGP10B 100V 1A switching diode

COMPONENT PANELS

Z525 Contains 11 800mA 60V 2N5061 SCRs. 11 6V8 zeners. 11 1N4004 diodes plus Rs, Cs, etc. Only **£1.**
Z529 74 Series ICs — Gates and complex logic, 20 asstd ICs on panels **£1;** 100 ICs **£4.**
Z527 2×6V reed relays. 6×2S030 or 2S230. 6×400V rects, plus Rs. Only **50p.**

TTL, LINEAR, OPTO

All new full spec — Fairchild/SGS:
TTL: 5400, 5401, 5402, 5403, 5404, 5405, 5410, 5421, 5430, 5450, 5451, 5453, 5460 — **All 12p ea.** 5470, 5472, 5474, 5475, 5476, 5480, 5486, 5490, 54107, 54121, 54122 — **all 20p ea.** 5482, 54126 — **40p ea.** Others (74S, H) on B/L 12 (SAE please).
LINEAR: 9665 or 9666, 7 x 50V Darlingtons in 16 Dil **60p;** 75452 or 4 dual periph driver **70p;** XK1444 7 CMOS P-channel buffers, 15V 16 DIL **24p.**
OPTO: Isolators, FCD831 **60p;** TIL115/118 **60p;** FPE100/106 Infra red LED **£2.50;** FND847 7 seg 0.8" CA **£2.00;** FND850 CC **£2.00.** (Data on request for linear & opto devices).

BULK BUYERS LIST — Big bargains for quantity buyers. Resistors from **£3.50**/k, caps **£7**/k. Send SAE for list.



FREE WATCH OFFER on all Thandar test equipment

WORTH UP TO £30

If you are interested in purchasing a hand-held digital multimeter, a bench digital multimeter, a hand-held frequency meter, bench frequency meter, a pulse generator, a function generator, a fully portable brief-case size oscilloscope, a 2" video monitor or even an eprom programmer and obtain a **quality watch free of charge** then why not take advantage of our special offer.

For purchases of between £39 and £99 we will send free of charge a gold-plated Digital LCD, ultra-slim, five-function watch. For purchases of £100 and over we will send a gold-plated, ultra-slim, analogue watch, as per photograph. Both these watches have leather straps. This watch offer is subject to availability and in any event we will send alternative watches with a retail value of £12 and £30 respectively. YOUR WATCH MAY BE SENT SEPARATELY TO ANY ADDRESS WITHIN THE UK IF REQUIRED.

Hand-held digital multimeters
PDM 35 L.E.D. hand held DMM £39.68
TM 354 L.C.D. hand held DMM £45.94
TM 352 L.C.D. hand held DMM £57.44

Bench digital multimeters
DM 235 L.E.C. digital multimeter £60.38
DM 350 L.E.D. digital multimeter £83.38
TM 353 L.C.D. digital multimeter £96.60
DM 450 L.E.D. digital multimeter £113.85
TM 351 L.C.D. digital multimeter £113.85

Hand-held frequency meter
PFM 200 frequency meter £57.27

Bench frequency meters
TF 040 bench frequency meter £126.50
TF 200 bench frequency meter £166.75

Pulse Generator
TG 105 pulse generator £97.95

Bench Function Generator
TG 100 function generator £90.85

Fully Portable Oscilloscope
SC 110 Oscilloscope £159.85

2" Video Monitor
MON 1A 2" Video monitor £109.25

Eprom Programmer
PKW 5000 Eprom Programmer £918.85

All prices include V.A.T. Official orders welcome. Mail order only, or callers at our warehouse by **prior** appointment. Barclaycard/Access welcome. Cheque/P.Os, etc., with order. Large s.a.e. for complete Thandar list. All items POST FREE.

B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex, SS9 5TY

Tel: Southend 527572

CALCULATORS

All equipment new boxed and fully guaranteed
Price includes V.A.T., Post and Packing

PRICES ANY CASIO, SHARP OR TEXAS CALCULATOR SENT FOR £1 LESS THAN ANY OTHER ADVERTISED PRICE IN THIS MAGAZINE (subject to stock)

CASIO

FX501P PROGRAMMABLE	£49.95
FX502P PROGRAMMABLE	£69.95
FA1 CASSETTE INTERFACE	£19.95
FX501P with FA1	£65.95
FX502P with FA 1	£85.95
FX100 10 DIGIT SCIENTIFIC	£14.95
FX 68 8 digit compact scientific	£18.95
FX 510 8 digit scientific best-seller	£18.95
FX 7100 credit card scientific clock/alarm	£23.95
FX 8100 8 digit scientific clock/timer/alarm, etc.	£23.95
BQ 1100 biorhythms	£15.95

★NEW

FX 180P PROGRAMMABLE 38 step	£18.95
FX 350P PROGRAMMABLE 38 step	£21.95
FX 2700P PROGRAMMABLE 38 step	£18.95
FX 6100 similar to 8100 less calendar	£18.95

SHARP

POCKET COMPUTER 1211 with interface	£106.95
EL 5101 PROGRAMMABLE 16 digit	£41.95
EL 5100 PROGRAMMABLE 24 digit	£51.95

TEXAS INSTRUMENTS

*TI 51-11 PROGRAMMABLE 32 step	£28.95
*TI 57 PROGRAMMABLE 50 step	£27.95
*TI 58 PROGRAMMABLE 480 step	£63.95
*TI 58C as above with constant memory and programme	£76.95
*TI 59 PROGRAMMABLE 960 step	£176.95
PC 100C printer for TI 58/58C/59	£173.95
*TI PROGRAMMER	£51.95

(* includes mains adaptor/charger)

TEXAS ELECTRONIC LEARNING AIDS

LITTLE PROFESSOR	£11.95	LETTER LOGIC	£21.95
DATAMAN	£16.95	SPEAK & SPELL	£39.95

TELEPHONES

CORDLESS PRO FF 3000 up to 600 feet range	£139.95
CORDLESS PHONE 4001 up to 500 feet range	£108.95
FLIP PHONE 788 with memory redial, easy to connect as extension	£28.95

MINIATURE V.H.F. F.M. TRANSMITTERS


MINI MICRON, 50 yards range 100-108 MHz	£14.95
MICRON 2 100 yards range 100-108 MHz	£18.95
MICRON X 1000 yards range 95-115 MHz	£28.95

FULL RANGE OF CASIO, SHARP AND TEXAS CALCULATORS AVAILABLE
SEND P.O., CHEQUE, ACCESS NUMBER OR ADD 75P FOR C.O.D. (up to £100)

CALCULATOR SALES & SERVICE

FREEPOST, REDDITCH, WORCS, B97 4BR

GUITAR NOTE EXPANDER

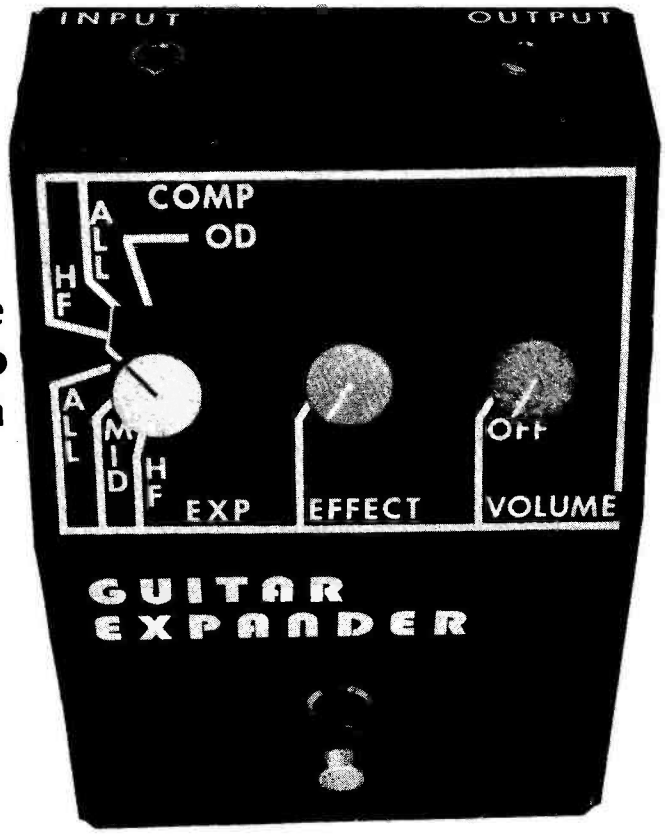

If you've ever built a conventional fuzz/sustain unit, you may have been disappointed by the harshness of the sound. If so, we present the answer to your problems — soft clipping. Design by Q.A. Rice. Development by Plamen Pazov.

A good number of fuzzbox circuits have appeared in the past which attempt to emulate the sound of an overdriven valve amp; the majority of these look great on a scope but still sound rough. The chief characteristic of valve amps is the way they overload; rounding off the peaks as opposed to transistor circuits which clip off the peaks, producing predominant odd harmonics. FET amps produce overload in a similar way to valve amps, and a cheaper and better (or worse) way to obtain this is to use CMOS gates in the linear mode. Figure 1 shows the overload for a triangular waveform. In the final circuit we have used a very versatile and much under-used CMOS IC, the CD4007 dual complementary pair and inverter. One complementary pair is wired as a second inverter — the two inverters are used as amplifiers and give a combined gain of 60 dB. One of the remaining CMOS FETs is used as a voltage-controlled resistor which can vary between from several megohms to a few hundred ohms. The output of the amplifier is passed to a detector which controls the resistance of the FET, and this is fed back to various parts of the circuit to give the expansion and compression effects. Figure 2 shows the input/output characteristics for the various functions. The compressor is effective over a 30 dB range.

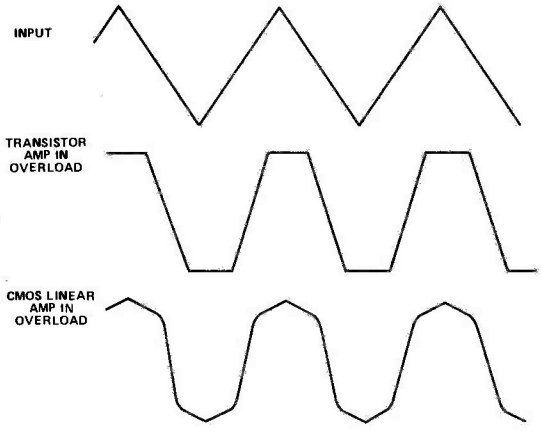


Fig.1 Clipping characteristics for two types of amplifier under overload conditions.

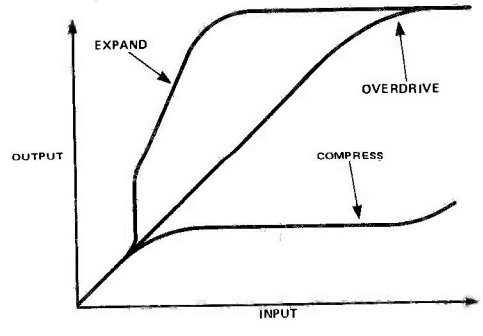


Fig.2 Input/output characteristics for various functions of the effects unit.


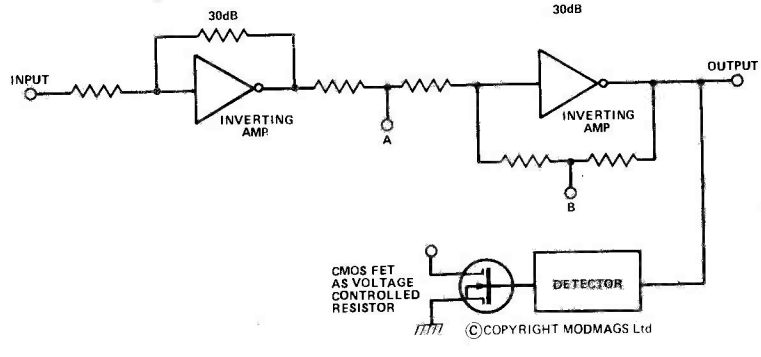


Fig.3 This diagram shows the basic principle of the unit.

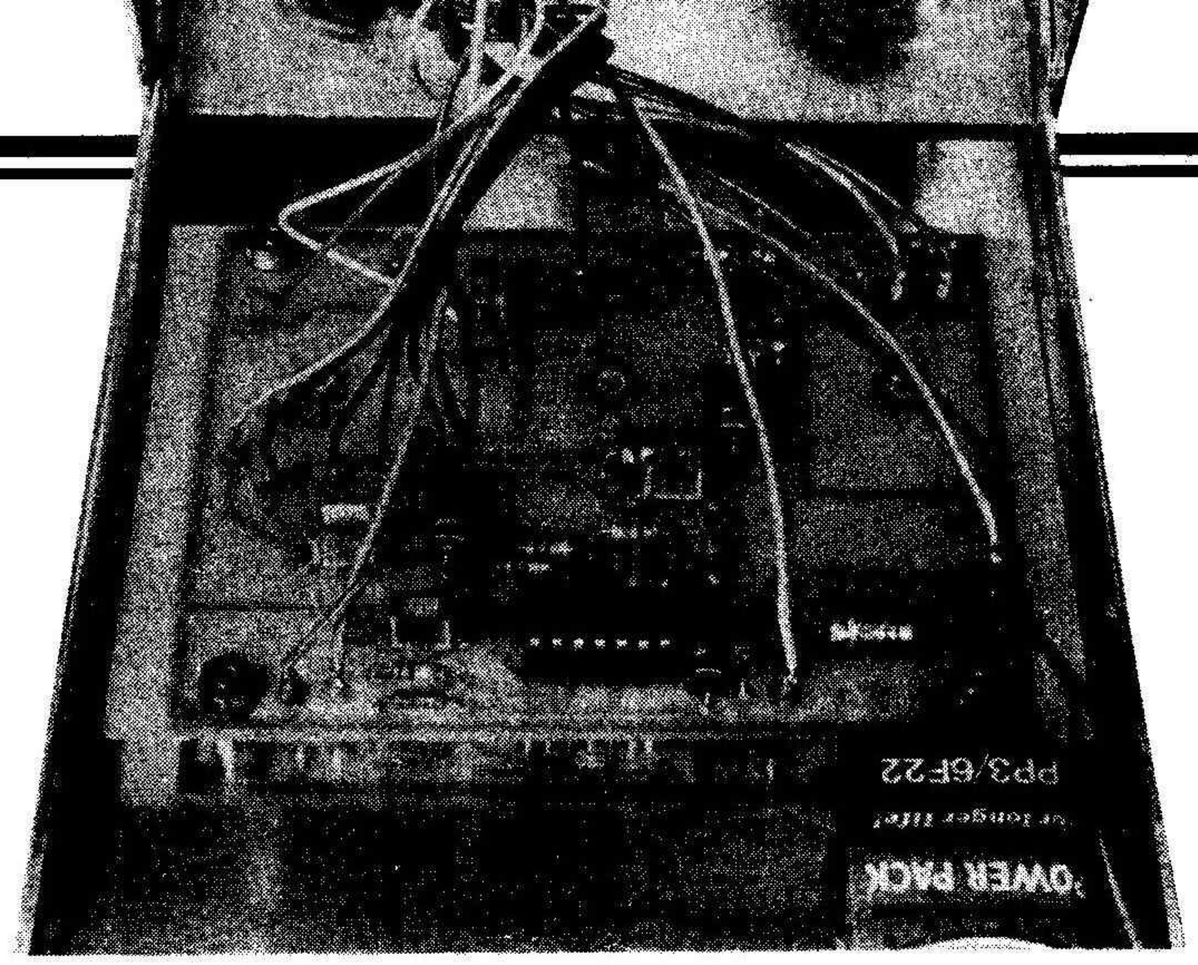

The unit has six functions, as follows:

1. Overall overdrive
2. Overall compression, for sustaining
3. High frequency compression, for bass overdrive
4. Overall expansion, for sustained overdrive
5. Mid expansion, for mid to high accentuation
6. High frequency expansion, for high accentuation

The effect of all these functions is variable, with the exception of overdrive.

Construction

The PCB is designed to accept the control components (SW2 and pots) if PCB-mounting of these components is preferred, to give a very compact construction. For the prototype this was not necessary as we used a custom-built housing (see Buylines). The box comes unpunched so if you want to arrange the controls and sockets differently you can get a drill and do your own thing. If you use a different housing remember that a metal case should be used to maintain proper screening.

We used a volume control with a built-in on/off switch instead of the standard method of using the input jack, as the latter approach produces a 9 V peak back into the source circuit and can cause damage if this circuit is active.

If the guitar has a low sensitivity pickup, it may be necessary to increase the value of R2 accordingly. The unit only consumes 3 mA so the batteries should last quite a while.

HOW IT WORKS

CMOS inverters may be used in the same manner as op-amps in the inverting mode, with the added bonus that they are self-biasing. The input is fed into IC1a, configured as a high gain, high impedance amplifier to give a gain of around 30 dB. This is decoupled and passed through a resistor pair to a second amplifier stage, which has a resistor pair in its feedback (see Fig. 3). If point A is now taken to ground via a resistance, gain is reduced; if this is done to point B, gain is increased. The final output is passed through a detector to give a voltage proportional to the signal level; this voltage is used to control the CMOS FET. If the FET is taken to point A or point B, then the overall gain is proportional to the final output signal. Thus if the output reduces the signal, it is self compressing. If it increases it, the signal is expanded. By making these gain variations frequency-dependant, we can accentuate or subdue the high frequency as required, at various break points to give the effects required. The output signal has to be attenuated to return it to its original level.

PARTS LIST

Resistors (all ¼W, 5%)

R1, 10	100k
R2	3M3
R3, 4, 7	4k7
R5, 6	150k
R8	1M0
R9	470k

Potentiometers

RV1	10k logarithmic
RV2	100k logarithmic with integral switch

Capacitors

C1	220n polyester
C2, 3, 4, 6, 10, 11	2u2 16 V axial electrolytic
C5	22n polyester
C7	3n3 ceramic or polycarbonate
C8	1n0 ceramic or polycarbonate
C9	10n polyester

Semiconductors

IC1	CD4007
D1, 2	OA91

Miscellaneous

SW1	DPDT latching footswitch
SW2	2-pole 6-way rotary switch
SK1, 2	mono jack sockets

Battery clip (PP3), metal box (see Buylines).



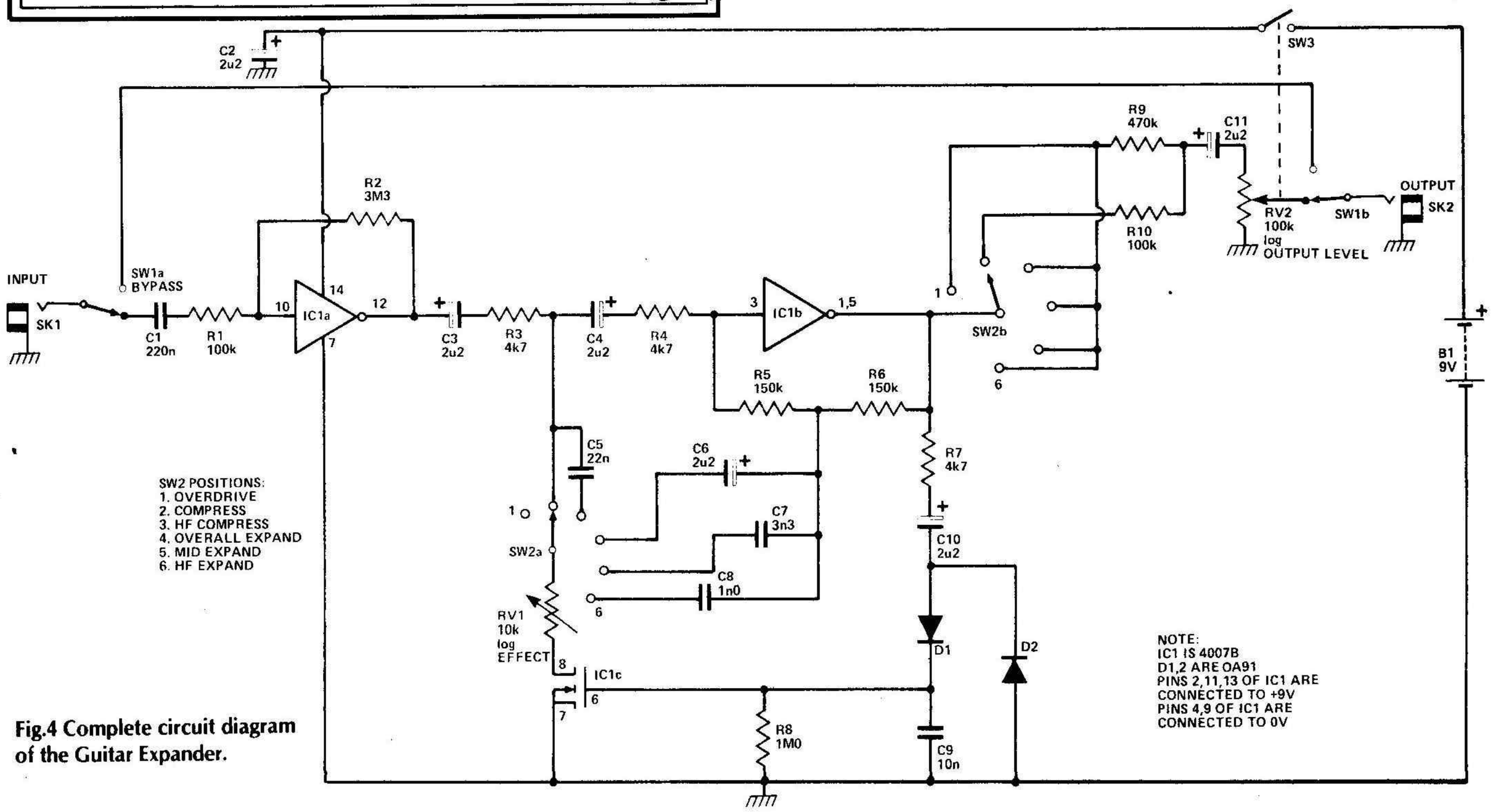


Fig.4 Complete circuit diagram of the Guitar Expander.

Fig.5 Component overlay.

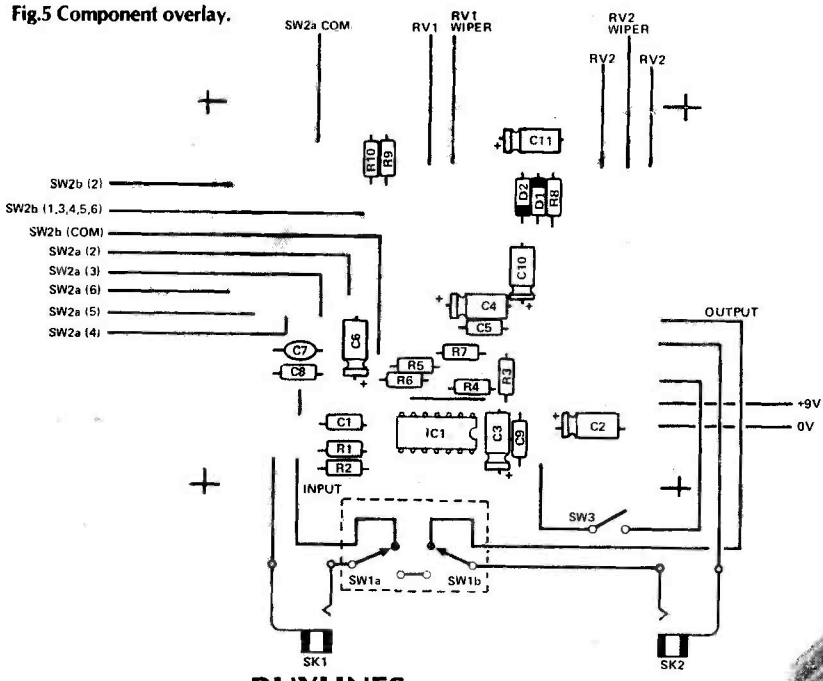

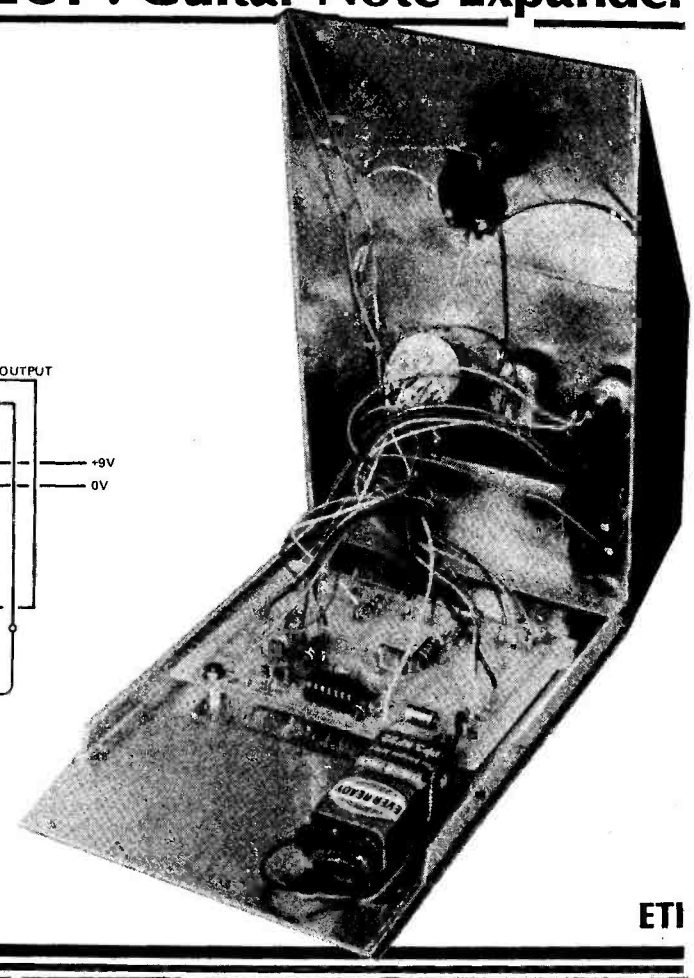

BUYLINES


As mentioned in the text, we have arranged for the construction of a custom case for this project, or indeed any other of your musical projects. H.L. Smith & Co Ltd, 287 Edgware Road, London W2 1BE will supply the box, ref. ETI-1 for the modest sum of £2.00.

All the other components should be readily available from most of the distributors advertising in this issue.

ETI

Join the Professionals...

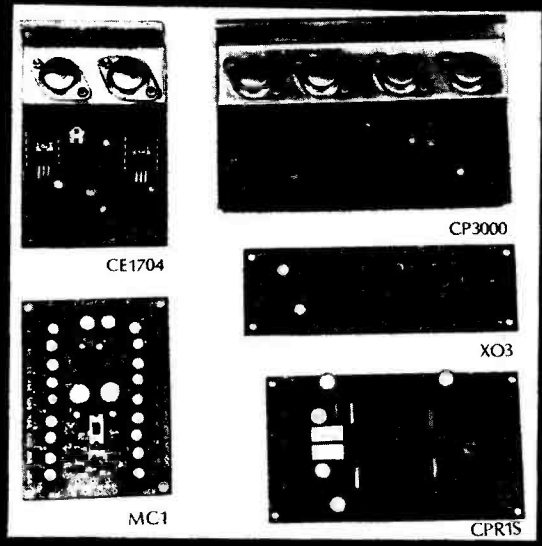Crimson modular audio amplifiers feature: ★Low values of transient and steadystate distortions ★Envelope distortion (below 500 Hz) less than 0.05% ★on-board electronic protection ★P.C.B. pin and edge connector termination ★Full range of complimentary components i.e. P.S.U.'s, heatsinks etc. available from Crimson



The Crimson range of amplifier modules are built to very high standards and have earned an enviable reputation in every field to which they have been applied. The boards come ready built and tested (guaranteed for two years) and can be used to advantage where high quality signal amplification is required. The power amplifier modules range from 60WRMS to 310WRMS with up to twice this amount in bridge mode. All feature substantial heatsink brackets which can be bolted to any available heatsink or the Crimson purpose designed types. Input sensitivity is set at 775mV and power supply requirements are catered for by one of the three Crimson toroidal power supplies. The Pre-amplifier module (CPR1) is basically a phono amplifier with sophisticated circuitry incorporating R.I.A.A. equalisation. Also on-board is auxiliary amplification for tape and tuner inputs. A separate module (MC1) is also available and gives the required boost for low output moving coil type cartridges. External components required are potentiometers for volume and balance, switches for signal routing and a regulated ±15V D.C. power source (REG1). Complimenting this range, are the electronic crossover modules XO2/XO3 which, with a special muting board (MU1) can be incorporated in all types of active speaker systems.

Numerous applications are possible with Crimson modules. For example, a complete Hi-Fi Pre & Power amplifier of 40-125WRMS/channel can be built using our Hardware kits (see Hobby Electronics review, August 1980). Alternatively, Mono or Stereo slave amps of up to 500WRMS can be built into proprietory flight cases, while other uses include active loudspeaker systems such as designed by R.I. Harcourt in Wireless World October/November 1980. Further details of how to use the modules are contained in the Users/Application Manual available at £0.50.

SPECIFICATIONS

Type	O/P8ohms*	O/P4ohms*	PSU	H/Sinks	Slew	S/N	Sensitivity	T.H.D (typ)	F.R.	Size
CE 608	38		CPS1	50mm	30V/µS	110dB	775mV	0.0035%	1.5Hz 50KHz (-3dB)	80 · 120 · 25
CE1004	44	70	CPS3	100mm	30V/µS	110dB	775mV	0.0035%	1.5Hz 50KHz (-3dB)	80 · 120 · 25
CE1008	65		CPS3	100mm	30V/µS	110dB	775mV	0.0035%	1.5Hz 50KHz (-3dB)	80 · 120 · 25
CE1704	85	121	CPS6	150mm/FM1	30V/µS	110dB	775mV	0.0035%	1.5Hz 50KHz (-3dB)	80 · 120 · 25
CE1708	125		CPS6	150mm/FM1	30V/µS	110dB	775mV	0.0035%	1.5Hz 50KHz (-3dB)	80 · 120 · 25
CP3000		250	CPS6	FM2	30V/µS	110dB	775mV	0.0035%	1.5Hz 50KHz (-3dB)	161 · 102 · 35
CPR1S†	Output	775mV	REG1		3V/µS	70dB	2.8mV/RMS	0.008%	20Hz 20KHz	138 · 80 · 35
MC1S†	Output	2mV	REG1			65dB	70mV/150Ω	0.008%	20Hz 20KHz	80 · 120 · 35
XO2 XO3	Output	775 2500mV	REG1		9V µs	90dB	775mV	0.01%	X over points	150 · 50 · 20

*Power output is quoted WRMS and is given for two modules run off the same power supply. Higher powers are obtainable if using one module per P.S.U. or if using a stabilised P.S.U.

PRICES HELD FROM MAY— TO FEB '80

Power Amplifier Modules		Power Supply Modules		Heatsinks	
CE 608	£21.00	CPS1 (80VA)	£19.50	50mm	£1.70
CE1004	£24.50	CPS3 (150VA)	£23.50	100mm	£2.70
CE1008	£27.50	CPS6 (250VA)	£30.00	150mm	£3.50
CE1704	£35.00	REG1	£9.30	FM1	£36.00
CE1708	£35.00	TR6	£2.50	FM2	£42.00

Pre-Amplifier Modules		Active Crossovers		Hardware	
CPR1	£34.00	XO2	£19.00	Pre-Amp	£39.80
CPR1S	£44.50	XO3	£28.35	Power Amp	£38.00
MC1	£26.00	MU1	£7.50	Thermal Cutouts	£1.90
MC1S	£37.00				

BARCLAYCARD VISA — We welcome Access

Prices include VAT, P&P to anywhere in the UK. COD £1.00 extra. Limit £100. Export — Pay by Access, Master Charge, Visa Card or write for pro forma.

Crimson Elektrik

9 CLAYMILL ROAD, LEICESTER LE4 7JJ, ENGLAND. Tel 0533 761920 Telex 34694 Chanco G CRIMLEK

PLEASE SEND ME MORE DETAILS OF ALL CRIMSON ELEKTRIK AMPLIFIERS

Name .....

Address .....

ETI 4.81

INTRUDER ALARMS

BRANDED INTRUDER ALARMS AT DISCOUNT PRICES FOR LIMITED PERIOD ONLY

Alarm with self-contained siren. Keyed and timed entry, using minimal power consumption on stand-by. With circuit fault indicator, 3 reed switches, 1 pressure mat, wire and full installation instructions.	£36.80
Siren extension unit to increase range	£11.75
Self-powered siren **(sounds if separately attacked)**	£25.00
Self-powered bell **(sounds if separately attacked)**	£29.00
Reed switches (surface)	£1.00
Reed switches (flush)	£0.90
Pressure Pad — 27" x 15"	£2.20
Pressure Pad — 22½" x 6¾"	£1.60

All above prices inclusive of V.A.T. and postage. Terms: Cash with order.
Write to Yale Security Products, Wood Street, Willenhall,
West Midlands WV13 1LA. Telephone: 0902 66911. Telex: 338251.

DISCO LIGHTING KITS!!!

First class constructional projects. c/w glass fibre P.C.B.'s & full instructions. No extra components needed to make a top rate working unit.

LK1 £9.90 — 3 channel sound-to-light. 300 w/channel 1v – 100w input

LK2 £17.90 — 3 channel 3kW zero voltage firing 200mV – 100 watts input.

LK3 £8.90 — 2kW slider dimmer suitable for clubs/pubs. A professional unit c/w **FACE PLATE**


LK4 £16.50 — 4 channel 4kW audio – forward/reverse auto – two speed ranges.



ALL KITS C/W circuit, comprehensive instructions & full parts guarantee

Carriage on above 70p

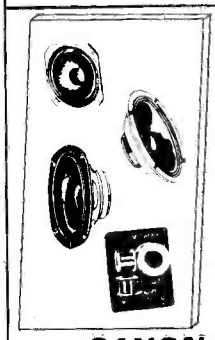Suitable case for LK 1/2/4 **£3.50**
100w spots ES or BC **£1.50.**
Coloured pigmy lamps **65p.**
8m rope lights **£49**



UNREPEATABLE HI-FI BARGAIN

3 WAY LOUDSPEAKER KIT C/W BAFFLE (pre-cut)

Comprises:
★ 6½" linen surround bass unit
★ 5" mid-range unit
★ 3" tweeter
★ 3 way crossover, fixing screws & baffle
★ 20 watts handling capability.
Full instructions provided
Must be heard to be believed!!

£10.50 or 2 kits for **£20** Carr. £1 per kit

SAXON ENTERTAINMENTS (ETI)
327-333 Whitehorse Rd., Croydon, Surrey CR0 2HS.
(01) 684 8007
Order by phone – Access/Barclaycard/C.O.D.
Open Mon. – Sat. 9am – 5pm.


CASTLE ELECTRONICS

SOUTH COAST MICRO CENTRE

Telephone Hastings (0424) 437875

TANGERINE microtan 65 £69

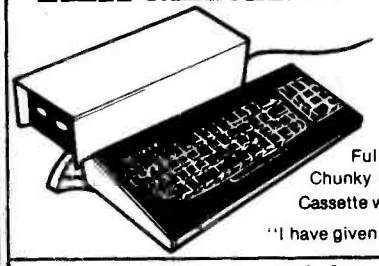Microtan 65 is the most advanced, most powerful, most expandable microcomputer available —it also happens to be the most cost effective.



6502 Microprocessor IK Tanbug IK User RAM Full TV Display **£79** (ready-built). 20-way KEYPAD—**£10.**
TANEX—£43
IK 16 parallel 1/0 lines. Cassette Interface—1 serial 1/0 line. 2 x 16 BIT counter timers OPTIONS TK RAM total—32 parallel 1/0 lines. 4 x 16 BIT counter timers—RS232. 20MA current loop.
10K MICROSOFT BASIC—£49
System Rack—**£49** in black/tangerine in brushed aluminium.
Full Ascii Keyboard with numeric pad—**£60.85.** Cabinet available—**£20.** Lower Case option—**£9.48.**
Chunky Graphics Pack—**£6.52.** Tanram Full Memory Expansion to 40K—**£119.00.** Mini Motherboard—**£10.00.**
Cassette with counter—**£21.70.**

"I have given TANGERINE five bonus points for getting just about everything right"—E.T.I. Mag., May 1980.



video genie

WITH
•16K user RAM plus extended 12K Microsoft BASIC in ROM •Fully TRS-80 level II software compatible •Self-contained, PSU, UHF modulator and cassette •Simply plugs into video monitor or UHF TV.

16K **£299** Expander from **£195.00**

COMMODORE	8K	£399.00
	16K	£499.00
	32K	£649.00
SHARP MZ80	20K	£449.00
APPLE	16K	£599.00
	Epsom Printer	£349.00

plus **BOOKS/MEMORIES/SOFTWARE**

ALL PRICES ADD 15% VAT. DELIVERY CHARGES WILL BE NOTIFIED
ACCESS AND BARCLAYCARD ORDERS TAKEN BY PHONE

7 CASTLE ST., HASTINGS, E. SUSSEX TN34 3DY Telephone: Hastings (0424) 437875

SHOP HOURS 0900 to 1730 MONDAY to SATURDAY. PERSONAL CALLERS WELCOME


Greenbank

Greenbank Electronics
(Dept T4E) 92 New Chester Road, New Ferry
Wirral, Merseyside L62 5AG
(Tel: 051-645 3391)

TERMS. VAT. CWO. Cheques etc payable to Greenbank Electronics and crossed. Add VAT to all prices at 15% except where stated otherwise. Post etc: UK 40p (+6p VAT = 46p) per order. Export: NO VAT but add 40p (Eire), £1 (Europe) and £3.50 elsewhere. Access, Barclaycard, Visa, telephoned orders accepted. (Polys, universities, govt depts, etc can telephone their orders for immediate despatch on account.)

BARCLAYCARD

UV 141, UV ERASER

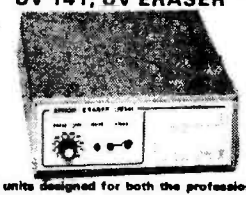


Two easy to use units designed for both the professional and amateur UV-prom user
Features

- Can erase up to 14 proms.
- Special short wave ultraviolet tube.
- Erase time variable between 5 and 50 minutes in 5 minute steps (preventing over exposure which may shorten prom life).
- Sliding tray carries proms on conductive foam.
- Safety Interlock switch prevents the timing circuit from operating and switching on the tube with the tray open.
- "Mains On" and "Tube On" indicators.
- Smart textured case.
- Complete instructions supplied.

Supplied complete with mains plug and flex

Model UV 141. Price £77.70
Also available without timer as
Model UV 140: Price £61.20

TEX MICROSYSTEMS "EPROMPT" UV ERASER

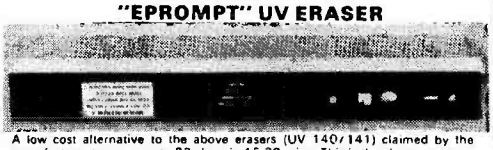

A low cost alternative to the above erasers (UV 140/141) claimed by the manufacturer to erase up to 32 chips in 15-30 mins. This is the cheapest eraser we have seen. The unit has no timer, power switch or safety interlock switch. The user places up to 32 chips into loose conducting foam in the erasure tray (16 along the base, 8 on each side). The chips are held in place by the UV tube which sits in the tray. (Unlike the UV 140/141, no special precautions have been taken to prevent the seepage of UV light, but the manufacturers state that "Incident light from this device is quite safe at distances above 12 inches".)

(Dimensions – 325×64×38mm)

EPROMPT ERASER **Price £33**

EUROCARD COMPUTER BOARDS

Custom 80' Modular Z80 Based System.Details in preparation, free on request.

"BIG BOARD" Z80 COMPUTER KIT

We hope this item will be in stock by the time this advert reaches you, but please check to see before sending any money! Features: 64K Dynamic RAM, Floppy Disk Controller, 80 x 24 Char. Video output **£395**. CP/M Disk Operating System to suit. **£99.**

MODULAR COMPUTER SYSTEM CARDS

A range of 'International' (114 x 203mm) size cards which may be purchased individually as desired, or to build up a complete system. Further details available on request. All boards are epoxy glass with gold plated edge plug.

VDU A, B, G (set of 3)	£27.20
SC/MP P SC/MP CPU	£9.40
MPA-7 Buffered SC/MP CPU	£9.40
MZ8-3 Z80-CPU	£9.40
MXA-1 2K of 2102	£9.40
MXA-3 8K of 2114	£9.40
MXD-2 16K of 4116	£9.40
PRM-2 4K of 5204	£9.40
PRM-8 8K of 2708	£9.40
RRM-14 8K of 2516 + 6K of 2114	TBA
SIO-2 RS-232 (two)	£9.40
TPA-2 Tape Interface	£8.90
IP-2 Input Port	£9.40
DCR-6 Keyboard Input	£8.90
OP-3 Output Port	£9.40
PP-2 PROM Programmer	£9.40
PSU-A4 Power Supply	£8.90
PSU-B 5V Power Supply	£5.50
PSU-C 25V Power Supply	£5.50
13-slot backboard, can be used with most of the above boards, 13" x 4¾".	
ISBUS-1.1	£11.50

CMOS

These cut prices for Amateur Users and Export. Note: Industrial users – quantity prices available. Mostly Motorola, RCA

4000	18p	4042	80p	4095	£1.97	4410	£8.55	4531	£1.45
4001	25p	4043	90p	4096	£1.97	4411	£10.72	4532	£1.30
4002	25p	4044	90p	4097	£5.98	4412VP	£14.93	4534	£5.60
4006	95p	4045	£2.63	4098	£1.92	4415V	£5.24	4536	£3.69
4007	18p	4046	£1.10	4099	£2.00	4422	£5.66	4537L	£26.10
4008	80p	4047	£1.71	40100	£1.92	4433	£12.30	4538	£1.20
4009	40p	4048	77p	40101	£1.69	4435V	£5.40	4539	97p
4010	50p	4049	45p	40102	£3.67	4450	£3.81	4541	£1.19
4011	25p	4050	49p	40103	£3.67	4451	£3.81	4543	£1.80
4012	18p	4051	80p	40104	£1.85	4461	£3.93	4549	£4.38
4013	50p	4052	80p	40105	£1.85	4462	£4.41	4552	£14.85
4014	84p	4053	80p	40106	92p	4490FP	£4.20	4553	£4.50
4015	84p	4054	£2.18	40107	£1.28	4490NP	£3.14	4554	£1.38
4016	45p	4055	£2.55	40108	£7.54	4500	£6.95	4555	78p
4017	80p	4056	£2.55	40109	£1.28	4501	29p	4556	72p
4018	89p	4059	£9.23	40110	£3.00	4502	£1.20	4557	£3.86
4019	45p	4060	£2.10	40114	£1.77	4503	70p	4558	£1.25
4020	99p	4062T	£10.00	40160	£1.54	4505	£5.71	4559	£4.38
4021	£1.10	4063	£1.90	40161	£1.54	4506	50p	4560	£2.50
4022	£1.00	4066	55p	40162	£1.54	4507	55p	4561	81p
4023	27p	4067	£7.21	40163	£1.54	4508	£2.90	4562	£5.60
4024	78p	4068	27p	40174	£1.54	4510	99p	4566	£1.59
4025	27p	4069	27p	40181	£5.03	4511	£1.50	4568	£2.38
4026	£3.25	4070	30p	40182	£1.90	4512	80p	4569	£2.50
4027	38p	4071	25p	40192	£2.41	4514	£2.85	4572	48p
4028	84p	4072	25p	40193	£2.41	4515	£3.00	4580	£4.77
4029	89p	4073	25p	40194	£3.27	4516	£1.10	4581	£2.52
4030	74p	4075	25p	40208	£7.54	4517	£4.46	4582	£1.14
4031	£4.31	4076	£1.07	40257	£2.31	4518	£1.00	4583	90p
4032	£1.31	4077	29p	4160	98p	4519	80p	4584	90p
4033	£2.63	4078	29p	4161	98p	4520	£1.00	4585	£1.27
4034	£2.00	4081	27p	4162	98p	4521	£2.50	4597	£2.44
4035	£1.10	4082	27p	4163	98p	4522	£1.11	4598	£2.38
4037	£1.99	4085	£1.35	4174	90p	4526	£1.08	4599	£6.95
4038	£1.20	4086	£1.35	4175	£1.15	4527	£1.50	4700	£1.75
4039	£2.78	4089	£2.91	4194	£1.16	4528	£1.20		
4040	£1.00	4093	80p	4408	£9.37	4529	£1.30		
4041	£1.59	4094	£2.50	4409	£9.37	4530	70p		

74C

		74C76	57p	74C163	£1.15	74C894	57p	74C925	£5.81
		74C83	£1.34	74C164	£1.88	74C895	£7.53	74C927	£5.81
		74C85	£1.34	74C165	£1.88	74C896	57p	74C928	£5.81
74C00	29p	74C86	67p	74C173	92p	74C897	57p	74C929	£17.00
74C02	29p	74C89	£4.62	74C174	92p	74C898	£1.00	74C930	£17.00
74C04	29p	74C90	80p	74C175	92p	74C899	£1.00	80C95	85p
74C08	29p	74C93	80p	74C182	£1.15	74C910	£7.48	80C86	92p
74C10	29p	74C95	£1.00	74C183	£1.15	74C911	£7.30	80C87	89p
74C14	89p	74C107	£1.27	74C195	£1.88	74C912	£7.30	80C96	92p
74C20	29p	74C150	£3.81	74C200	£7.48	74C914	£1.48	82C10	£6.28
74C30	29p	74C151	£2.98	74C221	£1.41	74C915	£1.18	80C20	£2.98
74C32	29p	74C154	£3.81	74C373	£1.79	74C918	£1.18	80C90	£2.98
74C42	98p	74C157	£2.29	74C374	£1.79	74C921	£17.87		
74C48	£1.43	74C160	£1.48	74C901	57p	74C922	£3.78		
74C73	57p	74C161	£1.15	74C902	78p	74C923	£3.86		
74C74	58p	74C162	£1.18	74C903	57p	74C925	£5.81		

74LS

		74LS55	30p	74LS151	96p	74LS244	£1.70	74LS374	£1.95
		74LS63	£1.50	74LS153	76p	74LS245	£3.50	74LS375	£1.80
74LS00	14p	74LS73	46p	74LS154	£1.70	74LS247	£1.98	74LS377	£2.12
74LS01	14p	74LS74	41p	74LS155	96p	74LS248	£1.90	74LS378	£1.84
74LS02	16p	74LS75	48p	74LS156	96p	74LS249	£1.90	74LS379	£2.15
74LS03	15p	74LS76	40p	74LS157	76p	74LS251	£1.34	74LS384	89p
74LS04	16p	74LS78	40p	74LS158	96p	74LS253	£1.42	74LS386	89p
74LS05	20p	74LS83	£1.15	74LS160	£1.28	74LS257	£1.18	74L 390	£2.30
74LS08	22p	74LS85	£1.18	74LS161	96p	74LS258	£1.46	74LS393	£2.30
74LS09	22p	74LS86	43p	74LS162	£1.38	74LS259	£1.60	74LS395	£2.18
74LS10	20p	74LS90	60p	74LS163	£1.18	74LS261	£4.58	74LS396	£2.15
74LS11	22p	74LS91	£1.04	74LS164	£1.14	74LS266	52p	74LS398	£2.76
74LS12	23p	74LS92	89p	74LS165	75p	74LS273	£2.44	74LS399	£2.30
74LS13	38p	74LS93	89p	74LS166	£2.26	74LS275	£2.98	74LS445	£1.50
74LS14	75p	74LS95	£1.16	74LS170	£2.88	74LS279	66p	74LS447	£1.44
74LS15	30p	74LS96	£1.16	74LS173	£1.05	74LS283	£1.92	74LS490	£1.80
74LS20	20p	74LS107	44p	74LS174	£1.06	74LS290	£1.28	74LS668	£1.82
74LS21	22p	74LS109	55p	74LS175	£1.10	74LS293	£1.28	74LS669	£1.82
74LS26	48p	74LS112	55p	74LS181	£3.98	74LS295	£1.85	74LS670	£2.48
74LS27	28p	74LS113	50p	74LS183	£2.98	74LS298	£1.54		
74LS28	48p	74LS114	50p	74LS190	£1.40	74LS324	£2.40		
74LS30	22p	74LS122	70p	74LS191	£1.40	74LS325	£2.80		
74LS32	27p	74LS123	70p	74LS192	£1.30	74LS326	£2.94		
74LS33	39p	74LS124	£1.80	74LS193	£1.30	74LS327	£2.86		
74LS37	39p	74LS125	60p	74LS194	£1.86	74LS347	£1.48		
74LS38	39p	74LS126	60p	74LS195	£1.36	74LS348	£1.86		
74LS40	28p	74LS132	95p	74LS196	£1.00	74LS352	£2.28		
74LS42	98p	74LS136	55p	74LS197	£1.40	74LS353	£2.28		
74LS47	98p	74LS138	85p	74LS221	96p	74LS365	65p		
74LS48	£1.28	74LS139	85p	74LS240	£2.36	74LS366	65p		
74LS49	£1.20	74LS145	£1.08	74LS241	£2.32	74LS367	65p		
74LS51	24p	74LS147	£1.70	74LS242	£2.32	74LS368	66p		
74LS54	29p	74LS148	£1.73	74LS243	£2.32	74LS373	£1.80		

QUARTZ

32.768KHz (Watch)	£3.23
80 KHz	£9.95
100.0 KHz	£3.62
200.0 KHz	£3.92
204.8 KHz	£3.92
262.144 KHz	£3.92
307.2 KHz	£3.92
312.5 KHz	£3.92
455.0 KHz	£4.95
1.000 MHz	£3.62
1.008 MHz	£3.92
1.280 MHz	£3.92
1.6 MHz	£4.25
1.8 MHz	£4.25
1.8432 MHz	£3.62
2.000 MHz	£3.62
2.097152 MHz	£3.23
2.4576 MHz	£3.62
2.500 MHz	£3.92
2.56250 MHz	£3.62
3.000 MHz	£3.92
3.2768 MHz	£3.23
3.579545 MHz	£1.95
3.93216 MHz	£3.92
4.000 MHz	£2.90
4.032 MHz	£3.23
4.096 MHz	£3.23
4.194304 MHz	£3.23
4.433619 MHz	£1.25
4.608 MHz	£3.23
4.800 MHz	£3.23
4.9152 MHz	£3.23
5.000 MHz	£3.23
5.0688 MHz	£3.23
5.120 MHz	£3.23
5.185 MHz	£3.23
6.000 MHz	£3.23
6.144 MHz	£3.23
6.400 MHz	£3.23
6.55360 MHz	£3.23
7.000 MHz	£3.23
7.168 MHz	£3.23
7.680 MHz	£3.23
7.86432 MHz	£3.23
8.000 MHz	£3.23
8.08333 MHz	£3.62
8.388608 MHz	£3.23
8.867237 MHz	£3.23
9.375 MHz	£3.92
9.600 MHz	£3.92
10.000 MHz	£3.23
10.245 MHz	£3.23
10.700 MHz	£3.23
10.92 MHz	£3.62
11.000 MHz	£3.92
12.000 MHz	£3.92
14.0 MHz	£3.92
14.31818 MHz	£3.23
16.000 MHz	£3.92
18.000 MHz	£3.23
18.432 MHz	£3.23
20.000 MHz	£3.62
20.1134 MHz	£3.23
24.0 MHz.	£3.92
26.690 MHz	£2.10
27.0 MHz	£3.92
27.145 MHz	£2.10
27.648 MHz	£3.92
38.6666 MHz	£3.23
48.000 MHz	£3.23
100.000 MHz	£3.23
116.000 MHz	£3.23

VERSOBOARD

0.1" Pitch with copper strips

2½"×1" (pack of 5)	£1.01
2½"×3¾"	73p
2½"×5"	83p
2½"×17"	£2.91
3¾"×3¾"	89p
3¾"×5"	95p
3¾"×17"	£3.28
4.7"×17.9"	£4.38

0.1" Plainboard (no strips)

3¾"×2½"	82p
3¾"×5"	78p
3¾"×17.9"	£2.11
Terminal pins	£1.80/500
V-Q RF board	£1.50
DIP breadboard	£3.99
Spot face cutter	£1.10
Pin insertion tool	£1.82

SOLDERCON PINS

100 50p 1000 £3.95

DIL SOCKETS

8/14/16 pin 10p/12p/13p
18/20/22 pin 18p/20p/22p
24/28/40 pin 30p/40p/50p
24 pin Textool lever type zero insertion force £7.80

EDGE CONNECTORS

43 way, 0.1" pitch, wire wrap, polarizing slot pin 37
Single sided (1×42) £3.11
Double sided (2×42)£4.10

TIMER ICs

NE555/556 29p/48p

OP-AMPS (All Mini dips)

CA 3130E	84p
CA 3140E	35p
UA 741 (Texas)	22p

LED DISPLAYS

DL-704E	99p
DL-727E/728E	£2.00
DL-747E/750E	£1.80
FND 500/560	£1.20

LIQUID CRYSTAL DISPLAY

4×0.5" Digits 40 pin DIL £8.75

CLOCK CHIPS

AY-5-1224A	£2.60
MK 50253	£5.80
MK 50366	£6.50

SIX DECADE COUNTERS

MK 50395/6/7	£8.90
MK 50398/9	£7.50

SWITCH MODE PSUs



AC 5221S 5V/10A	£89.90
AC 9221S 5V/5A, 12V/1A, −12V/1A, −5V/0.1A	£86.80
AC 5421S 5V/20A	£99.20
AC 9421S 5V/10A, 12V/2A, −12V/2A, −5V/0.1A	£126.50

OPEN CARD SWITCH MODE PSU

FULLY ASSEMBLED P.C.B. CARD 197 x 108 x 52mm. Outputs +5V/6A, −5V/0.5A, +12V/1A, −12V/1A.

Type AC9251 £79.80

FLOPPY DISK CONTROLLER BOARD

This is used in conjunction with 'Kemitron' Z80 boards to interface to twin single density S/S 8" floppy disks. It is not available as a bare board, but only built and tested. Regrettably Kemitron do not supply circuit diagram **£166.00**

To run CP/M on the system a serial interface (e.g. SIO board) to some sort of VDU or terminal is required, and 48K of RAM (e.g. three MXD-2 boards). The MZ8-3 board has facilities for 'power on jump' and a 'boot prom' to load the CP/M operating system from the disk.

Boot PROM (2708)	£10.95
CP/M (8" floppy disk)	£99.00

8" FLOPPY DISK DRIVES
DRE Model 7100 **£360.00**

60 KEY ASCII KEYBOARD

High quality. Capacitive switches, metal mounting frame £49.70

T.V. MONITOR P.C.B. for OEM users

This is an assembled P.C.B. size 130 x 190mm, which you add to your own 12"/14" black and white C.R.T. (90 degree, 20mm dia. neck), to obtain a T.V. monitor at modest cost. (Regrettably we cannot supply the C.R.T. at present.)

Preset controls, contrast, brightness, etc., are included, and the only inputs needed are 15 Volts ± 10% AC at 1.5 Amps and 1 Volt pk-pk composite video input.

Supplied with circuit diagram £33.50

KEYBOARD CASES

405 x 210mm. Panel size 330 x 188mm	£10.14
510 x 340mm. Panel size 430 x 115mm	£26.22

DOT MATRIX PRINTER

This is about the same price as for example the Anacom Imp, but has many features only previously found in models costing hundreds of pounds more:

Standard interfaces (not 'extras') RS-232, 20mA, NEC 488. Centronics I/O. 15 baud rates to 9600, 100 characters per second, 64, 72, 80, 96, 120 or 132 characters per line, rear, bottom or front paper loading, friction or tractor feed, can accept user defined characters, can also print graphics under program control, has 'self-test' facility. Supplied with mains cable and full operator's manual.

Base 2 Model 800 £325.00

QUME DAISYWHEEL PRINTER

High quality printer for use with word processing packages running under CP/M. 45 characters per second, RS-232 interface. (Check stock position before ordering.)

Qume Sprint 5 Model 45/RO	£1595.00
Also available on lease.	

QUME SUPPLIES AND ACCESSORIES

Forms Tractor	£110.00
Standard Printwheels	£6.60
Word Processing Printwheels	£8.80
Ribbons (in packs of 12)	
Medium Inked Fabric Black	£27.60
Multi Strike Black	£27.60
Single Strike Black	£40.55

EUROCARD 19" CARD FRAME

Kit of 2 end plates + angles, 2 front and 2 rear 16 bars, 4 guide location strips £28.84

Accessories

Card guides (pack of 10)	£1.53
Eurocard Plug (64 way DIN 41612)	£2.22
Eurocard Socket (64 way DIN 41612)	£3.38
Connector mounting strips (pair)	£3.27
Case conversion kit (or fit into separate 3U 19" D-type case)	£19.80 £32.58

MICROPROCESSORS

6502

6502	£8.95
6520/21	£4.95
6522	£8.95
6532	£8.25

Z80

Z80A-CPU	£7.93
Z80A-PIO	£5.75
Z80A-CTC	£5.75

8000

8080 MPU	£5.95
8802 MPU	£8.95
8809	£19.95
6810 (128 × 8 RAM)	£3.25
8A10 (128 × 8 RAM)	£3.75
8820, 6821 PIA	£3.50
6845	£22.30
6850 ACIA	£4.85
MC6880	£2.64

SC/MP II RAM I/O

SC/MP II (AMHz)	£10
INS 8154 RAM I/O	£9.40
INS 8255 I/O	£4.75

CMOS

COSMAC CDP 1802CE	£8.50
COSMAC CDP 1802E	£10.85
CDP 1854	£7.25

STATICS (Mostly 450nS)

2102–1K x 1	£1.20
2111–256 x 4	£2.25
2112–256 x 4	£2.25
2114/4045–1Kx 4	£2.25
8 x 2114	£15.36
2114L–1K x 4	£1.98
4118–1K x 8	£8.95

DYNAMICS

4116 16K 200nS	£1.99
8 x 4116	£15.36

UV ERASABLES

5204 (512 x 8)	£9.95
2708 1K x 8	£3.43
2716/2516 2K x 8 single 5v	£4.99
2532 4K x 8 (5v)	£14.95

5204/2708/2516 Programming Service £7.50/£7.50/ £15.00 each prom. (Price does not include prom. We accept handwritten/typed source code – must be hexadecimal)

PROM WASHING SERVICE
50p each prom

UV PROM ERASER

UV140	£61.20
UV141	£77.70
EPROMPT	£33.00

INTERFACE

81LS95/6/7/8	£1.60
1488 (RS232)	99p
75491 LED driver	59p
75492	82p
Z8425	£3.95
8T26/8T28	£2.64
1.74	48p
AY-3-8910	£8.50
FD 1771	£29.00

CRT Controller: Starts

AY-5-1013	£4.60
AY-5-1013A	£4.75
AY-3-1014A	£5.00
AY-3-1015	£5.00
6402	£4.50
1402	£4.50

CHAR. GEN. KEYBOARD ENCODER

MM 2302	£18.20
RO-3-2513 (Ne Uppercase)	£4.75
DM 8578 CAG	£14.27
AY-5-2376	£7.80

SOFTWARE

To suit Z80 Tiny Basic
Moonlander Game Cassette £1.00
Listing £1.00
Knights and Crosses Cassette £1.00
Listing £1.00

FIRMWARE

ZBASIC for Z80 (1 x 2708) £14.95
2K Tiny BASIC for Z80 (2 x 2708) £19.95
4K MBL for SC/MP (4 x 2708) £49.95
4K MBL-MON for SC/MP (4 x 2708) £40.95
1K Various, for SC/MP (1 x 2708) £14.95

(Descriptive leaflet available on above, incl SAE, 5p)

1K Elekter Junior (1x2708) £19.95
1¼K ELBUG (3 x 5204) £35.80
ETBUG 1 (1 x 5204) £14.95
ETBUG 2 (1 x 5204) £14.95
SCMP/KB (1 x 5204) £14.95

UHF MODULATORS

UM1111 E36 Video modulator, T.V. game or chomp computer type £2.80

UM1231 E36 Wide bandwidth, computer VDU type, pos./neg. transfer characteristic £4.95

UM1233 E36 Wide bandwidth, computer VDU type £4.70

UM1284 E36 Combined wide bandwidth video modulator with intercarrier sound, high performance £8.25

VOLTAGE REGULATORS

7805	75p
7808	£1.00
7812	97p
7912	£1.00
78H05	£5.61

VOLTAGE CONVERTER MODULES

Ideal for use in otherwise 5V only systems, to obtain +12V, −12V, or dual ± 12V power for ASCII keyboards, RS-232 interfaces, dynamic RAMs etc. All types need +5V input.

Size of each module (excluding pins) 34 x 28 x 10mm.

Type ADDP-12A10
+12V output, (25-84mA) £4.95
Type ADDN-12A10
−12V output, (25-84mA) £4.95
Type ADDD-12A10
± 12V dual output, 2 x (12-42mA) £9.25