Practical Electronics

DECEMBER 1964 PRICE 2/6

FREE INSIDE

2 BLUEPRINTS

TO BUILD

ULTRASONIC REMOTE CONTROL

DEC 64

QUALITY TAPE RECORDER
MT 1000 or TC 601. Fully Transistorised, Self-contained, Economical, Loudspeaker, Playback, Eraser, etc. **£8.19.6.**

PROFESSIONAL RECORDER
TP 703, Six Transistor, Capstan Drive, Two Speeds, Dual Track, Push-button Controls, Tape, Ideal Speech and Music, Many Refinements, **£16.16.0.**

INTERCOM OR BABY ALARM
Fully Transistorised, Low Running Cost, Super Performance, absolutely complete, **£3.19.6.**

TELEPHONE AMPLIFIER
TA790. Loudspeaker Speech by Transistor Amplifier with Magnetic Pick-up, only **59/6**

MULTIWAY INTERCOM SYSTEM
1P-7. Completely Transistorised Master Unit with Extension Indicators, Selector Switches, Volume Control, Completely Self-contained, Takes up to Six Extension Units, **14 Guineas.**

EXTENSION UNITS
2 Guineas each.

COMMUNICATION RECEIVER
RX. 60. 10-550 m. Continuous in Four Bands, 8 meter, Noise Limiter, Band Spread, B.F.O., 5" Speaker, etc., Three Aerials supplied giving professional reception, Quality Finish, **£24.15.0.**

PROFESSIONAL COMMUNICATION RECEIVER
RX 80. Double Superhet, Five Wave Band, Calibrated Electrical Band Spread on 80m, 40m, 20m, 15m, 10m Bands, S Meter, Q Amplifier, Aerial Trimmer, etc., **£45.0.0.**

12 VOLT 20 WATT P.A. AMPLIFIER
CA512. Ideal Street Broadcasting, Sports Events, Small Size, Terrific Performance, 4Ω, 8Ω, 16Ω, Output. 3 Inputs. **£22.**

10 WATT P.A. SPEAKERS
Compact Horn, High Efficiency, ideal for CA512 Amplifier. **£5.5.0.**

8-WATT STEREO AMPLIFIER
8A.80. Frequency Response 60-15,000 ±1db, Sensitivity 100 mV Stereo-Mono-Tuner-Phono, completely enclosed Gold/Black Quality Case, **£9.10.0.**

NEW LOWER PRICES
EAGLE PRODUCTS
COMPLETE WITH INSTRUCTIONS WHERE NECESSARY
SEND S.A.E. FOR FURTHER DETAILS OF ANY ITEM TO TECHNICAL TRADING CO., BRIGHTON

30-WATT STEREO AMPLIFIER
SA. 300. Superb Reproduction, Gold enclosed finish, Many features including Hum Balance, Speaker Phasing, Rumble Filter, Integrated Tone Controls, Five Inputs, Selector Switch, Function Switch, 4, 8 and 16 ohm Outputs, Fantastic Value, **£29.10.0.**

40-WATT TRANSISTOR STEREO AMPLIFIER
TSA. 218. Five Separate Inputs, Rumble Filter Scratch Filter, 18 Transistors, 115-240 VAC, Loudness Switch, Mode Switch, Input Selector, Bass-Treble Balance Volume Controls, Superb Quality, Years of Trouble-free Use, **£49.10.0.**

HIFI FM TUNER
FMT. 640. Matches above Amplifiers, Sensitive 8-valve Circuit, Superb Styling, A.F.C. Built-in Power Pack, Individually factory aligned, **19 Guineas** (+64/- P.T.).

LOUDSPEAKERS
DUAL CONE 8"
6-Watt, 50-16,000 C.P.S., 16 ohms, Total Flux 53,000, **67/3.**
CR.12.AE. 12"
Twin Cone Peak Power 20-Watts, 16 ohms, **7 Guineas.**
CR.30.AE.12"
Three-way Speaker, Woofer made Range Radiator and Tweeter all within single speaker system, Phenomenal Realism, 16 ohms, **9 Guineas.**
12" Ultra Linear Speaker, Peak 25-Watts, 86 ohms, Total Flxx 200,000, Unbelievable performance, **12 Guineas.**

SLIM AUDIO PANEL 601 SPEAKER SYSTEM
A Built-in Crossover Network, Amazingly Realistic Performance, Superbly Finished Walnut Cabinet 21¼" × 17½" × 4½", Response 50-18,000 C.P.S. 10-Watts, 16 ohms, **15 Guineas** (+50/6 P.T.).
AP.801. As above, but 20-Watts, 40-20,000 C.P.S., Size 29" × 21" × 4½", **21 Guineas** (+ 70/9 P.T.).

HORN TWEETER CT10
10-Watts, 15-18,000 C.P.S., 16 ohms, High Sensitivity, Amazing Value **27/6.**

HT.20. 20-Watts, Rectangular Heavy Cast Finish, 16 ohms, **69/6.**

MM-4 FOUR CHANNEL MICROPHONE MIXER
Ultra Compact, Fully Transistorised, Gain 6 db, Gold Finish, Four Volume Controls, Uses 9-V Battery, **49/6.**

MICROPHONES
MM-71. Crystal, Compact Finish, screened lead, jack plug, **12/6.**
100 C. Three-Way Crystal "Stick" mic., Professional Finish, Built In/Off Switch, Detachable Shielded Cable, Neck Cord, Chrome Finish, **32/6.** MS 100 Desk Stand to match, **8/-.**
DM614. Miniature Stick Dynamic Mike with Stand and Neck Cord, **32/6.**
MC. 70. Studio Crystal mic., 360° Pick-up includes Sensitive Variable "D" Cartridge, Complete Shielded Cable, Swivel Mounting, **52/6.**
DM.14.S. Miniature Dynamic mic. with Stand, Cradle Chrome Finish, **62/6.**
DM. 11. Dynamic mic. with Base, 360° Swivel, 60-12,000 C.P.S., Superb Mist Blue Finish, **5 Guineas.**
DM.16.HL. Dual Impedance Dynamic Striking Design, Outstanding Performance, Self-Adjusting Swivel Action, 40-15,000 C.P.S., 50 ohms Low, 50K High, **£4.9.6.**
DM.17.HL. As DM.16.HL. but Directional Heavy Chrome Stick, On/Off Switch, Stand Adaptor, **£4.2.6.**

MICROPHONE STANDS
MS.100 Desk Stand, Grey Base with Short Chrome Stick, Standard Fitting, **8/-.**
DS.2. Heavy Duty Desk Stand, **29/6.**
FS.3. Floor Stand, Heavy Duty Variable Height, Cast Iron Base, Takes Standard Microphones, **£2.17.6.**

PICK-UP ARMS
PP. 190. Adjusted Arm Rest, Mono/Stereo Quality Turnover Cartridge, Magnetic Stylus Pressure, Professional Finish, **39/6.**

MULTI-METERS
TK.20.A. 8 Ranges AC/DC/Current/Resistance 0-100K, Moving Coil, **49/6.**
EP.10.K. 10,000 OPV, High Quality, 15 Ranges AC/DC/Current/Resistance, Accuracy + or — 3%, **£3.19.6.**
EP.20.K. 20,000 OPV, more sensitive version of EP.10.K., **£4.19.6.**
EP.30.K. 30,000 OPV, 18 Ranges including Resistance to 10 meg., **£6.19.6.**
EP.50.K. Professional Quality, 22 Ranges, AC / DC / Volts / Current / Response / Decibels/Capacitance, **£9.19.6.**

TEST EQUIPMENT
1T1-1 Transistorised Signal Injector, Complete with Transistor Oscillator with Indicator Lamp, Detachable Test Probe and instructions, **35/-.**
RF Field Indicator RF.40. Tunes 1-250 Mc/S in Five Calibrated Bands with Telescopic, Aerial Earphone and UA Meter, **69/6.**

Tubes
HIGHEST QUALITY—COMPARE OUR PRICES

		GUARANTEED 6 Months	GUARANTEED 12 Months	NEW TYPES
Carr. & Ins. 12/6. MOST MULLARD, EMITRON, EMI-SCOPE, BRIMAR, MAZDA, COSSOR, FERRANTI TYPES	12 in.	£1.15.0	£3.10.0	MW 31/74 £4-0-0
	14 in.	£2. 0.0	£4. 0.0	NW 36/24 £5-0-0
	15/17 in.	£2.15.0	£4.15.0	CRM 173 MW 43/64 £6-0-0
	21 in.	£3.15.0	£5.15.0	

100 RESISTORS ½—2W. 6/6

100 CONDENSERS 10/-
Miniature Ceramic and Silver Mica.

SPECIAL TEMPORARY OFFER
Due to huge Bulk Special Purchase, we are offering **MW 31/74 Tubes** at the unrepeatable price of **29/-.** MW 36/24 ditto, **39/-.** P.P. 12/6. The above are guaranteed for 6 months.

SILICON RECTIFIERS
Guaranteed performance. Top Make. Tested 250V working.
100mA (3 for 9/6) **3/9** 500mA (3 for 19/6) **7/6**

4 watt AMPLIFIER
excellent amplifier with high gain preamp stage, 10 F3 driving 10 P14 output stage, complete with 8in. speaker. In attractive 2-tone case, Tone control, negative feedback, ready for immediate use, individually tested. Amazing volume and clarity, ideal for guitars, record players, p.a. in small halls, baby alarms, etc. Easily worth £5. Our price while stocks last. **47/6**
Carr., Packing, etc. 4/-

GERMANIUM DIODES
General Purpose miniature detector (or 6/6 doz.) **8d.**
Gold Bonded highest quality All tested. (or 9/6 doz.) **1/-**

TRANSISTORS
Top Quality
Huge reductions. **Red Spot** standard L.F. type now only 1/6; **White Spot** R.F. **2/-. Mullard Matched Output Kits** (OC81D and 2-OC81's), 12/6. **Receiver Kits,** OC44, OC45(2), OC81D, OC81(2), six transistors. **24/-**

AF102	15/-	OC26	12/6	OC81	5/6
AF114	8/-	OC36	14/-	OC81D	5/6
AF115	7/6	OC44	5/6	OC82	7/6
AF116	7/6	OC45	6/-	OC170	8/6
AF117	7/-	OC71	5/-	OC171	8/6
AF127	9/6	OC72	5/6	XB104	5/6

CO-AX standard and low loss, 25 yds, 12/6; 50 yds., 22/6; 100 yds., 42/6. Co-ax. Plugs 1/3. Wall outlet boxes 3/6.

CONDENSERS. 25 Mixed, Electrolytic. Many popular sizes. List value £5. Our price **10/-.**

CONDENSERS. Electrolytic, 25 popular sizes. List value £5. Our Price **10/-.**

25 TAG STRIPS, 2, 4, 6, 10-way, etc. **4/-**

12 POTS. Popular values. 5K to 2 Meg. Unused, mixed, pre-set, long sp., switch, etc. **4/6**

P.M. SPEAKERS. 3Ω Top Makes. 6½in. **7/6** 5in. 7×4in. **8/6**

MAINS TRANSFORMERS
Excellent Quality. Guaranteed Upright mounting 250-0-250V 60mA, 6.3V 3A Ditto semishrouded 9/6. Ditto upright 80 mA 12/6 **9/6**

100 HI STABS 9/6
1% to 5% 100Ω to 5MΩ.
EKCO L.O.P.T. unused replacements for Perspex cased 1954/7 models complete with E.H.T. rect. unrepeatable **39/-**

VALUE in VALVES
BY RETURN OF POST—
GUARANTEED 3 MONTHS

Satisfaction or Money Back Guarantee on goods if returned unused within 14 days.
ALL VALVES ARE NEW UNLESS OTHERWISE INFORMED.
FREE TRANSIT INSURANCE. POSTAGE 1 valve 6d., 2-11 1/-; FREE OVER 12.

OZ4	4/6	6K8GT	8/3	14S7	14/6	EBC41	6/3	EZ41	5/9	R19	9/6
1A7GT	9/6	6K25	8/6	19AQ5	7/9	EBC81	5/9	EZ80	5/9	SP41	2/3
1C5GT	7/6	6L1	9/6	20D1	8/9	EBF80	7/6	EZ81	6/-	SP61	2/-
IH5GT	8/9	6L6	7/6	20F2	9/6	EBF89	7/9	FC4	8/-	T41	6/9
1N5GT	8/9	6L6G	6/6	20L1	16/-	EBL21	9/9	GZ32	7/6	TDD4	7/-
1S4	7/6	6L18	7/9	20P1	9/6	EBL31	19/6	HVR2	9/-	U14	7/6
2D21	5/6	6L19	12/6	20P3	11/-	EC52	4/9	KT33C	3/9	U18	7/6
3A4	4/-	6LD20	7/9	20P4	17/-	ECC32	4/-	KT36	14/-	U22	6/9
3A5	6/-	6P25	8/6	25A6G	8/-	ECC34	9/-	KT44	6/-	U24	12/6
3D6	4/-	6P28	9/9	25L6GT	7/9	ECC40	6/9	KT45	8/6	U25	8/3
3Q4	5/-	6Q7G	4/-	25Z4G	7/-	ECC81	4/9	KT61	8/6	U26	7/-
5R4GY	8/-	6Q7GT	8/-	30F5	6/-	ECC82	4/9	KT73	5/9	U35	12/6
5U4G	4/-	6SA7	5/9	30FL1	9/6	ECC83	5/9	KT66	12/-	U50	4/6
5Y3G	4/6	6SG7	4/9	30L15	8/9	ECC84	7/6	KT76	8/6	U107	12/6
5Y3GT	4/-	6SK7	5/-	30P4	9/6	ECC85	6/-	KT88	17/6	U191	9/-
5Z4	9/-	6SL7GT	5/6	30P12	7/-	ECC88	9/6	KTW61	5/9	U281	8/6
5Z4G	7/-	6SN7GT	4/6	30PL1	9/3	ECF80	6/-	KTW63	5/-	U282	15/-
5Z4GT	9/6	6SQ7	5/9	35C5	8/6	ECF82	8/3	KTZ63	7/-	U301	12/6
6/30L2	9/-	6U4GT	8/-	35L6GT	8/-	ECH21	11/6	MU14	7/-	U329	8/6
6A8G	7/9	6V6G	4/6	35W4	6/-	ECH35	7/6	N37	10/6	U801	19/-
6AG7	7/6	6V6GT	6/-	35Z4GT	5/6	ECH42	8/6	N78	13/-	UABC80	7/-
6AK5	4/3	6X4	4/6	50L6GT	8/6	ECH81	7/-	N108	13/-	UAF42	7/9
6AL5	5/-	6X5G	5/-	80	5/-	ECH83	6/3	PC86	10/-	UB41	6/6
6AT6	5/-	6X5GT	5/6	185BT	19/6	ECL80	6/6	PC97	7/6	UBC41	7/6
6AV6	7/-	7B6	9/-	185BTA	19/6	ECL82	8/-	PCC84	6/6	UBC81	6/-
6AV6	6/-	7B7	5/6	807(A)	5/-	ECL83	10/6	PCC85	6/6	UBF80	7/9
6BA6	5/6	7C5	7/3	807E	4/9	ECL86	10/3	PCC88	11/9	UBF89	7/6
6BE6	5/6	7C6	7/6	813	49/-	EF36	3/-	PCC89	8/6	UBL21	9/6
6BG6G	15/-	7H7	5/-	866A	12/6	EF39	4/6	PCC189	13/6	UCC85	7/3
6BH6	5/-	7S7	8/9	954	3/6	EF40	11/-	PCF80	6/9	UCF80	8/6
6BJ6	5/-	7Y4	4/6	955	2/3	EF41	8/-	PCF82	6/-	UCH21	9/3
6BR7	8/6	10C1	9/-	956	2/-	EF54	3/3	PCF84	12/-	UCH42	7/3
6BW6	6/9	10C2	14/6	9001	3/6	EF80	3/6	PCF86	7/6	UCH81	7/9
6BW7	5/-	10F1	4/9	9002	4/9	EF85	6/-	PCL82	7/9	UCL82	8/-
6C4	2/3	10LD11	14/6	9003	5/6	EF86	7/6	PCL83	9/-	UCL83	10/-
6C5	5/6	10P13	8/6	ATP4	2/6	EF89	6/9	PCL84	7/3	UF41	6/6
6C6	5/6	10P14	9/6	AZ31	6/-	EF91	3/-	PCL85	7/6	UF42	4/9
6C9	11/-	12AH7	7/-	B36	4/6	EF92	3/-	PCL86	10/6	UF80	6/3
6CD6G	17/-	12AH8	9/-	CBL31	19/-	EF183	9/9	PEN25	3/9	UF85	7/6
6D6	3/-	12AT6	6/6	CL33	9/-	EF184	9/6	PEN45	8/6	UF89	5/9
6F1	4/9	12AT7	4/9	CY31	7/6	EL32	3/9	PEN46	4/6	UL41	7/6
6F6G	3/6	12AU6	9/-	DAF91	4/6	EL33	6/6	PL33	8/6	UL44	14/-
6F13	4/3	12AU7	4/9	DAF96	7/3	EL34	11/6	PL36	9/6	UL46	8/3
6F14	9/6	12AV6	6/3	DF91	3/-	EL35	6/-	PL38	17/6	UL84	7/-
6F15	9/6	12AX7	6/-	DF92	3/-	EL38	12/6	PL81	7/9	UR1C	7/6
6F23	6/6	12BA6	7/-	DF96	7/3	EL41	8/-	PL82	6/6	UM80	9/6
6J5G	3/-	12BE6	6/6	DK91	5/6	EL42	7/9	PL83	6/6	UU6	8/9
6J5GT	4/3	12BH7	8/9	DK92	7/-	EL84	6/6	PL84	7/6	UU8	11/-
6J6	2/6	12E1	17/6	DK96	7/3	EM34	8/6	PY31	8/-	UY21	9/6
6J7G	4/9	12J7GT	8/-	DL92	5/-	EM80	7/9	PY32	10/-	UY41	6/-
6J7G7	7/6	12K7GT	4/-	DL94	6/6	EM81	6/9	PY80	6/6	UY85	5/-
6K6GT	6/-	12K8	9/9	DL96	7/3	EM84	8/9	PY81	5/9	VR105	5/6
6K7	5/9	12K8GT	9/6	EABC80	6/6	EM85	8/6	PY82	5/9	VR150	5/-
6K7G	1/-	12Q7GT	5/-	EAF42	3/3	EY51	7/6	PY83	5/9	X66	7/9
6K7GT	4/6	12SA7	6/3	EB41	5/-	EY86	7/3	PY88	9/-	6	6/-
6KS	8/6	12SK7	2/9	EB91	2/-	EY88	8/6	PY800	6/3	Z66	8/6
6K8G	5/-	12SQ7	7/6	EBC33	4/9	EZ40	6/8	PZ30	9/6		

Post: 2 lbs. 2/-, 4 lbs. 2/6, 7 lbs. 3/6, 15 lbs. 4/-, etc. (C.O.D. 2/- extra). ALL ITEMS LESS 5% AND POST FREE IN DOZENS.

TECHNICAL TRADING CO.

SHOPS RETAIL ONLY
350-352 Fratton Road, Portsmouth (Tel. 22034)
72 East Street, Southampton (Tel. 25851)
ALL MAIL ORDER, RETAIL SHOP AND HI-FI ROOM
11-12 NORTH ROAD, BRIGHTON. Tel. 67999

Amplifier by

Be first to own the only amplifier of its kind in the world

10 WATT OUTPUT

NO HEAT SINK

1mV INPUT SENSITIVITY

GIVES FANTASTICALLY GOOD REPRODUCTION


THE SINCLAIR X-10 is a high fidelity integrated power amplifier and pre-amp using 11 transistors and having a transformerless output of 10 watts for feeding into a 15 ohm loudspeaker system. It requires only the addition of tone and volume controls plus a twelve volt D.C. power supply to make it a complete mono high fidelity assembly of exceptional quality. Stereo is achieved by using two X-10 amplifiers and ganged or separate controls. Input sensitivity is sufficient for all crystal or magnetic pick-ups and the manual supplied with the X-10 gives detailed instructions for connecting the controls and for using the amplifier in a wide variety of applications.

This radically new transistor amplifier (patents applied for) is the first to be marketed anywhere in the world using the Pulse Width Modulation principle (P.W.M.).

This technique permits an enormous reduction in the power dissipation in the output transistors of an amplifier; and in the case of the Sinclair X-10, the output efficiency is about 95% as compared with about 60% for conventional class B output stages. Thus the dissipation is only $\frac{1}{8}$th or less of that occurring in all other amplifiers. That is why no heat sink is used and why the X-10 will operate from two 4/- batteries with normal use for about 3 months.

NEW *DESIGN PRINCIPLES PERFORMANCE* !

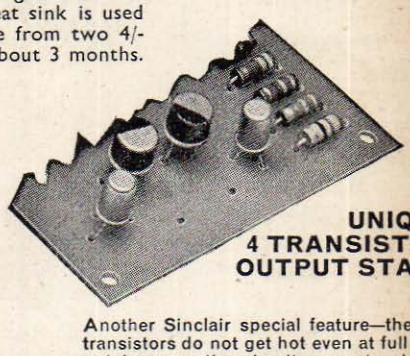- ★ **Number of transistors 11**
- ★ **Overall size 6″ x 3″ x ¾″**
- ★ **Input Sensitivity 1mV**
- ★ **Total harmonic distortion < 0·1%**
- ★ **Output power 10 watts**
- ★ **Frequency response 5-20,000 c/s ± 0·5dB**
- ★ **Speaker impedance 15Ω**
- ★ **Damping factor Greater than 100**
- ★ **Quiescent consumption 75mA**
- ★ **Supply voltage 12 to 15 volts**



UNIQUE 4 TRANSISTOR OUTPUT STAGE

Another Sinclair special feature—these 4 transistors do not get hot even at full output because the circuit converts almost 100% of the power from battery or mains unit into audio power for the loudspeaker.

SINCLAIR X-10

COMBINED 10 WATT AMPLIFIER & PRE-AMP

Guarantee

If you are not completely satisfied with your purchase (we are confident you will be delighted) your full purchase price will be refunded instantly and without question.

FULL SERVICE FACILITIES ALWAYS AVAILABLE TO SINCLAIR CUSTOMERS

Build it for

£5-19-6

inclusive of all parts and instructions manual

READY BUILT AND TESTED


£6-19-6

including instructions manual

ANOTHER WINNING DESIGN FROM **SINCLAIR RADIONIC**

Breakthrough

SINCLAIR

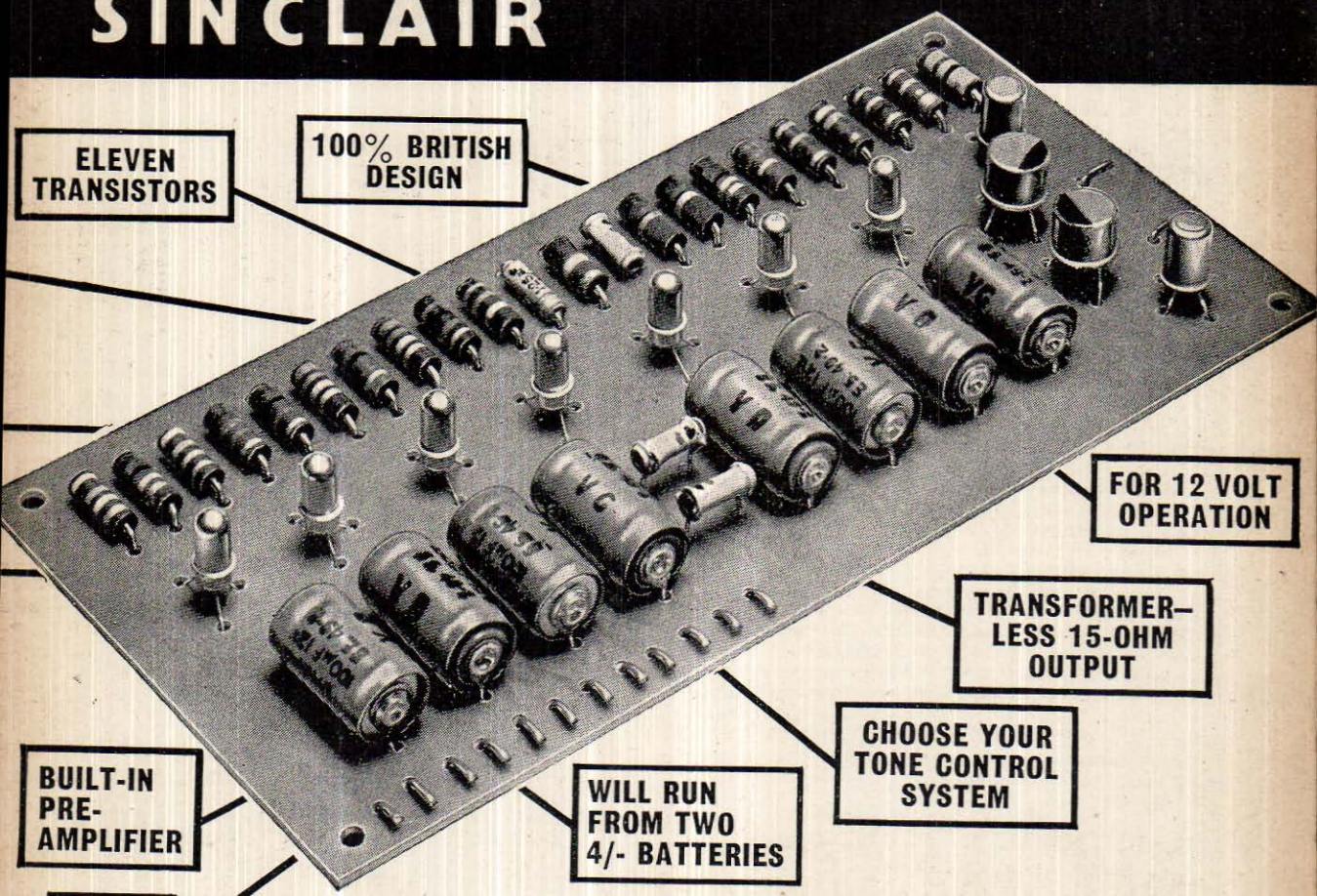

PWM *is the answer!*

THE SINCLAIR X-10 is the only amplifier in the world to give you the unique benefits of Pulse Width Modulation. Briefly, with this system, the audio signal from pick-up, radio, microphone or tape head modulates a high-frequency square wave "carrier" by varying the mark-space ratio. These variations are converted to energy in the output stage. Being independent of the transfer characteristics of the output transistors, the output is an exact replica of the input signal. The improvement in the quality of reproduction from the loudspeaker is instantly apparent. Transient response is much clearer, there is no falling off in the higher audio-frequencies, no intermodulation distortion and the response curve so flat you could draw it with a ruler! A new type of output stage and P.W.M. plus many other circuit refinements result in an amplifier which is compact, rugged, stable and does not require a heat sink—and it costs so little. The X-10 may be used with low-input pick-ups such as Decca Deram, Ortofon, etc., as well as with tape playback heads. Used in pairs the X-10 brings new depths to stereo listening and there are no channel matching problems.

SINCLAIR X-10 MANUAL

supplied with every every X-10, built or in parts, this 12 page manual explains how the amplifier functions and how you can add the correct tone and volume control system to suit your requirements exactly. A variety of systems is shown for mono and stereo use, none of which will add more than a few shillings to the original cost of your Sinclair X-10 amplifiers.

FREE WITH AMPLIFIER. AVAILABLE SEPARATELY, PRICE 1/-.

MAINS POWER SUPPLY UNIT (A.C. 200/240V)

£2-14-0

* *Order form and further Sinclair designs on next pages*

EWH

LTD. COMBERTON, CAMBRIDGE. Telephone COMBERTON 682


sinclair

Micro-

GUARANTEED DESIGNS FOR THE CONSTRUCTOR

It's easy to build the SMALLEST RADIO IN THE WORLD


THE SINCLAIR MICRO-6 is an entirely British design which remains unchallenged as the most remarkable receiver of its kind ever made available to the public anywhere in the world. It has special 6-stage circuitry and is, at the same time, the smallest set on earth. Everything except the lightweight earpiece is contained in the smart, minute white, gold and black case which is appreciably smaller than a matchbox, as the illustration shows. With vernier-type tuning control, bandspread over the higher frequency end of the medium waveband and powerful A.G.C. to ensure fade-free reception of the most distant stations, the Micro-6 provides remarkable standards of performance. Quality of reproduction is outstandingly good and, again and again, the set is reported to give excellent results where other sets cannot be used at all. The Micro-6 cannot be too highly recommended, both as an intriguing design to build, and a most practical radio to use. Over 9,000 have been built and are in daily use throughout the world.

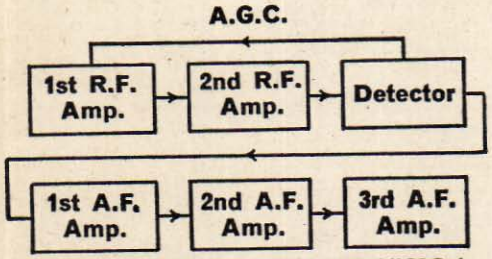

BLOCK DIAGRAM OF SINCLAIR MICRO-6

SIX-STAGE POWER AND SELECTIVITY

The Micro-6 uses special Sinclair Micro-Alloy Transistors in a completely new circuit. Two stages of R.F. amplification are followed by an efficient double diode detector which drives a high-gain 3-stage A.F. amplifier. Powerful A.G.C. applied to the first R.F. stage ensures fade-free reception from the most distant stations tuned in. Everything including micro-components never before made available to home constructors, special ferrite-rod aerial and 2 batteries each smaller than an aspirin tablet and giving about 70 hours working life is contained within the elegant tiny case.

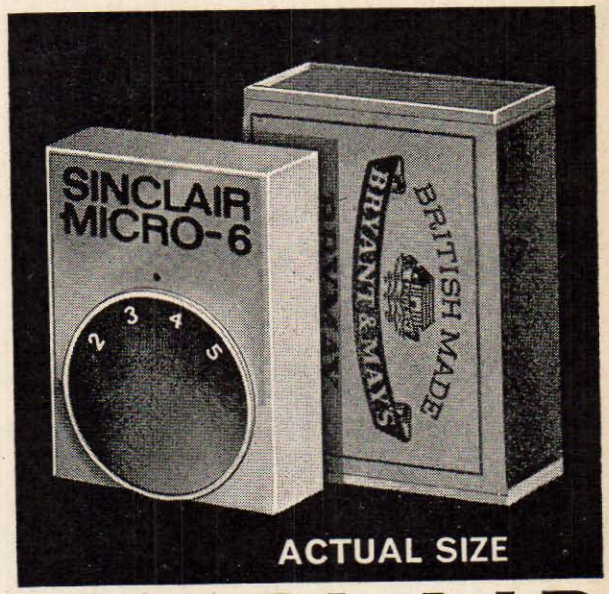

SINCLAIR MICRO-6

SIX-STAGE POCKET RECEIVER

Build it in an evening!

59/6

Building is simple and straightforward when the meticulously detailed instructions are followed. All parts including MAT transistors, diodes, printed circuit board, lightweight earpiece, case and dial, and 8-page instruction manual come to

'TRANSRISTA' black nylon wrist strap for wearing the Micro-6 like a wrist watch (*see illustration opposite*) **7/6**

MALLORY MERCURY CELL ZM312 (*two required*) each **1/11** Special pack of 6 **10/6**

- **SIZE** $1\frac{1}{5}'' \times 1\frac{3}{10}'' \times \frac{1}{2}''$
- **WEIGHT** Less than 1 oz. (with batteries)
- Tunes over medium wave band
- Bandspread over higher frequency and brings in Luxembourg like a local station
- Vernier-type tuning
- Plays in car, train, bus, plane, etc.
- Brings in Continental as well as B.B.C. stations
- Can be used as a radio-jack for tape-recorders
- Wonderful quality, tone and volume


Full service facilities available to all Sinclair customers

sinclair

SINCLAIR RADIONICS LTD., COMBERTON, CAMBRIDGE
Telephone: COMBERTON 682

Masterpieces

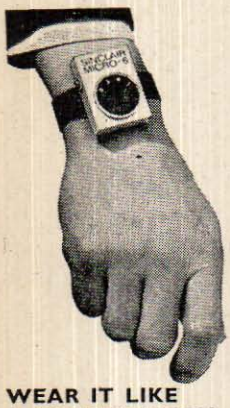FROM BRITAIN'S LEADING TRANSISTOR SPECIALISTS




WEAR IT LIKE A WRIST WATCH

A novel and convenient way to use the Micro-6 is to fix it on to the 'Transrista' Wrist Strap and wear it like a watch. Particularly useful for sportsmen, travellers, etc.



SPORTS EVENTS

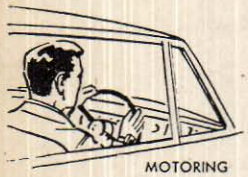

MOTORING




TRAVELLING

SINCLAIR TR750 POWER AMPLIFIER

Designed specially for use with the Micro-6 and Slimline Receivers

★ **MAKES A CAR RADIO, DOMESTIC RADIO, PORTABLE, INTERCOM, Etc.**

MEASURES 2″ x 2″

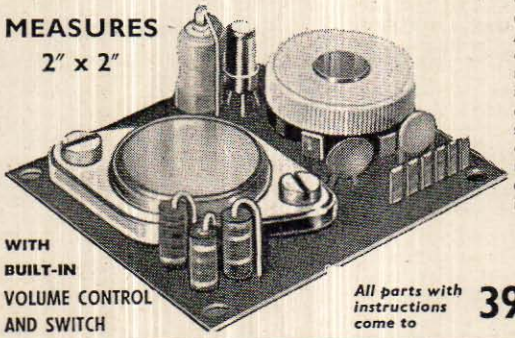

WITH BUILT-IN VOLUME CONTROL AND SWITCH

Measures only 2in. x 2in. yet includes its own volume control and switch. It will provide powerful loudspeaker reproduction from the Micro-6 or Slimline which can then be used as a car radio, or domestic or portable loudspeaker set. A plug is supplied for connecting to either Sinclair set. The TR750 also has many other applications such as record reproducer, intercom or baby alarm. An output of 750 milliwatts for feeding into a standard 25-30Ω loudspeaker requires only a 10mV input into 2KΩ. Frequency response 30-20,000 c/s ± 1dB. Power required 9 to 12 volts. Assembling and installing is very easy.

ANOTHER OUTSTANDINGLY SUCCESSFUL SINCLAIR DESIGN.

All parts with instructions come to **39/6**

READY BUILT AND TESTED with instructions **45/-**

UNIQUE SINCLAIR Guarantee

The following unconditional guarantee applies to everything you buy from Sinclair Radionics Ltd.:—

If you are not completely satisfied with your purchase immediately on arrival (we are confident you will be delighted) your full purchase price will be refunded instantly and without question.

● **FULL SERVICE FACILITIES AVAILABLE TO ALL SINCLAIR CUSTOMERS**

Post your order today

SINCLAIR SLIMLINE

The extra-easy-to-build 4-stage pocket receiver



Particularly recommended for newcomers to transistor set building. Measures 2¼″ x 1¾″ x 1″. Everything is contained within the gold-trimmed royal blue case, including standard PP.5 battery and ferrite-rod aerial. Uses vernier-type tuning to cover the medium waveband with reception of many British and Continental stations. Listening is by means of the featherweight earpiece which switches the set on when plugged in. The building instructions make success assured, even if you have never built a set in your life. Operates from a standard PP5 battery, obtainable anywhere.

All parts inc. case, transistors, earpiece and instructions come to **49/6**

If you do not wish to cut the coupon from this page, please mention "Practical Electronics," December, when ordering

To SINCLAIR RADIONICS LTD., COMBERTON, CAMBRIDGE

Please send items detailed below:— £ s. d.

.....

.....

.....

.....

TOTAL £

For which I enclose CASH/CHEQUE/MONEY ORDER

NAME.....

ADDRESS.....


.....

..... Pre. 12

Why NOT BUILD ONE OF OUR PORTABLE TRANSISTOR RADIOS...

BACKED BY OUR SUPER AFTER SALES SERVICE

ROAMER SEVEN Mk III

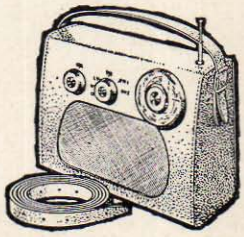

5 WAVEBAND PORTABLE OR CAR RADIO

Amazing performance and specification ★ *Now with PHILCO MICRO-ALLOY R.F. TRANSISTORS*


● **9 stages—7 transistors and 2 diodes**

Covers Medium and Long Waves, Trawler Band and two Short Waves to approx. 15 metres. Push-pull output for room filling volume from rich toned heavy duty 5in. speaker. Air spaced ganged tuning condenser. Ferrite rod aerial for M & L Waves and telescopic aerial for S Waves. Real leather-look case with gilt trim and shoulder and hand straps. Size 9 × 7 × 4in. approx. **The perfect portable and the ideal car radio.** (Uses PP7 battery available anywhere).

Total cost of parts now only **£5.19.6** P. & P. 5/6

Parts Price List and easy build plans 3/-

TRANSONA FIVE

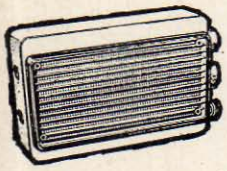


Home, Light, A.F.N., Lux. all at good volume.
G.P. Durham

● **7 stages—5 transistors and 2 diodes**

Fully tunable over Medium and Long Waves and Trawler Band. Incorporates Ferrite rod aerial, tuning condenser, volume control, new type fine tone super dynamic 2¾in. speaker, etc. Attractive case. Size 6½ × 4½ × 1¼in. with red speaker grille. (Uses 1289 battery available anywhere.)

Total cost of all parts now only **42/6** P. & P. 3/6 *Parts Price List and easy build plans 2/-*

MELODY SIX

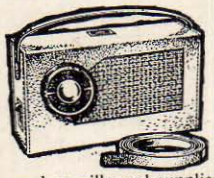


"... amazed at volume and performance, has really come up to my expectations". S.G., Stockton-on-Tees.

● **8 stages—6 transistors and 2 diodes**

Our latest completely portable transistor radio covering Medium and Long Waves. Incorporates pre-tagged circuit board, 3in. heavy duty speaker, top grade transistors, volume control, tuning condenser, wave change slide switch, sensitive 6in. Ferrite rod aerial. Push-pull output. Wonderful reception of B.B.C. Home and Light, 208 and many Continental stations. Handsome leather-look pocket size case, only 6¾ × 3¾ × 1⅞in. approx. with gilt speaker grille and supplied with hand and shoulder straps.

Parts Price List and easy build plans 2/- Total cost of all parts now only **£3.9.6** P. & P. 3/-

TRANSONA SIX

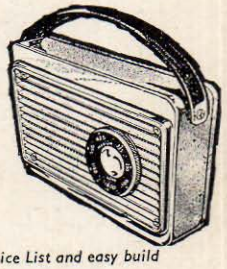

● **8 stages—6 transistors and 2 diodes**

This is a top performance receiver covering full Medium and Long Waves and Trawler Band. High-grade approx. 3in. speaker makes listening a pleasure. Push-pull transformers for ample power. Ferrite rod aerial. Many stations listed in one evening including Luxembourg loud and clear. Attractive case in grey with red grille. Size 6½ × 4½ × 1¼in. (Uses PP4 battery available anywhere.)

Total cost of all parts now only **59/6** P. & P. 3/6 *Parts Price List and easy build plans 2/-*

COMPONENT BARGAINS ALL POST FREE

TRANSISTORS

PHILCO MADT Type 2N1727 Maximum frequency of oscillation 150 Mc/s .. .. 8/6.

PHILCO MADT Type 2N1728 Maximum frequency of oscillation 150 Mc/s ... .. 9/6.

PHILCO MADT (Micro Alloy Diffused) Type 2N503 Maximum frequency of oscillation over 500 Mc/s 15/-

Diodes 1/6

Standard interleaved output transformers for valve output stages 3/6

SWITCHES

Slide, single pole, heavy springs 2/3

Yaxley 6-way, 2 pole .. 4/9

TUNING CONDENSERS

Air spaced fine quality German manufacture with slow motion drive. 0·0005 with oscillator section 9/6

Subminiature similar 00 with tuning and oscillator sections 7/6

Subminiature mica dielectric with trimmers. Tuning 200 pf. Oscillator 50 pf 5/6

Mica dielectric 0·0003 mfd. 3/10

BELLPHONES

Ex-G P.O. Suitable as sound powered telephones. Resistance of coil 60 ohms approx. 3in. U-shaped magnet .. 5/9

HEADPHONES

High fidelity miniature magnetic earpieces (2) on slim band with lead and plug. Easily converted to stereo. American manufacture 13/6

Miniature crystal earpiece with lead plug and socket 6/6

DIALS AND KNOBS

3in. dial with polished brass insert and M/L calibrated disc 6/6

1in. cream knobs with polished brass insert and rim 1/3 each


CASES

Real leather-look cases in chestnut shade with holes punched for tuning, volume control and switch. Also holes punched for car aerial socket and tone control. 9½ × 3½ × 7½in. approx. Complete with carrying straps 35/-

Plastic cases in grey polystyrene with red ornamental grille, 6½ × 4½ × 1¼in. approx. 6/9

Telescopic aerials with fixing socket 6/6

SUPER SEVEN

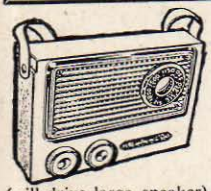


● **9 stages—7 transistors and 2 diodes**

Covers Medium and Long Waves and Trawler Band. The ideal radio for home, car, or can be fitted with carrying strap for outdoor use. Completely portable—has built-in Ferrite rod aerial for wonderful reception. Special circuit incorporating 2 RF Stages, push-pull output, 3in. speaker (will drive large speaker). Size 7½ × 5½ × 1¼in. (Uses 9v battery, available anywhere.)

Total cost of all parts now only **£3.19.6** P. & P. 3/6 *Parts Price List and easy build plans 2/-*

ROAMER SIX *NEW!!*

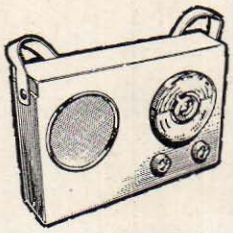NOW WITH PHILCO MICRO-ALLOY R.F. TRANSISTORS



● **6 WAVEBAND!!**

● **8 stages—6 transistors and 2 diodes**

Listen to stations half a world away with this 6 waveband portable. Tuneable on Medium and Long Waves. Trawler band and three Short Waves. Sensitive Ferrite rod aerial and telescopic aerial for short waves. Top grade transistors, 3-inch speaker, handsome case with gilt fittings. Size 7½ × 5½ × 1¼in.

★ Extra band for easier tuning of LUX., etc.

Parts Price List and easy build plans 2/- Total cost of all parts now only **£3.19.6** P. & P. 3/6 (Carrying Strap 2/6 extra.)

All components used in our receivers may be purchased separately if desired. Parts price lists and easy build plans supplied free with sets of parts or available separately at fixed prices stated.


RADIO EXCHANGE Ltd.

61a, HIGH STREET, BEDFORD. Phone: 2367

Callers side entrance Barratts Shoe Shop Open 9—5 p.m. Sats. 10—12.30 p.m.

CLOSED-CIRCUIT T.V. CAMERAS

Ideal for..

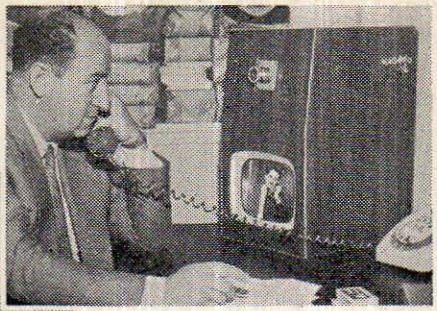



Excellent for Information Booths, Buyers' Offices, Hotel Reception, Paging, Holiday Camps, Hospitals, Night Clubs, Personnel Officers, etc.

AN UNREPEATABLE OPPORTUNITY FOR THE ENTHUSIAST!

The Components alone are worth Double

Manufacturers' Discontinued Line– BRAND NEW AND READY ASSEMBLED (But not Tested)

2-WAY VISUAL PHONE LINK





STUDIO DESK FOR MASS INSTRUCTION

Your own private C.C.T.V. System for Overflow Audiences, Dramatic Groups, Film Societies, Exhibitions, Demonstrations, Meetings, and a MUST for Technical Colleges, etc.





TRAFFIC CONTROL

Security, Time and Study, Building Sites, Gate Control, Bus/Railway Terminals, Sales Promotion, etc.

- ★ Fully Transistorised 100% Reliable
- ★ 405 LINE R.F. Band 1. Channels 1 to 5
- ★ Plugs in aerial socket of any size Domestic T.V. Set
- ★ Mains operated, 210/250 v. A.C. 50/60 cycle
- ★ C type 16 mm. cine lens mount (excluding lens)
- ★ Horizontal Resolution $2\frac{1}{2}$-3 M/cs.
- ★ 4 to 6 T.V. Sets can be used off one Camera
- ★ Weighs only 4lbs. Truly Miniature



Post & Ins. 28/-

LESS VIDICON TUBE AND LENS

E.M.I. VIDICON TUBES and 1" f1-9 LENSES for above (Each) **£9.19.6**


HORNTONS ELECTRONICS **LOMBARD HOUSE, GT. CHARLES STREET** (Next to Pan American Airways) **BIRMINGHAM 3.** *Phone: Cen 6283 or MID 0972*

SOLDER WITH
PRIMAX and PRIMAXA
SUPER EFFICIENT SPOTLIGHT SOLDERING GUNS




Distributors: S. KEMPNER LTD., LONDON, W.1
29 PADDINGTON STREET, Tel.: HUNter 0755

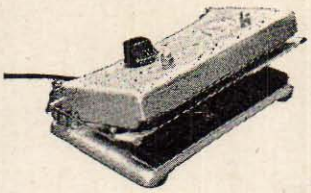
zeva
BRAND
HAND AND FOOT-OPERATED SEALING TOOLS FOR ALL KINDS OF PLASTICS



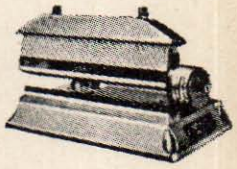The "PACKFIX" for cellophane and polythene bags. Hand or foot-operated, all voltages. From £10.



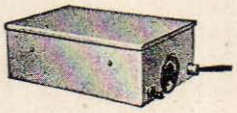
FLT cellophane and polythene bag sealer. Foot operated or magneto electrically driven. Seals bags up to 15¼" width. From £42.



Hot plates thermostatically controlled. Small and large sizes for cellophane, polythene and shrinking foils. From £12.

LET US SOLVE YOUR SEALING PROBLEMS.
WRITE FOR COMPLETE ILLUSTRATED LISTS TO DISTRIBUTORS:
S. KEMPNER LTD., 29 PADDINGTON ST., LONDON, W.1
TEL.: HUNTER 0755

YOURS FREE FOR 7 DAYS

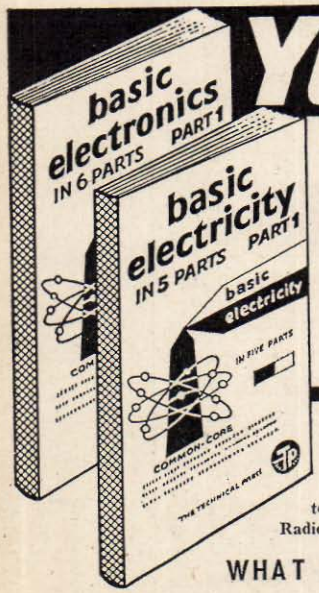

The New 'Picture-Book' way of learning
BASIC ELECTRICITY (5 VOLS.) ELECTRONICS (6 VOLS.)

You'll find it easy to learn with this outstandingly successful new pictorial method—the essential facts are explained in the simplest language, one at a time; and each is Illustrated by an accurate, cartoon-type drawing.

The books are based on the latest research into simplified learning techniques. This has proved that the Pictorial Approach to learning is the quickest and soundest way of gaining mastery over these subjects.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

"After reading section on Filter Circuits once, I understood more about them than in a whole year from the obscurities of other manuals." L.G. West Wickham. *"I must say they are the best books on the subject as they explain in simple language what other books make hard going of."* C.B. Hartlepools. *"They have a wonderful system of imparting the subject to the beginner."* H.C.L. Leicester. *"What a contrast to the many text books I have attempted to struggle through."* J.G. Rugby.

A TECH-PRESS PUBLICATION.

To Selray Book Co.
60 Hayes Hill, Hayes, Bromley, Kent

Please send me Without Obligation to Purchase, Basic Electricity/Basic Electronics on 7 Days' Free Trial. I will either return set, carriage paid, in good condition within 8 days or send down payment of 15/- (Basic Electricity) followed by 6 fortnightly payments of 10/-. Down payment of 15/- (Basic Electronics) followed by 6 fortnightly payments of 12/6. Alternatively, I will send 68/- (Basic Electricity—5 parts). 81/- (Basic Electronics—6 parts) post free. This offer applies to United Kingdom only.

Tick against set required (*only one set allowed on free trial*).
BASIC ELECTRICITY ☐ BASIC ELECTRONICS ☐

Signature.....
(*If under 21, signature of parent or guardian*)

Name .....
BLOCK LETTERS BELOW

FULL POSTAL Address P.E.1

POST NOW FOR THIS OFFER!!

SURBITON PARK RADIO LTD.

ALL ORDERS DESPATCHED SAME DAY ● **WE PAY POSTAGE AND INSURANCE**


SATISFACTION OR MONEY REFUND GUARANTEE

LEADING STOCKISTS OF MARTIN RECORDAKITS AND AUDIOKITS


MARTIN RECORDAKITS

		Dep.	&	Mthly. pmts. of
HALF TRACK				
TAPE AMPLIFIER FOR STUDIO DECK, with ready wired printed circuit, control and input panels, mains and output transformers, knobs, plans, screws etc.; EF86, ECC83, EZ80, EM85 and 2 EL84. 3 watts output. Magic eye, Radio & Mic. inputs, ext. speaker socket, tone and monitor controls. Can be used as an amplifier	£11.11.0	47/-	8	25/6
COLLARO STUDIO DECK, very latest model, 3 speeds, 3 motors, 7in. spools	£10.19.6	44/-	8	24/6
CASE for above with 8 × 5in. speaker, tone grey	£5.5.0			
COMPLETE KIT with tape and microphone	£29.19.6	120/-	12	44/-
QUARTER TRACK				
TAPE AMPLIFIER FOR STUDIO DECK, as above.	£12.12.0	52/-	8	27/6
COLLARO STUDIO DECK, fitted Marriott "X" Series heads	£13.19.6	56/-	12	20/6
CASE as above, two tone grey	£5.5.0			
COMPLETE KIT with tape and microphone...	£33.19.6	136/-	12	49/10
TAPE PRE-AMPLIFIERS				
HALF TRACK for **STUDIO** deck, 400m/V out.	£8.8.0	34/-	6	25/8
QUARTER TRACK, as above **SELF POWERED**	£9.9.0	39/-	6	28/4
TAPE HEADS, Bradmatic Half-Track Record/Replay and Erase on plate	£1.19.6	—	—	—

ARMSTRONG AMPLIFIERS AND TUNERS

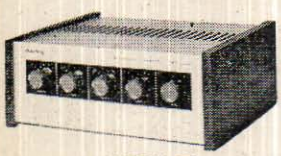

MODEL 222

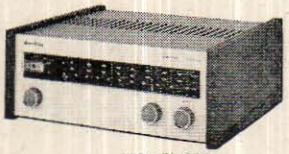

MODEL 223

222 Integrated Stereo Amplifier 10 + 10 watt..	£27.10.0	110/-	12	40/4
223 A.M.-F.M. Tuner	£28.15.0	115/-	12	42/2
224 F.M. Tuner	£22.10.0	90/-	12	32/2
127/M Mono Tuner/Amplifier 5 watt	£26.10.0	106/-	12	38/10
127 Stereo Tuner/Amplifier 5 + 5 watt	£37.10.0	150/-	12	55/-
227M Mono Tuner/Amplifier 10 watt	£36.15.0	147/-	12	53/-
227 Stereo Tuner/Amplifier 10 + 10 watt	£52.15.0	211/-	12	77/4
226 Stereo Tuner/Amplifier as 227 but with Mag. P.U.	£61.0.0	260/-	12	88/-
Shelf mounting Teak Case for any of above	£3.10.0			

MONO AMPLIFIERS

Linear L 45/A, 3 valve, 3 watt.	£6.6.0			
Dulci GA5, Integrated, 5 watts ECL86	£13.2.6	52/6	12	19/3
Tripletone Hi Fi Major, 10 watts 2 EL84 ...	£15.18.9	64/9	12	23/3
Leak TL12, 10 watt **Main Amplifier only** ...	£20.0.0	80/-	12	29/4
Leak Varislope Mono, Pre-amplifier	£15.15.0	63/-	12	23/1
Dulci DPA15, 15 watt with 2 valve pre-amplifier	£26.5.0	105/-	12	38/6

STEREO AMPLIFIERS

Leak Stereo 20, Pre-amplifier and Main amplifier complete	£55.9.0	229/-	12	80/8
Rogers Cadet Mk2 with Pre-amplifier 4 ECL86 valves	£26.15.0	107/-	12	39/2
Leak Transistor Stereo 30, Pre-amplifier and main amplifier	£49.10.0	198/-	12	72/7

F.M. TUNERS

Tripletone, F.M. Tuner Less power	£13.19.6	56/-	12	20/6
Tripletone, F.M. Tuner With power	£15.14.6	63/-	12	23/1
Jason JTV/2, F.M. and T.V. sound, Switched, self powered	£22.5.0	89/-	12	32/7

SURBITON PARK RADIO LTD.

48A SURBITON ROAD, KINGSTON-UPON-THAMES SURREY

Phone: KIN 5549

- ***ORDERS FOR CASH, C O D OR TERMS***
- ***HOURS 9 a.m. to 6 p.m. (1 p.m. Wednesday)***
- ***Easily reached by frequent trains Waterloo to Surbiton***

MARTIN AUDIOKITS

The new **Martin All Transistor Ten Watt Amplifier** kits represent excellent value for money. Each unit is complete, requiring only to be connected to the next. We show only the popular units here. Others available including stereo. The following would make up a **TRANSISTORISED AMPLIFIER 15 ohms MODEL**

		Dep.	&	Mthly. pmts. of
UNIT 1—FIVE INPUT SELECTOR. Size 3½ × 3in. Mag. PU, Crystal PU, Radio, Mic., Tape Head	£2.7.6	—	—	—
UNIT 4—PRE-AMPLIFIER AND CONTROL. Size 6½ × 2½in. Volume on/off, bass and treble control.	£3.2.6	—	—	—
UNIT 7—MAIN AMPLIFIER, 10 watts 6 transistor, transformerless Push Pull output. Mounted on heat sink. L.S. imp. 15 ohms	£6.12.6	—	—	—
UNIT 8—POWER SUPPLY. Gives 18 & 40 volts. Heavy duty transformer, rectifier and smoothing	£2.15.0	—	—	—
CONTROL PANEL for Units 1 and 4	10.6	—	—	—
ALL ABOVE FOUR UNITS WITH PANEL. 15 ohms	£15.8.0	62/-	12	22/6
TRANSISTORISED AMPLIFIER 3 ohms MODEL **UNIT 5 MAIN AMPLIFIER,** as Unit 7 but 3 ohms	£5.12.6	—	—	—
UNIT 6 POWER SUPPLY, as Unit 8 but 18–24 Volts	£2.12.6	—	—	—
ALL FOUR UNITS WITH PANEL 3 ohms	£14.5.0	57/-	12	20/10
SEND FOR LEAFLET OF COMPLETE RANGE				

Hi Fi LOUDSPEAKERS

W.B. HF812, 8in., 3.75, 7.5 and 15 ohms	£3.16.6	—	—	—
Goodmans Axiette, 8 in.	£5.5.7	—	—	—
Goodmans Axiom, 10 in.	£6.5.11	—	—	—
Goodmans 5K/20/XL, Tweeter and Crossover	£7.7.0	—	—	—
Goodmans 201, 12in. unit Full range 15 watt....	£10.17.6	43/6	8	24/3
W.B. HF1012, 12in., 3.75, 7.5 and 15 ohms...	£4.12.0	—	—	—
Goodmans X05000, £2.0.11. X0950	£5.10.11	—	—	—
Wharfedale Super 3, Tweeter	£5.16.8	—	—	—
Wharfedale Super 5, Tweeter	£5.19.7	—	—	—
Wharfedale Super 8 RS/DD, Full range unit...	£6.14.2	—	—	—
Wharfedale Super 10 RS/DD, Full range 10 unit	£10.18.0	44/-	8	24/3
Wharfedale Super 12 RS/DD	£17.10.0	70/-	12	25/8
Wharfedale RS/12/DD, 12in. unit Full range...	£11.10.0	46/-	8	25/6
Goodmans 301, 12in. unit Full range 20 watt...	£15.4.6	61/-	12	22/4
LEAFLETS AVAILABLE ON REQUEST				

GRAMOPHONE UNITS

B.S.R. UA25. Very latest model	£6.6.0	—	—	—
B.S.R. UA14 with TC8 Mono cartridge	£6.19.6	28/-	6	22/-
Garrard SRP10 Single player, Mono cartridge	£5.10.0	—	—	—
Garrard Autoslim, 4 Speed changer Mono ...	£7.17.0	33/-	6	24/-
Garrard AT/5/P Improved Autoslim, Stereo	£9.0.0	36/-	6	27/4
Garrard A.T.6 Autoslim de Luxe, mono ...	£11.9.0	47/-	8	25/3
Garrard AT/5/3000LM as **AT6,** but with slim arm, stereo	£11.12.0	46/6	8	25/9
Garrard 4H/F, Transcription unit Mono	£17.0.0	68/-	12	24/11
Garrard "Deccadek" Single Player with Decca "Deram" cartridge	£15.15.0	63/-	12	23/1
Garrard LAB. "A", Transcription changer Mono	£19.14.9	79/-	12	28/11
Garrard 301 Strobe, Transcription unit	£22.0.0	88/-	12	32/3
Philips AG1016, Stereo cartridge, will change 7in. records with adaptor 10/- extra	£12.12.0	50/6	12	18/6
Goldring GL58, with arm but less cartridge...	£17.1.0	69/-	12	24/11
Goldring GL70, with arm but less cartridge.....	£27.9.4	111/4	12	40/1
Goldring "88". Transcription less arm	£18.18.5	76/5	12	27/8
LEAFLETS ON REQUEST				

GUITAR SPEAKERS

Fane, 12in. Heavy duty unit 20 watt	£5.5.0	—	—	—
Goodmans Audiom 51, 12in. 15 watt Bass	£9.2.8	36/8	6	27/8
Goodmans Audiom 61, 12in. 20 watt Bass or Lead	£14.7.8	57/8	12	21/1
Goodmans Audiom 81, 15in.	£25.0.0	100/-	12	36/8
Goodmans Audiom 91, 18in. 50 watt Bass	£29.15.0	119/-	12	43/7
Wharfedale W 12/EG, 12in. 15 watt Lead ...	£10.10.0	42/-	8	23/6
Wharfedale W 15/EG, 15in. 15 watt Bass ...	£17.10.0	70/-	12	25/8
WRITE FOR GOODMANS LEAFLET				

GUITAR AMPLIFIERS

Linear Diatonic 12 watt 2 inputs	£13.2.6	52/6	12	19/3
Linear Conchord 30 watt 2 inputs with Cover	£19.4.6	77/-	12	28/2
Leak TL/25 25 watts amp and pre-amp	£42.5.0	169/-	12	61/11
Leak TL 50 50 watts amp and pre-amp	£51.5.0	205/-	12	75/2

MICROPHONES AND FLOOR STANDS

Reslo RBH/T, Ribbon High Impedance	£11.2.6	44/6	8	24/9
Reslo RBH/TS, Ribbon with on/off switch ...	£13.10.0	54/-	12	19/9
Reslo Heavy Duty Floor Stand	£7.0.0	—	—	—
Teisco DM304, Dual Impedance with switch...	£4.10.0	—	—	—
Piezo BM3, Crystal with switch, desk stand ...	£2.10.0	—	—	—
Jap, Floor Stand	£3.3.0	—	—	—

THE WORLD-FAMOUS KIT—SETS ANYONE CAN BUILD WITHOUT PREVIOUS EXPERIENCE

Heathkit DAYSTROM

THE PRACTICAL WAY to ENJOY ELECTRONICS

A WIDE RANGE OF WELL DESIGNED KIT-SETS TO CHOOSE FROM

YOU CAN SAVE £££s BY BUILDING ANY HEATHKIT MODEL



IO-12-U



S-3U

5 in. FLAT-FACE GENERAL PURPOSE OSCILLOSCOPE. Model IO-12U. An outstanding 'scope. "Y" sensitivity, 10 mV rms per cm at 1 kc/s; Bandwidth 3 c/s to 4.5 Mc/s. T/B 10 c/s to 500 kc/s in 5 steps. Kit **£32.12.6.** Assembled **£41.10.0.**

2½ SERVICE 'SCOPE, Model OS-1 Light (wt. 10½ lb.), compact, 5" × 8" × 14½". The ideal portable for servicemen. Kit **£22.18.0.** Assembled **£30.8.0.**

ELECTRONIC SWITCH, Model S-3U. Convert your 'scope to dual trace. Kit **£12.18.0.** Assembled **£18.10.0.**



IM-13U



HFW-1

6 in. DE LUXE VALVE VOLTMETER, Model IM-13U. Measures ac and dc volts 0-1.5 to 1,500V in 7 ranges. Res. to 1,000 MΩ in 7 ranges. Modern styling, with gimbal mount. Kit **£18.18.0.** Assembled **£26.18.0.**

VALVE VOLTMETER, Model V-7A. DC volts to 1,500, AC to 1,500 rms and 4,000 V pk. to pk. Res. 0.1-1,000 MΩ. Kit **£13.18.6.** Assembled **£19.18.6.** RF Probe 309-CU **£1.13.6** kit. HT Probe HV.336 **£2.19.6** kit. Will extend range of models V-7A or IM-13U.

TV ALIGNMENT GENERATOR, Model HFW-1. 3.6 to 220 Mc/s on fundamentals. Unique electronic sweep oscillator. Built-in fixed and variable marker generators (5 Mc/s crystal). Kit **£34.18.0.** Assembled **£44.10.0.**

"MALVERN" HI-FI EQUIPMENT CABINET. Will house all your Hi-fi equipment. Left "in the white." Size: 39⅛ × 32 × 21⅛ in. Kit **£18.1.0**

A wide range of other cabinets.

"COTSWOLD" HI-FI SPEAKER SYSTEMS. Acoustically designed enclosures, complete with 12 in. bass speaker, elliptical mid-range speaker, and tweeter to cover full frequency range of 30-20,000 c/s. Cross-over unit, level control, etc. Left "in the white." **Standard "Cotswold",** Size: 26 × 23 × 14 in. Kit **£23.4.0**

MFS "Cotswold" for the smaller room. Size: 36 × 16½ × 14 in. Kit **£23.4.0**

SSU-1 SPEAKER SYSTEM. A practical solution to the problem of a low-price speaker system. Two speakers. Without legs **£10.17.6** Kit With legs **£11.12.0** Kit

A wide range of speakers available. Send for details.



MALVERN

COTSWOLD

HI-FI FM TUNER. Range 88-108 Mc/s. Available in two units, sold separately. TUNER (FMT-4U) 10.7 Mc/s IF **£2.15.0** (inc. P.T.). IF AMPLIFIER (FMA-4U) power supply and valves **£13.3.0.** Total Kit **£15.18.0.**

9 + 9W HI-FI STEREO AMPLIFIER, Model S-99. Ganged controls. Stereo/Mono Gram., Radio, Tape inputs. P.C. board construction. Attractive presentation. Kit **£27.19.6.** Assembled **£37.19.6.**

"OXFORD" LUXURY TRANSISTOR PORTABLE, Model UXR-2. Beautiful solid leather case. Kit **£14.18.0**

GENERAL COVERAGE RECEIVER, Model RG-1. Freq. coverage 600 kc/s-1.5 Mc/s. 1.7-32 Mc/s in 6 switched bands. Many features incl. ¼ lattice crystal filter. Kit **£39.16.0** Assembled **£53.0.0.**



FM TUNER



S-99



UXR-2



RG-1

Send for FREE British Catalogue of Heathkit Range of Models

Deferred Terms over £10 in U.K.

Prices quoted include postage U.K.

AM/FM TUNER Covers FM 88-108 Mc/s, AM 16-50, 200-550, 900-2,000 M. Tuning heart (**£4.13.6** inc. PT) and IF Amp. Case. Total **£26.10.0** Kit

6W STEREO AMPLIFIER. Model S-33H. An inexpensive stereo/mono amplifier. Ideal for use with the Decca Deram lightweight pickup. Modern attractive styling. Kit **£15.17.6** Assembled **£21.7.6**

"GARRARD" AUTO RECORD PLAYER. Model AT.6. A four-speed stereo/mono unit with auto. record selection. Fitted with R.105 crystal pickup **£13.12.1.** With Decca Deram pickup **£14.6.1.**

5W MONO AMPLIFIER. Model MA-5. A general purpose amplifier based on model S-33. Separate bass and treble controls, gram and radio inputs. Printed circuit. Kit **£10.19.6.** Assembled **£15.10.0.**

JUNIOR ELECTRONIC WORKSHOP, Model EW-1. 20 exciting experiments can be made. Special solderless connections. Kit only **£7.13.6.**

MULTIMETER. Model MM-1U. Ranges 0-1.5v to 1,500v A.C. and D.C. 150 μA to 15A D.C.; 0.2 to 20 MΩ. 4½" 50 μA meter. Kit **£12.18.0.** Assembled **£18.11.6.**



PA-1



AT-6

R.F. SIGNAL GENERATOR, Model RF-1U. Freq. coverage from 100 kc/s-100 Mc/s or six bands, on fundamentals and up to 200 Mc/s on calibrated harmonics. Kit **£13.8.0.** Assembled **£19.18.0.**

DECADE RESISTANCE, Model DR-1U. Range 1-99,999Ω in 1Ω steps. Kit **£10.8.0.** Assembled **£14.8.0.**

DECADE CAPACITOR, Model DC-1U range. 100 μμF to 0.111 μF in 100 μμF steps. Kit **£7.5.0.** Assembled **£10.8.0.**

INTERNATIONAL MAIL ORDER SCHEME covering the American Heathkit range of 250 models. Illustrated American catalogue and full details can be obtained from us for 1/- post paid.

50W PUBLIC ADDRESS AMPLIFIER, Model PA-1. A multi-purpose unit, suitable for vocal and instrumental groups. 4 inputs for guitars, mics, etc. 2 heavy duty speakers, vol. indicator, variable tremolo, modern cabinet. Kit **£54.15.0.** Assembled **£74.0.0.**

50W POWER AMPLIFIER, Model MA-50. Ideal for sound reinforcing systems, etc. Kit **£19.18.0.** Assembled **£27.18.0.**

"MOHICAN" TRANSISTOR GENERAL COVERAGE RECEIVER, Model GC-1U. Freq. coverage 580 kc/s to 30 Mc/s in 5 bands. Electrical band spread on 5 additional bands covers "amateur" freq. from 80-10 M. B.F.O. Tuning and Zener diode. Send for details. Kit **£37.17.6.** Assembled **£45.17.6.**

80-10m AMATEUR TRANSMITTER, Model DX-40U. Crystal controlled. Power input 75w. c.w. 60w. peak controlled carrier phone. Output 40w. Kit **£33.19.0.** Assembled **£45.17.6.**

TRANSISTOR INTERCOM, Models XI-1U and XIR-1U. Ideal for home or business. Each master (XI-1U) will operate up to 5 remote stations. 9v. battery operation. XI-1U (Master) kit **£10.19.6.** Assembled **£16.19.6.** XIR-1U (Remote) kit **£4.7.6.** Assembled **£5.16.0.**

DAYSTROM LTD.

Dept. P.M. 12, GLOUCESTER, ENGLAND

WORLD'S LARGEST SELLING ELECTRONIC KITSETS

Please send me FREE BRITISH CATALOGUE (Yes/No)

Full details of model(s).....

.....

NAME .....

(BLOCK CAPITALS)

ADDRESS .....

PM-12

.....

FRANCIS
OF STREATHAM

include among their customers many who call personally from all over the country, because of the stocks and service in TAPE AND HI-FI EQUIPMENT to be found there. With so many shops to choose from, there must be excellent reasons why people prefer to buy from Francis. Perhaps you would care to find out by calling or writing to us about your requirements.

★ VERY LARGE STOCKS OF TAPE AND HI-FI EQUIPMENT
★ NO EXTRA FOR CREDIT UP TO 18 MONTHS
★ OWN SERVICE DEPARTMENT
★ FREE SERVICE DURING GUARANTEE PERIOD

FRANCIS OF STREATHAM
169-173 STREATHAM HIGH ROAD, LONDON, S.W.16

Between St. Leonards Church and Streatham Stn. • *Open all day Saturday* • *Phone STR 0192'0466*

ERSIN Multicore SOLDER

SAVBIT ALLOY
saves wear on soldering iron bits

The world-famous copper loaded alloy containing 5 cores of non-corrosive flux, that saves the soldering iron bit. Ersin Multicore Solder is also available in high tin quality alloys. 60/40 in 22 s.w.g. for printed circuits, transistors, etc.

SAVBIT SIZE 1 CARTON

Contains approximately 30 feet of 18 s.w.g. SAVBIT. It is also supplied in 14 s.w.g. and 16 s.w.g. Obtainable from radio and electrical stores.



5/- each

THE HANDY DISPENSER



Easy to find in the tool box—simple to use. Virtually a third hand for tricky soldering jobs. 12 feet 5 core 18 s.w.g. ERSIN MULTICORE SAVBIT alloy in a continuous coil used direct from free-standing dispenser.

2/6 each

BIB WIRE STRIPPER AND CUTTER

Strips insulation without nicking wire, cuts wire cleanly, adjustable to most thicknesses. Splits extruded plastic twin flex.




3/6 each

MULTICORE SOLDERS LTD.
MULTICORE WORKS · HEMEL HEMPSTEAD · HERTS. (BOXMOOR 3636)

CMMS 24

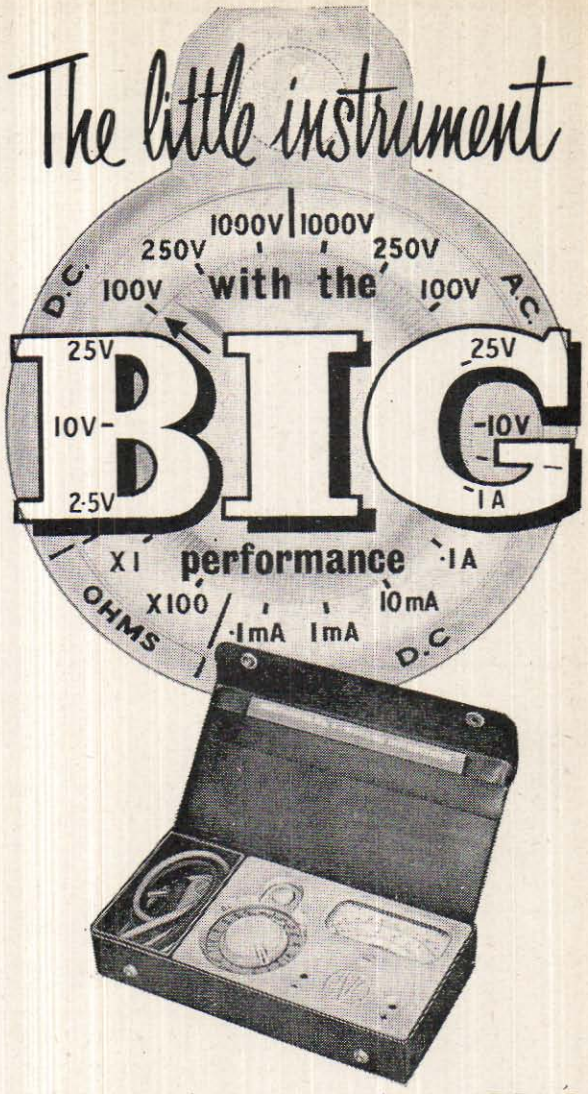The little instrument with the BIG performance



MULTIMINOR *Mk 4*

The newly improved model of this famous AVO pocket size multi-range instrument has been enthusiastically acclaimed in all parts of the world for its high standards of accuracy and dependability as well as for its modern styling, its highly efficient internal assemblies and its resistance to extremes of climatic conditions.


It is simple to use, one rotary switch for instant range selection, only one pair of sockets for all measurements, and a $2\frac{3}{4}$-inch clearly marked scale-plate. It is supplied in an attractive black carrying case complete with interchangeable test prods and clips, and a multi-lingual instruction booklet.

RESISTANCE: 0-2MΩ in 2 ranges, using 1.5V cell
SENSITIVITY: 10,000Ω/V on d.c. voltage ranges
1,000Ω/V on a.c. voltage ranges

Ask AVO to send you a full specification of this great little instrument. It measures only $7\frac{3}{4} \times 4 \times 1\frac{3}{8}$ ins. and weighs only 24 ozs.

AVO LTD
AVOCET HOUSE · 92-96 VAUXHALL BRIDGE ROAD · LONDON S.W.1
Telephone: VICtoria 3404 (12 lines)

MM19

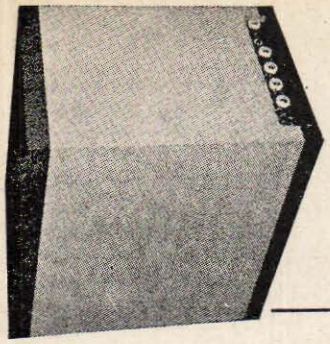

BASS-MAJOR 30 WATT GUITAR AMPLIFIER

A MULTI-PURPOSE HIGH FIDELITY, HIGH OUTPUT UNIT FOR VOCAL AND INSTRUMENTALIST GROUPS

Eminently suitable for bass, lead or rhythm guitar and all other musical instruments

- ★ Incorporating two 12in. heavy duty 25-watt high flux (17,000 lines) loudspeakers with 2in. diameter speech coils. Designed for efficiently handling full output of amplifier at frequencies down to 25 c.p.s.
- ★ Dual Cone in second speaker reproduces frequencies up to 17,000 c.p.s.
- ★ Heavily made cabinet of convenient size 24 × 21 × 14in. has an exceptionally attractive covering in two contrasting tones of Vynair.
- ★ For 200-250 v., 50 c.p.s., A.C. mains operation.
- ★ Four jack socket inputs and two independent volume controls for simultaneous connection of up to four instrument pick-ups or microphones.
- ★ Separate bass and treble controls providing more than adequate "Boost" or "Cut".
- ★ LEVEL frequency response throughout the audible range.
- ★ SUPERIOR TO UNITS AT TWICE THE COST.

39½ Gns.

Send S.A.E. for leaflet OR DEPOSIT of £4.3.0 and 12 monthly payments of £3.9.11. Carr. 17/6.

R.S.C. G5 GUITAR AMPLIFIER

5-watt high quality output. Incorporating high flux 12in. 10 watt 12,000 line loudspeaker. Sensitivity 50 m.v. High impedance jack input. Handsome strongly made cabinet (size 14 × 14 × 7in. approx.) finished in complementary shades of Rexine/Tygan. 200-250 A.C. mains.

£9.19.6 Or DEPOSIT 22/3 and 9 monthly payments of 22/3. Carr. 7/6.

LINEAR TREMOLO/PRE AMP. UNIT

Designed for introducing the Tremolo effect to any amplifier which is fitted with a reserve power supply point for smoothed H.T. and 6.3 v. A.C. L.T. This applies to practically all amplifiers of our manufacture, and to those of several other manufacturers. The unit plugs into power supply point and any input socket or amplifier. Controls are Speed (frequency of interruptions), Depth (for heavy or light effect), Volume and Switch. Three sockets are for two inputs and Foot Switch.

ONLY **4 Gns.**

R.S.C. 30-WATT ULTRA LINEAR

HIGH FIDELITY AMPLIFIER A10

A highly sensitive Push-Pull high output unit with self-contained Pre-amp. Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 dB down. Frequency response ±3 dB 30-20,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 807 output valves. All components are chosen for reliability. Six valves are used EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that **ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE.** The unit is designed for **CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUTDOOR FUNCTIONS,** etc. For use with Electronic **ORGAN, GUITAR, STRING BASS,** etc. For standard or long-playing records. **OUTPUT SOCKET PROVIDES** L.T. and H.T. for **RADIO FEEDER UNIT.** An extra input with associated vol. control is provided so that two separate inputs such as Gram and "Mike" can be mixed. Amplifier operates on 200-250 v. 50 c/s. A.C. mains and has output for 3 and 15 ohm speakers. Complete Kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. If required perforated cover with carrying handles can be supplied for 19/9. The amplifier can be supplied, factory built with EL34 output valves and 12 months' guarantee, for 14 gns. Send S.A.E. for leaflet.

11 Gns. Carr. 10/-

TERMS: DEPOSIT 33/9 and 9 monthly payments of 33/9. Suitable mikes & spkrs. available at competitive prices.

FANE HEAVY DUTY HI-FI SPEAKERS

12in. 15 ohms. Cast chassis. Exceptionally robust 2in. diam. Voice Coil Assemblies.

122/10 20 watt, 5 gns. 122/10A 20 watt, 6 gns.
122/12 20 watt, 7 gns. 122/12A 20 watt, 8 gns.
122/14 22 watt, 9 gns. 122/14A 22 watt, 10 gns.
122/17 25 watt, £11.17.6 122/17A 25 watt, £12.17.6

15in. 15 ohms. Cast chassis. Exceptionally robust 2in. diam. Voice Coil Assemblies.

152/12 20 watt, 12 gns. 152/12A 20 watt, 13 gns.
152/14 27 watt, 14 gns. 152/14A 27 watt, 15 gns.
152/17 35 watt, 16 gns. 152/17A 35 watt, 17 gns.

"A" indicates dual cone type. 30-17,000 c.p.s. Send S.A.E. for leaflets. Terms available.

FANE EXTRA HEAVY DUTY LOUDSPEAKER 15in. TYPE 153. 40 watts. Total flux 375,000 lines. Extremely high sensitivity. 15 ohm voice coil. Only 18 gns. or Deposit 37/6 and 12 monthly payments of 31/6.

R.S.C. SENIOR 15 WATT LEAD or RHYTHM GUITAR AMPLIFIER



High-fidelity push-pull output. Separate bass and treble "cut" and "boost" controls. Twin separately controlled inputs so that two instruments or "mike" and pick-ups can be used at the same time. Loudspeaker is a heavy duty high flux 12in. 20 watt model with cast chassis. Cabinet is well made and finished as Junior Model. Size approx. 18 × 18 × 8in.

Only **19 Gns.** Carr. 10/-

Send S.A.E. for leaflet. Or DEPOSIT 39/11 and twelve monthly payments of 33/4.

R.S.C. B20 BASS GUITAR AMPLIFIER


A highly efficient unit incorporating a massive 15in. high flux loudspeaker specially constructed to withstand heaviest load conditions. Rating 25 watts. Individual bass and treble controls give ample "boost" and "cut". Two high impedance jack socket inputs are separately controlled. All controls are conveniently positioned in a recess on top of the cabinet. Cabinet is of substantial construction and attractively finished in two contrasting tones of Rexine and Vynair. Size approx. 24 - 21 - 13in. Operation from 200-250 v. 50 c.p.s. A.C. mains.

Send S.A.E. for leaflet.

29½ Gns. Or Deposit £3.2.0 and 12 monthly payments of 51/8. Carr. 17/6.

HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11

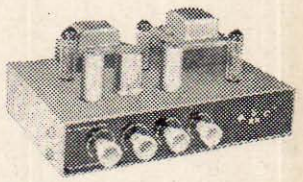PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP STAGES



Two input sockets with associated controls allow mixing of "mike" and gram., as in A10. High sensitivity. Includes 5 valves, ECC83, ECC83, EL84, EL84, EZ81. High Quality sectionally wound output transformer specially designed for Ultra Linear operation and reliable small condensers of current manufacture. INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut". Frequency response—3 dB 30-30,000 c/s. Six negative feedback loops. Hum level 60 dB down. ONLY 23 millivolts INPUT required for FULL OUTPUT. Suitable for use with all makes and types of pick-ups and microphones. Comparable with the very best designs for **STANDARD** or **LONG PLAYING RECORDS.** For **MUSICAL INSTRUMENTS** such as **STRING BASS, LEAD OR RHYTHM GUITARS,** etc.

OUTPUT SOCKET with plug provides 300 v. 30 mA, and 6.3 v. 1.5 a. for supply of a **RADIO FEEDER UNIT.** Size approx. 12 × 9 × 7in. For A.C. mains 200-250 v. 50 c.p.s. Output for 3 and 15 ohms speaker. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. Only **8 Gns.** Carr. (Or factory built 51/- extra.) 10/-.

If required louvred metal cover with 2 carrying handles can be supplied for 18/9. **TERMS ON ASSEMBLED UNITS: DEPOSIT** 24/9 and 9 monthly payments of 24/9. Send S.A.E. for illustrated leaflet detailing Cabinets, Speakers, Microphones, etc., with cash and credit terms.

R.S.C. CORNER CONSOLE CABINETS



Polished walnut veneer finish. Pleasing design.

JUNIOR MODEL. Size 20 × 11 × 8in. for 8 × 5in. or 10 × 6in. speakers, £2.9.9.


STANDARD MODEL. Size 27 × 18 × 12in. for 8 or 10in. speakers, £4.11.9.

SENIOR MODEL. Size 30 × 20 × 15in. for 12in. Speaker. Suitable Speaker systems below. Only 7 gns.

R.S.C. BASS REFLEX CABINETS, JUNIOR MODEL. Specially designed for W.B. HF1012 Speaker, but suitable for any good quality 10in. speaker. Acoustically lined and ported. Polished walnut veneer finish. Size 18 × 12 × 10in. Handsome appearance. Ensures superb reproduction for only £3.19.6.

STANDARD MODEL. As above but for 12in. speakers. Size 20 × 15 × 13in. For vertical or horizontal use. £5.19.6. Set of legs with brass ferrules, 19/6.

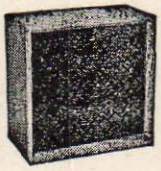12in. 10-WATT HIGH QUALITY LOUDSPEAKER. In walnut veneered cabinet. Gauss 12,000 lines. Speech coil 3 ohms or 15 ohms. Only £4.19.6. Carr. 5/-. Terms: Deposit 11/3 and 9 monthly payments of 11/3. **12in. 20 WATT HI-FI LOUDSPEAKERS IN CABINETS.** Size 18 × 13½ × 10in. Finish as above. Terms: Deposit 17/9 and 9 monthly payments of 17/9. Only £7.19.6. Carr. 8/6.



AUDIOTRINE HI-FI SPEAKER SYSTEMS. Consisting of matched 12in. 12,000 line, 15 ohm high quality speaker, crossover unit (consisting of choke, condenser, etc.) and Tweeter. The smooth response and extended frequency range ensure surprisingly realistic reproduction. Standard 10 watt rating £4.19.9. Carr. 5/-. Or Senior 15 watt, £6.19.9. Carr. 7/6.

HEAVY DUTY LOUDSPEAKERS IN SUBSTANTIAL REXINE COVERED CABINETS. Type BG1. Suitable for Bass Guitar. Speaker Unit 15in., High Flux, 15 ohms, 30 watts. Cabinet size approx. 24 × 21 × 13in. Only 19½ gns. Or Deposit 43/- and 12 monthly payments of 34/-.

R.S.C. (MANCHESTER) LTD.

MAIL ORDERS TO: ROOM 5, 54 WELLINGTON STREET, LEEDS 1.

Terms: C.W.O. or C.O.D. No C.O.D. under £1. Postage 2/9 extra under £2. 4/6 extra under £5. Trade Supplied. S.A.E. with all enquiries, please. Personal shoppers welcomed at any of the branches below. Open all day Saturday. **BRADFORD,** 54 Morley Street. Nr. Alhambra Theatre (Half-day Wednesday). **BRISTOL,** 14 Lower Castle Street (Half-day Wednesday). **BIRMINGHAM,** 6 Gt. Western Arcade, opp. Snow Hill Station (No half-day). **DERBY,** 26 Osmaston Rd., The Spot (Half-day Wednesday). **DARLINGTON,** 13 Post House Wynd (Half-day Wednesday). **EDINBURGH,** 133 Leith Street (Half-day Wed.). **GLASGOW,** 326 Argyle Street (Half-day Tuesday). **HULL,** 51 Savile Street (Half-day Thursday). **LEICESTER,** 32 High Street (Half-day Thursday). **LEEDS,** 5-7 County (Mecca) Arcade (No half-day closing). **LIVERPOOL,** 73 Dale Street (No half-day closing). **LONDON,** 238 Edgware Road (Half-day Thursday). **MANCHESTER** 8-10 Brown St. (Market St.) and extensive new premises at 60A and 60B Oldham St. (No half-day). **MIDDLESBROUGH,** 106 Newport Rd. (Half-day Wednesday). **SHEFFIELD,** 13 Exchange Street, Castle Market Bldgs. (Half-day Thursday).

The NEW Stern-Clyne ELECTRONIC CONCERT ORGAN

TO BUILD YOURSELF

DESIGNED —

— For the Electronic amateur seeking the most fascinating project.
— For the discriminating organist seeking an instrument which DOES sound like a pipe organ.


NEW —

— Constructional methods introducing "sectional complete instrument" building.
— Extended range of tone colours. Without unrealistic "Gimmick" effects.

THE MOST COMPREHENSIVE KIT OF PARTS AVAILABLE IN THIS COUNTRY

START BUILDING FOR AS LITTLE AS £68.10.0 approx. (H.P. Terms Available)

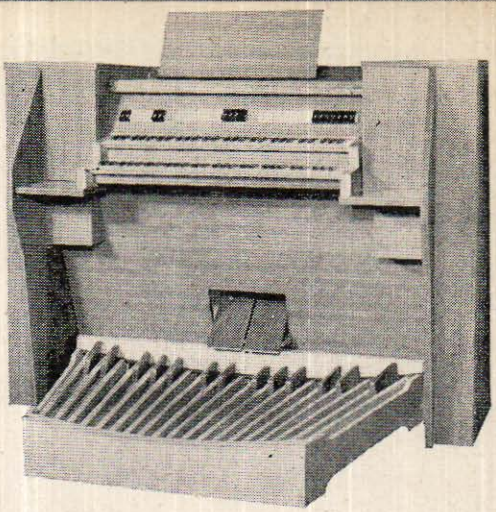Write today for brochure (enclosing 6d. stamp) to: **Electronic Organ Dept., 18 TOTTENHAM COURT ROAD, LONDON, W.C.1,** or call at your nearest branch.



VISIT OUR SHOWROOM AT 18 TOTTENHAM COURT RD., LONDON, W.1 and hear this fabulous new Electronic Concert Organ demonstrated.

STERN-CLYNE

GREAT BRITAIN'S GREATEST ELECTRONIC HOBBIES ORGANISATION

HERE'S WHY THOUSANDS OF ELECTRONICS ENTHUSIASTS BUY WITH CONFIDENCE FROM STERN-CLYNE —

- A wide range of exclusive equipment available including our own speciality — MULLARD DESIGNS — for the home constructor or ready assembled.
- The finest selection of Hi-Fi and Audio equipment by all leading manufacturers.
- A comprehensive range of electronic components for the build it yourself enthusiast available at all branches.
- Retail shops, showrooms and demonstration rooms throughout London and the provinces all carry extensive stocks.
- Finest Mail Order Service-geared to give prompt and efficient attention.
- Hire Purchase facilities available on orders of £11 10. 0 and over.
- Hi-Fi advisory service to help you in choosing the right equipment.
- After sales service — complete satisfaction guaranteed.

VISIT YOUR NEAREST STERN-CLYNE ELECTRONICS CENTRE

LONDON
18 Tottenham Court Rd., W.1. MUSeum 5929-0095. *Half Day Sat.*
23 Tottenham Court Rd., W.1. MUSeum 3451-2. *Half Day Thurs.*
309 Edgware Rd., W.2. PADdington 6963. *Half Day Thurs.*
109 Fleet St., E.C.4. FLEet St. 5812-3. *Half Day Sat.*
162 Holloway Road, N.7. NORth 7941. *Half Day Thurs.*
9 Camberwell Church St., S.E.5. RODney 2875. *Half Day Thurs.*

CROYDON
12 Suffolk House, George St. MUNicipal 3250. *Half Day Wed.*

BRISTOL
26 Merchant Street, Bristol 1. Bristol 20261.
Now open 6 days a week.

LIVERPOOL
52 Lord Street, Liverpool. Royal 7450.

MANCHESTER
20-22 Withy Grove, Manchester 4. BLAckfriars 5379.
Open 6 days a week.

SHEFFIELD
125 The Moor, Sheffield. Sheffield 29993.

MAIL ORDERS AND ENQUIRIES TO:
Dept. P.E., 3-5 Eden Grove, Holloway, London, N.7. NORth 8161-5.

HOME RADIO Ltd.

187 LONDON ROAD, MITCHAM, SURREY (MIT. 3282)

Shop hours:
9–5.30; Including Sat.
Fri. 9–6.30.
Closed all Wed.



SPECIAL OFFER TO READERS OF PRACTICAL ELECTRONICS!

FREE to every purchaser of our fabulous Resistor Pack—one Home Radio Colour Code Calculator. Our Resistor Pack contains 60 brand new ERIE TYPE resistors ½ and 1 watt, all preferred values between 33 ohms and 1 megohm. (Not more than 2 of any one value in each pack.)

60 Resistors, approximate value.....20/-
1 Colour Code Calculator 1/6
21/6

All this for 7/6, including postage and packing!

Don't delay, stocks are not unlimited!!



When you have read this copy of Practical Electronics we feel sure you will be itching to seize your soldering iron and start constructing. Then arises the problem—where to obtain all the parts? *The Home Radio Catalogue provides the answer!* It contains over 5,000 items, 800 of them illustrated, carefully indexed with extensive cross references, which make it particularly easy to use. Order forms are enclosed, and this is backed by the fastest Mail Order Service.

The catalogue costs 5/- plus 1/- postage, but five 1/- coupons are given with each catalogue, and each time you send an order valued £1 or over you enclose a coupon and deduct 1/- from the money you send. There is no time limit so if you purchase £5 worth of components from us—*even though spread over several years*—your catalogue will have cost you nothing!

AVOID DELAY– *fill in the Coupon and send for your Catalogue* **TODAY**

BLOCK CAPITALS please *Enclose P.O. for 6/-*

NAME .....

ADDRESS .....

.....

.....

HOME RADIO LTD., Dept. PE, 187 London Rd., Mitcham, Surrey

VOL. 1 No. 2
DECEMBER 1964

Practical Electronics

Opportunities Abound

We are all, nowadays, electronics conscious. Yes, even the layman, while not conversant with the technicalities involved, has a general appreciation of the vital part played by this young but exuberant branch of electrical engineering in the complex world of today . . . and this is but the beginning.

★ ★ ★

As we step over the threshold into a new exciting technological age, our dependence upon electronics is all too apparent: terrestrial developments centre around automation, with electronics providing the brain and guiding hand for power-operated machinery; extraterrestrial exploration relies utterly upon electronics for remote control, communications and telemetering services.

These grand scale developments have an impact on the entire field of electronics, for in their wake come new components, new circuits, new methods and, of course, new applications.

★ ★ ★

Without a doubt the amateur enthusiast will be eager to reap his share of these benefits of technological progress, as he has been indeed in the past. For it is true that amateurs have been conducting experiments and building electronic equipment since the earliest days of radio communication; even before the thermionic valve drove the crystal diode into (temporary) oblivion, and long before the very term "electronics" entered into general use.

But, in more recent times, the technical revolution triggered off by the invention of the crystal triode or transistor some 16 years ago has quite dramatically transformed the situation to the advantage of the home constructor.

★ ★ ★

Thanks to the transistor, gone largely is the need for a metal chassis and the tedious metal work this often entailed. Much transistorised equipment can be assembled satisfactorily on a piece of plastics board or even on an offcut of hardboard. A small battery replaces a bulky and heavy power pack and so demolishes what was undoubtedly a psychological barrier for some would-be constructors and experimenters—apprehension of high voltage supplies. With miniature components and simplified assembly methods, construction can indeed be a kitchen table operation nowadays.

Yes, truly can we say that in the realm of electronics a new emphasis has been given to the word *practical*.

THIS MONTH

CONSTRUCTIONAL PROJECTS

VARIABLE LOW VOLTAGE D.C. SUPPLY UNIT 99
TWO-WAY INTERCOM UNIT 100
PRECISION DECIMAL STEP PRE-AMPLIFIER 107
ULTRASONIC REMOTE CONTROL 116
5 WATT INTEGRATED AMPLIFIER 119
V.H.F. BROADCAST RECEIVER 124

SPECIAL SERIES

SOUND ON TAPE—2 103
BEGINNERS START HERE—2 143

GENERAL FEATURES

INTRODUCING ULTRASONICS 96
THE 73 PAGE 102
ELECTRONICS OF LIGHT OPERATED SWITCHES 110
RADIOACTIVITY EXPERIMENTS 129

NEWS AND COMMENT

EDITORIAL 95
ELECTRONORAMA 122
OFFICE WORK MADE EASY 128
DETACHED PARTICLES 136
NEW PRODUCTS 140

Our January issue will be published on Thursday, December 17

All correspondence intended for the Editor should be addressed to: The Editor, PRACTICAL ELECTRONICS, George Newnes Ltd., Tower House, Southampton Street, London, W.C.2. Editorial and Advertisement Offices: PRACTICAL ELECTRONICS, George Newnes Ltd., Tower House, Southampton Street, London, W.C.2 Phone: Temple Bar 4363. Telegrams: Newnes Rand London. Subscription Rates including postage for one year, to any part of the world, 35s. **© George Newnes Ltd., 1964. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is specially reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.**



introducing... ultrasonics....

The Ultrasonoscope transistorised flaw detector being used for checking structural parts of an aircraft

nature of ultrasonic waves ★ methods of producing and detecting ★ commercial applications ★ scope for amateurs

ULTRASONICS IN NATURE

In the year 1793 Lazzaro Spallanzani established after a long series of experiments that the common bat could navigate and detect its prey without being able to see. After establishing that any loss of acuteness in the bat's hearing resulted in a loss of ability to navigate, he put forward the hypothesis that they were able to navigate and detect their prey by emitting and receiving a vibration of the same nature as that of sound but with such high frequency that it was inaudible to the human ear.

The scientific minds of the day rejected this suggestion, and Spallanzani joined the ranks of those scientists whose reward for systematic investigation and logical thought was ridiculed.

It is now quite firmly established that these ideas were correct and that other creatures, including the porpoise are able to use ultrasonic emission and reception for various means.

The definition of an ultrasonic wave is very simple, being a pressure wave whose frequency is higher than that to which the human ear will respond. It is generally accepted that 20kc/s is the lowest usable ultrasonic frequency, although in fact human audibility does not reach this high level.

The properties of an ultrasonic vibration are, since they are fundamentally the same as sound vibrations, identical with the properties of sound. They may be propagated in gas, fluid or solid, may be absorbed by soft surfaces, reflected by hard surfaces and refracted by changes in temperature and pressure of the medium in which they are propagated.

PRODUCTION AND DETECTION OF ULTRASONIC VIBRATIONS

There are three main techniques by which ultrasonic vibrations may be produced.

1. Magnetostrictive methods.
2. Piezo-electric methods.
3. Oscillation of air or fluid jets.

The first of these methods uses the fact that certain materials when subjected to a varying magnetic field undergo very slight changes in dimensions. A nickel rod is usually used as the core of a coil through which a high frequency current is flowing. The result of this is that the nickel rod is subject to a slight length change with the same frequency as the current through the coil.

The second method relies on the fact that certain naturally occuring materials such as Rochelle Salt or Quartz and certain man-made materials such as ceramics, including Barium Titanate and Lead Zirconate Titanate, are subject to a change in dimensions with a directly applied voltage.

If an oscillatory voltage is applied to the opposite faces of such a slab of material the material will execute vibrations at twice the frequency of the applied voltage.

The reason for the frequency doubling effect is that the domains, i.e. groups of molecules, which are normally random in their orientation change direction according to the polarity of the applied electric field. Hence both the positive and negative peaks of the applied voltage will cause the corresponding expansion or contraction which results in the frequency doubling effects.

If the material is originally polarised, i.e. all the domains are arranged to lie in approximately one direction by means of application of a large electric field in the early stages of manufacture, then the fact

that these domains are not completely free results in the piezo-electric vibration being of the same frequency as the applied oscillatory voltage.

The third method of production is only of interest where very high power is required, usually for emulsification of suspensions, and relies on the principle of a high powered jet of gas or fluid impinging on a blade. Under these conditions the blade will execute ultrasonic vibrations, assuming due care has been given to the dimensions of the blade, which will be transmitted through the gas or fluid.

APPLICATIONS OF ULTRASONIC VIBRATIONS

Among the first fully developed applications of ultrasonics were the fields of cleaning, drilling, welding and soldering. In each of these cases the ultrasonic techniques have certain advantages over conventional techniques.

The advantage of cleaning, by immersing the object concerned into a tank of fluid in which ultrasonic vibrations are produced, is twofold: firstly, the tremendous reduction in time when compared with manual cleaning; secondly, the advantage that very delicate and complex assemblies, such as internal parts for valves or components, may be cleaned without the risk of physical damage which is present when using conventional cleaning methods.

By using an ultrasonic vibration in a solid rod one can drill through materials for which standard drilling methods are not very satisfactory, examples being crystals or glass, or other such brittle material. A second advantage when using this method for drilling is that one has dispensed with the necessity for a rotating bit, hence one can drill holes of any desired shape.

In the case of welding and soldering, the obvious advantage is that the tremendous production of heat which can destroy or impair the efficiency of delicate assemblies is avoided, and in the case of soldering the use of any form of flux becomes unnecessary. A further advantage to the soldering technique is that it can be used to solder materials not solderable by previous methods, for instance aluminium.

The third method of producing ultrasonic energy, the jet method, is used in the textile and food industries among others; a characteristic example of products which require a process of emulsification being peanut butter.

MEASUREMENT BY ULTRASONICS

Apart from applications involved in the field of production or manufacturing, such as those previously described, ultrasonic vibrations may be used for performing scientific measurements.

Examples of these are ultrasonic thickness gauges and flow meters.

If an ultrasonic vibration is propagated through a solid material, any change in the nature of the material will result in some reflection. By measuring the attenuation or the time taken for an ultrasonic wave to cover the total journey it is possible to estimate very accurately the thickness of the material. One example of the use of ultrasonics in this respect is the measurement of the thickness of fat on certain animals, such as pigs, and in this context has an obvious superiority over any other methods which might be devised.

By launching an ultrasonic vibration into a moving fluid and using the Doppler effect, i.e. apparent change in frequency with velocity, it is possible to measure the flow rate of the fluid concerned. Although there are simpler methods for flow rate measurement, this technique has the advantage that it may be used with either corrosive or very dangerous fluids. An example of the use of this technique lies in the measurement of the flow rate of molten sodium which is used for heat transfer in certain atomic reactors.

Although it is not a scientific measurement, the similar technique to that for thickness may be used to detect flaws in factory-made products without the necessity of destroying the product in the process of inspection. An ultrasonic vibration introduced at one face of perhaps a complicated plastics moulding will be reflected by any small voids or cracks in the material. These reflections may be compared with the pattern which is the result of a flawless product, hence inspection may be carried out very rapidly and without any destruction of the items concerned.


Probably the most dramatic use of ultrasonic energy is in the field of echo sounding. This is an extension of the thickness measurement technique by which a ship may launch an ultrasonic wave and establish the time taken for reflection from the ocean bed. This is a direct and continuous indication of depth.

Apart from indicating depth this technique may, of course, also be used to detect the presence and position of either ships or shoals of fish.

ULTRASONICS IN AIR

There are a number of ways in which the properties of an ultrasonic wave in air may be used to perform useful tasks. Probably the four main applications are in object detection, distance measurement, remote control and communications.

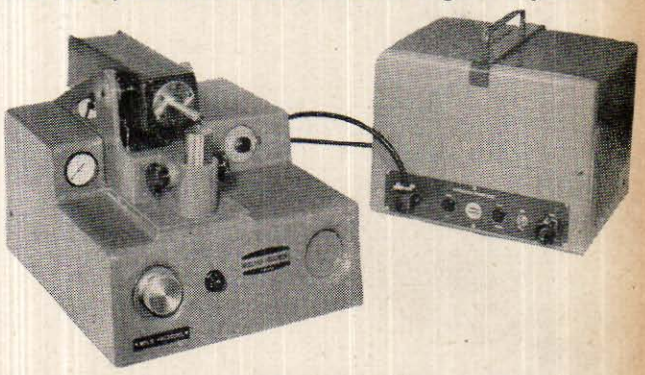The property of reflection may be used in air, as it is in water, to measure the distance to a given object.




An ultrasonic spot welder for welding thin ductile materials such as aluminium and copper

This is exploited in devices which are available for the measurement of height of such things as hovercraft, helicopters and possibly light aircraft when flying at very low levels.

When used for detecting objects the largest application is that of the burglar alarm. If a transmitter and receiver are set up some distance apart, and the incoming wave of ultrasonics to the receiver used via an amplifier to hold over a relay, anybody interrupting the beam will cut off the input to the amplifier, hence cause the relay to change position. This is used directly to indicate presence of intruders in factories, warehouses, etc.



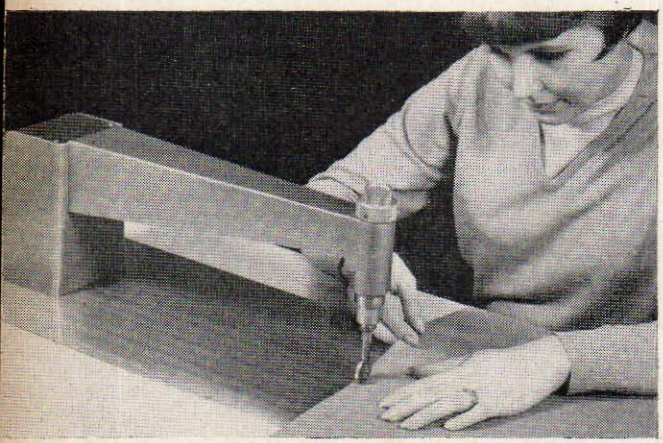This ultrasonic thickness meter incorporates a moving coil meter which indicates directly the thickness of metals being examined. It is fully transistorised and operates from dry cells



The Omega threadless stitcher. This uses a novel spot welding technique and is used in garment production with man-made fabrics

A similar system may be used for remote control or communication, but in this case the ultrasonic wave is directly controlled at the transmitter.

Since a pressure wave of this sort may be modulated in much the same way as a radio wave, with sufficiently sophisticated electronic equipment the transmitted ultrasonic wave may be either amplitude modulated, frequency modulated or pulse code modulated in order to transmit information or instructions over short distances.

Concerning the remote control of model boats, it must however be noted that control may be effected over much longer distances if the wave is transmitted through the water, since the attenuation of ultrasonic waves is considerably less in a liquid medium than in air.

The transmission of ultrasonic waves in air is a field which is very suitable for the experimenter as suitable transducers for transmitting and receiving are available commercially at comparatively low prices. Although the range of control is a little limited, something of the order of 100 to 300ft being the maximum practical at the moment, an ultrasonic system for remote control has certain advantages over radio control. The most obvious of these being the fact that the ancillary amplifiers are usually cheaper to make and considerably more simple. There is, of course, the added advantage that a transmitting licence is not required, as in the case of radio wave propagation.

ULTRASONIC TRANSDUCERS

When transmitting ultrasonic energy through air the direct use of a vibrating crystal is not the most satisfactory method since, although great power is available from such a crystal, the dimensions of the change in size are so small that the range would be very limited.

In order to improve this range a technique is used whereby the movement of the crystal is mechanically amplified to get a greater degree of movement from the transmitting element.

Fig. 1 shows the technique which is used to achieve this mechanical amplification. A thin crystal is cemented to a small thin round plate mounted on a central stem. As the crystal is energised it attempts to change its dimensions in the plane of its two parallel faces. Since it is securely cemented to the metal plate the latter is forced to bend with the movement of the crystal, and this results in an oscillatory bending movement of the metal plate at the frequency of the applied voltage—hence the transmission of a pressure wave into the air.

Correspondingly, a pressure wave impinging on the plate will cause very small movement of the plate which is sufficient to generate across the crystal a signal corresponding to the frequency of the incoming pressure wave.

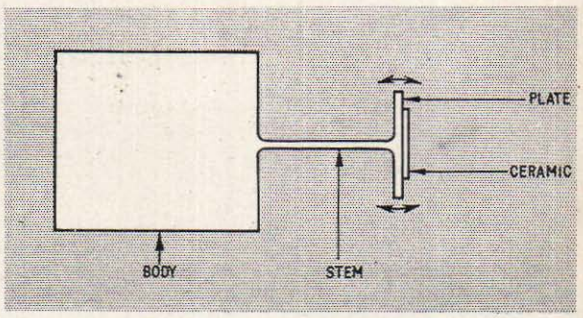


Fig. 1. Mechanical amplification of the transducer crystal is achieved by use of a small metal plate

THE EXPERIMENTAL APPLICATIONS OF ULTRASONIC ENERGY

Most amateurs, or indeed small industrial users, are limited to the application of ultrasonics directly in air, as this is the only application for which the general purpose transducers are available on the market.


There are a number of aspects of ultrasonics which are certain to capture the imagination of the enthusiastic amateur, especially in the field of remote control and voice communication.

The fact that in this medium the experimenter is free from the necessity to acquire transmitting licences is a major attraction of these techniques.

In the case of amateurs or small industrial users who feel sufficiently confident to manufacture their own transducers from fundamental ceramic materials which are freely obtainable, the field of underwater transmission could be particularly exciting. This has the previously mentioned advantage of considerably greater range and would offer at least one immediate application, this being the facility of direct voice communication between aqualung divers.

VARIABLE LOW VOLTAGE D.C. SUPPLY UNIT

PE BLUEPRINT

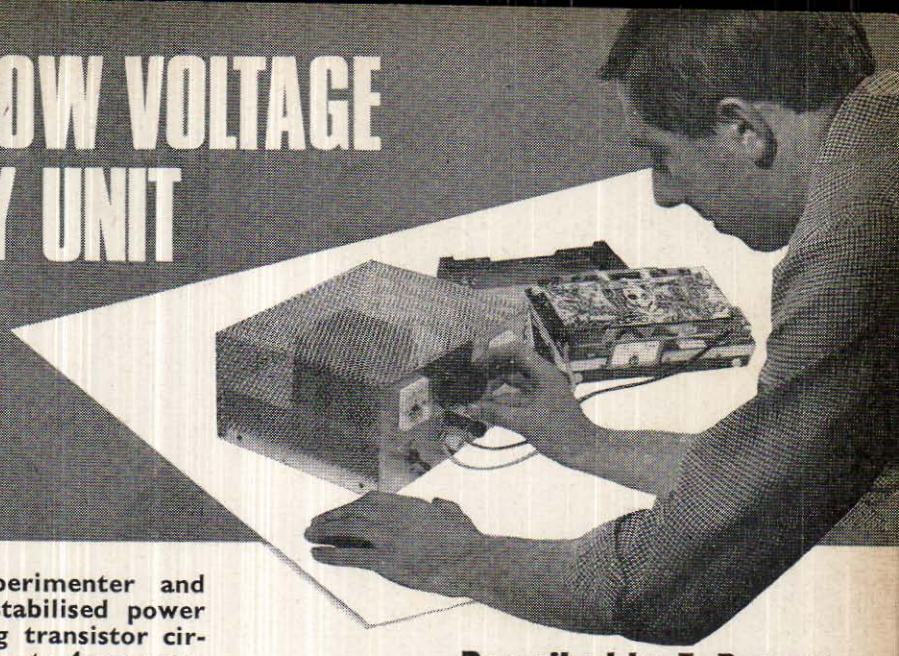

Designed to suit the experimenter and amateur constructor, this stabilised power supply is ideal for supplying transistor circuits with 0—14 volts d.c. at up to 4 amperes. It eliminates the need for expensive battery replacements when working on the test bench.

Described by E. Barnett

THE CIRCUIT (see Fig. 1 on blueprint) consists of a step down battery charger transformer T1 feeding into a bridge rectifier consisting of D1—D4, the output of which is smoothed by the 2,500μF capacitor C1 at about 22 volts off load.

The two Zener diodes D5 and D6 in series stabilise the base of TR1 to about 14 volts, thus maintaining the voltage at the top end of VR1 in the emitter circuit of TR1 at the same—since the gain of a grounded collector (or emitter follower) transistor is virtually unity.

Variation of the output voltage is carried out by "potting down" the variable resistance VR1, the slider of which feeds into the base of another grounded collector transistor TR2.

The output from across the TR2 emitter load is then fed into the bases of TR3 and TR4 connected in parallel, again in grounded collector configuration, the emitter load for these two transistors being the device to be supplied with power.


SEMICONDUCTOR DETAILS

When constructing the power supply, various precautions should be taken. Before mounting the transistors TR1–TR4 and bridge rectifier diodes D1–D4 ensure there are no burrs around the drilled holes in the chassis otherwise the insulating washers will be punctured and expensive smoke could be generated!


Also, prevent damage occurring to the face of the chassis where the transistors, diodes and heatsinks are to be mounted, since good thermal conductivity is essential for the long life of the semiconductors.

A smear of silicon grease on the chassis and semiconductor mating faces will assist heat conduction and maintain the insulation.

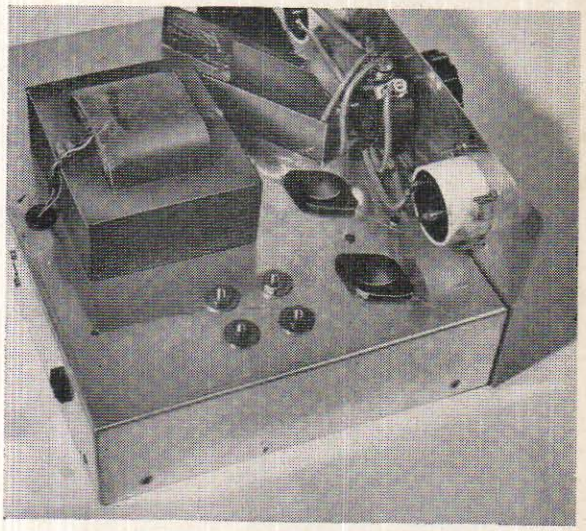The insulating sleeves for diodes D1–D4 inclusive were cut from the outer casing of some old television coaxial cable; however, any form of insulating sleeving will do provided it functions properly.



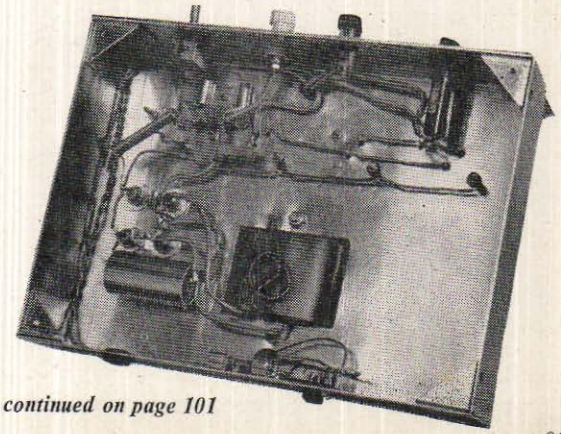Above is a top view showing heat sinks and transistors painted matt black for heat dissipation. An under chassis view is shown below




continued on page 101


TWO WAY intercom UNIT

PE BLUEPRINT

By K. Berry

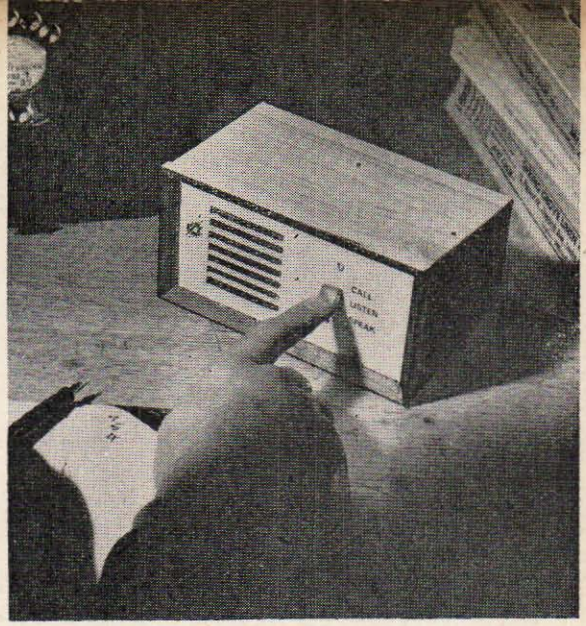

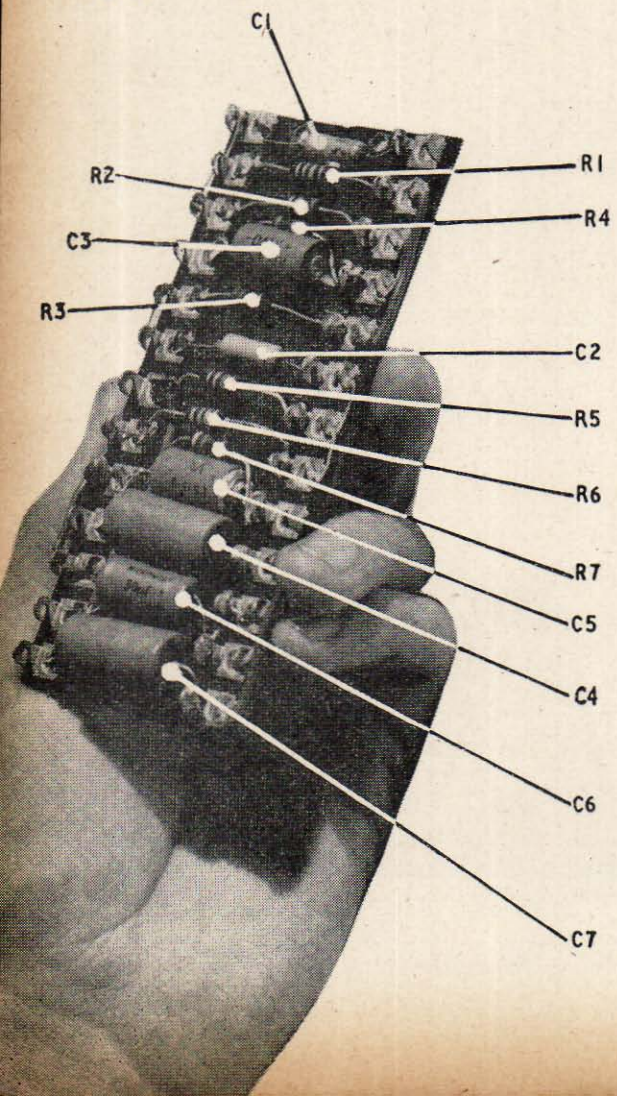Construction of the intercom unit is simple • its finished appearance will enhance any desk or table in home and office • installation is easy, requiring only a two-cored cable between a pair of units




THE CIRCUIT of the amplifier which is the heart of the equipment is shown in Fig. 1 of the blueprint. It is a simple two-stage common-emitter transistor amplifier using germanium alloy junction transistors. It will be seen that there is no d.c. path shown for the collector current of the output transistor. This is because the collector current of this transistor goes down one of the line conductors to the loudspeaker in the other unit returning via the other conductor. The 0·1μF capacitor C4 which is connected from the collector to the negative supply reduces the impedance of the collector load at the higher audio frequencies thus lowering the effective gain of this stage at these frequencies. This overcomes a tendency to high frequency oscillation. The 32μF capacitor C6 connected across the supply lines was found to be necessary to prevent low frequency oscillation ("motor-boating") occurring when the battery runs down.

In Fig. 2 is shown the circuit of the rest of the unit. A four-pole three-position switch S1 selects the various functions. This switch is biased to its centre position ("LISTEN") and in this position only the loudspeaker/microphone is connected to line. When the switch is thrown to the "SPEAK" position, the loudspeaker/microphone is connected to the input of the amplifier and the line to the output (as described above). The other switch position is "CALL", and when the switch is held in this position the line is connected to the output of the amplifier and a 0·1μF capacitor C7 is connected from the output of the amplifier to its input terminal. This causes the amplifier to oscillate violently at about 500c/s and results in a loud tone being emitted by the loudspeaker in the other unit.

CONSTRUCTION AND COMPONENTS

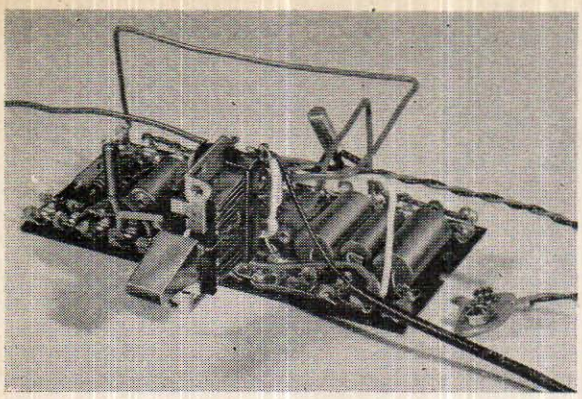An attractive cabinet constructed of wood with an aluminium facia panel is shown in detail in Fig. 4.



The photograph above shows the electronic assembly ready for inserting into the cabinet prior to connecting to the microphone/loudspeaker and battery

The transducer used as the loudspeaker/microphone is a Government surplus balanced-armature earpiece marked "I.T.B.A. No. 5", obtained from a pair of headphones. It might be possible to use a small high impedance moving coil loudspeaker (say 35 ohms) instead, *but this has not been verified.* In any case, the surplus headphones should be cheaper. *Note:* A suitable pair of headphones (type DLR5) from which two balanced-armature inserts may be removed is available from Z & I Aero Services, 44A Westbourne Grove, London, W.2.

The exact type of switch to be used will depend on what is available. Those used by the author were miniature key switches. The old Post Office key switch would serve the purpose well, but is rather large. Note that the switches used must be of the "break-before-make" variety.

TRANSISTOR VOLTAGES

Transistor	Collector	Base	Emitter
TR1	5·1	1·8	1·7
TR2	8·2	1·0	0·85

Total current consumption: 21mA "CALL"
16·5mA "SPEAK"
Above measurements made with AVO Model 8
Battery voltage 9V. Switch set to "SPEAK"

INSTALLATION AND OPERATION

Having made and tested the units on the bench, it only remains to install them. They should be connected by a two-core cable of sufficiently low resistance. The author has about 30 yards of 14/·0076 flat twin wire connecting his intercom units. Tests made on this installation show that a line "loop resistance" in excess of 220 ohms is acceptable. Using 14/·0076 wire this means a separation of up to 3,000 yards is possible, which should be quite enough for most purposes.

When connecting up it is desirable to connect the units so that the negative poles of the batteries in each unit are both connected to the same line.

To call the remote station, set the switch to the "CALL" position for about two seconds then release the switch and wait for the remote station to answer. When the remote station has answered, set the switch to the "SPEAK" position and pass your message. As soon as you have finished speaking, release the key so that you can hear the remote station. ★

VARIABLE LOW VOLTAGE D.C. SUPPLY UNIT

continued from page 99

The faces of heatsinks for TR3 and TR4 can be painted with a black paint which has a matt finish and must be heat resistant capable of withstanding temperatures of at least 100°C. The heatsinks (and transistors) should be painted *after* assembly since the mating faces must be clear of paint for good heat conduction.

The usual precautions of using heat shunts such as pliers and not applying heat for longer than is necessary should be taken when soldering.

CHASSIS DETAILS

The blueprint shows the chassis construction full size and from these drawings any dimensions can be taken off.

The chassis itself is a proprietry item that can be purchased from any dealer, and the cover was made from expanded metal and is fixed to the main chassis with self-tapping screws and washers.

When fixing the fuse holder for FS1 an insulating sheet is required between the chassis and holder otherwise a short circuit will occur.

Before fixing transformer T1 the fixing brackets were removed to facilitate "drop through" mounting to the chassis.

TESTING

Check for continuity and correctness of wiring and ensure polarity of connection of C1 is correct.

Check insulation of diodes D1–D4 and transistors TR1–TR4 between cases and chassis. Don't use a high voltage megohmmeter, the ohms×100 range is sufficient on an AVO model 8.

Once satisfied with the wiring, rotate potentiometer VR1 knob fully anticlockwise, connect the mains power to the unit and switch on.

When VR1 is rotated clockwise the indication on M1 should rise from zero to 14V d.c. in the fully clockwise position. Should the response be different to above switch off immediately and ascertain fault. Next connect a 4 to 5 ohm resistor of at least 20 watts rating to the output terminals and adjust VR1 until 14 volts is reached on M1.

The ammeter M2 reading should remain steady at about 3 to 4 amperes depending on the value of load.

Transistors TR3 and TR4 will get very hot and TR1 and TR2 quite warm. This is normal.

OPERATION

The fuse rating in FS2 position will depend upon the application. For example, an average transistor radio may take up to 100mA and a medium power inverter may take up to the maximum rating of 4A.

Currents of 5 amperes and more can be handled *intermittently* but for good transistor life 4 amperes should not be exceeded.

Ambient conditions are important, too. Allow plenty of air-space around the unit and avoid operating it in places or near to objects of relatively high temperatures.

Regulation is very good, the change in voltage from no load to 4 amperes at 6 volts is less than 0·25 volt and at 12 volts less than 0·5 volt. ★

SINCLAIR X-10 AMPLIFIER

With reference to our New Products feature last month, it has been brought to our notice that Technical Suppliers Ltd. are *wholesale* distributors only. All individual retail enquiries concerning this amplifier should be addressed to the manufacturers: Sinclair Radionics Ltd., Comberton, Cambridge.

the 73 page

by Jack Hum G5UM

Curtain Up

To half a million enthusiasts in 200 countries practical electronics means the art of radio communication—and half a million is the approximate number of actual or would be transmitting amateurs the world over. Collectively, licensed amateur stations far outnumber all the broadcast, point-to-point and other professional service stations put together—and note that word "service". The amateur movement is a "service" and is designated as such in the International Telecommunications Union regulations agreed at Geneva in 1959.

These half-million members of the Amateur Service are truly at the service of the communities in which they live. They contribute know-how in practical electronics—that all-pervasive phrase again! They contribute even their stations when emergency communications are needed. They intercommunicate in the universal language of "radio English" (more about this another month) on six world-spanning frequency bands and three more local v.h.f. ones, by morse, speech, teleprinter and video. They are at once diverse yet homogeneous.

* * *

It is about these people that the present feature will talk. The Editor's brief to the writer is that this feature should address itself primarily to readers who are at an early stage in amateur radio rather than those that have been in it for many years. This does not mean that we shall be writing "a beginner's guide" to the art of amateur radio: there are plenty of *those* to be had from various sources at various prices.

Rather, we shall aim to help as much as we can by discussing the type of questions that baffle enthusiasts with feet on a lowish rung of the amateur radio ladder hesitant to hoist them on to the next one up—questions such as "What type of receiver should I buy—or should I try to make one?"

Or again: "Which are the best bands to listen on and at what times—and what am I likely to hear on them?"

Recognising, too, that nearly every short wave listener aspires to acquire in time that coveted transmitting licence we will help as far as we can with advice on this most important point.

What of aerials? Or v.h.f.? Or "sideband"? Amateur radio's very diversity means that there is going to be much to discuss in *The 73 Page*, and we cannot promise to get round to covering all possible topics at short order. It will take time to deal with even a few of the subjects which currently occupy the attention of the amateur service.

However, we will try—and *your* comments will be welcome for discussion here should you feel inclined to write in on any aspect of this specialised part of practical electronics that interests you.

Meaningful Number

Before one proceeds further a word or two about the running title to this feature may be to the point, for this title will headline it each time it appears (nice recognisability!).

Why *The 73 Page*? Because *73* is the most meaningful set of digits in amateur radio. It is the last thing a transmitting amateur says before he signs off a contact with a colleague.

It means *Best Wishes*. It is sought after as a motor car number, even as a house number. The Radio Society of Great Britain has it as its telephone number.

Its origin, lost in the mists of the early days of the electric telegraph, is believed to stem from abbreviations invented by the pioneers of the American railroad for quick communication between lonely signal cabins strung out across the prairies.

Today it is the most venerated phrase in amateur radio. We feel that none more appropriate could head this column.


Heart of "The Shack"—the Receiver

So much by way of introduction. Leaving generalities, now, and coming down to brass-tack practicalities, there is one question above all others that must be answered by every aspirant to amateur radio before he can ever begin to make a start. We have mentioned it already. It is: "What receiver?"


To find an answer to this question is not easy; it is a many-sided one. For the fully fledged communicator nothing will do but an advanced design of superhet receiver which has all the current refinements. But there are thousands upon thousands of enthusiasts who have not reached that stage—perhaps do not even want to!—yet are seized with a desire to make something of their own that will help them "to get their feet wet", something with which to paddle around in the every fascinating short wave spectrum.

To recommend suitable designs of receiving equipment (note the word "equipment": it embraces converters as well as receivers) would occupy the remainder of this number of PRACTICAL ELECTRONICS. To embark on constructional details about them would occupy several!

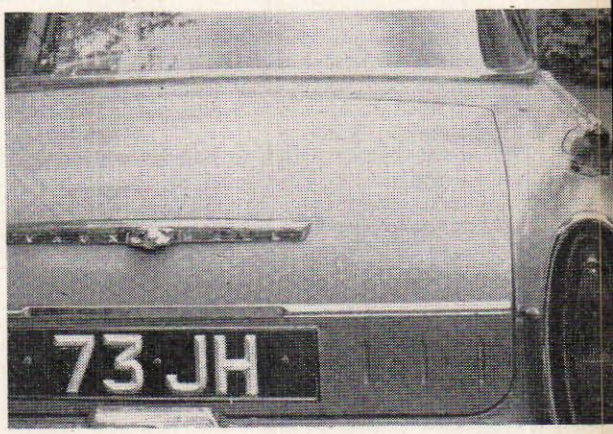There are nevertheless certain signposts along the route to short wave listening which will be examined on *The 73 Page* later on, and the destinations to which they lead explored. A number of them suggest methods of approach that offer the delights of h.f. reception at remarkably little cost, coupled with the fulfilment that comes from building equipment yourself.



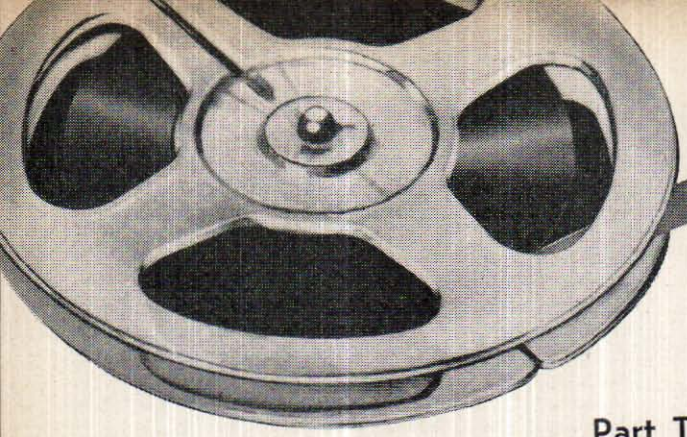A friendly greeting to fellow (radio amateur) travellers is conveyed by this car registration number. It should not be necessary to tell you the owner's name!



Sound on Tape

A SHORT SERIES FOR THE HOME RECORDING ENTHUSIAST

By H. W. HELLYER

Part Two

HAVING chosen the machine that suits both pocket and purpose, it is necessary to make the best use of it; not merely to tape the budgie and baby's first words, then relegate the recorder to the niche beneath the stairs. Like the car fanatic or the photography fiend, the tape recording enthusiast will soon be casting around for ways to improve upon his investment, and to obtain the best possible use from his machine.

First let us consider the microphone. If a microphone is supplied with the machine, it may be assumed that this suitably matches the input circuit of the recorder. But it may be required for an additional microphone to be used; there may indeed be a requirement for several microphones, plus a gramophone or radio input, to record a "programme", such as the commentary to a ciné film. Some care is necessary in selecting both microphones and that vital piece of equipment which is used to combine their outputs, i.e. a mixer.

MIXERS

There are two types of mixer, the *passive* and the *active*. The former type consists simply of a selection of sockets, with matching resistors and perhaps variable attenuators acting as level controls for the various inputs. The output from this device is plugged into the tape recorder so that the combined signal modulates the tape in the same way that a single microphone would. But such a device has severe limitations; there is bound to be an insertion loss, and it may not be possible to adjust the level controls to give sufficient combined output to modulate the tape correctly.

The answer to this problem is to use an active mixer, or mixer/pre-amplifier. There are many different types on the market, the simplest being a transistorised, single-stage amplifier to boost the low level signals to an acceptable voltage for the "radio/pick-up" input of the tape recorder, while mixing the microphone signals as before, and providing attenuation of the latter to match the inputs.

More comprehensive models use several separate pre-amplifiers for the different inputs, with individual gain controls, and perhaps a magic eye type of modulation level indicator. This type of device is intended to apply a signal to the high level input of the tape recorder, and will give better quality recordings because of the better signal-to-noise ratio.

The electronic mixer will have inputs for different types of microphone and other sources and should, properly, have a cathode follower output so that it may be used at a distance from the main machine, the signal transfer then being at low impedance.

For serious recording, a good mixer unit is indispensable. Fortunately, this is not a difficult item to construct, and circuits for suitable types will no doubt appear in future issues of PRACTICAL ELECTRONICS.

MODULATION LEVEL

Mention has already been made of the need for applying a signal of adequate strength to modulate the tape. The correct modulation level makes all the difference between a recording that is acceptable, and one that is either weak and hissy or overloading into distortion on peaks of sound.

It is worth while spending some time experimenting with one's tape recorder to find the correct modulation level for a known input.

If a magic eye is fitted, the leaves or bar of the eye should nearly meet on peaks, but not overlap, and the input gain should be adjusted for this optimum. If a weak input is used, the replay will have to be turned up more to compensate for this and the upshot will be a higher level of amplifier noise as well as the required signal.

The dynamic range of the individual machine will have to be determined by trial and error. At the lower level the hiss of tape noise will outweigh the recorded signal when this is played back. At the upper level the amplified signal will overload the machine and cause distortion.

Where a meter is used for signal level indication, or modulation level readings, it is possible to assess the optimum recording level more accurately. But the type of meter, and the associated circuit, needs some

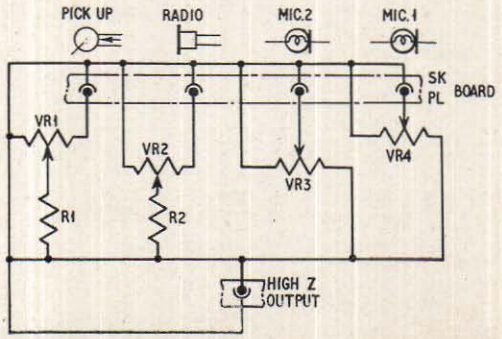


Fig. 2.1. A four-channel passive mixer. The values depend on matching and signal sources. If a low impedance microphone is used, a transformer is inserted with, as a refinement, a phase-reversal switch

consideration. Apart from the inherent sluggishness of a moving coil meter, compared with the quicker response of a magic eye to electrical changes, there are circuits deliberately designed to average out the sound changes and give a mean level indication. Some meters indicate volume units rather than peak readings. There are various methods of obtaining indications, and again, information concerning the conversion of a "domestic" tape recorder to more professional standards with meter indication in place of, or in addition to, the magic eye, will probably follow in due course. It is a subject worthy of some attention.

Whether a meter or magic eye is used, the aim is to record at a level which approaches the maximum modulation level. If the machine is correctly adjusted, this should give the best signal-to-noise ratio. But exceeding this value will bring about distortion, due to a clipping of peak voltages in the amplifier circuit. When using a meter, the correct level, if not indicated, must be assessed by trial and error. With a magic eye indicator, the illuminated "leaves" or "column" should approach one another, but not overlap.

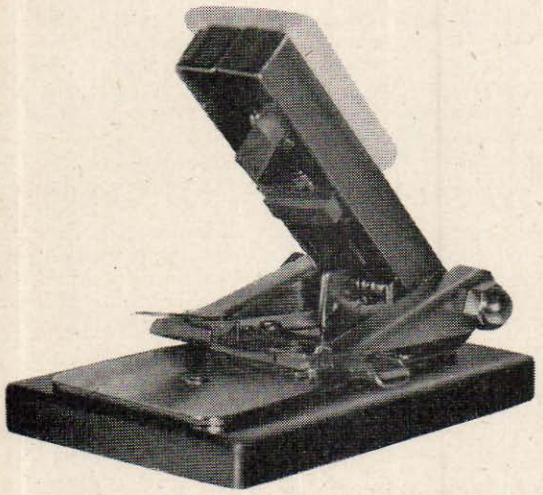


Fig. 2.2. A typical splicing block. Two cutters are incorporated; one makes a diagonal cut across the two ends of tape, the other is used to trim the edges of the jointing strip after this has been placed in position

The correctly modulated tape is then played back, and the controls adjusted for comfortable listening level. Control of tone is also carried out during playback. The circuits are intended to produce a "tailored response" during recording so that the replayed output follows the equalised response curve exactly. Tone modification can then be made to taste.

TEST SIGNAL

To test the correct setting of the modulation level indicator, a steady signal, as pure as possible, is required. We have a ready-made test source in the television test signal that precedes a programme and is also broadcast several times during the test card periods of the morning on both BBC and ITV. This is a steady tone, a sine wave, and, provided the television receiver is in good order, the output should be level and unvarying.

This signal is applied to the tape recorder—see later notes on this subject for the actual manner of connection—or alternatively the microphone can be used to pick up this sound, providing one is working in quiet surroundings.

Begin recording the tone on a clean tape, with the record gain control at its low level, and advance the control a regular amount every ten seconds. Note the position of the control and the closure of the magic eye. If a more accurate record of these steps is required, use a chinagraph pencil to mark the edge of the illumination on the glass envelope of this valve. These marks are easily rubbed off when the test is complete; the chinagraph pencil is a useful aid for editing purposes, enabling one to mark the outer surface of the tape, also, without damage.

Take a note of each step in this test, advancing the control until the illuminated portions overlap, and then a step beyond. Play back this recording, noting the steady increase in sound with each step, until an *edginess*, or harshness, is noted, with the sound at its loud level. Make a note of this portion of the tape, check against your listed magic eye indications and it should be found that the distortion has crept in at the stage when the illuminated portions just overlap. One has then a standard to which future recordings can be made.

A few tests like this will show why it is necessary to mix inputs correctly. There is an optimum level of input, at which the machine will give of its best. While a modern crystal microphone may give between 1 and 2 millivolts of signal, the output from a radio diode circuit may be 10 times as strong for adequate signal-to-noise ratio, and the output from a gramophone pick-up 10 times as strong again.

EDITING

Far too many tape recorders are purchased and then wasted. The tape that was supplied with the machine is used over and over again and there is an almost psychopathic abhorrence of editing.

Considering that the average tape of a radio programme has at least five cuts, and a playlet, for example, may require fifty splices of tape, there is certainly nothing to be lost be editing. Indeed, the experienced tape user will realise how much is gained by the excision of those agonising "ums and aahs" and the general tightening up of a script or programme.

TAPE SPLICING

There are many tape splicers on the market, varying from the simple slot in a block to the elaborate devices with clamps and clips and measuring scales. Whatever method is used, the technique is to make a cut which matches the angle of the joining piece of tape (which is why a splicer is a better idea than a kitchen knife on the corner of the table). The ends are laid together and a piece of jointing adhesive fixed across the back of the joint; that is, on the shiny side, not the duller, oxidised side, of the tape.

Ordinary adhesive tape must never be used for joining tape, however good its quality. When the tape is spooled and stored, the adhesive of "parcelling tape" tends to creep, causing the adjacent turns to stick and then jerk from the spool as the tape unwinds when next used.

The reason for the angled cut is to avoid a click as the splice passes the head on replay. For the same reason, a clean splice is required, with no gap between the ends. The duration of a splice passing the head gap is quite insignificant for ordinary work and, if properly done, should be unnoticeable.

OXLEY




LEAD THROUGH CAPACITOR

This is a useful capacitor which takes up a minimum of space.
The body and nut have 2BA threads and are silver plated. The ceramic tube is sealed into the body with an appropriate resin material under vacuum to withstand arduous climatic conditions.

NOMINAL VALUES
LT 1000–1000 pF.
LT 470– 470 pF.
LT 47– 47 pF.

TOLERANCE
−10% +80% or ±20%

WORKING VOLTAGE
350v D.C.

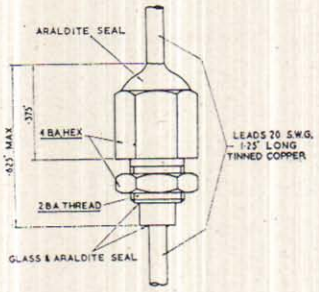

Write for technical details of these or any other Oxley products


OXLEY DEVELOPMENTS CO. LTD.
ULVERSTON, LANCASHIRE. Tel: Ulverston 2567

HOUSING HI-FI?

The three Nordyk Units illustrated comprises Speaker Enclosure (left) for 8″ hi-fi speakers 7 gns., Record Cabinet (centre) takes 150 records £5.17.6d., and Equipment Cabinet (right) for turntables and amplifiers 7 gns.

Available in teak, walnut or mahogany.

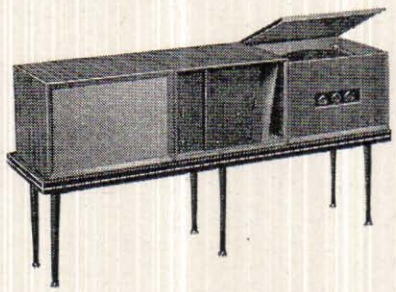Send for illustrated catalogue of 20 different models.



RECORD HOUSING
(Dept. P.E.12), Brook Road, London, N22
Telephone : BOWes Park 7487/8

FREE! COLOUR BROCHURE



This wonderful new, attractively illustrated FREE brochure brings you full details of the tremendous range of tape recorders and many unique features that we as BRITAIN'S LARGEST TAPE RECORDER SPECIALISTS offer you.
Full details of recorders we particularly recommend, and a comprehensive list of all models available today are contained in the brochure, together with our unique FREE TRAVEL VOUCHER entitling you as a customer to full refund of your travelling expenses to and from any of our showrooms.
Send for your FREE copy today, or call into any of our showrooms to see, hear and compare our fantastic selection of recorders.

5 STAR FEATURES

- ★ FREE TRAVEL TO AND FROM OUR SHOWROOMS
- ★ FREE DEMONSTRATIONS IN YOUR OWN HOME
- ★ OVER 300 MODELS FROM 15-243 GNS.
- ★ FREE ONE-YEAR SERVICING
- ★ FREE TECHNICAL ADVICE

Please send me your **FREE BROCHURE (P.E.2)**

Name.....

Address.....

.....

CITY & ESSEX TAPE RECORDER CENTRES LTD.
Head Office: Citex House, 191 Plashet Rd., London, E.13

CITY & ESSEX
TAPE RECORDER CENTRES

242/4 Pentonville Rd., N.1 (150 yds. from Kings Cross Station)	TER 8200
228 Bishopsgate, E.C.2 (Opposite Liverpool St. Station)	BIS 2609
2 Maryland Point Station, Stratford, E.15 (Adj. Station)	MAR 5879
205 High St. North, E.6 (Opposite East Ham Station)	GRA 6543
232 E. India Dock Rd., Poplar, E.14 (Adj. Blackwall Tunnel)	EAS 5978

NOTE: Bishopsgate Showrooms open Mon.-Fri. 9 a.m.—6 p.m. Sunday 9.30 a.m.—2 p.m. Closed Sat. Other Showrooms open Mon.-Sat. 9 a.m.—6 p.m. Thursday to 1 p.m.

RST

Cordially invite

Practical Electronics

readers

To try our unsurpassed

VALVE MAIL ORDER SERVICE

Vast quantities of modern and obsolete fully guaranteed valves available from stock at very moderate prices. Send S.A.E. for Full lists

SPECIAL 24 HOUR EXPRESS MAIL ORDER SERVICE

Callers welcome

AN EXAMPLE OF THE VALUE YOU GET from **RST**

BRAND NEW TRANSISTORS

OC35	10/-	OC72	8/-	OC81D	5/-
OC42	6/-	OC74	8/-	OC81m/pr	12/6
OC44	5/-	OC75	8/-	OC82	8/-
OC45	5/-	OC77	8/-	OC82D	6/-
OC71	5/-	OC81	5/-	OC170	6/-

SILICON RECTIFIERS

400 volts 350 mA ... ... 7/6 each

METAL RECTIFIERS

RM1 7/6 14A86	23/-	16RD 2-2-8-1	12/- (FC142)
RM2 8/- 14A97	26/-	16RE 2-1-8-1	10/- (FC150)
RM3 10/- 14A100	28/-	18RA 1-1-8-1	5/- (FC118)
RM4 17/6 14RA 1-2-3-2	21/- (FC301)	18RA 1-1-16-1	7/- (FC116)
RM5 19/6 14RA 1-2-8-3	25/- (FC31)	18RD 2-2-8-1	16/- (FC124)

SETS OF VALVES

IR5, IS5, IT4, 3S4, 3V4 ... ... Set of 4, 17/-
DAF91, DF91, DK91, DL92, DL94 ... ... Set of 4, 17/-
DAF96, DF96, DK96, DL96 ... ... Set of 4, 25/-


TERMS OF BUSINESS C.W.O. or C.O.D.
4/2 PACKING CHARGE ON ALL C.O.D. ORDERS. POSTAGE 6d. per VALVE

RST VALVE MAIL ORDER CO.

211a, STREATHAM ROAD, MITCHAM, SURREY


Telephone: MITcham 6202 & 6771

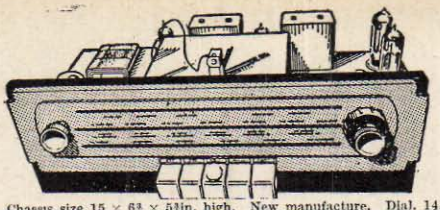Mon. – Sat. 9 a.m. – 5.45 p.m.
Wednesday 9 a.m. – 1 p.m.
Lunch 1.30 – 2.30



BRAND NEW AM/FM (V.H.F.) RADIO GRAM CHASSIS AT £13.13.0 (Carriage Paid)

Chassis size 15 × 6¾ × 5¾in. high. New manufacture. Dial. 14½ × 4in. in 2 colours, predominantly gold. 200-250v. A.C. only. Pick-up, Ext. Speaker, Ae., E., and Dipole Sockets. Five push buttons—OFF, L.W., M.W., F.M. and Gram. Aligned and tested. O.P. Transformer. Tone Control. 1000-1900 M.; 200-550 M.; 88-98 Mc/s. Valves EZ80 rect.; ECH81, EF89, EABC80, EL84, ECC85. Speaker 8 × 5in. and Cabinet to fit chassis (table model), **47/6** (post 5/-). 10 × 6in. ELLIPTICAL SPEAKER **25/-** to purchaser of this chassis. **TERMS:** (Chassis) **£3.10.0** down and 5 monthly payments of £2.4.0. Cheap Room Dipole for V.H.F., **12/6.** Feeder **6d.** per yard. **ALTERNATIVE DESIGN.** L.W. 1000-1900 M.; S.W. (9-15 Mc/s); M.W. 190-475 M.; V.H.F. 87-100 Mc/s: Gram position. Otherwise similar to above chassis. Price **£15.15.0** (carr. paid). **TERMS: £3.10.0** down and 6 monthly payments of £2.4.0. Circuit diagram **2/6.**

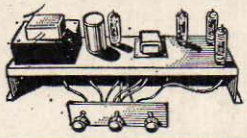

PUSH-PULL O.P. AMPLIFIER

£5.5.0 (6/- Carr.)

Brand new 200-240 A.C. mains Bass, treble and vol. controls, with valves EZ80, ECC83 and 2-EL84 giving full 8 w. Chassis 12 × 5¾ × 3¾in. With o.p. trans for 2-3 ohm speaker. Front panel (normally screwed to chassis) may be removed and used as "flying panel".

LAFAYETTE BRAND TAPE

MYLAR BASE

5in. Double play, 1,200ft.	15/–
5¾in. Double play, 1,800ft.	22/6
7in. Stand. play, 1,200ft.	12/6
7in. Long play, 1,800ft.	19/6
7in. Double play, 2,400ft.	25/–

TRIPLE PLAY

3in. 450ft.	12/6
4in. 900ft.	22/6
5in. 1,800ft.	42/6
5¾in. 2,400ft.	55/–
7in. 3,600ft. (unboxed)	75/–

FULLY GUARANTEED AT RECORD LOW PRICES

P.V.C. BASE

5in. Standard play 600ft.	8/6
5¾in. Standard play, 850ft.	11/6

ACETATE BASE


5in. Stand. play, 600ft.	8/–
5in. Long play, 900ft.	10/–
5¾in. Long play, 1,200ft.	12/6
7in. Long play, 1,800ft.	15/–

MESSAGE TAPES

3in. Stand. play, 150ft.	3/6
3in. Long play, 225ft.	4/11
3in. Double play, 300ft.	7/6
3in. Triple play, 600ft.	14/–

P. & P. 1/- extra per reel; 4 reels and over Post Free.

"REALISTIC" 'SEVEN'

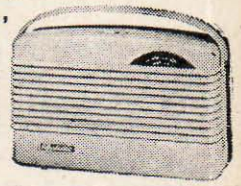


Transistor Superhet. 350 Milliwatt output, 4-inch speaker. All components mounted on a single printed circuit board size 5½ × 5¼in. in one complete assembly. Plastic cabinet with carrying handle, size 7 × 10 × 3¼in. External socket for car aerial. Ferrite rod aerial. Price for the complete parcel including Transistors, Cabinet, Speaker, etc. and full Construction Data: **£5.19.6.** P. & P. 4/6. PP9 Battery **3/9.** Data and instructions separately **2/6.** Refunded if you purchase the parcel. **Any parts supplied separately.**



SINGLE RECORD PLAYER USING EMI DECK AND PICK-UP

4 speed, 200/240 v A.C. Valves, rectifier and ECL82. Cab. size 12 × 11½ × 5¼in. attrac. coloured imitation leather finish. Takes 10in. records. **£7.19.6** carr. paid. **ALTERNATIVE TYPE OF SINGLE RECORD PLAYER** available, using BSR GU 7 motor and pick-up on one plate. Valves UY85 and UCL82. Cab. size 13¾ × 13 × 5¼in., red or blue rexine. Takes 12in. records. Price **£8.9.6** carr. paid.

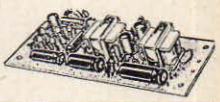4-TRANSISTOR MINIATURE PUSH-PULL AUDIO AMPLIFIER HIGH IMPEDANCE



PRINTED CIRCUIT. 4in. × 2¾in. 1¼in. over transformers. Output for 3-ohm speaker. Suitable for microphone, record player, guitar and intercom. 9 volt battery required. Frequency range 100 cps. to 25 Kc/s. Push-pull output class B. Instruction sheet provided. Fully wired ready for use. Two types. 200 mw. **29/6**; 1 watt, **41/-.** P. & P. 2/6.

4-SPEED AUTOCHANGERS

Carr. 5/- each

BSR-UA14	£5.19.6
GARRARD AUTOSLIM ..	£6.10.0
STEREO	£7.5.0
AUTOSLIM DE LUXE AT6	£10.19.6
STEREO	£11.10.0

2½-WATT AMPLIFIER

Our price ONLY **58/-** (post 5/-); a few hundred only; valves EF91 and ECL82 with metal rectifier; 6 × 4 × 1¾in. high (5in. over ECL82). Mains trans. and o.p. with vol. and tone controls; on-off; co-ax. input.

TAPE RECORDER AMPLIFIER

Fully built. Front panel 12½ × 3in. Chassis size 10½ × 5 × 4in. Valves EF86, ECC83 and 2EL84. Controls (1) MIC. Vol. (2) Tuner/P.U. Vol. (3) Play back or monitor. (4) Tone, 2 jack sockets for Tuner/P.U. and MIC-switch for superimpose. Separate power pack containing transf. & rectifier. For Collaro studio deck only. Price **£8.14.0** (6/- P. & P.).


ALL ITEMS ARE NEW AND FULLY BUILT UNLESS OTHERWISE STATED. TESTED BEFORE DESPATCH. Delivery by return.
Terms available on Items over £5. Send 6d. (stamps will do) for 20-page illustrated catalogue. C.O.D. 2/- extra
ALL ITEMS GUARANTEED 12 MONTHS. **VALVES 3 MONTHS**
Regret overseas orders cannot be executed.

GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants. (CLOSED WED.)

(2 mins. from Station and Buses). Aldershot 22240

PRECISION DECIMAL STEP PRE-AMPLIFIER

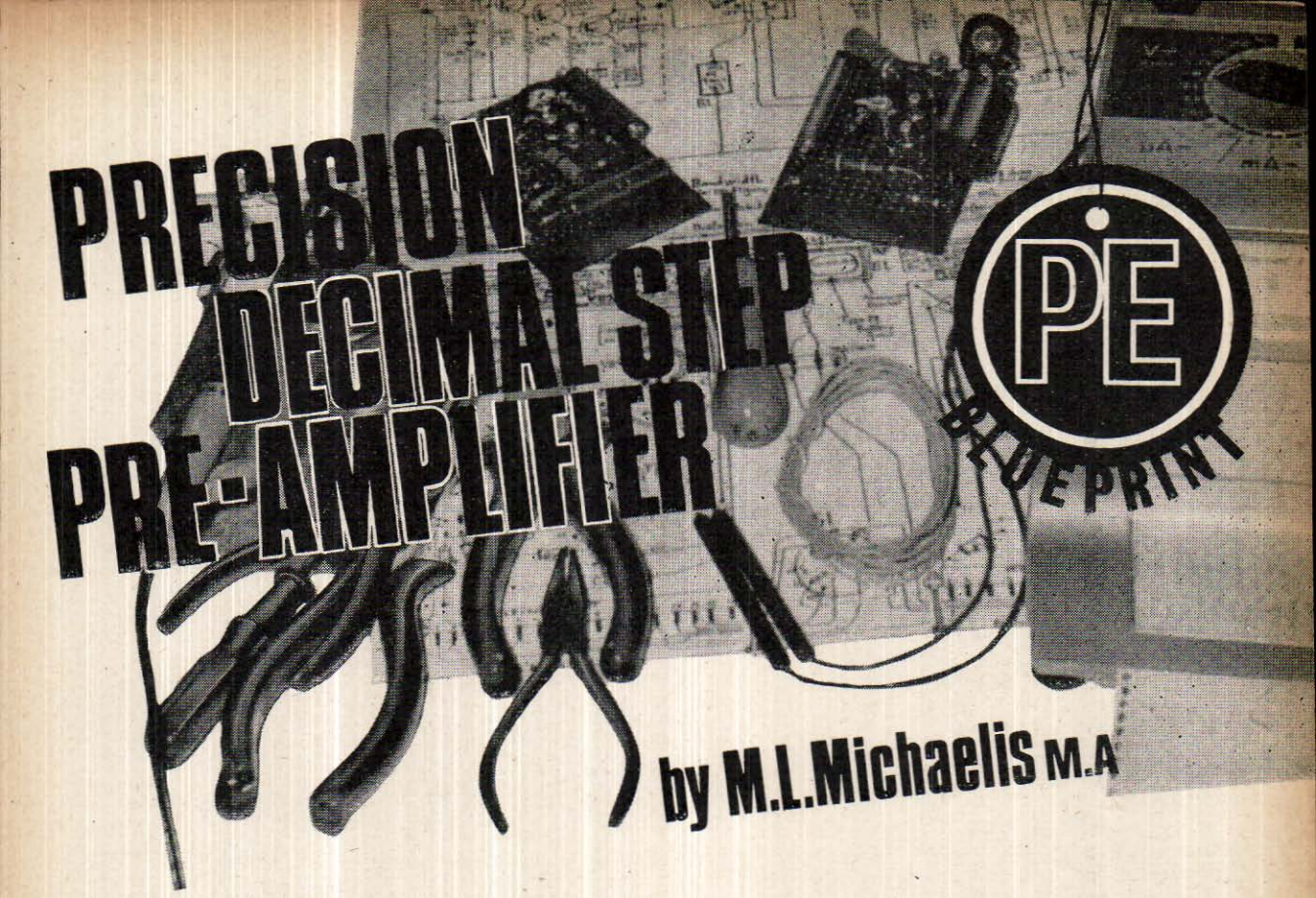

by M.L.Michaelis M.A

THIS article sets out to discuss some of the important practical questions involved in the design of a universal pre-amplifier with transistors, capable of both audio and metric applications. A complete design is given as well, detailed drawings appearing on the blueprint included in this issue of PRACTICAL ELECTRONICS. This pre-amplifier was developed and built by the author primarily for use between the probe and Y-amplifier input of an oscilloscope and for use with a transistorised tape recorder for various laboratory experimental purposes. Obviously many further applications exist.

GENERAL CIRCUIT DETAILS

Fig. 1 on the blueprint shows the complete circuit diagram of the prototype. This comprises two separate circuit cards, each having a gain of exactly 10. A central switch S1 connects either one or both of these cards between the input and output terminals, giving gains of exactly 10 or 100 respectively, or, in its third position, it switches the unit off.

The left hand card VB1 contains three cascade transistors TR1–TR3 and a d.c. peak bypass input circuit to the base of TR1. The latter is an essential feature in a universal unit of this nature, to prevent destruction of the transistors due to d.c. charging surges of anything up to several hundred volts when connecting the input to the anode circuits of valve equipment.

It may seem strange to use three transistors for a gain of only 10, but this is necessary to achieve the required high constancy. When properly built and adjusted, this circuit shows no perceptible change of gain (as displayed on an oscilloscope or meter) over temperatures from the freezing point up to over 50°C (over 122°F), or for battery voltage variations between 6V and 11V.

The pre-amplifier design here described should be suitable for tropical temperatures when shielded from the direct rays of the sun, or for European summers, outdoors in full sunshine. Even considerable heating indoors, due to standing the unit on top of valve operated items of equipment of high power dissipation, should give no gain fluctuations or other troubles.

With the assurance that the gain really is rock steady throughout all working conditions likely to be met, it was convenient to make it exactly 10 per circuit card, wherewith the complete unit is a decimal-step pre-amplifier. The great advantage thereof is that, when used in conjunction with calibrated oscilloscopes, or with a.c. voltmeters, the existing scales can still be read-off and mentally multiplied or divided by powers of 10, i.e. a mere shift of the decimal point is required.

The right hand circuit card VB2 contains another identical cascade of three transistors TR4–TR6, giving a gain of 10 once again. The only difference compared to the first card is that the d.c. peak bypass circuit is here omitted, because the input signal is always applied to VB1. The right hand circuit card VB2 also contains the emitter follower output stage TR7.

The circuit of VB1 is always operative, in both the gain 10 and gain 100 settings of the complete pre-amplifier. In the gain 10 setting, TR7 is switched directly onto the output of TR3 in VB1 and TR4–TR6 idle with C4 shorting the base of TR4 for a.c. to prevent parasitic instability. C4 is connected up to the negative supply line (and not to chassis) for this purpose, to prevent application of d.c. voltages of incorrect polarity; either connection would be just as good for pure a.c. signal considerations.

In the gain 100 setting, the output of VB1 is connected through to the input of VB2, via C4, and the output at TR6 is connected through to TR7.

IMPEDANCE

If the pre-amplifier is to be used for metric purposes between the probe and the input socket of an oscilloscope or valve voltmeter, the input impedance must be equal to that of the instrument in question.

In the published design the input impedance at PL1 has been adjusted to exactly 135 kilohms to match the Y-amplifier input impedance of the author's oscilloscope. *Adjustment of the input impedance to other values will be fully discussed later. But, in brief, it should be explained that this will involve a change of values for R3, R4, R6, R8, R9, VR1, and VR2, also possibly the replacement of TR3 by an OC304.*

The output impedance at PL2 is very low, as given by the setting of VR2 or VR4 (the respective base feeds for TR7 in the gain 10 and gain 100 settings) divided by the current gain of TR7 (about 20); it is, in fact, about 500 ohms. The purpose of this low output impedance is to permit arbitrary lengths of uncompensated co-axial cable between the output and the oscilloscope Y-amplifier input without loss of bandwidth due to cable stray capacity.

TABLE 1: GENERAL & EXPERIMENTAL USES OF THE DECIMAL STEP PRE-AMPLIFIER

AUDIO INPUT FROM	SET S1 FOR GAIN OF	AMPLIFIED OUTPUT TO
crystal microphone or moving coil microphone with transformer	100	gramophone socket (pick-up) of domestic radio or simple amplifier
moving coil loudspeaker as microphone, without transformer	100	ditto
moving coil loudspeaker as microphone, with reversed output transformer (step-up) as matching	10	ditto
magnetic pick-ups	10 or 100, according to type	ditto
any microphone, close to decimal step pre-amplifier	10 or 100, according to length of cable to main amplifier	microphone input of *distant* public address amplifier (field-work over large areas)
crystal set or simple diode receiver	100	4,000 ohm headphones
any audio signal arising during experiments (many pulsed signals can also be handled—e.g. from photocells, Geiger counters, etc.)	10 or 100, as required	wherever required, un-amplified signal having been insufficient

As far as audio uses are concerned, the low output impedance gives satisfactory performance on 4,000 ohm headphones, or even on ones of somewhat lower impedance, and long runs of screened cable are permissible from the output to a remote main amplifier without loss of treble when using the unit as a microphone head pre-amplifier.

PERFORMANCE

The bandwidth of the pre-amplifier as described in this article extends from 2c/s at the low frequency end on either gain setting to about 100kc/s at gain 100 or about 150kc/s at gain 10 at the high frequency end. These figures refer to the so-called 3dB-down points, i.e. the gain has dropped to one-half of that at mid-band frequencies at these limits. The response is substantially flat over the entire "hi fi" audio frequency range from 20c/s to 20kc/s and some way beyond either end.

Harmonic distortion is extremely low up to drives giving an output of 1 volt r.m.s.; it is not visible as deformation of a sinewave on an oscilloscope up to this signal level, a fairly sensitive visual test. Phase-shift is negligible, so that pulse and transient responses are excellent.

The unit is thus equally satisfactory for both high fidelity audio work and for waveform display on an oscilloscope.

APPLICATIONS

Fig. 8 shows the manner in which the pre-amplifier may be connected to increase the Y-deflection sensitivity of an oscilloscope. The input impedance of the pre-amplifier must of course be adjusted to match the oscilloscope.


Fig. 9 sketches the arrangement to be adopted when using the pre-amplifier to increase the sensitivity of any a.c. valve voltmeter. The impedance matching requirements are here the same as for oscilloscopes if one desires to use the existing probe of the valve voltmeter at the input of the pre-amplifier while maintaining exact decimal step sensitivity increases.

If a simple diode peak rectifier circuit is interposed between the pre-amplifier output and the meter input, d.c. valve voltmeters or high resistance multimeters

Complete unit External view ▼



Complete unit Internal view ▶

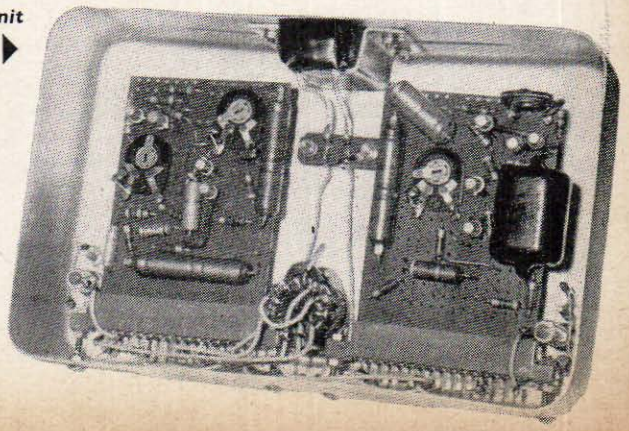

PRECISION DECIMAL STEP PRE-AMPLIFIER

PE BLUEPRINT

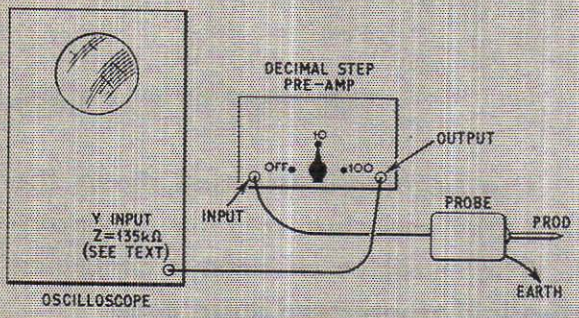


FIGURE 8

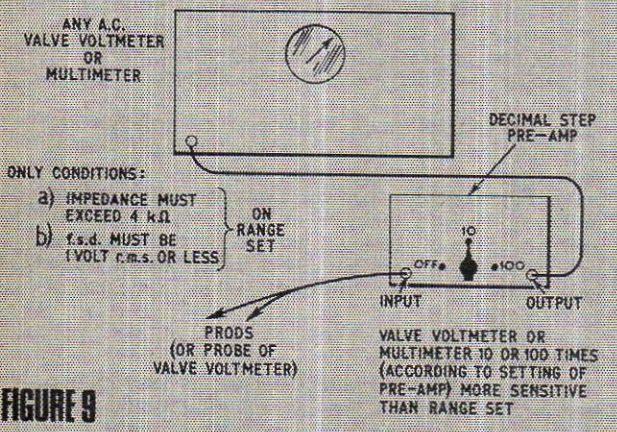


FIGURE 9

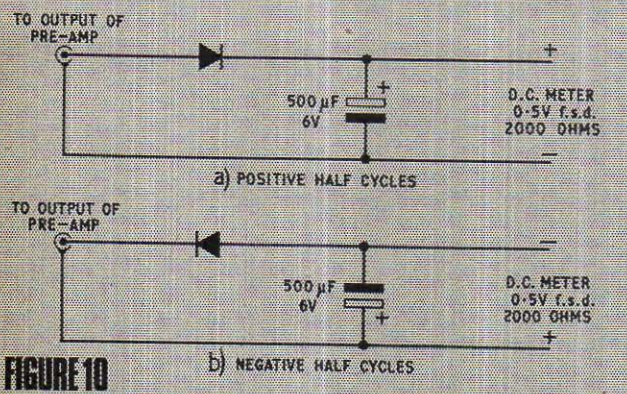


FIGURE 10

Fig. 8. Decimal step pre-amplifier used to increase Y-deflection sensitivity of an oscilloscope

Fig. 9. Method of increasing the sensitivity of an a.c. voltmeter

Fig. 10. Use of decimal step pre-amplifier to convert 0·5V f.s.d. meter to 5mV/50mV f.s.d. a.c. voltmeter

on low d.c. ranges may therewith be converted to sensitive a.c. "valve" (transistor) voltmeters. There are no impedance matching conditions to be observed in this case, provided that the meter and rectifier circuit impedance is much greater than the output impedance (500 ohms) of the pre-amplifier. Multimeters having a resistance of 4,000 ohms per volt and upwards on the d.c. ranges can thus be operated from the pre-amplifier output.

Fig. 10 shows a suitable rectifier circuit to make the meter indicate peak volts of one polarity. Reversing the diode and the connections to the meter makes it indicate peak volts of the other polarity. In the case of arbitrary non-sinewave signals applied to the input of the pre-amplifier, where the peak voltages on negative and positive half cycles may differ, corresponding different readings will be obtained.

Taking the Caby Model B20 multimeter as a typical example, we have a lowest d.c. voltage range of 0·5V f.s.d., 2,000 ohms impedance, available on the meter. This is satisfactory in every way for connecting to the output of the pre-amplifier via the rectifier circuit of Fig. 10 which may be built into the coaxial connecting cable fitting PL2 on the pre-amplifier at one end and the multimeter terminals at the other end. The multimeter is therewith an a.c. voltmeter giving full scale deflection for 50mV peak or 5mV peak (gain 10 or gain 100 settings respectively) applied to the pre-amplifier input, an excellent sensitivity. Moreover, the arrangement is usable not only at power mains frequency, but at any frequency over the entire hi fi audio range. If measuring positive and negative half cycles separately where these differ, it is important to remember that the pre-amplifier inverts the signal in the gain 10 setting, but not in the gain 100 setting.

Table 1 lists some typical audio applications of the pre-amplifier. These certainly do not require the accurate decimal step and stabilised gain, but it is, in the interests of universality, necessary to point out that the pre-amplifier is in every way suitable for such applications as well.

THE VEROBOARD SYSTEM

Although orthodox printed circuit panels would be used in commercial systems of this nature wherever the production numbers are at all high, the *Veroboard System* is more suitable for small production numbers and especially for amateur and experimental equipment.

The VB2503 panel is made of plastics card drilled over its entire surface with a square grid of holes having 0·15in spacing, 16 holes across the width and 21 holes along the length. The rear side only is fitted with 16 parallel strips of copper, each respectively running along one row of 21 holes along the length of the panel. These strips are thickened and gold-plated at one end, where the whole card plugs into a linear 16-contact socket.

Components are arranged on the front side (Fig. 2 and Fig. 4), where there are no copper strips; the wire ends are pushed through holes at respectively convenient positions, soldered with a spot of solder at the rear where they pass through the copper strip, and then cut off close.

If alterations are subsequently required, melt the solder by applying an iron at the rear while pulling the component wire with pliers from the front. Then jab a piece of bare tinned copper wire through the hole

continued on page 115

APPLICATIONS OF LIGHT-OPERATED SWITCHES

Described by G. J. KING

Our heading illustration shows the Mullard ORP cadmium sulphide photoconductive cell. The sensitive element is contained in a glass dish 14mm in diameter and 8mm deep

THERE are hosts of applications for a device capable of switching electrical contacts on or off automatically when its light-sensitive control element is subjected to changes in level of illumination. A typical application is for switching on a car parking light at dusk and switching it off again at dawn without human control.

A similar application is for switching on house, shop, office, factory or street lights when the ambient illumination drops below a predetermined level, and for switching them on again when it rises. This does away with the old-type time-switch. This application is also useful to discourage unwanted visitors when the house is left unoccupied for any lengthy period, such as during holidays and so forth.

Other applications include the automatic opening of the doors of a garage when the light-sensitive element picks up the rays of the headlights of the oncoming car, the counting of articles as they drop through and thus interrupt a ray of light which is directed onto the light-sensitive element, a smoke alarm, for use in smokeless zones, where a ray of light is interrupted by the presence of excess smoke in a chimney flue or stack, this reducing the intensity of light falling upon the light-sensitive element . . . and so on.

The basic functions of light-operated switches are the production of a potential, the change in a potential or the change in characteristics—such as resistance—of the light-sensitive control element. Such effects can be utilised to energise or de-energise a relay, thereby opening or closing a pair or more of electrical contacts, which in turn operate a light, bell or other alarm device, or an electric motor often in a form of servo arrangement.

BASIC CONTROL

In cases where the control current is very high, a secondary relay with a heavier set of contacts than those of the primary relay is controlled by the contacts of the primary relay. The basic controlling features are shown in Fig. 1.

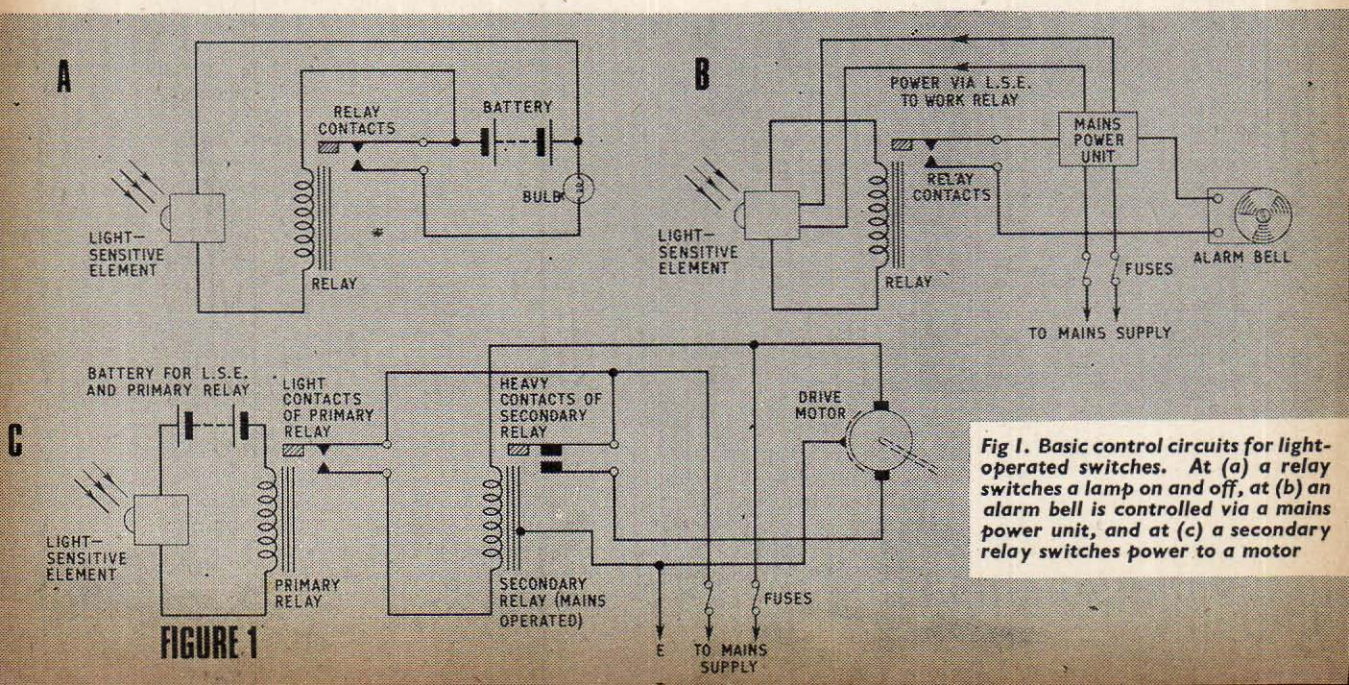


FIGURE 1

Fig 1. Basic control circuits for light-operated switches. At (a) a relay switches a lamp on and off, at (b) an alarm bell is controlled via a mains power unit, and at (c) a secondary relay switches power to a motor

At (a) we have the straightforward case, such as may be used to switch a parking light on and off. Here the battery could be the car accumulator (6 or 12V). This battery, being a d.c. supply, could both operate the relay by way of the light-sensitive element and work the bulb in the parking light.

The idea is that during the day the light-sensitive element in conjunction with its control circuit would pass insufficient current to energise the relay. The contacts thus remain open and the bulb extinguished. At lighting up time, however, the light-sensitive element and associated control produces an increase in current from the battery through the winding of the relay. This energises the relay, closes the relay contacts and thus passes battery current through the bulb which then lights.

At this juncture it should be noted that the arrangement could be reversed. That is, the relay could be energised during the daylight hours, under which condition the contacts would be *open*, and then de-energised during the night time, when the contacts would be closed to pass battery current through the bulb. It is just a matter of choosing the required light-sensitive element controlling circuit and relay.

At (b) we have a little more complicated arrangement, where a mains power unit is employed both to operate the alarm bell and the relay, the latter via the light-sensitive element and its associated circuit.

At (c) is shown an arrangement which features two relays. Here the primary relay is operated by a battery in the light-sensitive control circuit. When the contacts of this relay close, power from the mains supply is caused to pass through the winding of the secondary relay, which is a mains-operated type. The heavy contacts of this relay then close and pass mains power to the drive motor, which may work a garage door or some other mechanical device.

It is possible, of course, to make the whole control unit mains-operated to avoid the battery for the primary relay. This could be accomplished by an extension of (b), where a mains power unit supplies a d.c. voltage for the relay and light-sensitive control circuit, or by using a mains-operated primary relay.

So much, then, for the basic control and relay circuits, but what about the light sensitive element itself?

LIGHT-SENSITIVE DEVICES

An early light-sensitive element was the photo-electric cell. This was used extensively not only for controlling switching circuits by light but also for the replay of sound tracks on cine films. The photo-electric cell is, in fact, still used for the latter application, but other light-sensitive elements are better suited for control work. The photo-electric cell is a device which delivers a small amount of electricity (potential) when light is directed upon it. The greater the light intensity, the greater the potential, within limits, of course.

Recent innovations include the phototransistor and the photoconductive cell, the latter being illustrated in our heading, and it is mainly about these that this article will be concerned.

Let us first look at the phototransistor. This works in a similar way to a normal transistor into which light is allowed to enter. A transistor is, in fact, a light-sensitive device, but its usual opaque coating prevents it from responding to changes in level of illumination.

PHOTOTRANSISTOR

However, the phototransistor is a transistor designed to fully exploit the inherent photo-electric properties. It can be considered as a light-sensitive semiconductor junction diode (photodiode) in which the light current is amplified by the normal transistor action.

The forward current in any semiconductor diode is caused by a uniform interchange of current carriers across the junction. These can be electrons moving in one direction and positive holes moving in the opposite direction.

This unhindered flow across the junction, giving rise to the normal flow of electricity, results because the potential applied across the junction is in opposition to and outweighs the so-called "potential barrier" which is formed across the junction when it is manufactured, due to the initial diffusion of current carriers.

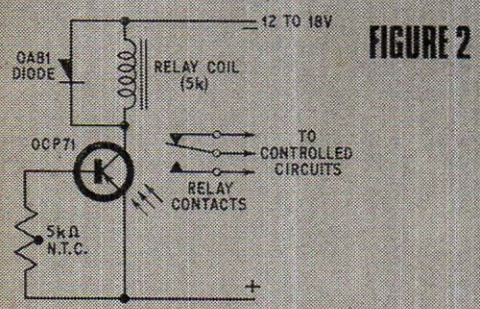


FIGURE 2

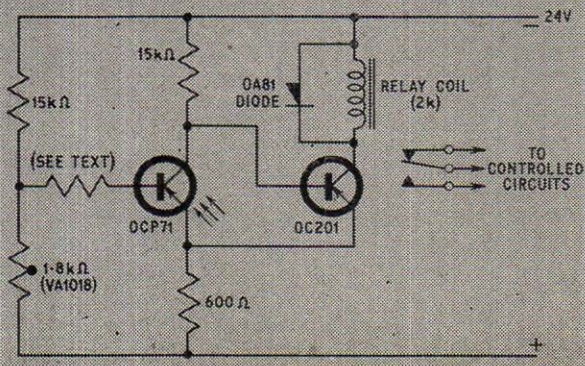


FIGURE 3

Fig 2. A basic switching circuit using the Mullard OCP71 photo-transistor
Fig 3. By the use of a transistor d.c. amplifier, the sensitivity and temperature stability are enhanced, as this circuit shows

The potential barrier is thus broken down by the applied forward potential.

Now, when the diode is biased in the reverse sense, the inherent potential barrier is effectively reinforced. This means that normal current flow is prevented because the barrier prevents the interchange of current carriers. Thus, we have the normal rectifier action where current can flow freely in one direction and is virtually prevented from flowing in the opposite direction. The same effect is exhibited by a diode valve, of course.

However, with a junction diode there is some difference. With a thermionic valve diode, if the anode is negative with respect to the cathode, no current whatsoever will be passed. But with a semiconductor diode, a "leakage current" results under this reverse-biased condition. This is because of a flow of "minority carriers" (these being positive holes in *n*-type material and electrons in *p*-type material).

In effect, the minority carriers tend to multiply when light is allowed to fall on the junction. The leakage current then rises, and as the light intensity increases, so does the leakage current increase. The normally low leakage current when no light is falling on the junction is called the "dark current", and the higher value of leakage current when the junction is illuminated is called the "light current".

The light-to-dark current ratio is enhanced considerably by amplification due to the normal transistor action of the device, and with a well designed circuit this ratio can be made as high as 480 at a temperature of 25 °C. Temperature comes into it because the minority carriers also tend to multiply as the junction temperature increases. Thus, at 45 °C the ratio may drop to around 20.

Under normal operating temperatures the sensitivity of the device is remarkable. For example, if a 2½V pea lamp is barely lit from a 1½V source, and the resulting small illumination is focused by a simple lens on to the sensitive area of the phototransistor over a distance of a few centimetres, the amplified current rises from the order of microamperes (the dark current) to in excess of 5 milliamperes! Thus, the usefulness of the phototransistor as a light-sensitive element can be appreciated.

SWITCHING CIRCUITS

Fig. 2 shows a simple switching circuit using the Mullard OCP71 phototransistor. Extra sensitivity and temperature compensation is given by the use of a transistor d.c. amplifier following the phototransistor, as shown in Fig. 3. Both of these circuits lend themselves to considerable experimentation to suit specific applications. The base resistor can give a degree of temperature compensation if of the negative temperature coefficient type. The actual value is best determined experimentally to suit both the conditions of maximum temperature and the light level. However, a component in the order of 5 kilohms is suitable for most applications.

The relay should have a coil of about 5 kilohms and it should pull-in at a power of about 5mW for reliable operation.

PHOTOCONDUCTIVE CELL

The photoconductive cell is essentially a resistive element made of cadmium sulphide which has the property of decreasing greatly in resistance when subjected to illumination. In complete darkness the resistance is in the order of 10 megohms and this can drop to as low as 75 ohms when the cell is fully illuminated. This very large dark-to-light resistance ratio means that the cell is extremely sensitive. More so, in fact, than the phototransistor.

The cell, which is often called a light-sensitive resistor (l.s.r., for short), is made by Mullard in three versions. There is the ORP12, which has maximum response in the red region and is intended for general purpose industrial applications and automatic contrast and brightness control in television receivers. This has a maximum limit of power dissipation of 200mW up to 40 °C. At higher temperatures the allowable dissipation reduces progressively to zero at 60 °C.

The RPY15 (formerly called the ORP15) has a maximum power dissipation of 400mW at 25 °C and is thus more suitable for applications where power is an important factor.

A low power unit is the RPY14. This has a maximum dissipation of 20mW at 25 °C and is designed essentially for exposure meters and automatic camera applications.

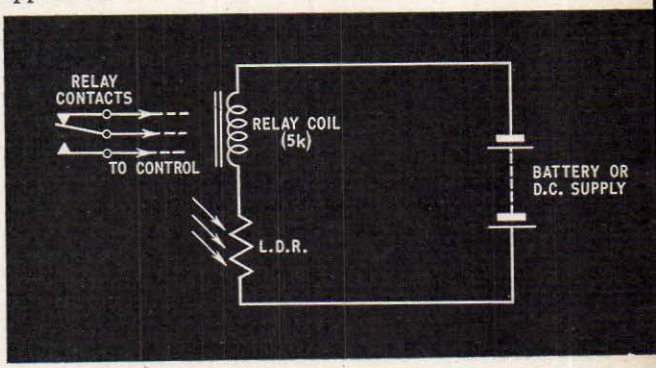


Fig. 4. A photoconductive cell (light-dependent resistor) can be arranged in this simple circuit to provide an effective light-operated switching action

The l.d.r. has several advantages over the phototransistor for certain applications. For one thing, the sensitivity that itself can convey to a control circuit is greater than that of the phototransistor. The larger versions can dissipate a greater power than the phototransistor, the collector dissipation of the OCP71, for instance, being limited to 100mW at 25 °C (50mW at 45 °C). Moreover, the l.d.r. can operate over a wider range of potentials than the phototransistor including operation at a.c., and polarity is not important. It can be arranged in a simple series circuit, as shown in Fig. 4.

SIMPLE L.D.R. CONTROL CIRCUIT

Here the l.d.r. is shown connected in series with a 5 kilohm relay coil and a 12V d.c. supply. If the relay is adjusted to pull-in at about 12mW (e.g. at a current of a little over 1·5mA), a very sensitive light-operated switching device can be evolved from the simple circuit. For reliable results, however, a sensitive relay is desirable.

A more robust Post Office type relay can be utilised by following the simple l.d.r. circuit with a transistor d.c. amplifier, as shown in Fig. 5. Here the l.d.r. is caused to change the base bias of the OC72 transistor and thus give an increase in collector current (and hence, relay current) when the resistance of the l.d.r. drops under the influence of illumination.

continued on page 115

THE WHARFEDALE Super Range

Each loudspeaker in this range is fitted with roll surround for low resonance and double diaphragm assembly for extended HF response.




SUPER 8/RS/DD

Impedance 10/15 ohms.
Ceramic Magnet.
Flux density 14,500 oersteds.
Total flux 60,000 maxwells.
Aluminium Voice Coil.
Max. input 6 watts rms or 12 watts peak.
Frequency range 40-20,000 c/s.
Bass resonance 50/60 c/s.
Price: 134/2 inc. P.T.


SUPER 10/RS/DD

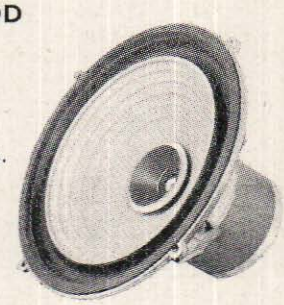
Impedance 10/15 ohms.
Flux density 16,000 oersteds.
Max. input 10 watts rms or 20 watts peak.
Frequency range 30-20,000 c/s.
Aluminium Voice Coil.
Bass resonance 38/43 c/s.
Price: 218/8 inc. P.T.



SUPER 12/RS/DD

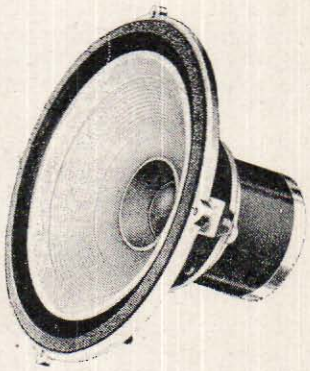Impedance 12/15 ohms.
Flux density 17,000 oersteds.
Total flux 190,000 maxwells.
Aluminium Voice Coil.
Max. input 20 watts rms or 40 watts peak.
Frequency range 25-20,000 c/s.
Bass resonance 26/32 c/s.
Price: 350/- (no tax).



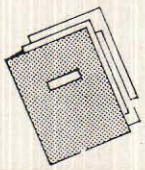

Write for informative and fully illustrated 12 page booklet

Wharfedale

WHARFEDALE WIRELESS WORKS LTD
IDLE BRADFORD YORKSHIRE

Telephone : Idle 1235/6
Telegrams : 'Wharfdel', Bradford.


THINKING TAPE? THINK *Brenell*

If you're thinking in terms of tape recording, then the Brenell deck and complete recorders should be uppermost in your mind. The reliability, the versatility and the quality of manufacture are seldom equalled in other tape recorders (even in those costing much more).

How many can equal or better this specification?

4 record/playback speeds 1⅞, 3¾, 7½ and 15 ips • 3 motors (capstan motor-hysteresis synchronous) • low 'wow and flutter' content (0.05% at 15 ips, 0.1% at 7½ ips, 0.15% at 3¾ ips and 0.25% at 1⅞ ips) • double-gapped ferrite erase head to minimise erase noise • narrow-gapped record/playback head to give extended frequency response • pause control • superimpose control • 8¼" dia. reels (to take 10½" dia. N.A.B. reels at extra cost) • fast rewind • digital rev. counter.

Mark 5 Series 2 Deck

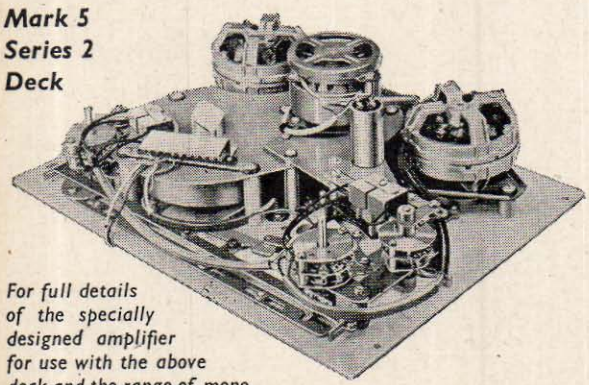

For full details of the specially designed amplifier for use with the above deck and the range of mono and stereo recorders, write or telephone the sole manufacturers:

Brenell

PLEASE NOTE OUR NEW ADDRESS:

BRENELL ENGINEERING CO. LTD.
231-5 LIVERPOOL ROAD, LONDON, N.1
Telephone: NORth 8271 (5 lines)

GD840

PROTECT YOUR TAPE RECORDER

WITH A STRONG, SMART COVER

Smart waterproof cover to give complete protection to your tape recorder. Made from rubberised canvas in navy, wine, tan, grey and bottle green with white contrasting pipings, reinforced base, handy zip microphone pocket and name panel.

Grundig	TK.1	... 49/6	Telefunken	75/15 & 76K	... 55/-	Stella	ST458	... 79/-
,,	TK.5	... 55/-	Philips	8108	... 57/6	,,	ST459	... 84/-
,,	TK.6	... 67/6	,,	3548		Saba		... 63/-
,,	TK.8	... 63/-	,,	3534	... 87/-	Elizabethan	FT.1	... 66/-
,,	TK. 14 & 23 & 18	... 59/6	,,	3459	... 79/6	,,	FT.3	... 75/-
,,	TK. 20	... 52/6	,,	EL3538	... 63/-	,,	LZ29	... 75/-
,,	TK. 24	... 55/-	,,	EL3542	... 63/-	Fi-Cord	1A	... 52/6
,,	TK. 25	... 55/-	,,	EL3536	... 70/-	Fidelity	Argyle	... 55/-*
,,	TK. 30	... 60/-	,,	EL3515	... 57/6	Clarion	(with strap)	52/6
,,	TK. 35	... 63/-	,,	EL3541/15	... 57/6	Brenell	Mk.5	... 77/-
,,	TK. 40 & 41	66/-	,,	3541H	... 72/-	,,	3 star	... 69/-
,,	TK. 46	... 82/-	,,	Starmaker	... 66/-	Truvox	R92 & 94	... 99/-
,,	TK. 55	... 63/-*	Cossor	1602	... 57/6	Robuk	RK.3	... 67/6
,,	TK. 60	... 75/-*	,,	1601	... 63/-	Ferrograph		... 88/-
,,	TK830/3D	63/-	,,	1604	... 79/-	Sony	521	... 90/-
,,	Cub	... 35/-*	,,	1605	... 84/-	Revox		... 84/-
Telefunken	85	... 65/-	Stella	ST455	... 63/-	Optacord	414 + 412	63/-
,,	95	... 69/6	,,	ST454	... 57/6	*Without Pocket		


A. BROWN & SONS LTD.
24-28, GEORGE STREET, HULL TEL: 25413, 25412

'SUPER SIX'

LONG & MED. WAVE TRANSISTOR RADIO KIT

NOW ONLY £4.17.6 (post 5/-)

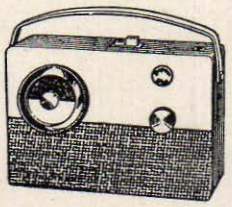Owing to a fortunate bulk component contract the price of this model is now reduced to £4.17.6. Purchasers who have already paid the previous higher price will have the difference refunded on application.



- All new parts.
- 6 transistors and diode.
- 350mW output.
- Superhet circuit, Ferrite rod aerial.
- Weymouth Radio printed circuit board.
- Component positions and references printed on back of board.
- Nicely styled wooden cabinet, 11 × 7½ × 3½in.
- Vinyl covered in various colours.
- 6 × 4in. speaker giving good bass and treble response.
- Full instruction booklet 2/-. Free with kit.
- I.F. frequency 470 kc/s.
- Lining up service if required.
- All parts supplied separately. Write for list. S.A.E. please.
- Set can be supplied fully built for **£6.17.6** tax and carriage paid.
- 9v. battery required. VT9 or P.P.9 (3/9 with kit).

"MINOR" RECORD PLAYER WITH "MAJOR" PERFORMANCE fully built, rexine covered, 10 × 7 × 5½ in. 4 transistor amplifier. Good volume. 7 in. records 45 & 33 r.p.m. **£6.7.6** (Post 5/-). Battery 3/9.

TRANSISTORS

Packet of 3 coded RF transistors (equivalent of OC44/5) **7/6** post paid. Set of 6 transistors and diode with circuit diagram. Neatly packed in foam-lined box; useful for presentation. **15/-** post paid.

Trade Supplied.

ELECTRONICS (Camberley) Ltd.
15 Victoria Avenue, Camberley, Surrey.
(Closed Saturday)

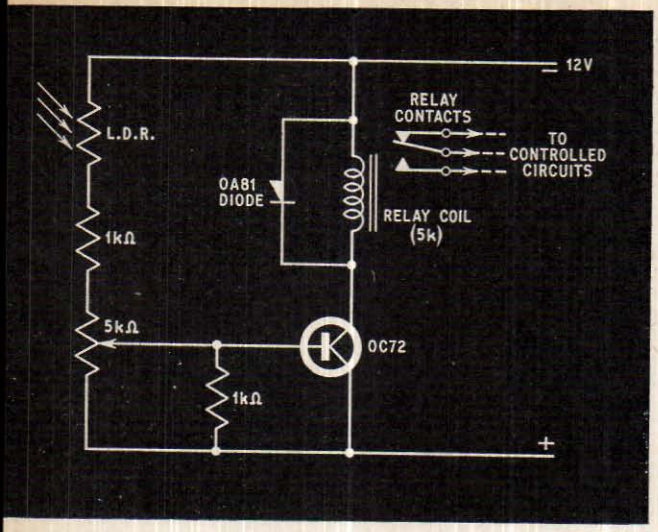


Fig. 5. A d.c. transistor amplifier following the l.d.r. allows the use of a more robust relay and provides a facility for sensitivity adjustment

The 5 kilohm potentiometer is used to adjust the base bias to give the required light/dark sensitivity conditions. Note that the diode across the relay winding in Figs. 2, 3 and 5 is to suppress the voltage surges which are otherwise likely to develop across the coil and damage the transistor during the switching cycle.

Several light-operated switches of the nature of those described in this article have been built by the author, and one application which has not yet been mentioned is for the measurement of speed.

This application is useful at race meetings of all types. At the finishing post a beam of light is arranged to cross the track and hold-on a relay of a light-operated switch. Now, when this beam is broken by the winner passing the finishing post, the relay switch changes over and operates a mechanical arrangement which stops a timing watch or other type of timer. Thus, provided the timing device is started when the race commences (this can be arranged automatically as well if needed) the winner himself stops the timing, and the actual time taken can be read off the dial in the ordinary way.

The experimenter in electronics will almost certainly find many other applications for the circuits described in this article. ★

PRACTICAL ELECTRONICS BINDERS

EASI-BINDERS specially designed to hold twelve issues of PRACTICAL ELECTRONICS are now available.

These binders are finished in maroon waterproof and greaseproof cloth and are embossed with gold lettering on the spine.

Order your binder from:

Binding Department,
George Newnes Ltd.,
Tower House,
Southampton Street,
London, W.C.2.

The price, per binder, is 13s. 6d., inclusive of postage.

PRECISION DECIMAL STEP PRE-AMPLIFIER

continued from page 109

rapidly while again applying the iron, to clear the hole of solder before inserting the new component.

It is advisable to use a miniature pencil-bit iron, e.g. of the 6 volt 10 watt variety. The copper strips on the cards take solder extremely rapidly and readily, so that it is possible to work quickly enough to prevent damage to transistors.

In the diagrams, Figs. 2, 3, 4, and 5, the rear copper strips have been numbered 1 to 16 from left to right as viewed from the front (components side) of the cards, and the 21 holes along any strip have been lettered A to U commencing from the socket end. Any hole can thus be specified by the corresponding number and letter combination. Where straps are shown between two holes these are simply short pieces of bare tinned copper wire cross-connecting different copper strips. Some of these straps are also located on the rear side, directly over the copper strips, as shown in Fig. 3 and Fig. 5.

The copper strips are to be interrupted at all the specified holes on the rear side of each card. Messrs. Vero Electronics sell a special hand awl, Cat. No. VB3011, for this purpose. This consists of a wooden tool handle carrying a small drill shaft of somewhat greater diameter than the width of the copper strips. A blunt pin extends at the front end of the drill shaft and exactly fits the holes in the circuit card. The drill is therewith held central while it scrapes the copper strip away at the desired point.

The two circuit cards, together with their associated sockets, can be accommodated quite conveniently in a box measuring approximately 8in by 5in and 2¼in deep. Fig. 7 shows the arrangement of the items inside the box and also details the interboard wiring.

Next month : the concluding part of this article will discuss some of the principles involved in the design of this pre-amplifier; factors which determine the input impedance will be explained and practical information given for adjusting this to some other value

Contributed Articles

The Editor will be pleased to consider for publication articles of a theoretical or practical nature. Constructional articles are particularly welcome, and the projects described should be of proven design, feasible for amateur constructors and use currently available components.

Intending contributors are requested to observe the style in our published articles with regard to component references on circuit diagrams and the arrangement of the components list.

The text should be written on one side of the paper only with double spacing between lines. If the manuscript is handwritten, ruled paper should be used, and care taken to ensure clarity, especially where figures and signs are concerned.

Diagrams should be drawn on separate sheets and not incorporated in the text. Photographic prints should be of a high quality suitable for reproduction; but wherever possible, negatives should be forwarded.

The Editor cannot hold himself responsible for manuscripts, but every effort will be made to return them if a stamped and addressed envelope is enclosed.

Ultrasonic Remote Control...

REMOTE control of apparatus is possible over distances upwards to 20 feet with this simple transmitting and receiving equipment.

The transmitter is housed in a popular type of torch case and is indeed as simple to operate as a normal electric torch. Just point the transmitter at the receiver, switch on and the ultrasonic beam radiated will be picked up by the receiving transducer, converted into electrical energy, and applied to operate a relay.

Unlike radio wave transmission, this "wireless" control system does not require a G.P.O. licence or other official sanction before it can be used.

APPLICATIONS

Apart from the obvious novelty value this ultrasonic equipment has certain very practical applications. We can only mention a few, but other applications will occur to many readers.

Remote channel selection on television receivers is possible if an electrically operated channel selector switch is fitted in the receiver. This switch would move one position for each pulse sent out by the transmitter. Radio receivers with preset tuning could be similarly controlled.

Any mains powered equipment could be brought into operation from a distance. For example, garage doors could be operated from inside a car, if the necessary electro-mechanical equipment is installed in the garage.

Although the effective range of the equipment as described in this article is 20ft maximum, some hints are given for increasing this upwards to 100ft for those who may wish to experiment further with ultrasonic remote control.

TRANSDUCERS

Two identical Gulton type 1404 ultrasonic transducers are used in this equipment. One functions as a transmitter—radiating pressure waves at a frequency of 40kc/s. The other transducer operates in the reverse manner converting the pressure waves back to electrical energy. The two units may be freely interchanged between the transmitter and the receiver.

Transducers should be bought as a pair, since it is important that their nominal frequencies be the same within $\pm$ 500c/s.

TRANSMITTER CIRCUIT

A pair of OC71 transistors are used in a feedback oscillatory circuit, this is shown in Fig. 4. The transducer X1 is connected in the feedback loop and provides a high Q circuit with a resonant frequency of 40kc/s.

Power for the transmitter is obtained from a miniature 9V battery (PP3 or DT3). The current consumption is 4mA.

RECEIVER CIRCUIT

A transducer of identical type to that used in the transmitter is incorporated in the receiver, see Fig. 1. A voltage is developed across this transducer X2 when it is subjected to pressure waves. This voltage is applied to the base of the first amplifying stage TR3. The collector of this transistor is directly coupled to the base of TR4 and the gain of these two stages is stabilised by means of overall negative feedback.

The signal is passed on via C2 to another two-stage directly coupled amplifier consisting of TR5 and TR6. Negative feedback is used here also to maintain constant gain. A tuned transformer T1 couples TR6 collector to the output stage TR7. This transformer is tuned to 40kc/s and ensures optimum sensitivity as well as providing rejection of other ultrasonic signals.

A relay RLA is connected in the collector circuit of TR7, and this becomes energised when TR7 is switched on by a signal passed on from the preceding stages of the receiver. The single-pole, make-break contacts of RLA can be used to switch power supplies or to operate other circuits in the apparatus it is intended to remotely control.

A 9V battery supplies the receiver. The consumption is 8mA.

RECEIVER CONSTRUCTION

All components for the receiver are accommodated quite easily on a laminated plastics board measuring 4in $\times$ 4½in. The prototype model described and illustrated here was built on a piece of Veroboard. It is not essential of course to use this particular material and if preferred a similarly sized piece of laminated plastics or even hardboard could be employed.

In such a case the components could be secured to terminal posts consisting of short pieces of 18 s.w.g. tinned copper wire inserted through holes drilled in appropriate positions (see Fig. 3). Use a drill slightly smaller than the wire to ensure a tight fit. Push the wire through the board until about ¼in emerges then cut off leaving a similar length protruding at the other side. Wire up the posts on one side of the board to agree with the diagram in Fig. 2 before mounting the components on the other side.

If the Veroboard is being used, remember to break the copper strips where indicated (see Fig. 2).

The relay coil is held in position by two loops of wire which pass through holes in the board.

INSTALLING THE RECEIVER

Mounting or housing arrangements for the receiver assembly will depend upon the application requirements or personal choice.

Generally speaking, it will be convenient to mount the receiver unit adjacent to the apparatus being controlled, or even within the same cabinet as for example in the case of a radio or television receiver. In this way the wiring from the relay to the controlled circuit is kept short.

The transducer must be mounted in such a manner that it will "look" directly towards the transmitter when the latter is brought into operation. If a 0·937in diameter hole is drilled in the front of the cabinet or container, the transducer can then be pushed through so it is flush with the front surface. If the cabinet material is not sufficiently thick to permit this method being adopted, a hole approximately ¾in diameter should be drilled and the transducer secured to the inside surface by means of a clip or bracket.

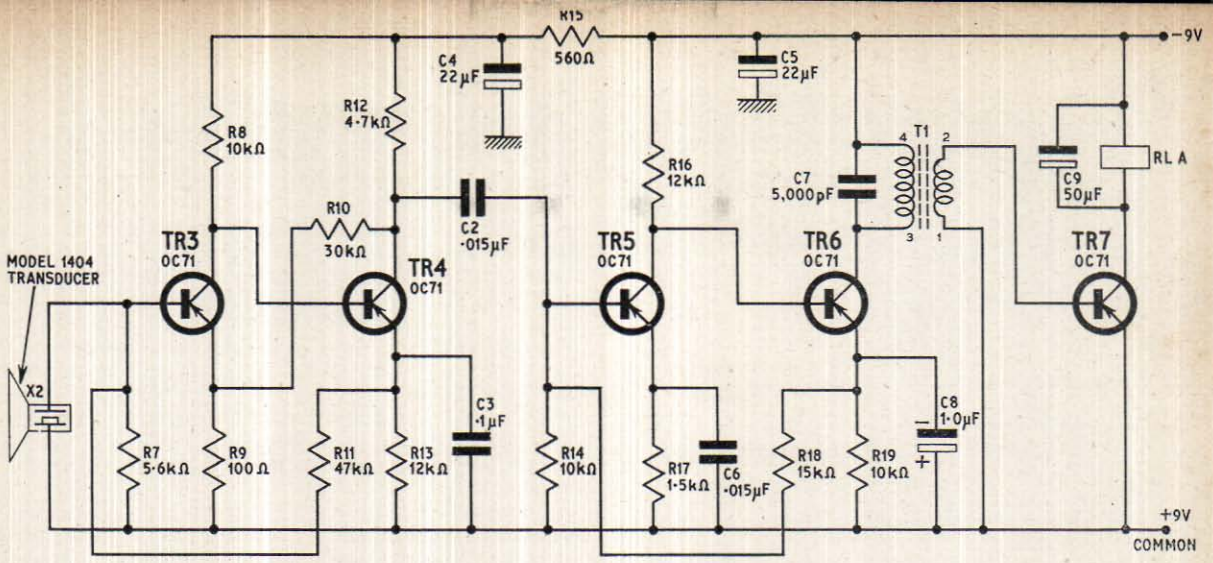


Fig. 1. The ultrasonic receiver circuit diagram

When wiring up the relay contacts to the controlled apparatus, ensure that these connections are well insulated and isolated from the components and wiring of the ultrasonic receiver.

The relay contacts have the following maximum ratings:


Power	.. ..	15W
Current	.. ..	1A
Voltage	.. ..	250V

Contact resistance is 0.05 ohm and the actuate time is 2msec.

TRANSMITTER CONSTRUCTION

The transmitter uses few components and the circuit is quite simple. However, due to the compact form of its assembly a certain amount of dexterity is called for during construction.

Fig. 2. The copper strips on the receiver Veroboard must be cut as indicated

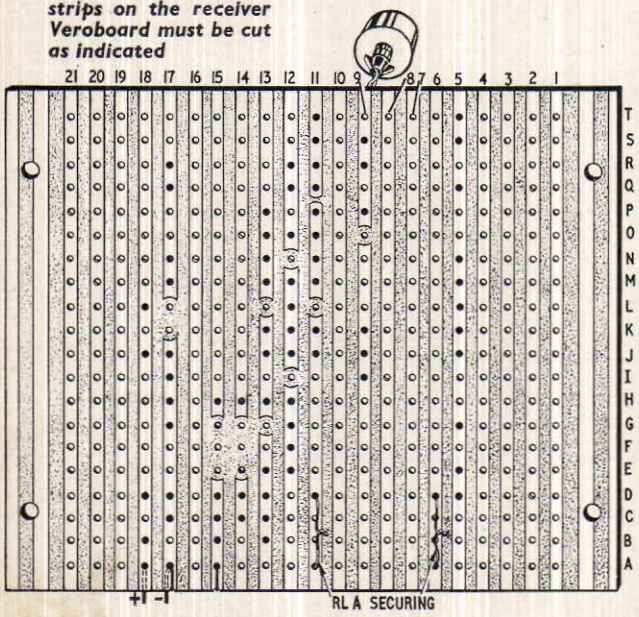


No insurmountable problems should arise if a torch case of the type and size specified is obtained. A larger torch case could be used if so desired; it would be necessary then to increase the width of the component panels to ensure a good fit in the case.

The first task is to prepare two small pieces of Veroboard as shown in Fig. 5.

Next mount the resistors and transistors in position on each board. The most tricky operation comes next. Solder one end of C1 to the (inner) side of panel A, at the point indicated in Fig. 5. Carefully manipulate the other lead on this capacitor to allow this to be soldered to panel B as indicated. Finally, secure this sandwich assembly by inserting short lengths of 20 s.w.g. tinned copper wire through facing holes in the two panels at the four positions 1A, 4A, 1J and 4J.

Initially solder these four wires to one panel only. Carefully adjust the position of the panels until there is a separation of $\frac{1}{4}$in between their inner surfaces, and then solder the other ends of the four wires to secure

Fig. 3. Layout of the receiver components on the other side of the Veroboard

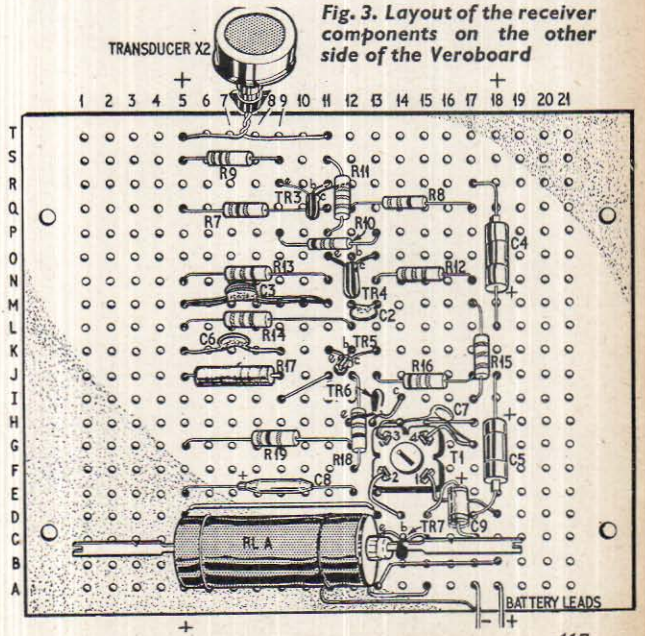


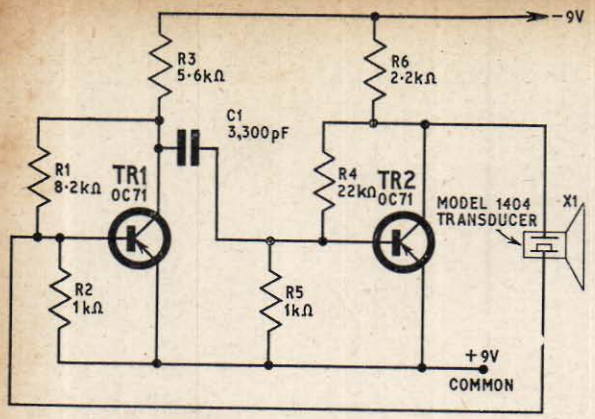


Fig. 4. Circuit diagram of the transmitter

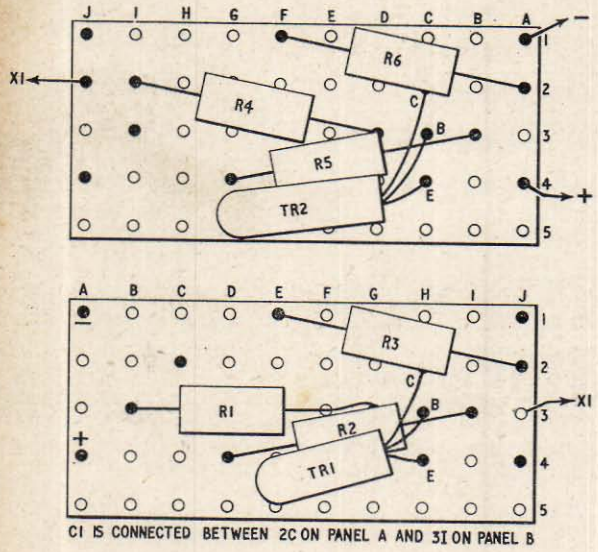

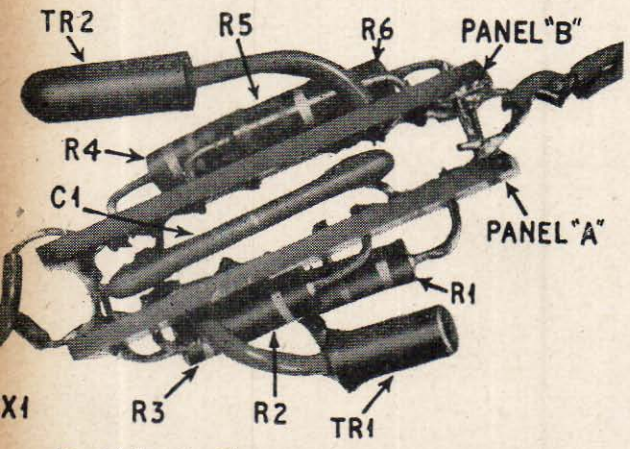


Fig. 6 (above). The transmitter assembly ready for insertion into the torch case

the whole assembly. The completed assembly is illustrated in Fig. 6.

Connect two insulated flexible leads to the miniature coaxial plug, twist these leads and cut off leaving a 1in length. Solder the free ends, one to panel A and the other to panel B as indicated "to × 1" in Fig. 5.

Connect a lead of about 3in length to the linking wire A1 as indicated in Fig. 5. Use blue coloured plastics covered flexible multi-strand wire. Single conductor leads are not at all suitable for this purpose—since their rigidity will inhibit the manoeuvres that are involved in the assembly process, and will probably result in breakages occuring at soldered connections.

TORCH CASE

A "Vesta" plastics torch case available at many multiple stores is used in this design. This particular case is made in a variety of colours, it is 5¾in long and has an internal diameter of 1in.

Remove the top cap from the torch case. Take out the glass, bulb, and reflector; these items are discarded.

Examine the switch mechanism. The brass tongue which protrudes towards the top of the case must be cut off as far down as possible. This can be performed with a pair of tin snips. Solder a (red coloured) plastics covered flexible lead to the stub and bring this lead down and out through the bottom of the case. Refer to Fig. 7. A small instrument type iron is essential, and care must be taken not to allow the bit to make contact with the plastics case. Place the transmitter assembly inside the lower portion of the case, but with its end protruding slightly.

Connect the red lead from the switch to point A4. Now gently push the assembly up inside the case until the coaxial plug emerges at the top. Fit the transducer to this connector. Refit the plastics top cap.

Move the assembly back down the case (applying *slight* pressure on the transducer face at the same time pulling *gently* on the blue battery wire) until the face of the transducer is level with the top edge of the torch cap.

continued on page 146


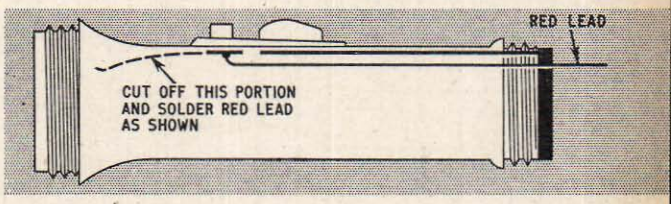


Fig. 5 (above, left). The transmitter panels showing the arrangement of components. Panel B is above; Panel A below. Each panel measures 1½in by ¾in

Fig. 7 (above). Modification to the torch switch

Fig. 8 (below). A sectional view of the torch case with the transducer, transmitter assembly, and battery installed

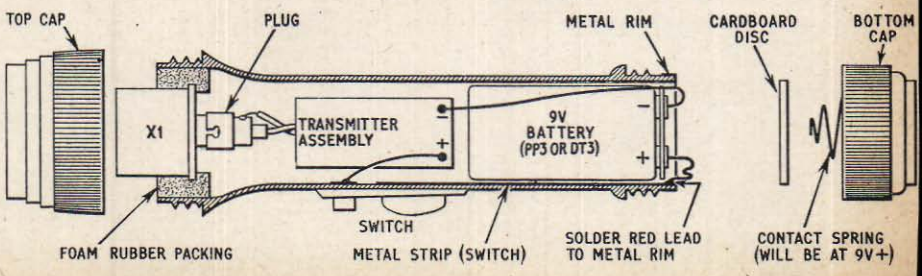

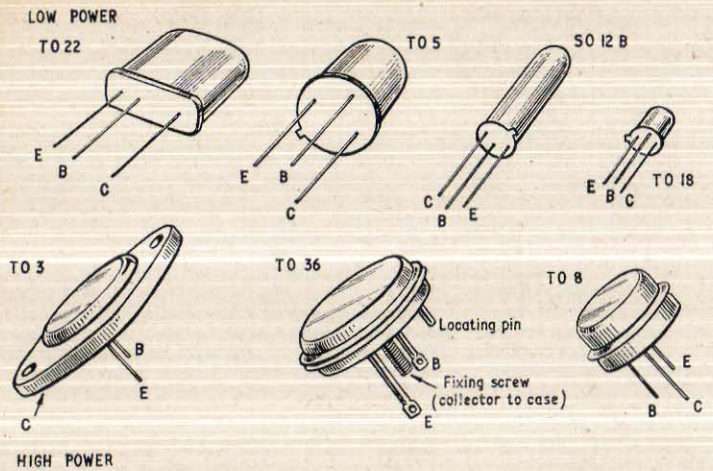


Fig. 16. Some typical transistor encapsulations from the Newmarket range

TRANSISTOR *DO*s AND *DON'T*s

DO:

1. Check polarity (*npn* or *pnp*).
2. Check battery supply polarity.
3. Identify leads correctly.
4. Ensure correct type.
5. Ensure whether transistor should be insulated from chassis.
6. Ensure contact of the faces of power transistors are smooth and that thermal contact with the heat sink is efficient.

DON'T:

1. Bend leads too close to the seal.
2. Solder leads without heat shunt.
3. Apply heat too long.
4. Mount in or near strong magnetic or electrostatic fields.
5. Operate transistors above maximum ratings.
6. Use "quick heat" gun type soldering irons.

Useful Tips

1. Silicone grease smeared on the surfaces in contact with the heat sink will increase heat conduction.
2. Black matt heat-resistant paint used on heat sinks and transistors helps dissipation of unwanted heat.
3. Long nose pliers, or a crocodile clip with two copper slugs soldered into the jaws, serve as heat shunts, when soldering into position. The heat shunt should be attached to the wire being soldered.

PRACTICAL electronics
Transistor Pocket Book
Presented in two parts with our December and January issues

THERMIONIC DEVICES
Diode

Construction

The circuit symbol and typical construction of a diode are shown in Figs. 1 and 2, with indirect heating to cause electron emission from the oxide coated cathode. Less common now is the method of direct heating where the cathode (often made of tungsten wire similar to an electric lamp filament) is directly heated by passing a current through it.

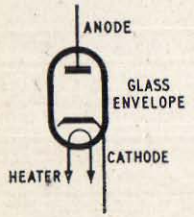


Fig. 1. Circuit Symbol

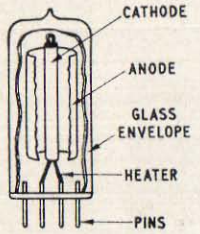


Fig. 2. Construction


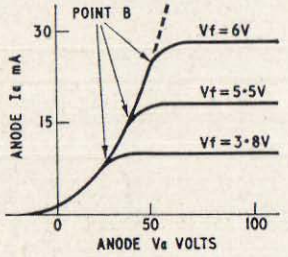


Fig. 3. Characteristics

Theory

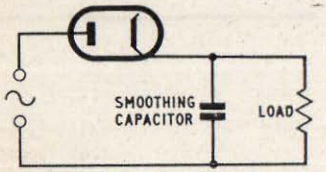
The curves of the characteristics in Fig. 3 conform to a definite law where the current through the valve $I_a = V_a^{3/2}$ and is known as the "threehalves law" up to point B on the curves. Above point B saturation occurs where all the electrons in the space charge around the cathode are being drawn to the anode and no further increase in anode current is possible for a given heater voltage V_f.




Applications

Diodes are used in numerous circuits some examples of which are shown in Figs. 4, 5, and 6.

Fig. 4. A.C. rectification (left)
Fig. 5. Detection (below left)
Fig. 6. Signal Limiting (below)

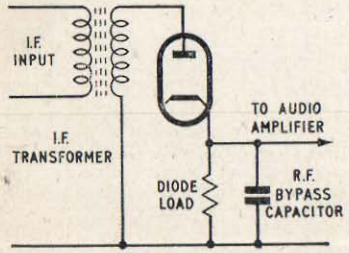

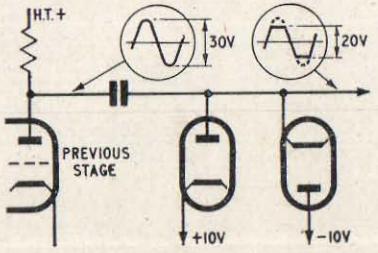

Basic Configurations

The circuits in Fig. 15 show the three basic configurations in which transistors are used and the table gives some typical characteristics and parameters of low power transistors.

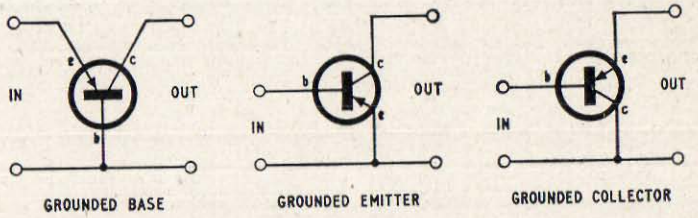


Fig. 15. Basic transistor configurations

	Grounded Base	Grounded Emitter	Grounded Collector
INPUT SIGNAL TO	Emitter	Base	Base
OUTPUT SIGNAL FROM	Collector	Collector	Emitter
CURRENT GAIN	approx. 1	approx. 50	approx. 50
VOLTAGE GAIN	High (approx. 160)	High (approx. 160)	Low (approx. 1)
INPUT IMPEDANCE	Low (200Ω)	Medium (1000Ω)	High (100kΩ)
OUTPUT IMPEDANCE	High (200kΩ)	Medium (40kΩ)	Low (1000Ω)
POWER GAIN	Medium (30dB)	High (40dB)	Low (16dB)
H.F. RESPONSE (POWER = 3dB DOWN)	High (400kc/s)	Low (12kc/s)	Dependant on Load resistance
PHASE SHIFT	0 deg (output in phase with input)	180 deg (output inverse to input)	0 deg (output in phase with input)

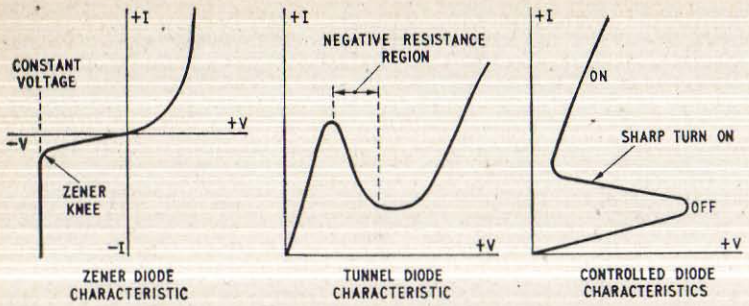


Fig. 13. Characteristics of special purpose diodes

Transistor

For the purpose of this booklet *pnp* transistors only will be considered but the information given will also apply to *npn* types except that biasing and h.t. supplies have reverse polarity d.c. voltages applied.

The addition of an extra element to the junction diode, *p*-type material in the *pnp* transistor and *n*-type in the *npn* transistor produced a device capable of amplification. In practice the *n*-type material in a *pnp* transistor is extremely thin. Typical constructions of some transistors are shown in Fig. 14.

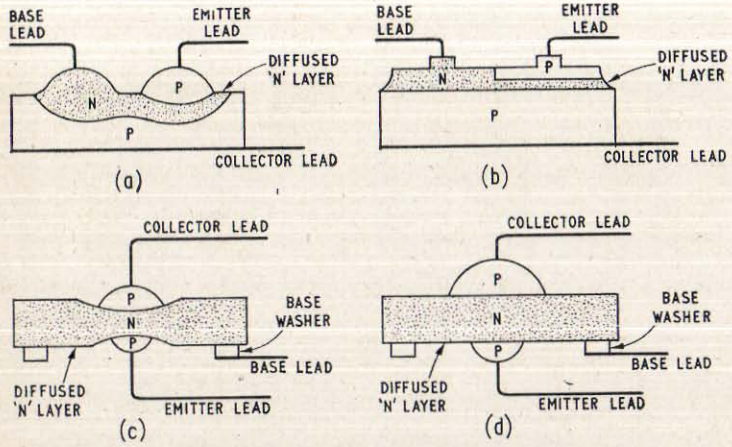


Fig. 14. Transistor construction methods
(a) post alloy diffused (p.a.d.t.) *(b) 'MESA' type*
(c) microalloy diffused (m.a.d.t.) *(d) 'Drift' type*

Triode

De Forest found that the addition of a third element or electrode (called a grid) to the diode placed close to the cathode relative to the anode enabled a small variation of voltage on the grid to produce a large variation of anode current. This discovery and its development precipitated a technological revolution, the implications of which the world still hasn't fully realised.

Construction

The varieties of triode types are too numerous to be treated fully by this booklet but a typical receiving triode, the construction of which is common to all types, is shown diagrammatically in Fig. 8. The grid can be seen to be a form of spiral wire. The electrons pass from cathode to anode through the spaces between each turn of the coil.

Theory

The characteristic curves given in Fig. 9 of anode current against anode voltage for various values of negative grid voltage are similar to those for the diode except that the grid voltage is the third parameter.

From the characteristics it can be seen that as the grid voltage is made more negative the anode current is eventually reduced to zero. It is this variation of anode current with grid voltage that produces amplification and is known as mutual conductance. The change in voltage across a load resistor, placed in series with the valve anode and h.t. positive rail, is greater than the change in grid voltage that produced it. More detailed information on this principle is given in the centre portion of this Data Booklet to be given with the January issue of PRACTICAL ELECTRONICS.

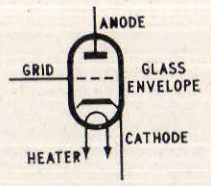


Fig. 7. Triode circuit symbol (left)

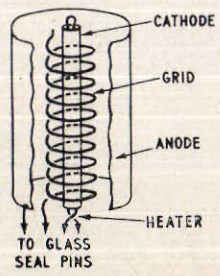


Fig. 8. Triode construction (below left)

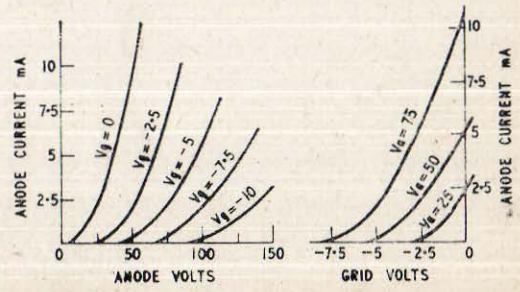


Fig. 9. Triode characteristics (below)

Applications

The applications of triodes are as varied as the different types, but generally speaking triodes are usually found in stages where a low noise factor is more important than high amplification or high frequency response. At high frequencies triodes become less effective due to the shunting effects of interelectrode capacitance, especially the capacitance between anode and cathode, known as the Miller Effect.

At very high frequencies special triodes are used which have very low capacitance. Special triodes are used in some transmitter circuits but neutralisation of the interelectrode capacitance by "external" means is still necessary.

In the tuner sections of television circuits an arrangement is often used whereby the anode load of a triode r.f. amplifier is in the form of another triode circuit with its grid grounded to a.c. This arrangement is known as a "cascode" amplifier; the grounded grid prevents feedback of the amplified signal and so reduces the Miller Effect.

Tetrode

The tetrode as its name suggests is a triode with an extra electrode interposed between the grid and anode. The fourth electrode is known as the screen grid and is held at a steady voltage approaching that of the anode, providing extra amplification and greater mutual conductance.

In the characteristics shown in Fig. 10, a region of what is known as "negative resistance" occurs due to the secondary emission of electrons from the anode resulting in the repulsion of electrons arriving at the anode from the cathode.

This condition is normally a disadvantage in most applications and is avoided. However, it has been found that it can be usefully employed in some types of oscillator.

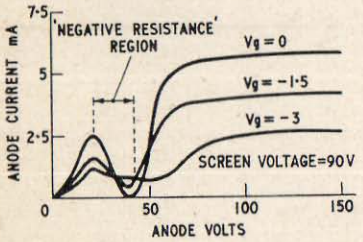


Fig. 10. Tetrode

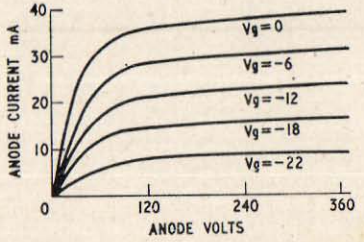


Fig. 11. Pentode

Pentode

The pentode has a fifth electrode interposed between the screen grid and anode and is normally held at cathode potential. Its function is to increase the effective working portion of the characteristic available by reducing secondary emission from the anode (Fig. 11). The "negative resistance" region described in the tetrode section is eliminated.

Continued on page 13

Continued from page 4

Other Types of Valves

Further additions of electrodes are often provided to facilitate the function of two or more valves inside one envelope. One example of this is the triode-hexode arrangement of the superheterodyne receiver. The triode section is the local oscillator while the hexode (six electrodes) is the r.f. amplifier. The two stages are combined to form the mixer, the resulting signal being passed on to the intermediate frequency amplifiers.

★ ★ ★

SEMICONDUCTOR DEVICES

The use of semiconductors dates back many years, in fact the "crystal and cat's whisker" device was probably the earliest type used. Later developments led to the "fixed" point contact diode which was found to be more reliable in radar applications during the Second World War. The outcome of post-war work led to the discovery of techniques for producing germanium junction diodes and triodes.

It is not intended to deal with point contact devices fully in this booklet due to their obsolescence. The physics of semiconductor devices has also been omitted because such information is adequately covered by many authoritative text books.

The main advantages of semiconductor diodes over thermionic diodes are:

(i) no heater power is required;
(ii) smaller physical size;
(iii) lower forward voltage drop.

The theoretical diagram of a *pn* junction is shown in Fig. 12 with typical forward and reverse biasing characteristics.

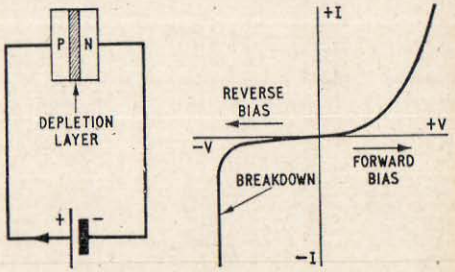


Fig. 12. Basic circuit and characteristics of a semiconductor diode

Further developments of the junction diode have produced unique devices such as the Zener diode, tunnel diode, silicon controlled rectifier, and gate controlled rectifier. Some of their characteristics are shown in Fig. 13.

INTEGRATED TRANSISTOR AMPLIFIER



FULL DETAILS ARE GIVEN HERE OF THE POWER AMPLIFIER SECTION

SIX transistors are employed in the power amplifier, the circuit of which is shown in Fig. 6. The first transistor, TR5, is connected as an emitter follower, the collector being grounded to a.c. by the 32μF capacitor C15. This mode of operation gives high current gain and zero phase shift between input and output, a good match therefore exists for practically any type of input. Stabilisation is achieved by C14 across the bias network.

The output from the emitter of the first stage is directly coupled to the high gain stage TR6. C17 assists in reducing the high frequency rising characteristic of this stage. The collector of this stage is directly coupled to the base of the phase reversing *npn* transistor TR8 and via D1 to the base of TR7.

TR7 and TR8 operate in the class B Darlington mode to increase current gain. This again has the advantage of push pull emitter follower operation. It will be noted that each stage is directly coupled throughout the amplifier; there is therefore no phase shift or frequency losses due to capacitive coupling.

SPECIFICATION

Frequency response
Substantially flat from 20c/s to 25kc/s

Sensitivity
An input of 50mV is required for full drive

Overall feedback
17dB

Output Impedance
Less than 1 ohm

H.T. Supply
28V normal, 32V maximum
50mA quiescent. 500mA for full sine wave output

Battery Operation
When powered by a 9V battery, an output of 300mW is obtainable

FORWARD BIAS

The output transistors TR9 and TR10 have a small forward bias to minimise crossover distortion. This bias is set by the voltage drop across the 1 kilohm resistors R26, R27 which are in parallel with their input. Capacitors C18, C19 are connected across these resistors and stabilise the circuit reducing the drive some 70 per cent at 30kc/s.

Transistors TR7 and TR8 are biased for the same reason by the voltage drop across the OA10 diode D1.

FUNCTION OF THE DIODE

A 70 ohm resistor could be used in place of the diode D1 to serve the same function; a resistor would not, however, give any temperature compensation and the bias would be disturbed accordingly. True thermistors could be used to compensate for the

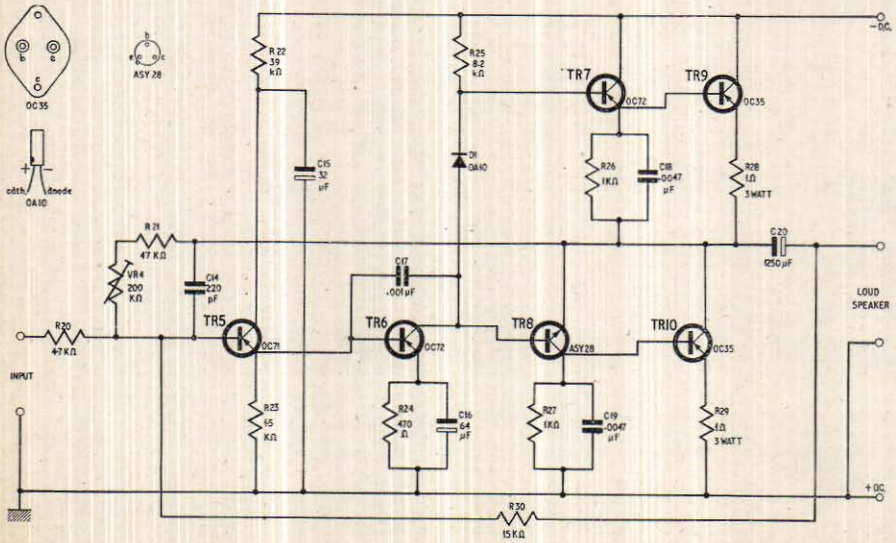


Fig. 6. Circuit diagram of the power amplifier with base details of transistors shown in the top left-hand corner of the drawing

temperature variation of the emitter base resistance, but their performance is not comparable with the OA10 diode which has characteristics similar to the germanium transistor.

Having explained the reason why the diode is used and its function in the amplifier circuit, it would be well to describe a precaution that must be observed in placing it in the circuit when constructing the amplifier.

The OA10 is a high current, low voltage germanium junction diode. It is important that no alternative diode is used in the amplifier and great care should be taken during construction that it is connected the correct way round in the circuit. The function of D1 is to assist in temperature stabilisation of the circuit and to couple the complementary pair TR9, TR10 in a correct push pull mode.

It is important that the base inputs to the driver transistors are never open circuit with respect to one another at any time. An equivalent condition arises should the OA10 diode be inadvertently reversed. If this happens the base of the driver transistor TR7 becomes more negative while the base of TR8 becomes more positive, moving towards the earth rail. The resulting large bias increase will cause the collector/junction resistance to become extremely low and the output transistors will then draw excessive current through the base in a matter of seconds resulting in collector to emitter short and the ruining of expensive transistors. (This is of course no different from connecting the grid of a thermionic valve to a 400V line.)

To enable the amplifier to be used with low-level sine wave testing, 1 ohm resistors are inserted in the emitter circuits of the output transistors, giving reverse bias and further aid to linearity.

The quiescent current is some 50mA rising to 500mA for full sine wave output.

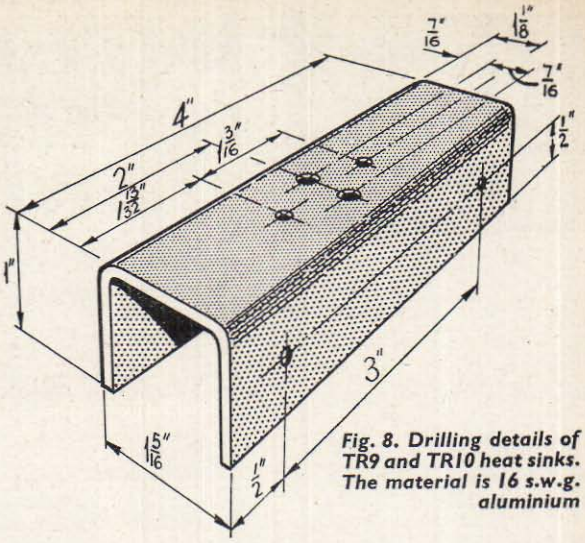


Fig. 8. Drilling details of TR9 and TR10 heat sinks. The material is 16 s.w.g. aluminium


The h.t. is normally 28 volts with 32 volts maximum. The amplifier will perform quite satisfactorily at a reduced output of 300mW when supplied by a 9V battery.

Overall feedback of some 17dB is applied via the 15 kilohm resistor R30 from the amplifier output to the base of TR5.

CONSTRUCTION

Construction is straightforward and follows similar lines to that of the pre-amplifier, as described in last month's article. If larger components than those shown in the layout diagram (Fig. 7) are used, the

Fig. 7. Layout of components and wiring

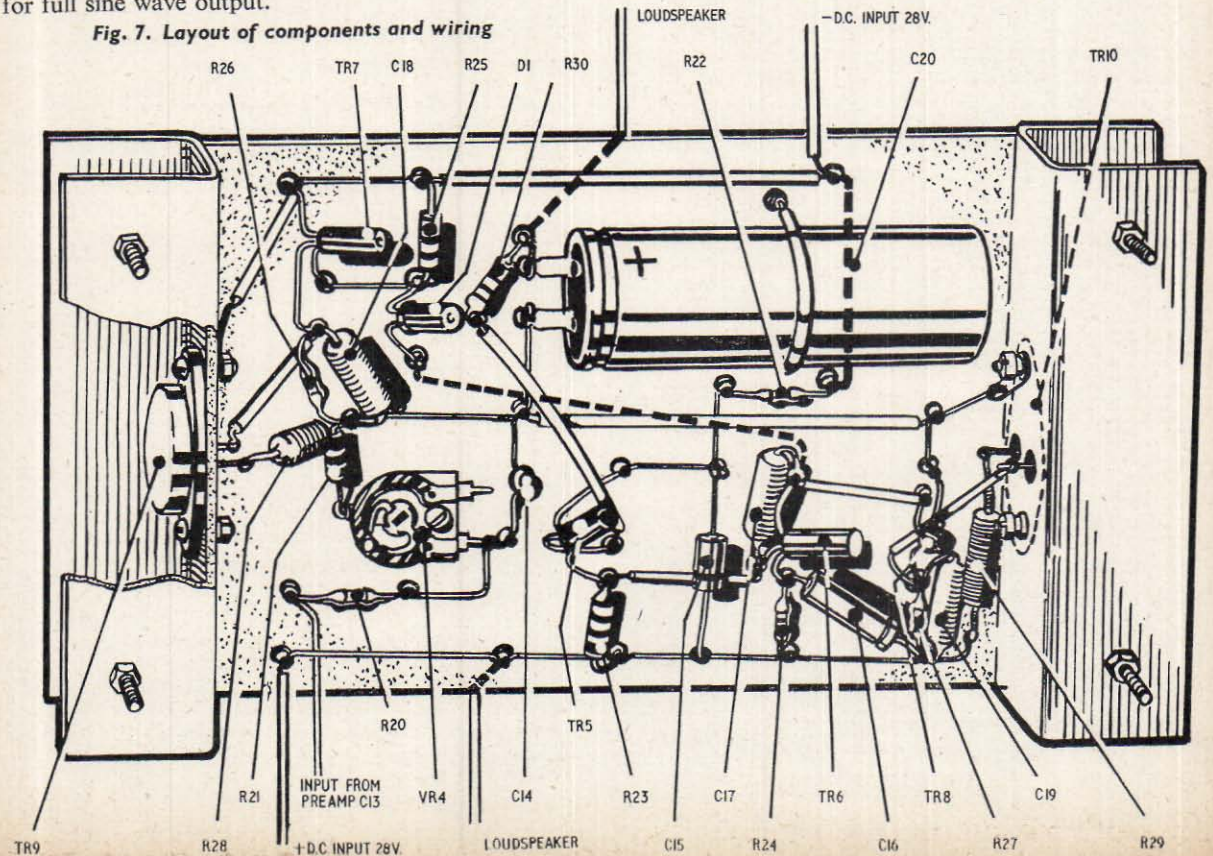

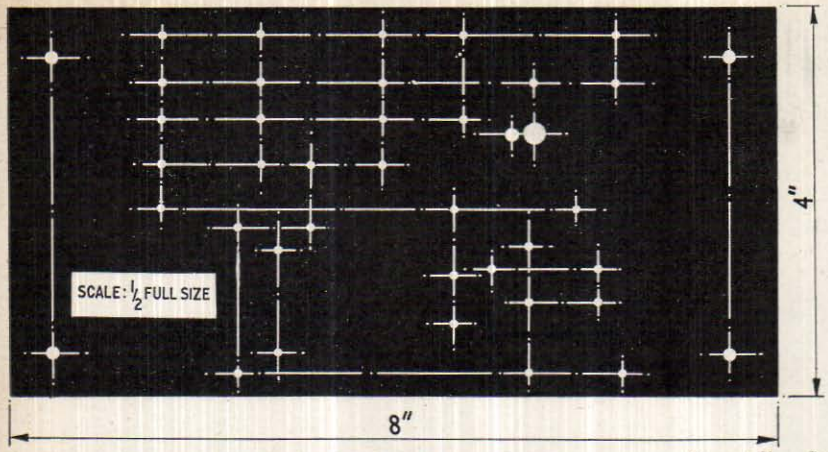


Fig. 9. Drilling details of the plastics board

circuit board (Fig. 9) may have to be enlarged accordingly, but providing the general layout arrangement is adhered to no difficulties should arise on this account.

There is no hum level to worry about and the whole unit is extremely stable.

The construction of the heat sinks is quite simple if the following procedure is adopted. Obtain a piece of hard wood 1½in square and 4in in length. From a sheet of 16 s.w.g. aluminium cut two pieces each measuring 4½in × 4in. Hold each piece in a vice and bend it round the mandrel to form a C channel heat sink. See Fig. 8.

In the centre section of each heat sink drill the holes for the power transistor fixing screws and the feed-through holes for the base and emitter connections. In the corners of each heat sink drill four holes for fixing the assembly boards into their final positions.

Special care must be observed when connecting the ASY28 *npn* transistor TR8. The collector looks towards the positive rail and the emitter towards the negative side of the output electrolytic C20. This is, of course, opposite to the connection of the OC72 *pnp* transistor TR7.

SETTING UP

When the power amplifier panel has been completed, check the connections carefully. A loudspeaker must be connected to the output terminals before power is applied to the amplifier. The output impedance of the amplifier is less than 1 ohm and ensures good loudspeaker damping. Any speaker having an impedance of from 3 to 15 ohms can be used.

If you have any doubts regarding the speaker impedance you propose using, remember a very easy way of finding the impedance is to measure the d.c. resistance and multiply this by $\sqrt{2}$. The power supply can be derived from either a battery or from a mains power unit giving a d.c. output of 32V.

The improved loudspeaker damping and absence of an output transformer (which is both costly and inefficient) are quite definite steps in the direction of true quality reproduction. Class B amplification has the advantage of low quiescent current and high efficiency at full output, the average current consumption on music being about one-third of that on maximum sine wave output.

BIAS ADJUSTMENT

In principle, the two output transistors should be biased to cut off; however, strict adherence to this condition results in crossover distortion which is most unpleasant to the listener. This serious disadvantage which takes the form of a thin reedy kind of noise, which at low input gives the impression of a displaced loudspeaker cone, can be overcome by applying a small forward bias to each transistor, as stated in the earlier description of the transistor functions stage by stage.

Any slight distortion discernable can be eliminated by careful adjustment of the variable voltage level control VR4 between the base of TR5 and emitter collector junction rail to TR9, TR10. The ease of this adjustment is only apparent when final setting up is taking place at a low volume of a piano recording of, say, Beethoven's "Moonlight Sonata". Once the correct position is set, no further adjustment is necessary.

CAUTIONARY NOTE

Do not attempt to use the amplifier at any time without a speaker or equivalent d.c. resistive load connected between the output capacitor C20 and earth. Always remove the d.c. supply before disconnecting the speaker: very large transient currents are built up in the large electrolytic capacitor and, if undamped by the low resistance of the speaker, will surge through the output transistors and damage them.

COMPONENTS . . .

Resistors

R20	4·7kΩ	R25	8·2kΩ
R21	47kΩ	R26	1kΩ
R22	39kΩ	R27	1kΩ
R23	1·5kΩ	R28	1Ω 3W
R24	470Ω	R29	1Ω 3W
		R30	15kΩ

All ⅛W, cracked carbon, high stability 5%, unless otherwise indicated

Potentiometers

VR4 200kΩ carbon preset (skeleton type)

Capacitors

C14	220pF ceramic	C17	1,000pF polyester
C15	32μF 10V	C18	4,700pF polyester
C16	64μF 10V	C19	4,700pF polyester
		C20	1,250μF 25V

All electrolytics, unless otherwise indicated

Transistors

TR5	OC71	TR8	ASY28
TR6	OC72	TR9	OC35
TR7	OC72	TR10	OC35


Diode

D1 OA10

The next and concluding article will describe a simple mains power supply unit giving 28V from a standard battery-charger transformer. This article will also include some advice on the stereophonic arrangements for those who are interested in stereo reproduction and do not mind the cost of duplicating the amplifier and pre-amplifier

ELECTRONORAMA

HIGHLIGHTS FROM THE CONTEMPORARY SCENE

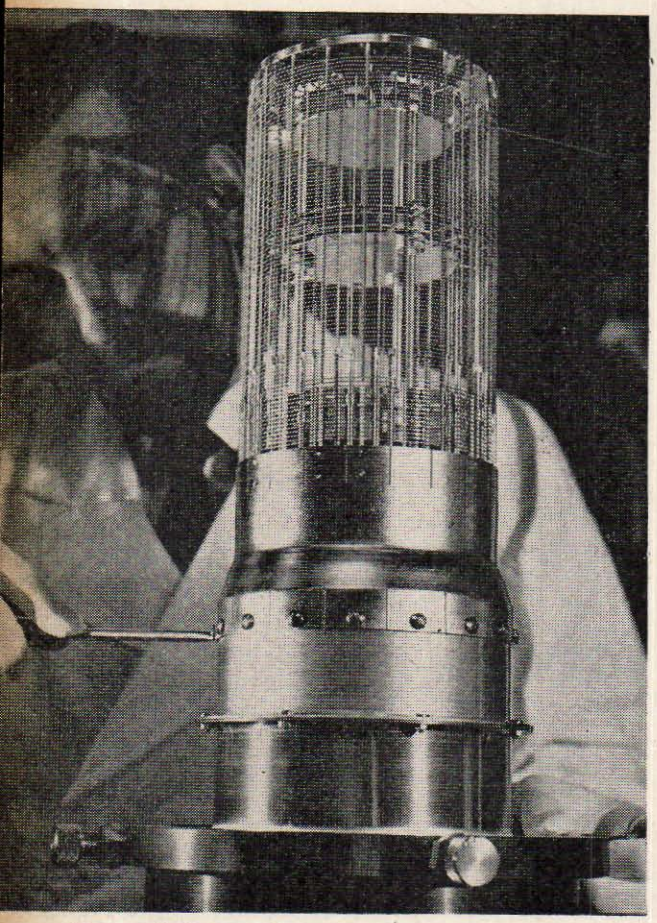

Valves Still Used Here!

THIS gigantic device is a new 200kW power transmitting triode, shown by the English Electric Valve Company at the recent British Exhibition in Sydney. The picture shows the structure of the grid and filament.

"Early Bird" with Travelling Waves

THE Post Office is installing water-cooled C-band travelling-wave tube amplifiers in the world's first commercial communications satellite system—"Early Bird". The tubes will give an operating power output of 10kW at 6,301Mc/s with a tuning range of the r.f. structure of 225 Mc/s and small-signal bandwidth better than 30Mc/s.

The satellite will be launched into a "stationary" position 22,000 miles above the Atlantic to provide a 24-hour link between North America and Europe. It will be able to transmit live television programmes of provide up to 240 two-way telephone circuits.

Olympic Relay

SYNCOM III satellite, which was used as a vital link for the transmission of television pictures of the 1964 Olympic Games, held in Tokyo in October, to Point Mugu in California, was not specifically designed for television transmission. The r.f. bandwidth of the satellite circuit, 13Mc/s, is insufficient to provide adequate bandwidth for a television signal with the high deviation f.m. system used. The video bandwidth of about 2·7Mc/s cannot be increased by reducing the deviation without degrading the signal/noise ratio. To overcome this problem a helical scan tape recorder was used in Tokyo.


Sound programmes were sent from Tokyo to Hawaii via the recently laid trans-Pacific telephone cable and thence to Vancouver by means of the Commonwealth Pacific telephone cable (COMPAC). Microwave radio links carried the signal across Canada to the Canadian transatlantic telephone cable (CANTAT) for linking to the British trunk telephone system in Scotland.


International Conference on Lasers

NEW possibilities in the fields of measurement and communication are being found by using lasers. The Conference on Lasers and their Applications, held at the I.E.E. in London in conjunction with the I.E.R.E. and the American I.E.E.E. in September, revealed some interesting advances in laser techniques.

The laser produces a very intense light beam with many properties, similar to radio waves, which ordinary light does not possess. Laser transmissions can be focused into very narrow beams enabling very long range and a high degree of accuracy to be obtained in rangefinding and communication applications. Laser beams can also be used for precision welding (see last month's issue) and cutting applications. It is envisaged that, due to the very high frequency which lasers provide, there is a possibility for virtually unlimited capacity for telephone and television transmissions.

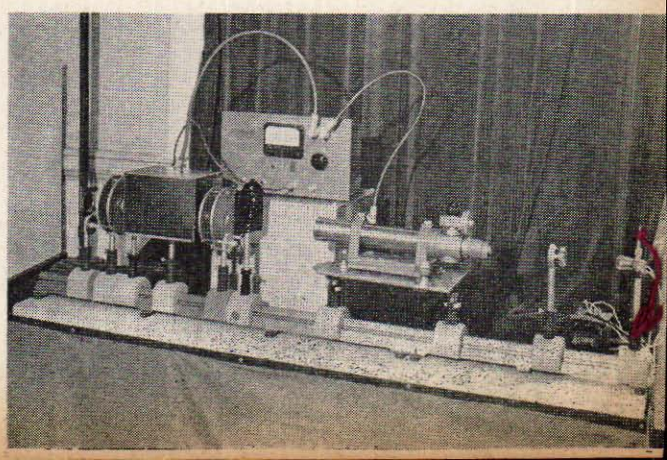The picture shows one application of the ruby laser exhibited by the University of Southampton as a bleaching agent for blue dye. When the laser is "pumped", oscillation first occurs with the dye absorbing. The ruby rod then sees the full reflectivity of the mirrors and Q-switched operation ensues.



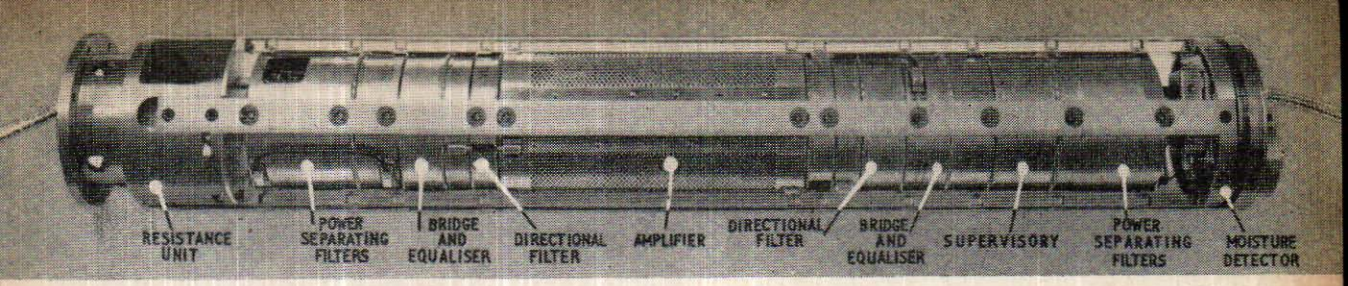


Denmark on the Dial!

THE FIRST high capacity telephone cable between Britain and Denmark was brought into service on 1 October to increase the number of telephone circuits between Britain and Germany, Denmark, and Holland. The cable, which is laid between Winterton in Norfolk and Esbjerg, will provide 120 high quality speech circuits.

This is the second of five cables planned to be laid across the North Sea by 1966. One of two to Germany was opened earlier this year. Two cables will be laid to improve the facilities to Holland. Twenty-four submerged repeaters are spaced evenly along the 300 nautical miles of cable to boost the speech signals. One of these is shown above giving a layout of the various units.

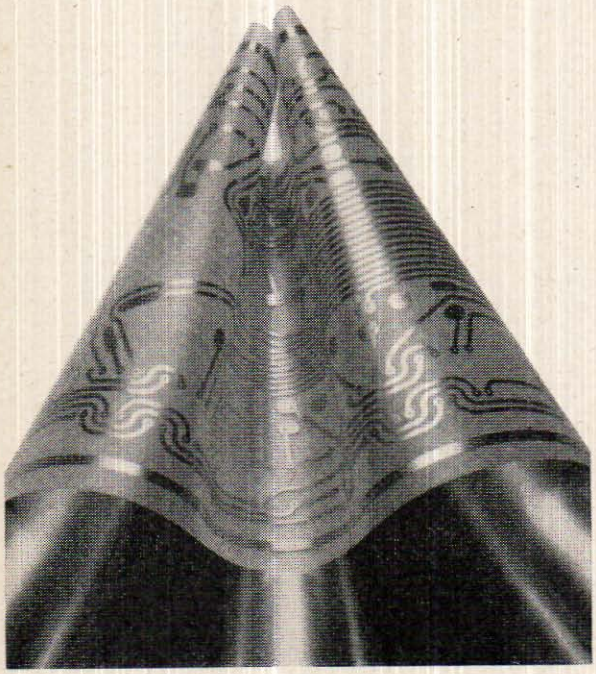International subscriber trunk dialling will be introduced from Britain to Denmark in the spring.



The Shape of Circuits to Come?


A NEW grade of copper-clad Bakelite laminated sheet has been developed for the preparation of printed circuits. The new grade is made by bonding copper foil to polyester film and may be coiled and folded. It could enable the size of an assembly to be considerably reduced. Processing is achieved in the normal way by etching or printing techniques.


It is expected to find useful applications in automobile wiring, computers, telephone and switchboard wiring, radio and domestic appliances.

Electronics "See" Ten-millionth of an Inch

A RESEARCH chemist in New York has been using an electron microscope, which is capable of seeing particles one ten-millionth of an inch in size, to study the crystal structure of silver halides during chemical reaction.

The enlarged electron micrograph in the picture below shows what is happening to silver bromide crystals in a solution of potassium iodide as seen by the microscope at 30,000 diameters. The crystals are being dissolved by the potassium iodide as silver iodide (small crystals) is formed.

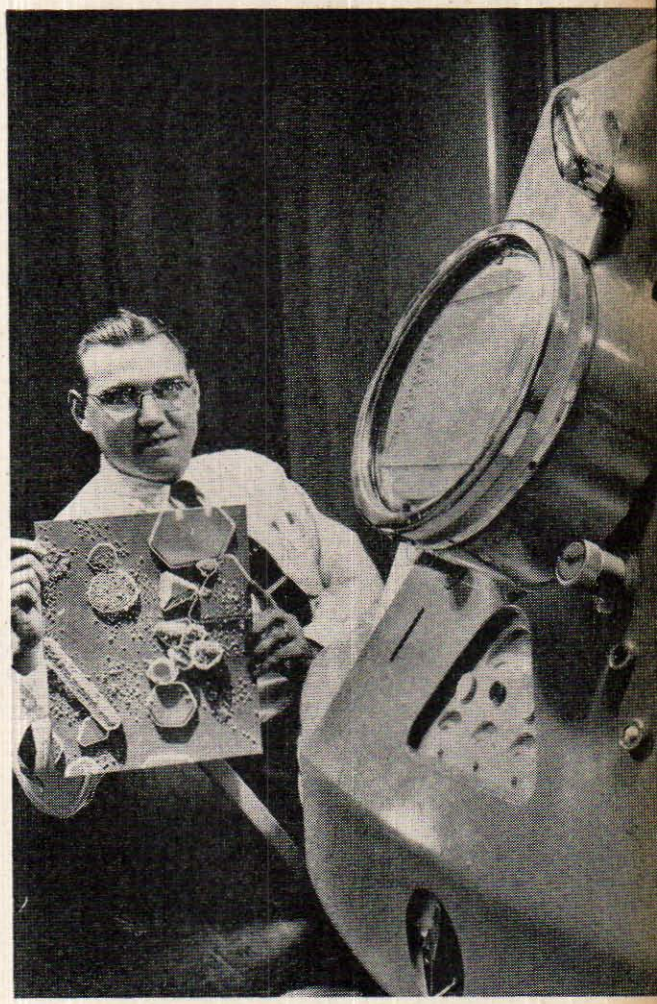

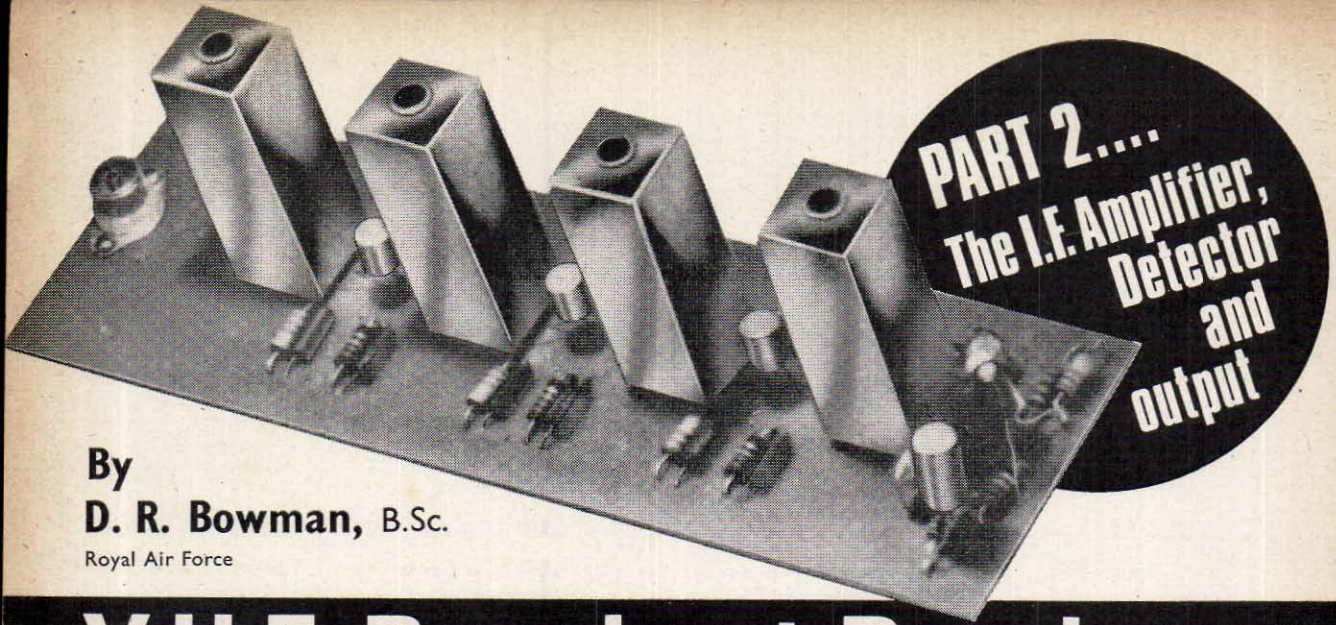

PART 2.... The I.F. Amplifier, Detector and output

By
D. R. Bowman, B.Sc.
Royal Air Force

V.H.F. Broadcast Receiver

THREE stages of i.f. amplification (at 10·7Mc/s) are employed, and these are followed by a ratio detector.

It is worth mentioning at this point that although some hi fi people would regard this with some surprise, the decision to use a ratio detector is backed by sound principles. Eyebrows may be lowered. The ratio detector is capable of just as linear a response as the Foster-Seeley or the earlier Rond-Travis discriminators, and although the Foster-Seeley has been the "standard" for valve users for a good many years, nowadays more and more designers are using the ratio detector.

For transistor circuits the Foster-Seeley has notable disadvantages unless a relatively low i.f. is used, and the bandwidth needed has to be obtained by a much more critical i.f. amplifier set-up.

The theoretical man will appreciate that the mathematics of either type of discriminator show just the same opportunities for distortion, and that this can be minimised by using an i.f. amplifier whose response curve is "gaussian"—that is, bell-shaped—giving the most linear phase change through resonance point. Any reasonably advanced text book on electric circuit analysis may be consulted on this point, for example M.I.T. Radiation Laboratory Series Vol. 18—Vacuum Tube Amplifier (Valley & Wallman; McGraw-Hill Book Co.).

What is very important is to see that the i.f. amplifier and detector overall response is a smooth curve, rising steadily (though rapidly) to a peak at resonance and dropping off thereafter in an equally steady and rapid way. Any bumps or spikes on this curve are reflected in irregularities of phase-change, and consequent kinks in the phase characteristic. Fig. 13 illustrates a good and a bad type of response curve, with the appropriate phase characteristic.

To ensure that the i.f. amplifier has the proper response fixed neutralisation has been abandoned, and variable neutralising capacitors are used instead, TC3, 4, and 5. These have to be adjusted, when the i.f. amplifier has been built, to get the proper response curve.

CRITICAL WINDINGS

The construction of the i.f. amplifier transformers is also somewhat critical, especially as regards the gauge of wire used and the spacing between primary and secondary. (Refer to data and Fig. 8 in last month's article.) Coupling has been arranged to be a little less than "critical", except in the detector stage where joint critical coupling is employed.

If any difficulty exists in deciding the spacing, one should err on the generous side, rather than bring the windings even fractionally too close. Also the wire must be wound close, that is, with the adjacent turns touching. Any systematic gap will increase the winding length unacceptably. This is not usually a bother when coils are wound by hand, but if a winder is used the coils should be carefully inspected after construction.

Correct spacing is best obtained by cutting a strip of drawing paper the exact width required, and with it winding a spacer centrally on the former. The windings can then be started from the centre, hard up against the spacer; the latter may be removed later, when the fixing cement is hard and dry, but there is no real need to do this.

With regard to the detector transformer T7, particular care is necessary here, since a number of associated components have to be fitted inside the screening can in addition to the actual transformer assembly. Provided the smallest size of components is used, the "long" can specified will accommodate all items shown inside the dotted line which represents the can in Fig. 11. Details of the assembly of these components on the coil former are given in Fig. 12.

THE ETCHED CIRCUIT BOARD

The etched circuit is set out on a piece of copper clad laminate measuring 2¾in by 8in, as shown in Fig. 10.

The conductors are relatively few, and may be drawn direct on to the laminate surface with an acid resist. Thinner cellulose paint may be used for this quite successfully, but the vapour is dangerous to inhale and the process should be done in the open—or at the least, in an extremely well-ventilated room.

The best resist the writer has discovered is a proprietary french polish type of fluid known and marketed as "Glitseal", which is obtainable from "do-it-yourself" shops. This has to be diluted with about one-third of its volume of methylated spirit, as it is too thick for accurate small work, and for visibility it is dyed with a few crystals of crystal violet, obtainable from any dispensing chemist.

The conductors may be drawn with this mixture, using a ruling pen preferably as a small brush cannot readily be set against a straight edge. It should be noted that the conductors N, P, Q, and R are the earthing strips for the i.f. transformer cans, and conductor S is the earth point for the coaxial socket output to the i.f. strip. The conductor A is the common "earth" connection, and is best made quite wide as several component leads have to be soldered to it.

When the "conductors" are dry and hard, a careful check should be made to see that all is well. Then the etching process may be carried out, using 30 per cent ferric chloride solution in the usual way—see last month's article.

The theoretical circuit of the i.f. amplifier, detector, and pre-amplifier is given in Fig. 11, and during the wiring-up procedure this diagram should be consulted frequently to ensure that no errors occur. When wiring is complete the circuit board should be given a coating of varnish—the "Glitseal" is excellent for this purpose—to protect the copper laminate against corrosion.

ALIGNMENT OF THE I.F. STAGES

To set up the i.f. amplifier the following method should be followed. This will enable a stable and well-tuned amplifier to be achieved, which is then trimmed for the correct response curve.

A multimeter is needed, and a signal generator capable of supplying a signal of 10·7Mc/s, amplitude modulated or unmodulated at will. The leads from the multimeter should be decoupled at the ends by means of 5 kilohm resistors, and these soldered lightly to tags 3 and 11 (across the stabilising capacitor of the ratio detector). The leads must be arranged to lie well away from the i.f. stages.

Set the multimeter to the 50μA or 100μA range, and the signal generator to high output.

Set the neutralising capacitors TC3, 4, and 5 to minimum. Disconnect the two 100Ω decoupling resistors R17, R21 from the B— line; this leaves only the ratio detector driver transistor and the pre-amplifier transistor in operation. The battery supply is now connected.

Most likely at this stage the microammeter will show a reading, indicating the stage is oscillating. Rotate the adjustment of TC5. Two positions will be found at which the stage breaks into oscillation, with a space between when no oscillations occur. Obtain the centre setting. Switch on the signal generator and bring the "live" lead near the base of TR6. Rotate both cores of T7 until maximum deflection of the meter is obtained, reducing the signal generator output if necessary. It may well happen that as the transformer is brought into line TC5 will require re-adjustment, but there is no difficulty at all in tuning up this stage and neutralising it.


Next tune the secondary of T5 until maximum meter deflection is reached, once again adjusting TC5 as necessary to recover stability. No contact should be necessary between the signal generator lead and the base of TR6, but if the signal generator output is small the lead may be connected via a small capacitor to the primary of T6 at the collector terminal of TR5.

Next transfer the signal generator lead to the base of TR5, again without physical contact, and re-tune the transformer T6. As the transistor for this stage is not working yet, a small reading only will be obtained unless the signal generator output is increased. Connect up the decoupling resistor of this stage (R21), to bring the stage into operation. Again, oscillation will probably result, and in the absence of an input signal a meter reading will be obtained. Adjust TC4 to stabilise the circuit, and tune the secondary of T5.

Couple in R17, and repeat the above adjustments with T4, T5, and TC3. At this stage it may well be found that *very small* adjustments of TC4 and TC5 are required to retain overall stability. These will amount only to a fraction of a turn—10 degrees or so of adjustment is usually enough.

Now that the i.f. amplifier is stable and roughly tuned the signal generator output lead should be plugged into the coaxial socket SK2, and the output reduced to a few microamps r.f. Re-tune the entire receiver for maximum output at the meter. It should

Fig. 9. A top view of the i.f. printed board showing component layout

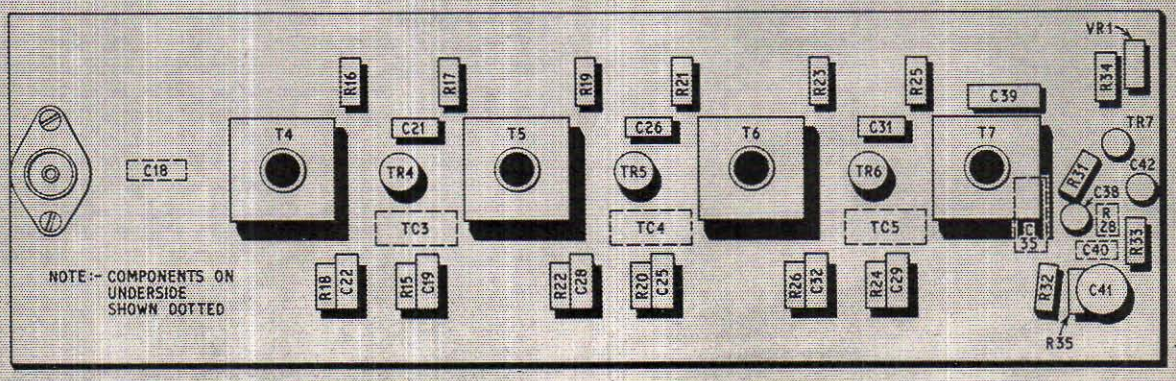

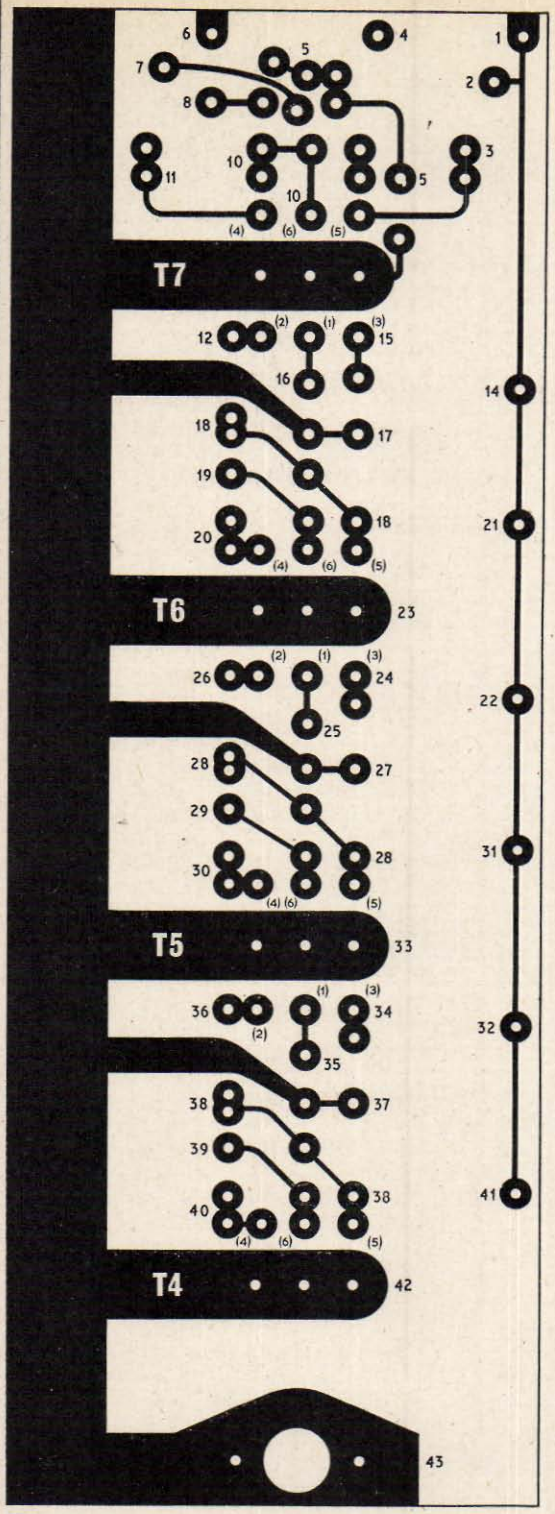


Fig. 10. Printed board. The small numerals refer to similarly numbered points on the circuit. The small numbers in brackets are the pin numbers of the coils. See Fig. 11. The common earthing strip on the left-hand side is referred to as "A" in the text

be found that the stages tune quite independently. If not, neutralisation is not exact. *Very slight* adjustments of all three neutralising capacitors are now needed, with re-tuning of the transformers as necessary, until the transformers tune independently, and a change in the setting of one core does not affect the timing of the next stage.

VISUAL ALIGNMENT

If a wobbulator (i.e. frequency modulated oscillator) and an oscilloscope are available it is possible to align for the best response curve.

For this, deviation is set to the maximum; and the stabilising capacitor C38 temporarily disconnected from points 3 and 11, and the oscilloscope connected to these points. If necessary, one of these points may be earthed temporarily. Extremely slight adjustment of transformer tuning and of the neutralising capacitors will permit a smoothly-rounded curve to be obtained.

THE DETECTOR

The next step is to adjust the ratio detector. Re-attach the stabilising capacitor C38 between points 3 and 11, and connect a pair of headphones (or audio amplifier) to detect the modulated output. Connect the signal generator output to the coaxial input socket SK2. Switch on the modulation in the signal generator. Maximum sound output will not be obtained, but there should be some. Rotate the core of the secondary of the discriminator transformer T7 until *zero output* is obtained. This will be quite sharp.

Next, if a wobbulator is available set to 25kc/s deviation and connect its r.f. output to the input socket and the oscilloscope between points 5 and earth. While listening to the output, tune the wobbulator gently so that its output frequency slowly reaches the intermediate frequency to which the i.f. amplifier is tuned.

As the wobbulator comes into tune, the harsh-sounding third harmonic should disappear completely, leaving a pure tone. Meanwhile the trace should show a straight line inclined to the X axis. Increasing now the deviation to a large extent will reveal all or part of the phase response curve. If all has gone well, the trace should closely resemble Fig. 9a. If not, very slight further adjustments may be made until the perfect characteristic is approached.

If exceptionally high fidelity is not the aim, the wobbulator test may be omitted, the final check being to tune the signal generator gently through the i.f. with the meter connected across the stabilising capacitor C38 as before, and the amplitude modulation switched on. The output should be monitored aurally.

As resonance is approached the meter reading should rise steadily, in the same way as the amplitude characteristic of Fig. 9a, as the sound output increases. As resonance is approached the sound should die away to zero as the meter approaches maximum. A check should be made that the peaks of the most intense sound are equally spaced about the zero point. Also, by connecting a meter between point 10 or 13 and chassis, check that a zero reading is obtained at the zero sound output point and that equal positive and negative readings are obtained at equal frequencies off resonance.

The conditions necessary for this are that the ratio detector transformer should be absolutely symmetrical, and that it should be matched each side. The 470 ohm and 6·8 kilohm load resistors R29, R30, R31, and R32

should therefore be matched as exactly as possible from stock; for "hi fi" results, match should be to 1 per cent or better. In such a case a matched pair of OA79 diodes is useful, and if they differ (as supplied) by more than 10 per cent it may be advisable to increase the 470 ohm resistors to 680 ohms—also carefully matched.

The two 500pF capacitors C36 and C37 should also be close in value, but this is less important. It is better to get a close match between the load resistors than to be very precise about the actual numerical value.

OUTPUT ARRANGEMENTS

The pre-amplifier stage TR7 is arranged for pre-set output. If this receiver is to be used in association with a sensitive power amplifier (such as the 5W Integrated Amplifier currently appearing in our pages) it may be feasible to dispense with the gain of this stage and instead employ the transistor TR7 as an emitter-follower. This is recommended for the highest quality reproduction.

To effect this change, remove VR1 and connect the collector of TR7 direct to the B— rail. Change the value of R35 to 1·8 kilohm, and remove C41. Output at a few ohms impedance is then taken from the emitter of TR7.

If a coupling capacitor is to be used between this and the next audio stage, a 500μF capacitor should be used. It will be preferable however to use direct coupling into the base of the next stage if d.c. conditions can be achieved correctly.

I.F. INTERFERENCE

The author has found that in certain locations interference can be obtained from transmissions on the intermediate frequency of 10·7Mc/s if any r.f. signal finds its way into the i.f. amplifier. Provided the interfering signal is not so strong as to cause cross-modulation with the desired signal, direct r.f. pick-up can be avoided by good screening and by adequate selectivity in the r.f. stages.

However, in this receiver unit construction is employed, and connecting cables may cause a certain amount of pick-up at i.f.; added to which is the possibility of direct pick-up on the circuit wiring of the i.f. amplifier, unless an earthed screening box for the whole unit is made. Usually, however, it is possible to find a quiet spot within a few hundred kc/s of the nominal i.f., and this is the recommended procedure if interference is experienced.

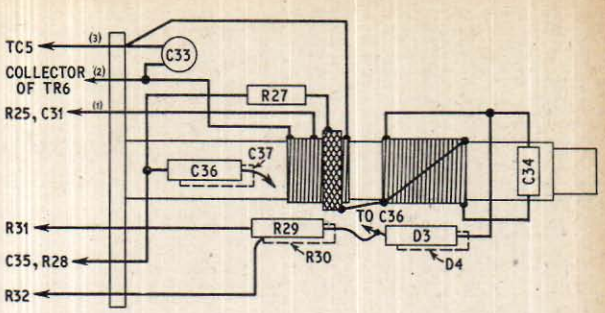


Fig. 12. Wiring of ratio detector circuit. D4, R30, C37 are behind D3, R29, C36, and are similarly wired. When assembled all components should be wrapped in a layer of thin polythene to ensure insulation from the can. For coil connections see Fig. 8 in last month's article

ALIGNMENT OF THE R.F. UNIT


Having roughly ascertained that the oscillator is working in the correct frequency band—in the way previously mentioned—all that remains is to effect a careful alignment using a meter. Either phones or a small loudspeaker may be connected between C42 and B+, or an a.f. amplifier may be attached.

A test oscillator or signal generator is required capable of giving a modulated output (preferably f.m.) over the range 85–100Mc/s. This is set to 87·5Mc/s, and connected to the aerial socket of the receiver; moderate output will be required, say 10mV. The volume control should be adjusted so that the receiver does not emit too much noise. Set the ganged capacitors to maximum (full interleaved) and rotate the core of the oscillator inductor (L2) until a signal is heard. If too loud reduce the signal generator output. Tune the oscillator for peak signal by means of the core. If the signal can be heard at two settings of the core, select the position corresponding to the smaller value of inductance.

Set the signal generator to 100Mc/s and the ganged capacitor to minimum. Adjust the oscillator trimming capacitance until maximum signal is heard. Next set the gang to the half-way position, and tune the signal generator for maximum output in the receiver. Rotate the core of the aerial coupling inductor and of the r.f. interstage transformer for maximum volume.

During the above procedure it will be found that when exact tuning with the signal generator is achieved the modulation disappears, unless the signal generator

Fig. 11. Circuit diagram of the i.f. unit

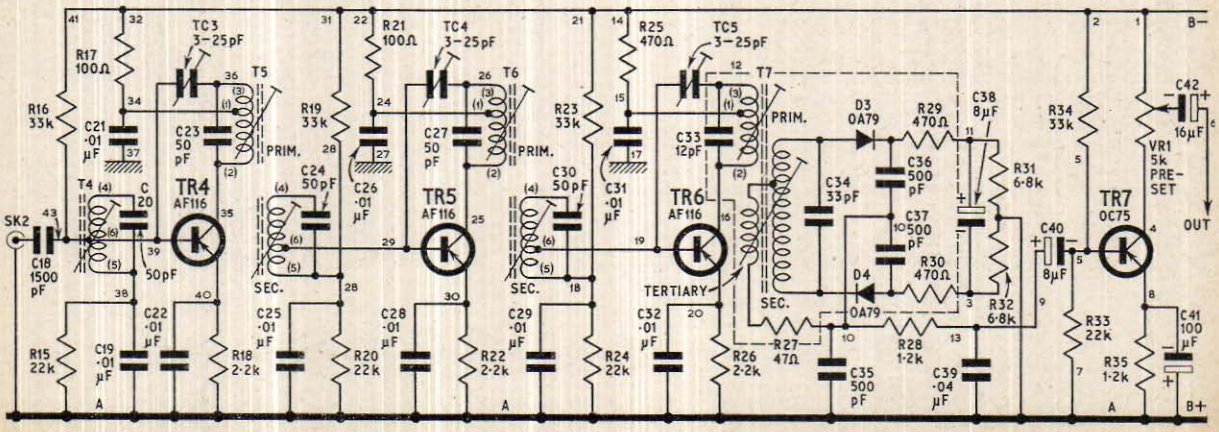

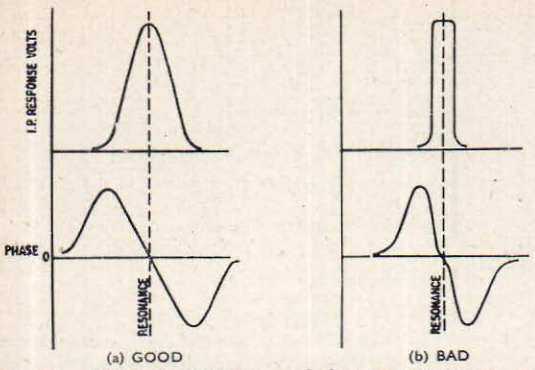


Fig. 13. The i.f. amplifier and detector response curve showing good (a) and bad (b) characteristics

is frequency-modulated. However, a slight mistuning one way or the other will bring in the modulation sufficiently well for the output to be estimated. The following procedure, however, should be carried out with an f.m. signal, or failing this with an extremely small input. The latter can be achieved by attaching the aerial to the receiver—using the signal generator as a low-power transmitter. The signals when received should be barely above the noise level, so that the limiting effect of the ratio detector is at its minimum. Alternatively, the broadcast stations themselves may be used for alignment, but this method is not as accurate and may take more time.

The procedure given in the above paragraphs should now be repeated, except that the aerial π-coupling should not be re-adjusted. Further repetition will give more accurate alignment, but it is seldom necessary to perform the operation more than three times in all.

If a meter is used for the alignment, it should be connected across the capacitor C38. The voltage developed, with an aerial input of 10μV, will be about 1V, but the response is highly non-linear and when the receiver is aligned the BBC transmissions may not give much more than this. Provided the signal generator output is kept as low as will give a reasonable meter deflection there should be no difficulty in achieving correct alignment. ★

COMPONENTS . . .

*Items marked * are not required if an emitter-follower output stage is employed.*

Resistors

R15	15kΩ	R22	2·2kΩ	R29	470Ω
R16	22kΩ	R23	22kΩ	R30	470Ω
R17	100Ω	R24	15kΩ	R31	6·8kΩ
R18	2·2kΩ	R25	470Ω	R32	6·8kΩ
R19	22kΩ	R26	2·2kΩ	R33	22kΩ
R20	15kΩ	R27	47Ω	R34	33kΩ
R21	100Ω	R28	1·2kΩ	*R35	1·2kΩ
	All ¼W carbon			R35	1·8kΩ

*VR1 5kΩ preset carbon potentiometer

Capacitors

C18	1,500pF	C30	50pF
C19	0·01μF paper	C31	0·01μF paper
C20	50pF	C32	0·01μF paper
C21	0·01μF paper	C33	12pF
C22	0·01μF paper	C34	33pF
C23	50pF	C35	500pF
C24	50pF	C36	500pF
C25	0·01μF paper	C37	500pF
C26	0·01μF paper	C38	8μF elect. 15V
C27	50pF	C39	0·04μF paper
C28	0·01μF paper	C40	8μF elect. 15V
C29	0·01μF paper	*C41	100μF elect. 15V

All silver mica or high quality ceramic, unless otherwise indicated

TC3, TC4, TC5 3–25pF

Transformers

T4, T5, T6 I.F. transformers—see text
T7 Detector transformer—see text

Transistors

TR4	AF116	TR6	AF116
TR5	AF116	TR7	OC75

Diodes

D3	OA79	D4	OA79

Miscellaneous

SK2 coaxial socket

OFFICE WORK MADE EASY . . .

ELECTRONICS is playing an important part in automation of office methods and it was evident from the Business Efficiency Exhibition, held at Olympia on 5–14 October, that the modern business establishment is finding new ways of speeding up office work and reducing the risk of error.

Among new developments there was the new electronic calculator, on show for the first time by Friden, which displays four rows of numbers and answers, including the decimal point and function signs, on a small c.r.t.

The decimal point can be positioned to give 0, 2, 5, 7, or 11 decimal place working, and any number of calculations can be made instantaneously by operating a simple 10-key keyboard.

The emphasis on quick and simple operation of dictating machines has been further enhanced by automatic tape threading and coupling to the take-up spool by the operation of a simple lever. The operator of one particular model, made by Philips, need not and indeed cannot touch the tape himself once the cassette is on the machine.

Another new dictating machine, developed by Grundig, uses foil, instead of the more conventional oxide coated plastic tape.

This unique museum piece, thought to be the earliest idea of an acoustically operated chain driven dictating machine, was on the Aga stand at the B.E.E. Let us hope it does not cause redundancy among shorthand typists!




RADIOACTIVITY experiments

Some Practical Applications of the Geiger-Muller ratemeter are described by

J. F. ROWLES

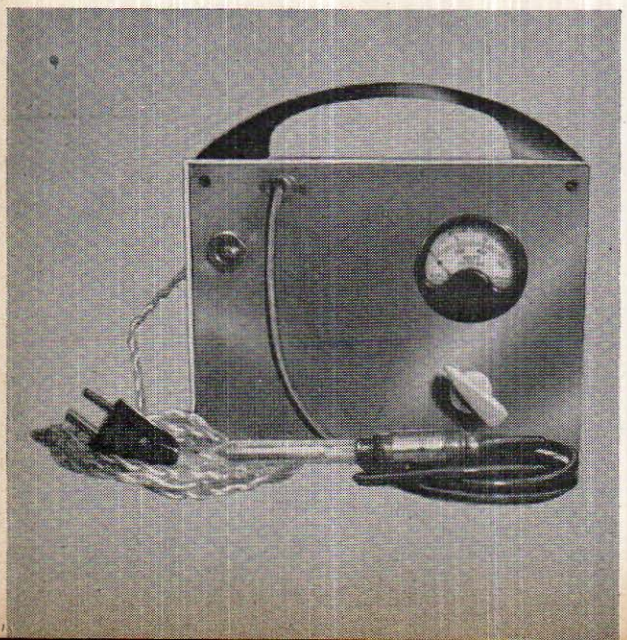These simple experiments can be performed quite safely by any amateur interested in investigating the nature of radioactivity.



LAST month instructions were given for the construction of a simple Geiger-Muller ratemeter. In this article it is proposed to describe a series of basic experiments that will give the user of the ratemeter an introduction to the nature of radioactivity.

Before beginning, it would probably assist if a few basic facts concerning the atomic particles emitted in radioactivity were mentioned. There are many particles that are emitted or can be emitted by an atom under different conditions. Here we are only concerned with natural radioactivity and will only consider *alpha*, *beta* and *gamma* radiation.

ALPHA PARTICLES

Alpha particles have the following properties:

Cause fluorescence; blacken photographic emulsions; produce ionisation in gases. They are easily absorbed by matter; deflected by magnetic and electric fields; and are emitted with large velocities.

The alpha particle has been shown in fact to be a helium nucleus,

$_2He^4$ (*a positively charged ion*)

BETA PARTICLES

Beta particles have the following properties:

Cause fluorescence, though not as great as alpha particles; blacken photographic emulsions; cause ionisation, but to a lesser extent than alphas. They have much greater penetration than alphas; are deflected by magnetic and electric fields; and have extremely high velocities.

Beta particles, in fact, consist of electrons moving with extremely high velocities. *They carry a negative charge.*

GAMMA RAYS

Gamma rays were found to have the same properties as X-rays:

Unaffected by electric or magnetic fields; travel with the velocity of light; cause fluorescence; blacken photographic plates; cause a small amount of ionisation. They very easily penetrate matter; can be diffracted; cause interference; and can eject electrons from material.

The gamma rays are electromagnetic waves of shorter wavelength than X-rays. The wavelength of the rays emitted depends on the emitting material.

RANDOMNESS IN RADIOACTIVE DECAY

The randomness of radioactive decay is very easily demonstrated using the ratemeter and a radioactive source such as the luminous face of a clock or watch.

Set up the ratemeter with the luminous dial near to the G-M tube. It will be noted that the ratemeter needle does not give a constant reading but fluctuates to a certain extent, showing that the atoms of the source are not emitting at a constant rate, their emission being quite random.

INVERSE SQUARE LAW OF GAMMA RADIATION

Like light radiation, gamma radiation obeys the inverse square law. This states that the intensity of radiation observed is inversely proportional to the square of the distance from the source.

To verify this is simple, all that is needed is a gamma source and the ratemeter. A suitable gamma source

IMPORTANT NOTICE

R1 and R2 should be 2·7MΩ and *not* 2·7kΩ as given in last month's article—pages 30 and 32.

is radium shielded by thin aluminium sheet to stop the unwanted beta and alpha rays. A luminous clock or watch face can be used, but it is better to have a more concentrated source such as some of the luminous paint used by watchmakers. This paint can be purchased from a wholesaler in such goods, and is packaged in a small test tube (of the type known as semi-micro test tubes).

The method of testing the inverse square law is to take the count rate at varying distances from the source and to plot a graph of 1/distance squared against the count rate. (See Fig. 1.)

Alternatively, a logarithmic graph can be plotted of log distance against log count rate. Here the relationship is verified more exactly as the assumption of the inverse square law applying is not assumed but the power to which the distance has to be raised to satisfy the equation is arrived at from the graph. (See Fig. 2.)

A typical set of results will now be treated to give the graphs mentioned:

Distance	$\frac{1}{(Distance)^2}$	*Count Rate*	*Log Distance*	*Log Count Rate*
2	0·25	100	0·3	2·0
3	0·1	45	0·48	1·65
4	0·063	25	0·6	1·4
5	0·04	15	0·7	1·178
6	0·03	10	0·78	1·0
7	0·02	8	0·85	0·9
8	0·0156	6	0·9	0·78

Mathematically, the inverse square law is expressed as

$$R = \frac{k}{d^2}$$

R = Count rate
d = distance

Taking logs,

$$\log R = -2 \log d + \log k$$

Thus the power to which d must be raised can be obtained from the log graph as above (data for these graphs were from actual records using the ratemeter described last month).

It can be seen that the power to which the distance had to be raised was not determined exactly as 2, but consideration of the errors involved in the experiment (mainly in taking the reading from the ratemeter) shows the result to be within the range of experimental error.

This may seem to be a high error, but the ratemeter was not designed to give extremely high accuracy, and it must be remembered that the needle of the meter flickers to some extent all the time, presenting a difficulty in determining exactly what the reading should be. Each experimenter will have his own idea of where the arithmetic mean of the flickerings lie.

HALF LIFE AND ITS DETERMINATION

In radioactivity the decay of a substance is exponential, it never being completely annihilated, hence to talk of its total active period is impossible; so the time taken for *half* the specimen to decay away by radioactivity is taken as a measure of its term of existence, this being called the *half life*.

Treating this mathematically, suppose a given sample of radioactive compound contains N radioactive atoms at some time t, and the probability that each of these will decay in any one second is represented by a constant a (the decay constant).

Then the average number of atoms dN that decay in a time dt is given by,

$$dN = -aNdt$$

Integrating this over a time t = 0 to t = t

$$\int_{N_0}^{N} \frac{dN}{N} = a \int_{t=0}^{t=t} dt$$

hence,

$$N = N_0 e^{-at}$$

Where No is the number of atoms present at time t = 0. The ratio N to N_0 is the fraction of radioactive atoms remaining unchanged after a time t.

The decay constant, a, is the fraction of the total number of atoms that decay in unit time (provided unit time is small enough). The units of the decay constant are reciprocal time, it usually being expressed as reciprocal seconds. Its value is constant and specific for a given nucleus.

Practically, this decay constant is not used, but half life, mentioned above.

At a time $t = \frac{1}{2}t_0$, the number of atoms remaining, N, equals $\frac{1}{2}N_0$. Substituting in the integral formula,

$$\frac{1}{2} = e^{-a\,\frac{1}{2}t}$$

or

$$\log_e \tfrac{1}{2} = -at_{\frac{1}{2}}$$


($t_{\frac{1}{2}}$ is the half life)


then,

$$t_{\frac{1}{2}} = \frac{\log_e 2}{a}$$

Fig. 2 (right). A logarithmic graph of log distance against log count rate

Fig. 1 (below). This graph shows 1/distance squared plotted against count rate

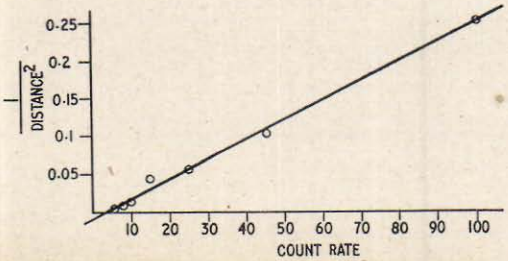

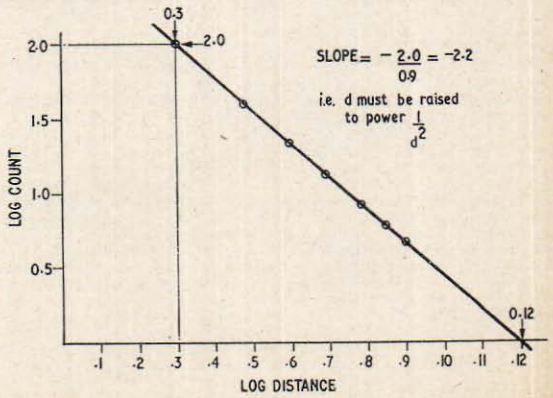

LEARN ELECTRONICS — AS YOU BUILD



over 25 CIRCUITS—

EXPERIMENTS — MODELS and TEST EQUIPMENT — including:

- Valve Experiments
- Transistor Experiments
- Electro-magnetic Experiments
- Basic Amplifier
- Basic Oscillator
- Basic Rectifier
- Signal Tracer
- Simple Counter
- Time Delay Circuits
- **CATHODE RAY OSCILLOSCOPE**
- Square Wave generator
- Morse Code Oscillator
- Simple Transmitter
- Electronic Switch
- Photo-electric circuit
- Basic Computer Circuit
- Basic transistorised radio receiver using *printed circuit*
- A.C. Experiments
- D.C. Experiments

The full equipment supplied comprises: valves, transistors, photo-tube, modern type chassis board; printed circuit board; full range resistors, capacitors and inductors; transformers; potentiometers; switches; transistors; valves; all hardware, wiring and every detail required for all practical work *plus* CATHODE RAY OSCILLOSCOPE for demonstrating results of all experiments carried out. All practical work fully described in comprehensive PRACTICAL MANUALS. Tutor service and advice if needed.

This complete practical course will teach you all the basic principles of electronics by carrying out experiments and building operational apparatus. You will learn how to recognise and handle all types of modern components; their symbols and how to read a completed circuit or schematic diagram. The course then shows how all the basic electronic circuits are constructed and used, and HOW THEY ACTUALLY WORK BY USING THE OSCILLOSCOPE PROVIDED. *An application is given in all the main fields of electronics, i.e. Radio; control circuits; computers and automation; photoelectrics; counters, etc., and rules and procedure for fault finding and servicing of all types of electronic equipment.*

- NO PREVIOUS KNOWLEDGE NEEDED
- SENT IN ATTRACTIVE BOX
- NO MATHS USED OR NEEDED
- COMPLETE ADVICE SERVICE
- REASONABLE FEE—NO EXTRAS REQUIRED
- EVERYTHING REMAINS YOUR OWN PROPERTY

A completely NEW up-to-date home study experimental course by BRITISH NATIONAL RADIO SCHOOL — Britain's Leading Electronic Training Organisation.

POST NOW FOR FREE BROCHURE

To: BRITISH NATIONAL RADIO SCHOOL, READING, BERKSHIRE. Please send free Brochure, without obligation, to:

NAME .....

ADDRESS .....

.....

Block Capitals Please

PE 12.64.

The actual rate of decay of a specimen is equivalent to the rate of emission of photons or particles, since each atom gives rise to a particle and/or a photon of radiation. This rate of emission is therefore the same as the absolute rate of decay, represented by,

$$\frac{-dN}{dt}$$

It is very difficult, however, to detect and record every single particle emitted from a radioactive mass, although it is possible to measure a constant fraction of that decay. This distinguishes between the count rate registered on the G-M ratemeter and the true rate of decay. The relationship between the two can be given as follows,

$$C = K\left(\frac{-dN}{dt}\right)$$

Where K represents the overall efficiency of the detection.

The numerical value C may replace the true rate of decay in the integrated decay equation.

$$C = C_0 e^{-at}$$

Hence,

$$\log_{10} = -0{\cdot}4343at + \log_{10} C_0$$

The logarithm of the measured count rate, C, plotted against the time, yields a straight line graph of slope 0·4343a, from which a and hence $t_{\frac{1}{2}}$ can be found. In practice it is easier to plot count rate on semi-logarithmic graph paper against the time, and read off $t_{\frac{1}{2}}$ directly. (See Fig. 3.)

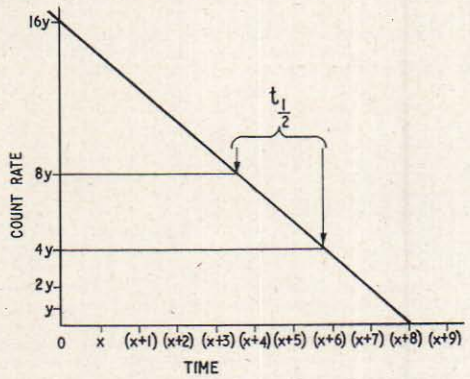


Fig. 3. Count rate plotted against time on a semi-logarithmic graph

It can be seen from the above description and the graph, that to obtain a value for the half life of a substance, a graph from which the slope can be easily determined or from which the half life is directly obtainable, is essential. This means that this method can only be employed for the determination of the half lives of substances in which that period is practicably short (say, up to one year). Thus the substances that the amateur normally deals with (uranium and radium mainly) whose half lives are extremely long (1,000 years at least) cannot easily be treated in this manner to obtain values for the half life period.

For the determination of the long half lives a special technique is employed. Here the rate of decay and the number of atoms present in the specimen are determined separately, these together with knowledge of the Avogadro number for the specimen (the number of molecules in one gram molecule of a substance). The value of the Avogadro number is $6{\cdot}02 \times 10^{23}$ molecules per mole. In the actual determination of the half life the quantities required are the decay rate, the weight of substance under examination (accurately in grams), the gram molecular weight (from tables), and the Avogadro number.

It must be remembered that the count rate recorded by the ratemeter is not the decay rate but a fraction of it, and before any determinations of half lives can be undertaken this relationship must be established.

A SIMPLE PIECE OF APPARATUS

It will be of great use if the following simple piece of apparatus is constructed and used when determining half lives. It consists of a short length of wood with mounts for the G-M tube and the source holder. No dimensions have been given as these depend on the size of G-M tube available. The tube is mounted through holes drilled in blocks of wood which are mounted in the positions shown in Fig. 4.

Once the relationship between count rate and decay rate has been determined for the apparatus it can easily be used for future determinations of half lives. The relationship can be determined in two ways: by consideration of the geometry of the arrangement and by experiment, assuming the half life of a substance.

Considering the geometry of the system, the source can be considered as a point source as the quantities used by the amateur are small. Referring to Fig. 5, the following measurements must be made:

1. The distance from the centre of the source to the G-M tube—"d".
2. The width of the G-M tube—"a".

Hence from the geometry of the figure,

$$\tan A = \frac{a}{d}$$

hence A can be found in degrees.


The constant relating count rate to decay rate is then 360/A, assuming that the specimen radiates equally in all directions.

Having determined the constant for the apparatus it can now be used to find half lives. The method is as follows.

The first consideration is the fraction of radioactive material in the specimen under examination. Consider a radioactive element, M, existing in a compound, MX, which is under examination. The fraction of M present is then the ratio of M to M + X. A practical examination will now be given. In the compound radium chloride, the fraction of radium present is found as follows

$$\text{Molecular weight of Ra } Cl_2 = 226 + (35{\cdot}5)2$$
$$= 297$$

Fig. 4. Simple apparatus for half life experiments

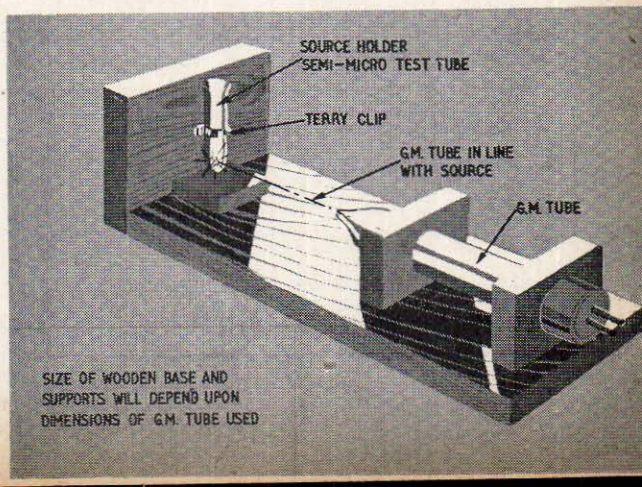

MINIATURE METALLIZED POLYESTER CAPACITORS



These small moulded metallized polyester capacitors are ideally suited to the applications to printed wiring panels and transistorised circuits. The use of the new dielectric material and unique construction combine the advantages of small physical size and superior electrical characteristics which meet the requirements of H.5 DEF. 5011 Specification.

CONSTRUCTION

The windings are virtually non-inductive and the wire terminations are soldered direct to the metal electrodes eliminating contact resistance and ensuring the minimum possible inductance.

Cap. Tolerance : ±20%

Voltage Rating :
Peak ripple voltage and D.C. voltage must not exceed rated D.C. voltage.


Power Factor :
≤0.01 at 1 Kc/s. at + 20°C.

Temperature Rating :
Suitable for working at + 85°C. without derating.

Insulation Resistance :
10,000 megohms or 2,000 ohm Farad whichever is less.

Terminations :
22 SWG solder coated parallel wires for vertical mounting.

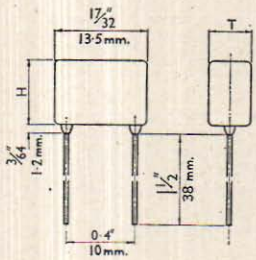
Finish :
Insulated—special non-cracking heat resisting thermosetting compound providing good insulation and good protection against the ingress of moisture.



Cap. μF	Dimensions H	Dimensions T	T.C.C. Type No.
250 V. D.C. at 85°C working			
0.01	11/32in. 9 mm	7/32in. 5.5 mm	PMX1
0.015	11/32in. 9 mm	7/32in. 5.5 mm	PMX7
0.022	11/32in. 9 mm	7/32in. 5.5 mm	PMX2
0.033	11/32in. 9 mm	7/32in. 5.5 mm	PMX5
0.047	11/32in. 9 mm	7/32in. 5.5 mm	PMX3
0.068	7/16in. 11 mm	9/32in. 7.2 mm	PMX8
0.1	7/16in. 11 mm	9/32in. 7.2 mm	PMX4
400 V. D.C. at 85°C working			
0.01	11/32in. 9 mm	7/32in. 5.5 mm	PMX41
0.022	11/32in. 9 mm	7/32in. 5.5 mm	PMX42
0.033	7/16in. 11 mm	9/32in. 7.2 mm	PMX45
0.047	7/16in. 11 mm	9/32in. 7.2 mm	PMX43

THE TELEGRAPH CONDENSER CO. LTD.
Electronics Division · North Acton · London · W.3. · Tel. ACOrn 0061 · Telex: 261383
(also at) CHESSINGTON, SURREY & BATHGATE, SCOTLAND

L.K. ELECTRONICS (VICTORIA) LTD.

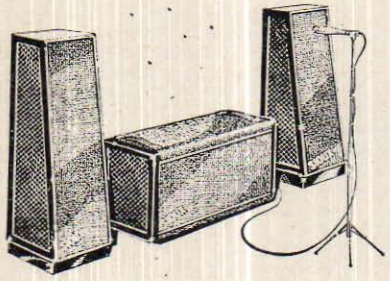

ARE NOW SOLE NATIONAL CONCESSIONAIRES FOR THE

SIOUX 60 WATT GUITAR AMPLIFIER

Incorporating

Ten High Duty Speakers in two columns of five designed to handle efficiently the full output of Amplifier at frequencies down to 25 c.p.s. ★ Heavily made Cabinet in two tone Vynair ★ For 200-250 v. to 50 c.p.s. A.C. Mains operation ★ Four jack socket inputs and two independent volume controls for simultaneous connection of up to four instrument pick-ups or microphones ★ Level frequency response throughout the Audible Range ★ Speakers, microphone, stand and leads included.

OUR PRICE ONLY 35 GNS

Please send S.A.E. for details to:

L.K. ELECTRONICS (VICTORIA) LTD.

17 GILLINGHAM ROW, LONDON, S.W.1

NOW *ANYONE* CAN AFFORD TO TRAIN TO BE AN EXPERT IN RADIO, TV, AND ELECTRONICS

Anyone can afford these amazing courses—anyone can understand this practical training—No complicated mathematics to hold you back—No old fashioned, obscure explanations to frustrate you!

The lessons are **CRYSTAL CLEAR, PRACTICAL, EASY TO MASTER AND USE**—Early lessons make fundamentals clear even to the beginner, while other lessons will give you the practical "know-how" of an expert!

Compares favourably with some courses costing very much more! By creating a mass market through large volume sales and eliminating individual letter writing we are able to pass on these savings directly to you!

Each course is printed on extra large quarto size sheets and bound into one manual to simplify handling and distribution.

Please select the course most suitable for your requirements from the following:

No. 1. RADIO COURSE. Fundamental facts—Electrons—Conductors and Insulators—Radio Batteries—Circuits—Magnetism—Ohm's Law—Resistor Colour Code—Chart—What resistor to use—Electro-Magnetism—Electromagnetic Induction—Self Induction—Radio Frequency Inductances—Capacity Coupling—I.F. Transformers—Radio Coils—Radio Capacitors—The Farad—Dielectric—Capacitor Colour Code—Alternating Current Theory & Filters—Reactance and Resistance—Charts to calculate Capacity Frequency and Inductance—Handy Radio Formulae—Practical Aspects of Radio Servicing—Radio Valves—Transistor Theory—N Type Germanium—P Type Germanium—Diode Action—Transistor Action—D.C. Stabilization—Transistor Bias Adjustment—R.F. Amplification—Superheterodyne Principles—A.V.C. Power Supplies—Meters—Multitesters and Valve Testers—Point to Point Servicing—Signal Generators and Signal Tracers—Using an Oscilloscope for Servicing—Alignment—Amplifiers and P.A. Equipment—High Fidelity—Advantages of Inverse Feedback—Speakers—Frequency Modulation—How to Obtain Radio Jobs. **Price for the complete course. ONLY 36/-. Plus postage 1/6.**

No. 2. ELECTRONICS COURSE. Includes most of the above lessons plus L.C. and R. Combined Circuits—Resonance Phenomenon—Behaviour at Resonance—How Meters Work—Making a Voltmeter—Ohm meter Connections—Valves—Electron Behaviour—Triode—Characteristic Curves—Power Supplies—Audio Amplifiers—Microphones—Resistance Coupling—Obtaining Grid Bias—Push Pull and Parallel—Phase Inverter Circuit—Radio Frequency Voltage Amplifiers—I.F. and Multiband Coils—Detection—Receiver Circuits—Results of Frequency Mixing—A.V.C.—Electronic Oscillators—Quartz Crystals—Radio Transmitter Circuits—Modulation and Tuning—Lines, Antennas and Radiation—Test Equipment Using Meters—Electronic Test Equipment—Thyratrons—Photo-Cell Equipment—Radio Compass—H.F. Heating—Electronic Shaping Circuits—Electron Microscope—Electric Strain Gauges—Inter-Communicators—Radio Servicing Techniques—Servicing Printed Circuits.

Price for the complete course. ONLY 39/6. Plus postage 1/6.
Graduates of the Electronics Course can qualify for a certificate—details sent with each order.

No. 3. TELEVISION COURSE. Effect of Mis-adjusted controls—Pictures of various faults—Service adjustments—Circuit Faults Indicated by a Poor Pattern—Finding Bad Valves by observing Picture Faults—Separate Channel I.F. System—Intercarrier I.F. System—Negative Picture—Interference—Antenna Principles and Practices—U.H.F. Transmission Lines—Facts About the T.V. Signal to Help you in Service Work—Synchronizing Separators—T.V. Interference Aids—All about Cathode Ray Tubes—Explanation of T.V. Circuits—Video Detector—Video Amplifier—D.C. Restorer Circuit—Automatic Gain Control Circuits—Oscillators—Deflection Coils—Automatic Frequency Control Circuits—Analysis of Stagger Tuned I.F. Receiver—Analysis of Three Inter-Carrier Type Receivers—The Vertical Deflection Circuit—The Horizontal Deflection Circuit—Waveforms—Schematics of various sections of a T.V.—U.H.F. Converters and Tuners—T.V. Test Equipment and Alignment—Analysis of Various Problems.

Price for the complete course. ONLY 36/-. Plus postage 1/6.

UNCONDITIONALLY GUARANTEED TO GIVE COMPLETE SATISFACTION
You must be convinced that this is the best value you have ever seen in Electronic, Radio or T.V. Training, otherwise you can return the course (or have your money refunded if sent with order) after you have examined it in your own home for a full seven days.

IF YOU SEND CASH WITH ORDER WE WILL INCLUDE A FREE 70-PAGE BOOK.
Tick on the coupon one book for each course ordered with full cash.

RADIO SERVICING FAULT FINDING BOOK. TELEVISION FAULT BOOK. OSCILLOSCOPE BOOK.

These free books are authoritative, and loaded with information. Would cost at least 5/- each if bought separately—by sending cash you reduce book-keeping and other costs, which savings we pass back to you!

FREE TRIAL OFFER

Pay only 5/- per week if you wish. Clip coupon right now for this special offer

To: Sim-Tech Book Company, Dept. EL2., Gater's Mill, West End, Southampton, Hants.

Please send the following courses for a full seven days' trial.

☐ **No. 1. RADIO COURSE.** 37/6, incl. postage.

☐ **No. 2. ELECTRONICS COURSE.** 41/-, incl. postage.

☐ **No. 3. TELEVISION COURSE.** 37/6, incl. postage.

(Free trial customers tick one only please).

If not delighted, I may return the course post-paid without further obligation on my part. Otherwise I will pay cash price **OR** 5/- weekly until purchase price plus 2/6 service charge has been paid.

☐ Tick here if enclosing fully purchase price.

Please send me ☐ **FREE. RADIO FAULT FINDING BOOK.**

☐ **FREE T.V. FAULT FINDING BOOK.** ☐ **FREE OSCILLOSCOPE BOOK.**

Amount enclosed £.....

I understand that you will refund this money in full if I am not 100% satisfied. Overseas customers please send full amount (including Ireland).

NAME.....

ADDRESS.....


.....

City..... County.....

MAINS POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6 v.—9 to 12 volts for up to 500 mA. (class B working). Takes the place of any of the following batteries. PP1-PP3-PP4-PP6-PP7-PP9 and others. Kit comprises: mains transformer-rectifier, smoothing and load resistor 5,000 and 500 mfd. condensers, zener diode and instructions. Real snip at only 14/6, plus 2/6 post.

OUR BARGAIN OF THE YEAR

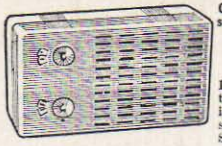


Complete kit of parts to build this 6-transistor 2 wave superhet receiver at only **39/6** plus 2/6 post and ins.

"CORONET" Mk. III

It fully covers the medium-wave band and that part of the long-wave band to bring in B.B.C. Light. The circuit includes a highly efficient slab aerial and 2½" P.M. speaker. Overall size approximately 4½ × 2½ × 1¼in. Supplied complete with carrying case.

MOTOR BARGAIN

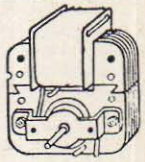

Silent running mains motor by very famous maker. Ideal for gramophone, tape recorder, fan, etc. etc. 200-250 volts. A.C. shaded pole start. Size approximately 2¾ × 2½ × 1¾in., 2,750 r.p.m. Spindle diameter 5/32in. Spindle length ¾in. Brand new guarantee. Price **12/6** plus 1/- post.

YAXLEY SWITCHES

POLES	2 WAY	3 WAY	4 WAY	6 WAY	8 WAY	10 WAY	11 WAY	12 WAY
1	2/8	2/10	3/1	3/6	4/-	4/6	4/6	4/8
2	3/3	3/8	4/1	4/11	6/-	7/-	7/-	7/6
3	3/11	4/6	5/2		8/-	9/6	9/6	10/3
4	4/6	5/4	6/2	7/10	10/-	12/-	12/-	13/-
6	5/9	7/-	8/3	10/9	15/-	17/-	17/-	18/6
8	8/-	8/8	10/4	13/8	18/-	22/-	22/-	25/-
10	10/-	10/6	12/5	16/9	22/6	27/-	27/-	30/-
12	12/-	12/6	14/6	19/8	27/6	32/-	32/-	36/-
14	14/-	14/6	17/-	22/6				
16	16/-	16/6	19/6	25/6				


5 WAY 1 pole 3/6 2 pole 4/9 **24 WAY** 1 pole 15/- 2 pole 22/6

Speaker Bargain



12in. High fidelity loudspeaker. High flux permanent magnet type with standard 3 ohm speech coil. Will handle up to 12 watts. Brand new, by famous maker. Price **27/6**, plus 3/6 post and insurance.

Adjustable Thermostat

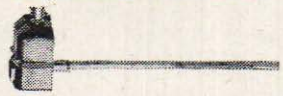

Suitable for Industrial or domestic purposes such as controlling furnace oven, immersion heater, etc. Can also be used as a flamestat or fire alarm. Made by Sunvic these are approximately 17in. long and adjustable over a range 0 to 550°F. The contacts are rated at 15 amps. 230 volts, and the adjustment spindle, which comes to the top, can be fitted with a flexible drive for remote control or just a pointer knob for local control. Listed at **£3** or **£4** each, these are offered at only **8/6**, plus 2/6 postage and insurance.

Timer Kit

Special offer of all components except metal box to make mains operated interval timer for photography, etc., **12/6** plus 2/6 post.

Waterproof Heater Wire

16 yd. length. 70 watts. Self regulating temperature control, **10/-** post free.

Building a Scope?



3in. oscilloscope tube. American made type No. 3FP7, base 6.3 v. 6 amp. heater electrostatic deflection, brand new and guaranteed, with circuit diagram of scope, **15/-** each plus 2/6 post and insurance.

Ice-Stat

This is a small thermostat which cuts on and off at round freezing point. Has many uses, one of which could be an ice warning device to be fitted under your motor car. Price **7/6**. Post 1/-.

Simmerstat Heater Regulator

Suitable to control elements, heaters, soldering irons and boiling rings up to 2,500 watts. Complete adjustable, normal price 55/- each, special snip price **12/6**, plus 1/6 postage and insurance.



Siemens High Speed Relay

Twin 250 ohm coils adjustable tension change over contacts—platinum points **7/6**. Post 1/-.

BARGAINS

Air Spaced Trimmers, good length ¼in. spindle 0-50pf, but easily converted down to 0-5 pf. **2/6** ea., post 1/-. Ditto but 2 gang for F.M. Tuners etc., **4/6** ea. Post 1/-.
High Voltage Condensers. 2 mfd. 1.2 kv. **4/6**, 4 mfd. 1.5 kv. **6/6**, 0.5 mfd. 4 kv. **6/6**, .01 mfd. 5 kv. **3/6**.
Trimmer Assortment. 3 doz. various sizes and types including doubles and ceramic air spaced. Retail list value over £4, all new and unused **10/-** for 36. Post 2/-.
Motor Generator, 6 v. input gives 12 v. output, suitable to run 12 v. car battery radio off 6 v. battery **17/6**, post and insurance 3/6.
Midget 3in. P.M. Loudspeaker 3 ohm, **12/6**, 8 ohm, **13/6**. **Midget** 208 pF+176 pF two-gang Tuning Condenser with trimmers for transistor set, **Price 9/-.**

Post Office Type Key Switch. 3 position 10 change over contacts **7/6**, post 1/-.
Rectifier Valves. 4 pin 4 v. 120 ma. full waves replace MU12 etc. **4/6**. P. & P. 1/-. **40/-** per doz. Post free.
Double Trimmers. Ideal for making preset station receiver 100 pf. plus 100 pf. **6/-** per doz. Post 1/-.
Mica Condenser. 100 pf. 200 pf. 300 pf. 500 pf. 1,000 pf. 3 doz. assorted list value £2. 36 for **5/-**. Post 2/-.
Litz Wire for coil winding. Normally over 40/- per lb. from makers, 1lb. reels **20/-**ea. Post and packing 2/-.
Hours Elapsed Meter. Fine American make unused but ex-equipment **35/-** ea., post 2/-. **12 v. 10 amp. Rectifier.** 8¾in. sq. plates **19/6**, post 2/-.

ELECTRONICS (CROYDON) LTD.
266 LONDON ROAD, WEST CROYDON, SURREY
Post orders to:
43 SILVERDALE ROAD, EASTBOURNE, SUSSEX

Therefore the fraction of radium present is

$$\frac{226}{297} = 0{\cdot}761$$

A weighed specimen of the substance under examination is then taken and the weight of radioactive material present is found. The count rate observed from the specimen in the above apparatus is noted. The half life is then found as follows.

Let the count rate be C, the constant of the apparatus be 360/A, the weight of specimen taken W, the fraction of radioactive material present 1/f, and the Avogadro number L. Let the molecular weight of the specimen be M. Then,

$$\text{Weight of radioactive substance present} = \frac{W}{f}$$

$$\text{True decay rate} = \frac{360C}{A}$$

Number of atoms present in the radioactive specimen

$$= \frac{W \times L}{f \times M}$$

The decay constant "a" therefore equals,

$$a = \frac{360CfM}{AWL}$$

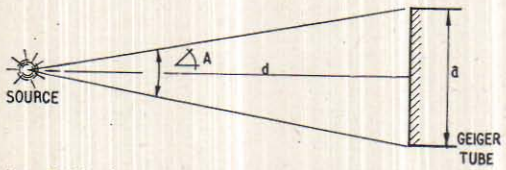


Fig. 5. Critical measurements in half life experiment set-up

A PRACTICAL EXAMPLE

A practical example from the author's own records will now be given.

Source to tube distance = 10cm
Weight of radium taken = 5×10^{-6} grammes
Diameter of G-M tube = 2cm
Count rate = 570/sec

$$\text{Angle of acceptance} = \tan^{-1}\frac{2}{10} = 11{\cdot}3°$$

therefore,

$$\text{Decay rate} = \frac{570 \times 360}{11{\cdot}3} = 18{,}150 \text{ counts/sec.}$$

Hence,

$$a = \frac{18{,}150 \times 226 \text{ (M.W. of radium)}}{6{\cdot}02 \times 10^{23} \times 5 \times 10^{-6}}$$

(the weight of radium taken was 5×10^{-6} grammes)
Hence,

$$t_{\frac{1}{2}} = \frac{\log_e 2 \times 6{\cdot}02 \times 10^{23} \times 5 \times 10^{-6}}{18{,}150 \times 226 \times 60 \times 60 \times 24 \times 365} \text{ years}$$

= 1,600 years (true value 1,595 years).

ASSAY OF ORES

The above determinations of the half lives of radioactive substances, while useful as an exercise, is not of much use to the amateur as the half lives of all the radioactive substances have been determined to a far greater degree of accuracy by professionals. The use of the above method, however, does enable the amateur to assay radioactive ores. The process is as follows.

Having determined the radioactive compound present by chemical analysis, a weighed sample of the ore is treated as in the above experiment. The half life and molecular weight of the specimen are taken from tables, leaving the weight of radioactive material present the only unknown factor.

Having determined this, the assay of the ore can be expressed as a percentage or as content of radioactive material per ton. To clarify this an example will be given.

Weight of uranium ore taken = 100 grammes
Molecular weight of uranium = 235
Avogadro number = $6{\cdot}02 \times 10^{23}$
Rate count = 1,470 counts/sec.
Half life of uranium = $7{\cdot}1 \times 10^{8}$ years

$$\text{Constant for apparatus} = \frac{360}{11{\cdot}3}$$

$t_{\frac{1}{2}} = \frac{\log_e 2LW}{RM}$ (symbols as before, R = decay rate)

Hence weight of radioactive material present is,

$$W = \frac{t_{\frac{1}{2}}RM}{\log_e 2L}$$

$$= \frac{7{\cdot}1 \times 10^{8} \times 60 \times 60 \times 24 \times 365 \times 235 \times 1{,}470 \times 360}{11{\cdot}3 \times 6{\cdot}02 \times 10^{23}}$$

= 0·593 grammes.

Hence, assay of material is 0·593 per cent of uranium 235.

EXAMINATION OF RAIN WATER

Readers will no doubt remember the consternation that was caused a few years ago by the discovery of radioactive iodine (I_{131}) in milk. The half life of this isotope is eight days so its presence can be easily detected by the first of the two methods described for determination of half lives. The iodine entered the milk via rain which fell on the pastures of cattle. The concentration of the isotope in the rain would be very small.

Investigation of radioactive material in rain first necessitates the concentration of the rain water. For this a special kettle reserved for the purpose should be used. About a gallon of rain water is collected. The kettle is filled with this water and boiled almost to dryness; it is then refilled and the process repeated until all the rain water collected has been concentrated (a gallon is the minimum for usable results).

The concentrate should be of the order of 50 to 100cc. This is then transferred to a conical flask of 250cc capacity where final concentration is carried out. The final volume should occupy about a half of one of the semi-micro test tubes.

The radioactivity of the specimen is observed over a period of time and a graph of count rate against time is plotted. One reading a day at the same time each day will be sufficient. If the graph adopts an exponential form, the half life of the radioactive material present can be found. Since the half life is peculiar to a particular nucleus, the substance present can be identified.

The specimen of rain water for concentration must be concentrated as soon as possible after it has fallen.

The above article by no means exhausts the possibilities of the use of the ratemeter, but it is hoped that it will serve as an introduction to radioactivity enabling the individual to devise his own experiments and lines of research. ★

DETACHED PARTICLES
By John Valence

IMPORTANT DATE

PERHAPS it is not altogether irrelevant for me to mention the General Election. After all this did take place on the same day that PRACTICAL ELECTRONICS made its debut (yes, 15 October 1964 was certainly a date of importance!). Furthermore, electronics played a notable part in the election proceedings, both during the campaign as candidates vied with one another to appear the more foresighted in technological matters—the words electronics and automation are now very much part of the politician's stock-in-trade—as well as after the poll when some of the largest and fastest computers in the country were mobilised by the BBC, ITV, and the Press to analyse the results.

But was it lethargy on the part of the Elliott 803 in the BBC studio or inefficiency of the humans feeding this robot which produced the state of affairs where one commentator was able to obtain the answer on his slide rule in much shorter time?

A BIASED VIEW?

IT is not, I trust, insularity on my part that makes me favour our term "valve" as opposed to the trans-Atlantic "tube". The latter word has always seemed to me a pretty inapt title for this important electronic device. All the more surprising that it was adopted by the Americans who generally have a gift for concocting imaginative and colourful terminology.

Actually I seem to remember reading sometime ago an admission by an American writer that the English term valve was a more appropriate choice than tube. The reason put forward in support of our word was rather odd though. It was suggested firstly that "valve" is synonymous with "amplifier", and secondly that all valves (or tubes) are amplifying devices.

What does this word valve in its general sense suggest to you? Do you think of, for example, a small lever or screw device controlling a large flow of liquid in a pipe line—if so then this is in truth an amplifier. Or do you visualise an object which is essentially a one-way device—such as the pneumatic tyre valve?

Coming back to the electronic valve, the one-way interpretation fits the envelope perfectly. On the other hand, the amplifier idea is logical all right when applied to triodes and upwards, but unfortunately excludes the humble diode.

SWEET AND LOW

HAVE you noticed how widespread the use of built-in background music is becoming? I really do mean "have you noticed". The sound that is nowadays being disseminated in many public places, shops, and restaurants is indeed of a very subtle character. It is far, far removed from the brash and forthright "music while you work" variety.

This background music is played more or less continuously and is designed not to intrude, but to be just audible. One may be hardly aware of the music—but sure enough it is doing its stuff on our subconscious mind!

Maybe it is all good therapeutic treatment, inducing calm into worried minds, and so aiding our digestive processes as we imbibe. Stores and supermarkets presumably find it commercially rewarding. The casual shopper, without realising exactly why, finds himself loath to depart from the comforting relaxing atmosphere, but lingers among the wares.

EXTRACTING THE FI

YOU may have your own ideas regarding the ethical or artistic aspects of this form of sound distribution. At any rate we can admire the technical expertise that has been applied to the planning and recording of programme material.

Musical items are carefully selected—strident sounds or heavily accentuated rhythmics are out. During the recording session amplitude compression is introduced, for it is essential that the sound level should remain constant throughout.

I suppose the engineers responsible for these recordings have their own particular problems and have no doubt evolved some ingenious circuits for their purpose. Perhaps it would be a trifle unfair to describe their end product as *no fi*.

But why employ all those musicians and then pass their recorded performance through an electronic mangle? Far more sensible to give the job to a computer, since this is an obvious case for synthesised music.

J.V. PREDICTS

FASHIONS do change, of course, and already I can see the next step: "Instal 'NOVOX' Ultrasonic Background System for that tranquil atmosphere . . . your clients will appreciate this aid to concentration when contemplating the menu or pondering over that special purchase . . ." etc., etc.

Ridiculous? I am not so sure.

A WEIGHTY MATTER

ACCORDING to the theory put forward by an archæologist, Stonehenge—that monumental array of stone circles on Salisbury Plain—is a neolithic age computer, and was probably used to calculate the movement of the Sun.


Solid state, without a doubt.



He's a wizard at miniaturisation

FOR – IMMEDIATE – DESPATCH – PHONE – US – TODAY

BUILD YOUR OWN RECORD PLAYER

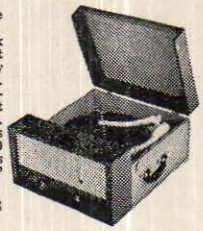

4 Speed Autochange 2-tone Cabinets 17 × 15 × 8½in. High flux loudspeaker and 3 watt 2 valve amplifier ready built. Quality output. Volume and Tone controls. All items fit together perfectly. Special instructions enable assembly in 30 minutes, only 5 wires to join. 12 months' written guarantee.

AUTOCHANGE KITS Complete—as above.

B.S.R. Monarch	£11/10/-	P.P. 5/-
Garrard Autoslim	£12/18/-	P.P. 5/-

QMAX CHASSIS CUTTER

The cutter consists of four parts: a die, a punch, an Allen screw and key.

⅛in.	14/6	1⅛in.	18/-	2in.	34/3
¼in.	14/6	1¼in.	18/6	2 3/32in.	37/9
5/16in.	15/6	1 5/16in.	20/-	2½in.	44/9
7/16in.	15/9	1⅜in.	20/-	1in. sq.	31/6
1in.	18/-	1½in.	20/6	1 1/16in. sq.	28/-
1 1/16in.	18/-	1⅝in.	22/6		

CRYSTAL MIKE INSERTS. High output.

Miniature size, 1⅛in. dia. × ⅝in.	6/6
ACOS MIKE INSERT 1¾ × ⅝in.	8/6
ACOS STICK MIKE 39-1	35/-
T.S.L. DE LUXE STICK MIKE	25/-
TELEPHONE CONTACT MIKE	10/6
GUITAR CONTACT MIKE	15/6
Moving Coil Mike 90/-, Floor Stand	57/-
TANNOY CARBON MIKE	5/6

FULL WAVE BRIDGE SELENIUM RECTIFIER: 2, 6 or 12 v., 1½ amp., 8/9; 2 a. 11/3; 4 a., 17/6.
CHARGER TRANSFORMERS. Tapped input 200/250 v. for charging at 2, 6 or 12 v., 1½ amps., 15/6; 2 amps., 17/6; 4 amps., 22/6. Circuit included.
4 AMP CAR BATTERY CHARGER with ammeter, Leads, Fuse Case, etc., for 6 v. or 12 v., 59/6.


MINIATURE PANEL METERS

Size 1⅝in. sq. Precision jewelled bearings, 2% accuracy, silvered dials, fine pointers, 0-1 mA. 27/6; 0-5 mA. 27/6; 0-300 V. 27/6; 0-50 μA 39/6: 0-500 μA 32/6. "S" meter 35/-

MOVING COIL MULTIMETER TK20A. 0-1000 v. A.C./D.C. ohms. 0-1001k, etc., 49/6. 0-150 mA Pocket size 2in. scale.

VALVE HOLDERS. EA50 6d. B12A, CRT. 1/3. Eng. and Amer. 4, 5, 6 and 7-pin 1/-. Printed circuit B9A, B7G, Int. Oct. 1/-. MORSE KEY 4/6; BUZZER 4/6.
MOULDED Int. Oct. or Mazda Oct. 6d.; B7G, B8A, B8G, B9A 9d. B7G with can 1/6. B9A with can 1/9. Ceramic EF50, B7G, B9A, Int. Oct. 1/-, B7G, B9A cans, 1/- each. Valve base plugs B7G, B9A, Int. Oct. 2/3.

1964 RADIOGRAM CHASSIS

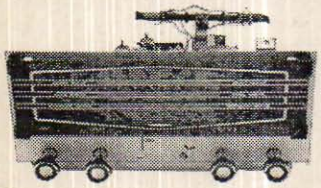

Three Wavebands
S.W. 16 m.-50 m.
M.W. 200 m.-500 m.
L.W. 800 m.-2,000 m.
Five Valves
Latest Mullard, etc.
ECH81, EF89, EBC81, EL84, EZ80
12-month guarantee. A.C. 200-250 v. 4-way switch. Short-Medium-Long-Gram. Ferrite Aerial. A.V.C. and Negative Feedback. 5 watts 3 ohm. Chassis 13½in. × 7in. high × 5in. deep. Glass dial size 13in. × 4in. horizontal wording. Two Pilot Lamps. Four Knobs. Aligned and calibrated. Chassis isolated from mains.

BRAND NEW £9.15.6 Carr. 4/6.
Matched Speakers 8in. 17/6; 10in. 25/-; 12in. 30/-

Famous Manufacturers' Surplus Bargain

Ferguson Quality Amplifier 4 Watts

Size 6½ x 5 x 4in. 200-250 AC double wound mains transformer. Volume and tone controls. Sensitivity 200 mv. Response 25 to 20,000 cps. Price with valves, etc. **49/6** *each. Complete Brand new. 2 units matched for stereo etc., 89/6.*

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 4 sides, riveted corners, lattice fixing holes, 2½in. sides, 7 × 4in., 5/6; 9 × 7in., 6/6; 11 × 3in., 6/6; 11 × 7in., 7/6; 13 × 9in., 9/6; 14 × 11in., 12/6; 15 × 14in., 15/-.
ALUMINIUM PANELS. 18 s.w.g. 12 × 12in., 4/6; 14 × 9in., 4/-; 12 × 8in., 3/-; 10 × 7in., 2/-; 8 × 6in., 2/-; 6 × 4in., 1/6.

MAINS TRANSFORMERS 200/250 AC Post 2/- each

STANDARD 250-0-250, 80 mA. 6.3 v. 3.5 a., tapped 4 v. 4 a. Rectifier 6.3 v. 1 a. tapped 5 v. or 4 v. 2 a. 22/6
Ditto 350-0-350 ..... 29/6
MINIATURE 200 v. 20 mA., 6.3 v. 1 a. 10/6
MIDGET 220 v. 45 mA., 6.3 v. 2 a. 15/6
SMALL 250-0-250 v. 45 mA., 6.3 v. 2 a. 17/6
STANDARD 250-0-250 65 mA., 6.3 v. 3.5 a. 17/6
HEATER TRANS. 6.3 v. 1½ a. 7/6
Ditto tapped sec. 1.4 v., 2, 3, 4, 5, 6.3 v. 1½ amp. 8/6
HEATER TRANS. 6.3 v. 4 a. 10/6
GENERAL PURPOSE LOW VOLTAGE. Outputs 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. at 2 a. 22/6
AUTO TRANS. 150 w., 0, 115 v. 200, 230, 250 v. 22/6
AUTO TRANS. 500 w. 0, 115, 200, 230, 250 v. 82/6
MULLARD "510" MAINS TRANS. TO SPEC. 33/6
300-0-300 120 mA., 6.3 v. CT 4a., 0, 5, 6.3 v. 2 a.

MAINS POWER PACKS. Ready built with Mains Transformers, Rectifiers and Condensers etc., providing H.T. and L.T.
200 v. 20 mA. D.C. ½ wave 6.3 v. 1 a. A.C. 25/6
220 v. 50 mA. D.C. ½ wave 6.3 v. 2 a. A.C. 35/6
250 v. 80 mA. D.C. Full wave 6.3 v. 4 a. A.C. 45/6

"THE POWER MITE" 45/-

PM9 Mains Unit 9 volt for Transistor Radios. Same size as P.P.9 (200-250V.) Miniature PP3 model. 19/6

4 TRANSISTOR PUSH-PULL AUDIO AMPLIFIER

Size 3 × 1⅞ × 1in.
A ready built miniature push-pull amplifier with Driver and output transformers, 4 transistors. Ideal for use with record players, intercoms, BABY ALARMS, etc., Complete with full instructions and circuit.
Price **47/6** 9 v. Batt. 2/3, 2½in. Speaker 15/-

NEW MULLARD TRANSISTORS

OC71 6/-, OC72 7/6, OC81D 7/6, OC81 7/6, AF115 10/6, AF114 11/-, OC44 8/-, OC45 8/-, OC171 9/-, OC170 8/6, AF117 9/6. Transistor Holders 1/3.
Sub Miniature Condensers. 0.1 mFd., 30 v., 1/3. 1, 2, 4, 5, 8, 16, 25, 30, 50, 100 mFd., 15 volt 2/6 each.

TRANSISTOR 4 CHANNEL MIXER with 4 separate input-output controls, 59/6


Volume Controls

Long spindles. Midget 5K ohms to 2 Meg. L/S 3/-. D.P. 4/6.
Stereo L/S 10/6, D.P. 14/6. Linear or Log Tracks.

80 Ohm CABLE Coax

Semi-air spaced 6d. yd. 40 yd. 17/6, 60 yd. 25/-.
Low loss 5dB per 100ft. at 500 mc/s. Ideal 625 lines 1/6 yd.

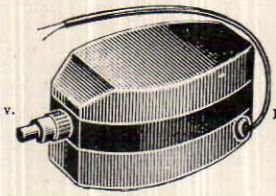THE "INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETIZER




35/-
200/250 v. A.C.
Leaflet S.A.E.

B.T.H. TAPE MOTORS 115 v A.C.
28 w. 12/6 pair, for 200/250 v. (in series)

BAKERS *'Selhurst'* LOUDSPEAKERS

THE CONNOISSEUR'S CHOICE

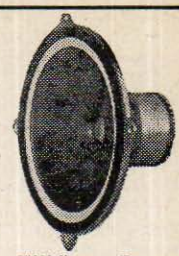

8in. JUNIOR SPECIAL 8w. 17000 lines Foam Suspension 40-20,000 c.p.s. **5 gns.**

12in. GUITAR HEAVY DUTY 25w. 15 ohm voice coils. Unlimited Applications. Response 20 to 10,000 cps. Magnet 12,000 lines. Genuine Musical Instrument Loudspeaker. **5 gns.**

12in. STANDARD HEAVY DUTY 20w. More powerful magnet 14,000 lines special suspension. 40-14,500 cps. Recommended wherever a high standard of reproduction is desired. **7 gns.**

12in. BASS HEAVY DUTY 25w. New 1964 high power model. Aluminium coil former with magnetic damping 25-15,000 cps. Ideal for all electric guitars. **12 gns.**

15in. AUDITORIUM MODEL 35w. Improved magnet alcomax with heavy plated assembly, weight 160lbs., 17,000 lines, 20-12,000 cps. Heat proofed Coil Former. Ideal for all Electric Guitars. **18 gns.**

Bakers offer a full repair service. Specials made to order. Older types updated.

BOOKS (*List S.A.E.*)

"W.W." Radio Valve Data	7/6
High Fidelity Speaker Enclosures	5/-
Valves Transistors, CRT Equivalents	9/6
At a Glance Valves, CRT Equivalents	3/6
TV Fault Finding	5/-
Mullard Audio Amplifier Manual	8/6
Radio Valve Guide, Books 1 2, 3, or 4 ea.	5/-
Practical Radio Inside Out	3/6
Master Colour Code	1/6
Coil Design and Construction Manual	5/-
Radio, TV and Electronics Data Book	3/6
International Radio Stations List	2/6
Boys' Book of Crystal Sets	2/6
Stroboscopic Disc 33, 45, 78 r.p.m.	1/-
How to Receive Foreign T.V.	5/-

WAVE-CHANGE SWITCHES
2 p. 2-way, or 2 p. 6-way, long spindle 3/6
3 p. 4-way, or 1 p. 12-way, long spindle 3/6
4 p. 2-way, or 4 p. 3-way, long spindle 3/6
8 p. 4-way, 2 wafer, long spindle 6/6
Wavechange "MAKITS" Wafers available; 1 p. 12-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 6 p. 2-way. Prices include click spindles, adjustable stops, 1 wafer, 8/6; 2 wafer, 12/6; 3 wafer, 16/-. Extra wafers up to 12, 3/6 each.
TOGGLE SWITCHES, s.p., 2/-; d.p. 3/6; d.p.d.t., 4/-. Rotary Toggles, s.p., 3/6; d.p. 4/6. Min. Slide d.p. 3/6.
JACKS. English open-circuit 2/6, closed-circuit 4/6. Grundig type 3-pin 1/3; Grundig Lead Type 3/6. Phono Plugs 6d. Socket 1/-. Banana Plugs 1/-. Sockets 1/-.
JACK PLUGS STANDARD Screened 3/-. Grundig 3-pin 3/6.
BULGIN NON-REVERSIBLE PLUGS and SOCKETS. P74 2-pin 4/3; P73 3-pin 4/6; P194 6-pin 6/6; P466 6-pin 12/6; P360 3-pin 4/-; Mains selector panel with plug 1/-.

TRIPLETONE HI-FI MAJOR £15.18.9



12 watts 15 to 20,000 c.p.s. 5 valves A.C. mains isolated. 12in. x 5⅛in. x 6in. high. Built-in pre-amp. and mixer. Two inputs and volume controls. Sensitivity mic. 10 mV.; Gram 250 mV. 3 tone controls, Bass, Treble and Middle. Auxiliary power supply. Ideal for all Electric Guitars. Cabinet with handle, 30/- extra.

RETURN OF POST MAIL ORDER SERVICE *EXPERTS ANSWER ALL ENQUIRIES* *NO ORDER TOO SMALL*

RADIO COMPONENT SPECIALISTS

337 WHITEHORSE ROAD, WEST CROYDON Telephone **THO 1665**

Written guarantee with every purchase. Buses 133, 68 pass door. S.R. Stn. Selhurst. *Post 1/-, Full List 1/-, C.O.D. 2/- extra.*

(Export welcome. Send remittance and extra postage, no C.O.D.)

THE MOST SUCCESSFUL HI-FI PLAN EVER OFFERED TO CONSTRUCTORS



IT'S MONEY SAVING, TOO!

You save pounds by building with ***MARTIN AUDIOKITS*** *- and there are so many units to chose from that it is a simple matter to select just the units to suit you best.*

Coupon brings brochure by return

MARTIN ELECTRONICS, 154 HIGH ST., BRENTFORD, MIDDLESEX

Leaflet showing Details of all Martin Audiokits, please to

NAME.....

ADDRESS .....

.....

P.E.12 .....

The new, easy way to build

MARTIN AUDIOKITS comprise a cleverly designed range of prefabricated transistorised units from which you can build from a single pre-amp stage to an integrated 20 watt series hi-fi assembly suitable for use with today's finest accessories. Assembling these tested and guaranteed units could hardly be simpler, but the final results appear thoroughly professional. Quality is superb; attractive knobs and escutcheons are available. As new units come along, they can be added to your assembly stage by stage so that Audiokits are never outdated.

FROM A PRE-AMP TO A 20 WATT STEREO ASSEMBLY

MARTIN Audiokits

MARTIN ELECTRONICS LTD., 154/5 HIGH ST., BRENTFORD, MIDDLESEX

Phone : ISLeworth 1161/2

Z & I AERO SERVICES LTD.

Head Office and Warehouse: **44A WESTBOURNE GROVE, LONDON, W.2.**

Retail Shop: **85 TOTTENHAM COURT ROAD, LONDON, W.1**
Tel.: LANgham 8403

Tel.: PARK 5641/2/3

OA2	6/-	5Y3GT	5/-	6C4	2/6	6SN7GT	4/6	12J5GT	3/-	42	5/-	DC70	8/-	EBF89	6/9	EF93	4/9	EZ80	5/6	PY33	9/-	UBC41	6/6
OB2	6/-	5X4G	8/-	6C5G	5/-	6U4GT	10/6	12J7GT	7/6	50B5	7/-	DCC90	7/-	EBL1	14/-	EF94	6/-	EZ81	4/6	PY81	5/6	UBC81	7/-
OB3	6/-	5Z3	6/-	6C8G	7/-	6U8	7/6	12K7GT	7/-	50C5	6/6	DET12	40/-	EBL21	11/-	EF95	5/6	GZ30	8/6	PY82	5/-	UBF80	6/6
OC3	6/-	5Z4GT	8/-	6CB6	5/-	6V6	9/-	12K8	10/-	50CD6G	25/-	DF33	8/-	EC80	8/-	EF98	10/-	GZ32	10/-	PY83	6/-	UBF89	7/-
OD3	5/-	6/30L2	10/-	6CD6G	17/-	6V6G	5/-	12Q7GT	5/-	50L6GT	6/6	DF96	6/-	EC88	12/-	EF183	8/-	GZ34	10/-	PY88	8/6	UBL21	11/-
1A5GT	5/-	6A3	8/-	6CL6	9/-	6V6GT	7/6	12SA7	7/-	80	6/-	DF72	7/-	EC90	2/6	EF184	8/-	GZ37	9/-	PY800	8/6	UCC84	9/-
1A7GT	8/-	6A6	4/-	6CW4	12/-	6X4	4/-	12SG7	4/-	83	8/-	DF73	7/-	EC91	5/-	EFP60	10/-	KT66	15/-	PX25	10/-	UCC85	6/6
1AD4	7/-	6A8	8/-	6CY5	10/-	6X8GT	5/6	12SJ7	4/-	85A1	25/-	DF91	3/-	EC92	6/6	EL33	12/6	KT88	20/-	QQV03/10		UCF80	9/6
1B3GT	7/-	6AB4	6/6	6D3	7/6	6Y6G	6/-	12SK7	5/-	85A2	8/6	DF92	2/6	ECC31	5/-	EL34	10/-	MU12/14	8/-		35/-	UCH21	8/6
1G6GT	7/-	6AB7	4/-	6D4	15/-	7R7	12/-	12SY7	6/-	85A3	5/6	DF96	6/-	ECC32	4/-	EL35	5/-	N78	15/-	R2	8/-	UCH42	7/6
1H4GT	6/-	6AC7	3/-	6DK6	6/-	7R8	16/-	13D3	6/-	150B2	12/-	DH63	6/-	ECC40	9/-	EL36	9/-	N8P1	25/-	R10	15/-	UCL82	7/-
1H5GT	7/-	6AF4	11/-	6DS4	15/-	9BW6	7/-	19AQ5	5/-	150B3	8/-	DK32	8/-	ECC81	4/-	EL37	17/6	N8P2	22/-	R17	8/-	UCL83	10/-
1L4	2/6	6AG7	6/-	6E5	7/-	10C1	10/-	19G3	25/-	807	9/-	DK40	11/-	ECC82	5/-	EL38	17/6	OCP71	24/-	R19	7/-	UCL82	7/-
1L6	17/-	6AH6	10/-	6EV5	12/-	10C2	12/-	19G6	15/-	829B	60/-	DK91	5/-	ECC83	6/-	EL41	7/6	ORP12	12/-	RL18	12/6	UF41	7/6
1N5GT	8/-	6AK5	5/6	6F6	8/-	10D1	7/-	20F2	15/-	832	20/-	DK92	9/-	ECC84	6/6	EL42	8/-	ORP60	10/-	S130	12/6	UF42	7/6
1Q5GT	8/-	6AK6	7/-	6F7	5/-	10F1	14/-	20L1	14/-	954	5/-	DK96	7/6	ECC85	6/6	EL81	8/6	PC86	12/-	SU2150A		UF80	6/6
1R4	6/-	6AM5	2/6	6F8G	5/-	10F9	10/-	20P1	14/-	955	3/-	DL66	12/-	ECC88	10/-	EL83	7/-	PC88	12/-		10/-	UF85	7/-
1R5	5/-	6AM6	4/-	6F13	6/-	10F18	9/-	20P3	12/-	956	2/-	DL68	10/-	ECF80	7/6	EL84	5/-	PC97	9/-	TH41	10/-	UF86	10/-
1S4	5/-	6AN5	10/-	6F23	9/6	10L1	7/6	20P4	14/-	957	5/-	DL69	12/6	ECF82	7/6	EL85	8/-	PC84	5/6	TH233	6/-	UF89	6/-
1S5	4/6	6AQ5	6/-	6F24	11/-	10LD11	10/-	20P5	12/-	958	4/-	DL70	7/-	ECF86	11/-	EL86	7/6	PC85	7/-	TH2321	7/-	UL41	7/6
1T4	3/-	6AQ6	8/-	6F28	10/-	10P13	12/6	25A6G	5/-	959A	8/-	DL73	12/-	ECH21	10/-	EL90	6/-	PC88	10/6	TP22	5/-	UL84	6/-
1T5GT	6/-	6AR5	6/-	6F33	6/-	10P14	12/-	25Z4G	7/-	2051	6/-	DL92	5/-	ECH42	8/-	EL91	2/6	PCC89	10/-	TP25	5/-	UM4	10/-
1U4	5/-	6AR6	6/-	6J4	9/-	11D3	7/-	25Z5	7/6	5696	6/-	DL93	4/-	ECH81	6/-	EL95	6/-	PCC189	10/-	TP2620	7/6	UM80	7/-
1U5	6/-	6AS6	5/-	6J5G	4/-	11D5	7/-	25Z6GT	8/6	5763	12/-	DL94	5/6	ECH83	7/6	EM4	10/-	PCF80	6/-	TT15	35/-	UU5	8/-
1X2A	7/-	6AS7G	22/6	6J6	3/6	12AC6	8/-	27M1	60/-	6080	25/-	DL95	6/6	ECL80	6/6	EM31	5/-	PCF82	7/-	TT21	32/-	UU10	8/-
1X2B	7/-	6AT6	4/-	6J7G	5/-	12AH7GT		28D7	7/-	6146	27/6	DL96	6/-	ECL82	7/6	EM34	9/6	PCF84	8/-	TT22	32/-	UY21	8/-
2CW4	12/-	6AU6	6-	6J7GT	7/6		5/-	29C1	20/-	9002	5/6	DM70	5/-	ECL83	9/-	EM80	6/6	PCF86	8/-	TZ40	40/-	UY41	5/6
2D21	6/-	6AV6	6/-	6K7	5/-	12AH8	11/-	30C1	20/-	9003	9/-	DY86	8/-	ECL86	9/-	EM81	7/6	PCF801	10/-	U12/14	8/-	UY85	5/-
3A4	4/-	6B7	5/-	6K7GT	5/-	12AQ5	7/-	30C15	10/-	9003	9/-	E88CC	14/-	EF36	4/6	EM84	8/-	PCF806	13/-	U22	6/-	W81M	6/-
3A5	7/-	6B8	5/-	6K8	8/-	12AT6	5/-	30C17	12/-	A2293	15/6	E88CC	14/-	EF37A	8/-	EM85	9/-	PCL81	9/-	U25	11/-	X66	8/-
3B7	5/-	6BA6	4/9	6K8GT	8/-	12AT7	4/-	30F5	9/-	AZ1	9/-	E90CC	12/-	EF39	5/-	EM87	7/-	PCL82	6/6	U50	5/-	X79	18/-
3D6	4/-	6BE6	5/-	6L1	8/-	12AU6	6/-	30FL1	11/-	AZ12	9/-	E91H	12/-	EF40	9/-	EN31	10/-	PCL83	8/3	U76	4/-	Z66	10/-
3Q4	6/6	6BE6	6/-	6L6G	6/-	12AU7	5/-	30L15	12/-	AZ31	8/-	E92CC	7/-	EF40	9/-	EN32	10/-	PCL84	7/-	U191	11/-		
3Q5GT	6/6	6BH6	7/-	6L7	5/-	12AV6	6/-	30L17	13/-	AZ41	6/6	E180CC	8/-	EF41	7/6	EN92	6/-	PCL85	8/-	U251	12/6		
3S4	5/-	6BJ6	8/-	6L18	8/-	12AV7	8/-	30P12	10/-	CIC	5/-	E180F	15/-	EF42	6/-	EY51	7/-	PCL86	9/-	U281	13/-		
3V4	5/6	6BK7A	8/-	6N7	8/-	12AX7	6/-	30P19	14/-	CBL1	15/-	EABC80	6/-	EF54	6/-	EY70	12/6	PL36	8/6	U282	14/-		
4D1	4/-	6BN6	7/-	6P1	11/-	12AY7	10/-	30PL1	11/6	CBL31	16/-	EAF42	8/6	EF55	8/-	EY81	8/-	PL38	16/-	U301	12/-		
4THA	14/-	6BQ7A	8/-	6Q7G	6/-	12B4A	9/-	35L6GT	7/-	CL33	9/-	EB41	5/-	EF80	5/-	EY83	9/6	PL81	7/-	U403	7/-		
5RAGY	9/-	6BR7	11/6	6SC7	9/-	12BA6	6/-	35W4	5/-	CY31	6/6	EBC33	7/-	EF83	10/-	EY86	6/-	PL82	5/6	U801	18/-		
5T4	8/-	6BR8	8/-	6SG7	6/-	12BE6	5/-	35Z3	10/-	DAC32	7/-	EBC41	7/-	EF85	6/-	EZ35	5/6	PL83	6/-	U4020	7/6		
5U4G	5/-	6BS7	16/-	6SJ7	8/-	12BH7	8/-	35Z4G	4/-	DAF91	4/6	EBC81	6/6	EF86	6/-	EZ40	5/6	PL84	6/6	UABC80	5/6		
5U4GB	6/6	6BW6	9/-	6SK7GT	4/6	12BY7	10/-	35Z4GT	6/6	DAF92	6/-	EBF80	6/6	EF89	4/6	EZ41	6/6	PL500	15/-	UAF42	8/-		
5V4G	8/-	6BW7	9/-	6SL7GT	5/-	12F5GT	8/-	35Z5GT	6/-	DAF96	6/-	EBF83	7/6	EF91	4/-	EZ81	6/6	PL509	15/-	UBC41	6/6		

Mullard Transistors

OC26	8/-	OC44	6/-	OC72	8/-	OC139	12/-
OC28	17/6	OC45	6/-	OC75	6/-	OC170	8/-
OC35	15/-	OC70	5/-	OC76	6/-	OC171	9/-
OC42	8/-	OC71	5/-	OC77	8/-	OC204	10/6

Set of 2 matched
OC81 and 1 OC81D 12/6

R.C.A. TRANSISTORS: 2N410 (OC45), 3/6; 2N412 (OC44) 3/6.
G.E.C. TRANSISTORS: GET115, 7/-; GET573, 20/-, 35/- matched pair.
MICRO-ALLOY TRANSISTORS: MAT101 (60 Mc/s) 8/6; MAT121 (120 Mc/s) 8/6.
DIODES: OA81, 2/-; BYZ10, 7/6; GJ3M, GJ5M, GJ7M, 3/6.

All our valves carry three months guarantee.
Any faulty item replaced free of charge.

Write for full Catalogue of Valves and Tubes.

Please add 2/6 in £ for postage. Minimum charge 1/6.
Please address all correspondence to the Head Office.

FREE INSIDE NEXT MONTH'S Practical Electronics

2 DOUBLE SIDED BLUEPRINTS

TO BUILD

1. HIGH IMPEDANCE VOLTMETER

* * *

2. PHOTOTIMER

* * *

3. ELECTRONIC GUITAR







PLUS

4 MORE PAGES OF ELECTRONIC DATA

Other Outstanding Features including

Loudspeaker Enclosures for Transistor Amplifiers

FILL IN AND HAND TO YOUR NEWSAGENT

ORDER YOUR COPY NOW!

TO.....(Name of Newsagent)


Please send/reserve* PRACTICAL ELECTRONICS (2/6) every month, commencing with the January issue, on sale December 17th.

NAME .....

ADDRESS.....

.....

NEW PRODUCTS

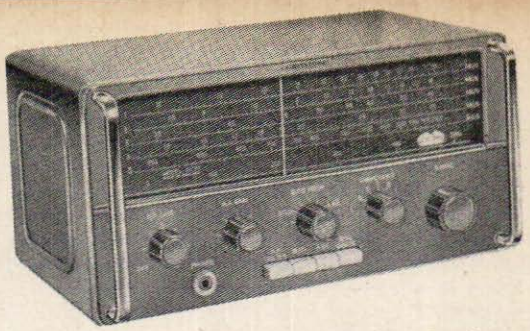


Communications Receiver

Stratton & Co. Ltd., Eddystone Works, Alvechurch Road, Birmingham 31.

A fully transistorised communications receiver which is in big demand is the Eddystone EC10. It has excellent performance throughout the 550kc/s to 30Mc/s range. Powered by six U2 type cells the current drain depends on the audio output, being 36mA quiescent, 77mA at 50 milliwatts output, and 180mA at 500 milliwatts. Independent r.f. and a.f. gain controls enable the gain to be balanced to suit strong or weak signals. As our photograph shows some of the controls are push button type. The b.f.o. pitch control has marked settings for reception of upper and lower sideband signals. The tuning control is flywheel-loaded and operates a gear drive with a reduction ratio of 110 to 1; frequencies are clearly marked on the large scale to a calibrated accuracy of within 1 per cent. Also, to allow dial settings to be recorded an auxiliary vernier and logging scale are incorporated in the tuning system.

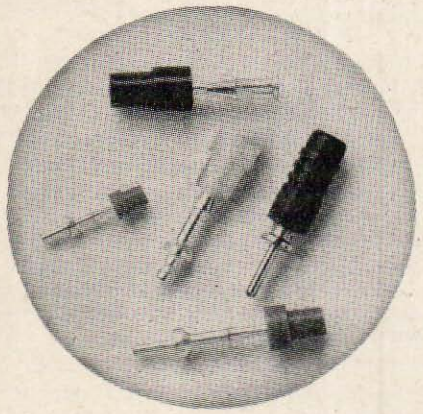The receiver is listed at £48 0s. 0d. in the U.K.



Miniature Insulators

Oxley Developments Company Ltd., Priory Park, Ulverston, Lancs.

It is easy for the amateur to purchase transistors, resistors and capacitors of miniature size. But try purchasing miniature accessories such as plugs, sockets and insulators for small work! Our photograph shows various types of miniature insulators, available to the amateur as well as professional, which are ideal for printed boards and perforated boards.


The same firm also manufacture miniature plugs, sockets and trimmers.

Recorded Lessons

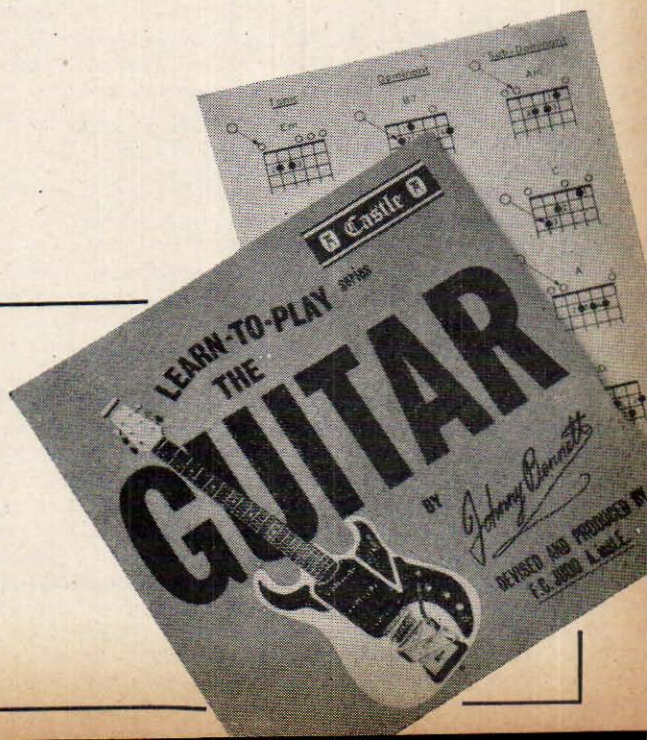F. C. Judd (Sound Recording) Ltd., 174 Maybank Road, South Woodford, E.18.

Since language courses on records have proved such a success to people who cannot spare the time for regular study F. C. Judd (Sound Recording) Ltd., are now producing a 10in L.P. record, in conjunction with Rapid Recording Ltd., entitled "Learn To Play The Guitar" by Johnny Bennett, price 25/-.

The record comes complete with modern chord guides, practice and tuning charts.



RETURN-OF-POST SERVICE

We offer a really efficient Mail Order Service on all items stocked. All cash orders are dealt with on the day of receipt.
● Hire purchase orders are subject to slight delay but this is kept to the absolute minimum.

● SPECIAL OFFER!! STEREO CARTRIDGES

RONNETTE 105 Stereo/Mono Cartridge. Complete with fixing bracket and styli. List 59/4. OUR PRICE **23/6.** Post Free.

● ILLUSTRATED LISTS

Illustrated lists are available on LOUDSPEAKERS, TAPE DECKS, TEST GEAR, GRAMOPHONE EQUIPMENT, AMPLIFIERS. Any will be sent free upon request.

● AMPLIFIER KITS

We have full stocks of all components for the Mullard 510, Mullard 3-3, Mullard 2 and 3 Valve Pre-amp. Mullard Stereo, Mullard Mixer.
Fully detailed list on any of these sent upon request.
Instruction Manual: All Mullard Audio Circuits in "Circuits for Audio Amplifiers", 9/5. Post free.

● LATEST TEST METERS

	Cash Price	Hire Purchase Deposit	Mthly/Pmts.
AVO Model 8 Mark III	**£24. 0.0**	**£4.16.0**	12 of **£1.15.2**
AVO Model 7 Mark II	**£22. 5.0**	**£4. 8.0**	12 of **£1.12.9**
AVO Multiminor Mark 4	**£9.10.0**	**£1.18.8**	12 of **14/4**
T.M.K. TP10	**£3.19.6**	**£1. 3.6**	3 of **£1.2.0**
T.M.K. TP5S	**£5.19.6**	**£1.15.6**	3 of **£1.11.4**
T.M.K. Model 500	**£8.19.6**	**£1.15.6**	12 of **13/8**
TAYLOR MODEL 127A	**£10.10.0**	**£2. 2.0**	12 of **15/8**

Full details of any of the above supplied free on request.
The AVO models 7 and 8 are both latest models from current production—not to be confused with Government Surplus.

● TAPE RECORDING EQUIPMENT

TAPE DECKS ALL CARRIAGE FREE	Cash Price	Hire Purchase Deposit	Mthly/Pmts.
COLLARO STUDIO, latest model,			
Two track, Bradmatic Heads	**£10.19.6**	**£2. 3.6**	12 of **16/4**
Four Track, Marriott Heads	**£17.17.0**	**£3.12.0**	12 of **26/2**

MARTIN TAPE AMPLIFIER KITS

Tape Amplifiers
For Collaro 8311-V 2-Track **£11.11.0.** 8311-4-V 4-Track **£12.12.0.**
Tape Pre-amplifiers
For Collaro 8319-CP 2-Track **£8.8.0.** 8319-4-CP 4-Track **£9.9.0.**
Drop through assembly for mounting 8319 Pre-Amp under Collaro Deck, **£1.11.6.**
Carrying Cases with speaker. For Collaro Deck and 8311 Amplifier, **£5.5.0.**
H.P. TERMS available on decks, amp. and cases. Ask for quote.

MULLARD TAPE PRE-AMPLIFIER KIT

We stock complete kits and all separate components for the Mullard Tape Pre-Amplifier. Fully detailed list available.

● GRAMOPHONE EQUIPMENT

ALL LATEST MODELS ALL POST FREE	Cash Price	Hire Purchase Deposit	Mthly/Pmts.
RECORD CHANGERS			
GARRARD AUTOSLIM (Mono PU fixed head)	**£6.17.6**	**£1.12.6**	6 of **£1**
GARRARD AUTOSLIM De-luxe AT6 (Mono PU)	**£11. 9.0**	**£2. 6.0**	12 of **16/11**
GARRARD AUTOSLIM AT6 (Stereo/Mono PU)	**£12. 5.4**	**£2. 9.4**	12 of **18/-**
GARRARD AUTOSLIM (Mono PU plug in head)	**£7.19.6**	**£1.10.6**	6 of **£1.4.0**
GARRARD A.T.5 (Mono PU plug in head)	**£10. 8.2**	**£2. 4.2**	12 of **15/4**
B.S.R. UA15 (TC8 Mono PU)	**£7.15.0**	**£1.18.0**	6 of **£1.2.0**
B.S.R. UA15 (TC8S Stereo/LP/78)	**£8.15.0**	**£2. 6.0**	6 of **£1.4.0**

Many of the above can be supplied for stereo working. See our Gramophone Equipment List for details.

● JASON F.M. TUNERS

We stock all parts needed for the construction of these excellent tuners. All parts can be supplied separately but we can offer attractive reductions in price if all items are purchased at same time as follows:

FMT2 (less power), £7.15.0.; FMT2 (with power), £9.12.6.
FMT3 (less power), £9.9.6.; FMT3 (with power), £11.7.6.
FMT1, £6.12.6.; Mercury 2, £10.14.6.; JTV/2, £14.12.6.
Hire Purchase Terms available. Ask for list.

● HI-FI LOUDSPEAKERS

GOODMANS: Axiette 8in., **£5.5.7;** Axiom 10in., **£6.5.11;** 12in. Axiom 201, **£10.17.4;** 12in. **Axiom 301, £15.4.6;** 12in. **Audiom 51 Bass, £9.2.8;** 12in. **Audiom 61 Bass, £14.7.8; Trebax Tweeter, £6.10.2; XO5000 Crossover unit, £2.0.11.**
WHITELEY: HF1016 10in., **£7.7.0; HF1012** 10in., **£4.12.0; HF816** 8in., **£6.6.0; T816** 8in., **£5.19.6; T10 Tweeter, £4.12.0; T359 Tweeter, £1.12.3; CX3000 Crossover unit, £1.13.3; CX1500 Crossover unit, £2.2.0.** H.P. Terms available on all speakers.

● OUTPUT TRANSFORMERS

GILSON: W0696A, W0696B, **60/6,** post 2/6. W0892, **75/-,** post 2/9. W0767, **32/6,** post 1/6. W01796, **66/-,** post 2/6. W1796A, **66/-,** post 2/6. W01932, **92/6,** post 3/-.
PARTRIDGE: P3667, **75/-,** post 2/9. P4131, **75/-,** post 2/9.
PARMEKO: P2629, **49/9;** P2642, **47/3;** P2643, **49/9.** All plus post 2/9. P2641 **30/9,** post 2/-; P2928, **16/9,** post 2/-; P2932, **43/-,** post 2/6.

● MAINS TRANSFORMERS

GILSON: W0741A, **75/-,** post 4/-; W0839, **58/6,** post 2/9; W01328, **69/6,** post 3/6; W01288, **69/6,** post 3/6; W01566, **96/-,** post 4/6; W01341, Choke, **43/-,** post 2/-.
PARMEKO: P2631, **37/-,** post 2/9; P2630, **57/3,** post 3/3; P2644, **80/-,** post 4/-; P2930, **43/-,** post 3/-; P2931, **59/6,** post 3/3.

WATTS RADIO (Mail Order) LTD

54 CHURCH STREET, WEYBRIDGE, SURREY

Telephone Weybridge 47556

Please note: Postal business only. Callers welcome by appointment.

★ TERMS OF BUSINESS

Cash with order or C.O.D. We charge C.O.D. orders as follows: Up to **£5** minimum of 4/2. Over **£5** and under **£10,** 2/8. Over **£10,** no charge. **Postage extra on CASH order under £5 except where stated. Postage extra on overseas orders irrespective of price.**

★ HIRE PURCHASE TERMS AVAILABLE

EXCEL in ELECTRONICS

Through this ICS 3-way Training Method:

1 MASTER THE THEORETICAL SIDE

From basic principles to advanced applications, you'll learn the theory of electronic engineering, quickly and easily through ICS. That's because each course is set out in easy-to-understand terms.

2 MASTER THE PRACTICAL SIDE

ICS show you how to develop your practical abilities in electronic engineering—*alongside* your theoretical studies. It's the only sure way to success. All training manuals are packed with easy-to-follow illustrations.

3 MASTER THE MATHEMATICAL SIDE

To many this aspect is a bitter problem. Even more so because no electronic engineer is complete without a sound working knowledge of maths. But new ICS teaching makes mathematics easier to learn.

Wide range of courses available include:
Radio/T.V. Engineering and Servicing, Colour Television, Electronics, Electronics Maintenance, Instrumentation and Servomechanisms, Telemetry, Computers, etc.
NEW! Programmed Course on Electronic Fundamentals.

EXPERT COACHING FOR:

INSTITUTION OF ELECTRONIC AND RADIO ENGINEERS
CITY AND GUILDS TELECOMMUNICATION TECHNICIANS
CITY AND GUILDS SUPPLEMENTARY STUDIES
R.T.E.B. RADIO/T.V. SERVICING CERTIFICATE
RADIO AMATEURS' EXAMINATION
P.M.G. CERTIFICATES IN RADIOTELEGRAPHY

And there are practical "learn as you build" radio courses as well.

Member of the Association of British Correspondence Colleges.

FOR **FREE** HANDBOOK POST THIS COUPON TODAY

I.C.S., Dept. 151, INTERTEXT HOUSE, PARKGATE ROAD, LONDON, S.W.11

NAME .....

ADDRESS .....

.....

OCCUPATION ..... AGE 12.64

INTERNATIONAL CORRESPONDENCE SCHOOLS

LINEAR

FOR AUDIO — EQUIPMENT

HIGH SENSITIVITY — **HIGHEST FIDELITY**

MAXIMUM RELIABILITY — **REASONABLE COST**

We regret to announce that after maintaining our prices for seven years (with the exception of one unit) we are reluctantly announcing a revised price list.

L.50. 50 watt Amplifier approximately 14 x 10 x 8 in. Sensitivity 25 m.v. output for 3 and 15 ohm Speakers. *Retail price* **22 guineas.**

CONCHORD. 30 watt Hi-Fi Amplifier with two separately controlled inputs. *Retail price* **17 guineas.**

L.10. 10 watt Hi-Fi Amplifier with separate pre-amp. *Retail price* **16 guineas.**

L.1/10. 10 watt Hi-Fi amplifier with integral pre-amp. *Retail price* **13½ guineas.**

DIATONIC. 10/14 watt Hi-Fi Amplifier with integral pre-amp *Retail price* **12½ guineas.**

L.5/5. Stereophonic Amplifier. Output 5 watts each channel. *Retail price* **12½ guineas.**

L.T.45X. Tape Amplifier with equalisation adjustment for 1⅞, 3¾ and 7½in. per second. Suitable for Collaro Studio Tape Transcriptor. Complete with integral power pack. *Retail price* **12½ guineas.**

LP.1 Tape Pre-Amplifier. As above but less power pack facilities. *Retail price* **9½ guineas.**

L.45A. 4/5 watt Amplifier. *Retail price* **6 guineas.**

L.G. 34. 3/4 watt Amplifier. Shelf mounting type for gram use. *Retail price* **£5.10.0.**

TREMOLO UNIT. For Guitar purposes to plug into mains Amplifier. *Retail price* **4 guineas.**

Trade and Export Enquiries invited—

LINEAR PRODUCTS LTD. **ELECTRON WORKS ARMLEY, LEEDS.**

Tel. Leeds 63-0126 (3 lines).

S.A.E. for catalogue.

JOY'FUL NEWS No. 2

"AMAZING! FANTASTIC!"

These are the superlatives most commonly used by our customers.

"JOYMATCH TYPE 3"

An extremely robust and compact H.F. BAND aerial matching unit for receivers and L.P. transmitters. Unbelievably peaks all amateur and H.F. signals from 30 Mc/s. to Radio Luxembourg on 208 M.
YOU WILL ASK YOURSELF HOW YOU HAVE EVER MANAGED WITHOUT IT!
AMAZING VALUE 39/6 plus 1/6 p. & p.

"JOYMATCH TYPE 2"

Similar to above but mainly intended for the MEDIUM WAVE BROADCAST BAND. BRINGS WEAK DISTANT STATIONS IN LIKE LOCALS! Covers all frequencies, 30 Mc/s. to 530 Kc/s. Bring those weak stations **ROARING IN!!!**
45/- plus 2/- p. & p.

THE FABULOUS "JOYSTICK"


variable frequency aerial

The WORLD FAMOUS, sensational, unique **"JOYSTICK"** all band aerial—short waves, medium waves, amateur and broadcast, transmit and receive, just 7ft. 6in. long. The flat dweller's dream aerial. World patents pending. £3 10s. 0d. carr. paid. Testimonials galore.

All the above products are covered by our MONEY BACK GUARANTEE


PARTRIDGE ELECTRONICS LTD.
7 SOWELL ST., BROADSTAIRS
KENT, ENGLAND

BBC2 (625 LINE) TV AERIALS

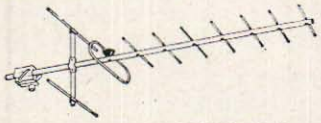

MAST MOUNTING ARRAYS, 9 element 45/-; wide spaced high gain, 11 element 55/-; 14 element 62/6. **WALL MOUNTING WITH CRANKED ARM,** 9 element 60/-; wide spaced high gain, 11 element 67/6; 14 element 75/-. **CHIMNEY ARRAYS COMPLETE,** 9 element 72/-; wide spaced high gain, 11 element 80/-; 14 element 87/6. **LOFT ARRAYS,** 7 element 32/6; wide spaced high gain, 11 element, **WITH TILTING ARM** 62/6; 14 element 70/-. **ALL HIGH GAIN UNITS HAVE SPECIAL MULTI-ROD REFLECTOR. LOW LOSS CO-AXIAL CABLE** 1/6 yd.

BBC + ITV + F.M. AERIALS

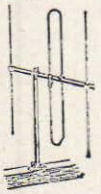

B.B.C. (BAND 1). Telescopic loft 21/-. External S/D 30/-.

I.T.V. (BAND 3). 3 Element loft array 25/-. 5 element 35/-. Wall mounting, 3 element 35/-. 5 element 45/-.

COMBINED B.B.C./I.T.V. Loft 1+3, 41/3; 1+5, 48/9. Wall mounting 1+3, 56/3; 1+5, 63/9. Chimney 1+3, 63/9; 1+5, 71/3.

F.M. (BAND 2). Loft S/D, 12/6. "H", 30/-. 3 element, 52/6. External units available. Co-ax. cable 8d. yd. Co-ax. plugs, 1/3. Outlet boxes, 4/6. Diplexer Crossover Boxes 12/6. C.W.O. or C.O.D. P.P. 3/-. Send 6d. stamps for illustrated lists.

K.V.A. ELECTRONICS (Dept. 2)
3b, Godstone Road, Kenley, Surrey.
CRO 2527

ELECTRONICS DATA HANDBOOK, by M. Clifford. 23/-. Postage 1/-.

UNDERSTANDING TUBE & TRANSISTOR CIRCUITS. Foulsham-Sams. 35/-. Postage 1/-.

TRANSISTOR IGNITION SYSTEMS HANDBOOK, by B. Ward. 20/-. Postage 9d.

UNDERSTANDING & USING TEST INSTRUMENTS. Foulsham-Sams. 35/-. Postage 1/-.

BASIC MATHEMATICS FOR RADIO & ELECTRONICS, by F. M. Colebrook & J. W. Head. 17/6. Postage 9d.

BASIC THEORY & APPLICATIONS OF TRANSISTORS. U.S. Dept. of Army. 10/-. Postage 1/-.

HI FI YEAR BOOK, 1964, 10/6. Postage 1/-.

RADIO ELECTRONICS, by S. Seely. 37/6. Postage 1/-.

HANDBOOK OF ELECTRONIC TABLES & FORMULAS. D. Herrington & S. Meacham. 15/-. Postage 9d.

REFERENCE MANUAL OF TRANSISTOR CIRCUITS, by Mullard. 12/6. Postage 1/-.

RADIO & TELEVISION TEST INSTRUMENTS, by G. J. King. 25/-. Postage 1/-.

RADIO VALVE DATA 7th Ed. Compiled by "WW". 7/6. Postage 10d.

COMPLETE CATALOGUE. 1/-.

THE MODERN BOOK CO.


BRITAIN'S LARGEST STOCKISTS
of British and American Technical Books

19-21 PRAED STREET
LONDON, W.2

Phone: PADdington 4185
Open 6 days 9-6 p.m.

BEGINNERS start here... 2

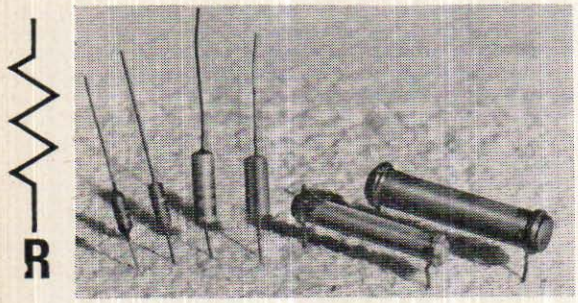An Instructional Series for the Newcomer to Electronics



CARBON RESISTORS

A WORD or two now about *practical* resistors as used in electronic equipment. Last month we mentioned that wire wound resistors are not usually made in values greater than 100,000 ohms. In fact, the kind of resistor most commonly encountered in electronics is of the *carbon* fixed value variety.

Wire wound resistors have rather limited and specialised applications: they are used whenever a *precise* value of resistance is required; also as "voltage droppers" in power supply circuits, where high currents and voltages are involved. And of course, wire wound resistors suit our requirements perfectly in the present series of experiments.

One important thing to remember. All the basic laws that we are demonstrating for ourselves in this series of experiments hold good for all types of resistors —no matter whether they be made of wire, or of carbon or any other substance.

Last month we showed a group of typical wire wound resistors. This month our photograph shows a selection of carbon fixed-value resistors. These are the kind of components you will constantly be handling as you become involved in building electronic devices. A word or two about their characteristics—physical and electrical—will not be out of place at this stage.

There are two main types; carbon composition and carbon film.

Carbon *composition* resistors consist of a rod of carbon black or graphite. Connecting wires are wrapped around the ends of the rod and the latter is given a protective coating of paint. This type is known as *non-insulated.*

There are also insulated composition resistors. These are made by enclosing the rod of resistive material in a plastics moulding or ceramic tube. The connecting wires emerge straight out from the ends of the tube.

The film type of resistor is made by depositing a thin film of a carbon mixture upon a glass or ceramic tube or rod. The rod is encased in moulded plastics or in a ceramic tube. Outwardly, these resistors resemble the insulated composition type.

Most carbon resistors are colour coded. This colour code indicates the value in ohms and sometimes provides additional information. You will find the PRACTICAL ELECTRONICS Colour Code Calculator (presented with our first number) an extremely useful tool. If you have access to an assortment of resistors, it is a good idea to practice reading off the colours of a randomly selected component. Take our word for it—this will be to your benefit in the future.

RESISTORS IN PARALLEL

Our next exercise is to find out what happens when we connect resistors in parallel, that is, side by side instead of end to end. To do this you will need to connect the "shorting wire" of the last experiment to points A and C of the resistor and the slider contact to point B (see Fig. 2.1). You will find that the slider can be moved along the resistor from end to end and the bulb will now light all the time. Why is this so?

To enable you to understand quite clearly the present circuit arrangement, we have drawn an "intermediate" diagram: imagine the end A of the resistor bent back so that it nearly touches end C (Fig. 2.2), as you move the slider from the central position towards one end you are reducing the resistance of that branch and so increasing the current flow. The circuit is shown in its final and conventional form in Fig. 2.3.

As the bulb lights now at all positions along the resistor, it follows that the total resistance must be much less than the original short section (11cm) measured in the first experiment. Once again, we can calculate the value of the total resistance using a formula:

$$\frac{1}{R\ total} = \frac{1}{R1} + \frac{1}{R2}$$

Your resistance element has an approximate value of 75–80 ohms and hence you can mark the baseboard into divisions of, say, 5 ohms each. By setting the slider at any random point you can now read off the value of resistance either side of it. If the slider is set at 20 ohms (R1), the remaining resistance (R2) will be 60 ohms. Substituting these values in the above formula we get

$$\frac{1}{R\ total} = \frac{1}{20} + \frac{1}{60} = \frac{3+1}{60} = \frac{4}{60} = \frac{1}{15}$$

$$R\ total = 1/_{15} = 15\ ohms.$$

We would like you to work out half a dozen calculations (one has already been done for you!) taking the value of R1 as 5 ohms, 10 ohms, 15 ohms, etc. and make a small list showing the values of R total, R1 and R2. You should find that the value of R total goes from 17½ ohms down to nearly 1 ohm.

You will see from this list that, when R1 is much smaller than R2, the total resistance or *equivalent*

resistance is nearer R1 in value than R2. This can be very important in electronic circuits when you have a component with a resistance of perhaps 1,000 ohms in parallel with another component of 1 megohm. Let's do another calculation to show why:

$$\frac{1}{\text{R total}} = \frac{1}{1{,}000} + \frac{1}{1{,}000{,}000} = \frac{1{,}000+1}{1{,}000{,}000}$$

$$= \frac{1{,}001}{1{,}000{,}000}$$

Thus

$$\text{R total} = \frac{1{,}000{,}000}{1{,}001} = 1{,}000 \text{ ohms approximately.}$$

You can see then that if the value of one resistance is very high you can ignore it and consider only the value of the small one.

SECOND RESISTANCE ELEMENT

Now it is necessary to add the second resistance element to our apparatus. Here we use a 1,000 watt (1 kilowatt, or 1kW) fire element. Push the spare plastics knitting needle through the vacant hole in one of the wooden support pieces, thread it through the coiled element and insert in the hole provided in the second support. Ensure that the turns of wire are evenly spaced along the length of the needle.

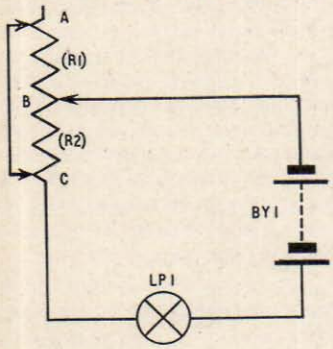


Fig. 2.1. The shorting wire is connected across the resistance element and sections R1 and R2 are thus in parallel

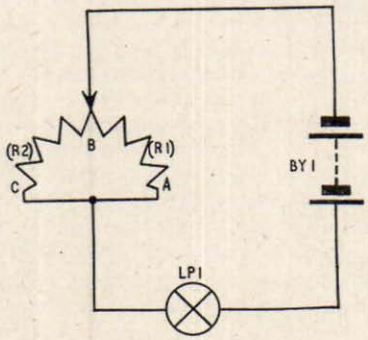


Fig. 2.2. This is the same set-up as Fig. 2.1 but the diagram has been redrawn to show more clearly the fact that R1 and R2 are in parallel

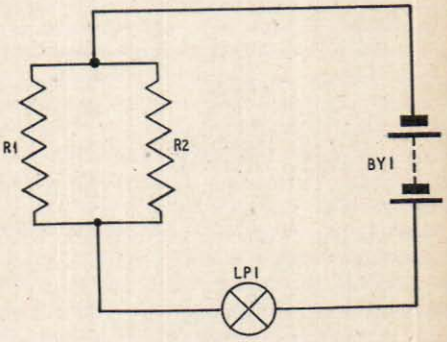


Fig. 2.3. Here, finally, the circuit is drawn in the normal, conventional manner

THE UNIT OF POWER

You may be wondering at this moment: what is meant by a kilowatt?

The basic unit of a watt is the unit of power that is the rate of doing work. To calculate the power in an electrical circuit you must multiply the voltage by the current; this is shown by the formula:

$$W = V \times I$$

where W stands for watts, V for volts, and I for current in amperes.

If you are unable to measure the voltage but know the resistance then you can use a second formula, which is

$$W = I^2 \times R \text{ (or } W = I \times I \times R)$$

A third form of the equation is

$$W = V^2 \div R \left(\text{or } W = \frac{V \times V}{R}\right)$$

If you look at the list of components in other articles in PRACTICAL ELECTRONICS, you will notice that resistors are quoted at $\frac{1}{4}$W, $\frac{1}{2}$W, 1W, etc. This is as important in electronic circuits as having the correct value of resistance (in ohms). Say, for example, you had a resistance of 100 kilohms and a voltage of 300V, then the current flowing through it would be

$$\frac{300}{100{,}000} = 0{\cdot}003 \text{ amperes or 3mA.}$$

Working out the power as above ($W = V \times I$) would give

$$300V \times 0{\cdot}003A = 0{\cdot}9W$$

You would thus need a resistor rated at 1 watt and if you used one of perhaps $\frac{1}{2}$ watt or $\frac{1}{4}$ watt then it would quickly overheat and break down. This heat is caused by the current flowing through the resistor and we use this to our advantage in electric fires, water heaters and electric light bulbs.

The higher the wattage rating of a carbon resistor, the larger its physical size. Refer to the photograph: the two smallest sized resistors are $\frac{1}{4}$W types, the next pair are $\frac{1}{2}$W, and the other two 1W and 2W respectively.

Now to return to the experiments. If you have the two fire elements or coils wound on the needles you can experiment on your own by connecting them in different ways, shorting out sections of them and calculating the value of resistance in circuit. The 1kW coil will have a resistance between 50 and 55 ohms so you can mark out the base board in equal sections and measure off the resistance values direct.

You may also like to see the effect of increasing and decreasing the voltage to 6 volts and 3 volts respectively by substituting other batteries for the present $4\frac{1}{2}$ volt battery. If you increase the voltage you will need more of the resistance in circuit to get the bulb just glimmering as compared with the amount needed with the $4\frac{1}{2}$V supply. Obviously then you will have less resistance in circuit when a 3V battery is used.


We have used a bulb to indicate that current is flowing through the circuit and our next project is to make a simple type of meter that also tells us current is flowing. Many of you may have seen and used meters at school and know that there are many different types to measure voltage, current, resistance, etc.

Next month we will show you how to make a simple meter that you can set up with your battery and use for approximate measurements in later experiments.

SHOPPING LIST

One 1,000 watt electric fire replacement element.

EXCLUSIVE OFFER TO ALL OUR READERS !

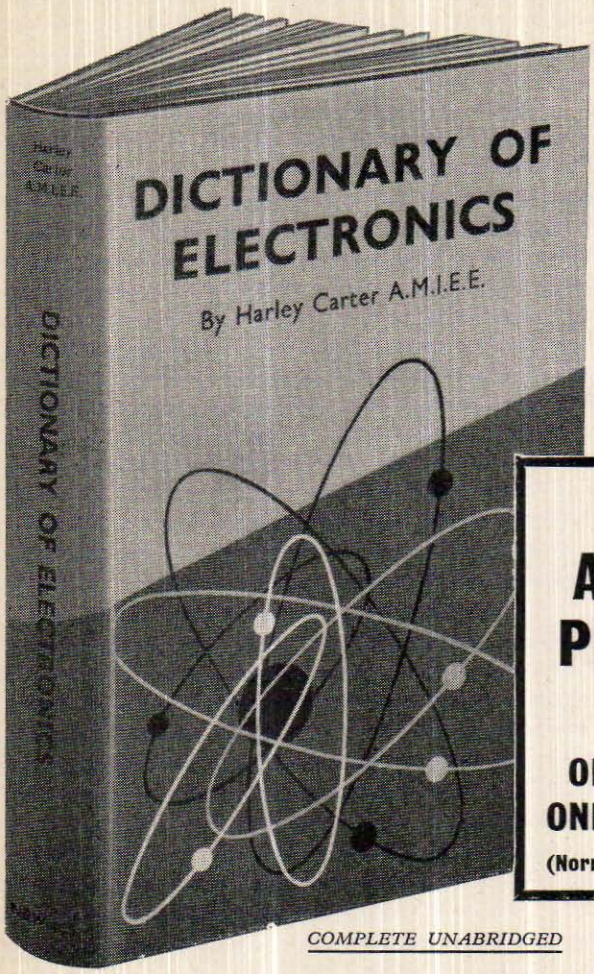

Special Edition of

DICTIONARY OF ELECTRONICS

by HARLEY CARTER, A.M.I.E.E.

AT THE AMAZING PRIVILEGE PRICE OF ONLY 10/6

(Normal Edition sells at 35s.)

AN INDISPENSABLE DESK REFERENCE VOLUME FOR ENGINEERS TECHNICIANS EXECUTIVES APPRENTICES AND STUDENTS

COMPLETE UNABRIDGED

★416 PAGES★ WITH EXTENSIVE CROSS-INDEXING

★265 DRAWINGS★ & CIRCUIT DIAGRAMS

This comprehensive Dictionary contains concise, explanatory definitions of all facts and terms related to Radio, Television, Communications, Radar, Industrial Electronics, Instrumentation and other branches of Electronics. Also sections on Units and Abbreviations; Greek Letters used in Electronics; List of Symbols; Graphical Tables; The Electro Magnetic Spectrum; Frequency Wave-Length Conversion; Valve Bases; Rationalised M.K.S. Units. This unique work will be of continual use to all whose work or interest requires them to understand modern electronic terminology.

COMPLETE AND SEND ORDER FORM OVERLEAF!

Pack the space between the transducer and the wall of the top cap with foam rubber. A piece of ½in thick material, cut into a strip measuring approximately ¾in × 4in should serve this purpose adequately. Other similar material may be used, the important factor being to wedge the transducer firmly and centrally within the case.

Returning now to the bottom end of the case, first check that the battery can be accommodated inside, and recessed at least ⅛in from the bottom edge. If not, the transmitter assembly must be pushed gently upwards, but without, if possible, disturbing the transducer.

Solder a 1½in long lead (red coloured sleeving) to the metal strip which makes contact with the metal rim of the case. Fit the battery, base foremost, inside, ensuring that the blue and red leads are not trapped.

These two battery leads should extend about 1½in from the bottom of the case; cut off any surplus and solder these leads to the battery press stud connectors observing the correct polarity, i.e. red for positive, blue for negative.

Fit the connectors to the battery terminals and carefully push down the looped ends of the leads.

From a piece of stout cardboard, cut out a disc approximately ⅞in diameter. Place this disc over the battery before screwing on the end cap.

This cardboard insulating disc is essential, since the spiral spring connector in the end cap will be connected to the positive side of the battery when the cap is screwed home. The insulating disc prevents the spring coming into contact with the negative battery terminal—if this should happen the battery will be shorted.

SETTING UP

Place the transmitter so that its transducer is looking directly at the receiver transducer, and the two are not more than a couple of feet apart.

Connect an ohmmeter to the relay contacts, and connect the receiver battery.

Switch on the transmitter. Rotate the core of T1 until the relay operates, as indicated by zero reading on the ohmmeter. Withdraw the transmitter further from the receiver while making adjustments to T1 in order to obtain the optimum tuning point.

When the receiver is correctly adjusted, the relay should pull in at a current not exceeding 5mA with a d.c. supply of 4½V.

The receiver should response at a distance of at least 20ft from the transmitter.

This range can, however, be increased upwards to 100ft if OC44 transistors are used in the first three stages of the receiver (TR3–TR5) and simple cones are placed over the transducers. Paper cones tapering out to about 6in are quite effective for this purpose. ★

COMPONENTS . . .

Resistors

R1	8·2kΩ	R8	10kΩ	R14	10kΩ
R2	1kΩ	R9	100Ω	R15	560Ω
R3	5·6kΩ	R10	30kΩ	R16	12kΩ
R4	22kΩ	R11	47kΩ	R17	1·5kΩ
R5	1kΩ	R12	4·7kΩ	R18	15kΩ
R6	2·2kΩ	R13	12kΩ	R19	10kΩ
R7	5·6kΩ				

All ¼W carbon

Capacitors

C1	3,300μF silver mica	C5	22μF elect. 25V
C2	0·015μF disc ceramic	C6	0·015μF disc ceramic
C3	0·1μF disc ceramic	C7	5,000pF disc ceramic
C4	22μF elect. 25V	C8	1μF elect. 25V
		C9	50μF elect. 25V

Transistors

TR1–7 OC71 (7)

Miscellaneous

RLA Relay, 400Ω 5mA
T1 H.F. transformer (Osmor type QHF9)
X1, 2 Transducer (Gulton type 1404)
BY1 9V battery, Ever Ready PP3 or Exide DT3
BY2 9V battery
Two miniature coaxial plugs
Veroboard : one piece 4in × 4½in; two pieces 1½in × ¾in

Note: The Gulton transducers, the reed relay, and other essential components can be obtained from: DTV Group, 126 Hamilton Road, West Norwood, London S.E.27

DICTIONARY OF ELECTRONICS

*

ORDER FORM

To George Newnes Ltd., 136 Long Acre, London, W.C.2.

Please send me DICTIONARY OF ELECTRONICS. I enclose remittance for 10s. 6d.

NAME .....

ADDRESS .....

.....

I have/have not* reserved a copy on the Reservation Form in last month's "Practical Electronics".

*Delete as applicable

L. K. ELECTRONICS

The Cheapest — The Best

The Quickest Service

● **Famous Autochanger or Single Player Units** supplied with brand new, two-tone, de-luxe portable cabinets, 17×15×8½in. Strong carrying handle, gilt finish clips and hinges are used by famous make for 22 gn. model. Ready cut out motor board, 14×13in. Front baffle 7×4in. High flux loudspeaker and 3 watt amplifier. Amplifier ready built on metal chassis with output transformer, volume and tone controls. All items fit together perfectly. Assembly in 30 minutes. Only 5 wires to join. 12 months' written guarantee. Available separately or package deals as below.
Our NEW MK II Superb Kits are now being dispatched.

L K PRICES FOR COMPLETE KITS:

Autochanger Kits as above

B.S.R. U.A. 14, T.C. 8 Mono	**£10.17.6**	P.P. 5/6
Garrard Autoslim, Mono	**£11.7.6**	P.P. 5/6

Single Player Kits as above

Garrard S.R.P. 10, Mono	**£10.12.6**	P.P. 5/6
E.M.I. Autostop, Mono	**£10.17.6**	P.P. 5/6

Individual Prices for those who wish to purchase separately.

Record Player Cabinet with Cut-out Board	**£2.15.0**	P.P. 3/6
Amplifier with 7×4in. speaker	**£3.10.0**	P.P. 2/6

● **SCOOP! B.S.R. U.A. 25 Autochangers.** T.C. 8 Mono P.U. Brand new and boxed. Wired for stereo. Note **OUR** price **£5.7.6.** P.P. 5/-. The very, very latest model.

● **SCOOP! B.S.R. U.A. 14 Autochangers.** T.C. 8 Mono P.U. Brand new and boxed. Wired for stereo. Note **OUR** price **£5.7.6.** P.P. 5/-. Latest model.

● **SCOOP! Garrard Autoslim.** Mono P.U. Brand new and boxed. Wired for stereo. Latest model. Note **OUR** price **£6.0.0** only. P.P. 5/-.

● **SCOOP! Garrard A.T.5.** Wired for stereo, inclusive of head and mono cartridge (A.T.5 is an auto transcriptor). The finest changer of them all. **OUR** price, brand new and boxed, **£7.10.0** only. P.P. 5/-.

AUTOCHANGERS

Single Players

E.M.I. Autostop, Mono	**£5.7.6**	P.P. 4/6
Garrard S.R.P. 10, Mono	**£5.5.0**	P.P. 4/6
E.M.I. Separate Pick-up	**£3.0.0**	P.P. 3/6

Transcription Units—Stereo Head—Mono

Garrard 4 H.F. Stereo	**£14.10.0**	P.P. 5/-
Philips A.G. 10/16. Stereo	**£12.0.0**	P.P. 5/-
Garrard A.T.6, Stereo	**£9.19.6**	P.P. 5/-
Garrard 301	**£16.10.0**	P.P. 5/-

● **SCOOP! Record Player Cabinets.** Two-tone, de-luxe finish with cut-out board. These are brand new and product of very famous national manufacturer. **OUR** price **£2.15.0** only. P.P. 3/6.

● **SCOOP! 3-watt Gramophone Amplifier.** Complete with 5in. Speaker, **49/6.** P.P. 5/-.
The amplifier is complete, on a fabric-covered baffle board. Output transformer included. Tone and volume controls and on/off switch. Ready to switch on and play. Terrific volume. Size 12½in.×6in.×3½in. back to front. For 200-250 v. A.C. Output 3 watts.

● **SCOOP!** Diodes—over 1,000,000 in stock—ideal substitute O.A.81 vision detector.
Note **OUR** price **£1.0.0** per 500. P.P. 2/-. (In 500 lots only).

● **SCOOP! Transistor Tape Recorder.** The best obtainable by very famous manufacturer. Brand new, boxed, guaranteed. Reduced from 12 gns. **OUR** price **£7.10.0.** P.P. 3/6. Complete with microphone, tape, batteries and operational booklet. Features push-pull amplifier, two motors, single switch operation, pause, speed, wind, rewind, record, play back. Can be used in any position, indoor or outdoor.

● **SCOOP! Hi-Fidelity Speakers,** 15-watt. Very famous national manufacturer—we cannot mention name. 45-13,000 c.p.s., 3 or 15 ohm voice coils, response 45–13,000 c.p.s. Magnet 15,000 lines. In carton—unopened and unused. **OUR** price **£4.4.0** only.

● **SCOOP! A Stereophonic Amplifier** with the following features. A twin gauged tone control in a special negative feedback circuit, giving a wide range of tone correction. A balance control enabling the amplifiers to be equalized in output to compensate for pick-up, lead, speakers, recording differences. A speaker switch. M1, single amplifier. M2, dual amplifiers for increased Monaural output. S.3, two speakers at 5 watts per channel. Twin gauged volume controls and all four controls placed equidistant along the front of the chassis. Designed, made and guaranteed by Brittamer Ltd. Brand new and at a fraction of original cost. **OUR** price **£7.10.0** only.

● **SCOOP! Cartridges — Ceramic Diamond Stylii — Stereo — By Acos.** Limited Number only at one ¼ of original price—**10/- only** + P.P. 1/-. While stocks last.

● **SCOOP! 1964 Radiogram Chassis. Stereo** 3-wave bands, long, medium, short. 5 watts per channel. 6 valves. Latest Mullard A.C. 200/250 v. Ferrite aerial. Glass dial. Horizontal wording. Size 13in.×4in. Aligned and calibrated. Concentric controls. Isolated chassis. Size 13½in.×9in. high × 5in. deep. Product of famous national manufacturer. Brand new and boxed. Maker's guarantee.
OUR price **£13.10.0.** List price £19.8.0. P.P. 5/6. Our Chassis List quotes prices—the keenest in the Trade. We are Main Agents for the complete range of Brittamer Chassis and Amplifiers. "Brittamer"—makers of Radiogram Chassis to the Top Names in Radio.

● **SCOOP!** For **£25.0.0** only. A fabulous offer. **Garrard A.T.5 Transcriptor,** plus 2 12in. 15 watt Hi-Fidelity speakers, plus the very latest Continental push-button chassis by Brittamer. Stereo, 3-wave band, 6 valves, 5 watts per channel. The finest chassis of its type in the world. You will be amazed at performance and quality. We unhesitatingly recommend this chassis.

● **SCOOP!** Limited number only. **Miniature Superhet 4-valve Portable Radios.** Ferrite rod aerial. Hide leather case. Complete with valves, speaker and circuit. To clear **OUR** price **50/-** only. Cannot be repeated.
Speakers ex Equipment. 5in. **5/-,** 7in.×4in. **6/-,** 6in. **6/6,** 8in. **7/-.** P.P. 1/6 each.

● **SCOOP! Microphones.** Complete Lead Coax. Plug, Brand New. **OUR** price **5/-** only. P.P. 1/6.

TRANSISTOR SECTION

● **SCOOP!** A first-class **2 wave-band 3 transistor superhet chassis** by world famous manufacturer. Fully built, aligned, tested, guaranteed. Full coverage long and medium waves. Note **OUR** price **£5.4.0** only. Suitable speaker **10/6.** A few cabinets can be supplied at **22/6** each. **OUR** price for the package deal **£6.10.0** only. Ideal for Caroline.

● **SCOOP!** A Limited Number Only. **Tape Decks by B.S.R.** Latest model. A.C./200/240 v. Brand new and boxed.
OUR price **£6.10.0** only. P.P. 4/6.

● **SCOOP! Tape Recorder Amplifiers.** Suitable for B.S.R. or Collaro Decks. Price: **£6.10.0** for B.S.R. Deck; **£6.12.0** for Collaro Deck. P.P. 6/-.
Mk. III. Fully built, high gain, low noise, printed circuit. The amplifier is supplied complete with the switch wafer fully wired for B.S.R. deck. For Collaro deck, a completely wired separate switch with spindle is supplied. Magic Eye.
S.A.E. enquiries please. Our Complete Lists 1/- only—credited against your order

● **IF NOT ADVERTISED IT IS STILL IN STOCK**

L.K. ELECTRONICS (Victoria) LTD.

★ **17 GILLINGHAM ROW, WILTON ROAD, LONDON, S.W.1.** ★

Practical Electronics Classified Advertisements

The pre-paid rate for classified advertisements is 1/- per word (minimum order 12/-), box number 1/6 extra. Semi-displayed setting £3.5.0 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL ELECTRONICS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Advertisement Manager, PRACTICAL ELECTRONICS, George Newnes Ltd., Tower House, Southampton Street, London, WC2, for insertion in the next available issue.

SERVICE SHEETS

GENUINE SERVICE SHEETS, Radio/TV/T Recorders. S.A.E. with enquiries: REDWATT ELECTRICAL, 41, Denmark Street, Wakefield, Yorks.

SERVICE SHEETS, Radio, TV, etc.: List 1/-. S.A.E. Enquiries: TELRAY, Maudland Bank, Preston.

STATE MODEL NO. Radio **2/-**. TV **2/6**. S.A.E. DARWIN, 19, George Street, St. Helens, Lancs.

SERVICE SHEETS for all makes of Radio and TV 1925-1964. Prices from **1/-** with free fault-finding guide. S.A.E. inquiries. Catalogue of 6,000 models, **1/6**, Valves, modern and obsolete. Radio/TV Books. S.E.A. lists, HAMILTON RADIO, Western Road, St. Leonards, Sussex.

SERVICE SHEETS

4/- each, plus postage.

We have the largest display of Service Sheets for all makes and types of Radios, Televisions, Tape Recorders, etc. in the country, and can supply by return of post.

To obtain the Service Sheet you require, please complete the attached coupon:

From:

Name: .....

Address: .....

.....

.....

To: **S.P. DISTRIBUTORS**
44 Old Bond St., London, W.1

Please supply Service Sheets for the following:

Make: .....
Model No.: ..... Radio/TV
Make: .....
Model No.: ..... Radio/TV
Make: .....
Model No. .....

I also require list of Service Sheets at 1/6.

I also require list of Manuals at 1/-

(please delete items not applicable)

I enclose remittance of .....

MAIL ORDERS ONLY

TAPE RECORDERS, TAPES, ETC.

TAPE TO DISC RECORDING. 10in LP, **42/-**; 12in LP, **48/-**; 7in EP, **21/-**. S.A.E., Leaflet, DEROY SOUND SERVICE, 52, Hest Bank Lane, Hest Bank, Lancaster. Tel.: HB.2444.

JOIN BRITAIN'S LARGEST, Friendliest Tape Exchange: "WORLDWIDE TAPETALK," The Gardens, Harrow, Middlesex. S.A.E. for particulars.

FOR QUALITY consult our sixty-page (photographically illustrated) latest Hi-Fi equipment catalogue (**4/6d.**). Unbiased advice, preferential terms to members, LP-s from your precious tapes. AUDIO SUPPLY, 10 Clifford Street, London W.1.

MISCELLANEOUS

CONVERT ANY TV SET into an Oscilloscope. Diagrams and Instructions, **12/6**. REDMOND, 42, Dean Close, Portslade, Sussex.

HAMMER FINISH PAINT. The modern finish for electronics. Can be brushed or sprayed. Blue or silver, 2½oz tins **3/6**, ½ pint **7/6**, 1 pint **15/-**. Post 6d. on any order. Trade supplied. FINNIGAN SPECIALITY PAINTS, (PE), Mickley Square, Stocksfield, Northumberland.

METAL WORK

CABINETS • CASES
CHASSIS

Anything in metal. **"One-offs"** a pleasure
Send your drawing for quote
Stove enamelled in any professional finish

MOSS, WATSON
40 Mount Pleasant Street, Oldham, Lancs. *MAIN 9400*

EDUCATIONAL

B.Sc.(ENG.), A.M.I.MECH.E., A.M.I.E.R.E., City & Guilds, etc., on "NO PASS—NO FEE" terms. Wide range of guaranteed Home Study Courses in Electronics, Computers, Radio, T.V., etc. 156-page Guide—FREE. Please state subject of interest. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY, 151 College House, Wright's Lane, London, W.8.

HOME STUDY COURSES in Practical Electronics. Free Brochure without obligation from: BRITISH NATIONAL RADIO SCHOOL, Reading, Berks.

EDUCATIONAL

(continued)

STUDY RADIO, TELEVISION AND ELECTRONICS with the world's largest home study organisation. I.E.R.E., City & Guilds, R.T.E.B., etc. Also Practical Courses with equipment. All books supplied. Write for FREE Prospectus stating subject to I.C.S. (Dept. 577), Intertext House, Parkgate Road, London, S.W.11.

A.M.I.MECH.E., A.M.I.E.R.E., City & Guilds, G.C.E., etc., bring high pay and security. "NO PASS—NO FEE" terms. Over 95% successes. For details of Exams and courses in all branches of Engineering, Building, Electronics, etc., write for 156-page Handbook—FREE. B.I.E.T., (Dept. 152), London, W.8.

SITUATIONS VACANT

RADIO TECHNICIAN

A number of suitably qualified candidates will be required for training, leading to permanent and pensionable employment. (Normally at Cheltenham but with opportunities for service abroad or appointment to other U.K. stations).

Applicants must be 19 or over and be familiar with the use of Test Gear and have had Radio/Electronic workshop experience. They must offer at least "O" level GCE passes in English Language, Maths and/or Physics, or hold the City and Guilds Telecommunications Technician Intermediate Certificate or equivalent technical qualifications.

Pay according to age, e.g. at 19 £722, at 25 £929 (highest pay on entry) rising by four increments to £1,067.

Prospects of promotion to grades in salary range £997–£1,634.

Annual Leave allowance of 3 weeks 3 days, rising to 4 weeks 2 days.

Normal Civil Service sick leave regulations apply.

Apply
Recruitment Officer (RT/54)
Government Communication Headquarters
Oakley
Priors Road
Cheltenham

Practical Electronics Classified Advertisements

CONTINUED

TRANSFORMERS

ROTARY TRANSFORMERS

TV from your OWN Car Battery



Famous **DELCO** transforms 12 or 24v. supply to mains Power for TV, ¼" drills, etc. **ONLY** 75/- C.O.D. 2/6 extra. **CARR. PAID.**

SMALLER MODEL. 12/24v. input, 110/250v. output **22/6**

HOOVER ROTARY TRANSFORMERS. 6v. input, 250v. output. 12v. input, 490v. output. 32 watts. **Brand New**..... **25/-**

New but Store Soiled **21/-**

REMOTE CONTROL RELAY. 12 volts 40 amp. contacts. **Each** **12/6**

INDOOR T.V. AERIALS. Single Dipole extending to 5ft. **Each** **15/-**

VIBRATOR POWER-PAK. Step 12v. up to MAINS output. For Universal AC/DC razors, small fluorescent fittings, radios, etc. ..... **Only** **32/6**

LARGE ROTARY TRANSFORMER. 12v. input, over 1,200v. output. New. For experimental purposes **£5**

VOLTMETERS DC,

5" dia. 0-200 volt **50/-**

3½" dia. 0-350, need shunt **27/6**

Send NOW—Delivery by Return

JAMES WALKER, ELECTRONICS DIVISION

36 Alexandra Street, Thurmaston, Leicester

WANTED

NEW VALVES WANTED

Any type, or quantity

CASH PAID

R.S.T. Valve Mail Order Co.

211A Streatham Road

Mitcham, Surrey

Telephone: MITCHAM 6202

FOR SALE

TRANSISTORS UNMARKED UNTESTED. 40 for **10/-**, P. & P. 1/-. 4 packets post free. Relays, thousands of types, special catalogue free. General Catalogue of Mechanical & Electrical Gear, Tools, etc., 5,000 items, free. K. R. WHISTON (Dept. PET), New Mills, Stockport.

RELAYS, EX-GOVERNMENT. **£3** for 12, our selection, post paid. WALTONS WIRELESS STORES, 15 Church Street, Wolverhampton.

VENNER TIME SWITCHES reconditioned, 14-day clock, once on, once off every 24 hours, jewelled movement, fully guaranteed, 5 amp., **32/6**; 1 amp, **25/-**, P. & P. 2/6. A. R. BATCHELOR (P.E. Dept.), 4 Park Road, Bromley, Kent.

5-TON FACTORY CLEARANCE, Radio, TV Electrical Components, in mixed parcels. Example: 28lb. mixed parcel **£1**, pp 7/6d. Speakers, grilles, valves, bases, i.f.s. covers condensers, etc. Hundred other items. S.A.E. List and Postal Orders to P. NEWTON, 16 Shalcross Crescent, Hatfield, Herts.

FOR SALE

(continued)

CONDENSER BARGAIN! Miniature paper condensers, ⅛in × ⅛in. Ideal for transistor sets, .0001, .001, .002, .005, .02, .04μf. Your choice, **7/6d.** per 100 or **£3** per 1,000. G. F. MILWARD, 17 Peel Close, Drayton Bassett, Staffs.

ARMATURE REWINDS. Hoover Junior Exchange Service. Models 375/119/1224, **32/6** inc. post. Fields **15/-**. Send for lists. JERVIS & TONGE LTD., Ringwood Road, Brimington, Chesterfield, Derbys. Tel. Chest. 75267.

RECEIVERS AND COMPONENTS

TRANSISTORS! Give-away price. NKT124/5 Power Type. 6 for **10/-**. 2SO17 4W, up to 60mc/s, **5/-** each. Post free, G. F. MILWARD, 17 Peel Close, Drayton Bassett, Staffs.

RESISTORS! You can't resist this! ½W, 1W, 2W Polythene wrapped on cards of 10. Mixed values and wattages. **£2/10/-** per 1,000. G. F. MILWARD, 17 Peel Close, Drayton Bassett, Staffs.

A.1 POST FREE BARGAINS. Guaranteed reclaimed valves. Send for full list to: Dept. MO/E, A.1 RADIO COMPONENTS, 14, The Borough, Canterbury, Kent.

TESTED TRANSISTORS

All new, few equivalent.

OA202

1/- each, Red or White Spots.

2/- each, XA101. XA102, XB103, OA90, OC430, XA112, XA111.

3/- each, OC44, OC45, OC70, OC71, OC81, OC81D, OC200, GET16.

4/- each, AF114, AF115, AF117, OC170, OC171, SX658, XU611.

5/- each, OC72, OC139, OC140, OC204, ORP60, BY100, GET8.

10/- each, OC35, OC26, OC28, GET57, 2SO13. All new, few equivalent.

ZENER DIODES 4.7 v. to 33 volt ¼ watt, **3/6** each. 1.5 watt, **5/-** each, 7 watt, **6/-** each.

Send 3d. stamp for Full Price List and Free Equivalent Chart.

B. W. CURSONS

78 BROAD STREET

CANTERBURY, KENT

RECEIVERS AND COMPONENTS

(continued)

R. & R. RADIO & TV SERVICE

44 Market Street, BACUP. Tel. 465

SALVAGE VALVES

6F13	4/6	10P14	5/-	PL82	3/6	20P4	6/6
6L18	4/6	20P5	6/6	U801	7/6	30P16	5/-
EF80	1/6	30P4	7/-	10F1	1/6	PCC84	4/-
ECC82	3/-	6F15	5/-	20F2	5/6	PCL83	5/-
ECL80	3/-	EB91	1/-	30FL1	5/-	PY81	3/6
30F5	5/-	EF85	5/-	PY32	6/-	U301	6/-
PL38	6/-	EF37	6/-	6U4GT	5/-	10P13	5/6
PCF80	4/-	20P3	6/-	6F1	1/6	20D1	1/6
PL81	5/-	30PL1	6/-	ECC81	3/-	30P12	6/-
PZ30	5/-	PL36	6/-	EY86	4/-	PY82	4/-
U329	5/-	PCL82	5/-				

Post 6d. per valve, 3 or more post free.

Speakers ex T.V. 5 inch round 3/6, 6 by 4 inch 3/6, 8 inch round 6/-, post 2/-.

Ex T.V. printed circuit panels, containing valve holders, resistors, condensers, etc., 5/6, post 2/-.

Assorted mains droppers ex T.V. 2/6 each, 10 £1.

Pre-set controls £1 per doz. assorted values, post 1/-. Resistors, New: ½ watt 3½d., 1 watt 5d., 2 watt 9d., all 10%. Silver mica, paper and electrolytics in stock. New Mullard transistors and condensers also in stock. S.A.E. with all enquiries. All goods subject to satisfaction or money refunded.

TELEVISION TUBE SHOP

FOR

Unused, Guaranteed Tubes

OVER 2,000 IN STOCK

All prices from 50% to 75% of List Price

All tubes tested before despatch and Guaranteed for 12 months

CARRIAGE 10/- via B.R.S. or 15/- via passenger train

TERMS £2 down (plus carriage) and £1 per month

See our advertisement in PRACTICAL TELEVISION for exact prices, or write for details

TELEVISION TUBE SHOP

48 BATTERSEA BRIDGE ROAD

LONDON, S.W.11. BAT 6859

OPEN ALL WEEK AND SATS. UNTIL 4 p.m.

CONTINUED OVERLEAF

Key Switch, 3 position, centre off, 3 c/o + 4 c/o, **6/-**

Ferox Cubes LA12, wound, **5/-**

Panel Lamps, Min. Liliput screw, White Bezel, **3/-**

DLR5 Headphones, with plug and socket, **12/6**

Min. Liliput screw bulbs, 12 volt, **1/6**

High Speed Relay, c/o 1,000 + 1,000 ohm, **6/6**

400 ohm P.O. Relay, 1B, **5/-**; 1B 1M, **6/-**

2,000 ohm P.O. Relay, 1M, **5/-**; 1M 1B, **6/-**

G.P.O. Hand Sets, with Press to Talk in handle, **15/-**

G.P.O. Jack Plug, with lead, **3/-**

Isolated Jack Socket, **2/6**

Breast Set Mike, with fittings, **6/-**

500 Micro Amp Meter and Meter Switch, **15/-**

Toggle Switch, SP on/off, **2/6**

Push Button Switch, DP on/off, on when press only, **2/6**

Power Supply and LF Amplifier, N/O 1, **15/-** for N/O 38 set

6 core min. Cable, 3 amp screened PVC outer, **3/-** yard; 12 core ditto, both fitted with Plessey plugs and sockets, in 10 yard lengths only

New range of High Stability Resistors, 5% to 1%, ¼ to 5 watt, send for full lists.

Telescopic Drawer Slides, 17½in. to 20in., **12/6** pair

Copper Laminate Board, single or double sided, **5/-** sq. ft., or 3ft. by 4ft. panels, **33/-**

Jones Plugs and Sockets, 4-12-18-24-32 way, **5/-** pair

Plessey Plugs and Sockets, 2-4-6-12-25 way, **5/-** pair

31 way P.O. Cable, **2/-** yard. Minimum 5 yards.

Ever Ready Batteries, 90V + 7½V, **4/6** or 12 for **30/-**

Mallory Mercury Cells, 6·75V, **3/6**

8 Tag Panels, with 150 Resistors, Condensers, Diodes, **10/-**

2ft. 9in. Mobile Aerials, **6/6**

30 meg. Oscillator Unit, 3 valve tunable to 27 meg., **12/6**

Parcel of ex-Government valves, 20 for **10/-**

Small Component Boxes, 7 divisions, 60 for **12/6**

Printed Circuit Preset Pots, 10K, **2/-**

115 volt Western Electric Magslips, **50/-** each

230 volt BTH Magslips, **90/-** each

Electro Magnetic Counters, P.O. 4 digit, **4/6**

Mu Metal Screen for 5UP7 tubes, **6/6**

30 + 30 pF Variable Condensers, **4/-**

¼ amp Fuses, **5/-** per 100, 1¼in. × ¼in.

Mic. Jacks, 3 for **3/-**

Small Instrument Cases, 5in. × 5in. front, 4½in. deep, with grey plastic front, **6/-** each. Rack to house two of these, side by side, **7/6**

Transformer PL1101, output 7 volt at 4 amp, three times plus 7 volt at 125 mA, **18/-**

H.T. Transformers, 1,800 volt plus 1,800 volt at 500 mA, and 600 volt plus 600 volt at 500 mA, **60/-**

PARMEKO NEPTUNE TRANSFORMERS
115 volt or mains input. Output 450-0-450 at 260 mA; 275-0-275 at 45 mA; 132 volt at 20 mA; 30 volt at 30 mA; 6·4 volt at 16 amp; 6·4 volt at 4·5 amp; 6·3 volt at 1·2 amp; 5 volt at 6 amp. These are oil filled, packed in own drum, **70/-** each

PARMEKO NEPTUNE CHOKES OIL FILLED
10 henry at 260 mA, **22/-**; 15 henry at 45 mA, **12/6**; 5 henry at 20 mA, **6/6**

PAPER BLOCK CONDENSERS

MFD	Volts wkg	Price
1	350	**1/3**
1	500	**1/6**
1	600	**2/-**
1	800	**2/6**
1	1,200	**4/-**
1	3,400	**5/-**
2	350	**1/9**
2	700	**3/-**
2	1,000	**4/-**
4	400	**4/-**
4	600	**4/6**
4	800	**5/-**
4	1,200	**7/6**
4	2,000	**8/-**
8	400	**5/6**
8	600	**6/-**
10	250	**4/-**
10	700	**7/-**
0·5	5,000	**9/-**
2	2,000	**14/6**

ON ALL ORDERS UNDER 20/- PLEASE ADD 2/- POST AND PACKING

SUPER BREAKDOWN UNIT

Remote Control Unit Type F. New in sealed cartons, containing P.O. Relay 2,000 ohms Resistance, 100 volt Plessey Hand Generator, Telephone Ringing Bell A.C. 8 amp Morse Key on base, 2 D.P. D.T. Key Switches, Double Phone Jack, moulded, 5 position 6 pole Yaxley Switch, Induction Coil tapped 1-17-33 ohms, 7 Brass Screw Terminals on panels, plus Resistors, Condensers, Pointer Knobs. All in a handy metal box with hinged lid and side fasteners. Also web carry strap. Size 10½in. × 10in. × 7in., **25/-**, post free. Or items may be purchased separately. Relay **5/-**, Hand Generator **7/6**, Bell **5/-**, Morse Key **4/6**, Key Switches **5/-** pair, Double Phone Jack **2/6**, Yaxley Switch **2/-**, Ind Coil **2/-**, Terminals 7 for **2/-**, all post free.

Also available Key Switches. 4 pole 2 throw **3/6** each or 3 position D.P. plus D.P. centre off **5/-** or rotary switch 6 pole 3 way **3/-**.

Speakers, 3 ohm P.M. 5in. **5/-**, 6in. **6/-**, 7 × 4in. **7/-**, 8in. **8/-**, 10in. **12/6**.

U.K. ONLY


E. R. NICHOLLS

Mail Order and Retail Shop:

46 LOWFIELD ROAD off SHAW HEATH


STOCKPORT, CHESHIRE

WHEATSTONE BRIDGE

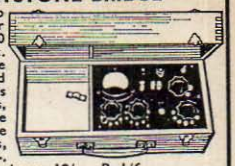

Centre Zero Galvanometer Scaled 20-0-20 2½in. movement. 2·5 mA. full scale deflection, 3 stud switch controls 0-10, 0-100 ohms, 0-Inf. Complete in carrying case with instructions, **45/-**. Post 5/-.
Spare meters for above, 10/-. P. 1/6.

RCA CANADIAN No. 29

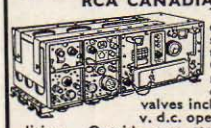

Transmitter/Receiver 2-8 Mc/s., separate Manual tuning R.F. and Osc., also preset motor operated ditto, 25 miniature valves including 2/815's. 12/24 v. d.c. operation. Unused condition. Outside case store soiled, **£12/10/-**. Carr. £2. English version. Manual tuning only. Complete station, **£8/10/-**. Carr. £2.

TELESCOPIC AERIAL MASTS. Tubular steel copperised, spray finish, ring cam locking on each section provides for full or any height required. Suitable all fixings and base locations. Bottom section 1¾in. diameter. 20ft. (4 section) Closed 5ft. 9in. Weight 16lb. **55/-**. Carr. 5/-. 34ft. (6 section) Closed 6ft. 6in. Weight 20lb. **75/-**. Carr. 5/-. Further height by adding 3-4 Whipsections, **13/6**. Carr. 1/6. Special price for quantities.

CREED TELEPRINTERS. 7B Used condition, **£12/10/-**. Carr. 30/-.

B44 Mk. III. Dipole and rod aerials 30/- per set, P. & P. 5/-. Microphone with connecting plug, **15/6**, P. & P. 2/-. Battery input and phone plugs, 5/- each, P. & P. 1/6.

POWER UNIT 110/230v A.C. input. 'C' type drop through Parmeko Transformer. 315-0-315v, 6.3v output. Double choke and paper tap smoothing. Combined 4 valve including 4Z4 rectifier, 6B6 o.p. A.F. Amplifier. Self contained rack or table mounting. Fully fused. Indicator light. Mains switch. Brand new in makers cartons. **65/-** Carr. 5/-. (Quality enquiries invited.)

TRANSMITTER. 1·75-16 Mc/s., 3 waveband tuneable, grid modulation using 813. Used complete with all valves, circuit, **£7/10/-**. Carriage 10/-. **(Many other bargains.)**

A. J. THOMPSON,
"Eiling Lodge" Codicote, Hitchin, Herts.
Phone: Codicote 242

PADGETTS RADIO STORES

OLD TOWN HALL, KNOWLER HILL, LIVERSEDGE, YORKS.

Telephone: Cleckheaton 2866

Single Phase 230 V. 1400 r.p.m. ¼ h.p. motor with pulley, **26/-**. Less pulley, **24/-**. Fully guaranteed ex-washing machine. Carr. 8/6.

One Sixth H.P. Motor 15/-. Post 6/9.

New Indicator Unit. C.R.T. 100. Complete with two tubes, type VCRX393 and VCRX298 plus 21 small valves. Relays removed, **57/-** or less valves **32/-**. carr. 10/-. Sorry no details on the unit.

New Boxed Test Set. 100 only. Type 350, complete with meter and case. No details. **37/6.** Post 6/9.

New Condenser Parcel. Mixed. Send **6/-**. Post paid.

New 12in. Speaker with built in tweeter. 15 or 3 ohms. **28/6.** Post paid.

P.M. Speakers, all 3 ohm, ex-TV Sets. 6in. round, 6 × 4in. and 5in., **3/-**. Post **2/-**, 6 for **20/-**. Post paid. 8in. round, **6/-**. Post 2/-. 7 × 4in. **5/-**. Post 2/-.

VALVE LIST

Ex equipment. 3 months guarantee.
All Post Paid

EL91	1/6	20P3	4/-	PY80	3/-
ECL80	2/-	20P4	8/6	PL82	3/-
EC82	3/-	20P1	4/-	PL83	3/-
EY51	2/6	30P4	8/-	PL33	3/-
EBF80	4/6	U801	8/6	PY81	3/-
EB91	9d.	U281	5/-	PY82	3/-
EL38	5/-	U232	5/-	PCF80	4/-
EY85	6/6	U329	5/-	PCC84	4/-
EF91	9d.	KT36	5/-	PCL85	6/6
6F1	1/-	KT66	8/-	PCL82	6/6
6F14	5/-	6V6GT	4/-	VR150/30	3/-
6F15	5/-	6B8	1/6	IT4	1/9
6LD20	5/-	6K25	5/-	12AT7	3/-
10C2	5/-	6P25	3/6	6CH6	1/6
10F1	1/-	6U4	5/-	6X4	3/-
10P13	5/-	PY33	6/6	R18	3/6
10P14	5/-	PL33	6/-	ARP12	1/6
20D1	2/-	PL81	4/-	807	5/6
20L1	5/-	PL38	8/-		

EF50 **1/-**, doz. **6/-**; 6K7 **1/3**, doz. **10/-**; 6V6 **1/9**, doz. **18/-**; 6K8 **1/9**, doz. **18/-**.
Send S.A.E. for rare valve enquiry.

Breaking up Mark III Type 19 Sets. Meter, 500 micro-amp., **5/-**. Post 1/9. Jack Socket 1/-. Post 6d. Doz. **10/-**. Post paid. Jack 1/5. Post 6d. Toggle Switch Metal 6d. Post 6d. Doz. **10/-**. Post paid. Relay Type 3000 **1/9**. Post 1/9. Doz. **20/-**. Post paid. Any other spare send 2/- plus post to cover.

TV Sets. 13 channels. Untested but complete. 14in. **30/-** 17in. **50/-**. Carr. 10/-. Well packed but sent at owner's risk.

Reclaimed Tubes Six months guarantee. 14in. Mullard and Mazda **17/-**. Carr. 7/6. 17in. **30/-**. Carr. 7/6.

LASKY'S RADIO

For the Finest Value and Service to the HOME CONSTRUCTOR AND THE ELECTRONICS ENTHUSIAST

We consider our construction parcels to be the finest value on the home constructor market. If on receipt you feel not competent to build the set, you may return it as received within 7 days, when the sum paid will be refunded less postage.

TRANSISTOR PORTABLES

THE SKYROVER AND SKYROVER DE LUXE

★ **LONG WAVEBAND COVERAGE IS NOW AVAILABLE FOR THE SKYROVER and SKYROVER DE LUXE.** A simple additional circuit provides coverage of the 1400/1950M band (including 1500 M. Light programme). This is in addition to all existing Medium and Short wavebands. All necessary components with construction data. Only **10/-** extra Post Free. **This conversion is suitable for Skyrover and Skyrover De Luxe receivers that have already been constructed.**



GENERAL SPECIFICATION
7 transistor plus 2 diode superhet, 6 waveband portable receiver.
The SKYROVER and SKYROVER DE LUXE cover the full Medium Waveband and Short Waveband 31-94M, and also 4 separate switched band-spread ranges, 13M, 16M, 19M and 25M, with Band Spread Tuning for accurate Station Selection. The coil pack and tuning heart is completely factory assembled, wired and tested. The remaining assembly can be completed in under three hours from our easy to follow, stage by stage instructions.

SPECIFICATION:
Superhet, 470 Kc/s. All Mullard Transistors and Diode. Uses 4-U2 batteries. 5in. Ceramic Magnet P.M. Speaker. Easy to read Dial Scale. Band Spread Tuning. 500 MW Output. Telescopic Aerial and Ferrite Rod Aerial.

WAVEBAND COVERAGE: 180-567M; 31-94M and Band Spread on 13, 16, 19 and 25 metre Bands.

The SKYROVER

Controls: Waveband Selector, Volume Control with on/off Switch, Tuning Control. In plastic cabinet, size 10 × 6½ × 3½in. with metal trim and carrying handle.
Can now be built for £8.19.6 P. & P. 5/- extra.
H.P. Terms: £1 deposit and 11 monthly payments of 16/6.

The SKYROVER De Luxe

Tone Circuit is incorporated, with separate Tone Control in addition to Volume Control. Tuning Control and Waveband Selector. In a wood cabinet, size 11½ × 6½ × 3in. covered with a washable material, with plastic trim and carrying handle. Also car aerial socket fitted.
Can now be built for £10.19.6 P. & P. 5/- extra.
H.P. Terms: 25/- deposit and 11 monthly payments of 20/-.
Data for each receiver: 2/6 extra. Refunded if you purchase the parcel. **Four U2** batteries 3/4 extra. All components available separately.

REALISTIC SEVEN

Fully tunable long and medium bands. Uses 7 Mullard Transistors; plus Diode OA70.
STAR features:
● 7 Transistor Superhet. ● 350 Milliwatt output 4in. high flux speaker. ● All components mounted on a single printed circuit board, size 5½in. × 5½in. in one complete assembly. ● Plastic cabinet, with carrying handle, size 7in. × 10in. × 3½in., in blue/grey. ● Easy to read dial. ● External socket for car aerial. ● I.F.-frequency 470 Kc/s. ● Ferrite rod internal aerial. ● Operates from PP9 or similar batt. ● Full comprehensive data supplied with each Receiver. ● All coils and I.F.s etc., fully wound ready for immediate assembly. An outstanding Receiver.



Can be built for
£5 . 19 . 6
P. & P. 4/6.

REALISTIC SEVEN De Luxe

By popular request a De Luxe version of the well-known Realistic Seven now available. With the same electrical specification as standard model—PLUS A SUPERIOR WOOD CABINET IN CONTEMPORARY STYLING covered in attractive washable material, with super-chrome trim and carrying handle. Also a full vision circular dial, externally mounted to further enhance the pleasant styling. **ONLY £1 EXTRA**
Both models: Battery 3/9 extra. (All components available separately.) Data and instructions separately 2/6, refunded if you purchase parcel.



TWO SINCLAIR SUPER MINIATURES

THE MICRO-6 Self-contained pocket radio. Size only 1 4/5 × 1 3/10 × ⅞in. A marvel of modern miniaturisation—truly amazing performance. Without a doubt the most advanced transistor circuit ever offered to home constructors—yet may be built in an evening. Complete with earphone and detailed construction data. **Can be built for only 59/6** All parts sold separately. Mercury cell 1/11 extra (2 required).

THE SLIMLINE The new amazing performance 2-transistor pocket radio size only 2¾in. × 1¾ × 1¼in. Micro alloy transistorised and printed circuit. Easy to assemble. **CAN BE BUILT FOR 49/6** All components available separately.

TRANSFILTERS

By BRUSH CRYSTAL CO. Available from stock.

TO—O1B 465 kc/s. ± 2 kc/s.	TO—O2D 470 kc/s. ± 1 kc/s.	**6/6 EACH**
TO—O1D 470 kc/s. ± 2 kc/s.	TF—O1B 465 kc/s. ± 2 kc/s.	
TO—O2B 465 kc/s. ± 1 kc/s.	TF—O1D 470 kc/s. ± 2 kc/s.	**P. & P. 6d.**

CONSTRUCTORS BARGAINS

The "Sixteen" Multirange METER KIT



This outstanding meter was featured by *Practical Wireless*, in the Jan. '64 issue. Lasky's are now able to offer the complete kit of parts as specified by the designer.

RANGE SPECIFICATION:
D.C. volts: 0-2.5-25-50-250-500 at 20,000Ω/V.
A.C. volts: 0-25-50-250-500 at 1,000Ω/V.
D.C. current: 0-50μA, 0-2.5-50-250 mA.
Resistance: 0-2000Ω, 0-200kΩ, 0-20 MΩ.
Basic movement: 40μA f.s.d. moving coil. With universal shunt full scale deflection current is 50μA.
Size/finish: Black plastic case—3¾ × 5¾ × 1¾in.
Controls: 12 position range switch: separate slide switch for A.C. volts—D.C. ohms; ohms zero adjustment pot. meter; meter zero. External connections: Two 4 mm. sockets for test lead plugs.

Power requirements: One 15v. and one 1.5v. batts. Complete with all parts and full construction details.

H.P. Terms: 21/- deposit and 5 monthly payments of 21/-. Data and circuit available separately, 2/6; refunded if all parts bought. Pair of batteries 2/- extra.

LASKY'S PRICE **£5.19.6** P. & P. 5/-.

BUILD A HIGH QUALITY TAPE RECORDER

Using the famous Collaro "STUDIO" deck and MARTIN pre-assembled amplifiers 2- or 4-track models.

COLLARO STUDIO TAPE DECK.
Latest model 3 speed, 3 motors. Take 7in. reels. Fitted with half-track heads. **LASKY'S PRICE £10/10/-.** New and Unused. Carr. & Pack. 7/6.


COLLARO STUDIO TAPE DECK. As above but fitted with the latest quarter-track heads. **LASKY'S PRICE £13/19/6.** Carr. & Pack. 7/6.

MARTIN TAPE RECORDER AMPS. Designed for use with Collaro Studio Tape Deck. In sub-assemblies for immediate installation. 6-valve circuit. Comprehensive instructions make final assembly as simple as possible. Everything supplied including valves, etc. Monitoring facilities. 3-ohm output, speed equalising, etc. For 200-250 v. A.C. mains.

PRICES ½-track Model **£11/11/-.** ¼-track Model **£12/12/-.** P. & P. 2/6. Portable carrying case designed to take the Collaro Studio Tape Deck and the Martin Tape Amplifier. Fitted with 9 × 5in. speaker. Price complete with speaker **£5/5/-.** P. & P. 5/-.

SPECIAL INTEREST ITEMS!

VIKING "SOUND 30" AMPLIFIER

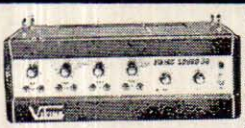

High quality guitar and P.A. amplifier. A.C. Mains operated—30 watt output. 8 inputs. Fitted with 4 separate volume controls for mixing also bass and treble controls. 15 ohms out. impedance. British made—highest quality components used throughout—fully guaranteed. In strong portable case, size approx. 20 × 9 × 6in.

LASKY'S PRICE **35 GNS.** Carr. & Pack. 7/6 extra.

NEW! ANOTHER SINCLAIR SUPER MINIATURE

THE X10 10 watt power amplifier fitted with integrated pre-amplifier. Requires only 1 mV. for an output of 10 watts undistorted. Frequency response is flat ¼ dB from 5 c/s. to 20 kc/s. Size only 6 × 3 × ⅞in. Weight 5 oz. Built on printed circuit. Operates from 12 v. D.C. at 75 mA. quiescent. Circuit uses 7 M.A.T.s and 4 RF power transistors. **KIT PRICE £5.19.6** Post Free

AVAILABLE READY BUILT, TESTED AND GUARANTEED, £6.19.6 Post Free. 3 pots. for volume, Bass and Treble, 7/6 the 3 extra. Mains power pack if required, **54/-.**



DEAC RECHARGEABLE NICKEL CADMIUM CELLS

Rating 1.22 v. 3.5 A.H. at 10 hour rate. 1,001 uses for model makers, miniature electronic equipment, portable radios, transistor radios, T.V's, tape recs., transceivers, photo flash, etc. Hermetically sealed. Size 3½ × 1⅞ × 1⅛in. Listed at 35/- each.
LASKY'S PRICE 15/- each. POST FREE. BANK of 9, **79/6.**

THE HARROW POWER PACK

Battery eliminator for portable radios, etc. Converts your battery radio to A.C. mains. Replaces 4½ v., 6 v. and 9 v. batts. Size only 3in. × 2in. × 2½in. State voltage required when ordering.
LASKY'S PRICE **29/6** P. & P.

TRANSISTORS

ALL BRAND NEW AND GUARANTEED

GET 81, GET 85, GET 86 **2/6**; 837A, 874P **3/6**; OC45, OC71, OC81D **4/6**; OC 44, OC 70, OC 76, OC 81 (match pair **10/6**); AF 117, **5/6**; OC 75, OC 170, OC 200 **6/6**; OC 23, OC 42, OC 43, OC 73, OC 82D **7/6**; OC 201, OC 204 **15/-**; OC 205, OC 206 **19/6**; OC 28 **24/6.**

207 EDGWARE ROAD, LONDON, W.2.
Near Praed St. PADDINGTON 3271/2
BOTH OPEN ALL DAY SAT. Early Closing Thurs.

33 TOTTENHAM COURT ROAD, W.1.
Nearest Stn., Goodge St. MUSEUM 2605
Mail Orders to Dept. P.W., 207 Edgware Rd., W.2.

152/3 FLEET STREET, LONDON, E.C.4.
Telephone: Fleet Street 2833
OPEN ALL DAY THURSDAY. Early Closing Sat.

LASKY'S FOR SPEEDY MAIL ORDER SERVICE

TYGAN FRET (Contem. pat.), 12 × 12in. 2/-; 12 × 18in. 3/-; 12 × 24in. 4/-, etc.
EXPANDED ANODISED METAL—Attractive gilt finish ¼ in. × ⅛ in. diamond mesh 4/6 sq. ft. Multiples of 6 in. cut. Max. size 4ft. × 3ft., 47/6, plus carr.
ENAMELLED COPPER WIRE—½lb. reels 14g-20g, 2/6; 22g-28g, 3/-; 30g-34g, 3/9; 36g-38g, 4/3; 39g-40g, 4/6, etc.


Volume Controls—5K-2 Meg. ohms, 3in. Spindles. Morganite Midget Type 1½in. diam. Guar. 1 year. LOG or LIN ratios less Sw. 3/-. DP. Sw. 4/6. Twin Stereo less Sw. 6/6. DP. Sw. 8/-. **Specials to order.**

SPECIAL BARGAIN

¼ Meg. VOL. Controls DP. Sw. ¼" flatted spindle. Famous Mfrs. **4 for 10/-**, post free.

BONDACOUST Speaker Cabinet Acoustic Wadding (1in. thick approx.) 12in. wide, any length cut, 1/6 ft., 4/- yd. **TINNED COPPER WIRE.** 16-22g. 2/6 ½lb. **ERSIN MULTICORE SOLDER.** 60/40 4d. per yard. Cartons 2/6, etc.

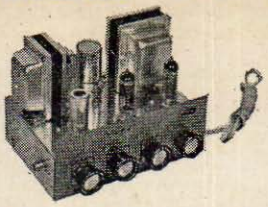MULLARD "3–3" HI-FI AMPLIFIER
3 VALVES 3 WATT



3 ohm and 15 ohm Output. A really first-class Amplifier giving Hi-Fi quality at a reasonable cost. Mullard's latest circuit: Valve line-up: EF86, EL84, EZ81. Extra H.T. and L.T. available for Tuner Unit addition. This is the ideal companion Amplifier for FM tuner units.

TECHNICAL SPECIFICATION—Freq. Response: ±1dB. 40 c/s-25 kc/s. Tone controls, max. treble cut 12dB at 10 kc/s. Max. Bass Boost 14dB at 80 c/s sensitivity: 100MV for 3W output. Output Power (at 400 c/s): 3W at 1% total harmonic distortion. Hum and Noise Level: At Least 70dB below 3W.

COMPLETE KIT (incl. valves, all components. wiring diagram and special quality sectional Output Trans.) **BARGAIN PRICE £6.19.6** carr. 4/6. Complete wired and tested, **8 gns.** Wired power O/P socket and additional smoothing for Tuner Unit, **10/6** extra.

Bronze Escutcheon Panel, Printed Vol., Treble, Bass, On-Off, supplied with each kit.
Recommended Speakers—R. Allen 12" with tweeter **42/6**, WBHF10-12 **£4.7.6**, Goodmans Axiette **£5.5.0**, Axiom 10 **£6.5.0**, Audiom 51 **£8.10.0**. Carr. extra.

TRANSISTOR COMPONENTS

Midget I.F.'s—465 Kc/s $\frac{5}{16}$in. diam. **5/3**
Osc. Coil M. & L.W. **5/9**
Midget Driver Trans. 3.5:1 ..... **6/9**
Midget Output Trans. Push-Pull—
3 ohms **6/9**
Elect. Condensers—Midget Type 1 mfd.-50 mfd. ea. **1/9**, 100 mfd. **2/-**, 12V.
Condensers 150 v. working: .01 mfd., .02 mfd., .03 mfd., .04 mfd. **9d.**; .05 mfd., .1 mfd., **1/-**; .25 mfd., **1/3**; .5 mfd., **1/6**, etc.
Midget Tuning Condensers. J.B. "OO" 208 pF and 176pF, **8/6**; ditto with trimmers, **9/6.** J.B. 220pF and 105pF conc. slow motion **10/6.** 365pF single **7/6.**

Condensers—Silver Mica. All values 2pF to 1,000pF, **6d.** each. Dittos Ceramics **9d.** Tub. 450V T.C.C. etc. 0.001 mFd to 0.01 and 0.1/350V. **9d.** 0.02-0.1/500V., **1/-.** 0.25 Hunt, **1/6.** 0.5 T.C.C. **1/9**, etc., etc. **Close Tol. S/Micas**—10%, 5pF-500pF, **8d.** 600-5,000pF, **1/-.** 1%, 2pF-100pF, **9d.** 100pF-500pF, **11d.** 575pF-5,000pF, **1/6. Resistors**—Full Range 10 ohms-10 meg. ohms 20% ½ and ¼W, **3d.**, ¾W, **5d.** (Midget type modern rating) 1W, **6d.**, 2W, **9d. Hi-Stab.** 5% ¼W, ½W, **6d.** (100 ohms-1 meg). Other values **9d.** 1% ¼W, **1/6**, etc., etc.

New Boxed VALVES Reduced Bargain Prices

1T4	3/6	ECC83	7/-	PCC84	8/-
1R5	6/-	ECL82	10/-	PCF80	8/-
185	6/-	ECL80	9/-	PCL83	10/6
384	7/-	EF80	7/6	PCL84	10/-
3V4	7/-	EF86	8/6	PL81	9/6
DAF96	8/-	EL84	7/-	PL82	9/-
DF96	8/-	EY51	9/-	PL83	8/-
DK96	8/-	EY86	9/-	PY32	10/6
DL96	8/-	EZ81	7/-	PY81	8/-
ECC81	7/-	GZ32	9/6	PY82	7/-
ECC82	7/-	EM84	8/6	U25	10/6

RECORDING TAPE

Famous American Columbia (CBS) Premier quality tape at NEW REDUCED PRICES. A genuine recommended Quality Tape—TRY IT. Brand new, boxed and fully guaranteed. Fitted with leader and stop foils.

Standard		Double Play		Long Play	
5" 600'	13/-	1,200'	31/6	900'	17/6
5½" 900'	16/-	1,800'	37/6	1,200'	19/6
7" 1,200'	21/-	2,400'	47/6	1,800'	28/6

Post & Package per reel, 1/- plus 6d. each for additional reels.

SPECIAL OFFER 3" Message tape 150', 3/9; 3" L.P. 225', 4/9; 3" D.P. 300', 6/6. P. & P. per reel 6d.
TAPE REELS Mnfrs. surplus 7", 2/3; 5½", 2/-; 5", 2/-; 3", 1/3; Plastics spool containers, 5", 1/9; 5½", 2/-; 7", 2/3.

TRIMMERS, Ceramic (Compression Type)—30pF, 50pF, 70pF, **9d.**; 100pF, 150pF, **1/3**; 250pF, **1/6**; 600pF, **1/9.**
PHILIPS. Bee Hive Type (conc. air spaced)—2-8pF, 1/-; 3-30pF, 1/-.
KNOBS—Modern Continental types. Brown or Ivory with Gold Ring; 1" dia., **9d.** each; 1¼", 1/- each; Brown or Ivory with Gold Centre, 1" dia., **10d.** each; 1¾", 1/3 each. LARGE SELECTION AVAILABLE.
METAL RECTIFIERS. STC Types—RMI, 4/9; RM2, 5/6; RM3, 7/6; RM4, 16/-; RM5, 21/-; RM4B, 17/6.

TUB-ELECTROLYTICS-CAN

25/25v. 50/12v. 1/9; 8+8/450v. 4/6; 50/50v. 100/125v. 2/-; 32 + 32/275v. 4/6; 8/450v. 4/350v. 2/3; 50/50/350v. 6/6; 16 + 16/450v. 5/6; 60/250/275v. 12/6; 32 + 32/450v. 6/6. 100 + 200/275v. 12/6.

CO-AX 80 ohm CABLE

High grade low loss Cellular Air Spaced Polythene—½in. diam. Stranded Cond.
Now only 6d. yard

BARGAIN PRICES—SPECIAL LENGTHS
20 yds. 9/-; P. & P. 1/6. Coax. Plugs 1/-; 40 yds. 17/6; P. & P. 2/-. Sockets 1/-; 60 yds. 25/-; P. & P. 3/-. Couplers 1/3.


Speakers P.M.—3 ohms 2½" E.M.I. **15/6.** Goodmans 3½" **16/6.** 5" Rola **15/6.** 6" Elac **16/6.** 7" × 4" Goodmans **15/6.** 8" Rola **19/6.** 10" R. × A. **25/-.** 9" × 6" Goodmans **22/6.** E.M.I. Tweeter **22/6.** **Jack Plugs.** Standard 2½" Igranic Type, 2/6. Screened ditto, 3/3. Miniature scr. 1¼", 2/3. Sub-min. 1/3.

TRS Est. 1949

RADIO COMPONENT SPECIALISTS

70 Brigstock Rd., Thornton Heath, Surrey. *Hours: 9 a.m.-6 p.m., 1 p.m. Wed.*
THO 2188. *Terms C.W.O. or C.O.D. Post and Packing up to ½ lb. 9d.; 1 lb. 1/3; 3 lb. 2/3; 5 lb. 2/9; 8 lb. 3/6.*

GUITAR AMPLIFIERS WITH TREMOLO

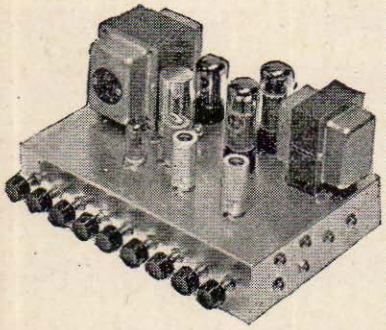

Five jack socket inputs, four with separate mixing volume controls, and one input "straight through". All inputs are of very high sensitivity only 10 millivolts input is required for full output, making them suitable for all types of guitars and microphones. Separate Bass and Treble controls, giving a wide range of lift and cut. Separate master gain control. Tremolo speed and depth controls. Jack socket for remote tremolo switching.

Outputs for 3 and 15 ohms speakers. Valves used in the 30 watt and 50 watt amplifier ECC83, ECC83, EL34, EL34, GZ34. In the 15 watt amplifier ECC83, ECC83, EL84, EL84, EZ81. An extra valve ECC83 is used in the tremolo circuit. The chassis is complete with baseplate and is solidly made of 18 gauge steel, finished silver grey hammer. Size 12 × 8 × 6½ inches high.

PRICES—

50 watt with tremolo	**£20.10.0**
50 watt less tremolo	**£19.10.0**
30 watt with tremolo	**£15.10.0**
30 watt less tremolo	**£14.10.0**
15 watt with tremolo	**£12.10.0**
15 watt less tremolo	**£11.10.0**

Add carriage 10/- any amplifier. Send for free descriptive leaflet.

STROUD AUDIO

PAGANHILL LANE, STROUD, GLOS. Stroud 783

PARKER'S SHEET METAL FOLDING MACHINES

NEW BENCH MODEL



Capacity 36in. wide x 18-gauge mild steel. Forms channels and angles down to 45 deg., which can be flattened to give safe edge. Depth of fold according to height of bench. Will form flanges.

Weight approx. 2 cwt.

Price £23/0/0, carr. free. Also the well-known vice models of:

36in. x 18-gauge capacity	...	£11	10	0
24in. x 18-gauge capacity	...	£6	15	0
18in. x 16-gauge capacity	...	£6	15	0

} *Carriage free*

One year's guarantee: money refunded without question if not satisfied. Send for details:

A. B. PARKER, Wheatcroft Works

WELLINGTON STREET, BATLEY, YORKS. Tel. 426

HIGH QUALITY TAPE AMPLIFIER KIT

Suitable for use with tape decks having a high impedance record head and a low impedance erase head. Magic eye recording level. 3 ohm 4 watt output. 2 inputs with tone control. Provision for monitoring. Simple point to point wiring instructions. This tape amplifier is also available completely built and tested. Ideal for use with Collaro and B.S.R. decks.



Kit Price £7.10.0
Ready Built £9.17.6
p & p 3/6

ELECTROSURE LTD., Fore Street, Exeter

CLEAR PLASTIC PANEL METERS



First grade quality, Moving Coil panel meters, available ex-stock. S.A.E. for illustrated leaflet. Discounts for quantity. Available as follows:

Type MR. 38P. 1 21/32in. square fronts.			
50μA	32/6	1A D.C.	22/6
100μA	29/6	5A D.C.	22/6
200μA	27/6	3V D.C.	22/6
500μA	25/-	10V D.C.	22/6
50-0-50μA	29/6	20V D.C.	22/6
100-0-100μA	27/6	50V D.C.	22/6
500-0-500μA	22/6	100V D.C.	22/6
1-0-1mA	22/6	150V D.C.	22/6
1mA	22/6	300V D.C.	22/6
2mA	22/6	500V D.C.	22/6
5mA	22/6	750V D.C.	22/6
10mA	22/6	15V A.C.	22/6
50mA	22/6	50V A.C.	22/6
100mA	22/6	150V A.C.	22/6
150mA	22/6	300V A.C.	22/6
200mA	22/6	500V A.C.	22/6
300mA	22/6	"S" Meter	
500mA	22/6	1mA	29/6
750mA	22/6		
Type MR.52P. 2¾in. square fronts.			
50μA	57/6	100mA	32/6
100μA	47/6	1A D.C.	32/6
500μA	37/6	300V D.C.	32/6
50-0-50μA	57/6	300V A.C.	32/6
100-0-100μA	47/6	"S" Meter	
1mA	32/6	1mA	39/6
10mA	32/6		
Type MR.65P		**3¾ × 3¼in. fronts**	
50μA	59/6	1mA	35/-
100μA	49/6	10mA	35/-
500μA	39/6	100mA	35/-
50-0-50μA	59/6	1A D.C.	35/-
100-0-100μA	49/6	300V D.C.	35/-
VU meter	59/6	300V A.C.	35/-
Type MR-85P 4½in. × 4¼in. FRONTS			
50μA	69/6	1mA	45/-
100μA	59/6	10mA	45/-
200μA	55/-	50mA	45/-
500μA	49/6	100mA	45/-
50-0-50μA	69/6	1 amp D.C.	45/-
100-0-100μA	59/6	5 amp D.C.	45/-
500-0-500μA	49/6	300 V A.C.	45/-
1-0-1mA	45/-	300V D.C.	45/-

POST EXTRA

BAKELITE PANEL METERS



First grade quality 3¼in. square fronts.

5mA	29/6		
10mA	29/6		
50mA	29/6		
100mA	29/6		
1A D.C.	29/6		
5A D.C.	29/6		
25μA	65/-	*1A A.C.	29/6
50μA	42/6	*5A A.C.	29/6
100μA	39/6	*10A A.C.	29/6
500μA	35/-	*30A A.C.	29/6
50-0-50μA	42/6	*50A A.C.	29/6
100-0-100μA	39/6	300V D.C.	29/6
50mv.	39/6	*300V A.C.	29/6
100mv.	39/6	300V A.C.	35/-
1mA	29/6	VU Meter	49/6

*Moving iron, all others moving coil

POST EXTRA.

ILLUMINATED "S" METERS

Cal. in "S" units. 1mA basic. 1 21/32in. sq. front 29/6. P. & P. 1/-. Ditto, 2¼in. sq. front, 39/6. P. & P. 1/-.


SEMI-AUTOMATIC "BUG"



Super speed key. 7 speed adjustments. 10WPM to as high as desired. Weight scale for reproductible settings. Precision tooled, anti-rust nickel plated brass and stainless steel operating parts. Size 6¼in. × 3in. × 2¼in. Brand New **84/10/-**. P. & P. 2/6.

BEST BUY!

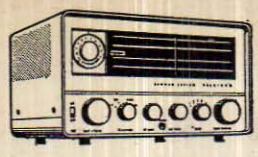Send 1/- P.O. for full Catalogue and Lists. Open 9 a.m. to 6 p.m. every day Monday to Saturday. Trade supplied.



NEW LAFAYETTE COMMUNICATION RECEIVER

MODEL HA-63. only £27.10.0. Carr. 10/-.

● 7 valves plus metal rectifiers ● 4 bands covering 550 kc/s.-31 mc/s. ● Illuminated "S" Meter ● 1.5 Microvolt Sensitivity ● Electrical bandspread ● Aerial trimmer ● Noise limiter ● B.F.O. ● R.F. stage ● Big slide rule dial ● Output or headphones or 4/8Ω speaker ● Modern steel cabinet size 13in. × 7 4/5in. × 10in. ● Operation 220/240 volt A.C. S.A.E. for Full Details. Matching Speaker in Cabinet 55/-.

FULL RANGE OF OTHER LAFAYETTE RECEIVERS IN STOCK

MODEL HE-40. 4 Bands, 550 kc/s to 30 Mc/s. **£19.19.0.** Carr. 10/-

MODEL HE-30. 9 Valves, 4 Bands, 550 kc/s to 30 Mc/s. **£35. 0.0.** Carr. 10/-

Each receiver supplied brand new and fully guaranteed complete with manual. All models for operation on 220/240 volt A.C. S.A.E. for illustrated leaflet. Generous part exchange allowances.

MODEL DA-I TRANSISTORISED FULLY AUTOMATIC ELECTRONIC KEYER



230V. A.C. or Battery operated. Incorporates built-in monitor oscillator, speaker and keying lever. Fully adjustable speeds giving either auto., semi auto. or hold. 7 transistors, 4 diodes. **£16/10/-.** P. & P. 4/6.

MINIFLUX ¼-TRACK TAPE HEADS


Set of three, record, playback, erase. Only **29/6** set. P. P. 9d.

TS-76 20,000 O.P.V. PUSH BUTTON MULTI-TESTER



Large clear plastic scale, simple operation, D.C. volts up to 1,000 v. A.C. volts up to 1,000 v. Resistance up to 10 megohm. Current up to 250 mA. Decibels — 20 to + 36 db. Size 6in. × 4⅛in. × 2¼in. Complete with leads, batteries and instructions. Only **£5/5/0.** P. & P. 2/-.

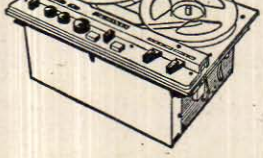PROFESSIONAL 4-TRACK STEREO RECORD AND PLAYBACK TAPE DECK



Complete with 4 valve/4 transistor preamplifier. Will record and playback ¼ track stereo or ¼ track mono at 7½ or 3¾ IPS. Twin meter level indicators, digital counter. Mic/gram/tuner inputs. Audio output 500 MW. Bias and Erase 80 Kc. Response 40-18,000 CPS at 7½; 40-12,000 CPS at 3¾ IPS. Motor 4 pole H.D. induction. Tape size up to 7 in. 220/240v A.C. Size 15" × 10½" × 6½". Line up: 4 × 28B173, 2 × 12AT7, 1 × 12 AU7, 1 × 12 BH7.

S.A.E. FOR FULL DETAILS

PRICE 42 GNS. CARR. 15/-.

AR.88 L.F. RECEIVERS

New release. 75-550 Kc/s and 1.5-30.5 Mc/s on 6 bands. 110/230 v. A.C. operation. Available in excellent condition, fully tested and checked. **£35** each. Carr. 30/-. A few AR.88D model receivers available in as new condition. **£65** each. Carr. 30/-.

ERSKINE TYPE 13 DOUBLE BEAM OSCILLOSCOPE

Time base 2 c/s-750 kc/s. Calibrators at 100 kc/s and 1 Mc/s. Separate Y1 and Y2 amplifiers up to 5.5 Mc/s. Operation 110/230 volt A.C. Supplied in perfect working order. **£27/10/-.** Carriage 20/-.

DOUBLE BEAM C.R.T.s. Cossor 89D. **59/6.** P.P. 4/6. Dumont K1051P1. **59/6.** P.P. 4/6.

MULTI-METERS



Brand New—Fully Guaranteed—Lowest ever prices

Supplied with leads, batteries, instructions

MODEL PT-34. 1,000 O.P.V. 0/10/50/250/500/1,000 v. A.C. and D.C. 0/1/100/500 MA. D.C. 0/100kΩ. **39/6.** P. & P. 1/6.

MODEL 500. 30,000 o.p.v. 0/.5/1/2.5/10/25/100/250/500/1,000V D.C. 0/2.5/10/25/100/250/500/1,000V. A.C. 0/50μA/5/50/500mA 12 amp. D.C. 0/60K/6 Meg/60 MegΩ. **£8/17/6** Post Paid.

MODEL NH-400 10,000 O.P.V. 0/.3/3/30/120/300/600/1,200 v. D.C. 0/12/60/120/300/1,200 v. A.C. 0/120μA/30/300 MA. D.C. 0/2K/200K/2 Meg.Ω. 100 PF.—.2 MFD **79/6.** P. & P. 2/6.

MODEL AR-620 20,000 O.P.V. 0/10/50/250/500/1,000 v. A.C. and D.C. 0/500μA/10/250 MA. 0/10K/100k/1 Meg.Ω. 250 PF—.02 MFD. 0.500 Henrys **92/6.** P. & P. 2/6.

MODEL NH-201 30,000 O.P.V. 0/.25/1/10/50/250/500/1,000 v. D.C. 0/10/50/250/500 v. A.C. 0/50μA/10/250 MA. 0/5K/500K/5 MegΩ. **99/6.** P. & P. 2/6.

MODEL ITI-2. 20,000 O.P.V. 0/5/25/250/500/2,500 v. D.C. 0/10/50/500/1,000 V. A.C. 0/50μA/25/250 mA. D.C. 0/60K/6 Meg. Ω. .01-3 MFD. **82/6.** P. & P. 2/6.

MODEL TE-12 20,000 O.P.V. 0/.06/6/30/120/600/1,200/3,000/6,000 v. D.C. 0/6/30/120/600/1,200 v. A.C. 0/60μA/6/60/600 MA. 0/6K/600K/6 Meg./60 Meg. Ω. P.P.-2 MFD. **£5/19/6.** P. & P. 2/6.

MODEL 250J. 2,000 O.P.V. 0/10/50/500/2,500 V.D.C. 0/10/50/500/2,500 V.A.C. 0/2 MegΩ. 0/250 mA. — 20 to + 36 db. **94/6.** P.P. 2/6.

FIELD TELEPHONES "F"

2 line connection, generator bell ringing. Complete telephone intercom. Supplied fully tested complete with batteries, **£4/19/6** per pair. Carr. 5/-.

TE-20A R.F. SIGNAL GENERATOR

A precision signal generator of extremely high accuracy and quality. Six ranges from 120 kc/s to 130 Mc/s. on fundamentals with calibrated harmonics from 120 to 390 mc/s. 400 cps. INT. MOD. OR EXT. MOD. OUTPUTS, MOD R.F. UNMOD. R.F. OR 400 c/s audio R.F. output in excess of 100 mv. Large clear 5-inch dial. Handsome grey metal case with handle. Size 7¼in. × 10⅝in. × 4¼in. Complete with leads. Operation 220/240 volts A.C. Supplied brand new and guaranteed. **£12/19/6.** Carr. 5/-.

MARCONI TF 144G/4 STANDARD SIGNAL GENERATORS

First release of this late mark. 85 kc/s to 25 Mc/s. ±1%. Output variable from 1μV. to 1 volt. Internal sine wave, modulation 400 c/s up to 75% depth. Operation 200/250 volt A.C. Offered in really excellent condition, like new, fully tested and guaranteed, **£25.** Carr. 30/-

SILICON RECTIFIERS

250 v. P.I.V. 750mA.	3/-
400 v. P.I.V. 3 amp.	7/6
200 v. P.I.V. 6 amp.	5/6
1,000 v. P.I.V. 650 mA	7/6
800 v. P.I.V. 500mA.	5/6
400 v. P.I.V. 500mA.	3/6
200 v. P.I.V. 200 mA.	3/-
95 v. P.I.V. 3 amp.	5/6
70 v. P.I.V. 1 amp.	3/6
150 v. P.I.V. 165mA.	1/-

Discounts for quantities. Post extra.

MINE DETECTOR No. 4A

Will detect all types of metals. Fully portable. Complete with instructions. **39/6.** Carr. 10/-. Battery 8/6 extra.

NEW LOW IMPEDANCE HEADSET

Latest Military type. Rubber moulded fitted with std. jack plug. Brand new boxed, **17/6.** P. & P. 1/6.

MOVING COIL PHONES

Chamois padded ear muffs, with Jack plug. New boxed, **22/6.** P.P. 1/6. Ditto with moving coil microphone **25/-.** P.P. 2/6.

AUTO TRANSFORMERS

Step up or step down. Tapped 0/115/200/230/250V. 20W. **9/-**; 60W. **12/6**; 75W. **15/6**; 150W. **18/6**; 200W. **27/6**; 300W. **42/6**; 500W. **67/6**; 1,000W. **90/-**; 1,500W. **£6/19/6**; 3,000W.* **£7/10/-**; 7,500W.* **£15.** (*Only tapped 0/110/230V.) Post extra.

LAYFAYETTE HI-FI STEREO HEADPHONES



★ **Air cushioned headband** ★ **Soft rubber ear pads.** ★ **Frequency response,** 25 to 15,000 cycles. ★ **High sensitivity.** Impedance 8 ohms per phone. Supplied complete with all cables, wires, overload junction box and 3-connection plug. **82/6.** P. P. 2/6.

2 WAY RADIOS



New Improved Models. **TYPE 1.** 3 transistor. Range up to 1 MILE **£8/17/6** per pair.

TYPE 2 9 transistor. Range up to 5 miles. **£21** per pair.

Postage extra. S.A.E. for full details.

G.W. SMITH & CO (RADIO) LIMITED

Phone: GERRARD 8204/9155

Cables: SMITHEX LESQUARE

3-34 LISLE STREET, LONDON, W.C.2



T615 PORTABLE
12v. TRANSISTOR
AMPLIFIER
15wt. OUTPUT
INBUILT MICROPHONE
PRE-AMPLIFIER

Details and Nearest Stockist from:

Messrs. E. K. ELECTRONICS (I.A.) LTD.
BROTHERTON HALL, BROTHERTON
KNOTTINGLEY, YORKSHIRE

HEAVY DUTY SHROUDED AUTO TRANSFORMERS, 240-110 V. Fitted with 2 pin American sockets or terminal blocks. State which type. Brand new and Guaranteed. 1,000 watts, **£4.15.0**, carr. 5/-; 500 watts, **£3.10.0**, carr. 4/-; 300 watts, **£2.7.6**, carr. 3/6; 150 watts, **£1.17.6**, carr. 3/-.

2 KV. In metal case, with handle, 2 American socket outputs, **£9.10.0**. Carr. 7/6.

EX-MINISTRY INDUSTRIAL TYPES. Tapped 250, 240, 230, 220, 120, 115, 110, 105 volts 10 KVA, **£29.10.0**; 5 KVA **£19.10.0**. Ex warehouse. Both types enclosed in heavy metal case.

We have London's largest selection of Low Tension Transformers, Variable Voltage Transformers, Smoothing Chokes, Capacitors, Sliding Resistors, Low Tension D.C. Supply Units. Send for lists now, or visit our walk round dept., where we have thousands of genuine electronic bargains.

L.T. TRANSFORMERS

Pri. tapped 200-260 v. Sec. tapped 28, 29, 30, 31 v. 25 amps, conservatively rated, **£6.19.6**, carr. 10/-; Pri. 200-250 v. Sec. 25-0-25 v. 7 amps, pri. earth shielded, **£5.17.6**, carr. 7/6; Pri. tapped 200, 225, 240 v. Sec. tapped 12, 18, 24, 30, 36 v. 10 amps, **£5.15.0**, carr. 7/6; Pri. 240 v. Sec. tapped 4, 6, 11 v. 200 amps, **£10.19.6**, carr. 10/-; Pri. 240 v. Sec. tapped 53.5, 55.2 v. 6 amps, **£3.17.6**, carr. 7/6; Pri. 220-240 v. Sec. tapped 6-12 v. 20 amps, **£3.12.6**, carr. 6/-. Pri. 230 v. Sec. 70 v. 5 amp. "C" core sealed, **£4.5.0**, c. 7/6. Hundreds more available. Send for list now.

SAMSON'S ELECTRONICS LTD.
9-10 CHAPEL STREET
Tel. PAD 7851 LONDON, N.W.1. Tel. AMB 5125

All you need to know for a sound grasp of electronics—in one comprehensive volume . . .

ELECTRONICS POCKET BOOK

Edited by **J. P. Hawker** and **J. A. Reddihough**

Specialist Contributors: Ian D. L. Ball, B.Sc., Maurice C. Bumstead, A.M.I.E.E., A.M.Brit.I.R.E. John Gilbert, Assoc.Brit.I.R.E., Terence L. Squires, A.M.Brit.I.R.E.

294 pages

203 diagrams

FULLY COVERS . . .

FUNDAMENTALS: Behaviour of Electrons in Electric and Magnetic Fields—Emission of Electrons—Conduction and Current-Voltage Relationships. **CIRCUIT ELEMENTS:** Diodes—Thermionic Triodes—Tetrodes and Pentodes—Thyratrons—The Transistor—Four-Layer Semiconductor Devices—Cathode-Ray Tubes—Electron Multipliers—Hall Multiplier—Thermistors and Non-Linear Elements—Photo-Electric Cells—Transducers. **ELECTRO-MAGNETIC DEVICES:** Solenoids—Relays. **AMPLIFIER CIRCUITS:** Voltage Amplification—Distortion—Bandwidth—Power Amplifiers—Classification of Amplifiers—Feedback—Special Circuits—D.C. Amplifiers. **PULSE CIRCUITS:** Self-Oscillating Pulse Generators—Single-Stroke Pulse Generators—Sawtooth Voltage Generators—Wide-Range Pulse Generators. **FURTHER ELECTRONIC CIRCUITS:** Electronic Switching—Diode Clamps—Phase-Sensitive Detectors—Pulse Modulation. **COUNTING DEVICES AND CIRCUITS:** Counting Circuits—Radiation Detectors. **POWER SUPPLIES:** A.C. Rectification — Rectifier Circuits — Ripple Reduction — Voltage Regulation — D.C. Converters. **THE MAGNETIC AMPLIFIER, ELECTRONIC MEASUREMENT AND TEST GEAR:** The Moving Coil Meter—Valve Voltmeters—Resistance and Impedance Measurement—Measurement of Non-Electrical Quantities—Cathode-Ray Oscilloscopes—Frequency Measurement. **INDUSTRIAL ELECTRONIC CONTROL:** Thyratron Control—The Silicon Controlled Rectifier—Electronic Ward-Leonard Systems—The Ignitron—The Nevitron—Cold-Cathode Tubes—Sensing Systems. **ELECTRONIC COMPUTERS:** Digital Computers—Analogue Computers. **INSTALLATION AND MAINTENANCE:** Installation—Maintenance. **UNITS.**

Only 21s. FROM ALL BOOKSELLERS
or, in case of difficulty 22s. 3d. by post from George Newnes Ltd., Tower House, Southampton St., London, W.C.2.

NEWNES

BATTERY ELIMINATORS

The ideal way of running your TRANSISTOR RADIO, RECORD PLAYER, TAPE RECORDER, AMPLIFIER, etc. Types available: 9v; 6v: 4½v (single output) 39/6 each. P. & P. 2/9.
9v + 9v; 6v + 6v; or 4½v + 4½v (two separate outputs) 42/6 each. P. & P. 2/9. Please state output required. All the above units are completely isolated from mains by double wound transformer ensuring 100% safety.

R.C.S. PRODUCTS (RADIO) LTD.
11 Oliver Road, London, E.17

"PRACTICAL ELECTRONICS" CONSTRUCTIONAL DESIGNS

All specified 1st grade Components, complete Metalwork, full range of Materials, engraved Panel Plates, Ancillary Equipment and Assembled Units. *Comprehensive lists available for each "P.E." Constructional Article.*
Please send 6d in stamps for each design

MALVYN ENGINEERING WORKS
Engineers to the Radio and Electronic Industries
7 CURRIE STREET, HERTFORD, HERTS
TELEPHONE : HERTFORD 2264

T.V. TUBES

17in. – 35/- 14in. – 15/-

Most makes and types available. Set Tested. Guaranteed good picture. Ex Rental Service Depts. Stock. Carriage 5/- extra.

SEND FOR LATEST FREE LIST

DUKE & CO. (LONDON) LTD.
621/3 Romford Rd., Manor Park E.12 ILFord 6001-2-3

AN EXTRA ROOM IN YOUR LOFT



Make your loft usable. Fit a Benson disappearing loft ladder. Rigidly constructed. Folds out of sight. Closes trap automatically.

ONLY **£12-19-6** carr. paid

Handrails 25/- each extra
ALL TYPES OF LADDERS SOLD

Write now for illustrated brochure, floor strengthening details and terms—all post free

BENSON (LOFT) LADDERS
(Dept. P.E.), Pontefract Ave., Pontefract Lane, York Road, Leeds 9
Tel. 34918 (2 lines)

TRAINING

Full-time courses in RADAR and RADIO-TELEGRAPHY for prospective marine Radio Officers. Govt. approved exam. centre.

Also courses in basic ELECTRONICS, RADIO, TELEVISION and PRACTICAL SERVICING.

Apply:—Director, British School of Telegraphy, 20 Penywern Road, Earls Court, London, S.W.5

RES/CAP. BRIDGE 39/6 p. & p. 2/6

Checks all types of resistors, condensers 6 RANGES
Built in 1 hour. Direct reading
READY CALIBRATED
Stamp for details of this and other kits

RADIO MAIL (Dept. CB)
Raleigh Mews, Raleigh St., Nottingham

FOOTBALL POOL COMPUTER

Novel low-cost circuit for forecasting

Analogue Computer. Multiplication and division by electrical analogue. Simple demonstration of computer principles. Both above circuits for 3/6 post free.

Noughts and Crosses Machine. Full circuit and instructions for our fabulous design 3/6. Cannot be beaten!

Multimeter Kit. 18,000 o.p.v. 25 range kit with Weston 50 μA meter, only 65/-. (2.5A range 4/- extra). Stamp for details.

Multimeters. Illus. leaflet on request. TK20A, 1,000 o.p.v. 33/-, post 1/6; EP10K, 10,000 o.p.v. 69/6, post 1/6; EP30K, 30,000 o.p.v. 95/6, post 2/-; EP50K, 50,000 o.p.v. 130/-, post 2/6.

High Stab. Resistors, ½W, 1%, 2/-.

PLANET INSTRUMENT CO.
25 DOMINION AVENUE, LEEDS 7

EVERYTHING YOU NEED...

from

direct TV Replacements LTD

Dept. P.E., 126 Hamilton Road, West Norwood, London, S.E.27
Telephone: GIPsy Hill 6166 (PBX)

● **The DTV Group hold the largest stocks of the widest range of rectifiers, valves, test equipment, transformers, components and accessories of all kinds. Send s.a.e. for free lists. Terms of Business: C.W.O. or C.O.D.**

TRANSDUCERS

As specified for use in the Ultrasonic Control System featured in this issue.




Gulton Transducers can be used for simple remote control without cables or electronic links, two units only being required. The Transducers are suitable for both transmitting and receiving. Ideally suited for the experimenter and designer for remote control systems of all kinds. Free TX/RX circuit with each order.

55/- each or two for £5

Components for use with the Transducers:

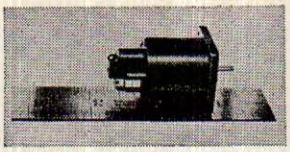QHF9 Transformer .. .. 4/- each
Set of 3 transistors 15/-
Low current reed relay .. 24/- each (7v.9mA)



MICRO-MOTORS

This new Sleyride Motor is precision made and prototype tested by RAE Farnborough. Only 1 in. dia., 2 in. long and weighs only 1.3 oz. Rated 1/1,000 h.p., normal running speed 5,000 r.p.m. Spindle dia. 3/32 in., length 11/32 in. For 1½, 6 or 12 v. Reversible.

25/- each
plus 1/6 p. & p.

TRANSISTOR TESTER

The Unique

D.909



Tests Alpha Gain (A.C. Gain) and Beta Gain (D.C. Gain) with transistors in place. Facilities also provided for testing leakage between Collector and Emitter and Collector Base. Exclusive Variable Voltage Smoothed D.C. Power Supply, continuously variable from 0/25 v. up to 25mA. Output voltage can be used as centre-tapped voltage supply enabling modern transistorised receivers to be tested. **£10** each

Send S.A.E. for detailed leaflet

TRANSISTORS

AC113	5/6	OA79	3/-	OC74	8/-
AC115	4/-	OA81	2/-	OC75	5/6
AC155	4/-	OA85	3/-	OC76	8/6
AC156	5/6	OA86	4/-	OC78	8/-
AC154	5/6	OA90	3/-	OC79	8/-
AC157	7/-	OA91	3/-	OC81	5/6
AD140	25/-	OA95	3/6	OC82	10/-
AF102	27/6	OC16W	35/-	OC83	4/-
AF114	11/-	OC19	25/-	OC84	8/-
AF115	10/6	OC26	25/-	OC139	8/-
AF116	5/-	OC35	12/-	OC140	19/-
AF117	9/6	OC36	21/6	OC141	31/-
AF118	20/-	OC41	8/-	OC169	10/-
AF124	11/-	OC42	6/-	OC170	8/6
AF125	10/6	OC43	12/6	OC171	6/-
AF126	10/-	OC44	5/-	OC200	10/6
AF127	9/6	OC45	5/-	OC201	29/-
BY100	7/6	OC70	6/6	OC202	24/6
BY114	6/-	OC71	4/3	OC203	13/-
GET113	6/9	OC72	5/6	OC204	19/-
GET114	6/6	OC82	8/-	MAT100	7/9
GET115	9/6	2xOC72		MAT101	8/6
GET116	17/-	matched pair	16/-	MAT120	7/9
OA70	3/-	OC73	16/-	MAT121	8/6
OA73	3/-			ADT140	15/-

SETS OF TRANSISTORS

Set No. 1: comprising OC44, 2 × OC45, OC81, matched pair OC81 20/-.

Set No. 2: comprising OC81, matched pair OC81 12/6.

CATALOGUE

Our latest 1964/65 Catalogue is now available. Copies have been sent to many of our regular customers. If you have not received your copy please drop us a card. Please send 1/- in stamps.

TERMS: Cash with Order or C.O.D. Postage and Packing Charges extra. Single valves 9d., Minimum Parcel Post charges 2/-. Please include sufficient postage with your order. Minimum C.O.D. fees and postage 3/6. These Postal Rates apply to U.K. only. For full terms of business see inside cover of catalogue. Personal shoppers 9 a.m. to 5 p.m. Mon. to Friday, Saturday 10 a.m. to 1 p.m.

ALPHA

RADIO SUPPLY CO.

103 LEEDS TERRACE
WINTOUN STREET
LEEDS 7



MICROPHONES		MULTI-RANGE TESTMETERS	
MIC 39/1	32/6	Eagle TK30A	£2.9.6
MIC 40	19/6	Leather Case for above	19.6
MIC 45 GK	19/6	Eagle EP50K	£9.19.6
Foster DFI Dynamic 600 ohms	39/6	Leather Case for above	£1.9.6
Foster DFI Dynamic 50K ohms	39/6	Caby MI	£2.14.0
DX 62 Dynamic	69/6	Caby A10	£4.17.6
DX 29	49/6	Caby B40	£6.2.6
CM21 Planet	12/6	Altham 200H	£5.5.0
DM175 Dynamic	49/6	Taylor 127A	£10.10.0
DM11 Dynamic	105/-	Leather Case for above	£2.5.0
GCM5 Guitar	12/6		
BM3	45/-		

All the above are listed and illustrated in our current catalogue along with mic. stands, etc.

MAINS TRANSFORMERS	Primaries 200/230/250V	
230-0-250v 80mA 0-4-6.3v	4A 0-4-5v 2A	21/9
300-0-300v 80mA 0-6.3v	4A 0-6.3v 1A	22/6
350-0-350v 80mA 0-4-6.3	4A 0-4-5v 2A	21/9
250-0-250v 100mA 0-6.3v	4A 0-5v 2A	27/6
350-0-350v 100mA 0-6.3v	4A 0-5v 2A	27/6
350-0-350v 200mA 0-6.3v	4A 0-5v 3A	55/-

BIG REDUCTIONS IN EAGLE RANGE

TP.703	Tape Recorder	£16.16.0	UD.19HL	Microphone	£12.12.0
TL.206	Intercom	£3.19.6	MM4	Microphone Mixer	£2.9.6
TA.790	Telephone Amplifier	£2.19.6	K4.16	Volume Control	3.0
100C	Microphone	£1.12.6	PVC.105	Variable Condenser	3.0
DM.614	Microphone	£1.12.6	TP.100	Telephone PU Coil	9.6
MC.70	Microphone	£2.12.6	MC.1	Crystal Cartridge	4.6
DM.14S	Microphone	£3.2.6	EP.10K	10,000 OPV Multimeter	£3.19.6
DM.17HL	Microphone	£4.2.6	MR.2P	500 uA Panel Meter	£1.9.6
DM.16HL	Microphone	£4.9.6	OMB.	Capacitance Sub Box	£1.2.6
SMD.100	Microphone	£6.19.6	OMG.	Resistance Sub Box	£1.12.6

IN ADDITION WE ARE NOW STOCKING:

FMT.640	F.M. Tuner	£19.19.0 + £3.4.0 Tax	OC.34	Standard Socket	2.0
			EC.36	Hi-Fi Cable	14.0
P.31	Standard Plug	2.6	SE.25	Hi-Fi Extension Cord	18.6
SP.31	Standard Shield Plug	3.6	EC.25	Microphone Extension Cord	£1.9.6


MULTI-RANGE TESTMETERS

Eagle TK20A, £2.9.6. Eagle EP10K, £4.9.6. Eagle EP20K, £4.19.6. Eagle EP30K, £6.19.6. Leather Case for above, 19.6. Eagle EP50K, £9.19.6. Leather Case for above, £1.9.6. Caby M1, £2.14.0. Caby A10, £4.17.6. Caby B40, £6.2.6. Altham 200H, £5.5.0. Taylor 127A, £10.10.0 Leather Case for above, £2.5.0.

RECORD PLAYER AND TAPE DECK UNITS

B.S.R. Monarch UA14, £6.6.0. Stereo Version, £6.17.6. B.S.R. Monarch UA15, £6.19.6. Stereo Version, £7.15.0. B.S.R. Monarch TU12, £3.10.0. Battery version of above, £3.17.6. B.S.R. Monarch GU7, £3.17.6. Battery version of above, £4.4.0. B.S.R. Monarch TD2 Tapedeck, 2 track, £8.8.0. 4 track version of above, £9.9.0. Garrard Autoslim, £6.19.6. B.S.R. Monarch TD10 Tapedeck, 2 track, £9.9.0. 4 track version of above, £10.10.0. Garrard Autoslim De Luxe Model AT6, £11.5.0.

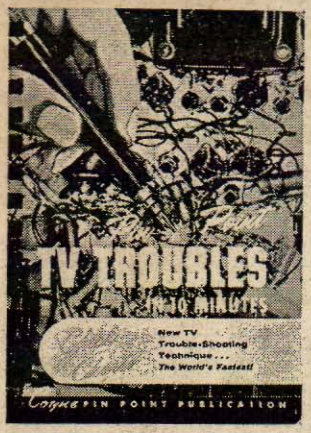TAKES HEADACHES OUT OF ALL SERVICING PROBLEMS



Your most useful' on-the-job "tool"! Quickly and easily pin-points the exact trouble in any TV set. Covers 70 symptoms, 700 trouble spots. Over 340 cross-indexed pages; 50 time-saving Check Charts; 290 diagrams and photos; explanation of circuits and designs.

SIMPLE CHECK-CHART SYSTEM SAVES TIME !

This amazingly practical handbook shows you how to find the trouble in any TV circuit FAST! Simple cross-index tells you in what section you'll find cause of trouble. Handy Check-Charts then help you accurately locate the EXACT trouble spot. Cut waste time, eliminate hours of aggravation, get right to the heart of the trouble in minutes.

USE THIS BOOK RIGHT ON THE JOB— NO NEED TO MEMORIZE!

This Pin-Point Book was designed especially for on-the-job trouble-shooting. You simply turn to the indexed section, locate the circuit description and Check-Chart, and in minutes you have the trouble spot located and ready for repair. No complicated theory or mathematics. Down-to-earth, practical circuit description, service methods and trouble-shooting techniques. Published by the famous Coyne Electrical School and approved by leading authorities in the field. Don't miss out any longer. Time wasted now locating T.V. faults could be saved by quick reference to this lightning fast T.V. problem answer book. Send for your trial copy now, then when you decide to keep it (as we are sure you will), pay only 5/- per week until completed.

The price? Only 39/6 plus postage 1/6.

FREE ELECTRONIC DATA HANDBOOK WITH EVERY ORDER

IRONCLAD GUARANTEE

This book must be able to earn you more than its cost within two weeks or your money refunded!
Free 88 page oscilloscope book will be included if you send cash with order.

FREE TRIAL OFFER!

TERMS ONLY 5/- PER WEEK

To SIM-TECH TECHNICAL BOOKS
Dept. ETV2
West End, Southampton, Hants.

☐ Please send "T.V. Troubles" for a full seven days' free trial. If not delighted I may return the manual, post paid without further obligation on my part. Otherwise I will pay cash of 5/- weekly until paid.

☐ Tick here if enclosing full price of 41/- (which includes 1/6 postage). You get free Oscilloscope Book. Same 7-day money back guarantee. Overseas customers please send full amount (including Ireland).

Name .....

Address .....

.....

City ..... County.....

CLEARANCE SALE



MAKE 5 DIFFERENT TRANSISTOR RADIOS for 35/-

Amazing Radio Construction Set! Become a radio expert for 35/-. A complete Home Radio Course. No experience needed. Parts include instructions for each design, Step-by-Step plan, all Transistors, loudspeaker, personal phone, knobs, screws, etc., all you need. Box size 14" × 10" × 2" (parts avail. sep.). Originally £6. **NOW 35/- + 3/- P. & P. (3/- C.O.D.)**

ASTONISHING CIGARETTE RADIO 18/6 only



Yes, a perfectly ordinary packet of cigarettes!—but watch your friends astonishment on hearing it fetch in station after station, loud and clear! Still holds 10 Cigarettes—yet cleverly conceals highly sensitive, fully transistorised circuit (including tiny battery). Even a young boy can assemble it in under 2 hours. No soldering. **No experience necessary.** Only 16 connections to make. Ideal for taking to work with you. From our bulging testimonial file, Mr. D.B. of Huddersfield writes:—"... *I have fitted the parts in and it is working wonderfully ...*" ALL PARTS including Semi-Conductors, A.B.C. Plans, etc. **ONLY 18/6d. plus 1/6d. post, etc. (C.O.D. 1/6d. ex.)**

CONCORD ELECTRONICS LTD
(P.E.12) **9 Western Road, Hove**

2 METRES 4

The thrills of VHF Amateur Radio can now be yours for as low as 42/6 complete kit (by post, carriage and packing, 2/6 extra). Tuning range 70-150 Mc/s. Stamped addressed envelope for free copy of literature and full details. Newcomers to Short-Wave Radio ask for details of the famous "Globe-King" kits and receivers. Home and Overseas Sales.

JOHNSONS (Radio)
St. Martins Gate, Worcester

BLANK CHASSIS

Precision made in our own works from commercial quality half-hard Aluminium. Two, three or four sided. SAME DAY SERVICE of over 20 different forms made up to YOUR SIZE.

Order EXACT size you require to nearest 1/16" (maximum length 35", depth 4"). *Specials dealt with promptly.* SEND FOR ILLUSTRATED LEAFLETS or order straight away, working out total area of material required and referring to table below, which is for four-sided chassis in 18 s.w.g. (for 16 s.w.g. add $\frac{1}{3}$th)

48 sq. in.	4/-	176 sq. in.	8/-	304 sq. in.	12/-
80 sq. in.	5/-	208 sq. in.	9/-	336 sq. in.	13/-
112 sq. in.	6/-	240 sq. in.	10/-	368 sq. in.	14/-
144 sq. in.	7/-	272 sq. in.	11/-	and pro rata	
P. & P. 2/6		P. & P. 2/9		P. & P. 3/-	

FLANGES ($\frac{1}{2}$", $\frac{3}{4}$" or 1") 6d. per bend.

STRENGTHENED CORNERS 1/- each corner.

PANELS. The same material can be supplied for panels, screens, etc., at 4/6 sq. ft. (16 s.w.g., 5/3) plus P. & P. (over £2 post free)

H. L. SMITH & CO. LTD.
287-289 EDGWARE ROAD, LONDON, W.1
PAD 5298/7595

INSULATION TESTERS (New)

500 volt, 500 megohms. Price £22, carriage paid. 1,000 volts, 1,000 megohms, £28, carriage paid.

SOLENOID. Overall length 3$\frac{1}{4}$in., stroke $\frac{1}{16}$in. to $\frac{1}{4}$in. Maximum push 8 oz. 12-24V. D.C. operation. D.C. resistance 35 ohm. Price 8/6. P. & P. 1/6.

TRANSISTORISED FULLY AUTOMATIC ELECTRONIC KEYER. 230V. A.C. or Battery operated. Incorporates built-in monitor Oscillator, Speaker, and Keying Lever. Adjustable speeds. Keying either auto., semi-auto. or hold. 4 diodes. 7 transistors. Price £16/10/- Plus 4/6 P. & P.

SPECIAL REVERSING 24 VOLT D.C. QUADRANT MOTOR 2 AMPERE. Quadrant moves 90 degrees with limit switches. Ideal for opening doors, etc. Price 32/6. P. & P. 3/-.

CARPENTER POLARISED RELAY. Type 5A13 (Z) 2 × 7,600 turns at 1,000 ohms. New 22/6 P. & P. 1/-. Bases for above 3/6 each.

LATEST HIGH SPEED MAGNETIC COUNTERS, 4 figure, 10 impulses per second. Type 100D, 4.1 ohm coil, 3-6V. D.C. operation. Type 100A, 500 ohm coil, 18-24V. D.C. operation. Type 100B, 2,300 ohm coil, 36-48V. D.C. operation. Any type 15/- each, plus 1/6 P. & P.

RESETTABLE HIGH SPEED COUNTER. 3 figure, 1,500 ohm coil, 40-50V. D.C. operation. Brand new. 50/- each, plus 1/6 P. & P.

BUILD AN EFFICIENT STROBE UNIT FOR ONLY 37/6

The ideal instrument for workshop, lab. or factory. This wonderful device enables you to "freeze" motion and examine moving parts as stationary. We supply a simple circuit diagram and all electrical parts including the NSP2 Strobe tube which will enable you to easily and quickly construct a unit for infinite variety of speeds, from 1 flash in several seconds to several thousands per minute. New modified circuits bring price down to 37/6 plus 3/- P. & P.
NSP2 CV2296 STROBOTRON FLASH-TUBE made by Ferranti, brand new. I.O. base. Price 15/-. P. & P. 1/-.



VARIABLE VOLTAGE TRANSFORMER £4.10.0 *Post Paid*

Input 230v. A.C. Output 0-260v. at 1 amp., fully shrouded, new. Also available 2.5, 5, 8, 10, 12, 20, 37.5 and 50 amp. Write for details.

SIEMENS SEALED HIGH SPEED RELAYS
H96A, 2.2± 2.2 ohm. H96B, 50± 50 ohm. H96C, 145± 145 ohm. H96D, 500± 500 ohm.
All above 12/6
H96E 170± 170 ohm., ex-equip, 16/6

14-DAY CLOCKWORK TIME SWITCHES
USED but guaranteed 5 amp. type, 35/6. P. & P. 2/6.

A.C. AMMETERS
0- 1 amp. F.R. 2$\frac{1}{2}$" Dia. 0-15 amp. F.R. 2$\frac{1}{2}$" Dia.
0- 5 " " 0-20 " "
0-10 " " All at 21/- each

VAN DE GRAAFF ELECTRO-STATIC GENERATOR, fitted with Motor drive for 230v. A.C. giving a potential of approx. 50,000 volts. Supplied absolutely complete, including accessories for carrying out a number of interesting experiments, and full instructions. This instrument is completely safe, and ideally suited for School demonstrations. Price £6.6.0, plus 4/- P. & P.



LIGHT SENSITIVE SWITCH
Kit of parts, including ORP .12 Cadmium Sulphide Photocell, Relay, Transistor and Circuit, etc., price 25/- plus 2/6 P. & P. ORP .12 including circuit, 10/6 each, plus 1/- P. & P.

ULTRA VIOLET BULBS
Easy to use source of UV for dozens of practical and experimental uses.
12 volt 36 watt AC/DC SBC 6/6, P. & P. 1/-.
12 volt 60 watt AC/DC SBC 8/6, P. & P. 1/-.
Transformer to suit the above: Input 200-240 A.C. Output 12 Volt A.C. 36 watt, 16/6. P. & P. 2/6. Input 200-240 A.C. 12 volt A.C. 60 watt, 22/6. P. & P. 3/6.
Set of four colours **FLUORESCENT Paint.** Orange, Yellow, Green and Red, in $\frac{1}{2}$oz. tins. Ideal for use with the above Ultra Violet Bulbs, 9/6. P. & P. 1/6.

SERVICE TRADING CO.

All Mail Orders also callers

47-49 High Street, Kingston on Thames
Tel. KINgston 9450
Personal callers only

9 Little Newport Street, London, WC2
(off Leicester Square) Tel: GERrard 0576

Practical Electronics

DECEMBER 1964 PRICE 2/6

FREE INSIDE

2 BLUEPRINTS

TO BUILD

ULTRASONIC REMOTE CONTROL