PRACTICAL
# ELECTRONICS
AUGUST 1970
PRICE 3/6

# IT COULDN'T BE EASIER!



## Project Building for BEGINNERS

ALSO INSIDE:
ANEMOMETER : DECIMAL CURRENCY CONVERTER

# ADCOLA Soldering Instruments add to your efficiency

## ADCOLA 64

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16″ (4.75 mm) diameter, detachable copper chisel-face bit*.
Standard temp. 360°c at 23 watts.
Special temps. from 250°c—410°c.

***Additional Stock Bits** (illustrated) available

COPPER

- B 38 1/8″ — 3.2 mm CHISEL FACE
- B 14 3/32″ — 2.4 mm CHISEL FACE
- B 24 3/16″ — 4.75 mm SCREWDRIVER FACE
- B 12 3/16″ — 4.75 mm EYELET BIT
- B 58 1/4″ — 6.34 mm CHISEL FACE

LONG LIFE

- B 42 LL 3/16″ — 4.75 mm CHISEL FACE
- B 38 LL 1/8″ — 3.2 mm CHISEL FACE
- B 14 LL 3/32″ — 2.4 mm CHISEL FACE
- B 44 LL 3/16″ — 4.75 mm SCREWDRIVER FACE




**Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service . . . reliability . . . from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.**

ADCOLA (Regd Trade Mark)

* *Write for price list and catalogue*

**ADCOLA PRODUCTS LTD.,**
(Dept. L ), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.
Telephone: 01-622 0291/3 · Telegrams: Soljoint London Telex • Telex: Adcola London 21851

## EX RENTAL TV's

17″ SLIMLINE 405 ONLY £11.10.0

2 YEARS' GUARANTEE

FREE ILLUSTRATED LIST OF TELEVISIONS 17″—19″—21″—23″

19″ SLIMLINE 405/625 BBC 2 39 gns.



WIDE RANGE OF MODELS SIZES AND PRICES *DEMONSTRATIONS DAILY*

CARR. INS. 30/-



**RECORD PLAYER CABINET 49/6**



Cloth covered. Size 16½″ × 14½″ × 7½″ Takes any modern autochanger. P. & P. 7/6.

**TWO-YEAR GUARANTEED REGUNNED TUBES**



70° & 90° 14in.—**79/6**, 17in.—**99/6**, 21in.—**109/6**. 110° 17in., 19in. & 21in. —**109/6**. 23″ (not bonded)—**129/6**. Exchanged Bowls. Carr. 10/6.

**SPEAKERS GALORE. BRAND NEW 10/-.** P. & P. 1/-. 2½″ 8Ω, 3½″ 25Ω, 4″ 10Ω, 3″×5″ 8Ω, 7″×4″ and 8″×3″ 3Ω.

**TRANSISTOR CASES, 4 FOR £1.** Cloth covered, many colours. Size 9½″×6½″×3½″. P. & P. 9/6. Similar cases in plastic.

**RECORD PLAYER & TAPE MOTORS 10/- BRAND NEW** P. & P. 3/6.


**TRANSISTORS 2/6 EACH.** OC44, OC45, OC71, OC81, OC81D, AF114, AF117, AC128.

**DUKE & CO. (LONDON) LTD.**
**621/3 Romford Road, Manor Park, E.12**
Phone 01-478 6001-2-3 Stamp for Free List

## PRINTED CIRCUIT KIT

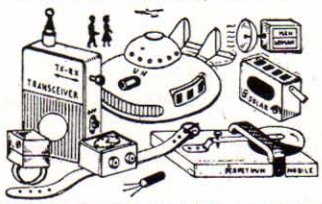**BUILD 40 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX**

CONTENTS: (1) 2 Copper Laminate Boards 4½″ × 2½″. (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleanser/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs*. (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit. (10) Essential Design Data, Circuits, Chassis Plans, etc. for 40 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time, including 10 new circuits.




**EXPERIMENTER'S PRINTED CIRCUIT KIT**

**8/6**

Postage & Pack. 1/6 (UK)

Commonwealth:
SURFACE MAIL 2/-
AIR MAIL 8/-
Australia, New Zealand South Africa, Canada.


(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photocell Radio. (8) "TRI-FLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World. 3 Subminiature Radio Receivers based on the "Triflexon" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1·62″ × ·95″ × ·25″. (11) Wristwatch Radio 1·15″ × ·80″ × ·55″. (12) Ring Radio ·70″ × ·70″ × ·55″. (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P/P Amplifier. (16) Intercom. (17) 1-valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal, Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive-Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wire-less Microphone. (32) Rain Alarm. (33) Ultrasonic Switch/Alarm. (34) Stereo Preamplifier. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Telephone "Photophone". (37) Light-Beam Transmitter. (38) Silent TV Sound Adaptor. (39) Ultrasonic Transmitter. (40) Thyristor Drill Speed Controller.


**YORK ELECTRICS**
**335 BATTERSEA PARK ROAD, LONDON, S.W.11**

*Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects Assembled.*

# SINCLAIR IC-10
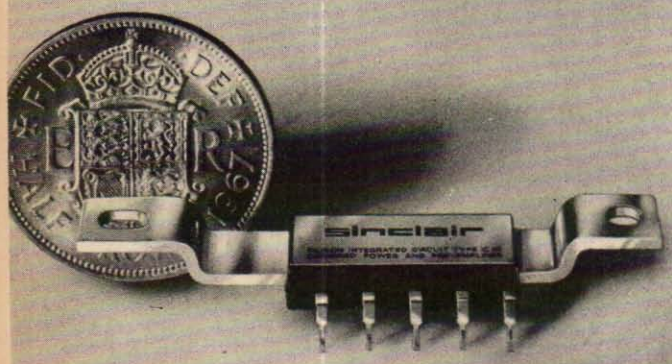
## MONOLITHIC INTEGRATED CIRCUIT AMPLIFIER AND PRE-AMP


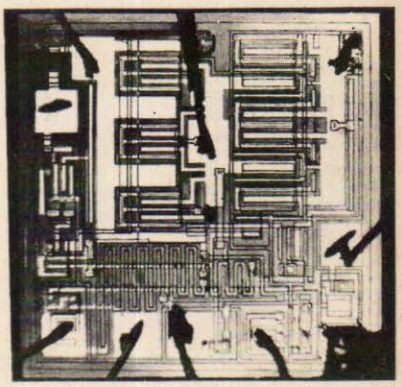
# the world's most advanced high fidelity amplifier

The Sinclair IC-10 is the world's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself, a chip of silicon only a twentieth of an inch square by a hundredth of an inch thick, has an output 5 watts R.M.S. (10 watts peak). It contains 13 transistors (including two power types), 2 diodes, 1 Zener diode and 18 resistors, formed simultaneously in the silicon by a series of diffusions. The chip is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins. This exciting device is not only more rugged and reliable than any previous amplifier, it also has considerable performance advantages. The most important are complete freedom from thermal runaway due to the close thermal coupling between the output transistors and the bias diodes and very low level of distortion.

The IC-10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of such components as tone and volume controls and a battery or mains power supply. However, it is so designed that it may be used simply in many other applications including car radios, electronic organs, servo amplifiers (it is d.c. coupled throughout) etc. The photographic masks required as part of the process of producing monolithic I.Cs are expensive but once made, the circuits can be produced with complete uniformity and at very low cost. This enables us to cover every IC-10 with the Sinclair guarantee of reliability.

### ■ SPECIFICATIONS

| | |
|---|---|
| Output | 10 Watts peak, 5 Watts R.M.S. continuous. |
| Frequency response | 5 Hz to 100 KHz±1dB. |
| Total harmonic distortion | Less than 1% at full output. |
| Load impedance | 3 to 15 ohms. |
| Power gain | 110dB (100,000,000,000 times) total. |
| Supply voltage | 8 to 18 volts. |
| Size | 1 × 0.4 × 0.2 inches. |
| Sensitivity | 5mV. |
| Input impedance | Adjustable externally up to 2.5 M ohms. |

### ■ CIRCUIT DESCRIPTION

The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. Class AB output is used with closely controlled quiescent current which is independent of temperature. Generous negative feedback is used round both sections and the amplifier is completely free from crossover distortion at all supply voltages, making battery operation eminently satisfactory.

### ■ APPLICATIONS

Each IC-10 is sold with a very comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include stabilised power supplies, oscillators, etc. The pre-amp section can be used as an R.F. or I.F. amplifier without any additional transistors.

**SINCLAIR IC.10** *with IC-10 manual* **59/6**

**POST FREE**

sinclair

**SINCLAIR RADIONICS LIMITED**
**22 NEWMARKET ROAD · CAMBRIDGE**
**Tel. 0223 52731**

# Project 60


## laboratory standard modular high fidelity

**Sinclair Project 60** comprises a range of modules which connect together simply to form a complete stereo amplifier with really excellent performance. So good, in fact, that only 2 or 3 amplifiers in the world can compare in overall performance. Now with the addition of three new modules to the range, the constructor has choice of assemblies with either 20 or 40 watts output per channel, with or without filter facilities.

The modules are: **1.** The Z.30 and Z.50 high gain power amplifiers, each of which is an immensely flexible unit in its own right. **2.** The Stereo 60 preamplifier and control unit. **3.** The Active Filter Unit with both high and low audio frequency cut – offs. **4.** The PZ.5 and PZ.6 power supplies. A complete system could comprise, for example, two Z.30's one Stereo-60, and a PZ.5. The PZ.6 is stabilised and should be used where the highest possible continuous sine wave rating is required. An A.F.U. may be added as required. In a normal domestic application, there will be no significant difference between PZ.5 or PZ.6 unless loudspeakers of very low efficiency are being used, in which case the PZ.6 will be required. For assemblies using two Z.50's there is the new PZ.8 supply unit to ensure maximum performance from these amplifiers.

All you need to assemble your Project 60 system is a screwdriver and soldering iron. No technical skill or knowledge whatsoever is required and, in the unlikely event of you hitting a problem, our customer service and advice department will put the matter right promptly and willingly. Project 60 modules have been carefully designed to fit into virtually all modern plinth or cabinets and only holes need be drilled in the wood of the plinths to mount the control unit and A.F.U. Any slight slip here will be covered by the aluminium front panels of the Stereo 60. The Project 60 manual gives all the buildings and operating instructions you can possibly want, clearly and concisely. Perhaps the greatest beauty of the system is that it is not only flexible now but will remain so in the future as the latest additions to the range show. A stereo F.M. tuner is next to come. These and all other modules we introduce will be compatible with those already available and may be added to your system at any time. And because Sinclair are the largest producers of constructor modules in Europe. Project 60 prices are remarkably low.

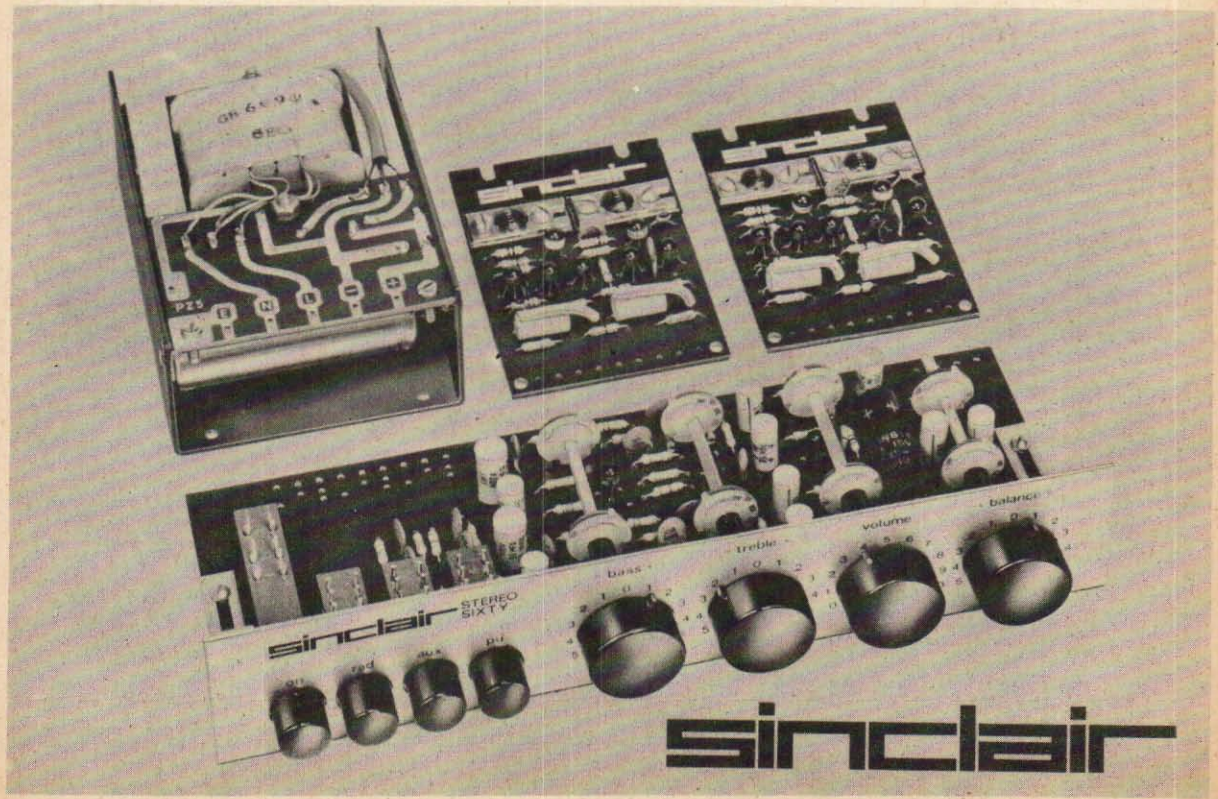**SINCLAIR RADIONICS LIMITED · 22 NEWMARKET ROAD · CAMBRIDGE** **Telephone: 0223 52731**



# Z.30 20 WATT R.M.S. POWER AMPLIFIER (40 WATTS PEAK)

# Z.50 40 WATT R.M.S. POWER AMPLIFIER (80 WATT PEAK)

The Z.30 together with the higher powered Z.50 are both of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0·02% at full output and all lower outputs. Whether you use the Z.30 or Z.50 power amplifiers in your Project 60 system will depend on personal preference, but they are both the same physical size and may be used with other units in the Project 60 range equally well. The Z.30 is unique in that it may be used with any power source between 8 and 35 volts without need for adjustment and may thus be driven from a car battery for example. For operating from mains, for the Z.30 use PZ.5 power supply unit for most domestic requirements, or PZ.6 if you have very low efficiency loudspeakers. For Z.50, use the PZ.5, PZ.6 or the PZ.8 described below.


**Power Outputs**

**Z.30** 15 watts R.M.S. into 8 ohms, using 35V/20 watts R.M.S. continuous into 3 ohms using 30 volts.
**Z.50** 40 watts R.M.S. into 3 ohms: 30 watts R.M.S. into 8 ohms, continuous, using 50V.
**Frequency response** 30 to 300,000Hz ± 1dB
**Distortion** 0·02% into 8 ohms
**Signal to noise ratio** better than 70dB unweighted
**Input sensitivity** 250mV into 100 Kohms
For speakers from 3 to 15 ohms impedance
Size 3¼" × 2¼" × ½"


**APPLICATIONS**

Hi-fi amplifier; car radio amplifier; record player amplifier fed directly from pick-up; intercom; electronic music and instruments; P.A.; laboratory work, etc. Full details for these and many other applications are given in the manual supplied with the Z.30.

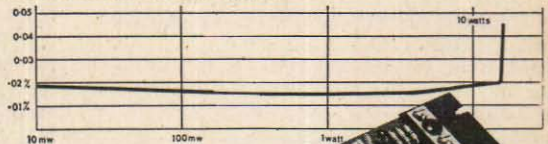***The Z.50 is completely interchangeable with the Z.30 and can be used in all Z.30 applications.***



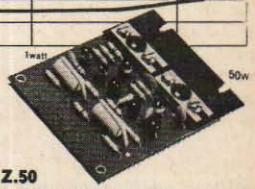
*Power versus distortion curve of Sinclair Z.30 and Z.50 amplifiers*



**Z.30**
*Built, tested and guaranteed with circuits and instructions manual*
**89/6**

**Z.50**
*Built, tested and guaranteed with circuits and instructions manual*
**109/6**

## STEREO 60 Preamp/Control unit


The Stereo 60 is a stereo preamplifier and control unit designed for the Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout and great attention has been paid to achieving a really high signal-to-noise ratio and excellent tracking between the two channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs. The tone controls are also very carefully designed and tested.

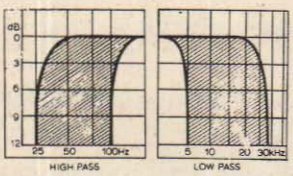
### STEREO 60 SPECIFICATIONS

- Input sensitivities—Radio—up to 3mV Mag. p.u.—3mV: correct to R.I.A.A. curve ±1dB; 20 to 25,000Hz. Ceramic p.u.—up to 3mV: Aux.—up to 3mV.
- Output—250mV.
- Signal-to-noise ratio—better than 70dB.
- Channel matching—within 1dB.
- Tone controls—TREBLE +15 to −15dB at 10KHz: BASS +15 to −15dB at 100Hz.
- Power consumption 5mA.
- Front panel—brushed aluminium with black knobs and controls.
- Size 8½ × 1½ × 4in.



***STEREO 60***
*Built, tested and guaranteed*
**£9.19.6**



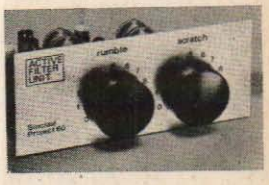




## ACTIVE FILTER UNIT High Pass and Low Pass

For use between Stereo 60 unit and two Z.30s or Z.50s, the Active Filter Unit matches the Stereo 60 in styling and is as easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible by reason of the careful design and generous negative feedback employed.

Two stages of filtering are incorporated—rumble (high pass) and scratch (low pass).
Supply voltage—15 to 35V. Current—3mA
H.F cut-off (−3dB) variable from 28kHz to 5kHz
L.F cut-off (−3dB) variable from 25Hz to 100Hz
Filterslope, both sections 12dB per octave
Distortion at 1kHz (35V supply) 0·02% at rate output

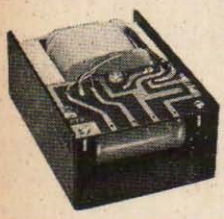**Built, tested and guaranteed**
**£5.19.6**



## SINCLAIR POWER UNITS

**PZ-5** *30 volts unstabilised* **£4.19.6**

**PZ-6** *35 volts stabilised* **£7.19.6**

**PZ-8** *45 volts stabilised (less mains transformer) for use with Z.50* **£5.19.6**



## BUILDING A PROJECT 60 ASSEMBLY

The illustration here shows quite clearly how easily Project 60 can be contained in one of today's slim, modern plinths. Very little space is required to house these Sinclair units, and within the space of the motor plinth, you can install a stereo amplifier of the very highest quality. If, for example you have already put together an assembly as illustrated here, adding the Active Filter Unit would be very easy.

If at any time within 3 months of purchasing Project 60 modules from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

sinclair

**To: SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE**

*Please send* .....
.....
.....
.....
.....


*NAME* .....
*ADDRESS* .....
.....
.....
..... P.E.8/70

*for which I enclose cash/cheque money order*

SINCLAIR

# Q.16
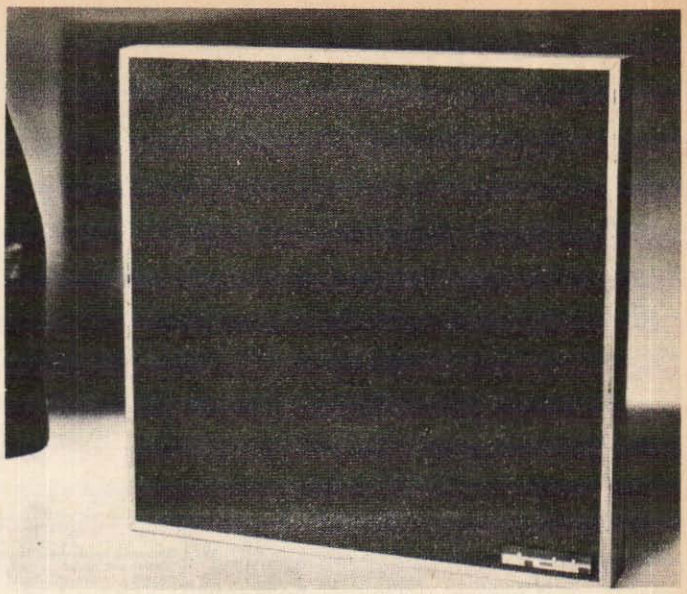
## new elegance in an outstanding loudspeaker



All the superb features which went to make the Sinclair Q.14 have been incorporated in the new Q.16 which gives an exciting new opportunity for you to match your Sinclair equipment with modern decor. Employing the same well proven acoustic system in which materials, processing and styling are used in such a radical and successful departure from conventional design, this speaker presents an entirely new appearance with its attractive teak surround and all-over special cellular foam front chosen as much for its appearance as for its ability to pass all audio frequencies without loss. The Q.16 is compact and slim. Its new styling makes it eminently suitable for shelf mounting, but it is no less versatile than its famous predecessor. Listen to a pair of Q.16s in stereo and marvel at the standards of quality and clarity they give. At the price, this Sinclair speaker represents outstanding value as you will discover the moment you see and hear it.

The Q.16 will handle loading up to 14 watts R.M.S. and presents an 8 ohm impedance to the amplifier output. Frequency response extends from 60 to 16,000 Hz. with exceptional smoothness. A specially designed driver system is used in a sealed and contoured pressure chamber to ensure good transient response at all frequencies. Size: $9\frac{3}{4}$" square × $4\frac{3}{4}$" deep from front to back.

**£8.19.6**
**POST FREE**

# SINCLAIR MICROMATIC

The world's most successful miniature radio




**Specifications**
**Size:**
$1\frac{11}{16}$" × $1\frac{1}{4}$" × $\frac{1}{2}$" (46 × 33 × 13mm).
**Weight incl. batteries:**
1 oz. (28·35gm) approx.
**Tuning:**
Medium wave band with bandspread at higher frequency end.
**Earpiece.**
Magnetic type.
**Case:**
Black plastic with anodized aluminium front panel, spun aluminium dial.

*Complete kit incl. earpiece, case, solder and instructions in fitted pack.*

**49/6**
*Inc. P/Tax*

*Ready built, tested and guaranteed, with earpiece.*

**59/6**
*Inc. P/Tax*

*Mallory Mercury Cell RM675 (2 required) each 2/9d.*

Considerably smaller than an ordinary box of matches, this is a multi-stage A.M. receiver meticulously designed to provide remarkable standards of selectivity, power and quality. Powerful A.G.C. is incorporated to counteract fading from distant stations; bandspread at higher frequencies makes reception of Radio 1 easy at all times. Vernier type tuning plus the directional properties of the self-contained special ferrite rod aerial makes station separation much easier than with many larger sets. The plug-in magnetic earpiece which matches exactly with the output provides wonderful standards of reproduction. Everything including the batteries is contained within the attractively designed case. Whether you build your Micromatic or buy it ready built and tested, you will find it as easy to take with you as your wristwatch, and dependable under the severest listening conditions.

**SINCLAIR GENERAL GUARANTEE**

Should you not be completely satisfied with your purchase when you receive it from us, return the goods without delay and your money will be refunded in full, including cost of return postage, at once and without question. Full service facilities are available to all Sinclair customers.

**USE THIS COUPON FOR MICROMATIC AND Q.16 ORDERS**

**To : SINCLAIR RADIONICS LIMITED, 22 NEWMARKET ROAD, CAMBRIDGE**

*Please send*

.....

.....

.....

*For which I enclose cash/cheque/money order.*

*NAME* .....

*ADDRESS* .....

.....

.....

P.E.8/70

sinclair

SINCLAIR RADIONICS LIMITED
**22 NEWMARKET ROAD, CAMBRIDGE Tel. 0223 52731**

# CRESCENT RADIO LTD.

**11 & 40 MAYES RD. N.22** 888-3206

**MAIL ORDER DEPT.** No.11 MAYES RD. N.22



## CRESCENT CASSETTES

Top quality cassettes at unbeatable prices (complete with standard storage case): C60, 7/6; C90, 12/6; C120, 17/6. Plus 1/- P. & P.

## STEREO HEADSET

8 ohm impedance, complete with plug and 5ft lead. A very comfortable phone set. Listen to stereo without noise interrupting the pleasure.

Wonderful value **59/6** Plus 4/- P. & P.



## STEREO JUNCTION BOX

For stereo amplifiers without stereo jack socket.

**22/6** Plus 1/6 P. & P.

## MICROPHONE STANDS

All have standard fittings for average Mics.

| | |
|---|---|
| Desk Stand 14in extended length | 32/6 |
| MS4. 3-Section floor stand, 4ft 8in E/L | £3.10.0 |
| MF811. 2-Section floor stand, 5ft E/L | £4.10.0 |
| BMS1. 5ft floor stand with 2ft 9in boom | £6.19.6 |
| BMS2. Super quality boom stand | £9.9.0 |

Plus 5/- P. & P.



## STANDARD GOOSE NECKS

(will fit our mic. stands)

| | |
|---|---|
| 8in | 12/9 |
| 12in | 15/9 |

Plus 1/6 P. & P.




## SOLID STATE BLOCK MODULES

Phono pre-amp E1311: input, 100K; gain, 28db; max. out, 3-volt; max. in, 50M/V; power, 9V.
Tape pre-amp E1312, as above.
Mic. pre-amp E1313, as above.
Power amplifier E1314: input, 1,000 ohms; gain, 20db, 300M/W; power, 9-volt d.c.
Electronic organ, tone osc. E1315: tone freq., 200~1kHz; output, 80M/W; power, 9V; current, 15M/A.
Dual flasher E1318: flasher time, 1/4 secs; power, 6V; current, 150M/A; lamp, 6V 150M/A.
We also stock the morse code practice modules in this range.

ALL AT **25/-** Plus 2/- P. & P.



## BATTERY ELIMINATOR

Plug your Transistor Radio, Amplifier, Cassette, etc., into the a.c. mains through this compact eliminator. 2¼in × 2in × 3in approx.

| | |
|---|---|
| 4½ volt | 29/6 |
| 6 volt | 29/6 |
| 9 volt | 29/6 |

7½ volt complete with cable and plug for Philips Cassette

**39/6** Plus 2/- P. & P. each

## TTC G1105



High quality imported headphones.
1,000Ω per phone .. .. 15/11
2,000Ω per phone .. .. 17/6
Plus 2/- P. & P. per pair



## TELETON TYPE NM.33 MAGNETIC CARTRIDGE

Stereo with diamond styli. This ever popular cartridge now at economy price: Diamond Stylus, ·7 mil; Frequency, 20-20kHz; Separation, 20db at 10kHz.

**79/6** Plus 1/6 P. & P.



## SHELF UNIT

Two teak finish shelves on a black frame (overall size: 28in × 25in × 12in). Ideal for hi fi equipment: amplifiers, speaker cabinets etc. The perfect answer for housing unit audio and equipment. This unit is wall mounting.

**50/-** Plus 8/6 P. & P.

## INTERNATIONAL TAPE

A now famous brand of tape. 7in 2,400ft, 25/-; 7in 1,800ft, 21/-; 7in 1,200ft, 13/6; 5½in, 1,200ft, 15/-; 5½in 1,800ft, 22/6; 5in 600ft 9/9; 5in 900ft, 12/6; 5in 1,200ft, 16/-. Please note the postage and packing is FREE.




**A TAPE BARGAIN**

Emitape 3in 175ft in EMI case **5/-** EACH



## WESTON MILLIAMMETER

Modern Clear Plastic Design.
1M/A full scale calibration 0–100. 2¼in × 2¼in × 1¼in.

**45/-** Plus 2/6 P. & P.

## COMPONENTS CORNER

| | |
|---|---|
| 8in × 6in one sided printed circuit board | 2/- each |
| BY100 type rectifier 800 p.i.v. 750M/A | 3/3 each |
| 4 pin transistor holders | 6d each |
| 2½in 80 ohm loudspeaker | 5/6 each |
| 2½in 25 ohm loudspeaker | 5/6 each |
| 2½in 8 ohm loudspeaker | 6/6 each |
| U2 battery holders (blue plastic) | 1/- each |
| Flick switches 1¼in dolly mains type | 3/6 each |
| Model motors 6–12 volt | 4/6 each |
| 10 ohm W/W pot loudspeaker control | 2/6 each |
| OC81 double heat clips | 6d each |
| S. G. Brown 4,000 ohm phones (used but in good condition) | 10/- per pair |
| Tape recorder rev. counters | 5/- each |

Please include P. & P.

Send 3/- for our Component Catalogue and Flog Lists



# YOURS FREE FOR 7 DAYS




## The 'New Picture-Book' way of learning

# BASIC ELECTRICITY (5 VOLS.) ELECTRONICS (6 VOLS.)

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

**The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.**

## WHAT READERS SAY

*"I have looked at each book and must confess they are very good, everything is made so simple, which makes reading a pleasure."*
R.H.H.G., Blandford.

*"I find the information contained very aptly illustrated and composed."*
D.G., Twickenham.

*"I would like you to know once again that I have read parts of each volume and think they are excellent reading material. Easy to understand, easy to read and the subjects are not flooded with reams of unnecessary calculations which most electrical books delight in."*
P.B., New Malden.

**A TECH-PRESS PUBLICATION**

**POST NOW FOR THIS OFFER!!**

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY 75/-. Cash Price or Down Payment of 20/- followed by 3 fortnightly payments of 20- each. BASIC ELECTRONICS 90/-. Cash Price or Down Payment of 20/- followed by 4 fortnightly payments of 20/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

**Tick Set required** *(Only one set allowed on free trial)*

**BASIC ELECTRICITY** ☐ **BASIC ELECTRONICS** ☐

Prices include Postage and Packing.

**Signature** .....

*(If under 18 signature required of parent or guardian)*

**NAME** .....

**BLOCK LETTERS**

**FULL POSTAL ADDRESS** .....

.....

## BELCO AF–5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR



Sine 18–200,000Hz; Square 18–50,000Hz. Output max +10dB (10kΩ). Operation internal batteries.
Attractive two-tone case 7¼in × 5in × 2in.
Price **£17.10.0** Carr. 3/6.

## CLASS D WAVEMETERS




A crystal controlled heterodyne frequency meter covering 1·7–8 Mc/s. Operation on 6V d.c. Ideal for amateur use. Available in good used condition. **£5.19.6.** Carr. 7/6, or brand new with accessories. **£7.19.6.** Carr. 7/6.

## CLASS D WAVEMETERS No. 2

Crystal controlled. 1·2–19 Mc/s. Mains or 12V d.c. operation. Complete with calibration charts. Excellent condition. **£12.10.0.** Carr. 30/–.
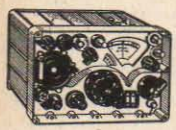
## R209 MK II COMMUNICATION RECEIVER

11 valve high grade communication receiver suitable for tropical use. 1·20 Mc/s on 4 bands. AM/CW/FM operation. Incorporates precision vernier driver, BFO. Aerial trimmer, internal speaker and 12 V d.c. internal power supply. Supplied in excellent condition, fully tested and checked.



**£15** Carr. 20/–.

## TYPE 13A DOUBLE BEAM OSCILLOSCOPES



An excellent general purpose D/B oscilloscope. T.B. 2 c/s–750 kc/s. Bandwidth 5·5 Mc/s. Sensitivity 33 mV/CM. Operating voltage 0/110/200/250 V. a.c. Supplied in excellent working condition. **£22.10.0.** Carriage 30/–.

## MARCONI CT44/TF956 AF ABSORPTION WATTMETER



1 μ/watt to 6 watts. **£20.** Carr. 20/–.


**SOLARTRON CD. 711S2 DOUBLE BEAM OSCILLOSCOPES.** D.C. to 9 Mc/s. Perfect order. **£65.** Carr. 50/–.

## TO-2 PORTABLE OSCILLOSCOPE

A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth 2 CPS–1 MHZ. Input imp. 2 megΩ 25 P.F. Illuminated scale. 2in. tube. 115 × 180 × 230mm. Weight 8lb. 220/240 V a.c. Supplied brand new with handbook. **£22.10.0.** Carr. 10/–.


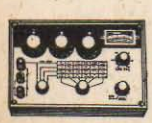
## TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE




A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω–11·1 megΩ 6 Ranges ±1%. L. 1 μH – 1 1 1 1 HENRYS 6 Ranges –2%, C. 10pF ±1110mFd. 6 Ranges ±2%. TURNS RATIO 1:1/1000–1:11100. 6 Ranges ±1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7½ × 5 × 2in. **£20.** P. & P. 5/–.

## UNR-30 4-BAND COMMUNICATION RECEIVER

Covering 550 Kc/s–30 Mc/s. Incorporates BFO. Built-in speaker and phone jack. Metal cabinet. Operation 220/240V. a.c. Supplied brand new, guaranteed with instructions. Carr. 7/6 **13 gns.**




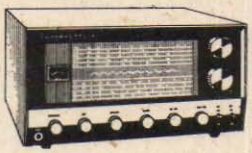**TRIO JR-310 NEW AMATEUR BAND 10-80 METRE RECEIVER.** In stock. **£77.10.0.**



## LAFAYETTE SOLID STATE HA600 RECEIVER

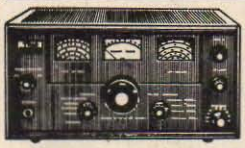**5 BAND AM/CW/SSB AMATEUR AND SHORT WAVE 150 kc/s–400 kc/s and 550 kc/s–30 Mc/s FET front end ● 2 mechanical filters ● Huge dial ● Product detector ● Variable BFO ● Noise limiter ● S meter ● 24in Bandspread ● 230V a.c./12V d.c. neg. earth operation ● RF gain control. Size 15in × 9¾in × 8¼in. Weight 18lb. EXCEPTIONAL VALUE. £45. Carr. 10/–. S.A.E. for full details.**



## TRIO COMMUNICATION RECEIVER MODEL 9R-59DE

4 band receiver covering 550Kc/s to 30Mc/s. continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. SSB-CW ● ANL ● Variable BFO ● S meter ● Sep. bandspread dial ● IF 445Kc/s ● Audio output 1·5W. ● Variable RF and AF gain controls. 115/250V A.C. Mains. Beautifully designed. Size: 7 × 15 × 10in. With instruction manual and service data. **£42** Carriage paid.
**TRIO COMMUNICATION TYPE HEADPHONES** Normally **£5.19.6.**
OUR PRICE **£3.15.0** if purchased with above receiver.

**TRIO JR-500SE 10-80 Metre AMATEUR RECEIVER £65**

**TRIO TS 510 AMATEUR TRANSCEIVER with speaker and mains P.S.U. £180**

## VARIABLE TRANSFORMERS

Input 230V a.c. 50/60Hz. Output variable 0–260V.


**BENCH MOUNTING**
1 amp, **£5.10.0**; 2½ amp, **£6.15.0**; 5 amp **£9.15.0**; 8 amp, **£14.10.0**; 10 amp, **£18.10.0**; 20 amp, **£37.0.0.**

**PANEL MOUNTING**
1 amp, **£5.10.0**; 2½ amp, **£6.12.6.**
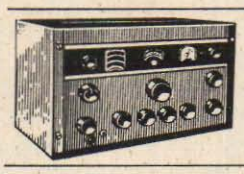
## B.C. 221 FREQUENCY METERS

latest release 125kHz to 20MHz. Excellent condition. Fully tested and checked and complete with calibrator charts. **£27.10.0.** each, Carr. 10/–.

**LAFAYETTE HA.800 6-BAND AMATEUR RECEIVER. £57.10.0.** Carr. Paid.




## RCA COMMUNICATION RECEIVER AR88D


Latest release by ministry BRAND NEW in original cases. 110–250V a.c. operation. Frequency in 6 Bands. 535Kc/s–32Mc/s continuous. Output impedance 2·5–600 ohms. Incorporating crystal filter, noise limiter, variable BFO, variable selectivity, etc. Price **£65.** Carr. £2.
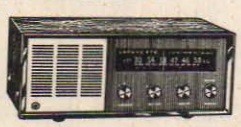
## LAFAYETTE PF-60 SOLID STATE VHF FM RECEIVER

A completely new transistorised receiver covering 152–174 Mc/s. Fully tuneable or crystal controlled (not supplied) for fixed frequency operation. Incorporates 4 INTEGRATED CIRCUITS. Built in speaker and illuminated dial. Squelch and volume controls. Tape recorder output. 75Ω aerial input. Headphone jack. Operation 230V. A.C./12V. D.C. Neg. earth. **£37.10.0.** Carr. 10/–.


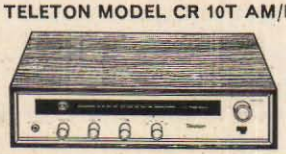
## TELETON MODEL CR 10T AM/FM STEREO TUNER AMPLIFIER



A new model from Teleton. 31 solid state devices. 4 + 4 watt output. Inputs for ceramic/crystal cartridge. Frequency range AM 540-1600 KHz FM 88-108 MHz. Automatic FM stereo reception. Stereo indicator. Controls: Tuning, function selector, Tone and R & L volume controls. AFC switch. Stereo headphone socket. Size: 13¾" × 3½" × 9½" approx. Price **£34.** Carr. 7/6.

## CLEAR PLASTIC PANEL METERS



First grade quality Moving Coil panel meters. Type MR 38P. $1^{21}/_{32}$in square fronts.

| | | | | | |
|---|---|---|---|---|---|
| 500–0–500μA | 27/6 | 50mA | 27/6 | 150V. D.C. | 27/6 |
| 1mA | 27/6 | 100mA | 27/6 | 300V. D.C. | 27/6 |
| 1–0–1mA | 27/6 | 150mA | 27/6 | 500V. D.C. | 27/6 |
| 2mA | 27/6 | 200mA | 27/6 | 750V. D.C. | 27/6 |
| 5mA | 27/6 | 300mA | 27/6 | 15V. A.C. | 27/6 |
| 10mA | 27/6 | 500mA | 27/6 | 50V. A.C | 27/6 |
| 50μA | 40/– | 750mA | 27/6 | 3V. D.C. | 27/6 |
| 50–0–50μA | 37/6 | 1 amp | 27/6 | 10V. D.C. | 27/6 |
| 100μA | 37/6 | 2 amp | 27/6 | 15V. D.C. | 27/6 |
| 100–0–100μA | 35/– | 5 amp | 27/6 | 20V. D.C. | 27/6 |
| 200μA | 35/– | 20mA | 27/6 | 100V. D.C. | 27/6 |
| 500μA | 40/– | Full range of other sizes in stock. | | | |

150V. A.C. 27/6
300V. A.C. 27/6
500V. A.C. 27/6
S meter 1mA. 32/–
VU meter 42/–
Send s.a.e. for leaflet.

## POWER RHEOSTATS



High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock Single hole fixing, ¼in. dia. shafts. Bulk quantities available.
**25 WATT.** 10/25/50/100/250/500/1,000/1,500/2,500 or 5,000 ohms, **14/6.** P. & P. 1/6.
**50 WATT.** 10/25/50/100/250/500/1,000/2,500 or 5,000 ohms, **21/–.** P. & P. 1/6.
**100 WATT.** 1/5/10/25/50/100/250/500/1,000 or 2,500 ohms, **27/6.** P & P. 1/6.

## CRYSTAL CALIBRATORS No. 10



Small portable crystal controlled wavemeter. Size 7" × 7½" × 4". Frequency range 500 Kc/s. 10 Mc/s (up to 30 Mc/s on harmonics). Calibrated dial. Power requirements 300 V.D.C. 15mA and 12 V.D.C. 0.3A. Excellent condition. **89/6.** Carr. 7/6.

## T.E.40 HIGH SENSITIVITY A.C. VOLTMETER



10 meg. input 10 ranges: ·01 / ·003 / ·1 / ·3 / 1 / 3 / 10 / 30 / 100 / 300V. R.M.S. 4c/s.-1·2Mc/s. Decibels −40 to +50dB. Supplied brand new complete with leads and instructions. Operation 230V a.c. **£17.10.0.** Carr. 5/–.

## LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS

Frequency 0·20 Kc/s on 2 ranges. Output 500Ω or 5kΩ. Operation 200/250V. A.C. Supplied in perfect order. **£12.10.0.** Carr. 10/–.

## TE-65 VALVE VOLTMETER



High quality instrument with 28 ranges. D.c. volts 1·5–1,500V. A.c. volts 1·5–1,500V. Resistance up to 1,000 megohms. 220/240V a.c. operation Complete with probe and instructions. **£17.10.0.** P. & P. 6/–. Additional Probes available: R.F. **42/6.** H.V. **50/–.**

## COSSOR 1049 DOUBLE BEAM OSCILLOSCOPES

D.c. coupled. Band width 1kc/s. Perfect order. **£25.** Carr. 30/–.

## AM/FM SIGNAL GENERATORS



Oscillator Test No. 2. A high quality precision instrument made for the ministry by Airmec. Frequency coverage 20–80Mc/s. AM C.W./FM. Incorporates precision dial, level meter, precision attenuator 1μV-100mV. Operation from 12V d.c. or 0/110/200/250V a.c. Size 12 × 8½ × 9in. Supplied in brand new condition complete with all connectors fully tested. **£45.** Carr. 20/–.

## RUSSIAN C1-16 DOUBLE BEAM OSCILLOSCOPES

5MHz Pass Band. Separate Y1, Y2 amplifiers. Calibrated triggered sweep from 0·2μsec to 100msec/cm.
Supplied complete with all accessories and instructions, **£87.** Carr. paid.

**EDDYSTONE VHF RECEIVERS MODEL 770R.** 19–165 Mc/s. Excellent condition. **£150**



**TE-16A Transistorised Signal Generator.** 5 ranges 400 kHz–30 mHz. An inexpensive instrument for the handyman. Operates on 9v battery. Wide, easy to read scale. 800 kHz modulation. 5½ × 5½ × 3½. Complete with instructions and leads. **£7.19.6.** P.&P. 4/–.

## HOSIDEN DH-02S STEREO HEADPHONES

Wonderful value and excellent performance combined. Adjustable headband. 8 ohm impedance. 20–12,000 cps. Complete with lead and stereo jack plug.



ONLY 47/6. P.&P. 2/6.

## AUTO TRANSFORMERS

0/115/230v. Step up or step down. Fully shrouded.

| | |
|---|---|
| 150 W. | **£2.2.6.** P. & P. 3/6 |
| 300 W. | **£3.5.0.** P. & P. 4/6 |
| 500 W. | **£4.10.0.** P. & P. 6/6 |
| 1,000 W. | **£6.10.0.** P. & P. 7/6 |
| 1,500 W. | **£7.19.6.** P. & P. 8/6 |
| 7,500 W. | **£15.10.0.** P. & P. 20/– |

G. W. SMITH & CO (RADIO) LTD.

Also see oppos. page

## ARF-100 COMBINED AF-RF SIGNAL GENERATOR



**A.F. SINE WAVE** 20–200,000 c/s. Square wave 20–30,000 c/s. O/P. **HIGH IMP.** 21V. P/P 600Ω 3·8 V. P/P. TF 100 kc/s–300 Mc/s. Variable R.F. attenuation int/ext. modulation. Incorporates dual purpose meter to monitor AF output and % mod. on R.F 220/240 V a.c. **£32.10.0.** Carr. 7/6.

## TE-20D RF SIGNAL GENERATOR



Accurate wide range signal generator covering 120kc/s to 500Mc/s on 6 bands. Directly calibrated. Variable RF attenuator, audio output. Xtal socket for calibration. 220/240V a.c. Size 140 × 215 × 170mm. Brand new with instructions. **£15.** Carr. 7/6.

## TY75 AUDIO SIGNAL GENERATOR



Sine Wave 20c/s to 200kc/s. Square Wave 20c/s to 30kc/s. High and low impedance output. Output variable up to 6 volts. 220/240 volts a.c. Size 210 × 150 × 120mm. Brand new with instructions. **£16.** Carr. 7/6.

**MARCONI TF142E DISTORTION FACTOR METERS.** Excellent condition. Fully tested. **£20.** Carr. 15/-.

## LAFAYETTE TE46 RESISTANCE CAPACITY ANALYSER



2pF-2,000 mfd 2 ohms–200 megohms. Also checks impedance, turns ratio, insulation, 200/250V a.c. **Brand New £17.10.0.** Carr. 7/6.

## ADVANCE TEST EQUIPMENT

**Brand new and boxed in original sealed cartons.**

**J1B. AUDIO SIGNAL GENERATOR.** 15 c/s to 50 Kc/s. Sine wave. Output 600 ohms or 5 ohms. **£30.0.0.**

**VM79. UHF MILLIVOLT METER.** 100 Kc/s to 1,000 Mc/s. a.c. 10 mV to 3V. D.c. 10 mV to 3V. Current 0·01 μA to 0·3 mA. Resistance 1 ohm to 10 megohm. **£125.0.0.**

**TT1S. TRANSISTOR TESTER.** Full range of facilities for testing PNP or NPN transistors in or out of circuit. **£37.10.0.** Carriage 10/- per item.

## TO-3 PORTABLE OSCILLOSCOPE



3in. tube. Y amp. Sensitivity 0·1v p-p/CM. Bandwidth 1·5 cps–1·5 MHz. Input imp. 2 meg Ω 25pF X amp. sensitivity 0·9v. p-p/CM. Bandwidth 1·5 cps –800 KHz. Input imp. 2 meg Ω 20pF. Time base. 5 ranges 10 cps–300 KHz. Synchronization. Internal/external. Illuminated scale 140 × 215 × 330 mm. Weight 15½ lb. 220/240V. A.C. Supplied brand new with handbook. **£37.10.0.** Carr. 10/-

**TE111. DECADE RESISTANCE ATTENUATOR**



Variable range 0–111dB. Connections. Unbalanced T and Bridge T. Impedance 600Ω range (0-1dB × 10) + (1dB × 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200kHz (—3dB). Accuracy: 0·05dB. +indication dB × 0·01. Maximum input less than 4W (50V). Built in 600Ω load resistance with internal/external switch. Brand new **£27.10.0.** P. & P. 5/-.

## BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR



New high quality portable instrument. Sine 1Hz to 100kHz. Square 20Hz to 20kHz. Output max. +10dB (10kΩ). Operation 220/240V a.c. Size 215mm × 150mm × 120mm. Price **£27.10.0.** Carr. 5/-.

# Latest Catalogue

The latest edition giving full details of a comprehensive range of HI FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. . . . Over 230 pages, fully illustrated and detailing thousands of items—many at bargain prices. FREE DISCOUNT COUPONS VALUE 10/-



***SEND NOW—ONLY 7/6*** *P&P 1/6*

# GARRARD

**FULL CURRENT RANGE OFFERED, BRAND NEW AT FANTASTIC SAVINGS**

| | | | |
|---|---|---|---|
| 1025 stereo | £7.19.6 | SL72B | £25. 0.0 |
| 2025T/C stereo | £8.17.6 | AP75 | £16.19.6 |
| 40 MKII stereo | £8.8.0 | SL75 | £25.19.6 |
| 3000 stereo | £9.19.6 | SL75B | £28. 0.0 |
| SP25 MKII | £11. 9.6 | SL95B | £35. 0.0 |
| SL55 | £11.12.6 | A70/11 | £11.19.6 |
| SL65B | £14.19.6 | 401 | £25. 0.0 |

Carriage 7/6 extra each item.



TEAK PLINTHS AND PERSPEX COVERS
1. For SP25, SL65, SL55, 3000, 2025T/C, 2025, 1000. **£4.10.0**
2. For AP75, SL75, SL95. **£5.19.6**
3. For SP25 etc. to operate with lid in place **£5.19.6**

Carriage 7/6 extra each type. Full range of Garrard accessories available.

## SPECIAL OFFERS!

Garrard SP25 fitted Goldring G800 cartridge and wooden plinth. Total list price £32.8.5.

OUR PRICE **£19.15.0.** Carr. 10/-.

GOLDRING GL69 fitted Goldring G800 cartridge complete with deluxe base and cover. Total list price £50.16.0.

OUR PRICE **£39.** Carr. 20/-.

## RTC 249 4 TRACK TAPE DECK



British made. Speed 1⅞", 3¾", 7½" P.S. Marriott Heads. 7" reel size. Push button controls, fully interlocking. Size 13" × 10" × 1¾" above unit plate, 4½" below. Full instructions. **£13.19.6.** Carr. 7/6.

# MULTIMETERS *for EVERY purpose!*




**TE-51. NEW 20,000Ω/VOLT MULTIMETER** with overload protection and mirror scale. 0/6/60/120/1,200V a.c. 0/3/30/60/300/600/3,000V d.c. 0-50μA/12/300mA d.c. 0/60K/6 meg. ohm. **92/6.** P. & P. 2/6.



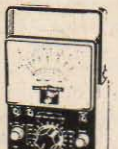**TE-900 20,000Ω VOLT GIANT MULTIMETER**

6in. full view meter. 2 colour scale, overload protection. 0/2·5/10/250/1,000/5,000V a.c. 0/25/12·5/10/50/250/1,000/5,000V d.c. 0/50μA/110/100/500mA 10A d.c. 20K/200K/20MΩ. **£15.** P. & P. 5/-.



**MODEL AS-100D. 100KΩ/VOLT.** 5in., mirror scale. Built-in meter protection. 0/3/12/60/120/300/600/1,200V d.c. 0/6/30/120/300/600V a.c. 0/10μA/6/60/300MA/12 Amp. 0/2K/200K/2M/200MΩ. —20 to +17dB. **£12.10.0.** P. & P. 3/6



**MODEL TE300 30,000 O.P.V.** Mirror scale, overload protection. 0/0·6/3/15/60/300/1,200V d.c. 0/6/30/120/600/1,200V a.c. 0/30μA/6mA/60mA/300mA/600mA. 0/8K/80K/800K/8 meg. —20 to +63dB. **£5.19.6.** P. & P. 3/-.



**MODEL TE-90 50,000 O.P.V. MIRROR SCALE OVERLOAD PROTECTION** 0/3/12/60/300/600/1,200V d.c. 0/6/30/120/300/1,200V d.c. 0·03/6/60/600MA d.c. 16kΩ/160kΩ/1·6/16MΩ. —20 to +63dB. **£7.10.0.** P. & P. 3/-.



**MODEL TE12. 20,000 O.P.V.** 0/0·6/30/120/600/1,200/3,000/6,000V d.c. 1/6/30/120/600/1,200V a.c. 0/60μA/6/60/600MA. 0/6K/600K/6meg./60. Megohm 50PF. 2 MFD **£5.19.6.** P. & P. 3/6.



**MODEL TE-70. 30,000 O.P.V.** 0/3/15/60/300/600/1,200V. d.c. 0/6/30/120/600/1,200V. a.c. 0/30μA/3/30/300mA. 0/16K/160K/1·6M/16megohm **£5.10.0.** P. & P. 3/-.



**LAFAYETTE** 57 Range Super 50,000 O.P.V. Multimeter. D.c. Volts 125V-1,000V A.c. Volts 1·5V-1,000V D.c. Current 25μA-10 Amp. Ohms. 0-15 Meg Ω dB.—20 to +81dB. Overload Protection. **£12.10.0.** Carr. 3/6.



**MODEL PT-34.** 1,000 O.P.V. 0/10/50/250/500/1,000V a.c. and d.c. 0/1/100/500mA d.c. 0/100KΩ **39/6.** P. & P. 1/6.

**SAVE UP TO 33⅓% ON HI-FI EQUIPMENT**
**Send for discount price list**

## AVO CT471A MULTIMETER

**Battery operated, fully transistorised. Sensitivity 100mΩ/v. Measures AC/DC Voltages 12mV to 1,200v. AC/DC Current 12uA to 1.2 Amp. Resistance 12 ohm to 120 mΩ HF, VHF, UHF, Voltage with multiplier 4v to 400v up to 50 Mc/s, 40mV to 4V up to 1,000 Mc/s.**
**Offered in perfect condition. £55 each. Carr. 10/-.**

## TRANSISTORISED TWO-WAY TELEPHONE INTERCOM



Operative over amazingly long distances. Separate call and press to talk buttons. 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets.
**£6.19.6.** P. & P. 3/6.

## SINCLAIR EQUIPMENT

Project 60. Package offers. 2 × Z30 amplifier, stereo 60 pre-amp, PZ5 power supply, **£19.0.0.** Carr. 7/6. Or with PZ6 power supply, **£21.** Carr. 7/6. 2 × Z50 amplifier, stereo 60 pre-amp, PZ8 power supply, **£21.10.0.** Carr. 7/6. Transformer 4 PZ8, **59/6** extra. Add to any of the above **£4.17.6.** for active filter unit and **£16** for a pair of J16 speakers.



All other Sinclair products in stock. 2,000 amplifier, **£23,** Carr. 7/6. Neoteric amplifier, **£46,** Carr. 7/6.

## PEAK SOUND PRODUCTS

Full range of Amplifiers, Kits, Speakers in stock.

## SOLID STATE VARIABLE A.C. VOLTAGE REGULATORS



Compact and panel mounting. Ideal for control of lamps, drills, electrical appliances, etc. Input 230/240V a.c. Output continuously variable from 20V to 230V.
Model MR2305 5A 68 × 46 × 43mm. **£8.7.6.** Model MR2310 10A 90 × 68 × 60mm. **£11.19.6** Postage 2/6.

## HOSIDEN DH04S 2-WAY STEREO HEADSETS



Each headphone contains a 2½in woofer and a 2in tweeter. Built in individual level controls. 8Ω imp. 25-18,000c/s. with cable and stereo plug.
**£5.19.6.** P. & P. 2/6.

## RECORDING HEADS

**COSMOCORD** ¼-track heads. High imp. record/playback **65/-.** Low imp. erase **20/-. MARRIOTT** ¼-track heads. High imp. record/playback **65/-.** Low imp. erase **20/-.** Post extra.

**RACAL MA.168 TRANSISTORISED DIVERSITY SWITCH.** Brand New Condition **£15.** Carr. 10/-.

## AMERICAN TAPE

| First grade quality American tapes. Brand new Discount on quantities. | |
|---|---|
| 3in. 225ft. L.P. acetate | 3/6 |
| 3½in. 600ft. T.P. mylar | 10/- |
| 5in. 600ft. std. plastic | 8/6 |
| 5in. 900ft. L.P. acetate | 10/- |
| 5in. 1,200ft. D.P. mylar | 15/- |
| 5½in. 1,200ft. L.P. acetate | 12/6 |
| 5½in. 1,200ft. L.P. mylar | 16/- |
| 5½in. 1,800ft. D.P. mylar | 22/6 |
| 5½in. 2,400ft. L.P. mylar | 39/6 |
| 7in. 1,200ft. std. acetate | 12/6 |
| 7in. 1,800ft. L.P. acetate | 15/- |
| 7in. 1,800ft. L.P. mylar | 20/- |
| 7in. 2,400ft. D.P. mylar | 25/- |
| 7in. 3,600ft. T.P. mylar | 45/- |

Postage 2/-. Over £3 post paid.

## TAPE CASSETTES

Top quality in plastic library boxes.
C60 60 min 8/6 3 for 24/6
C90 90 min 12/6 3 for 36/-
C120 120 min 15/- 3 for 43/6
Cassette Head Cleaner **11/3.** All Post Extra.

# G.W.SMITH & CO. (RADIO) LTD

All Mail Orders to—
147, Church Street, London, W.2
Tel: 01-262 6562
(Trade supplied)

3, LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204
34, LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155
311, EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387
OPEN 9-6 MONDAY TO SATURDAY (EDGWARE ROAD ½ DAY THURSDAY)

# R+TV RADIO & TV COMPONENTS (Acton) Ltd.

**21d High Street, Acton, London, W.3**
**Also at 323 Edgware Road, London, W.2**
**ALL ORDERS BY POST TO OUR ACTON BRANCH**
Terms C.W.O. All enquiries S.A.E.

# Complete Stereo System £41

WITH VISCOUNT F.E.T. FIELD EFFECT TRANSISTORS AMPLIFIER




This superb stereo system is a real price breakthrough. It comprises the VISCOUNT F.E.T. Mk. I amplifier on which full details are given below, the famous Garrard SP25 Mk. II (including teak veneer base and transparent cover) with diamond cartridge or 2025 TC and the very successful DUO type 2 speakers.

Measuring 17½in × 10¾in × 6¼in, the Duo type 2 speakers are beautifully finished in teak veneer with matching vynair grills. They incorporate a 10½in × 6½in drive unit and high frequency speaker, both of which are of 3 ohms. impedance. The Duo speaker system is also available separately at

**£6.6.0** each plus 15/- P. & P.

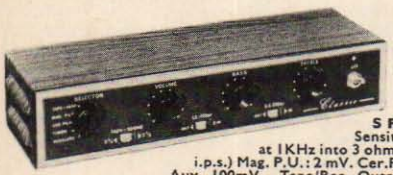Complete stereo system **£41** plus £2.10.0 P. & P.



## *The Classic*

Teak finished case

**£9.10**

Plus P. & P. 7/6

**SPECIFICATION:** Sensitivities for 10 watt output at 1KHz into 3 ohms. Tape Head: 3mV (at 3¾ i.p.s.) Mag. P.U.: 2 mV. Cer.P.U.: 80mV. Tuner: 100mV. Aux. 100mV. Tape/Rec. Output. Equalisation for each input is correct to within +2dB (R.I.A.A.) from 20Hz to 20KHz. *Tone Control Range: Bass:* 13dB at 60Hz. *Treble:* ±14dB at 15KHz. *Total Distortion:* (for 10 watt output) < 1·5%. Signal Noise: < −60dB. A.C. Mains 200–250V. Size 12¼in long, 4¼in deep, 2¾in high. **Built and tested.**



## THE RELIANT Mk. II

**SOLID STATE GENERAL PURPOSE AMPLIFIER**

**£7.5.0** Plus P. & P. 7/6

**In teak finished case**

**SPECIFICATION:** *Output:* 10 watts into a 3 ohms speaker. *Inputs:* (1) for mike (10mV). Input (2) for gram. radio (250mV) individual bass and treble control. *Transistors:* 4 silicon and three germanium. *Mains input:* 220/250 volts. *Size:* 10¼ × 4¾ × 2½in. Mk. I **£6.10.0** plus 7/6 P. & P. Less teak finished case.



## ELEGANT SEVEN Mk. III (350mW Output)


**7-transistor fully tunable M.W.-L.W. Superhet portable.** Set of parts. Complete with all components, including ready etched and drilled printed circuit board —back printed for foolproof construction. **MAINS POWER PACK KIT: 9/6 extra.**

**£5.5.0** Plus P. & P. 7/6. Circuit 2/6. Free with parts.

## THE DORSET (600mW Output)

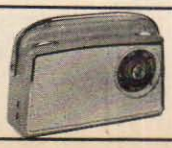**7-transistor fully tunable M.W.-L.W. Superhet portable** with baby alarm facility. Set of parts. The latest modulated and pre-alignment techniques makes this simple to build. Sizes: 12 × 8 × 3in. **MAINS POWER PACK KIT: 9/6 extra.**

**£5.5.0** Plus P. & P. 7/6. Circuit 2/6. Free with parts.



## *The Viscount* F.E.T. Mk. I £14.5.0 Plus 7/6 P. & P.

High fidelity transistor stereo amplifier employing field effect transistors. With this feature and accompanying guaranteed specifications below, the Viscount F.E.T. vastly surpasses amplifiers costing far more.

**SPECIFICATION**

Output per channel—10W rms.
Frequency bandwidth 20Hz to 20kHz ±1dB @ 1W.
Total distortion @ 1kHz @ 9W 0·5%.
Input sensitivities—CER. P.U. 100mV into 3 MΩ; Tuner 100mV into 100KΩ; Tape 100mV into 100kΩ.
Overload Factor—Better than 26dB.
Signal to noise ratio—70dB on all inputs (with vol. max).
Controls—6 position selector switch (3 pos. stereo and 3 pos. mono), separate vol. controls for left and right channels. Bass ±14dB @ 60Hz; Treble (with D.P.S. on/off) ±12dB @ 10kHz.
Tape recording output sockets on each channel.
Size 12½in × 6in × 2¾in in teak-finished case. Built and tested.

## Mk. II (MAG. P.U.) £15.15.0

Post & packing 10/- extra.

Specification same as Mk. I, but with the following inputs: Mag. P.U. CER. P.U. Tuner. Spec. on Mag. P.U. 3mV @ 1kHz input impedance 47kΩ. Fully equalised to within ±1dB RIAA. Signal to noise ratio—65dB (vol. max.).

## 50 WATT AMPLIFIER A.C. Mains 200-250V



**Price £28.10.0**

Plus 20/- P. & P.

An extremely reliable general purpose valve amplifier. Its rugged construction yet space age styling and design makes it by far the best value for money. **TECHNICAL SPECIFICATIONS** 3 electronically mixed channels, with 2 inputs per channel, enables the use of 6 separate instruments at the same time. The volume controls for each channel are located directly above the corresponding input sockets. **Sensitivities and Input Impedances.** Channels 1 and 2 4mV at 470K. These 2 channels (4 inputs) are suitable for microphone or guitars. Channels 3 and 4 300mV at 1m. Suitable for most high output instruments (gram, tuner, organ, etc.). Input sensitivity relative to 10W output. Tone Controls are common to all inputs. **Bass Boost** +12dB at 60 Hz/s. **Bass Cut** −13dB at 60 Hz/s. **Treble Boost** +11dB at 15 KHz/s. **Treble Cut** −12dB at 15KHz/s. With bass and treble controls central −3dB points are 30Hz/s and 20 KHz/s. **Power output.** For speech and music 50 watts rms. 100 watts peak. For sustained music 45 watts rms. 90 watts peak. For sinc wave 38·5 watts rms. Nearly 80 watts peak. Total distortion at rated output 3·2% at 1KHz/s. Total distortion at 20 watts 0·15% at 1KHz/s. **Negative feed back** 20dB at 1KHz/s. **Signal to noise ratio** 60dB. **Mains voltages.** Adjustable from 200–250V. A.C. 50–60Hz/s. A protective fuse is located at the rear of unit. Output impedance 3, 8 and 15 ohms.

# LIQUIDATED STOCK

# DANSETTE

## TOURISTE MK3 CAR RADIO




Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensures excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1 MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts. Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7″ × 2″ × 4½″ deep.

**Originally sold complete for £15.4.6**

**SET OF PARTS £6.6.0 plus 7/6 P. & P.**

**Circuit diagram 2/6, free with parts**

**Speaker, baffle and fixing kit 25/- extra plus 4/- P. & P.**

**Postage free when ordered with parts**

## RADIO & TV COMPONENTS (ACTON) LTD.

*Post orders to:*—**21d High Street, Acton, London, W.3**

**Also at 323 Edgware Road, London, W.2**

**Goods not despatched outside U.K.** **Terms C.W.O.** **All Enquiries S.A.E.**

RADIO & TV COMPONENTS · R+TV · (ACTON) LIMITED

# DIOTRAN SALES

P.O. BOX 5
WARE, HERTS
TEL.: WARE 3442

### SIL. G.P. DIODES

| | | |
|---|---|---|
| 300mW | 30 | 10/- |
| 40PIV (Min.) | 100 | 30/- |
| Sub-Min. | 500 | £5 |
| Fully Tested | 1,000 | £9 |

Ideal for Organ Builders.

Post and Packing costs are continually rising. Please add 1/- towards same. **CASH WITH ORDER PLEASE. GIRO No. 30-102**

**OVERSEAS QUOTATIONS BY RETURN SHIPMENTS TO ANYWHERE IN THE WORLD**

### OVER 2 MILLION SILICON ALLOY & GERM. TRANSISTORS AVAILABLE FOR IMMEDIATE DELIVERY

| TRANSISTORS Type and Construction | | Qty. Price 100 | Qty. Price 500 | Qty. Price 1,000 | Qty. Price 10,000 |
|---|---|---|---|---|---|
| A 1 Germ. A.F. NPN T0-1 | =AC127, NKT773, AC157, ASY86 | £3.10 | £15 | £25 | £200 |
| A 2 Germ. A.F. PNP T0-5 | =ACY17-21, NKT237-245 | £1 | £3 | £5 | £40 |
| A 3 Germ. A.F. PNP T0-1 | =AC128, NKT271, 2G381 | £1 | £3 | £5 | £40 |
| A 4 Germ. R.F. PNP T0-1 | =OC44-45, NKT72/125, ASY54 | £1.10 | £4.10 | £7.10 | £60 |
| A 5 Germ. R.F. PNP T0-5 | =2N1303, NKT164-7, 2G301-3 | £1.10 | £4.10 | £7.10 | £60 |
| A 6 Germ. V.H.F. PNP T0-1 | =AF116-7, KNT667, 2G417 | £3.10 | £15 | £25 | £200 |
| A 7 Assorted Germ. A.F.-R.F. PNP mixed cans, general purpose | | 15s. | £2.10 | £4 | £32 |
| A 8 Germ. A.F. S0-2 PNP | =2G371-89, ACY27-31, OC71-75 | £2 | £7.10 | £12.10 | £100 |
| A 9 Sil. Alloy PNP T0-5 | =2S301-5, BCY17-29, BCY30-34 | £2 | £7.10 | £12.10 | £100 |
| A10 Sil. Alloy PNP S0-2 | =2S321-325, OC200-205 | £2 | £7.10 | £12.10 | £100 |

A1 to A7 Guaranteed 80% Good usable Transistors ideal for low cost production work and experimental use. A8 to A10 are all perfect devices, factory tested, no open or short circuit Transistors in these lots.

### 1/6 each TESTED TRANSISTORS 1/6 each

**ONE PRICE ONLY PNP. NPN. SILICON PLANAR 1/6 EACH**

| | | | | |
|---|---|---|---|---|
| BC108 | 2N696 | 2N1132 | 2N2220 | 2S733 |
| BC109 | 2N697 | 2N1613 | 2N3707 | 2N3391 |
| BFY50 | 2N706 | 2N1711 | 2N3711 | TIS44 |
| BFY51 | 2N708 | 2N2904 | 2S102 | 2N2906 |
| BFX84 | 2N929 | 2N2905 | 2S103 | 2N2907 |
| BFX86 | 2N930 | 2N2924 | 2S104 | 2N2696 |
| BFX88 | 2N1131 | 2N2926 | 2S732 | 2N3702 |
| | | | | 2N3703 |

From Manufacturers' Over-runs—Unmarked Plastic and Metal cases. Devices similar to above Nos.

**BRAND NEW FULLY TESTED EPOXY CASE UNIJUNCTION TRANSISTORS.** Type TIS43 and BEN 3000 and replacement for 2N2646. Full data available. LOWEST PRICE AVAILABLE ANYWHERE. 100 off 4/- each = £20; 500 off 3/6 each = £87.10; 1,000 off 3/- each = £150. Sample devices 7/- each on request.

**HIGH QUALITY SILICON PLANAR DIODES.** SUB-MINIATURE DO-7 Glass Type, suitable replacements for OA200, OA202, BAY38, IS130, IS940. 200,000 to clear at £4 per 1,000 pieces. GUARANTEED 80% GOOD.

**SILICON PLANAR PLASTIC TRANSISTORS.** 2N3708A VcB30 Hfe 20-60. All marked, fully tested and guaranteed. 1 off 1/6 each; 100 off 10d. each; 500 off 9d. each; 1,000 off 7½d. each.

**OA90 GERM. DIODES 30PW 45MA DO-7 GLASS.** 30,000 Available New and Coded. Price £3 per 100. £11 per 500. £17 per 1,000 pieces. Once sold cannot be repeated.

**FULLY TESTED DEVICES AND QUALITY GUARANTEED—SURPLUS TO REQUIREMENTS**

**OA202** Silicon Diode. Fully Coded. 150 PIV 250mA Qty. Price £30 per 1,000 pieces.

**02A00** Silicon Diode. Fully Coded. 50PIV 250mA. Qty. Price £25 per 1,000.

**BY100** SIL. RECT'S 800 PIV 550mA. 1-49 2/6 each; 50-99 2/3 each; 100-999 2/- each; 1,000 up 1/10 each. Fully Coded. 1st Qlty.

**PLASTIC PNP SILICON TRANSISTORS.** Manufacturers' seconds from 2N3702-3 family. Ideal cheap trans. for manufacturing, etc. £8.0.0.—500, £13.10.0—1,000 pieces.

**PLASTIC NPN SILICON TRANSISTORS.** Manufacturers' seconds from 2N3707-3711 family. Ideal cheap trans. for manufacturing, etc. £7.10.0—500, £12.0.0—1,000 pieces.

**TO-18 METAL CAN PNP SILICON PLANAR TRANS.** High quality, 99% good. Type similiar to 2N2906-7, BC186-7, BCY70-1-2, £9 per 500. £15 per 1,000 pieces.

**TOP HAT RECTIFIERS.** All good. No short or open circuit devices. Voltage range 25-400PIV, 750mA. £3 per 100, £12.10.0 per 500.

**S.C.R.'s 16AMP (unplated)**

| | 1-24 | 25-99 | 100 up |
|---|---|---|---|
| 100PIV, 9/6 | 7/6 | 6/- |
| 400PIV, 14/- | 12/- | 10/- |

All tested perfect functional devices guaranteed.

### GERM. PNP AND NPN TRANSISTORS FULLY TESTED, UNMARKED SIMILAR TO 1/6 EACH

| | | | | | |
|---|---|---|---|---|---|
| AC125 | ACY22 | ACY36 | NKT677 | OC81 | 2G381 |
| AC126 | ACY27 | NKT141 | NKT713 | OC82 | 2G382 |
| AC127 | ACY28 | NKT142 | NKT773 | 2G301 | 2G399A |
| AC128 | ACY29 | NKT212 | OC44 | 2G302 | |
| AC130 | ACY30 | NKT213 | OC45 | 2G303 | |
| ACY19 | ACY31 | NKT214 | OC71 | 2G308 | 1/6 |
| ACY20 | ACY34 | NKT215 | OC72 | 2G371 | each |
| ACY21 | ACY35 | NKT271 | OC75 | 2G374 | |

### POWER TRANSISTORS

| | | | | |
|---|---|---|---|---|
| OC25 | OC35 | NKT403 | ASZ17 | 5/- each |
| OC26 | AD130 | NKT404 | T13027 | |
| OC28 | AD140 | NKT405 | T13028 | |
| OC29 | AD149 | NKT452 | T13029 | |

Manufacturers' Surplus Germ. A.F. All similar to above.

### TRANSISTOR EQVT. BOOK

2,500 cross references of transistors—British, European, American and Japanese. A must for every transistor user. Distributed by DIOTRAN SALES. 15/- EACH.

**TEXAS 2G371 A/B Eqvt. OC71 Germ. Gen. Purpose Trans.**

| | Each |
|---|---|
| 1-99 | 1/6 |
| 100-499 | 1/3 |
| 500-999 | 1/- |
| 1000 up | 9d. |

All Brand New and Coded.

**Vast mixed lot of subminiature glass diodes. Comprising of Silicon, Germ., Point Contact and Gold Bonded types plus some Zeners.** 500,000 available at Lowest of Low Price. 1,000 pieces £3.0.0. 5,000 pieces £13.10.0. 10,000 pieces £23.

# Build working radio receivers and electronic circuits in an evening




## Beginner or advanced student— you learn fast with Radionic kits

Circuits work first time with the Radionic 'no soldering' method. With the X30 kit, build 33 experiments : a printed circuit transistor radio, burglar alarm, morse code buzzer etc.

The more advanced kits are suitable for G.C.E., City and Guilds, National Certificate and higher. Every set includes construction notes and all circuit diagrams.

It's so easy for you to build *and* learn because you construct circuits that resemble the theoretical diagram. Re-use components easily, too—they're screw-in-mounted.

*Send off this coupon today.*

**TO: RADIONIC PRODUCTS LTD.,** P.E.1
**St. Lawrence House, Broad Street, Bristol BS1 2HF**

Please send me full details of all Radionic Kits/please send me one Radionic Kit X30, for which I enclose £7 19s. 6d.
*(delete where inapplicable)*

Name_____

Address_____

_____

RADIONIC
RADIO & ELECTRONICS CONSTRUCTIONAL KITS

# Kinver for Components

**SILICON TRANSISTORS FOR HIGH QUALITY EQUIPMENT**

| | | | | | | | |
|---|---|---|---|---|---|---|---|
| BC107 | 3/3 | BD123 | 24/3 | TIP32A | 23/– | 2N3055 | 15/9 |
| BC108 | 3/– | BDY20 | 24/3 | TIS44 | 1/9 | 2N3702 | 3/3 |
| BC109 | 3/3 | BF184 | 7/6 | TIS49 | 2/6 | 2N3703 | 3/3 |
| BC158 | 7/6 | BF194 | 7/– | TIS50 | 3/9 | 2N3704 | 3/9 |
| BC182L | 3/– | BFX29 | 9/6 | 2N696 | 4/6 | 2N3705 | 3/4 |
| BC183L | 2/5 | BFX84 | 6/8 | 2N697 | 5/– | 2N3707 | 3/9 |
| BC184L | 3/– | BFX85 | 8/8 | 2N706 | 3/– | 2N3708 | 2/5 |
| BC212L | 3/9 | BFY50 | 4/6 | 2N1132 | 10/9 | 2N3819 | 7/9 |
| BC213L | 3/9 | BFY51 | 4/2 | 2N2906 | 13/– | 2N3820 | 15/9 |
| BC214L | 4/– | BFY52 | 5/– | 2N2924 | 4/4 | 2N3826 | 5/11 |
| BCY70 | 4/9 | BSY95A | 3/9 | 2N2925 | 5/3 | 2N4058 | 4/6 |
| BCY71 | 8/6 | MJ481 | 27/– | 2N2926 | 2/6 | 2N4059 | 3/5 |
| BCY72 | 4/– | MJ491 | 29/6 | 2N3053 | 6/8 | 2N5457 | 9/9 |
| BD121 | 17/3 | TIP31A | 17/– | | | | |

**1 WATT AMPLIFIER MODULE TYPE PCM1**

This amplifier unit is a printed circuit module incorporating the popular and well tried PA234 i.c. amplifier. The unit is a complete AUDIO AMPLIFIER and requires no external components, you simply connect an 18 volt power supply and a 15 or 16 ohm speaker or head phone, even the supply smoothing capacitor and the output capacitor are included! The overall dimensions, including capacitors are 2½" × 3" × ¾". The input for 1 watt output at 1kHz is typically 300mV into 100 kohms.
This unit is available at only 36/– net complete with descriptive leaflet or 70/– net per pair. Send for free leaflet.

**ELECTRONIC COMPONENTS IN THE WEST MIDLANDS**

A wide range of components are available from stock for CALLERS, including the following:
RESISTORS (includes 5% ¼ watt, High stabs at only 2d. each in 100+ quantities of MIXED values of your choice in the E12 series from 10 ohm to 10 Mohm).
CAPACITORS (includes Polyesters, polystyrene, metallised film, miniature electrolytics, silver micas). SEMICONDUCTORS (includes integrated circuits, transistors, diodes, rectifiers).
PLUS ALL the usual components such as plugs and sockets, pots, Veroboard, etc.

**WE ARE AN INTERNATIONAL RECTIFIER SEMICONDUCTOR CENTRE**

Mail order, 1/6 P. & P. per order inland, Overseas at cost, min. 10/–. Open 9.00 a.m. to 12.30 p.m. 2.00 p.m. to 5.00 p.m. Weekdays, 9.00 a.m. to 12.30 p.m. Saturdays

ELECTRONICS LTD
Kinver
STONE LANE KINVER
STOURBRIDGE WORCS
Telephone KINVER 2099

# YATES ELECTRONICS

**RESISTORS**
High stability carbon film. Very low noise. 0·5 watt 5% 4·7Ω to 2·2MΩ **2d each.** 0·5 watt 10% 4·7Ω to 10MΩ **2d each.** 2 watt 20% 100Ω to 100kΩ **10d each.**

**DEVELOPMENT PACK**
0·5 watt 5% resistors 5 off each value 4·7Ω to 1MΩ
325 resistors E12 series **50/-.** 650 resistors E24 series **100/-.**

**MULLARD POLYESTER CAPACITORS ±10%**
400V: 0·001μF, 0·0015μF, 0·0022μF, 0·0033μF, 0·0047μF, **6d.** 0·0068μF, 0·01μF, 0·015μF, 0·022μF, 0·033μF, **7d.** 0·047μF, **9d.** 0·068μF, 0·1μF, **10d.**
160V: 0·01μF, 0·015μF, 0·022μF, 0·033μF, 0·047μF, 0·068μF, **7d.** 0·1μF, **9d.** 0·15μF, 0·22μF, **11d.** 0·33μF, **1/3.** 0·47μF, **1/6.** 0·68μF, **2/3.** 1·0μF, **2/6.**
250V: P.C. mounting miniature ±20%: 0·01μF, 0·015μF, 0·022μF, **7d.** 0·033μF, 0·047μF, 0·068μF, **8d.** 0·1μF, **9d.** 0·15μF, 0·22μF, **1/-.** 0·33μF, **1/4.**

**MYLAR FILM CAPACITORS**
100V: 0·001μF, 0·002μF, 0·005μF, 0·01μF, 0·02μF, **6d.** 0·05μF, 0·1μF, **8d.**

**CAPACITOR DEVELOPMENT PACK**
Selection of ceramic and polyester capacitors 100pF to 1·0μF. Total 100 capacitors. **£2.18.0.**

**MINIATURE ELECTROLYTIC CAPACITORS**

| | | | | | | | | | |
|---|---|---|---|---|---|---|---|---|---|
| 50μF | 6V | 16μF | 10V | 10μF | 12V | 40μF | 16V | 16μF | 40V |
| 100μF | 6V | 64μF | 10V | 16μF | 12V | 6·4μF | 25V | 50μF | 40V |
| 200μF | 6V | 125μF | 10V | 50μF | 12V | 25μF | 25V | 2·5μF | 64V |
| 320μF | 6V | 200μF | 10V | 100μF | 12V | 8μF | 40V | 10μF | 64V |

**1/- each.**
250μF 12V, 100μF 40V **1/6.** 1000μF 25V **6/-.** 2500μF 25V **9/-.** 500μF 50V **5/-.** 1000μF 50V **8/-.**

**CERAMIC DISC CAPACITORS**
10pF, 150pF, 220pF, 270pF, 330pF, 470pF, 560pF, 680pF, 1000pF, 2000pF, 5000pF, 10,000pF, **5d each.**

**GANGED STEREO POTENTIOMETERS**
¼ watt carbon track 5kΩ +5kΩ to 1MΩ +MΩ log or linear, **8/- each.**

**SKELETON PRE-SET POTENTIOMETERS**
Linear: 100, 250, 500 ohms and decades to 5M ohm ±20% ≤250kΩ, ±30%, —250kΩ. Horizontal or vertical P.C. mounting (0·1 matrix).
Miniature 0·3 watt **1/- each.**
Sub-miniature 0·1 watt **10d each.**

**SILICON RECTIFIERS**
BY236 800V 0·8 amp **3/- each.** BY237 1250V 0·8 amp **3/6 each.**

**VEROBOARD**

| | 0·15 Matrix | 0·1 Matrix | | 0·15 Matrix | 0·1 Matrix |
|---|---|---|---|---|---|
| 2½ × 3¾ | 3/3 | 3/6 | Pin insertion tool | 9/6 | 9/6 |
| 2½ × 5 | 3/9 | 4/3 | Pkt. 36 pins | 3/– | 3/– |
| 3¾ × 3¾ | 3/9 | 3/9 | Spot face cutter | 7/3 | 7/3 |
| 3¾ × 5 | 5/3 | 5/3 | | | |
| 17 × 3¾ | 14/6 | — | | | |

**C.W.O. please. 1/6 post and packing on orders under £1.**
**Export Enquiries welcome**

**YATES ELECTRONICS (FLITWICK) LTD.**
**29 LYALL CLOSE, FLITWICK, BEDS.**

# BI-PRE-PAK LIMITED

## FULLY TESTED AND MARKED

| | | | |
|---|---|---|---|
| AC107 | 3/- | OC170 | 3/- |
| AC126 | 2/6 | OC171 | 4/- |
| AC127 | 3/6 | OC200 | 3/6 |
| AC128 | 2/6 | OC201 | 7/- |
| AC176 | 5/- | 2G301 | 2/6 |
| ACY17 | 3/- | 2G303 | 2/6 |
| AF114 | 4/- | 2N711 | 10/- |
| AF115 | 3/6 | 2N1302-3 | 4/- |
| AF116 | 3/6 | 2N1304-5 | 5/- |
| AF117 | 3/6 | 2N1306-7 | 6/- |
| AF239 | 12/6 | 2N1308-9 | 8/- |
| AF186 | 10/- | 2N3844A | 5/- |
| AF139 | 10/- | **Power Transistors** | |
| BFY50 | 4/- | | |
| BSY25 | 7/6 | OC20 | 10/- |
| BSY26 | 3/- | OC23 | 10/- |
| BSY27 | 3/- | OC25 | 8/- |
| BSY28 | 3/- | OC26 | 5/- |
| BSY29 | 3/- | OC28 | 7/6 |
| BSY95A | 3/- | OC35 | 5/- |
| OC41 | 2/6 | OC36 | 7/6 |
| OC44 | 2/6 | AD149 | 10/- |
| OC45 | 2/6 | AUY10 | 30/- |
| OC71 | 2/6 | 2S034 | 10/- |
| OC72 | 2/6 | 2N3055 | 15/- |
| OC73 | 3/6 | **Diodes** | |
| OC81 | 2/6 | AAY42 | 2/- |
| OC81D | 2/6 | OA95 | 2/- |
| OC83 | 4/- | OA79 | 1/9 |
| OC139 | 2/6 | OA81 | 1/9 |
| OC140 | 3/6 | IN914 | 1/6 |

## FREE!

PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 10/- WITH ORDERS OVER £4

## SURPLUS INTEGRATED CIRCUITS

These are brand new genuine surplus stocks, marked and guaranteed to full makers' specification and not re-marked rejects.

| | | Price |
|---|---|---|
| NE808A | Single 8 I/P Nand Gate TTL | 7/- |
| NE816A | Dual 4 I/P Nand Gate TTL | 7/- |
| NE825A | D.C. Clocked J-K Flip-Flop TTL | 17/6 |
| NE840A | Dual 4 I/P Exclusive OR Gate TTL | 7/- |
| NE855A | Dual 4 Power Gate TTL | 7/- |
| NE870A | Triple 3 I/P Nand TTL | 7/- |
| NE880A | Quad 2 Nand TTL | 7/- |
| SP616A | Dual 4 Nand Gate DTL | 7/- |
| SP631A | Quad 2 I/P Gate Expander DTL | 7/- |
| SP670A | Triple 3 Nand Gate DTL | 7/- |
| SP806A | Dual I/P Expander TTL | 7/- |
| SP808A | Single 8 I/P Nand Gate TTL | 7/- |
| SP816A | Dual 4 I/P Nand Gate TTL | 7/- |
| SP825A | D.C. Clocked J-K Flip-Flop TTL | 17/6 |
| SP840A | Dual 4 I/P Exclusive OR Gate TTL | 7/- |
| SP855A | Dual 4 Power Gate TTL | 7/- |
| SP870A | Triple 3 I/P Nand TTL | 7/- |
| SP880A | Quad 2 I/P Nand TTL | 7/- |
| NE500K | Video Amplifier | 40/- |
| NE501K | Video Amplifier 40MHz | 40/- |
| NE806J | Dual 4 I/P Expander TTL | 7/- |
| NE808J | Single 8 I/P Nand Gate TTL | 7/- |
| NE816J | Dual 4 I/P Nand Gate TTL | 7/- |
| NE825J | D.C. Clocked J-K Flip-Flop TTL | 17/6 |
| NE840J | Dual 4 I/P Exclusive OR Gate TTL | 7/- |
| NE855J | Dual 4 Power Driver TTL | 7/- |
| NE880J | Quad 2 I/P Nand TTL | 7/- |
| ST620A | J-K Flip-Flop DTL | 17/6 |
| ST659A | Dual 4 Buffer/Driver DTL | 7/- |

Suffix A = DIP 14 lead; K = 10 lead TO5; J = Flat pack.

## NEW TESTED AND GUARANTEED PAKS

| | | | |
|---|---|---|---|
| B2 | 4 | Photo Cells, Sun Batteries. 0·3 to 0·5V, 0·5 to 2mA. | 10/- |
| B77 | 2 | AD161–AD162 NPN/PNP Trans. Comp. Output. Pair | 10/- |
| B81 | 10 | Reed Switches, mixed types large and small | 10/- |
| B89 | 2 | 5SP5 Light Sensitive Cells. Light Res. 400 Ω Dark 1M Ω | 10/- |
| B91 | 8 | NKT163/164 PNP Germ. TO-5 equivalent to OC44, OC45 | 10/- |
| B92 | 4 | NPN. Sil. Trans. AO6 = BSX20, 2N2369 500 MHz, 360mW | 10/- |
| B93 | 5 | GET113 Trans. equiv. to ACY17–21 PNP Germ. | 10/- |
| B96 | 5 | 2N3136 PNP Sil. Trans. TO-18, HFE 100–300 I.C. 600mA. 200 MHz | 10/- |
| B98 | 10 | XB112 and XB102 equiv. to AC126, AC156, OC81/2, OC71/2, NKT271, etc. | 10/- |
| H4 | 250 | Mixed Resistors. Post and Packing 2/- | 10/- |
| H7 | 40 | Wirewound Resistors. Mixed types and values. Postage 1/6 | 10/- |
| H8 | 4 | BY127 Sil. Recs 1000 PIV. 1 amp. plastic | 10/- |
| H9 | 2 | OCP71 Light Sensitive Photo Transistor | 10/- |

## LOOK! TRANSISTORS ONLY 6d EACH

**TYPE A**
PNP SILICON ALLOY TO-5 CAN
SPEC:—
ICER AT VCE=20v 1mA MAX.
HFE 15–100
THESE ARE OF THE 2S300 TYPE WHICH IS A DIRECT EQUIVALENT TO THE OC200/205 RANGE

**TYPE B**
PNP SILICON PLASTIC ENCAPSULATION
SPEC:—
ICER AT VCE=10v 1mA MAX
HFE 10–200
THESE ARE OF THE 2N3702/3 AND 2N4059/62 RANGE

**TYPE E**
PNP GERMANIUM FULLY MARKED AND TESTED.

AF. or RF.
PLEASE STATE ON ORDER

## RETURN OF THE UNBEATABLE P.1 PAK.
## NOW GREATER VALUE THAN EVER

FULL OF SHORT LEAD SEMICONDUCTORS AND ELECTRONIC COMPONENTS, APPROX. 170. WE GUARANTEE AT LEAST 30 REALLY HIGH QUALITY FACTORY MARKED TRANSISTORS PNP AND NPN, AND A HOST OF DIODES AND RECTIFIERS MOUNTED ON PRINTED CIRCUIT PANELS. IDENTIFICATION CHART SUPPLIED TO GIVE SOME INFORMATION ON THE TRANSISTORS.

PLEASE ASK FOR PAK **P.1** ONLY **10/-**
2/- P. & P. on this Pak.

**Make a Rev. Counter for your Car.** The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car. **20/- each**




## NEW UNMARKED UNTESTED PAKS

| | | | |
|---|---|---|---|
| B78 | 12 | Intergrated Circuits, Data and Circuits of types, supplied with orders | 10/- |
| B80 | 8 | Dual Trans. Matched O/P pairs NPN. Sil. in TO-5 can | 10/- |
| B82 | 10 | OC45, OC81D and OC81 Trans. Mullard glass type | 10/- |
| B83 | 200 | Trans. manufacturer's rejects all types NPN, PNP, Sil. and Germ. | 10/- |
| B84 | 100 | Silicon Diodes DO-7 glass equiv. to OA200, OA202 | 10/- |
| B66 | 150 | High quality Germ. Diodes. Min. glass type | 10/- |
| B86 | 50 | Sil. Diodes sub. min. IN914 and IN916 types | 10/- |
| B87 | 100 | Germ. PNP Trans. equiv. to OC44, OC45, OC81, etc. | 10/- |
| B88 | 50 | Sil. Trans. NPN, PNP, equiv. to OC200/1, 2N706A, BSY95A, etc. | 10/- |
| B60 | 10 | 7 Watt Zener Diodes Mixed Voltages | 10/- |
| H5 | 16 | 1 Amp. Plastic Diodes 50-1000 Volts | 10/- |
| H6 | 40 | 250mW. Zener Diodes DO-7 Min. Glass Type | 10/- |

**FREE CATALOGUE AND LISTS for:—**

**ZENER DIODES**
**TRANSISTORS, RECTIFIERS**
**FULL PRE-PAK LISTS**
**& SUBSTITUTION CHART**

MINIMUM ORDER 10/- CASH WITH ORDER PLEASE. Add 1/- post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

**P.O. RELAYS** **8 FOR 20/-**
Various Contacts and Coil Resistances. No individual selection. Post & Packing 5/-

**FREE! A WRITTEN GUARANTEE WITH ALL OUR TESTED SEMICONDUCTORS**

**BI-PRE-PAK LTD** DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

# LOOK!

**PRACTICAL!**
**VISUAL!**
**EXCITING!**


*a new 4-way method of mastering*

# ELECTRONICS

*by* ***doing*** *— and —* ***seeing . . .***

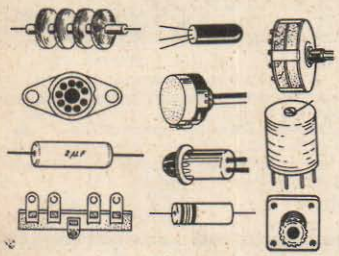
**1** **OWN and HANDLE a**

complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**




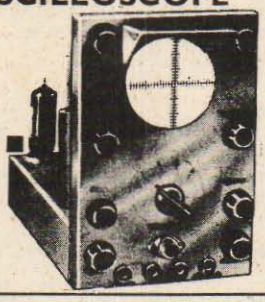**2** **BUILD and USE**

a modern and professional **CATHODE RAY OSCILLOSCOPE**



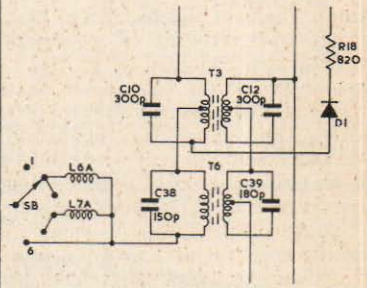**3** **READ and DRAW and UNDERSTAND CIRCUIT DIAGRAMS**




**4** **CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .**

- VALVE EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- AMPLIFIERS
- OSCILLATORS
- SIGNAL TRACER
- PHOTO ELECTRIC CIRCUIT
- COMPUTER CIRCUIT
- BASIC RADIO RECEIVER
- ELECTRONIC SWITCH
- SIMPLE TRANSMITTER
- A.C. EXPERIMENTS
- D.C. EXPERIMENTS
- SIMPLE COUNTER
- TIME DELAY CIRCUIT
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

**FREE** POST NOW for BROCHURE

or write if you prefer not to cut page

**To: BRITISH NATIONAL RADIO SCHOOL, READING, BERKS. Please send your free Brochure, without obligation, to:** *we do not employ representatives*

NAME..... BLOCK CAPS

ADDRESS..... PLEASE P.E.8

VOL. 6 No. 8
August 1970

# PRACTICAL ELECTRONICS

Editor F. E. BENNETT Assistant Editor M. A. COLWELL Editorial Assistants D. BARRINGTON G. GODBOLD M. KENWARD
Art Editor J. D. POUNTNEY Technical Illustrators J. A. HADLEY P. A. LOATES
Advertisement Manager D. W. B. TILLEARD

## FINE ART

INDUSTRIAL Art has become a recognised subject for comment and serious study. But surprisingly, electronic engineering is not given the amount of attention it would seem to deserve. At first, it may seem a trifle absurd to consider electronic hardware in terms of art. Yet there is a beauty of form and colour in many a humble mass produced component, and intricate patterns pleasing and attractive to the eye are composed by electronic assemblages making up severely functional equipment. No matter how practical and down-to-earth we may be, there is no reason why we should be blind to this aesthetical quality.

But this incidental, or accidental, art of the component manufacturer and the wireman is concealed from lay eyes by sombre metallic shrouds or wooden caskets which have for long been deemed the right and proper housing for much electronic equipment. For the general user, the outward sign of electronics is limited to the appendages mounted on a control panel. Notwithstanding the good styling of these adjuncts, and the obvious thought which is bestowed upon their arrangement, such items are not representative of the true "electronic art" which exists within.

Look again at those delicate nerve-like systems traced by multi-coloured leads of a cableform; at the variety of maze patterns provided by printed circuit boards; and at the mosaics built up from resistors and capacitors variegated not only in hue and shape but in their disposition, and those tiny semiconductor devices whose jewel-like resemblance is often most striking.

Here one would have thought is wealth indeed for artist and sculptor alike to contemplate and adopt for their particular purposes—with tremendous effect. In contrast, how pitiful are certain works of art that some of our artistic contemporaries have presented to the public gaze as representative of, or inspired by, electronic technology!

The moral would seem to be this. If electronics is to have an influence in the world of art commensurate with its great impact in strictly practical matters, it must reveal more to the public eye. Maybe some drastic rethinking by industrial designers and engineers is overdue. Why not make certain domestic equipments living works of art by using transparent cases; or even encapsulating complete assemblies in blocks of transparent resin. And why not think in terms of less conventional shapes for the complete equipment. Flexible printed circuits and wiring boards could free designers from the limitations of the commonplace rectangular box; would not spherical forms be more appropriate for the space age?

F.E.B.

## THIS MONTH

### CONSTRUCTIONAL PROJECTS

ANEMOMETER 606
OSCILLOSCOPE CALIBRATOR 627
DECIMAL CURRENCY CONVERTER 638
TRANSISTOR D.C. MULTIMETER 649

### SPECIAL SERIES

MAKING THE MOST OF LOGIC I.C's—2 643

### GENERAL FEATURES

ANALYTICAL ELECTRON MICROSCOPE 614

### BEGINNERS

PROJECT BUILDING 620
METRONOME 622
THIS WAY TO ELECTRONICS—5 632

### NEWS AND COMMENT

EDITORIAL 605
PRACTICAL ELECTRONICS! 613
SPACEWATCH 624
BOOK REVIEWS 631
POINTS ARISING 635
ELECTRONORAMA 636
MARKET PLACE 657

***Our September issue will be published on Friday, August 14***

© IPC Magazines Limited 1970. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Subscription Rates including postage for one year, to any part of the world, 45s.
Editorial and advertisement offices: Fleetway House, Farringdon St., London, E.C.4. Phone 01-236 8080

# ANEMOMETER

By J.S.HAGGIS

For anyone interested in meteorology, sailing, or just wind speed, the cost of an anemometer is rather high. When the author's son became interested in meteorology, an anemometer was required, so one was constructed using readily available components.

Many commercial remote anemometers work on the a.c. generator principle, that is the faster the generator armature is rotated by the wind force on the anemometer cups, the greater the voltage produced. This has the disadvantage of not giving a linear output, with the consequent difficulty of meter scale production. It also requires about a 5 m.p.h. wind to overcome the resistance of the magnetic poles of the generator before the cups will start to rotate.

With the anemometer described, wind speeds of less than 5 m.p.h. can also be measured, and the scale is linear. The design is suitable for use on sailing yachts, and details are given on how to run the unit from the boat's power supply.

If three anemometer cups are arranged to rotate freely in the wind, and a disc with a number of holes around the periphery is fixed to a shaft being driven by the cups, the holes can be counted as they revolve with the aid of a light source and a phototransistor. This count can then be made to register on a meter.

## CIRCUIT DESCRIPTION

When the holes in the rotating disc pass over the phototransistor, light is allowed to fall on the phototransistor (TR1) from the light source, producing a pulse at the collector of TR1 as indicated in Fig. 1, the circuit diagram of the anemometer. The pulse is squared off by transistors TR2 and TR3 which form a Schmitt trigger. The pulse is then differentiated by C2 and R8 to trigger transistors TR4 and TR5 which constitute a monostable. It is arranged by the selection of C2, that the monostable is in its unstable state for 3 milliseconds. This timing is such that at a wind speed of 100 m.p.h. (higher than one hopes to experience) the monostable has time to return to its stable state before the next pulse.

The time of 3 milliseconds is selected to correspond to the disc and hole size described in this article, and any increase or decrease in disc or hole size will have to be compensated for. Meter M1 integrates the 3 millisecond pulses which vary in frequency, but are all of the same duration.

At wind speeds of less than 5 m.p.h. the pulses are detectable on the meter as fluctuation of the needle. The fluctuation can be reduced by fitting a 100$\mu$F capacitor (C3) across meter M1; this does not completely eliminate the pulsing, so at very low speeds one can check that the system is not missing pulses by observing a regular flick on the meter.

## CIRCUIT POWER SUPPLY

It is essential for consistent reliability to have a good stabilised power supply. The mains power supply in Fig. 2, is stabilised with the aid of the Zener diode D7. It incorporates a series resistor which provides overload protection. When the anemometer is to be used from a 12 volt or 24 volt battery the supply for lamp and circuitry can be as shown in Figs. 3 and 4; all resistors used in these two circuits are wirewound types.


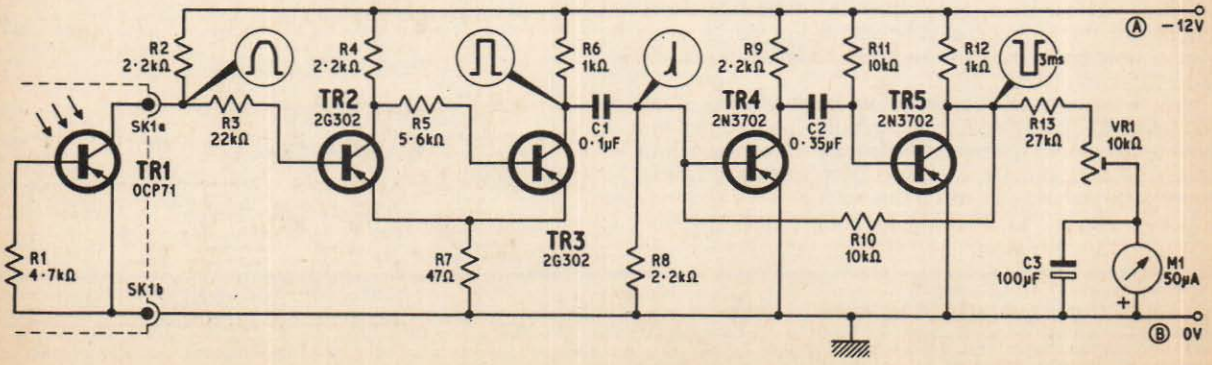



*Fig. 1. Circuit diagram of the basic anemometer*

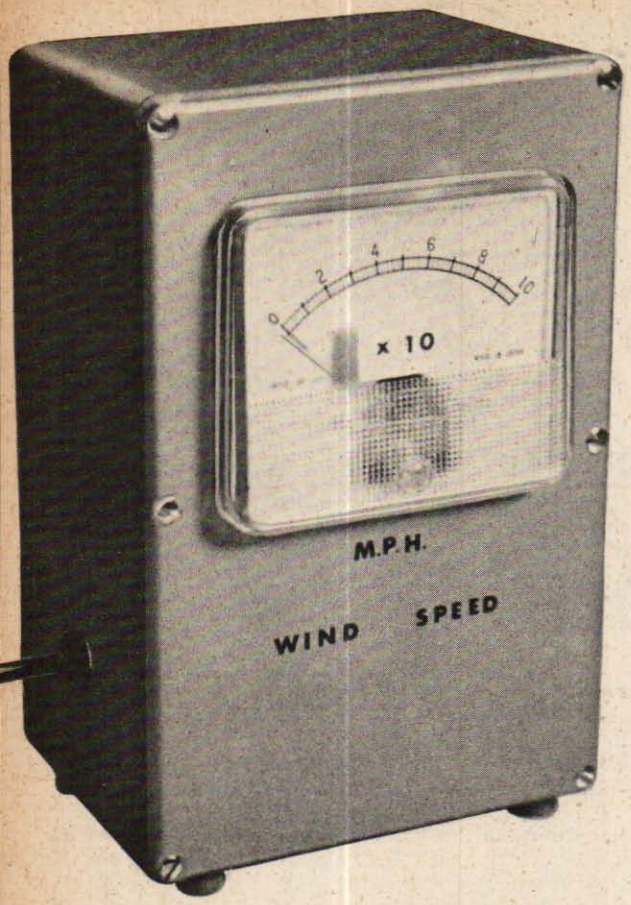

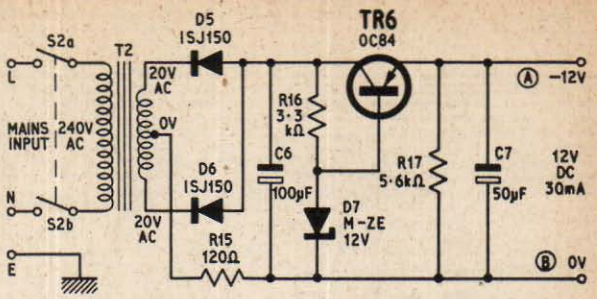




*Fig. 2. Mains power supply circuit for the anemometer circuit*

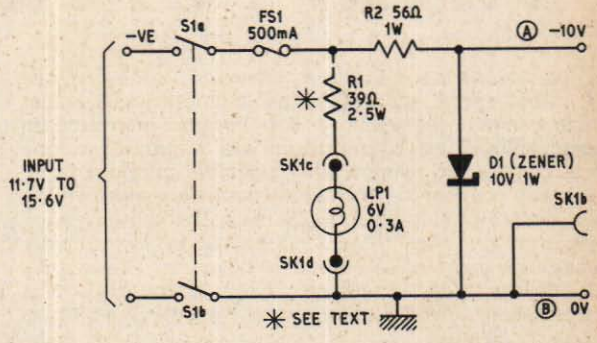



*Fig. 3. Power supply to operate the anemometer circuit and lamp from a 12V battery*

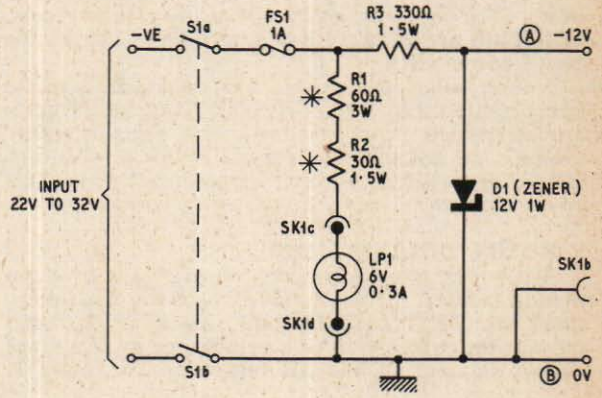



*Fig. 4. Power supply to operate the anemometer circuit and lamp from a 24V battery*

As can be seen from Fig. 3 the supply circuit for a 12 volt battery only provides 10 volts d.c. to the anemometer circuit. This is so that stabilisation of the 12 volt input can be effected by R2 and D1, the lower voltage will not affect circuit operation providing that the instrument is calibrated at the lower voltage, and not used at a higher voltage afterwards.

## LAMP POWER SUPPLY

A 6·5 volt 0·3 amp bulb is used to illuminate TR1; the voltage on the bulb should be kept as low as possible to increase bulb life. A mains operated circuit for the bulb supply is given in Fig. 5. A good d.c. supply must be used or the anemometer will be unreliable in operation.

The value of R1 Fig. 3, or R1 and R2 Fig. 4, or R14 Fig. 5, depends on the length of wire used to carry the supply to the anemometer; in most cases this will be many yards, therefore an appreciable volt drop can be expected. Bearing in mind the need to keep the bulb voltage as low as possible, the appropriate resistor may have to be slightly adjusted in value, as explained later.

## CIRCUIT CONSTRUCTION

The circuit is assembled on a printed circuit board, details of which are given in Fig. 6. Layout is not critical, but that detailed has proved successful. If the




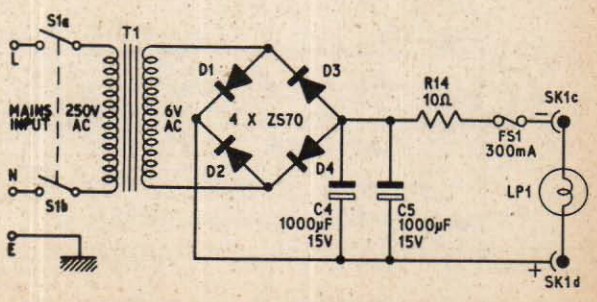



*Fig. 5. Mains power supply circuit for the lamp*

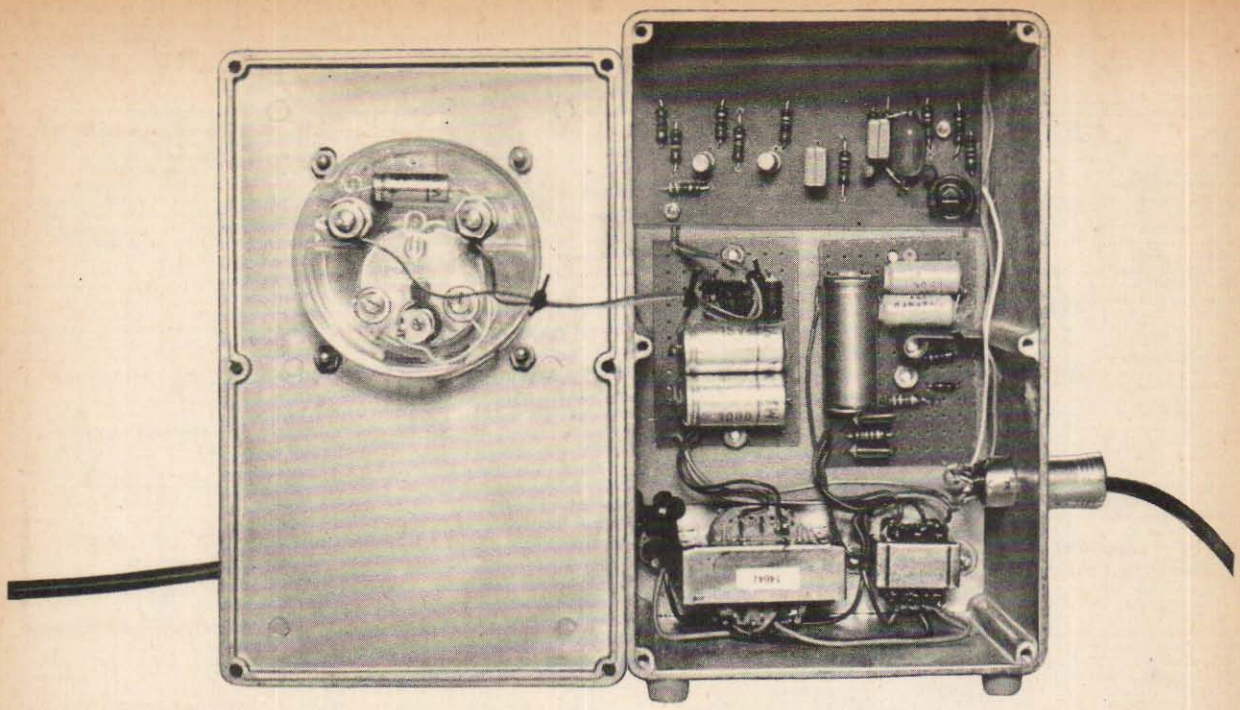

## ANEMOMETER CIRCUIT WIRING

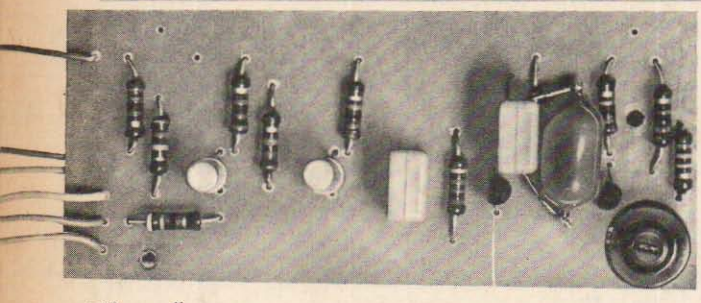

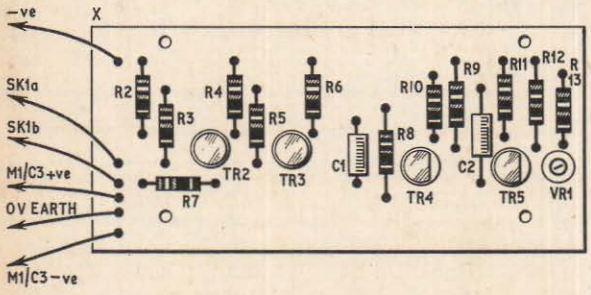

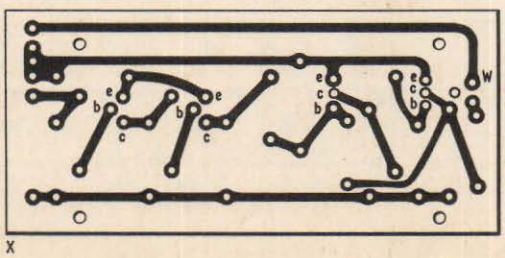




*Fig. 6. Layout of the anemometer circuit on a printed circuit board*

## COMPONENTS . . .

**Resistors**

| | |
|---|---|
| R1 | 4·7kΩ |
| R2 | 2·2kΩ |
| R3 | 22kΩ |
| R4 | 2·2kΩ |
| R5 | 5·6kΩ |
| R6 | 1kΩ |
| R7 | 47Ω |
| R8 | 2·2kΩ |
| R9 | 2·2kΩ |
| R10 | 10kΩ |
| R11 | 10kΩ |
| R12 | 1kΩ |
| R13 | 27kΩ |

All ¼W, 10% carbon

**Capacitors**

| | |
|---|---|
| C1 | 0·1μF polyester |
| C2 | 0·35μF polyester (0·1μF and 0·25μF in parallel) |
| C3 | 100μF elect. 12V |

**Transistors**

| | |
|---|---|
| TR1 | OCP71 (phototransistor) |
| TR2 | 2G302 |
| TR3 | 2G302 |
| TR4 | 2N3702 |
| TR5 | 2N3702 |

**Miscellaneous**

| | |
|---|---|
| VR1 | 10kΩ skeleton preset potentiometer |
| M1 | 50μA moving coil meter |
| SK1 | Miniature sealed four pin plug and socket |
| | Copper clad s.r.b.p. board 4½in × 2in |

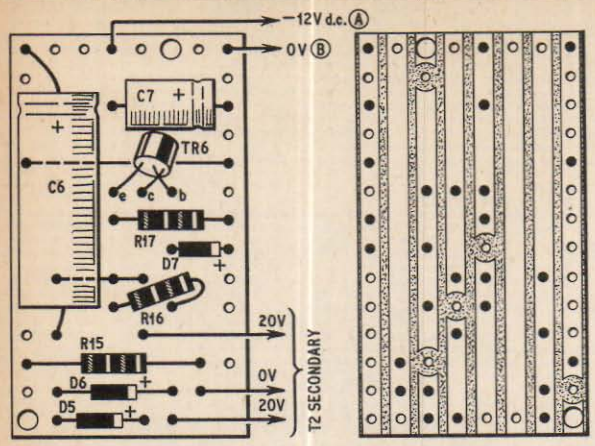



*Fig. 7. Layout of the mains power supply for the anemometer circuit using Veroboard*

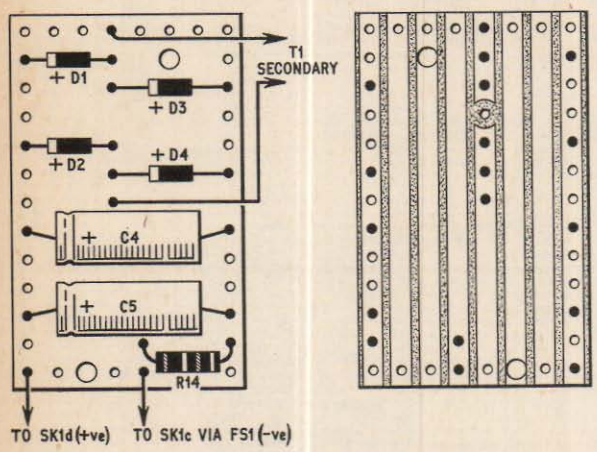



*Fig. 8. Layout of the mains power supply for the lamp using Veroboard*

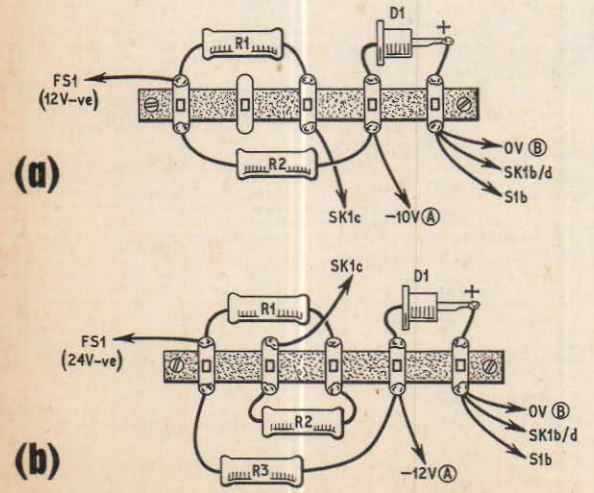



*Fig. 9. Layout of the battery supplies using a five-way tagstrip (a) for a 12V battery, (b) for a 24V battery*

## COMPONENTS . . .

### MAINS CIRCUIT SUPPLY

**Resistors**
R15 120Ω
R16 3·3kΩ
R17 5·6kΩ
All ¼W, 10% carbon

**Capacitors**
C6 100μF elect. 50V
C7 50μF elect. 25V

**Semiconductors**
TR6 OC84
D5, 6 ZS70 *or* SX641 *or* DD003 *or* ISJ150 (2 off)
D7 12V 250mW 5% Zener type M-ZE12 (Radiospares) or Z12

**Miscellaneous**
T2 Miniature mains transformer 220/240V primary 20V–0V–20V secondary (Radiospares)
S2 D.P.S.T. toggle switch
Veroboard 2in × 1¼in, 0·15in matrix

## COMPONENTS . . .

### MAINS LAMP SUPPLY

**Resistor**
R14 10Ω (see text)

**Capacitors**
C4 1,000μF elect. 15V
C5 1,000μF elect. 15V

**Diodes**
D1-4 ZS70 *or* DD003 (4 off)

**Transformer**
T1 Miniature mains transformer 220/240V primary 6V, 300mA secondary

**Miscellaneous**
FS1 300mA fuse and holder
S1 D.P.S.T. toggle switch
LP1 6·3V, 0·3A m.e.s. bulb
Clip on m.e.s. bulb holder (Radiospares)
Veroboard 2in × 1¼in, 0·15in matrix

constructor is not able to etch the component board, then Cir-kit copper strip can easily be made to follow the layout given.

Layout and wiring diagrams for the circuit and bulb supplies are given in Figs. 7, 8 and 9. The two layouts shown in Fig. 9 use tag strips because some of the components may warm up when the unit is in use. It is not normally necessary to provide a heat sink for the Zener diode as this diode will only pass current near to its maximum capability when no current is taken by the anemometer circuitry, and when battery voltage is at its highest.

The circuit boards, M1, and S1 can be mounted in a die cast box, the size of which will depend on the type of power supply used. If the unit is for use on a sailing boat, or will be out in the elements, both the inside and outside of the case should be painted; the lid, supply lead and SK1 should be sealed.

Meter M1 can be any 50μA type available with as large a scale as possible and is best mounted on a rubber



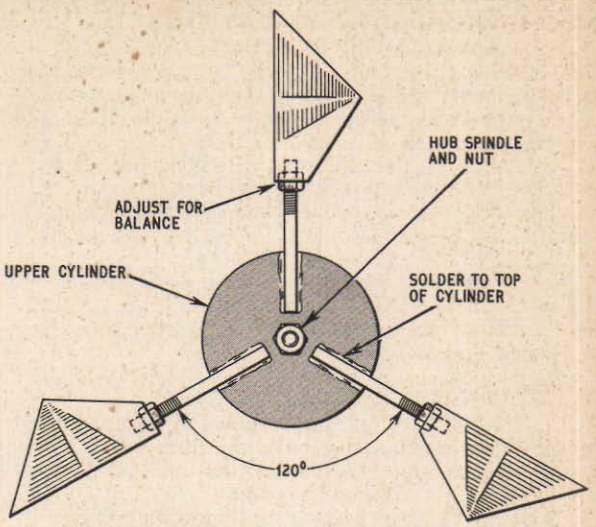



*Fig. 12. Arrangement of the cups and arms on the rotating cylinder*

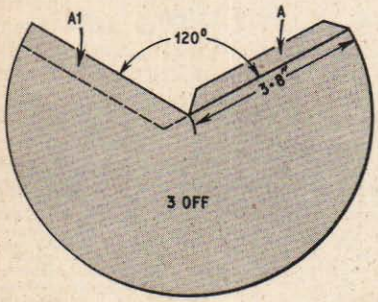



*Fig. 10. Development of one cup*

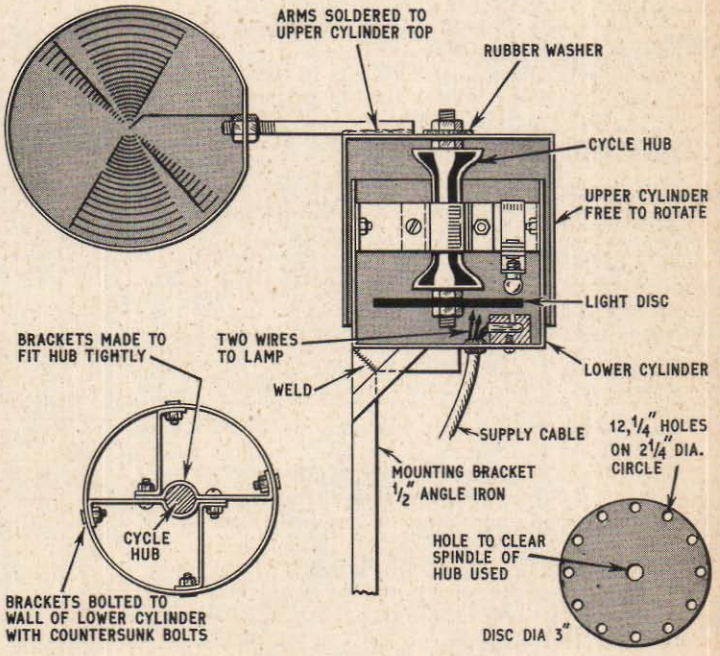



*Fig. 11. Construction of the anemometer head, a four core lead out wire is needed*

## MATERIALS . . .

Brass plate 3½in × 3½in × $\frac{1}{16}$in (disc)
Copper sheet 20in × 20in, 20 s.w.g. (cups, cylinders and hub brackets)
Round brass rod 12in × ¼in diameter (cup arms)
Whitworth nuts ¼in 6 off (cup fixings)
Bicycle front wheel hub complete with nuts (see text)
Nylon or rubber washer to fit hub
Countersunk bolts 4B.A., ½in, 4 off (hub bracket fixings)
Round head bolts 4B.A., ½in, 3 off (hub bracket and TR1 block fixings)
Nuts 4B.A., 6 off
Angle iron 12in × ½in × ½in (mounting bracket if required)
Tuffnol 1⅝in × ⅜in × ⅜in (TR1 and R1 mounting)
Diecast case (see text)
Veropins 3 off (TR1 and R1 mounting)

washer. The circuit boards can be mounted on foam rubber to provide shock protection where necessary.

## MECHANICAL CONSIDERATIONS

With reference to the *Handbook of Meterological Instruments*, it was found that the best arrangement is an anemometer using 3 cups of 5 inches diameter, the centre of the cups rotating $6\frac{1}{2}$ inches from the axis. As will be appreciated, the aerodynamics of the cups bear some relation to the efficiency of the rotation. The cups described here are not the ultimate in design, but they can easily be constructed and are quite adequate for the job, giving reasonable accuracy to the anemometer.

Ideally, all metal work is best made from copper or brass, as there is then no trouble from corrosion, bearing in mind that the instrument will suffer the worst of the elements.

## CUP CONSTRUCTION

A development of one cup is shown in Fig. 10; three of these are required to make the three cups. The copper is bent smoothly round so that tab "A" lies on "A1" where it is soldered in position.

On the edge of each cup, by the joint of tabs "A" and "A1", the shape is slightly flattened to take the arms, as shown in Fig. 11. The arms are made from $\frac{1}{4}$ inch brass rod 4 inches long, threaded at one end. The threaded end passes through a hole in the side of the cup wall near the periphery. One nut either side of the cup wall is used so that the position of the cups on the arms can be adjusted in order that the three can be balanced. It is best not to bolt the cups to the arms at this stage, but to wait until the arms have been soldered to the top of the anemometer body.

## BODY CONSTRUCTION

As can be seen in Fig. 11 the body of the instrument consists of two copper cylinders, one fitting over the other. The lower cylinder is fixed, while the upper cylinder is free to be rotated by the pressure of the wind on the cups. The upper cylinder has a diameter of 4·4 inches and is 4 inches deep, while the lower cylinder has a diameter of 4 inches and is 3·6 inches deep. The construction of these two open ended cylinders is quite simple therefore no further details will be given here.

Some form of bearing is required to support the upper cylinder; the prototype unit used the hub from a bicycle front wheel. It is quite important that this hub be in good condition, for if low and reliable wind speeds are to be recorded, there must be very little mechanical friction.

The hub must be secured to the walls of the lower cylinder; this is achieved by making 4 brackets from 20 s.w.g. copper strip as illustrated in Fig. 11. The brackets must be made to fit tightly around the hub—the diameter of the clip will depend on the make of hub used. The brackets should be about 1 inch deep.

The four brackets are bolted around the centre of the hub and placed inside the lower cylinder to ensure that the hub fits precisely in the centre.

The light disc is constructed from $\frac{1}{16}$ inch brass plate as shown in Fig. 11, and is 3 inches in diameter. A hole is drilled in the centre to take the spindle of the hub. Twelve $\frac{1}{4}$ inch diameter holes are drilled around the disc, the centre of the holes being $\frac{3}{8}$ of an inch from the periphery; the holes are set 30 degrees apart. It is advisable to paint the disc with matt black paint when complete, this will stop any chance of light reflections affecting the phototransistor. The inside of both cylinders should also be painted matt black.

## ASSEMBLY

The disc is bolted to one end of the hub spindle and the whole assembly, that is the hub complete with brackets and disc, is placed in the lower cylinder leaving a clearance of 0·8 inch between the disc and the bottom of the cylinder. The Tuffnol phototransistor mounting block is situated beneath the disc. No precise measurements are given for the fitting of the hub, because it depends a great deal on the type of hub used. With the hub held in the centre, and with 0·8 inch clearance between the disc and cylinder base, the 4 holes that secure the brackets to the cylinder walls can be drilled through the wall and bracket at the same time. It is necessary to countersink the cylinder holes as much as possible, this being done the brackets can be bolted to the cylinder. The heads of the countersunk bolts are then filed down to conform to the radius of the cylinder wall, to prevent them touching the inner wall of the upper cylinder. The spindle and disc should now spin freely in the lower cylinder.

The upper cylinder is completed by drilling a hole in the centre of the top to take the hub spindle. The arms are soldered in place on the top of the cylinder, they are placed at an angle of 120 degrees to each other, as shown in Fig. 12. The arms are not taken to the centre of the top, as a space is left in the centre to take the nut of the spindle.

When this has been done the cups can be fitted onto the threaded ends of the arms as shown in Figs. 11 and 12. The assembly can now be tried out in position over the lower cylinder by placing the top end of the hub spindle through the hole in the top of the upper cylinder. A nylon or rubber washer is placed over the spindle and the nut is screwed on and tightened; the nylon or rubber washer seals the spindle hole.

The upper cylinder, complete with cups, should be free to rotate over the lower cylinder without touching. Check that there is good clearance between the two all the way round and correct if necessary.

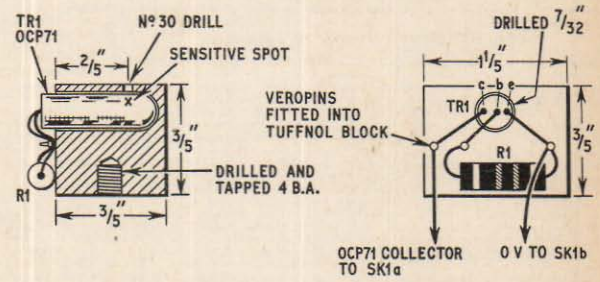



*Fig. 13. Mounting block for TR1 and R1*

## PHOTOTRANSISTOR MOUNTING

Phototransistor TR1 is mounted on a block of Tuffnol as shown in Fig. 13. A $\frac{7}{32}$ inch hole is drilled into the side of the block, as close to the top as possible, this hole is to hold the phototransistor. A second hole is drilled at right angles to the first hole with a No. 30 drill. The two holes connect with each other as shown in Fig. 13. The second hole is to allow light from LP1 to reach the sensitive spot of phototransistor TR1.

In the block, at the rear of TR1, three small holes are drilled to take three Veropins. These pins act as connecting points for TR1 and R1. Resistor R1 is mounted close to TR1 to reduce the number of wires from the anemometer head to the remote circuitry.

A 4B.A. hole is drilled and tapped in the base of the block to secure it to the base of the lower cylinder.

Inspection of the internals of the OCP71 will reveal two junctions, one either side of a flat plate, it is the smaller of these junctions that is sensitive to light, and it is this junction that must be positioned under the small hole in the mounting block. Once TR1 is in position with the sensitive spot placed correctly, a dab of adhesive is applied to prevent the phototransistor from moving.

The bulb to supply the light is mounted in a clip on bulb holder. The clip is pushed over one of the hub brackets, as shown in Fig. 11. It should be positioned close to the disc and directly over the holes.

## SETTING-UP

Before any setting up can be completed, the phototransistor block must be secured in position. To do this remove the upper cylinder from the spindle, and remove the hub and bracket from the lower cylinder. Remove the disc from the spindle, and replace the hub, less the disc, and secure. Now position the phototransistor block with its light hole immediately under the bulb and mark its position on the base of the cylinder. Remove the hub and secure the phototransistor block, complete with the phototransistor and R1, to the marked position.

The hole that secures the block to the base of the cylinder can be slightly larger than the 4B.A. bolt as this will allow the block to be finally adjusted. Now re-assemble the lower cylinder.

With the anemometer on the bench, rotate the disc until a hole is directly under the bulb so that light can fall on TR1. Connect the power supply to the anemometer circuit, ensuring the correct polarity, and connect up the bulb supply, using the same length of cable as will be required when the anemometer is installed.

Aim to apply the minimum voltage to the bulb to reliably operate the circuit. In the prototype, the component values shown in Fig. 5 were used. The circuit arrangements shown in Figs. 3, 4 and 5 apply approximately 4 volts to the bulb at the end of 40 yards of 14/0·0076 cable. The d.c. voltage supplied by the circuit of Fig. 5 has a ripple of 270 millivolts.

## COLLECTOR VOLTAGE

With light falling on TR1, collector voltage must be less than minus 0·5 volts. If the collector voltage is above 0·5 volts when measured with a d.c. meter, adjust the bulb position, or the position of TR1, until the voltage is correct. In some cases it may be necessary to reposition TR1 in the mounting block. If this fails, then the bulb voltage should be increased by changing the value of R1 in Figs. 3 and 4 or R14 in Fig. 5. Once the voltage has been set rotate the disc to cut off the light, and check that the collector voltage of TR1 has increased to almost the supply voltage. When a battery supply is to be used the above procedure should be carried out at the lowest normal battery voltage.

The upper cylinder complete with cups can now be fitted and revolved. If an oscilloscope is available observe the output from TR1 collector to ensure that the circuit is not missing any pulses. If no oscilloscope is available, connect meter M1 into the circuit with C3 disconnected. Revolve the cups slowly and check that the meter registers regular pulses.

## CALIBRATION

At a height of 33 feet above ground level, wind speeds will seldom exceed 70 m.p.h. in this country,

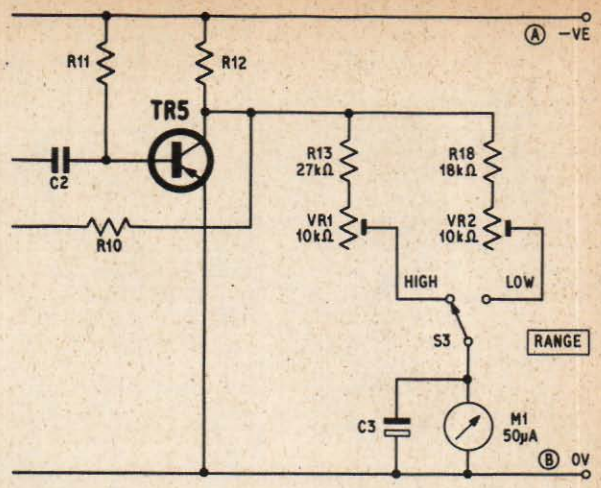



*Fig. 14. Diagram of the additional range circuitry*

therefore it is suggested that the maximum reading of the meter be 70 m.p.h. If it is required to operate in very exposed areas it may be necessary to have a full scale reading of 100 m.p.h., but the lower the maximum can be kept the better it will be for reading low wind speeds, unless a very large meter is used.

It is possible to add a lower scale to the anemometer by including a range switch and additional resistor and trimmer as shown in Fig. 14. If this is done both ranges will have to be calibrated as described below.

Having decided what maximum scale is required it is necessary to draw the scale on a plain meter backing card, numbering every 10 m.p.h. and marking every single m.p.h. The scale is linear.

The best way to calibrate the instrument is against the reading of an existing anemometer, but an alternative is to calibrate against a car speedometer. To do this a calm day is needed so that the only airflow is that of the cups through still air, and not against a wind adding to the required speed. Hold the anemometer as far away from the car body as possible to get away from any slipstream. With the car travelling at a steady 10 m.p.h. adjust VR1 until the meter of the anemometer reads 10 m.p.h. Then travel at greater speeds to check through the range.

## POSITION OF ANEMOMETER

The wind speed near the surface of the Earth varies rapidly with height and is also greatly affected by the presence of obstacles such as trees or houses. The *Handbook of Meteorological Instruments* defines the conditions under which measurements should be made for climatological records, as over open level terrain at a height of 33 feet above ground level. "Open level terrain" is defined as an area where the distance between the anemometer and any obstruction is at least 10 times the height of the obstruction above ground level at the anemometer.

It is unlikely that all constructors will be able to fulfill these requirements, but the position should be chosen with these requirements in mind and a suitable compromise can usually be reached.

The constructor may wish to build the mechanical parts of the instrument in a different manner than that described, or with slightly different dimensions. A pair of small roller bearings can be utilised if this is found to be more convenient than the "hub" system described. ★



# Practical Electronics!!

## By JUDITH TERRY

I AM constantly being re-assured of the advantages of this table-top hobby. One's husband can be at home, in fact in the very same room as his wife and still pursue his hobby —no gallivanting, leaving a distraught and worried wife at home wondering where on earth he is. True—and this as far as I can see is the only advantage of this hobby, though there *are* others, I am told.

Think of all the marvellous "mod-cons" one can have! The Jones' will really have their work cut out keeping up with us. Automatic garage doors and gates which save us the tedium of getting out of the car to open them; a lawn mower which goes scampering off round the lawn on its own, while my husband sits in a deck chair occasionally glancing up from his paper to see that it is not making a bee-line for him; the automatic camera which clicks each time a little bird sits on the bird table; the automatic chicken feeder which sprays food out to the free-range chickens at regular intervals; and the washing machine which miraculously switches itself on at four in the morning, and by the time we get up, all the weekly wash is done! So what am I complaining about? You may well ask.

As yet, these and many other ideas are only on the drawing board, so to speak, and some, not even as far advanced as that, but are only ideas lurking darkly in my husband's imagination. To begin with, we have not even our own house, let alone garage, gates and lawn and certainly no chickens! However, the projects go ahead as if we had all these things and each time we move, we leave behind a landlady bewildered by what she saw of those embryonic inventions!

Consider the words "table-top hobby". Indeed this is no misnomer! Oh no! There are always little "bits" (and some not so little!) on our dining room table and were it not for the fact that my husband likes food even more than electronics, we should never clear even the smallest space for our meals.

As it is, we sit amidst a jumble of soldering irons smoking ominously, circuit diagrams and hundreds of little striped things, with fine wiry legs which I am told are very expensive. Not that that makes them any the more acceptable!

I noted with a sigh this morning, that when we leave a bewildered landlady behind this time—we will leave an irate one because there are now a dozen little drill holes in that polished table.

When we move, and it seems we are destined to be an itinerant family, all the "bits" go with us. They are carefully and lovingly packed in tin boxes and huge wooden crates.


Amongst the things we carry round with us are several old washing machine motors, which "may come in handy" (I ask you!) and a pair of the most incongruous binoculars I have ever seen! These latter are almost 2ft long and weigh about 9lb and have to be *strapped* onto one's head. If you have ever tried strapping a 2ft long, 9lb weight onto your head (as if you would!) you will know that it results in your having to gaze permanently at your feet!

The strange thing with these binoculars is that one cannot actually *see* one's feet—or anything else for that matter. I am told the reason for this is that they have infra-red lenses. My husband hopes now to use them for his "anti-crash-on-motorways-in-fog" device but initially they were bought for seeing reindeer in the dark in Lapland! Curiouser and curiouser!

When we were in Germany, my husband discovered a "wonderful" electronics shop in Dusseldorf where one could buy all manner of switches, knobs, resistors, capacitors and the like. He and some other enthusiasts all left for Dusseldorf one Saturday morning at 7 a.m.—to be there when the shop opened.

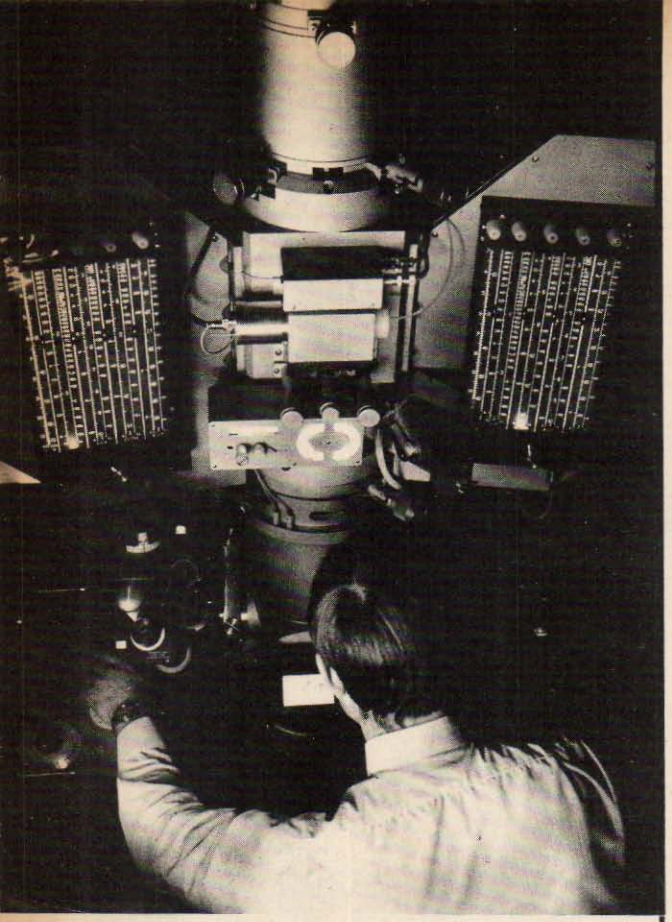My biggest agony is to be dragged round the electronics shops up and down the Tottenham Court Road (apologies to any advertisers!) Oh I know I *could* go shopping on my own in Oxford Street, but I know too that my husband would *never* meet me at the given time or place later. In fact, I very much doubt whether I would ever see him again. ★





# EMMA

## ANALYTICAL ELECTRON MICROSCOPE

A GREAT deal that has been written and said about electron microscopes may tend to be glamourised by their ability to show clear pictures of minute particles beyond the scope of conventional optical instruments.

Although the same can be said about the latest instrument, developed jointly by scientists from A.E.I. and Tube Investments Research Laboratories near Cambridge, it is now possible for the operator to correlate the results precisely with information on elemental composition. This information can be obtained from a much smaller area than has been achieved before, even with separate instruments.

In the new instrument, called "EMMA-4", thin film samples can be electron-optically magnified up to 160,000 times, with a resolution of about 10Å. For the first time, they can be simultaneously probed with an electron beam focused down to about 1,000Å in diameter (about four millionths of an inch) which is over ten times smaller than is possible in the normal electron microscope.

This permits both x-ray spectrometric analysis to identify the elements present, and the production of an electron diffraction pattern characteristics of the crystal structure and orientation, from the same very small selected area.


An important characteristic of any instrument designed to perform these functions is ease of operation; the operator must be able to select the facility he requires in a matter of seconds. Only then can the operation of the machine be truly problem-oriented.

It frequently arises, for example, that the classification of a field of particles into several different types requires repeated correlation between position and chemical analysis, with occasional checks on the type of crystal structure. Or again, in a tissue section, details of cell structure may be recognised only by their thin-section morphology, and the chemical analysis of any one feature must be correlated with its position within the cell.

For this reason, particular attention has been paid to the control layout; all controls are grouped on one console and the instrument can be switched very quickly from one mode of operation to another, and all necessary adjustments made from the operating position.

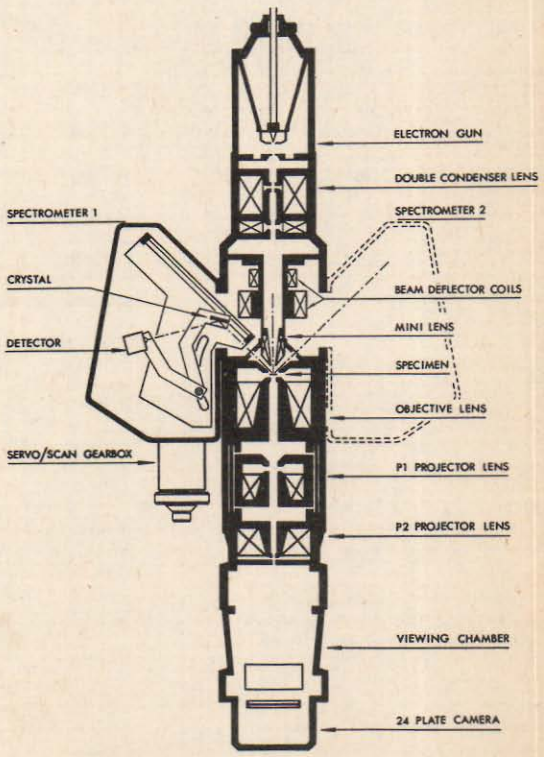
### HISTORY AND DEVELOPMENT

The ideas which have culminated in the production of EMMA-4 arose out of earlier work, whereby the first scanning microanalyser was produced. In this instrument, a finely focused electron beam was scanned over a



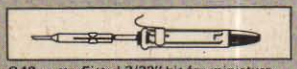
***Simplified section of EMMA-4. The transmission electron image is viewed on a screen at the bottom of the column. X-rays from the specimen are analysed by the crystal spectrometers. Note how the small size of the mini-lens leaves a clear exit path for X-rays from the specimen***




G 18 watts. Fitted 3/32" bit for miniature work on production lines. Interchangeable spare bits, 1/8", 3/16" and 1/4" available. For 240, 220 or 110 volts. 32/6.



E20 watts. Fitted with 1/4" bit. Interchangeable spare bits 3/32", 1/8", 3/16" available. For 240, 220, 110 volts. From 35/-




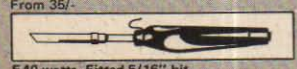ES25 watts. Fitted with 1/8" bit. Interchangeable bits 3/32", 3/16" and 1/4" available. Ideal for high speed production lines. For 240, 220, 110, 24 or 12 volts. From 35/-



F40 watts. Fitted 5/16" bit. Interchangeable bits 1/4", 3/16", 1/8", 3/32" available. Very high temperature iron. For 240, 220, 110, 24 or 20 volts. From 42/6
Spare bits and elements for all models and voltages immediately available from stock.

**Complete precision soldering kit**

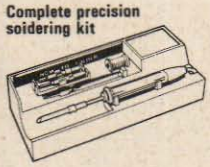

PLUS 36-page booklet on "How-to-Solder"—a mine of information for amateur and professional.

This kit—in a rigid plastic "tool-box" — contains

- Model CN 15 watts miniature iron, fitted 1/8" bit. Interchangeable spare bits. 3/32". 1/4".
- Reel of resin-cored solder
- Felt cleaning pad
- Stand for soldering iron

From Electrical and Radio Shops or send cash to Antex. **49/6**




**Model CN 240/2**
**15 watts - 240 volts**
Fitted with nickel plated bit (3/32") and in handy transparent pack. From Electrical and Radio Shops or send cash to Antex. **31/-**

A·N·T·E·X

PRECISION MINIATURE SOLDERING IRONS

Antex, Mayflower House, Plymouth, Devon.
Telephone: Plymouth 67377/8.
Telex: 45296. Giro No. 2581000.

☐ Please send me the Antex colour catalogue

☐ Please send me the following irons

Quantity Model Bit Size Volts Price

..... ..... ..... ..... .....

..... ..... ..... ..... .....

..... ..... ..... ..... .....

I enclose cheque/P.O./cash value

.....

NAME .....

ADDRESS .....

..... P.E.8

# VARIABLE VOLTAGE TRANSFORMERS


## LIGHT SENSITIVE SWITCH



Kit of parts, including ORP12 Cadmium Sulphide Photocell, Relay, Transistor and Circuit, etc., 6-12 volt D.C. op. price **25/-** plus 2/6 P. & P. ORP 12 including circuit, **12/6** each, Post Paid.

**A.C. MAINS MODEL.** Incorporates Mains Transformer, Rectifier and special relay with 2×5 amp mains c/o contacts. Price inc. circuit **47/6** plus 2/6 P. & P.

## LIGHT SOURCE AND PHOTO CELL MOUNTING

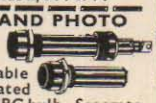

Precision engineered light source with adjustable lens assembly and ventilated lamp housing, to take MBC bulb. Separate photo cell mounting assembly for ORP. 12 or similar cell. Both units are single hole fixing. Price per pair **£2.15.0.** P. & P. 3/6.

## UNISELECTOR SWITCHES

*NEW*



**4 Bank 25 Way** 24V d.c. operation **£5.17.6,** P. & P. 2/6.
**6 Bank 25 Way** 24V d.c. **£6.10.0,** p.p. 2/6.
**8 Bank 25 Way** 24V d.c. operation. **£7.12.6** plus 4/6 P. & P.

## RELAYS New SIEMENS, PLESSEY, etc. miniature relays at COMPETITIVE PRICES

| Coil Ω | Working d.c. Volts | Contacts | | Price |
|---|---|---|---|---|
| 52 | 6–9 | 6M | | 12/6 |
| 170 | 9–12 | 4 c/o H.D. | | 14/6 |
| 170 | 9–12 | 3c/o +1 H.D. c/o | | 12/6 |
| 230 | 6–12 | 2 c/o | | 12/6 |
| 280 | 6–12 | 2 c/o | I.B. | 14/6 |
| 700 | 12–24 | 2 c/o | I.B. | 12/6 |
| 700 | 16–24 | 4 c/o | I.B. | 15/6 |
| 700 | 16–24 | 4M 2B | I.B. | 12/6 |
| 1250 | 36–45 | 6M | | 12/6 |
| 2500 | 36–45 | 6M | | 12/6 |
| 5800 | 80–85 | 4 c/o | | 12/6 |
| 9000 | 40–70 | 2 c/o | I.B. | 10/– |

H.D. Heavy Duty. POST PAID
I.B. = Including Base

### MINIATURE RELAYS

9–12V d.c. 2 c/o 500 M.A. contacts. Size 1 × ½ × ½in. Price **11/6** post paid.
24–36V d.c. 2 c/o 500 M.A. contacts. 3,200 ohm coil. Size 1 × ⅝ × 1⅛in. **8/6.** Post paid.

## 230 VOLT AC RELAY LONDEX 4 c/o


3 amp contacts. **18/6** inc. base, post paid.

## 18–24V. D.C. RELAY



2 c/o 3A contacts 400Ω coil. **NEW 9/6.** P. & P. 1/6 or **3 for 30/–** post paid.
**TYPE A.G.C.** 1M 1B 12V A.C. operation 3A contacts. **NEW 9/6** plus 1/6 P. & P. or **3 for 30/–,** post paid.
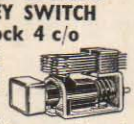
## T.M.C ILLUMINATED LOCKING PUSH BUTTON KEY SWITCH No. S.525594 Lock 4 c/o



Complete with mounting bracket, push knob and lenses (green, amber, red or clear—state colour preference).
Price **14/6** each excluding bulb, post paid. Discount for quantities of 200 and over.

## RING TRANSFORMER

*Functional Versatile Educational*



This multi-purpose Auto Transformer, with large centre aperture, can be used as a Double wound current Transformer, Auto Transformer, H.T. or L.T. Transformer, by simply hand winding the required number of turns through the centre opening. E.g., using the RT 100VA Model the output could be wound to give 8V at 12½A, 4V at 25A, 2V at 50A, etc.
Price: **RT 100VA** 3·18 turns per volt, **£2.5.0** plus 3/6, P. & P. **RT 300VA** 2·27 turns per volt, **£4.4.0** plus 5/6 P. & P. **RT 1kVA** 1·82 turns per volt, **£6.10.0** plus 6/6 P. & P. **RT 2kVA** 1·5 turns per volt, **£10.10.0** plus 9/6 P. & P. **RT 3kVA** 1·5 turns per volt, **£14.0.0** plus 9/6 P. & P.

**INPUT 230/240v. A.C. 50/60— OUTPUT VARIABLE 0-260v.**



**8 AMP**



**½ AMP**

**BRAND NEW**
**Keenest prices in the country. All Types (and Spares) from ½ to 50 amp. from stock.**

**SHROUDED TYPE**
**1 amp,** £5. 10. 0. **2.5 amps,** £6. 15. 0. **5 amps,** £9. 15. 0. **8 amps,** £14. 10. 0. **10 amps,** £18. 10. 0. **12 amps,** £21. 0. 0. **15 amps,** £25. 0. 0. **20 amps,** £37. 0. 0. **37.5 amps,** £72. 0. 0. **50 amps,** £92. 0. 0.

**OPEN TYPE** (Panel Mounting)
½ amp, **£3.18.6.** 1 amp, **£5.10.0.** 2½ amps, **£6.12.6.**
Carriage extra on open types.

## STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250v. A.C. operation.

**EXPERIMENTERS' ECONOMY KIT**
Speed adjustable 1 to 36 Flash per sec. All electronic components including Veroboard S.C.R. Unijunction Xenon Tube and instructions **£5.5.0** plus 5/- P. & P.

**NEW INDUSTRIAL KIT**
Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. Price **9 gns.** 7/6 P. & P.

**HY-LYGHT STROBE**
This strobe has been designed and produced in response to wide public demand, for use in large rooms, halls and the photographic field, and utilizes a silica plug-in tube for longer life expectancy, printed circuit for easy assembly, also a special trigger coil and output capacitor. Speed adjustable 0-30 f.p.s. Light output approx. 4 joules. Price **£10.17.6.** P. & P. 7/6.

**7-inch POLISHED REFLECTOR**
Ideally suited for above Strobe kits. Price **10/6.** P. & P. 2/6 or Post Paid with kits.

## 100 WATT POWER RHEOSTATS (NEW)



**AVAILABLE IN THE FOLLOWING VALUES:**
**1 ohm,** 10 a.; **5 ohm,** 4.7 a.; **10 ohm,** 3 a.; **25 ohm,** 2 a.; **50 ohm,** 1.4 a; **100 ohm,** 1 a.; **250 ohm,** .7 a.; **500 ohm,** .45 a.; **1 Kohm,** 280 mA; **1·5 Kohm,** 230 mA; **2·5 Kohm,** .2 a.; **5 Kohm,** 140 mA. Diameter 3¼in. Shaft length ⅝in., dia. ¼in. All at **27/6** each. P. & P. 1/6.
**50 WATT.** 1/5/10/25/50/100/250/500/1/1·5/2·5/5 Kohm **All at 21/- each.** P. & P. 1/6.
**25 WATT.** 10/25/50/100/250/500/1/1·5/2·5 Kohm. **All at 14/6 each.** P. & P. 1/6.

**VEEDER ROOT,** 230V a.c. 50 cycle, 5-figure counter (non-resettable). **18/6,** P. & P. 1/6.



**NICKEL CAD. BATTERY OUTFIT (Ex. W.D.)**
Two metal carrying cases each containing 10 × 1·2V 7AH (12V) Batteries, also 10 × 1·2V 22AH (12V) Batteries (40 batteries in all).
One dual voltage, dual meter thyristor controlled charging unit. Designed for charging the 7AH and 22AH batteries simultaneously. Input voltage can be adjusted between 100 and 250V a.c. Built to Ministry specification. Ideal power supply for field work. Offered at fraction of makers' price. Two sets of batteries, 1 charging unit. The set **£45.** P. & P. 30/–.



**SOLID STATE INTERVAL TIMER**
24–30V D.C. operation. Stabilised unijunction Timer and S.C.R. (30V 1 amp.), encapsulated in metal core. Timing interval adjustable from a fraction of a second to several minutes by means of external resistor or pot. By adding a 24V Relay many other complex timing Functions are possible. Price: **16/6** incl. circuit. P. & P. 2/6. Suitable relay **10/-** post paid.



## MOTOROLA MAC/11 PLASTIC THYRISTOR. 400 PIV. 8 AMP

Now available **EX STOCK.** Supplied with full data and applications sheet. Price **21/-** plus 1/6 P. & P.

## RE-CHARGEABLE BUTTON CELLS



2 × 1·2V, 250 MA/HR Nickel Cad. Cells, connected to give 2·4V @ 25 milliamp/10 hour rate, complete with 200/250V A.C. charger. Fully tested and unused. Price 9/6 each plus 1/6 P. & P. or 2 units for £1 post paid.



**INSULATED TERMINALS**
Available in red, white, yellow, black, blue and green. New Price **2/–** each.

# SERVICE TRADING CO

All Mail Orders—Also Callers—Ample Parking Space
**Dept. P.E. 57 BRIDGMAN ROAD, LONDON, W.4**
**Phone 995 1560 SHOWROOM NOW OPEN CLOSED SATURDAY**

Personal callers only
**9 LITTLE NEWPORT ST.**
**LONDON, W.C.2. Tel. GER 0576**

# THE RADIO AMATEUR'S HANDBOOK 1970

by A.R.R.L.

**48/-** Postage 4/6

**COLOUR TELEVISION, PAL SYSTEM** by G. N. Patchett. **50/.** Postage 1/-.

**SERVICING WITH THE OSCILLOSCOPE,** by Gordon J. King. **28/-.** Postage 1/-.

**110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR,** by R. M. Marston. **18/-.** Postage 1/-.

**TRANSISTOR SWITCHING AND SEQUENTIAL CIRCUITS,** by John J. Sparkes. **25/-.** Postage 1/-.

**TRANSISTOR AUDIO AND RADIO CIRCUITS,** by Mullard. **30/-.** Postage 1/-.

**SOLID STATE HOBBY CIRCUITS MANUAL,** by RCA. **17/6.** Postage 1/6


**BASIC THEORY AND APPLICATION OF TRANSISTORS. 17/-.** Postage 1/6.

**RADIO HANDBOOK,** by William I. Orr. **105/-.** Postage 4/6.

# THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books
**19-21 PRAED STREET**
**LONDON, W.2**
*Phone: PADdington 4185*
Closed Saturday 1 p.m.

# DIMMASWITCH

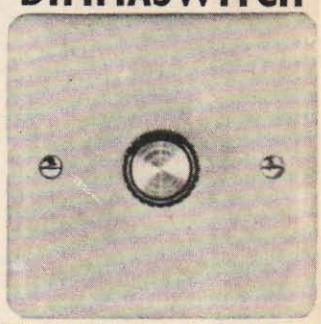

**This is a dimmer of standard size in ivory and chrome to replace modern light switches without wiring change—controls 40-600 watts, 200/250 volts at 50Hz of all lights except fluorescents**

**Two models are available with on/off switch to control from maximum to zero.**

**DS500/2 at £3 12s. 6d. with clockwise or reverse dimming, with the switch at full reverse rotation.**

**DS500/2/P at £3 18s. uses a patented switch giving on/off control at any position of dimming.**

**Both are available in D.I.Y. kit form at 10/- less. Fuse protection is available at 2/6 extra.**

*Please send C.W.O. to:*

**DEXTER & COMPANY**
**ULVER HOUSE, 19 KING STREET**
**CHESTER CH1 2AH**
**Tel.: Chester 25883**

*As supplied to H.M. Government Departments, Hospitals, Local Authorities, etc.*


solid specimen; the x-ray emission characteristic of one element present was used to produce an enlarged cathode ray tube image representing the distribution of the selected element over a chosen area. At the same time, the electrons back-scattered from the specimen could be used to present a picture comparable to that produced by an optical microscope.

This instrument proved extremely useful in the identification of local concentrations of residual elements in steel, and of non-metallic inclusions of great significance in the seamless tubemaking process.

A limitation of all instruments dealing with solid specimens is that, due to scattering of electrons within the specimen, the smallest area which can be probed at any instant is about 1$\mu$m across. At the same time, neither the electron image, nor the optical microscope with which such instruments are fitted, enables a very high magnification to be used.
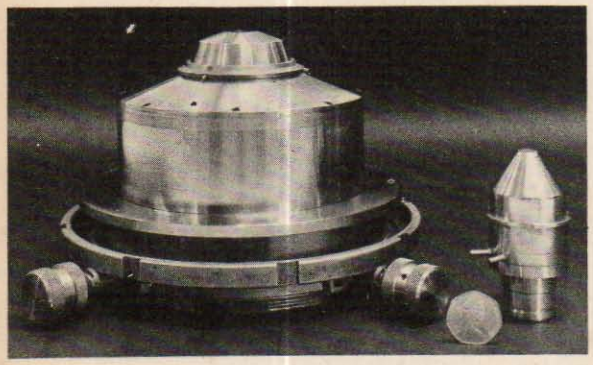
## EMMA-1

These limitations were overcome by the development of a new instrument in which a thin sample could be used; for example, a metal film, a carbon film carrying particles extracted from a bulk sample, or a thin section of biological tissue. The electrons could then be



***A conventional magnetic lens compared with the mini-lens. Elimination of the bulky and heavy iron core leads to a dramatic reduction in size and a great improvement in performance***


focused into a probe only 1,000Å in diameter, which passes straight through the specimen without appreciable sideways scattering, exciting x-rays from a region an order of magnitude smaller in diameter than is possible with a solid specimen.

Alternatively, the defocused beam could be used to illuminate a wider area of specimen. The transmitted electrons are then used to produce a magnified image on a fluorescent screen, as in a straightforward electron microscope.

This was found to be the first practical combination of electron microscope and microanalyser, and was called "EMMA-1", but was built for development of the technique itself without particular regard for convenience in use. The maximum beam energy was limited to 50keV for ease of construction.
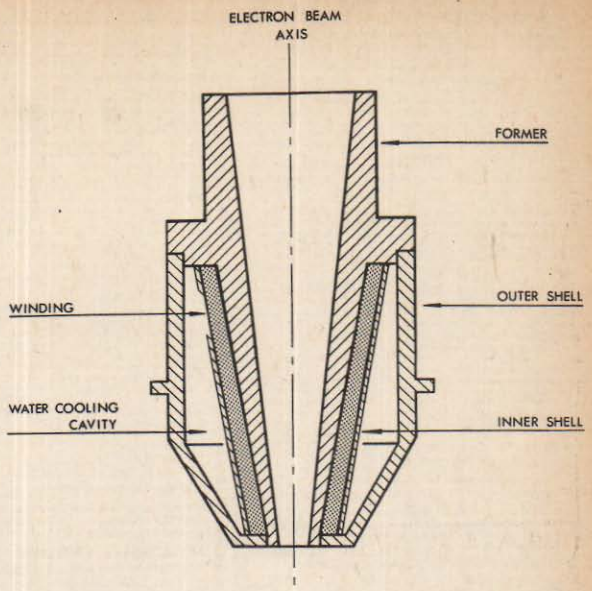
## SECOND SPECTROMETER

One early improvement was the addition of a second spectrometer, which permitted the simultaneous analysis of two elements. This was more than a time-saving addition; the ratio of the amounts present could be




***Simplified section of liquid-cooled mini-lens developed for EMMA-4. The precision winding is supported on a copper former, and there is no magnetic core of any kind. This design not only improves focusing performance but gives better access to the specimen***

measured independently of any slight instability of the specimen, since small drifts affect equally the x-ray intensity from each element.

It soon became evident, however, that the beam energy should be increased to a level similar to that of conventional electron microscopes—say 100keV, to give adequate penetration of a wide range of sample types. The main difficulty here was that this would require heavier lenses. In particular, the probe-forming lens would be a heavy and bulky item, tending to obscure the x-ray path into the spectrometer.

## MINI-LENS


It was at about this time that the Technical University of Delft showed that, if the lens windings could be formed accurately enough, no iron shield or pole-piece would be necessary. Elimination of these heavy and bulky components itself made even smaller windings possible, the result being a spectacular reduction in overall size of the lens—the now well-known "mini-lens", in fact.

It then became apparent that the new A.E.I. EM802 microscope would provide an ideal instrument in which to mount such a lens, having adequate space in the region above the specimen for this purpose, and room on the column to attach two spectrometers.

The joint development work was started, the prime aim being to add the microanalysis system to this microscope with a minimum of modification.

A special design of mini-lens was evolved by T.I. together with a new form of high-sensitivity spectrometer, while A.E.I. concentrated on the specimen stage and other aspects of the microscope. The work was completed in under two years with the emergence of the prototype "EMMA-3".

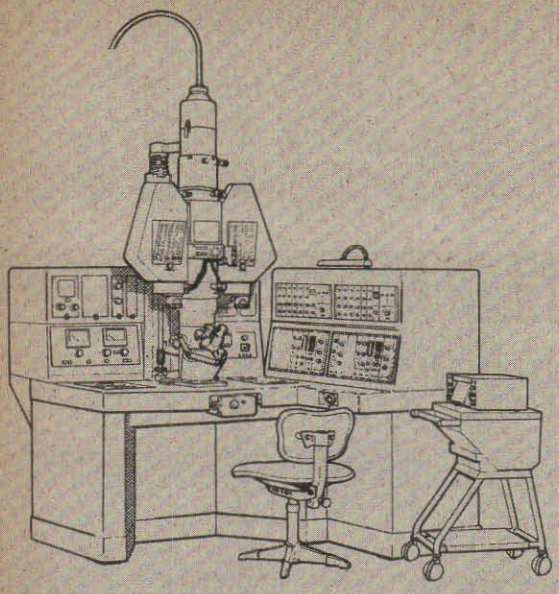The production version, "EMMA-4", differs from EMMA-3 only in having the instrument and control equipment fully integrated into a single operating console.



*Controls are conveniently grouped on the operating console in the production EMMA-4*

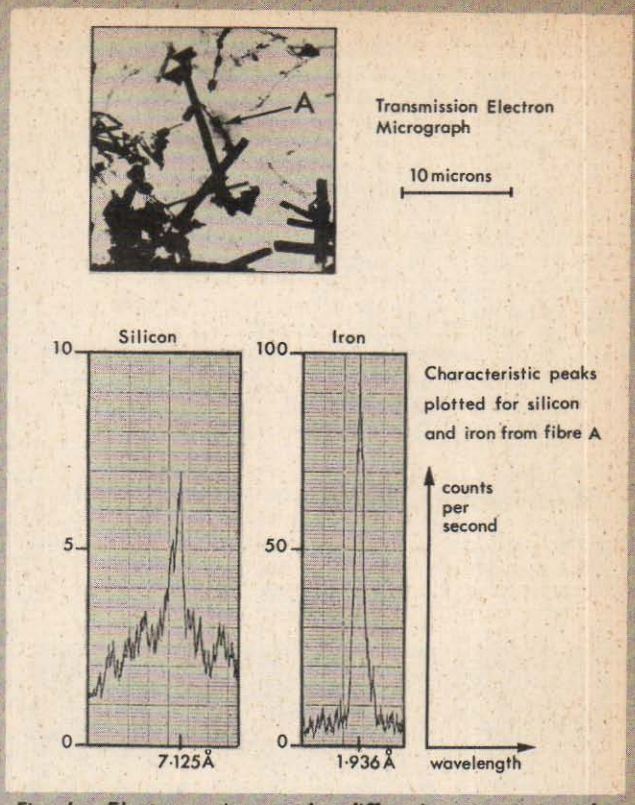



***Fig. 1. Electron micrographs diffraction pattern and spectrometer plots identifying fine particles of aluminium nitride in a tube steel***

## EMMA-4

The microscope column of "EMMA-4" is mounted in the centre of the console, the spectrometers attached on either side. Control of the spectrometers is simplified in that each one carries a tuning scale, which is set out something like that on a radio receiver. Four wavebands are selected by different crystals and each is calibrated directly in x-ray wavelength with each station marked by element name. Tuning may be carried out either by a fine manual control for accurate wavelength determinations or by a servo system, enabling any one of six preset elements to be selected by push-button. A complete spectrum may also be plotted on a chart recorder with the aid of a slow-scan motor. The instrument can analyse for all elements from atomic number 11 (sodium) to atomic number 92 (uranium).

Six specimens up to 3mm in diameter, some of which can be calibration standards for microanalysis, may be accommodated on the specimen stage. These are directly interchangeable without breaking the vacuum but when reloading is necessary, the stage may be withdrawn from the column through an airlock.

## APPLICATIONS

EMMA-4 offers unique facilities for the intensive and correlated examination of the morphology, chemical composition and crystallographic structure of extremely small specimen areas. It is expected to be useful in many fields of research where thin film examination is feasible and relevant. Obvious areas are metallurgy, where the prototype instruments have already provided valuable new information on the composition of precipitates and inclusions in steels; biology, in which it has great potential in the examination of bone and tissue sections; and generally for the analysis of particles deposited on thin substrates.

## DETECTING SURFACE CRACKS ON STEEL TUBING

During the final stages in the manufacture of steel tubing, the base material is subjected to very severe mechanical working at elevated temperatures. This can result in the surface of the tubes breaking up and the incidence of such defects can be related to the aluminium content of the material.

It is, therefore, important to find where the aluminium is located and since the distribution turns out to be on a very fine scale, the electron microscope is one of the few research tools which can be usefully employed. With the facilities afforded by EMMA-4 it is possible to identify one site for aluminium as a precipitate of aluminium nitride. The aluminium content of the particles is demonstrated by x-ray microanalysis and the specific compound confirmed by electron diffraction.

Fig. 1 illustrates the results of a study of an extraction made from a tube showing surface defects. The precipitates are supported on a carbon film in the conventional manner for electron microscopy. Particle A is identified as aluminium nitride and particle B, and its surrounding neighbours, as pearlite ($Fe_3C$)—a normal precipitate in the material. The smaller of these particles (A) measures only 1,500Å across and is therefore well below the detection limit of the normal electron probe microanalyser (about 1 micron).

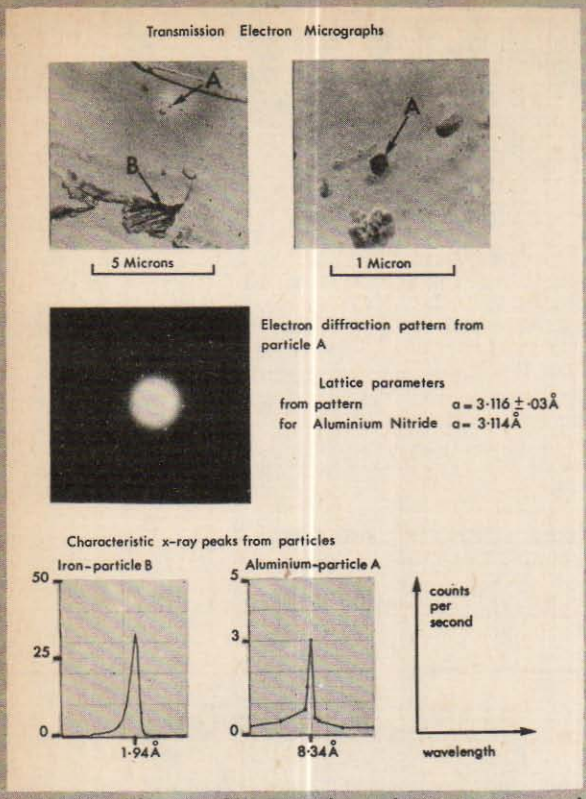



***Fig. 2. Electron Micrographs and spectrometer plots showing presence of AMOSITE asbestos fibres in human lung tissue***

## ASBESTOSIS IN HUMAN LUNG

An example of the application of the EMMA-4 technique in medical research concerns the study of asbestos fibres extracted from human lungs.

Recent work in several laboratories has demonstrated the danger of inhaling such fibres, and has shown that the ill-effects may not manifest themselves until many years after the inhalation. The problem therefore arises of establishing to which group of the asbestos materials particular extracted fibres belong, in order to be able to relate this to the lung damage and also to trace the source.

Fig. 2 illustrates the type of results obtained with the new instrument. The transmission image shows the fibres on this sample, a lung tissue section, to be as thin as about 1,000Å, often with "trains" of growth along them (top centre of the image). Surface and internal detail are also made visible.

The direct spectrometer output in the form of peaks plotted for silicon and iron (K) radiations from the fibre A is also shown in this illustration. Simply by measuring fibre composition in the form of element ratios from such peaks it is possible to identify these particular fibres as AMOSITE asbestos. Further confirmation can be obtained by electron diffraction, if required.

The essence of the problem posed by this particular specimen, i.e. the correlation of chemical, morphological and crystallographical information on a submicron scale is, of course, very general and it is for this reason that the scope for application of the new instrument is likely to be very widespread. ★


# SEPTEMBER

*Issue-On Sale....*

**AUGUST 14**




# HUMIDISTAT

**A simple, effective system of sensing and controlling humidity levels based on the psychrometer, and using two negative temperature coefficient thermistors to sense humidity. The Humidistat will prove extremely useful in areas where humidity has to be increased or decreased and it will operate for long periods without attention.**

# 'VALSTAB'

**POWER SUPPLY**

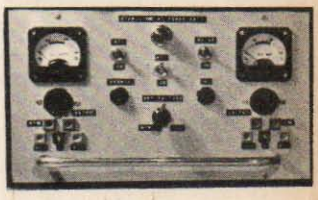


**To cater for existing valve circuits (including television) the "VALSTAB" can provide most of the requirements of experimental or temporary replacement power supplies. It has voltage stabilisation for variable loads and mains voltage. Outputs are 175-325 volts at 100mA; −150 volts at 10mA; 6·3 volts at 4A centre tapped.**

**The VALSTAB appears next month; look out for the matching "TRANSTAB" later.**

*Order Yours NOW*

PRACTICAL ELECTRONICS

# PROJECT

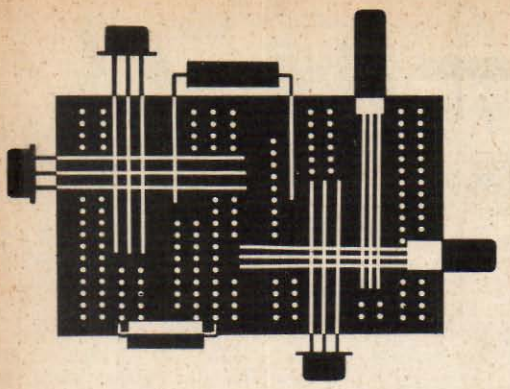

***THE new series of practical subjects for beginners to build commences in this issue. Subsequent articles in the series will be easily identified under the "Beginners" heading in the Contents and by the symbol which will appear at the beginning of each article.***

THE projects are shown built up on a "breadboard" system for four main reasons.

1. Whilst the initial cost of the systems may be high, this could be more than offset by the fact that components can be easily removed, re-positioned or used again in a more permanent construction.

2. The circuit can be assembled very quickly or expanded by adding extra functions later.

3. The actual layout of the components can follow a similar layout to that in the circuit diagram.

4. Soldering is only needed for connecting wires to large components, such as switches and potentiometers; inter-component wiring is already provided.

## USING T-DEC

The "breadboard" system used is called T-Dec. It is a manufactured plastics base plate with a matrix of numbered holes. Certain combinations of interconnection are provided by spring strips underneath the holes. These are snown in Fig. 1a corresponding to the raised lines moulded on to the surface of the board itself.

T-Dec is divided into two sections which are electrically isolated, enabling two or more separate circuits to be built on to the same board. If required any part of one circuit can be connected to any part of the other circuit by using single strand copper link wires.

Some components have very thin connecting wires; these should be helped into the holes by holding the wire with a pair of long-nose pliers.

Transistor and diode wires can be inserted directly into the holes if spacing permits. It may be necessary to open up the spacing of these wires; in which case, careful bending with pliers at least $\frac{1}{8}$in from the encapsulation can do this without damaging the transistor or diode seal. Alternatively, special adaptor plugs supplied by the T-Dec manufacturers can be used to mount these components.

The component wires should be at least $\frac{3}{8}$in and preferably $\frac{5}{8}$in long to ensure satisfactory connection. Longer wires will of course, make the components more versatile in their use. It is never good practice to trim these wires short if they are to be used again.

Whole systems of breadboarding can be built by fitting two or more boards together by the dovetail tongues and grooves around the sides. Small panels for switches, potentiometers, lamps and so on are provided and are easily fitted into the slots on the edge of the boards.

## HOLE IDENTIFICATION

Coming now to the numbering of holes for identification you will notice that the T-Dec has two blocks side by side with letter references A to H on both.

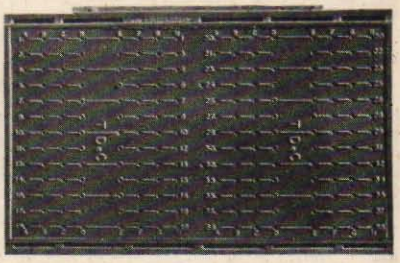


*Fig. 1a. The T-Dec breadboard. Notice the connections between holes are shown as raised lines*

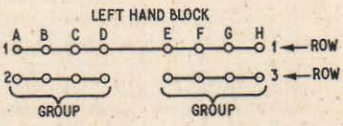



*Fig. 1b. How the T-Dec holes are identified. Only the first two rows are shown here*

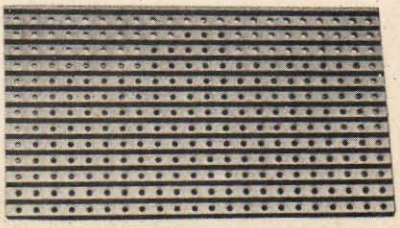


*Fig. 2a. Underside view of Veroboard showing the copper strips*

# BUILDING— for BEGINNERS

The numbers run in sequence for each row or group of holes in a row (see Fig. 1b). It is important not to be confused with these since, in each alternate row per block, there are two groups of four holes which are numbered separately.

In the other rows connection is already indicated between the two groups; these cannot be separated. If insufficient holes are available for a particular junction of components, a link wire can be carried to another vacant group elsewhere on the board.

## ALTERNATIVE CONSTRUCTION

Some readers may prefer to use alternative construction systems, perhaps in a more permanent form. These will probably require the use of a soldering iron and, although component recovery is possible, it is not as easy as with T-Dec.

Suggestions for some construction systems are given here, using mainly some form of s.r.b.p. sheet machined or treated by proprietary manufacturers.

In order to simplify translation from T-Dec to these other forms, the same basic layout is assumed and connection code numbers correspond. If the board is too large, it can be trimmed before commencement to the size required, but the basic layout remains the same.

## COPPER STRIP WIRING BOARD

Veroboard is the first of the alternative examples here because translation is very straightforward. Fig. 2a shows this board with the copper strips on the underside. To keep the same layout appearance the holes are numbered in sequence so that the top surface is that without the copper.

If the copper strips are cut to conform with the T-Dec

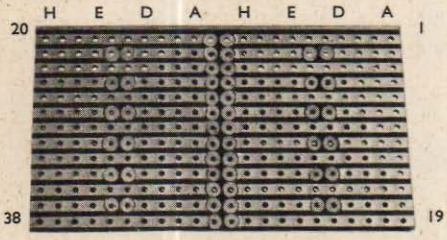



*Fig. 2b. Veroboard with the strips cut to show the T-Dec wiring pattern*

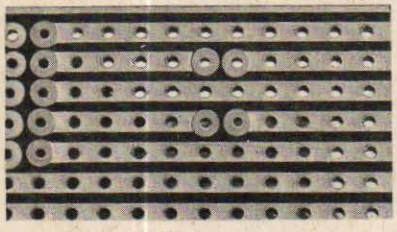


*Fig. 3a. Veroboard strips prepared for the first project*

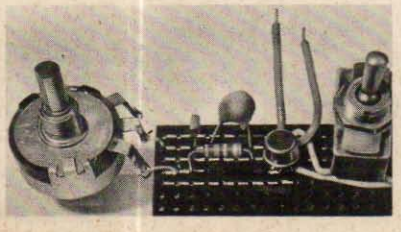


*Fig. 3b. The finished metronome project*

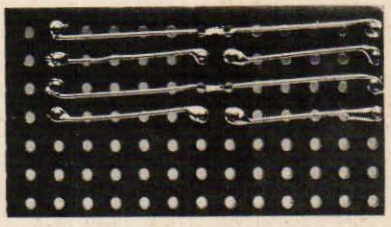


*Fig. 4a. Plain perforated s.r.b.p. sheet with copper wire connections and soldering pins*

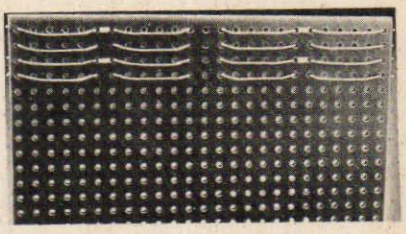


*Fig. 4b. Plain s.r.b.p. with the connecting wire hooked through the end holes in the rows*

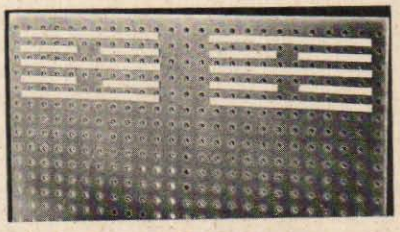


*Fig. 5. Cir-kit adhesive copper strips fixed between rows of holes on plain perforated board*

layout the appearance would be as shown in Fig. 2b.

The strips can be cut with a special spot-face cutter, a $\frac{1}{8}$in drill, or a sharp knife.

Before cutting any strips, study the project circuit layout in the practical article to see how many breaks are really necessary. If only one half of the T-Dec is used none of the centre breaks will be necessary. However, if at a later stage you decide to assemble another circuit on the same board, the copper around the centre columns of holes, between column H on the left and A on the right, will need to be cut. Before doing so, check to see if any links are needed between left and right, in which case leave the appropriate strips uncut.

Next look at the project layout to see if any connections are needed between column D and column E. Having established those required cut all the other copper strips between D and E to form the groups of four holes (Fig. 3a).

Now the columns and rows of holes can be numbered exactly as for T-Dec. You can do this by laying the board on a sheet of paper and marking through each required hole in the board with a pencil. Remember that the T-Dec numbering follows that for Veroboard that has the copper side face down.

Carry out the assembly and soldering making sure that no solder bridges two or more adjacent strips. Good clean soldering is the keynote to success; dry joints will not do. Fig. 3b shows the finished project.

## PERFORATED S.R.B.P. AND WIRE

The next system is simple and follows the same lines as with Veroboard, except that plain perforated board has no copper face. All connections are carried out using soldering pins and tinned copper wire; see Fig. 4a. However, do not fit wires that are unlikely to be used; this is a waste of materials and effort.

The pins can be dispensed with if the copper wire is hooked through the end holes of each row and secured with solder. An example of a typical layout is shown in Fig. 4b.

## STICK ON WIRING

The third system is a development of the previous one except that the wires are replaced by self-adhesive copper strips called "Cir-kit". The method is otherwise exactly the same (Fig. 5). The narrow strip will just fit between adjacent rows of holes on plain perforated board.


## PRINTED CIRCUIT

There is no reason why printed circuit board should not be used. This will require more patience by following the instructions given with the printed circuit kit. Not all kits carry instructions, so if you are unfamiliar with printed circuit techniques try and obtain a kit that has.

It will probably be necessary to sketch out a layout of the copper pattern corresponding to the project actually being built. It is recommended that an experienced friend helps you with this as mistakes can be expensive.

This short introductory article is not intended to provide comprehensive details of using these alternative methods. Full details and instructions can be obtained from manufacturers of these and other proprietary items which are advertised in this magazine.

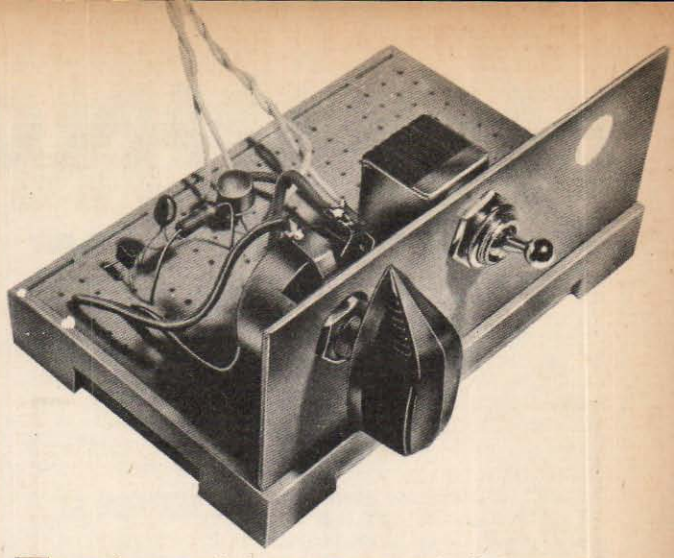The project which follows can be built very easily using one of the methods described here. Future projects in the same series are to be dealt with in a similar manner.



To study a musical instrument, one of the most important requirements is strict attention to playing speed. To assist in the correct interpretation of the music's tempo the composer conveniently heads his composition with a rough guide to the rate at which it should be played like *Andante* or *Allegro*, this usually being followed by the number of crotchets, quavers, etc. that should be played per minute.

Whilst the accomplished musician has little difficulty in interpreting these tempo marks, the beginner does need some sort of aid to assist in establishing a sense of time.

More than a hundred years ago Maelzel provided such an aid in his invention of the mechanical metronome which produced loud ticks with the movement of a weighted pendulum. With the simple electronic metronome to be described, we can reproduce these ticks just as effectively without the labour of winding up springs.

## RELAXATION OSCILLATOR

To simulate the sound of its mechanical counterpart the circuit of Fig. 1 was designed to produce asymmetric pulses of short width and rapid rise and fall times. The pulse generated across the loudspeaker LS1 is shown in this diagram, and it ensures a very rapid cone movement.

The frequency range extends from 40 to 220 beats per minute, which is adequate.

As this little device is very precise in its counting, it can also be used as an audible "darkroom" timer when set to 60 beats/minute.


The circuit itself is a simple relaxation oscillator where two complementary *npn* and *pnp* transistors are made to switch on and off at a rate determined by the resistance chain VR1, R1 and capacitor C1. With S1 closed, C1 charges until it reaches about 650mV when TR1 is switched on and immediately discharges the capacitor.

The current pulse produced by TR1 in turn switches on TR2 with the result that almost the whole of the supply voltage is made to appear across the loudspeaker.

The actual discharge time of the capacitor depends on the base-emitter impedance of TR1, the loudspeaker impedance and the output impedance of TR2 which collectively account for the exponential hump on the output pulse waveform.

With the completion of the pulse the capacitor again charges to the conduction potential of TR1, when the pulse cycle starts again.

# METRONOME

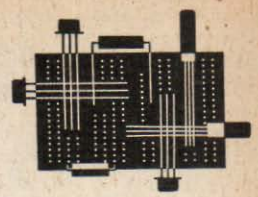

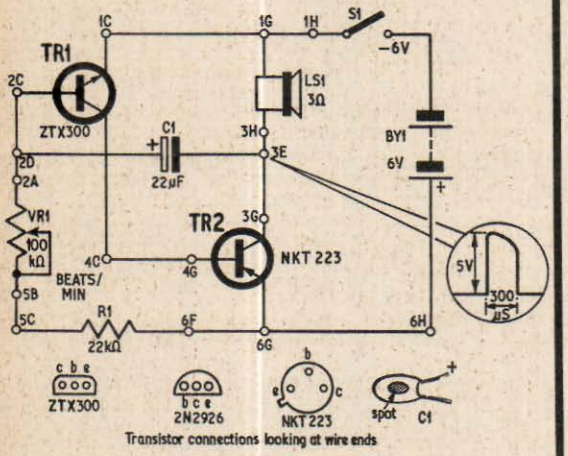



*Fig. 1. Circuit diagram of the metronome showing the T-Dec hole connections, transistor wire identification and output waveform*

## LOW LEAKAGE

In the application of this unit timing precision is important. The simple factor most likely to give trouble in this aspect is leakage current. The choice of a silicon transistor for TR1 and a tantalum electrolytic capacitor for C1 virtually eliminates the problem.

In the choice of speaker it will be found that sound output is a function of cone diameter. In practice, a 5in speaker proved very satisfactory.

## CONSTRUCTION

Construction of the unit merely involves plugging the components into the T-Dec as shown in the photograph. For the holes employed refer to Fig. 1, which shows the hole numbers for each junction.

If it is intended to make a permanent unit of this, the wiring configuration will readily translate to any of the board constructional methods outlined in the introductory article.

If such construction is undertaken the potentiometer setting must be calibrated in terms of the number of beats produced per minute. Using a wrist watch with seconds sweep or preferably, a stop watch, the potentiometer should be advanced at 20 beat intervals. These positions can be recorded on a piece of white card. A pointer knob attached to the potentiometer shaft will simplify this operation.

## COMPONENTS . . .

**Resistors**
R1 22kΩ 10% ½ watt carbon

**Potentiometers**
VR1 100kΩ linear carbon

**Capacitor**
C1 22μF tantalum elect. 16V

**Transistors**
TR1 ZTX300 (Ferranti) or 2N2926 orange spot
TR2 NKT223 (Newmarket) or GET102 (Mullard)

**Switch**
S1 on/off toggle switch

**Loudspeaker**
LS1 3Ω 5in permanent magnet moving coil unit

**Battery**
BY1 6V type 996

**Miscellaneous**
T-Dec.
Single strand connecting wire
Battery connectors or clips

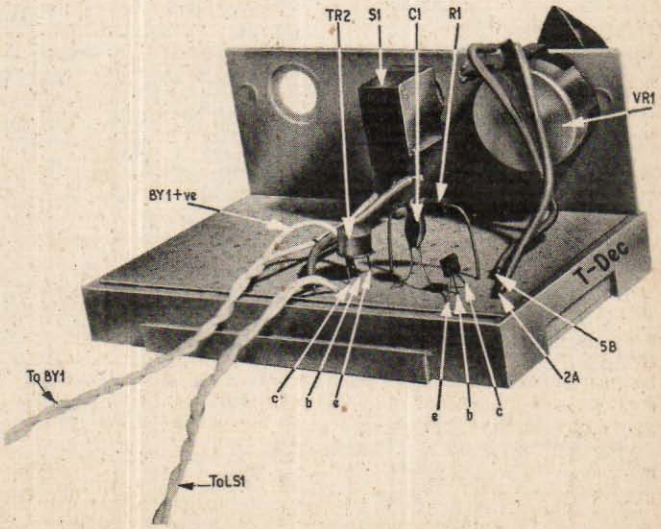



*Fig. 2. The layout of components on T-Dec. Make sure the battery is correctly connected*



# SPACEWATCH

By Frank W. Hyde

## APOLLO 13 RESULTS

The results of the special investigation into the results of the *Apollo 13* troubles have been released by the chairman of the committee, Edgar M. Cortright. The explosion was caused by the failure of two thermal switches in the system which controlled the heater inside the oxygen tank. The failure allowed the wires inside the tank to heat up to a high temperature, the insulations burned off and the spark resulting from the short circuit caused the explosion.

The cause of the failure of the switches is thought to be the detanking sequence which is part of the countdown procedure. This procedure does in fact place a much more severe strain on the system than the actual spaceflight. The reason for this is that during the checking sequence the heaters are on for a much longer period and at a higher current level than when in flight.

The necessary modifications are being carried out and at the time of writing the next launch is not likely to take place before December 3 this year.

## MARINER 7 PHOTOGRAPHS PHOBOS

Mars has two satellites, Phobos and Diemos, and one of these satellites has been successfully photographed by *Mariner 7*. Both are very small and near to the planet surface, Phobos being some 3,700 miles from the surface and Diemos about 12,500 miles.

The Mariner spacecraft was about 82,000 miles from Phobos when the picture was taken. The satellite was near one of the dark areas on Mars known as Syrtis Major, and appeared as a dark spot on the lighter background of the Aeria region.

Analysis of the photograph was carried out by Dr Bradford A. Smith of New Mexico State University, and he deduced that the satellite was oval shaped with a diameter of 13·75 miles in the plane of its orbit and 11·25 miles diameter across its poles. A significant result of the analysis is that the "albedo" (the ability to reflect light) has proved to be very low, the lowest in fact of any satellite or asteroid in the solar system.

The darkness of the satellite appears to be due to its small size and dust from the surface could easily escape due to the low gravity. In fact it is so low, that should one of the suggestions that it could be used as a space station be implemented, the personnel would have to be careful not to jump with too much enthusiasm or they might go into orbit. The escape velocity is 12 metres a second.

Since the satellite is elongated it is unlikely that it came into being by accretion and it is possible that it is a captured asteroid.

## GERMAN SATELLITE

The contract for the construction and systems management of *Aeros*, the second German satellite, has been awarded to the Dornier-System GmbH. *Aeros* is the successor to the recently launched *Azur* and is devoted to the study of the physical processes in the upper layers of the atmosphere. There will be five experiments, four German and one American and it is expected that it will be put into orbit in the summer of 1972, from the Vandenberg test range in California using an American *Scout* rocket.

The instruments to be carried for the German experiments are a mass spectrometer for the study of the atmosphere's chemical composition. This is done by measuring the number density of ions and neutral particles. An impedance probe will determine electron density in the ionosphere. A retarding potential analyser will measure the energy distribution of electrons and ions. An ultraviolet spectrometer will measure the flux and spectral distribution of the far ultraviolet radiation of the Sun.

The American experiment will measure the nitrogen present in the various layers of the upper atmosphere and the overall density of the neutral particles.

As the results of the last experiment are required for a NASA satellite due to be launched in 1973, it will be essential that the construction programme and launch date be on time. The planned orbit is a specially selected one and the satellite will be placed in a polar orbit with a perigee of 235km and an initial apogee of 1,000km. The friction of the atmosphere at these altitudes will cause the satellite to fall towards the Earth.

After 105 days the apogee will have been reduced to 580km; at this point it will be raised again by 200km using a hydrazine chemical rocket. The reason for doing this is to collect data from comparable altitudes at different times of the year.

After a period of six months at this new altitude the satellite will then enter the denser parts of the atmosphere and finally burn up. Measurements during the final phase of its life are expected to be of considerable interest.

After each measuring orbit there will be one or two idle orbits to allow the batteries time to be recharged and the stored data transmitted back to Earth. The satellite is an airtight cylinder with one flat and one conical end.

## *NIMBUS D* SATELLITE

*Nimbus D* was launched from the Western test range in California by a Thorad Agena D. The butterfly shaped satellite weighs 620kg, and is in a circular near polar orbit 1,110km above the Earth and orbits in 107·3 minutes.

The British experiment was developed by GEC-Elliot for Oxford and Reading Universities and uses a very sensitive selective chopper radiometer which can detect radiation at low levels over six discrete bands. The measurements will give the first complete continuous picture of the 15 micron radiation. The temperature field in the region 25–50km above the surface and the conditions below 25km will be of considerable importance to forecasting in the future.

GEC-Elliot are now working on *Nimbus E* due to be launched in late 1972. In this satellite the number of channels will be increased to 16. The Meterological Office will check the data against Radio Sonde measurements and provide daily charts for the Northern Hemisphere with information relating to several levels.



***An engineer uses a microscope to examine and find the cause of discolouration to the Surveyor 3 television camera landed on the moon in April 1967, and returned to Earth by the Apollo 12 astronauts last November.***

***The scientists expect the study to provide a guide in selecting materials and components for future space exploration.***


# DISCRETE



**T-DeC**
Primarily for discrete components but with IC capability.

# or

# IC's

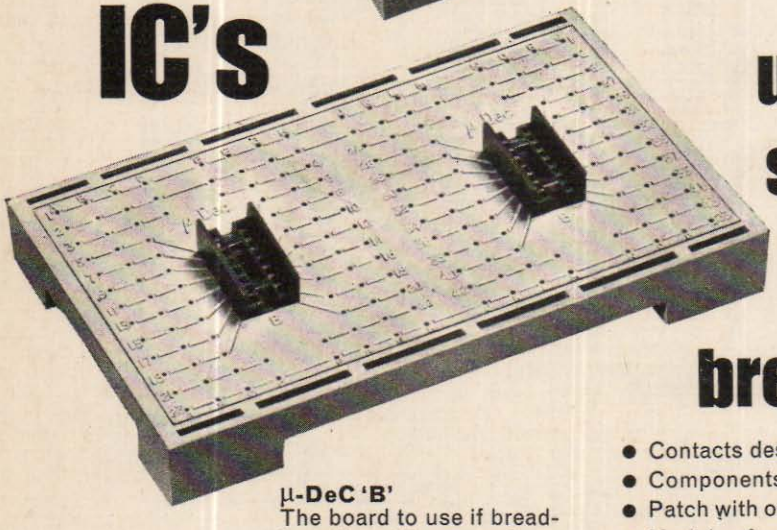

**μ-DeC 'B'**
The board to use if breadboarding with one package type.
If breadboarding with a variety of packages use μ-DeC 'A' general purpose breadboards.

# use DeC solderless modular breadboards

- Contacts designed for maximum life.
- Components inserted directly into board.
- Patch with ordinary wire.
- Modular, for economy and maximum use.
- Modules link to form any size of breadboarding.
- Slots accommodate heat sinks and control panels.
- Control panel supplied with every DeC.
- DeC's may be temperature cycled.
- Contacts available in a range of surface finishes.
- All contacts numbered for reference.
- All connection points shown on surface of DeC.

**S.D.C. ELECTRONICS (SALES) LTD.**

**34 Arkwright, Astmoor Industrial Estate, Runcorn, Cheshire. Tel: Runcorn 5041.**

# STEPHENS

ELECTRONICS
P.O. BOX 26
AYLESBURY, BUCKS.

**SEND S.A.E. FOR LISTS**
**GUARANTEE**
**Satisfaction or money refunded.**

## VALVES

| | | | | | | | |
|---|---|---|---|---|---|---|---|
| AZ31 | 9/6 | EF184 | 11/3 | PL38 | 18/- | 6U4 | 15/- |
| DAF91 | 8/3 | EH90 | 10/3 | PL81 | 10/3 | 6AT6 | 9/9 |
| DAF96 | 8/3 | EL34 | 9/9 | PL81A | 12/6 | 6U6A | 15/6 |
| DF91 | 9/- | EL41 | 10/- | PL82 | 7/3 | 6AV6 | 6/6 |
| DF96 | 9/- | EL81 | 9/6 | PL83 | 10/3 | 6BA6 | 9/6 |
| DK91 | 11/6 | EL84 | 7/9 | PL84 | 8/3 | 6BE6 | 12/- |
| DK96 | 11/6 | EL95 | 9/- | PL500 | 16/6 | 6BR7 | 15/- |
| DL92 | 7/6 | EM81 | 11/6 | PL504 | 17/- | 6BR8 | 19/- |
| DL94 | 7/6 | EM84/7 | 12/9 | PL505 | 29/- | 6BW6 | 16/6 |
| DL96 | 9/3 | EY51 | 7/6 | PL508 | 20/- | 6BW7 | 13/9 |
| DY86/7 | 8/- | EY86/7 | 7/9 | PL509 | 30/9 | 6CD6G | 28/- |
| DY802 | 8/6 | EX40/1 | 7/6 | PL802 | 17/3 | 6V6G | 8/- |
| EABC80 | 10/6 | EZ80 | 6/6 | PL805 | 17/3 | 6X4 | 7/6 |
| EBC33 | 11/- | EZ81 | 5/9 | PY32 | 10/- | 6X5 | 9/6 |
| EBC41 | 9/6 | GY501 | 14/6 | PY33 | 10/9 | 12AU6 | 15/- |
| EBC81 | 6/6 | GZ30 | 9/6 | PY81 | 8/3 | 12BA6 | 9/6 |
| EBC90 | 9/6 | GZ32/4 | 11/9 | PY800 | 8/3 | 12BE6 | 12/- |
| EBF80 | 8/- | GZ33/7 | 16/3 | PY801 | 8/3 | 12BH7 | 14/- |
| EBF83 | 8/- | KT66 | 25/6 | PY82 | 7/- | 35W4 | 9/6 |
| EBF89 | 8/- | KT88 | 32/6 | PY83 | 10/- | 50C5 | 12/6 |
| EB91 | 5/3 | N37 | 15/6 | PY88 | 8/3 | 6F23 | 15/6 |
| ECC81 | 8/- | N339 | 25/6 | PY500 | 20/- | 6F24/5 | 12/6 |
| ECC82/3 | 8/6 | PC86/8 | 10/3 | PZ30 | 16/- | 6F26 | 8/3 |
| ECC84/5 | 8/6 | PC900 | 10/3 | R19 | 13/- | 6F28 | 11/6 |
| ECC88 | 11/- | PC95 | 7/3 | R20 | 15/- | 6/30L2 | 15/6 |
| E88CC | 12/6 | PC97 | 8/3 | UABC80 | 10/6 | 10F1 | 15/- |
| ECF80/2 | 9/6 | PCC84 | 9/3 | UBF89 | 8/- | 10F18 | 10/- |
| ECF86 | 11/- | PCC85 | 8/6 | UBC41 | 9/9 | 10P13 | 16/- |
| ECH35 | 13/6 | PCC88 | 14/- | UCC85 | 9/3 | 10P14 | 19/- |
| ECH42 | 13/3 | PCC89 | 12/3 | UCH42 | 13/9 | 20P4 | 20/- |
| ECH81 | 10/3 | PCC189 | 12/3 | UCH81 | 10/9 | 30C1 | 10/3 |
| ECH83 | 8/- | PCF80 | 10/3 | UCL82 | 10/3 | 30C15 | 13/9 |
| ECH84 | 9/6 | PCF82 | 10/6 | UCL83 | 12/3 | 30C17 | 15/9 |
| ECLL800 | 20/- | PCF84 | 9/6 | UF41/2 | 11/- | 30C18 | 13/6 |
| ECL80 | 8/- | PCF86 | 12/3 | UF80/5 | 7/6 | 30F5 | 16/6 |
| ECL82 | 9/9 | PCF200/1 | 16/3 | UF89 | 8/3 | 30FL1 | 12/9 |
| ECL83 | 11/6 | PCF801 | 12/3 | UL41 | 11/6 | 30FL12 | 17/6 |
| ECL86 | 9/9 | PCF802 | 12/3 | UL84 | 11/- | 30FL14 | 13/6 |
| EF39 | 10/6 | PCF805 | 13/- | UM80/4 | 9/- | 30L1 | 9/3 |
| EF80 | 8/- | PCF806 | 12/3 | UY41 | 8/- | 30L15 | 15/3 |
| EF83 | 10/- | PCF808 | 13/6 | UY85 | 6/9 | 30L17 | 14/6 |
| EF85 | 8/3 | PCH200 | 11/6 | U25 | 15/- | 30P12 | 15/6 |
| EF86 | 13/3 | PCL82 | 10/3 | U26 | 15/- | 30PL1 | 12/9 |
| EF89 | 8/- | PCL83 | 12/3 | U191 | 14/6 | 30P4MR | 20/- |
| EF91 | 8/6 | PCL84 | 10/3 | U193 | 8/3 | 30P19 | 12/9 |
| EF92 | 10/- | PCL85 | 10/6 | U301 | 17/- | 30PL13 | 18/6 |
| EF93 | 9/6 | PCL86 | 10/3 | W729 | 11/- | 30PL14 | 18/6 |
| EF94 | 15/6 | PD500 | 30/6 | Z759 | 24/6 | 30PL15 | 18/6 |
| EF95 | 12/6 | PFL200 | 14/9 | 5Y3 | 8/6 | | |
| EFI83 | 11/3 | PL36 | 12/9 | 5Z4 | 9/6 | | |

**90% B.V.A. BOXED (NORMAL GUARANTEE) OR OWN VALVES SUPPLIED, 1 YEAR'S GUARANTEE. ADD 6d PER VALVE ON ORDERS UNDER 6, OTHERWISE FREE POST AND PACKING.**

## SEMICONDUCTORS

| | | | | | | | |
|---|---|---|---|---|---|---|---|
| AC117 | 12/- | BC115 | 6/6 | BF225 | 6/- | 2N1305 | 4/10 |
| AC126 | 4/4 | BC117 | 7/9 | BF257 | 9/6 | 2N1306 | 6/2 |
| AC127 | 4/9 | BC118 | 7/9 | BF22A | 9/6 | 2N3055 | 15/- |
| AC128 | 4/6 | BC134 | 11/6 | NKT125 | 5/9 | 2N3392 | 5/- |
| AC176 | 7/4 | BC147 | 5/8 | NKT281 | 4/- | 2N3702 | 5/6 |
| ACY17 | 6/- | BC148 | 4/4 | NKT401 | 17/6 | 2N3705 | 4/6 |
| ACY20 | 6/- | BC152 | 5/6 | OC25 | 9/6 | 2N3711 | 4/9 |
| AD149 | 11/8 | BC175 | 5/6 | OC44 | 5/6 | 2N3819 | 9/- |
| AD161 | 6/9 | BC187 | 5/8 | OC45 | 5/4 | 2N3826 | 6/- |
| AD162 | 6/9 | BC213L | 5/4 | OC71 | 4/4 | 2N4062 | 4/6 |
| AFI14 | 4/8 | BDY20 | 30/6 | OC72 | 5/4 | 2N4289 | 4/6 |
| AFI15 | 4/8 | BFY50 | 5/- | OC77 | 5/6 | | |
| AFI16 | 4/9 | BFX84 | 7/- | OC78 | 5/- | | |
| AFI17 | 4/6 | BFX29 | 7/6 | OC81 | 4/- | **RECTIFIERS** | |
| AFI18 | 12/- | BFI15 | 5/6 | OC81D | 4/- | BY126 | 4/4 |
| AFI26 | 4/8 | BFI17 | 9/6 | (GET113) | | BY127 | 5/- |
| AFI27 | 4/8 | BFI63 | 7/- | OC84 | 5/- | | |
| AFI39 | 8/8 | BFI67 | 6/- | OC169 | 4/8 | | |
| AFI78 | 9/- | BFI73 | 7/- | OC171 | 6/- | | |
| AFI79 | 9/- | BFI78 | 7/- | OC200 | 6/6 | **DIODES** | |
| AFI80 | 12/4 | BFI80 | 8/- | OC202 | 9/6 | AA119 | 2/- |
| AFI81 | 9/4 | BFI81 | 8/- | OC203 | 6/6 | OA47 | 1/9 |
| AFI86 | 13/4 | BFI82 | 8/- | OCP71 | 12/6 | OA79 | 1/10 |
| AF239 | 8/6 | BFI84 | 5/- | P346A | 4/6 | OA81 | 1/10 |
| BC107A | 5/- | BFI94 | 5/- | 2N456A | 17/6 | OA91 | 2/- |
| BC108B | 4/6 | BFI97 | 6/4 | 2N697 | 5/10 | OA202 | 2/- |
| BC109C | 5/- | BF200 | 7/4 | 2N698 | 10/6 | BZY88 | |
| BC113 | 5/6 | BF224 | 6/- | 2N1132 | 11/6 | (SERIES) | 6/6 |

## CATHODE RAY TUBES

New and Budget tubes made by the leading British manufacturers Guaranteed for 2 years. In the event of failure under guarantee, replacement is made without the usual time wasting forms and postage expense.

| Type | | New £ | Budget £ |
|---|---|---|---|
| MW36-20 | | | 4.10.0 |
| MW36-21 | | | 4.10.0 |
| MW43-69Z | CRM171 | | |
| | CRM172 | 6.12.0 | 4.12.6 |
| MW43-80Z | CRM173 | 6.12.0 | 4.12.6 |
| AW43-80Z | CME1702 | 6.12.0 | 4.12.6 |
| | CME1703 | 6.12.0 | 4.12.6 |
| | CME1706 | 6.12.0 | 4.12.6 |
| | C17AA | 6.12.0 | 4.12.6 |
| | C17AF | 6.12.0 | 4.12.6 |
| AW43-88 | CME1705 | 6.12.0 | 4.12.6 |
| AW47-90 | | | |
| AW47-91 | A47-14W | 7.13.4 | 5. 7.6 |
| A47-14W | CME1901 | 7.13.4 | 5. 7.6 |
| | CME1902 | 7.13.4 | 5. 7.6 |
| | CME1903 | 7.13.4 | 5. 7.6 |
| | C19AH | 7.13.4 | 5. 7.6 |
| A47-13W | CME1906 | 10. 5.6 | 8.10.0 |
| A47-11W | CME1905 | 8.17.3 | 7. 0.0 |
| A47-26W | CME1905 | 8.17.3 | 7.15.0 |
| A47-26W/R | CME1913R | 9. 6.8 | |
| A50-120W/R | CME2013 | 10.17.0 | |
| AW53-80 | | 8.18.8 | 6. 5.0 |
| AW53-88 | CME2101 | 8.18.8 | 6. 5.0 |
| AW59-90 | | | |
| AW59-91 | CME2303 | 9.11.8 | 7. 4.0 |
| A59-15W | CME2301 | | |
| | CME2302 | | |
| | CME2303 | 9.11.8 | 7. 4.0 |
| A59-11W | CME2305 | | |
| A59-13W | CME2306 | 13.13.0 | 10.19.6 |
| A59-16W | CME2306 | 13.13.0 | 10.19.6 |
| A59-23W | CME2305 | 12.12.0 | 10.10.0 |
| A59-23W/R | | 12.12.0 | 10.10.0 |
| PORTABLE SET TUBES | | | |
| TSD217 | | | 6.15.0 |
| TSD282 | | | 6.15.0 |
| A28-14W | | 9. 3.4 | Not supplied |
| CME1601 | | | 7.15.0 |
| CME1602 | | | 8. 0.0 |

A discount of 10% is also given for the purchase of 3 or more New tubes at any one time.
All types of tubes in stock. Carriage and insurance 15/-.

## TRANSISTORISED UHF TUNER UNITS

### NEW AND GUARANTEED FOR 3 MONTHS

Complete with Aerial Socket and wires for Radio and Allied TV sets but can be used for most makes.
Continuous Tuning, 90/-; Push Button, 100/-.

## STYLII

TC8, GC2, GP59, GC8, DC284, Stereo 105, 106, 208, 2/- each (individually boxed); ST3/5, ST8/9, 9TA, 9TA/HC, GP91, 8/-, Diamond. Post and packing 5d per item for orders under 24.

## TAPES (Polyester PVC)


4in L.P., 8/6; 3in L.P., 5/6.
Standard Play: 600ft 5in, 8/6; 900ft 5½in, 10/6; 1,200ft 7in, 12/6.
Long Play: 900ft 5in, 11/-; 1,200ft 5½in, 13/-; 1,800ft 7in, 18/-.
Double Play: 1,200ft 5in, 16/-; 1,800ft 5½in, 19/-; 2,400ft 7in, 28/-.
Philips type Cassettes (in plastic library pack): C60, 10/6; C90, 12/6; C120, 19/6.
Post and packing 1/6 on all orders.

## ACOS CARTRIDGES

GP91-1—Medium output Mono Crystal, 21/- inc. P. Tax.
GP91-3sc—High output Mono Crystal (TC8H, TC8M, BSR X3H, X3M), 21/- inc. P. Tax.
GP93-1—Stereophonic Crystal, 24/9 inc. P. Tax.
GP94-1—Stereophonic Ceramic, 31/- inc. P. Tax.
GP95-1—Stereophonic Crystal, 24/9 inc. P. Tax.
GP96/1—Stereophonic Ceramic, 31/6 inc. P. Tax.

**ADD 5d. PER ITEM FOR POST AND PACKING FOR ORDERS UNDER 24 PIECES.**

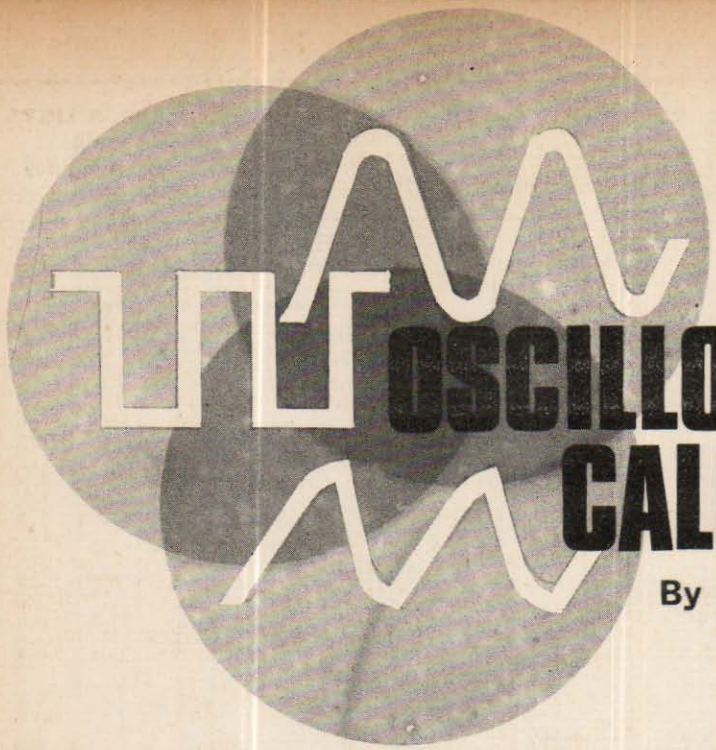**TERMS, CASH WITH ORDER ONLY. POST AND PACKING PAYABLE ON ORDERS UP TO £3, AFTER THAT, FREE EXCEPT C.R.T.'s.**



# OSCILLOSCOPE CALIBRATOR

By R. CARTWRIGHT

A square wave generator for calibrating oscilloscope Y amplifiers, and the frequency compensation of probes and attenuators.

Is also useful as a general purpose unit for checking audio amplifiers, tone control circuits, Schmitt triggers, monostables, etc.

## SPECIFICATION

| | | | |
|---|---|---|---|
| OUTPUT | Square wave, 10V peak-to-peak max. | OUTPUT LEVEL | 0·1V, 0·2V, 0·5V, 1V, 2V, 5V, 10V |
| FREQUENCIES | 1kHz, 10kHz, and 25kHz | | |
| CALIBRATION | With ordinary d.c. voltmeter | RISE TIME | Better than 1$\mu$s |

ONE problem often associated with home constructed projects is that of calibration. This article describes a small unit for calibrating the "Y" amplifier of an oscilloscope.

The best calibration waveform for this purpose is the square wave, its flat top and bottom make it easy to see and align with graticule markings. It can also be used for adjusting the frequency compensating capacitance of an attenuator or probe. Having decided on the waveform, we need a method of calibrating the calibrator.

## USING A VOLTMETER

A conventional multimeter could be used on the a.c. voltage ranges (but see end of article). Rather old a.c. meters are not recommended because their meter rectifiers tend to change their characteristics with age. In any case, multimeters are usually considered to be more accurate and are more easily checked on the d.c. ranges. It would, therefore, be more convenient to use the d.c. ranges because the meter is an average reading instrument.

If we try to measure a square wave voltage on a d.c. meter, the reading will be zero (Fig. 1a) because the positive parts of the waveform cancel the negative sections. If we offset the d.c. level to the bottom of the square wave, the meter will read half the maximum (Fig. 1b).

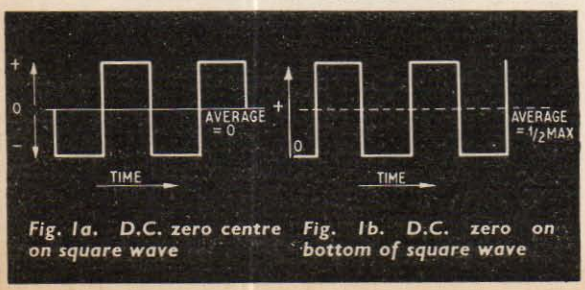



*Fig. 1a. D.C. zero centre on square wave*

*Fig. 1b. D.C. zero on bottom of square wave*

## EMITTER TIMING CIRCUIT

The circuit (Fig. 2) is quite straightforward, consisting of a multivibrator followed by an output stage. The multivibrator, TR1 and TR2, has the timing components in the emitters and uses only one capacitor. This is an advantage if different frequencies are required since only one capacitor is required for each frequency.

It is also possible to adjust the frequency by varying the value of the collector resistor of TR1. This makes it possible to set the multivibrator to an exact frequency if required.

The basic frequency of the instrument is 1kHz; this is a "standard" frequency for voltage calibration and is used on commercial oscilloscopes.

The output transistor TR3 has its current set to 10mA

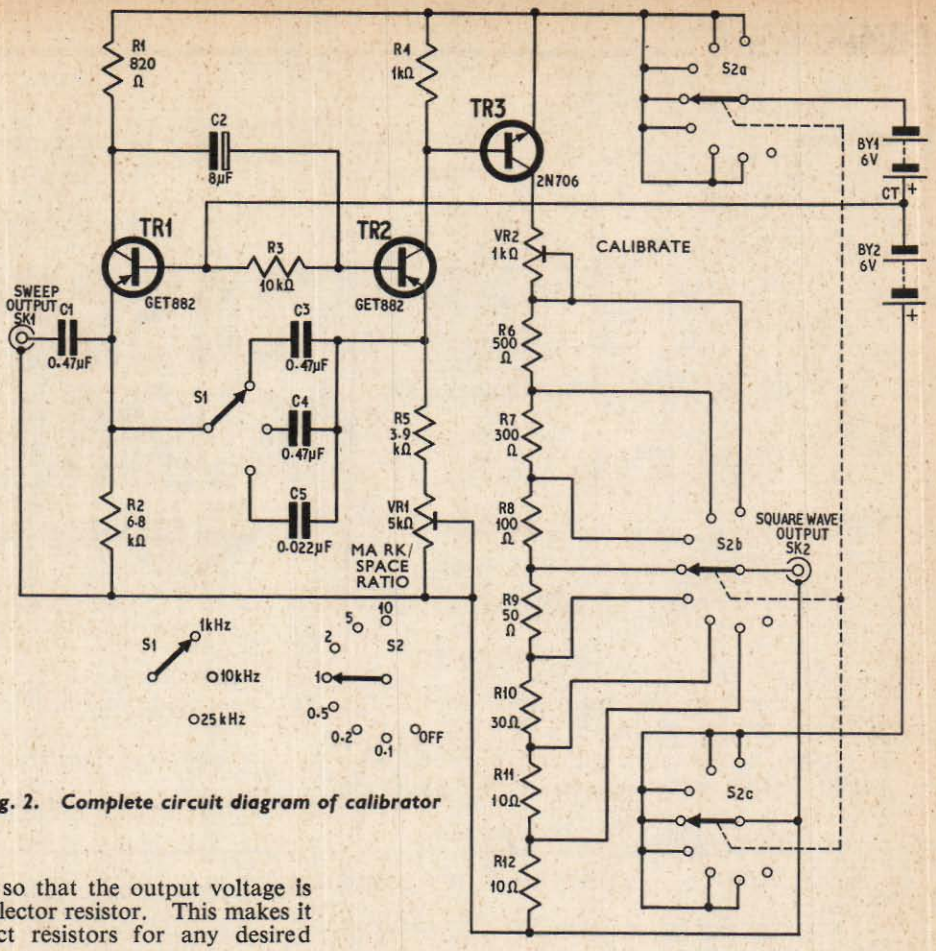



*Fig. 2. Complete circuit diagram of calibrator*

by VR2 (see setting up) so that the output voltage is directly related to the collector resistor. This makes it a simple matter to select resistors for any desired sequence of output voltages.

The output is taken from this resistor, the earth being the positive side of the supply. This method of connection gives the d.c. level to the signal. This resistor is divided into sections which subdivide the output voltage in a 1, 2, 5 sequence from 100mV to 10 volts peak-to-peak.

Only the 10 volts position of output voltage selector needs to be adjusted; all other positions depend on the accuracy of the resistors used.


## CONSTRUCTION

Layout is not critical, except that the voltage selector switch and VR2 should be close to TR3. See Fig. 3. The resistors used in the voltage selector switch should be selected to 2 per cent or better from 5 per cent stock; all other resistors can be 5 per cent.

Any transistors having similar specifications to those quoted should work satisfactorily. Take care to connect them correctly; the first two are *pnp* and the output transistor is an *npn* type.
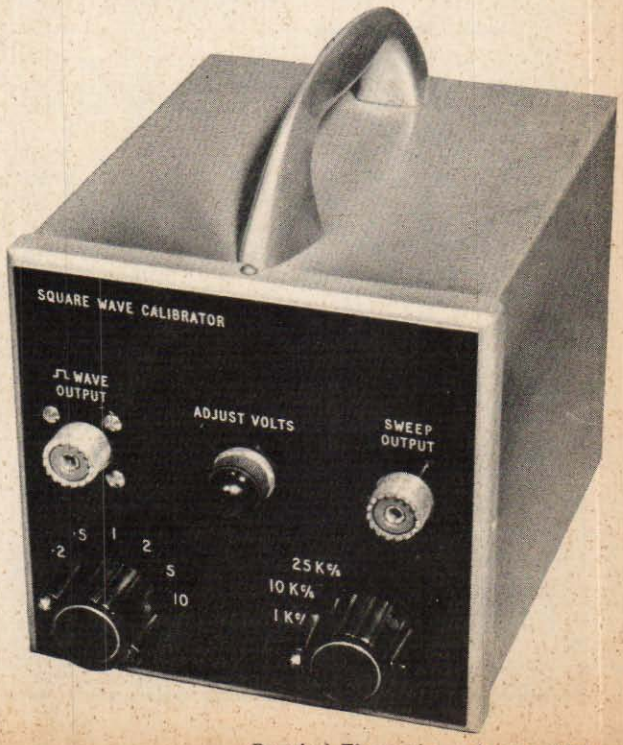
## SETTING UP

After checking the wiring for errors, switch on and view the output on the oscilloscope. Set the mark space ratio to exactly 1:1 by adjusting VR1. Then, set the output switch to the 10 volts position, connect a d.c. voltmeter to the output socket and adjust the set output control until the reading is 5 volts. The unit is now ready for use. Connect it to the "Y" amplifier input on the oscilloscope.



# COMPONENTS . . .

**Resistors**

| | |
|---|---|
| R1 | 820Ω 5% |
| R2 | 6·8kΩ 5% |
| R3 | 10kΩ 5% |
| R4 | 1kΩ 5% |
| R5 | 3·9kΩ 5% |
| R6 | 500Ω (1kΩ + 1kΩ in parallel) |
| R7 | 300Ω (150Ω + 150Ω in series) |
| R8 | 100Ω |
| R9 | 50Ω (100Ω + 100Ω in parallel) |
| R10 | 30Ω (15Ω + 15Ω in series) |
| R11 | 10Ω |

All ¼ watt, 5% carbon except R6 to R11 at 2%

**Potentiometers**

| | |
|---|---|
| VR1 | 5kΩ skeleton preset *or* slider preset |
| VR2 | 1kΩ linear preset control |

**Capacitors**

| | |
|---|---|
| C1 | 0·47μF polyester 5% |
| C2 | 8μF elect. 15V |
| C3 | 0·47μF polyester 5% |
| C4 | 0·047μF polyester 5% |
| C5 | 0·02μF polyester 5% |


(See Table 1)

**Transistors**

TR1, TR2 GET882 *or* 2N1305 (2 off)
TR3 2N706

**Switches**

S1 Single pole, 3-way rotary switch
S2 3-pole, 7-way (8 positions minimum) can be made up from wafer switch parts, two or three wafers, up to 12-way, 8 used

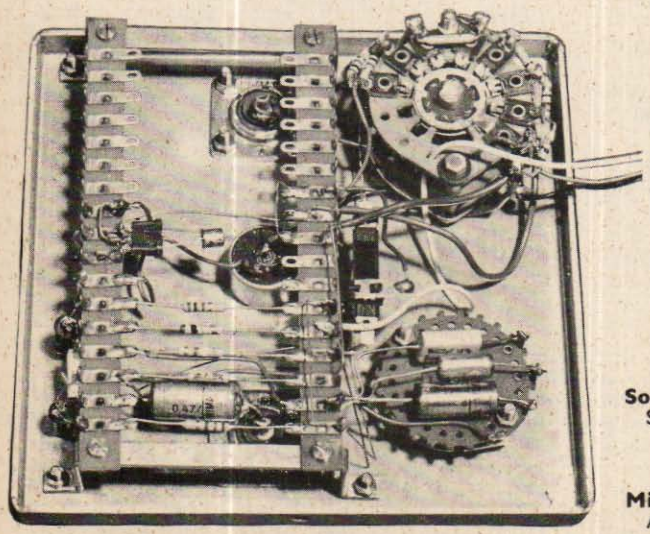

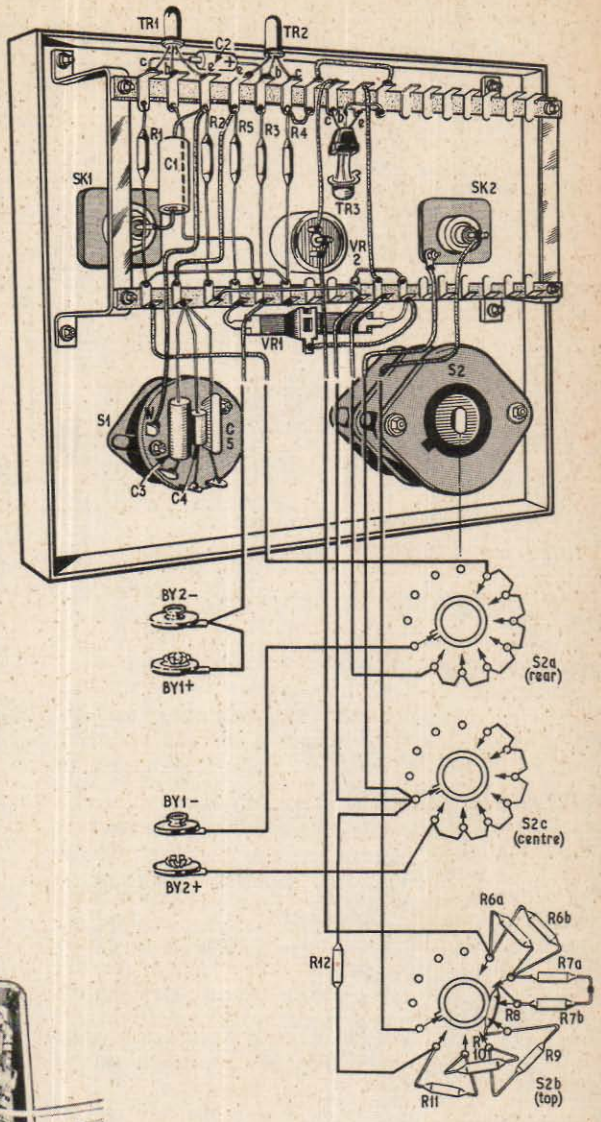



*Fig. 3. Wiring and component layout*

**Sockets** (with plugs)

SK1, SK2 Coaxial panel mounted sockets and plugs *or* "u.h.f." style p.t.f.e. connectors as on model

**Miscellaneous**

Aluminium case to hold components and batteries approx. 6in × 5in × 5in
Miniature tag strips, knobs and wire

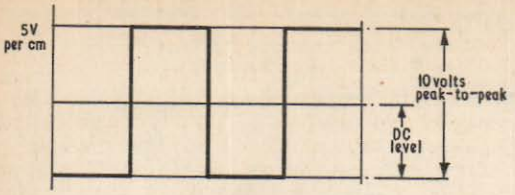



*Fig. 4. Square wave of 10V peak-to-peak represented on graticule*

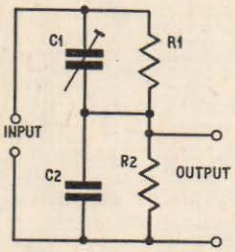



*Fig. 5. Oscilloscope attenuator with frequency compensation*

## USING THE CALIBRATOR

To calibrate an oscilloscope, set the calibrator output voltage switch to the 10 volts position, set the "Y" input switch on the 'scope to 10 volts per centimetre and adjust the preset "Y" gain control until the top and bottom of the square wave are in line with graticule lines 1 centimetre apart (Fig. 4).

Repeat this for the other ranges, checking that the square wave is not distorted on any of them. If it is, adjustment of the attenuator trimmer should correct this to a good waveform with a square corner and flat top. Incorrect compensation will show up as overshoot of the leading edge (over compensated) or as a rounded corner (under compensated).

It does not matter if the 'scope is a.c. or d.c. coupled. If the 'scope is a.c. coupled it will be immune to the d.c. level in the signal. If the 'scope is d.c. coupled a slight readjustment of the "Y" shift control is all that is required.

The signal has a d.c. level so that the unit can be calibrated using an ordinary d.c. voltmeter (preferably an Avo "8"). Once the mark space ratio is set to 1 : 1 the d.c. level is always half the peak to peak value. This feature makes it unnecessary to use Zener diodes to stabilise the supplies, since it only takes a moment to check the calibration.

## FREQUENCY COMPENSATION

As well as voltage calibration the unit is also useful for frequency compensation of attenuators and probes.

The risetime is better than 1$\mu$s and the top is flat so that observation of the unit's waveform on the 'scope under test will show if adjustment of the 'scope is required.

The circuit of a typical 'scope attenuator section is shown in Fig. 5. When in correct adjustment the time constant of C1, R1 will be equal to that of C2, R2.

Because a square wave contains high frequency components in the verticals and low frequency components in the flat sections, a square wave at the input will be undistorted at the output only if $C_1 R_1$ equals $C_2 R_2$.

In practice the unit is connected to the 'scope input, the waveform is observed and any departure from the correct waveform is compensated for by adjustment of the trimmer C1 in Fig. 5.

## OTHER USES

Apart from these two jobs the unit is useful as a square wave generator for general purposes. Checking audio amplifiers, tone controls, Schmitt triggers, monostables and other switching or CR circuits.

The ramp output SK1 is for checking trigger circuits. If the oscilloscope is fitted with a "Trigger Level" control it should be possible to select any point on the ramp and trigger at that point.

To make the unit more useful as a general purpose square wave generator, two other frequencies are available. These are (on the author's unit) 10kHz and 25kHz. When the original was built, these two frequencies were chosen, together with a slightly different output stage which gave a much faster rise time, for work on oscilloscope delay lines.

They are rather high for audio work though, and some constructors may prefer lower frequencies such as 500Hz and 5kHz for this work. All that needs to be done is to change the timing capacitor, C2, as indicated in Table 1.


**Table 1. EMITTER COUPLING CAPACITANCE**

| Capacitance | Frequency |
|---|---|
| 1·0$\mu$F | 500Hz |
| 0·5$\mu$F | 1kHz |
| 0·1$\mu$F | 5kHz |
| 0·05$\mu$F | 10kHz |
| 0·025$\mu$F | 20kHz |
| 0·02$\mu$F | 25kHz |

## METER MEASUREMENTS

There is sometimes confusion about measurements with moving coil meters and especially about the terms "average" and "r.m.s." when applied to readings taken with such meters. The output waveform from the meter rectifier on sine waves is shown in Fig. 6. If the

*continued on page 654*

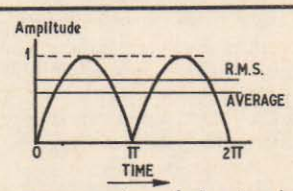


To find the average value of the sine between zero and $\pi$, find the area and divide by the base.

$$\text{Area} = \int_0^{\pi} \sin x \, dx = \Big[ -\cos x \Big]_0^{\pi} = [1] - [-1] = 2 \text{ sq. units.}$$

$$\text{Average} = \frac{2}{\pi} = 0{\cdot}637$$

$$\text{Form factor} = \frac{0{\cdot}707}{0{\cdot}637} = 1{\cdot}11$$

*Fig. 6. Meter rectifier output wave form for sine wave input. To find the average value of the sine between zero and $\pi$ find the area and divide by the base*



# BOOK REVIEWS

## PHOTOELECTRONIC DEVICES

**By J. B. Dance, M.Sc., B.Sc.**
**Published by Iliffe Books Ltd.**
**172 pages, 8½in × 5½in. Price 42s.**

MUCH of the usefulness of modern electronics is due to the exploitation of the photoelectronic effect. It follows that full appreciation of electronic circuits is not possible without a good knowledge of photoelectronic devices. This book is timely and offers a sound introduction to the subject to readers who have a previous knowledge of basic physics to about G.C.E. "advanced" level.

After an introduction to the basic physics of infrared, visible light and ultra-violet radiation, there follow chapters on semiconductor fundamentals, with emphasis on electron energy levels, and photoemissive materials. The remainder of the book deals with a variety of different devices: evacuated tubes, such as photoemissive diodes, photomultiplier tubes, and image intensifiers and converters; semiconductor photodevices, including junctionless photoconductive cells such as the familiar cadmium sulphide and cadmium selenide devices; junction photodevices such as phototransistors, and more sophisticated integrated circuit light detectors, based on new principles.

The final chapter is devoted to electroluminescent devices and provides a valuable curtain raiser to what is undoubtedly going to be a most exciting development area in the future.

To the student and amateur enthusiast alike, the value of this book is enhanced by the inclusion of practical circuits illustrating some everyday applications for the devices described. Component values are included, and device types are specified.

F.E.B.

## 110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR

**By R. M. Marston**
**Published by Iliffe Books Ltd.**
**125 pages, 8½in × 5½in. Price 18s (soft back).**

BASIC differences between silicon and germanium transistors and their circuit configurations provide an essential introduction to the common usage of silicon devices. From here on this book describes many well established circuits or "building bricks" which can be found elsewhere.

With a title such as this book carries, one would expect to find more practical details in addition to theory, such as is found in the book "Using Semiconductors" (reviewed in our May issue). This book has no practical guidance at all, and it is left to the "home constructor" to sort out the information himself. He can do much the same by obtaining technical application reports.

The circuits dealt with include one- and two-stage linear amplifiers (small signal only), switching circuits, regulators, f.e.t. amplifiers, unijunction oscillators, s.c.r. switching at low voltages, and a variety of circuits using the simple "dual gate" integrated circuit.

M.A.C.

## CIRCUIT CONSULTANT'S CASEBOOK

**By T. K. Hemingway**
**Published by Business Books Ltd.**
**210 pages, 9in × 5¾in. Price 75s.**

FOR circuit designers and trouble shooters alike, this excellent volume goes a long way towards attacking design defects that are all too often overlooked.

Although a circuit can be designed to function fairly easily by using reference works, there are factors which can make the reliability of long term safe operation an unknown quantity. The principle concern of the author here is to safeguard transistors in spurious, irregular, or transient overload conditions.

As Head of Electronic Technology at the Guided Weapons Division of B.A.C., it is easy to understand that diagnosis and cure are by-products of a reliability conscious designer. Yet he has attempted here to help other designers to adopt such an approach to first principles design philosophy.

The text is written in an absorbing manner and should be of value to designers with a fairly broad background in circuit design.

While openly admitting that the examples given are not intended to be the last word in all applications, the author does set the designer on his toes for some of the more common pitfalls.

This book is divided into two parts: Part 1 discusses basic design problems, common errors and their correction; Part 2 deals with the ways of meeting specification requirements not readily achieved by standard textbook circuits. The maths is kept to a minimum and only involves the simple algebra normally expected in basic principles.

It is a curious thing that some of the best books on electronics tend to be pricy, but 75 shillings spent on this could save several pounds on damaged components.

M.A.C.

## LUMINESCENT SCREENS, PHOTOMETRY AND COLORIMETRY

**By J. Kalmer M.Sc.**
**Published by Iliffe Books Ltd.**
**200 pages, 8½in × 6½in. Price 60s**

AS THE title of this book suggests, colorimetry and photometry form the subject matter, it is not concerned with luminescence generally, and anyone expecting an explanation of the luminescence mechanism will be disappointed.


The author is concerned only with cathodoluminescence (this is the principle used in cathode ray tubes where phosphors are excited by an electron beam) and then only with the testing of emitted light rather than production of the radiation. Other forms of luminescence, photoluminescence, electroluminescence, etc. are defined on page 1 and then disregarded.

As a book on television screen testing, however, it is difficult to rival. The author, a Czechoslovakian, has had many years experience in objective methods for assessing TV picture quality in both monochrome and colour and practically all aspects are covered. Chapter four, "Colour Measurements" is particularly good.

This book is likely to be of interest to the television enthusiast, particularly with regard to colour, but it is not for casual, general interest reading. The testing methods described are not for the amateur, they are rigorous and require a well equipped laboratory. Mathematical treatment is used throughout.

In all, a very specialised book, but certainly an authoritative work in its field.

K.J.M.

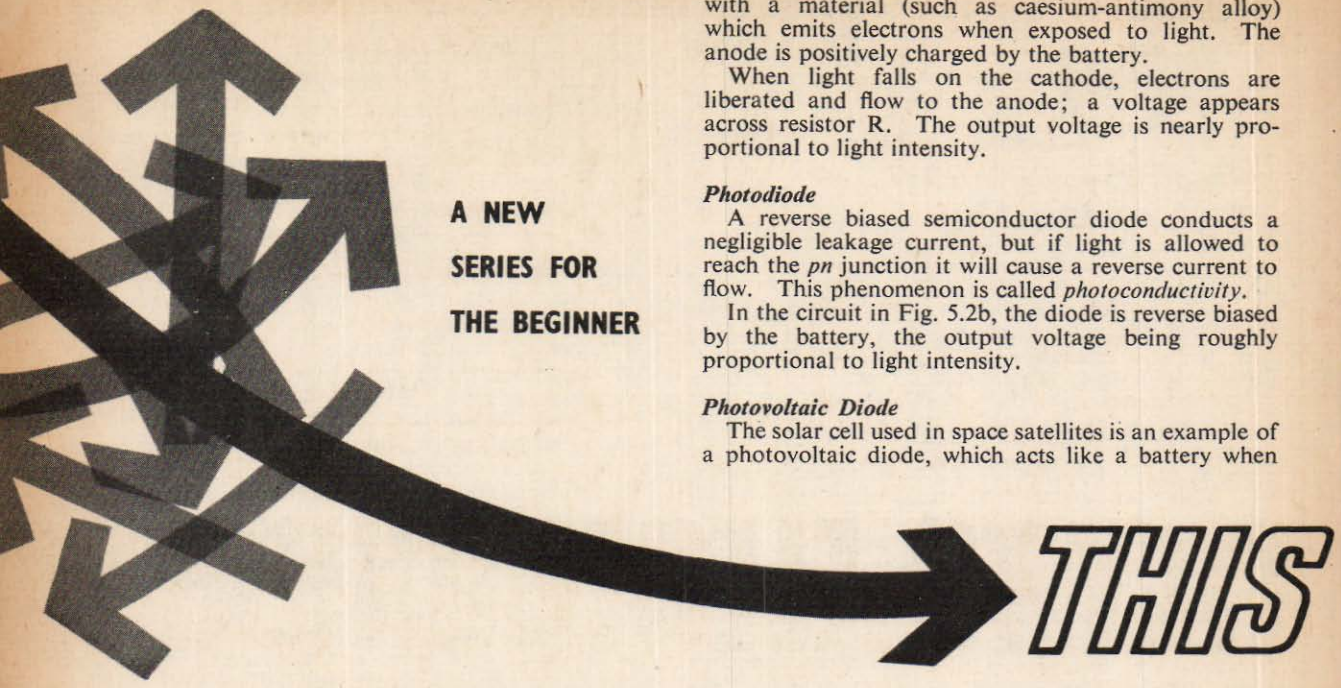


IF the input or output device connected to an electronic circuit converts one form of energy into another it is called a "transducer".

The block diagram in Fig. 5.1 shows a typical transducer application, the Geiger counter. A Geiger Müller tube converts energy resulting from radioactive decay processes into pulses of electrical energy, which are then amplified for conversion into "clicks" of sound energy by a loudspeaker.

In the following descriptions transducers are grouped under six main headings; light, heat, sound, magnetism, motion, and atomic radiation, denoting the type of energy conversion involved.

## LIGHT SENSORS

### *Photoemissive Cell*

The photoemissive cell in Fig. 5.2a consists of two electrodes in a vacuum or gas. The cathode is coated with a material (such as caesium-antimony alloy) which emits electrons when exposed to light. The anode is positively charged by the battery.

When light falls on the cathode, electrons are liberated and flow to the anode; a voltage appears across resistor R. The output voltage is nearly proportional to light intensity.

### *Photodiode*

A reverse biased semiconductor diode conducts a negligible leakage current, but if light is allowed to reach the *pn* junction it will cause a reverse current to flow. This phenomenon is called *photoconductivity*.

In the circuit in Fig. 5.2b, the diode is reverse biased by the battery, the output voltage being roughly proportional to light intensity.

### *Photovoltaic Diode*

The solar cell used in space satellites is an example of a photovoltaic diode, which acts like a battery when exposed to light (Fig. 5.2c). A small silicon photovoltaic diode will generate a current of several milliamps at a potential of about 0·5V in direct sunlight.

Photovoltaic cells used in photographic light meters employ selenium as the photosensitive material.

### *Light Dependent Resistor*

A photoresistor or light dependent resistor (Fig. 5.2d) has a resistive element, usually made of cadmium sulphide, contained in a transparent case. When light shines on the element its resistance decreases. In the circuit in Fig. 5.2d, the output voltage increases with illumination.

The photoresistor is not polarised like a diode, and behaves like an ordinary resistor under conditions of constant illumination, so can be fed from an a.c. as well as d.c. source.

### *Phototransistor*

The phototransistor has a built-in amplification characteristic. Light on the base-emitter junction causes an internal base current to flow, even when the base lead is left disconnected, and this gives rise to a much larger collector current. In the circuit in Fig. 5.2e, the output varies inversely with light intensity.

### *Response*

There is a limit to the speed with which a photosensor will respond to rapid changes of light intensity. For example, the output signal from cadmium sulphide photoresistors and selenium cells tends to fall off if the light input is made to pulsate rapidly at frequencies in excess of a few hundred hertz.

Ordinary silicon phototransistors and photodiodes can respond quite well to light pulsating at 20kHz, while special photoconductive diodes will reach 300MHz. The upper frequency limit of photoemissive cells is theoretically high, but is usually limited in practice, by the high impedance of the device, to around 25kHz.

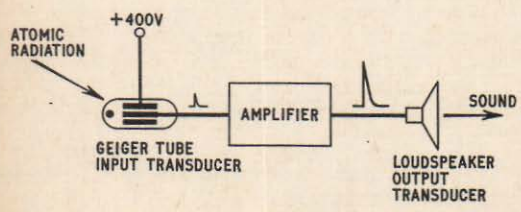



*Fig. 5.1. Block diagram of a simple Geiger counter with the circuit symbol for a Geiger-Müller tube*

## LIGHT SENSORS

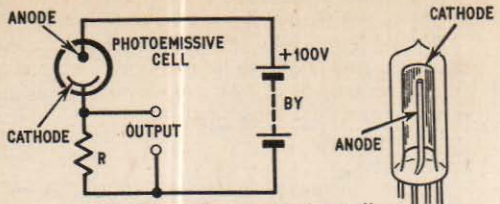



*Fig. 5.2a. Photoemissive cell*

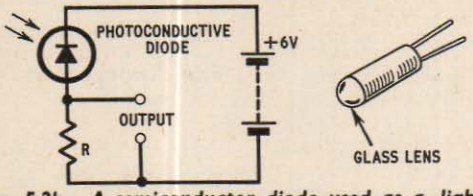



*Fig. 5.2b. A semiconductor diode used as a light-sensor*

## LIGHT EMITTERS

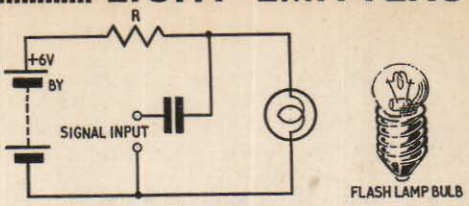



*Fig. 5.3a. Tungsten filament lamp*

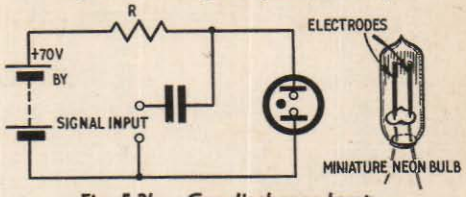



*Fig. 5.3b. Gas discharge lamp*

# WAY TO ELECTRONICS 5

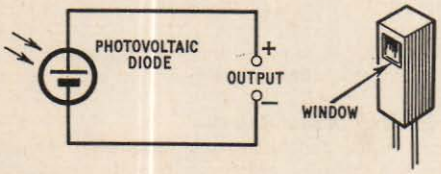



*Fig. 5.2c. Photovoltaic diode or solar cell*

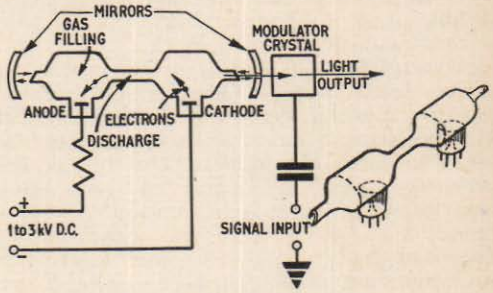



*Fig. 5.3c. Laser tube*

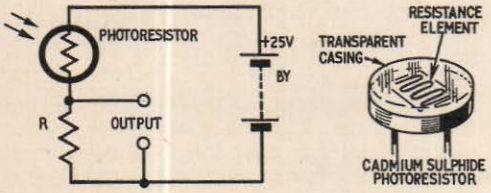



*Fig. 5.2d. Light dependent resistor*

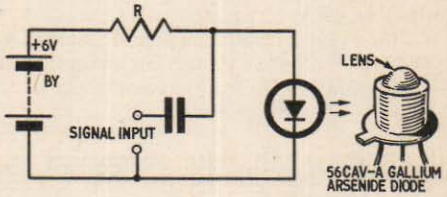



*Fig. 5.3d. Gallium arsenide diode*

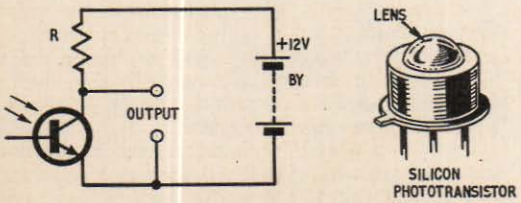



*Fig. 5.2e. Phototransistor has light sensitive base emitter junction*

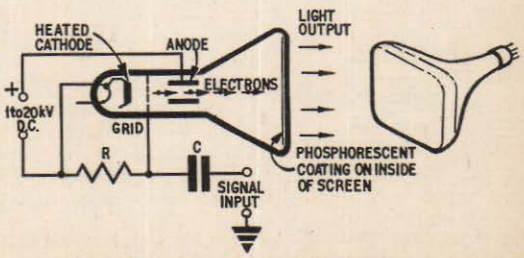



*Fig. 5.3e. Cathode ray tube*

## LIGHT EMITTERS

### *Filament Lamp*

Tungsten filament lamps can be used as output transducers to convert an electrical signal into a modulated light signal, (Fig. 5.3a) examples being colour organs, psychedelic displays, and systems for transmitting information by modulating light instead of radio waves to one of the photosensors mentioned above.

Unfortunately, the tungsten filament transducer is hampered by thermal inertia and cannot respond efficiently to a.c. input signals of more than a few hundred hertz.

### *Gas Discharge Tube*

Gas discharge tubes (Fig. 5.3b) can give pulsating light outputs up to several kilohertz when fed from a high voltage input signal. Applications are similar to those of the tungsten lamp, but also include the stroboscope and photographer's electronic flash gun.

The light amplifier or laser shown in Fig. 5.3c is basically a gas discharge tube, arranged so that most of its light output is reflected back into the tube by mirrors, thus causing a build-up of energy. The output taken from a small orifice in one of the mirrors can be a narrow, high intensity parallel beam of coherent light or infra-red.

One method of modulating the light output is to pass the beam through a crystal which exhibits variable light transmission with applied voltage. Lasers also make effective heat emitters due to the high energy content of the beam.

### *Semiconductor Diode*

Semiconductor diodes made of gallium arsenide will emit infra-red energy (just beyond the red end of the visible spectrum) when forward biased (see electroluminescent diode Fig. 5.3d). Light output is proportional to forward current and can be modulated up to 100MHz.

### *Cathode Ray Tube*

In a television cathode ray tube, a narrow, controlled beam of electrons bombards a phosphorus coating and causes it to emit visible light, Fig. 5.3e.

Although the cathode ray tube is electrically capable of responding to high frequency signals, and can give a fine definition picture of slow moving images, the rate at which the phosphorescent output can change state from white to black is restricted by the afterglow properties of the coating.

Special phosphors used with film scanners can have an afterglow persistence of less than 0·2$\mu$s, equivalent to a modulated light output of 5MHz, but ordinary television tubes are much slower than this, say 50$\mu$s or more.

## HEAT SENSORS

A heat sensor can either work by conduction, in direct physical contact with a heat emitting substance or device, or by radiation when infra-red energy is absorbed. The energy and wavelength of infra-red radiation is dependent on temperature. Several types of light sensor will also respond to infra-red emissions from substances which are not quite red hot, say at 300 degrees C, but are unsuitable for lower temperatures.

There are certain semiconductor devices—mainly confined to the laboratory—that will detect the heat of the human body, but they usually have to be refrigerated in a cryostat at near absolute zero temperature. For temperatures below 300°C there remain the devices which operate by conduction.

## HEAT SENSORS

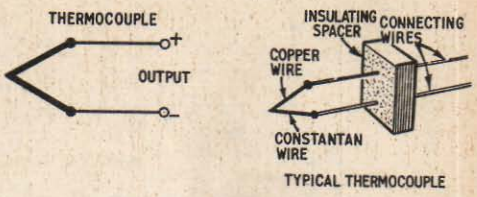



*Fig. 5.4a. Thermocouple*

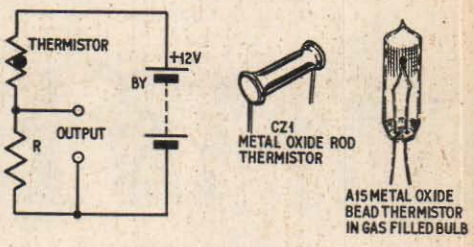



*Fig. 5.4b. Thermistor*

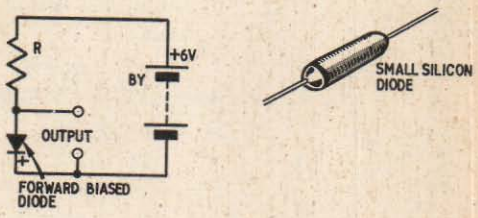



*Fig. 5.4c. Heat sensitive diode*

### *Thermocouple*

The first example of a heat sensor is the thermocouple in Fig. 5.4a. Two wires of dissimilar metals, say copper and constantan, are joined together to form a bimetal junction. A voltage will be produced across this junction when it is heated or cooled relative to the connecting wires. Output is zero at ambient temperature and of opposite polarities for hot and cold.

### *Thermistor*

A thermistor (Fig. 5.4b) has an exaggerated negative temperature coefficient, that is to say its resistance

## HEAT EMITTERS

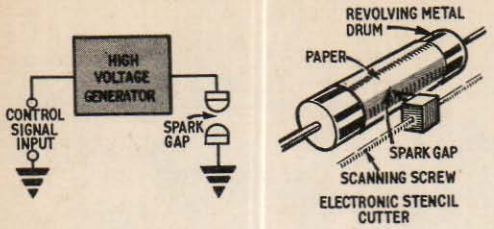



*Fig. 5.5a. Electronic stencil cutter*

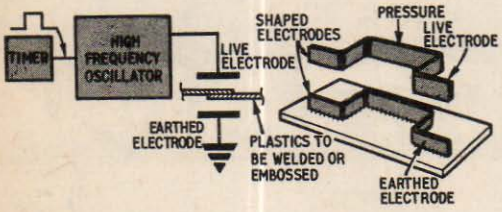



*Fig. 5.5b. Dielectric heater*

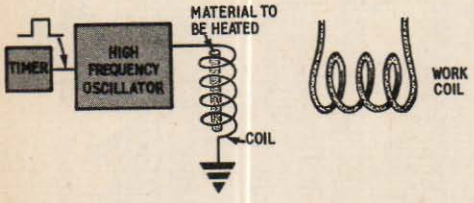



*Fig. 5.5c. Inductive heater*

decreases markedly with a rise in temperature. In the circuit in Fig. 5.4b, a thermistor is arranged in series with a resistor, so that output voltage will increase with temperature.

The response of a thermistor to temperature is not linear, but varies exponentially with inverse absolute temperature (°K). Positive temperature coefficient thermistors are shown in circuit diagrams with a small circle in place of the black dot.

### *Heat Sensitive Diode*

An ordinary silicon signal diode of the type commonly encountered in electronic circuits will act as a heat sensor when forward biased. The output voltage taken from across the diode in the circuit of Fig. 5.4c is inversely proportional to temperature.

## HEAT EMITTERS

Heat emission occurs in electronic circuits as a by-product when resistive components are conducting a current, but this is not the deliberate use of heat as output energy from a transducer.

### *Spark Maker*

The humble electric spark is a heat emitter which is often taken for granted. For instance, the output from an electronic car ignition system is applied at precise intervals by means of a spark.

Then there is the electronic stencil cutter which employs a spark to burn holes of variable diameter in ink duplicator stencils, see Fig. 5.5a. A similar idea is sometimes used to reproduce weather maps from satellite transmissions, on heat sensitive paper.

### *Dielectric Heater*

A dielectric heater—resembling a capacitor—can weld or emboss sheets of thermoplastic material, in the manufacture of motor car seats, purses, wallets, and so on (see Fig. 5.5b).

The plastics to be heated are inserted between two cold electrodes of almost any desired shape and surface finish, which are then pressed together by a spring. One electrode is earthed and the other is fed from the output of a powerful high frequency oscillator (30–50MHz at 1–10kW).

Molecular disturbance within the plastics generates internal heat without appreciable heating of the electrodes, thus softening the plastics. A microwave household oven works on a very similar principle to cook food right through in a short time.

### *Inductive Heater*

Inductive heaters (Fig. 5.5c) are suitable for heat treatment of conductive materials, or materials enclosed in a conductive container. Processes such as melting, hardening, tempering, annealing, soldering, brazing, and sintering can be performed with great precision in this manner.

In Fig. 5.5c an oscillator supplies a.c. to a coil of copper tubing, into which the work to be heated is placed. At low frequencies the work will be heated uniformly, but if the oscillator is tuned to several megahertz, heating will take place only at the surface of the workpiece.

### *Gas Discharge*

Lasers have been successfully employed as heat emitters for micro-spot welding of metals and for fixing detached retinas in eye operations, refer back to Fig. 5.3c.

Part six next month will continue the section on transducers and the series will be concluded with descriptions of miscellaneous electronic devices.

## POINTS ARISING

**MUSICAL STAVE** (*May 1970*)

In the paragraph relating to power output the r.m.s. output voltage should have been given as $\frac{9}{2\sqrt{2}}$ since a sinusoidal swing would be between $\pm 4\frac{1}{2}$ volts. As the actual output from the circuit is rectangular, the power available will vary with the signal mark-space ratio reaching a peak of 580 milliwatts when the ratio is unity.



# ELECTRONORAMA


## B.B.C. Automatic Data Exchange

ON April 6 the B.B.C. brought into service a new automatic message switching system using an STC 6350 automatic data exchange (ADX).

The B.B.C.'s Teleprinter network for the transmission of news and other messages serves 60 outstations in London and the Regions. It handles more than 700,000 messages each year and has had an annual growth rate of some 3 per cent. The hub of the system is at the London Communications Centre in Broadcasting House.

Before the introduction of the new system a point had been reached where further expansion was not possible and the congestion that inevitably occurred at peak periods, due to manual connection to addressee outstations, could not be relieved. This congestion created delays in message transmission. Moreover, a substantial amount of urgent news traffic for non-metropolitan stations had to be diverted to the public telephone service to ensure immediate delivery.

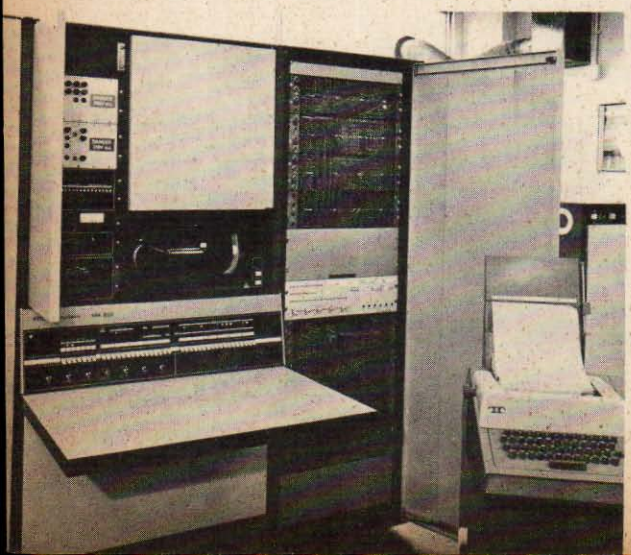In addition to routing and retransmitting messages automatically through the communications centre with a transit time of only milliseconds, some of the major facilities provided by the new 6350 ADX system, the computer section of which is shown below left, are:





On-line message preparation for messages telephoned into the centre or delivered by messenger, there are six 8-unit code 100 word per minute teleprinters, shown above, which feed the messages to the ADX system that immediately puts the messages into the standard format and transmits them to various outstations according to the addressing information given.

Connection to the automatic Telex network; under licence from the Post Office connections to the network have been included to cater for both incoming and outgoing messages.

System reporting and control facilities that report abnormal conditions for supervisory action. These facilities include a visual display unit, shown in operation above, for the inspection and correction of messages rejected by the ADX because of incorrect or incomplete routing information.




## Climatological Station


THE photograph below shows a "Hy-Met" recorder test set being used to check the functioning of a Climatological Recording Station. Both the equipments in the photograph are manufactured by the Environmental Sensors Division of Plessey.

The Climatological Station makes and records over 55,000 measurements. It is self-contained and can monitor such parameters as rainfall; humidity; wind speed and direction; air, soil and water temperatures; barometric pressure; solar radiation; water level, flow and pH.

The equipment can be installed on land, drilling rigs, or on board ships and the information is recorded on standard ¼ inch magnetic tape. This tape is translated using standard Plessey equipment to provide computer compatible paper tape.

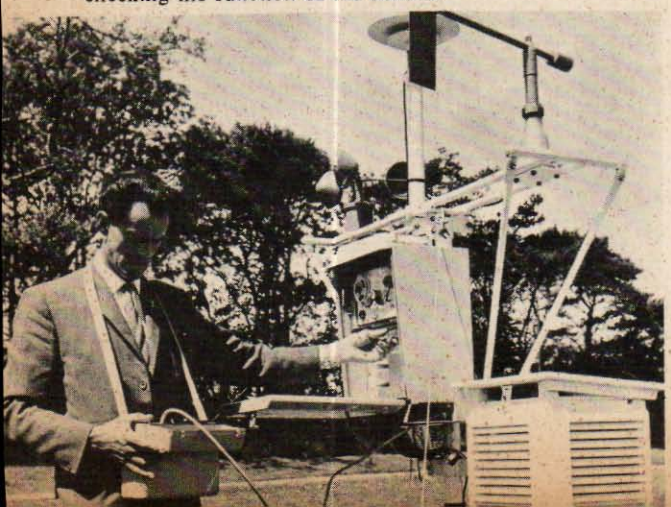Designed for use with Plessey hydrological and meteorological monitoring and recording systems, the "Hy-Met" recorder test-set provides facilities for readily checking the function of the station.



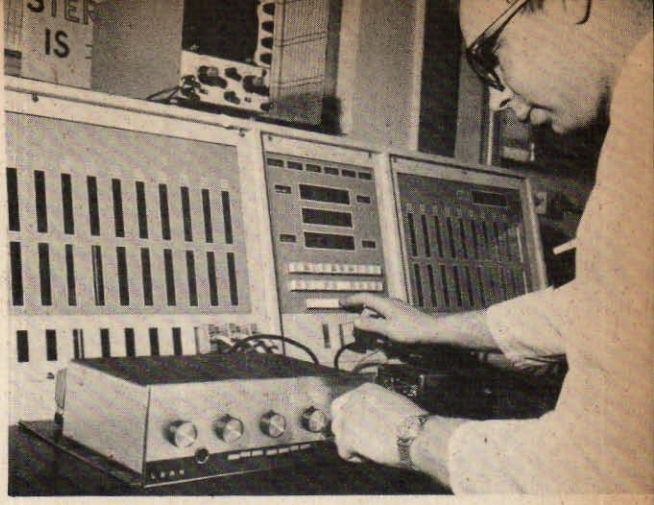

## Electronic Test Equipment

TWO recently announced electronic circuit test equipments are shown above and left, they are: the Fixit (left), an inspection test system for checking mass-produced electronic circuit board assemblies, and the test console (above) used by H. J. Leak for checking tuners and amplifiers.


Fixit, a plugboard or tape programmed test system, has been introduced by Systomation, Inc., New York. The system has the ability to check the exact values of electronic components, such as resistors, diodes, transistors, etc., even though they are wired together in complex parallel electronic circuits. The system is already in use in the United States.


The comprehensive final testing of high fidelity tuners and amplifiers takes up to forty-five minutes by hand. Now H. J. Leak, part of The Rank Organisation, are using a £10,000 Ethermatic test console that carries out an exhaustive test procedure on each unit in about one-tenth of that time. A print-out of all readings made on a tuner or amplifier is available at the end of each test cycle. The unit is shown in use testing a stereo hi-fi amplifier.
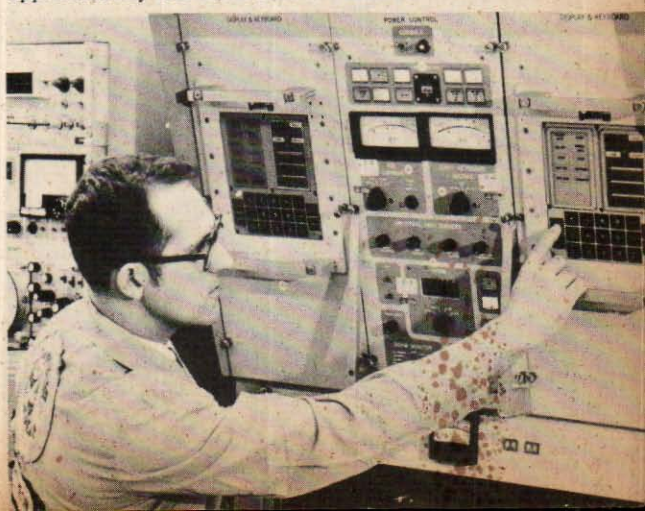
## Mini-Computer

THE latest commercial mini-computer from Raytheon Computers is only 16 inches high and weighs 75 pounds, yet has a memory expansion of up to 32,000. The computer is particularly suitable for applications relating to instrument and process control, data communications and data acquisition as well as basic scientific research.

A small Raytheon digital computer that was produced specifically for space flight is shown being programmed via a display keyboard, during testing, below. The "brain" of the Apollo flights, these computers are only approximately one cubic foot in volume.



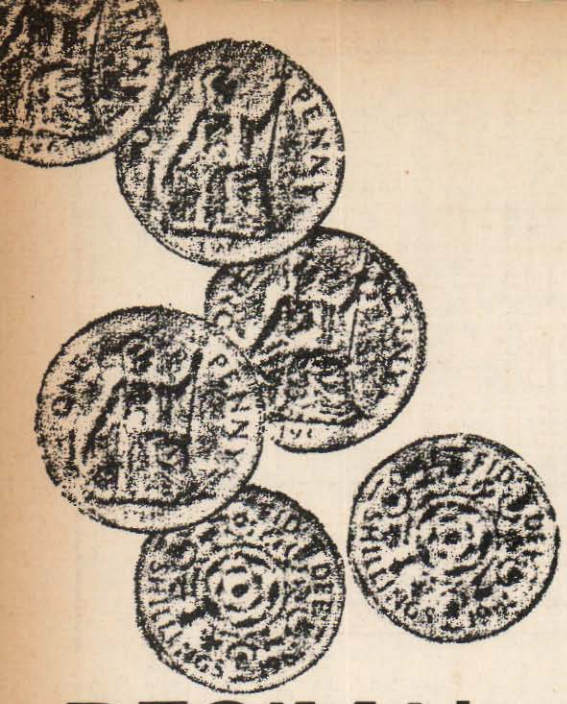

# DECIMAL CURRENCY CONVERTER



By G. A. Cozens

THE change to decimal currency in the U.K. on February 15, 1971 draws nearer as the series of new coins is introduced. But the fact remains that we have undertaken a very difficult operation by maintaining the pound as the major unit of currency, and created the task of relating 24 old pennies to 10 new pence.

Electronic methods of conversion to cope with all the 199 values under £1 fall into two categories: analogue or digital computer techniques.

The analogue method using a simple Wheatstone bridge type of balance was tried, but it was difficult to obtain a sufficient degree of accuracy, it being necessary to be within 0·5 per cent. It is difficult to achieve this, even with quite sophisticated circuits and impossible with simple electronics using dials or meters, so this method was abandoned.

## DIGITAL CONVERSION

When one tries the digital method it is then that the problems which our planners have imposed become apparent. The instrument finally devised uses switches to select the shilling and pence values, while lamps show the new pence equivalents. Some way of combining the switches and reducing the number of lamps had to be found to reduce the cost of the instrument. It is emphasised at this stage that this instrument carries out conversion only and is not suitable for use as an adding machine. The circuit diagram of the Decimal Currency Converter is shown in Fig. 1.

## DIODE LOGIC

This conversion unit uses diode logic. Following the front panel layout in Fig. 2, the selector switches are divided into three rows, one for the even values of shillings (two to eighteen), one row for the odd values of shillings (one to nineteen) and one row for the old pence values—1d, 2d and 3d, 4d, 5d, 6d, 7d, 8d, 9d and 10d, and 11d, thus giving a total of 28 switches. Notice that 2d and 3d are combined on one switch, so are 9d and 10d.

The lamps are arranged in two vertical columns, the left-hand column of nine lamps representing 10p at the bottom of the column, 20p, 30p and so on up to 90p at the top. There is a single lamp to the right of these columns which correspond to ½p.

In this way any of the 199 values of shillings and old pence can be selected using two switches. The equivalent value in new pence will appear in the columns of lamps, one lamp in each column lighting up.

The lamps can be 6 volt 0·1A m.e.s. bulbs or 6V 0·75W l.e.s. bulbs. The relay coil must also be rated for 6 volts operation. Of course, other lamp and relay voltages can be used, but care must be taken not to use current ratings which are too heavy for the diodes to handle.

These diodes are small silicon types such as OA200 or OA202. Some suitable types of diodes are available at very low cost and it may be possible to economise considerably by selecting from these. They are germanium types and are obtainable for as little as 2·5p (6d) each when purchased in bulk quantities.

## SWITCH WIRING

Starting with the 1d value, this switch S28 is wired directly in series with the ½p lamp LP19, and S29. See Fig. 3. The 2d and 3d values are combined in the next switch, which is in series with the 1p lamp.

The 4d switch is also in series with this lamp, but there is a diode D1 between the switches and the lamp, which will conduct when either switch is closed.


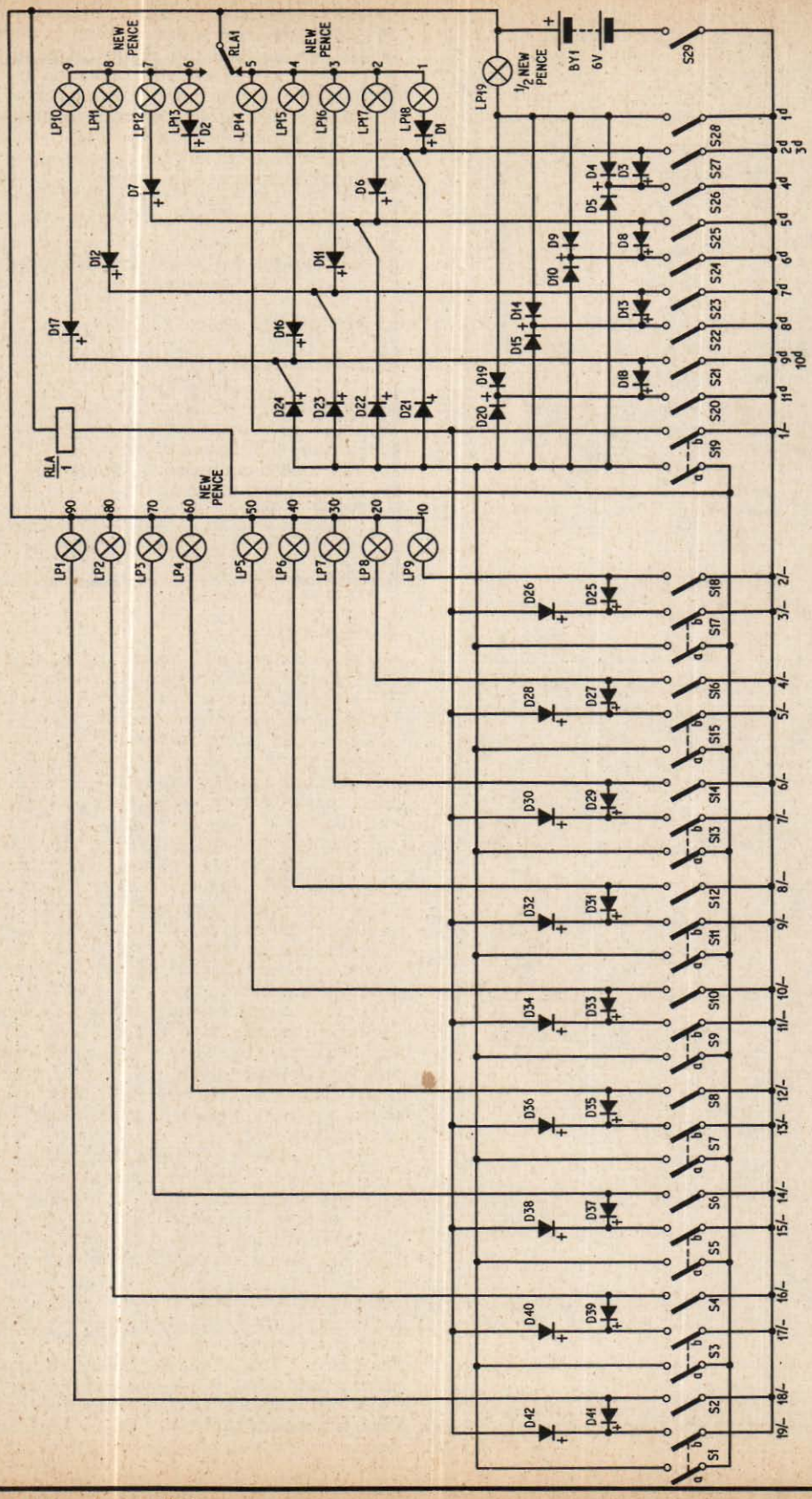



*Fig. 1. Complete circuit diagram of the decimal currency converter*

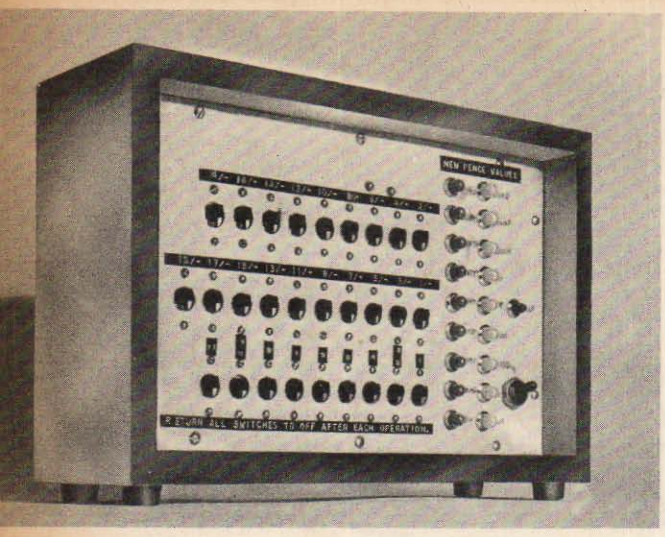


*Front view of the converter giving layout positioning of components. All switches must be returned to the off position after each calculation*

## COMPONENTS . . .

**Diodes**
D1–D42 Any type that will carry 100mA or more (42 off)

**Lamps**
LP1–LP19 6 volt 0·1A or less; with panel lamp-holders (19 off)

**Relay**
RLA Any 6V type with at least one set of change-over contacts

**Switches**
S1 to S28 Double-pole changeover slide *or* toggle switches (28 off)
S29 Single-pole, on/off, toggle switch (S2, S4, S6, S8, S10, S12, S14, S16, S18, S20 to S28 can be single pole)

**Battery**
BY1 6V type 996 *or* 2 × 3V type 800

**Miscellaneous**
Single row tag strips, $\frac{1}{4}$in pitch, 7in long (2 off)
Wood for case, p.v.c. covered wire, lettering

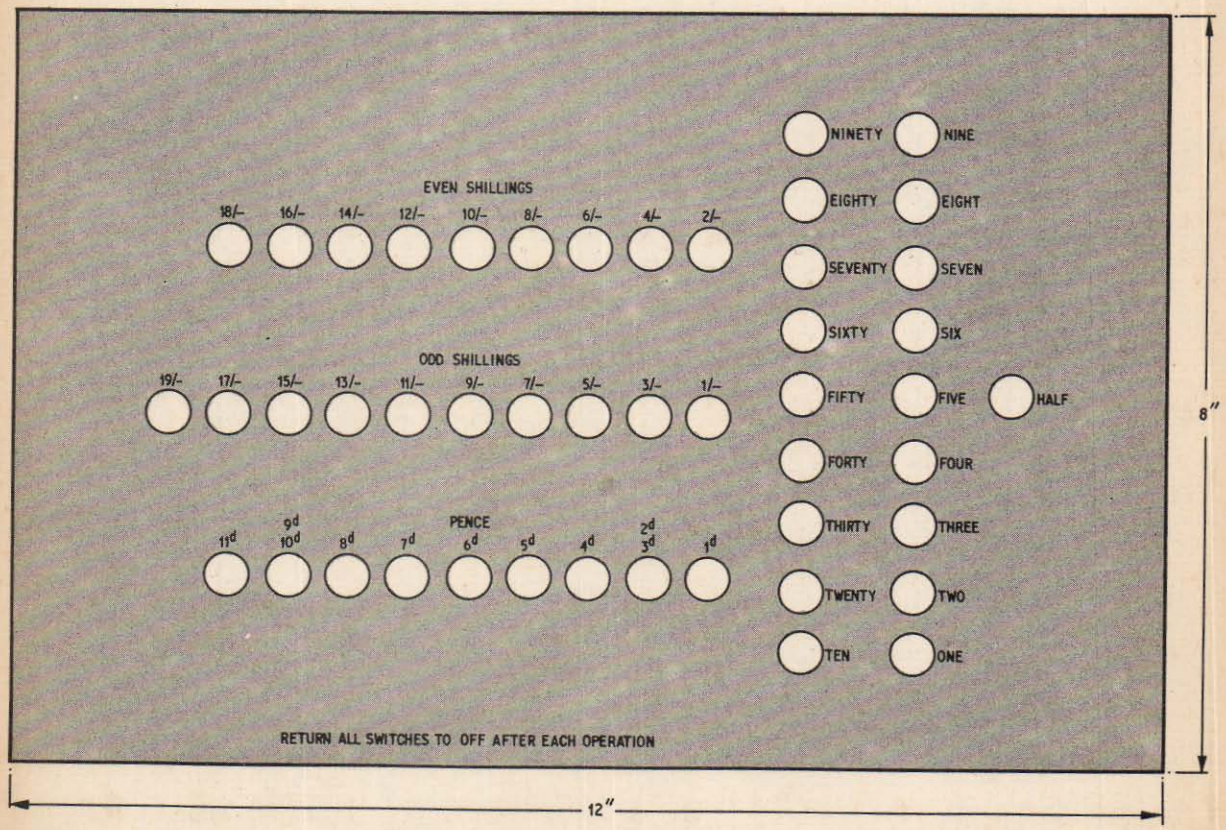



*Fig. 2. Front panel layout of lamps and switches*


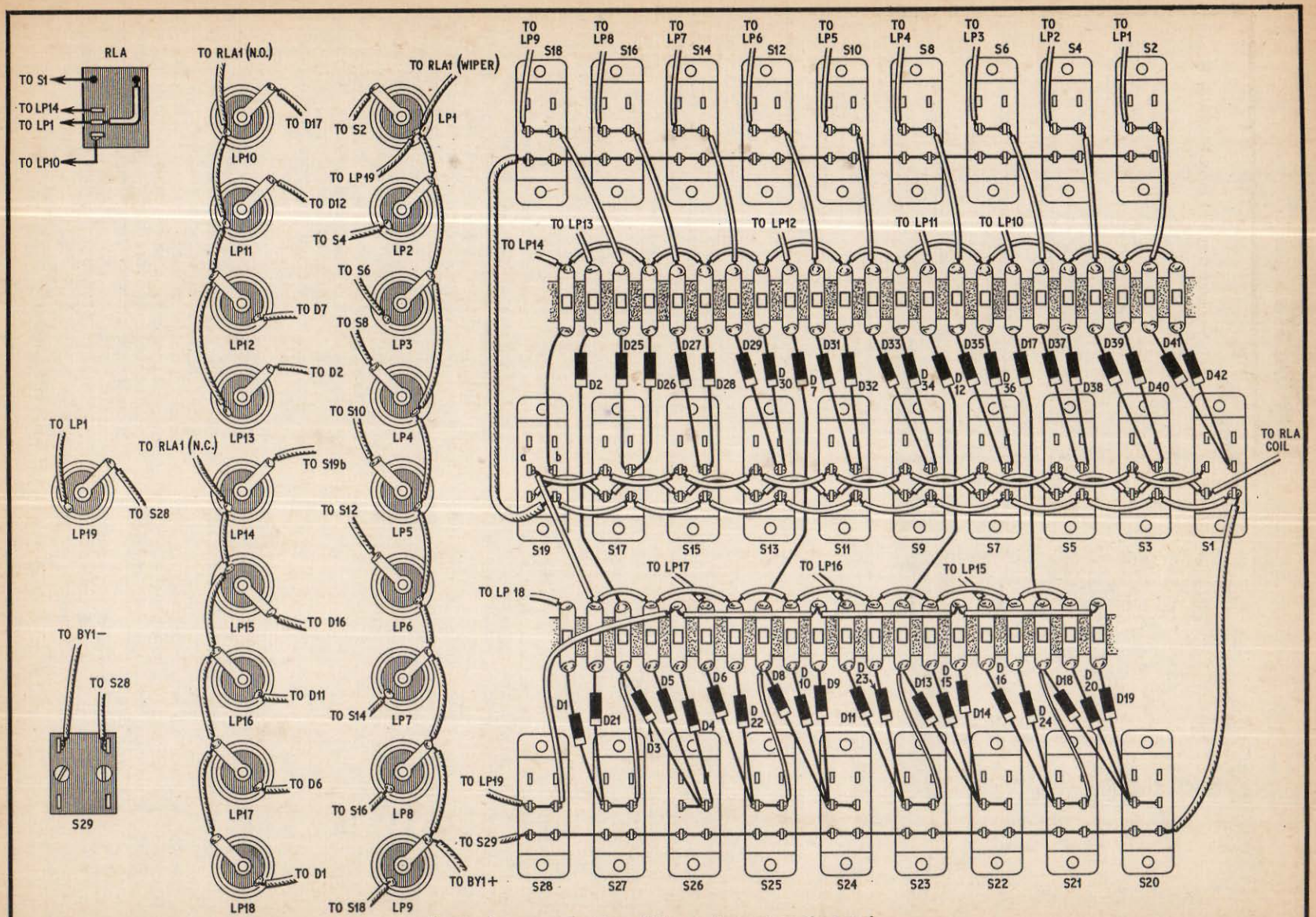



*Fig. 3. Layout and wiring of the components on the panel*

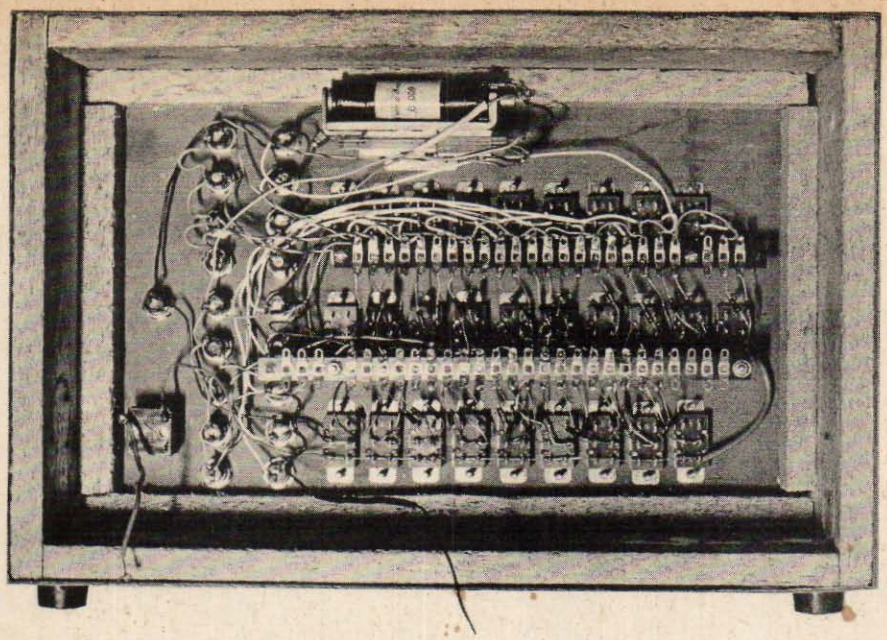

*Rear view of the converter showing components and wiring. The relay can be mounted in any convenient position on an aluminium bracket screwed to the case*

Diode D3 separates the 4d switch from the 2d/3d switch and D4 connects the 4d switch to the ½p lamp.

This pattern is repeated for all the values up to 1s, so that the 5d switch turns on the 2p lamp, and the 6d switch the 2½p lamp, the 7d switch the 3p lamp, and the 8d switch the 3½p lamp. The values 9d and 10d and combined in one switch which operates the 4p lamp and the 11d switch operates the 4½p lamp. The 1s switch operates the 5p lamp.

The 2s switch at the start of the row of even shillings switches is in series with the 10p lamp at the bottom of the left hand column of lamps. The even shillings switches are each in series with a corresponding lamp up to the 18s switch, which operates the 90p lamp at the top of the column.

The line of switches corresponding to the odd numbers of shillings calls for comment since these switches are double-pole, single-throw types. One side is in series with the coil of a relay and a diode. When any one of the odd value paths is completed through another diode, and the "pence" switch and back to the battery, the relay operates.

## RELAY CONTACTS

The relay contacts are single-pole changeover, changing the battery return lead for the 1p, 2p, 3p, 4p and 5p lamps, so that the 6p, 7p, 8p, and 9p lamps are operated. In this way 5p are added to the value each time an odd number of shillings is selected.

For example, suppose we select the value 2s 11d. The 2s switch operates the 10p lamp, and the 11d switch operates the 4p lamp via diodes D18 and D16, and the ½p lamp via diode D19.

Now try the value 15s 6d. The 15s switch operates the 70p lamp via D37. When the 6d switch is made the circuit through the relay coil is completed via the second contact on the 15s switch and diode D10. The relay contacts change over and the 7p lamp is lit by the circuit through D8 and D7. The ½p lamp is lit through D9.

Thus the 70p lamp, and 7p lamp and the ½p lamp give a complete reading of 77½p.

The fact that the 15s switch and the 6d switch must both operate to bring on the 7p lamp make this an example of the classic AND gate.

## COMPONENTS

The bulb holders used in this model are instrument panel indicators. If a protruding lamp is used, it is sometimes difficult to see when the lamp is on in conditions of bright sunlight; the front panel can be set back so that the sides of the case shield the lamps.

The whole instrument can incorporate a small power pack for mains operation; a 6 volt mains transformer and rectifier only is necessary. These should be capable of handling the total current consumption from the relay and the maximum number of lamps in operation at any time. The model shown here used two 3 volt batteries in series; a high capacity 6 volt battery would be equally suitable, for example type 996.

The relay can be almost any type that will operate at 6 volts and has a set of changeover contacts. Examples are Post Office type 600 or Omron type MH2. It is recommended that the coil resistance is as high as is practical to conserve battery power.

## TAG STRIPS

This instrument does not lend itself to any of the modern wiring methods; that shown in the diagram uses long tag strips between the switches.

It is important to make sure that the diodes are connected correctly. The end with the coloured spot or band corresponds to the cathode and is shown on the circuit diagram with a + sign. Relay contacts RLA1 are shown in the non-operative position.

The layout of the instrument with component positions is shown in Fig. 3. It is not essential to follow this rigidly. The drilling details of the front panel will depend on the sizes of the lamps and switches; it should not be beyond the ingenuity of the constructor to arrange these as he chooses. ★

# MAKING THE MOST OF LOGIC IC'S

## PART TWO—By R. W. COLES

## PRACTICAL RTL DICE

ARMED with the basic facts of RTL from Part 1, we can now consider a simple "novelty" application, an electronic dice unit, which will take the place of the usual cube of dots used in so many games of chance.

Anyone interested in RTL will find plenty to get his teeth into, as the design employs the main elements of this family as well as interface circuits and a multivibrator.

This article will describe the design of a small electronic unit which will replace the conventional playing dice.

It must be appreciated that this is intended purely as an exercise in the use of RTL; it is possible to design a more simply way of simulating dice.

The system is designed around RTL logic integrated circuits, and serves as a useful introduction to the use of these versatile devices, which are now available quite cheaply from several different advertisers in this magazine.

### OPERATION OF THE SYSTEM

The operation of the system is quite simple: a free running astable multivibrator is used as the input to a binary counter, which is programmed to divide by six. The six separate states of the counter are decoded by a system of gates, and are used to illuminate six miniature lamps, only one of which will be on at a given time.

Each of the bulbs is assigned a decimal value between one and six, and the bulb which is illuminated at the end of the count represents the "up" side of the dice.

The element of chance is introduced by allowing the "thrower" to control the input to the counter by means of a push button. The multivibrator, or "clock", speed is arranged to be fast enough to prevent the eye from following the count, which will be "frozen" when the button is released.

The unit employs a total of five integrated circuits: two ML914 dual two-input negative logic NAND gates and three ML923 JK bistable flip-flops. These i.c.s are also shown as $\mu$L914 and $\mu$L923 in suppliers' lists. In addition, eight *npn* silicon bulb-driver stages, ten resistors, and two capacitors are employed.

The "clock" is made by a.c. coupling a dual gate to form a multivibrator which oscillates at approximately 1kHz, and gives a square-wave output to drive the counter. The circuit of the ML914, with the two resistors and two capacitors which set the frequency and pulse width of the output, is shown in Fig. 2.1. To enable the clock to be switched on and off, a push button switch is connected in its positive supply line.

### BINARY COUNTER

The divide by six counter is formed from three JK bistables, with feedback to prevent it cycling in unwanted states (because a three-stage counter would normally have eight separate states), each stage dividing by two. The "text-book" way to make a divide by six counter is to force a divide by eight counter to reset to zero when a count of seven is decoded by an AND gate. However, by using JK flip-flops, the same result can be achieved in a simpler way, with the added advantage that bulb decoding gating can also be made simpler than would be the case with a conventional binary divider.

The simplest way to set about designing a counter which is not required to divide to a binary multiple (two, four, eight, 16, etc.), is to divide the required divisor by two until the lowest odd integer is obtained. A counter, with feedback, is then designed to divide by this number, followed by (or preceded by) a number of divide by two stages, to make the final divisor up to the required number.

Our divide by six counter can be constructed by using a divide by three counter followed by one divide by two stage. A further divide by two stage would turn it into a divide by 12 counter, and so on. The advantage of using this method is that it is much simpler to arrange the feedback for resetting a divide by three counter than for a complete divide by six counter.

There is a disadvantage which could be important in some other applications, the counter outputs are not in the natural binary code, as can be seen from the truth tables of the two types of counter discussed (see Fig. 2.2).

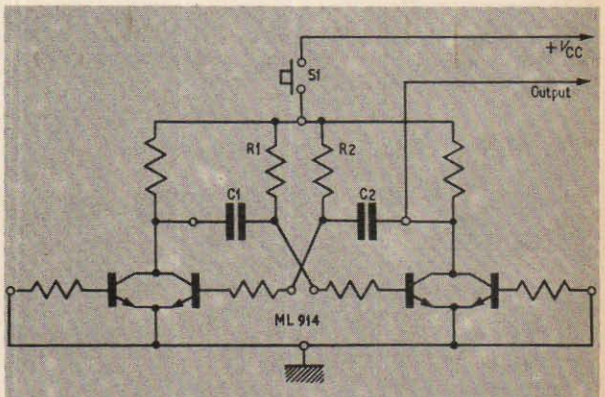



*Fig. 2.1. Clock pulse generator made up from two 2-input NAND gates with C1, C2, R1 and R2 added to make up an astable multivibrator. R1=R2=1kΩ. C1=C2=0·68μF*

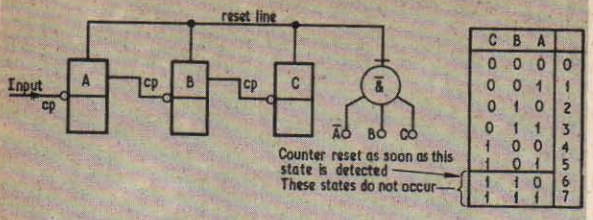



*Fig. 2.2a. Conventional ÷6 counter*

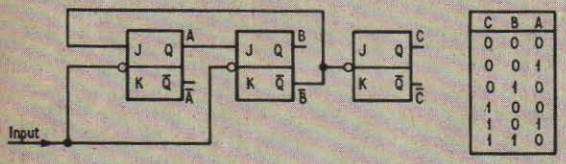



*Fig. 2.2b. This ÷6 counter is used in the dice system*

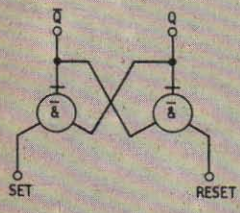



*Fig. 2.3a. Simple latch bistable*

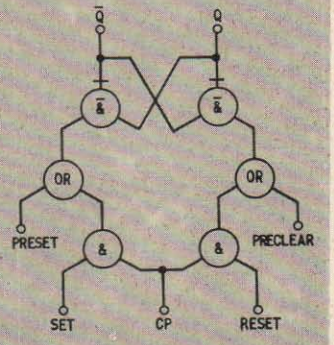



*Fig. 2.3b. Shift register bistable*

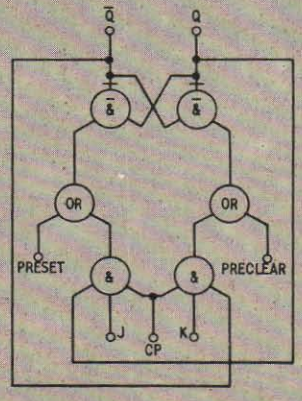



*Fig. 2.3c. Simplified logic diagram of a JK bistable*

## VERSATILE JK

Perhaps it might be as well to consider the way in which the JK has developed to become the "do-anything" device, suitable for use in memory circuits, shift registers, and various forms of counters, used in logic circuitry today.

The simplest form of bistable is the set/reset or latch, which is formed simply from two NAND or NOR gates, as in Fig. 2.3a. The inputs to this circuit must be complementary, and there is no provision for a clock input, so its use is limited and confined to simple memory applications.

The first step in improving the set/reset type is to add AND gates to the inputs, enabling information to be gated in synchronism with a clock pulse, which is common to both gates. The asynchronous inputs of the simple latch can be retained if required by adding an OR gate between the bistable and the AND gates. A circuit of this type is shown in Fig. 2.3b.

This is a useful circuit which may be used in shift registers, but the inputs must still be complementary to ensure proper operation. To enable the circuit to be self-complementing, feedback can be provided from the collector outputs of the bistable to the inputs of the AND gates, ensuring that if two "ones" are present at the inputs of the AND gates, the bistable will change state. This circuit is the basis of the JK flip-flop, and is shown in Fig. 2.3c.

It must be appreciated that this is a simplified representation, and there are some problems which have not been considered in this treatment.

## DICE COUNTER

The complete logic system of the electronic dice is shown in Fig. 2.4. A divide by three synchronous counter is made up from the JK flip-flops A and B. The third JK flip-flop C is a divide by two stage. The complete counter conforms to the truth table given in Fig. 2.2.

The decoding of the six separate states of the counter is likely to appear very complicated to those unfamiliar with the "dodges" which are often used in this type of circuitry. A knowledge of Boolean algebra is necessary to design such circuits, but a simple explanation will be given here. By using this in conjunction with the truth table a constructor should be able to sort out exactly what is going on.

The transistors used to drive the bulbs are also used as a form of AND gate. This is possible as a transistor requires both that its base be taken positive, and that its emitter be grounded, before it will turn on, assuming *npn* transistors are used.

Therefore, if we let bistable C control the grounding of the emitters of the bulb drivers, we can see from the truth table that output C is down for three counts. Output $\overline{C}$ is down for the other three counts, enabling the emitters of bulb drivers 1, 2 and 3 to be connected together and ground them through another transistor, whose base is controlled by the $\overline{C}$ output. Drivers 4, 5, and 6 can be similarly controlled by the C output.

Having dealt with the C bistable, A and B can be decoded having gone through two complete counts of three in any count of six. The bases of drivers 1 and 4, 2 and 5, 3 and 6 can be connected together in pairs and driven from the decoded states, which represent the three separate states of bistables A and B.

The decision as to whether 1 or 4, 2 or 5, 3 or 6 is illuminated is carried out by bistable C, switching on only one emitter of each pair.

# Laskys

## SCOOP Garrard 3000



### CUSTOM UNIT *BY FAMOUS BRITISH MANUFACTURER*

A deluxe custom styled and built record player unit made by world famous British manufacturer. The unit incorporates the renowned Garrard 3000 four speed autochanger with lightweight tubular pick-up arm FITTED WITH SONOTONE 9T/A STEREO CARTRIDGE with diamond stylus. The beautifully made plinth is finished in richly figured teak veneer with tinted perspex panels in the lid and with attractive charcoal grey "mirror" insert panel on front. All metal trim parts are in satin chrome. Blackleather grain underside. The lid allows the player to operate fully automatically when closed and has snap action "stay" when raised. Mains socket and 5 pin DIN audio output socket are at rear. Overall size 15½ × 7¼ × 14in.

*LASKY'S SPECIAL PRICE* **£16.15.0** Post 15/-

## SONICS AS-57


### *ELEGANT BUDGET PRICED BOOKSHELF SPEAKER SYSTEMS*



The AS-57 is a real space saver. This fine bookshelf high-fidelity speaker system will provide good quality sound anywhere in your home at remarkably low cost. Designed for use where space is at a premium, the AS-57 system is ideal for the small apartment or isolated area. The special high efficiency 5 × 7in. full range speaker has a frequency range of 70-18,000 Hz with a peak handling capacity of 10 watts. Imp. 8 ohms. Finish: oiled walnut. Size: 5½ × 15½ × 8½in.

*LASKY'S PRICE* **£15 per PAIR** Post 10/-

## EXCLUSIVE DIGITAL CLOCK SCOOP!

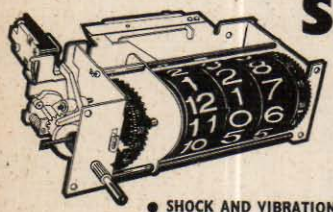

- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
- MAINS OPERATION
- 12-HOUR ALARM
- AUTO "SLEEP" SWITCH
- HOURS, MINUTES AND SECONDS READ-OFF
- FORWARD AND BACKWARD TIME ADJUSTMENT
- SILENT OPERATION SYNCHRONOUS MOTOR
- SHOCK AND VIBRATION PROOF
- BUILT IN ALARM BUZZER

This unique DIGITAL CLOCK is now available **EXCLUSIVELY FROM LASKY'S** in chassis form for you to mount in any housing that you choose.
All settings are achieved by two dual-concentric controls at the front including: ON-OFF-AUTO and AUTO ALARM, "sleep" switch, 10 minute division "click" set alarm (up to 12 hour delay), time adjustment. Ultra simple mechanism and high quality manufacture guarantee reliable operation and long life.
The sleep switch will automatically turn off any appliance—radio, TV, light etc. at any pre-set time up to 60 min. and in conjunction with the AUTO setting will switch on the appliance again next morning.
The clock measures 4¾W × 1¾ × 3¾D (overall from front of drum to back of switch). SPEC: 210/240V AC 50Hz operation; switch rating 250V, 3A. Complete with instructions, complete with full set of knobs. **HUNDREDS OF APPLICATIONS FOR THE ELECTRONICS HOBBYIST.**

*LASKY'S PRICE* **£6.19.6** POST 3/6

*SPECIAL QUOTATIONS FOR QUANTITIES*

## Garrard

FROM STOCK

### SP.25 Mk II

*THE U.K.'s MOST POPULAR HI-FI TURNTABLE*



4-speed single record playing deck features include: heavy precision-built turntable, pick-up arm bias compensation, calibrated stylus-force adjustment, cueing device. After play, the arm automatically rises, returns to rest and switches off motor. Finish: dark green polychromatic and silver.

*LASKY'S PRICE* **£11.19.6**

SP 25 Mk. II with A.D. 76K Stereo Magnetic Cartridge **£15 10 0**

*OTHER GARRARD UNITS FROM STOCK*

AUTOCHANGERS

| | | | |
|---|---|---|---|
| SL72B | £25 0 0 | SL65B | £15 10 0 |
| 2025TC with stereo cartridge | £8 17 6 | SL95B | £35 0 0 |
| 3000 complete with STAHC stereo cartridge | £9 19 6 | SL75B | £28 0 0 |

SINGLE PLAYERS
AP 75, **£18.10.0.** AP75 with AD76K mag. cart., **£21.10.0.** 401 Transcription Unit **£20.0.0.**

BASES AND COVERS FOR GARRARD UNITS
Type WB1 and WB5 for models 2025TC, 3000, SL65B 1025. SP25 Mk II Price WB1 **£3.16.6.** WB5 **£5.12.6.** Type WB4 for models SL72B, SL75B, SL95B Price **£5.12.6.** Perspex covers: SPC1 for WB1. **£3.14.1.** SPC4 for WB4 and WB5 (allows unit to be played with the cover in place)—price **£4.8.0.**

### PACKAGE DEALS

AP75 complete with AD76K Stereo magnetic cartridge teak plinth and perspex cover **£30.0.0** Post 10/-
SP25 Mk II complete with AD76K cartridge, teak plinth and perspex cover **£19.0.0** Post 7/6
1625 complete with J2108 stereo ceramic cart., teak plinth and perspex cover **£11.19.6** Post 7/6
Post on Garrard units: 6/- extra—except AP75, SL75B, SL95B and 401 7/6 extra. Post on bases and covers 5/- extra.

### SPECIAL OFFER—BSR UA-15

**4 speed autochangers with modified tubular tone arm. Comp. with stereo cart. £6.19.6.** Post 5/-

## Audio Tronics 70

The 1970 edition of Lasky's famous Audio-Tronics catalogue is available FREE on request. The 28 tabloid pages many in full colour are packed with 1000's of items from the largest stocks in Great Britain of everything for the Radio and Hi-Fi enthusiast, Electronics Hobbyist, Servicemen and Communications Ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals). Tape recording and Audio accessories plus Lasky's amazing money saving vouchers worth over £25.

**SEND TODAY.** *Send: Your name, address and 2/- for the post and inclusion of your name on our regular mailing list.*

*THIS MONTH'S VOUCHERS WORTH 50/-*

## Lasky's Radio Limited

207 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 3271
33 TOTTENHAM CT. RD, LONDON, W1P 9RB. Tel: 01-636 2605
Open all day. 9 a.m.–6 p.m. Monday to Saturday
109 FLEET STREET, LONDON, E.C.4. Tel: 01-353 5812
152/3 FLEET STREET, LONDON, E.C.4. Tel: 01-353 2833
Open all day Thursday, early closing 1 p.m. Saturday

*HIGH FIDELITY AUDIO CENTRES*
42-45 TOTTENHAM CT. RD, LONDON, W1P 9RD. Tel: 01-580 2573
Open all day. 9 a.m.–6 p.m. Monday to Saturday
118 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 9789
Open all day Saturday early closing 1 p.m. Thursday

hfda member

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E1 2BN Tel: 01-790 4821

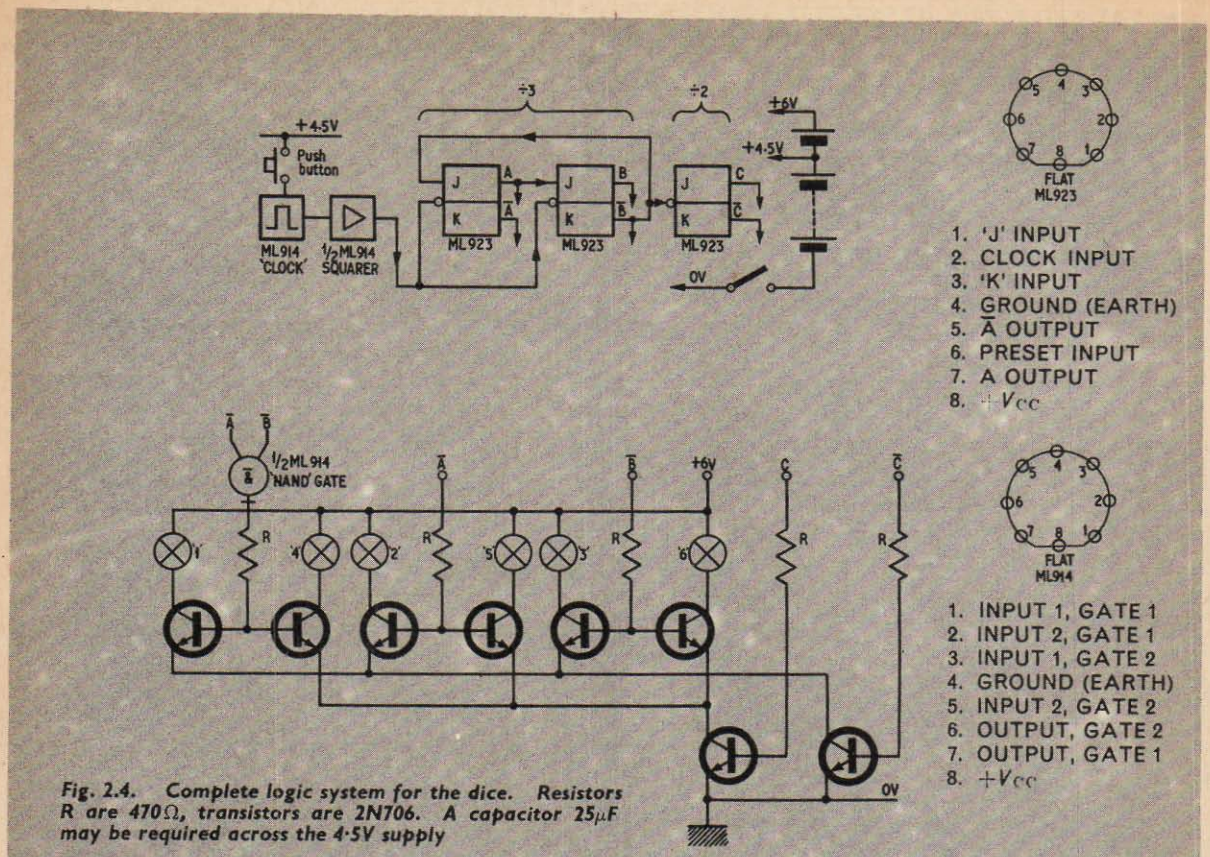



*Fig. 2.4. Complete logic system for the dice. Resistors R are 470Ω, transistors are 2N706. A capacitor 25μF may be required across the 4·5V supply*

The decoding of each of the three states of A and B is rendered simple by the type of counter employed. The first state has to be described in terms of A and B, but states 2 and 3 are described merely by deciding whether the A output or the B output is "up". A gate is only necessary to decode counts 1 and 4; counts 2 or 5 can be driven by the NOT output of bistable A, as this is positive only during these two states. Similarly, counts 3 and 6 can be driven by the $\bar{B}$ output.

The gate used to decode the first stage of the counter uses half of an ML914, used as a 2-input negative logic NAND gate, its inputs being A and $\bar{B}$, which are both negative at a count of one only.

As a bit of light relief, let us see what has happened to the spare half of the ML914, left over from the decoding circuit. It is in fact being used as an amplifier, with both its inputs connected together, to square up the edges of the clock waveform.

This is necessary, as the JK flip-flop needs a very fast negative edge on the clock input, for it to operate correctly; our clock multivibrator cannot be relied upon to produce such edges.

## PRACTICAL DETAILS

This completes the circuit description, except for a few practical details. The supply voltage used poses a bit of a problem, the RTL i.c.s. specified are designed for a supply voltage of 3·6 volts. Since this is not easily obtained from dry batteries, a compromise is used of 4·5 volts, and an extra cell is used to boost this to 6 volts for the bulb circuitry.

The bulbs used must be low consumption types, requiring in the region of 50mA at 6V. Although they will be slightly under-run, due to the saturation voltages of the two driver transistors appearing in series with each of them, this is not a bad thing from the point of view of reliable readout.

The actual layout of the circuit can be safely left to the constructor, as there are no special problems involved, but perhaps a few hints would be useful. There are several kinds of perforated baseboard suitable for the support of this kind of circuit on the market. Veroboard is one which can be used for this particular application.

Using this type of board in the 0·1in matrix size the integrated circuits can be directly inserted, but due to the component density, a good deal of the connections will have to be made using "jumper" wires to realise a compact unit.

The i.c. leads can be left at least ½in long, if desired, but to be sure of re-use of the i.c.s, Lektrokit board can be used. In this case a ring of terminal pins can be used for the i.c.s, which can be mounted upside down on the board, wiring being carried out underneath.

A miniature soldering iron is a virtual necessity when working on this sort of layout, unless the constructor possesses a very steady pair of hands.

The completed unit can be accommodated in a small plastics box, the only controls being the on/off switch, the push button, and a row of six miniature lamp holders.

Next month's article in this series will look into Diode Transistor Logic or DTL.

# LIND-AIR AUDIO

## E.M.I. COMBINATION LOUD-SPEAKERS



13½in × 8in elliptical tweeters; 8 ohm impedance; power handling 10W. Brand new guaranteed. **Lind-Air Price 89/6** P. & P. 7/6

## HI-TONE RECORDING TAPE

BRITISH MADE TOP QUALITY

| | | | | | |
|---|---|---|---|---|---|
| J1001 | 3in | L.P. | PVC | 225ft | 5/6 P. & P. 1/2 |
| J1002 | 3in | T.P. | Poly | 600ft | 10/6 P. & P. 1/2 |
| J1003 | 5in | L.P. | PVC | 900ft | 10/- P. & P. 1/8 |
| J1004 | 5in | D.P. | Poly | 1,200ft | 15/- P. & P. 1/8 |
| J1005 | 5¾in | L.P. | PVC | 1,200ft | 12/6 P. & P. 2/- |
| J1006 | 5¾in | D.P. | Poly | 1,800ft | 22/6 P. & P. 2/- |
| J1007 | 7in | S.P. | PVC | 1,200ft | 12/6 P. & P. 2/6 |
| J1008 | 7in | L.P. | PVC | 1,800ft | 17/6 P. & P. 2/6 |
| J1009 | 7in | D.P. | Poly | 2,400ft | 25/- P. & P. 2/6 |
| J1010 | 7in | T.P. | Poly | 3,600ft | 50/- P. & P. 2/6 |
| C60 | Cassette (Library cased) | | | | 8/6 P. & P. 1/- |
| C90 | Cassette (Library cased) | | | | 13/- P. & P. 1/- |
| C120 | Cassette (Library cased) | | | | 18/- P. & P. 1/- |




## DE-LUXE STEREO HEADPHONES



With soft rubber earpieces. Impedance 8–16ohms. Frequency response 23–13,000Hz. With lead and stereo plug. **Only 59/6.** P. & P. 3/6.

## VHF AIRCRAFT BAND CONVERTOR

When placed within 1in of a MW band radio full coverage of VHF Aircraft Band 108–135Me/s can be obtained. All transistor. 9V battery operation. Fully tunable 18¼in × 7 section telescopic aerial. Size 4 × 2½ × 1¼in. **79/6.** P. & P. 3/6.



## C.1001 MULTI-TESTER



Overload protection 20,000 ohms per volt; a.c. volts 10, 50, 250, 1,000V; d.c. volts 5–25, 125; 500, 2,500V; d.c. current 0—50μA, 0—250mA; Resistance 0—60kΩ 0—6MΩ; decibels —20 to +22dB. Size of meter 4¼in × 3¼in × 1in. Complete with leather case. **85/-**, P. & P. 3/6.


## NEW! STP.800 8-TRACK STEREO CARTRIDGE HOME PLAYER

TELETON STP.800 8-TRACK STEREO CARTRIDGE HOME PLAYER
A complete solid state unit ready to plug in and play. Hi-Fi reproduction at 3¾ i.p.s. Player unit incorporates volume, tone and balance controls and push-button track selector. Size 14¼in × 10¼in. Matched speakers, size 11in × 8in × 5¼in each.




**LIND-AIR PRICE**
**49 Gns.** Carr. 30/-

## S-DEC BREADBOARD

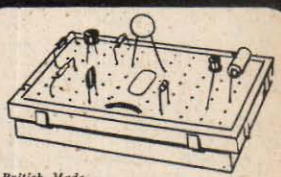

*British Made*
Solderless breadboard panels, for fast reliable component connections.
Single DeCs. One S-DeC with Control Panel, Jig and Accessories for solderless connections to controls, etc., with booklet "Projects on S-DeC" giving construction details for a variety of circuits. **29/6.** P. & P. 2/6.
4-DeC KIT. Four S-DeCs with two Control Panels, Jigs and Accessories and the booklet "Projects on S-DeC" all contained in a strong attractive plastic case. Ideal for the professional user. **£5.17.6.** P. & P. 3/6.
T-DeC KIT **£5.17.6.** P. & P. 3/6.

## 62.D. MULTI-TESTER




20,000 ohms per volt; d.c. voltage 5, 25, 50, 250, 500V, 2·5kV (20,000 ohms per volt), a.c. voltage 10, 50, 100, 500, 1,000V (10,000 ohms per volt); d.c. current 0–50μA, 0–2·5mA, 0–250mA; resistance 0–6kΩ, 0–6MΩ (300 ohms and 30kΩ at centre scale); capacitance 10F to 0·001mF, 0·001μF to 0·1μF; decibels —20 to +22dB. Size 4¼in × 3¼in × 1in. **71/-**. P. & P. 3/6.

## WHARFEDALE SPEAKER KITS



Complete with all components for building into suitable cabinets.
Unit 3 Kit ..... **£11.19.6** each
**£21** pair
Unit 4 Kit ..... **£16.0.0** each
**28 Gns.** pair
Unit 5 Kit ..... **£23.10.0** each
**39 Gns.** pair
P. & P. 10/- each, 15/- pair
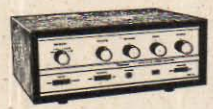
## TELETON SAQ203 TRANSISTOR STEREO AMPLIFIER



Superb quality hi-fi. 10W per channel music power. Inputs for gram (magnetic and crystal), tuner and auxiliary. Tape record output. Controls: volume, balance, bass, treble. Attractive oiled walnut cabinet with brushed aluminium front panel.
List Price £28.7.0.
**Our Price 22 Gns.**
P. & P. 10/-.

## LIND-AIR LA.20



A fantastic stereo amplifier made exclusively for Lind-Air and represents considerable advance in solid state stereo amplifiers. Inputs for gram and radio tuner and provision for direct tape recording. Attractive and modern panel with bass, treble balance and volume controls also on/off and stereo/mono switch. Output 5W per channel music power. Frequency response 40-20,000Hz 8-16 ohm speaker matching. Size 16¼in × 14in × 4in.

**LIND-AIR PRICE £24** P. & P. 10/-

## SAVE ON AKAI!



AKAI 4000 Stereo Tape Recorder.
List Price £124.18.0.
**Our Price 99 Gns.**
Carr. 30/-

AKAI 4000D STEREO TAPE DECK. (As illus.)
List Price £89.19.1.
**Our Price 69 Gns.**
Carr. 30/-

## SPECIAL LIND-AIR OFFER!

### ROTEL 100 AMP STEREO AMPLIFIER



Fully transistorised with all facilities for the home hi-fi system.
List price £45
**Our Price £37.10.0**
Carr. 10/-

## Garrard HI-FI TURNTABLES



| | |
|---|---|
| 2025 T/C with stereo cartridge | £8.19.6 |
| 3000 with Sonotone 9TAHCD stereo cartridge | £10.19.6 |
| SP25 Mk. II | £10.19.6 |
| SL65B | £15.19.6 |
| Base and cover for above | £5.19.6 |
| AP75 | £18.10.0 |
| SL72B | £24.19.6 |
| SL75B | £28.7.0 |
| SL95B | £39.9.0 |
| 401 | £28.10.0 |
| Base and cover for above | £8.19.6 |

P. & P. Decks, 12/6; Base and Cover, 10/–; Deck/Base/Cover, 17/6.

**SPECIAL OFFERS!**

| | |
|---|---|
| SP25 Mk. II with base | £14.10.0 |
| | P. & P. 15/- |
| SP25 Mk. II with Sonotone 9TAHCD cartridge and base | £15.15.0 |
| | P. & P. 15/- |
| Sonotone 9TAHCD cartridge | £2.15.0 |
| | P. & P. 1/6 |

## SINCLAIR IC-10 INTEGRATED CIRCUIT

10W Amplifier. Size only 1in × 0·4in × 0·2in. A true hi-fi amplifier complete with manual giving details of a wide range of applications and instructions. Guaranteed 5 years. **ONLY 59/6.** P. & P. 1/6.

**SPECIAL TRANSFORMER FOR OPERATING SINCLAIR IC-10** from a.c. mains 230/250V. Output 13V at 0·5A, **16/6.**

**18/19,25 & 53 TOTTENHAM CT. ROAD, LONDON W.1.**
**Telephone: 01-580 2255/4532/7679**
**Open 9-6 pm. Monday to Saturday. Thursday until 7 pm.**

**All Mail Orders and correspondence to Dept L4/8, Kirkman House, 54a Tottenham Court Road, London, W.1. Tel: 01-580 7041/2.**

**HOME RADIO (Components) LTD.**
**Dept. PE**
**234 London Road, Mitcham CR4 3HD**
Telephone 01-648 8422




**A** Purchase a Home Radio Catalogue, using the Coupon below. Please enclose a cheque or postal order for 12/6 (8/6 plus 4/- packing and postage). Your catalogue will be sent by return of post.

**B** Choose your components. In the Home Radio Catalogue over 8,000 components are listed and more than 1,500 illustrated. A comprehensive index helps you to locate your requirements easily.

**C** Join our Credit Account Service. Full details are enclosed with every catalogue.

**D** Order your components. Having joined our Credit Account Service, you may order either by phone or post. If you phone out of office hours, a recording machine takes your message.

**E** Get started on that project! Whether it's constructing or servicing work, the fact that you can obtain the right components easily, without having to chase from shop to shop, will put you in the right frame of mind to make a better job of it.




Whether or not you want to use the Credit Account Service mentioned above, you certainly need the Home Radio Components Catalogue, if you construct or repair radio, television and electronic gadgets. By the way, the catalogue contains six vouchers, each worth a shilling when used as instructed, and with the catalogue we supply a 30-page Price Supplement and a Bookmark giving electronic abbreviations.

**Post the Coupon today, with 12/6.**

*The price 12/6 applies only to catalogues purchased by customers residing in the U.K.*

*Please write your Name and Address in block capitals*

Name.....

Address.....

.....


**HOME RADIO (Components) LTD.**
**Dept. PE, 234-240 London Road, Mitcham CR4 3HD**

# Never Built a Kit Before?

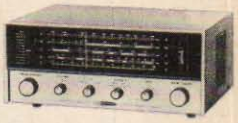**Why not prove how easy it is the HEATHKIT way. Build one of these beginner kits.**



**Stereo Record Player**
**Kit: K/SRP-1 - - £27.6.0**
Carr. 11/-



**Economy SW Receiver**
**Kit: K/GR-64 - £24.16.0**
Carr. 9/-



**Deluxe Car Radio**
**Kit: K/CR-1 (less Spks.) £12.12.0**
Carr. 5/-

**Versatile Service 'VVM'**



**Kit: K/IM-18U - £16.14.0**
Carr. 5/-



**'SEVERN' AM/FM Radio**
**Kit: K/SEVERN - £18.18.0**
Carr. 5/-



**Car Tune-up Meter**
**Kit: K/ID-29 - £17.8.0**
Carr. 5/-




**Model Builder's Tacho**
**Kit: K/GD-69 - - £11.0.0**
Carr. Paid



**D.I.Y. 2-Speaker System**
**Kit: K/SCM-3 (less cab.) £12.6.0**
Carr. 6/-

Many more kits in the FREE CATALOGUE
★ **Please send me FREE Catalogue**
**NAME**.....
**ADDRESS**.....
.....
25/8 ..... **POST CODE**.....

HEATHKIT
*A. Schlumberger Company*

**HEATH (GLOUCESTER) LTD.**
**GLOUCESTER GL2 6EE**

# TRANSISTOR D.C. MULTIMETER

By W. CLELAND

In this, the final part of the "Transistor D.C. Multimeter", we give mounting details of the components and boards inside the diecast case, final wiring details and setting up instructions.

## CASE DETAILS

The multimeter is housed in a diecast case of outside dimensions $8\frac{3}{4}$in × $5\frac{3}{4}$in × $2\frac{5}{32}$in. The box is used upside down, since the screws of the lid prevent the lid from being used as the top panel. The lid, therefore, becomes the underside of the instrument, to which four rubber feet are screwed, and the bottom of the box makes a satisfactory top panel. Top panel dimensions are $\frac{1}{16}$in less than the overall dimensions, because, with a diecast box, the sides taper slightly inwards. When drilled, as in Fig. 9, the case is painted to protect it; paint has to be removed from openings and from the edges and interior of the case when dry.

The neon signal lamp is mounted just under the edge of M1 and is raised $\frac{1}{8}$in, by fitting a piece of black Bakelite under it as shown in Fig. 10. This is positioned on the top panel between the milliammeter and the Perspex switch escutcheon. On final assembly, the signal lamp is fastened from the inside, by pushing on a spire nut, over the plastic lampholder.

## SWITCH ESCUTCHEON

The Perspex switch escutcheon is shaped to fit between the signal lamp and terminals, and is dimensioned as shown in Fig. 11. Two $\frac{3}{4}$in diameter holes enable it to fit around the nuts securing the range switches, and it is held in place by two 8B.A. countersunk screws. These are situated under the knobs of the range switches.

To set the switch knobs accurately, a small depression has to be drilled in the shaft for the grub screw. The smooth end of the grub screw can be scored with a file, so that the grub screw will leave a mark on the shaft at the required position. An indentation is made on this spot with a small drill.

***NOTE: It is recommended that a suitable meter be obtained before drilling the box. Modifications to layout and drilling may be necessary to accommodate other meters such as the MR-65P***

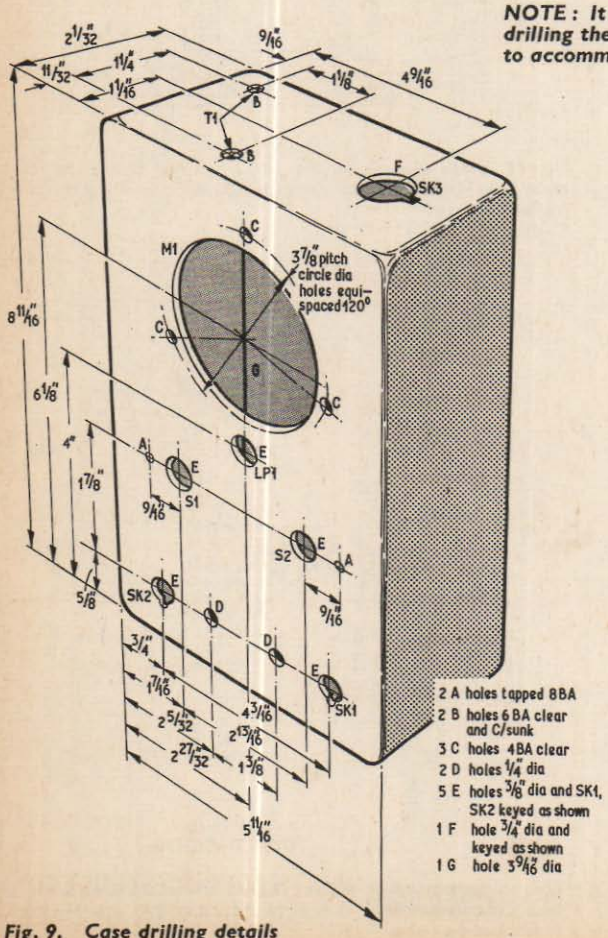



*Fig. 9. Case drilling details*

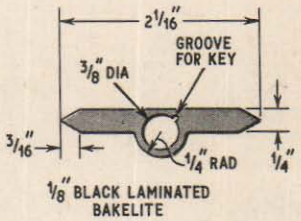



*Fig. 10. Signal lamp surround*


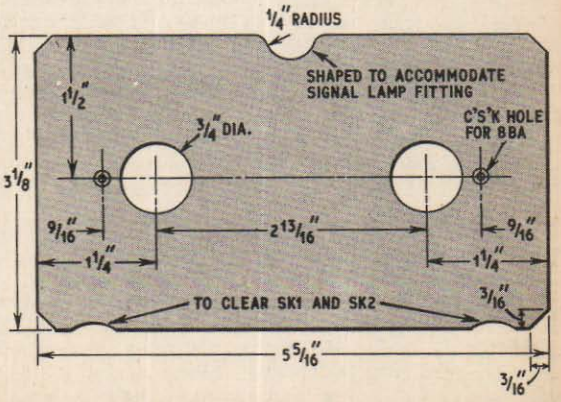



*Fig. 11. Perspex switch escutcheon*

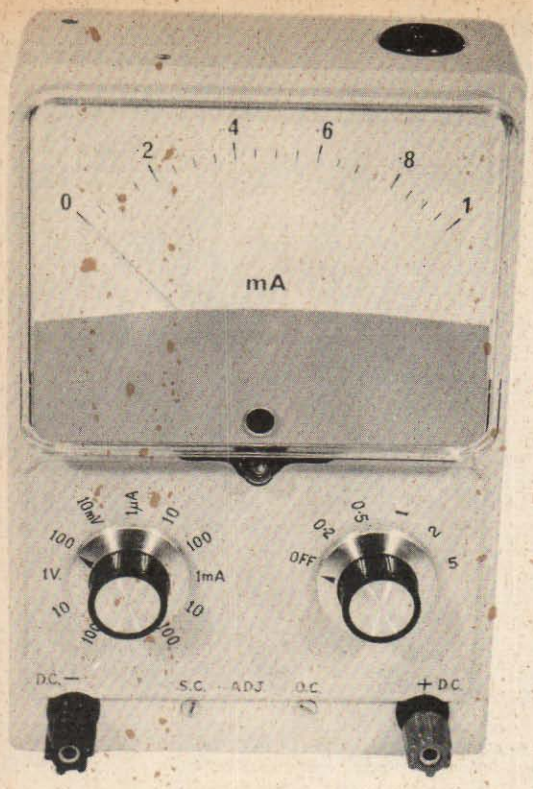


Adequate clearance has to be ensured between the knobs and the Perspex escutcheon. The escutcheon can be marked, as shown in the photograph, to give switch positions and potentiometer designations.

## MAINS WIRING

The metal case of the testmeter has to be earthed to the mains earth via SK3. *The circuit of the testmeter is in no way connected to the metal case or to mains earth.*

The insulated mounting for the miniature mains transformer T1 (Fig. 12) insulates it from the metal case, and provides a junction box for the transformer connections. The p.v.c. insulation of the connecting leads is carried into the insulated mounting, which consists of three rectangular pieces of insulating material sandwiched together. Parts B and C are of $\frac{1}{8}$in laminated Bakelite, and can be bonded with adhesive. These are bolted at two corners to part A, which is of $\frac{1}{16}$in material. A pair of 6 B.A. countersunk bolts at the other corners, secure the mounting to the inside of the case.

The insulated leads from the signal lamp are hardly long enough to reach the mains switch S26, and to avoid running these wires very close to the range resistors, it is necessary to increase the length of the existing leads.

Details are given in Fig. 13 of a special insulated cover for the mains switch, which ensures safety if tests have to be made on the low voltage wiring with the unit turned on. All the mains wiring is double insulated, by wrapping each pair of p.v.c. covered wires with cloth insulation tape, avoiding an excessive thickness.

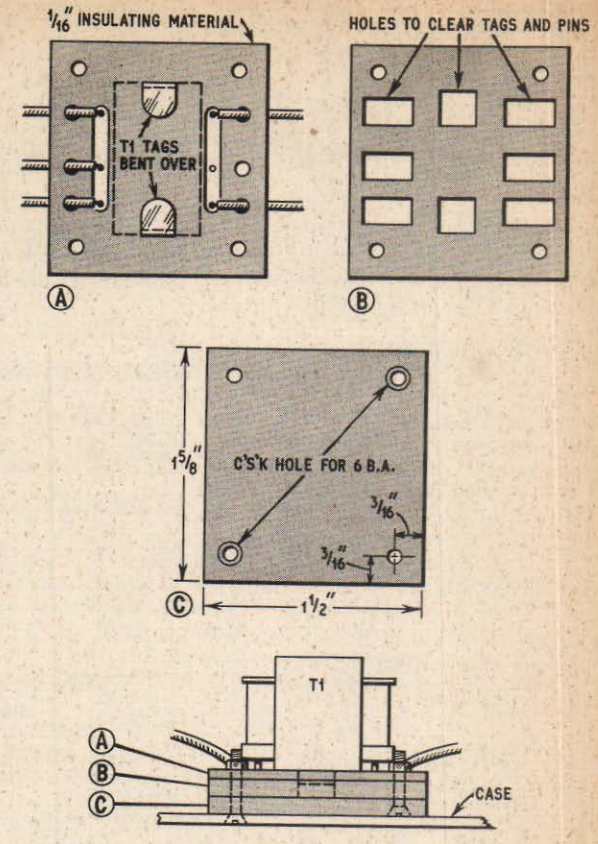



***Fig. 12. Insulated mounting for T1, holes are arranged to clear transformer tags. Sections B and C are $\frac{1}{8}$in thickness Bakelite***

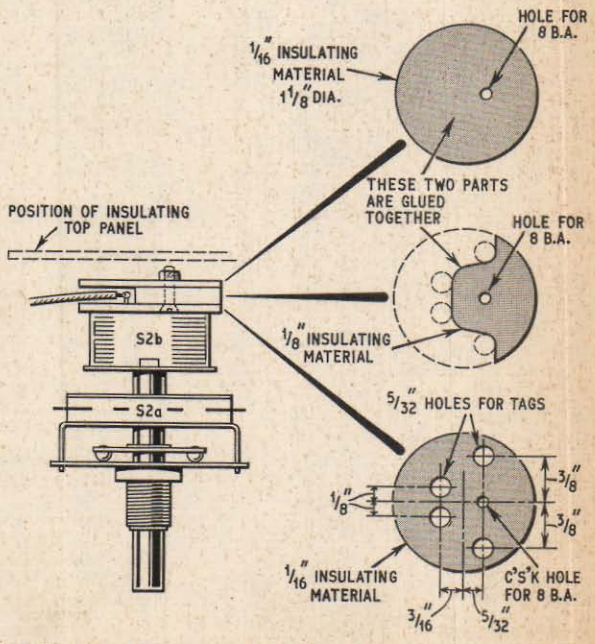



***Fig. 13. Insulated cover for S2b. The lower section with the screw in position should be fitted before the wiring is connected to the switch***

## BSR 4-SPEED SUPERSLIM AUTO RECORD CHANGER



Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. Size 13½ × 11½in. Above motor board 3½in. below 2½in. AC 200/250v.

with STEREO/MONO XTAL **£6.19.6** Post 5/6

BSR UA70 Stereo/Mono Transcription Auto Changer. Calibrated Stylus Pressure. **£12.19.6**

BSR Minichanger UA50 Stereo/Mono. Size 12 × 8½in. AC 200/250v. Post 5/6. **£7.19.6**

GARRARD PLAYERS with Sonotone 9TA Cartridges. Stereo Diamond/Mono Sapphire. SP25 Mk II £14.19.6. AT60 Mk II £14.19.6. Model 3000 £12.19.6. Post 5/6.

RECORD PLAYER PORTABLE CABINET Space for amplifier and autochanger.' Post 5/-. **75/-**

RCS DE-LUXE 3 WATT AMPLIFIER. Ready made and tested. A 2-stage unit using triode pentode valve, giving 3 watts output. Tone and volume controls. Isolated mains transformer. With knobs, loudspeaker and valves ECL82, EZ80. Frequency response 50-12,000 cps. Sensitivity 200mV. Post 5/6. **89/6**

R.C.S. TEAKWOOD BASE Ready cut out for mounting (state player make and model). **77/6**

R.C.S. PLASTIC COVERS FOR ABOVE BASE. Durable tinted plastic, attractive appearance. **77/6**

EMI PICK-UP ARM. Complete with mono cartridge 29/6.


EMI JUNIOR 4 SPEED RECORD PLAYER Mains operated motor, turntable and pick up complete. Post 5/6. **59/6**

HI-FI PICK UP CARTRIDGES
GP94 55/-; GP93 45/-; GP91 30/-; GP67 19/6, ACOS L.P. only 10/6. All standard fixing complete with stylus.

### CRYSTAL MIKE INSERTS

1½" dia. 6/6. ACOS 1½" dia. 12/6. BM3, 1" dia. 9/6

## PORTABLE AMPLIFIER

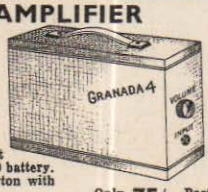


Portable mini p.a. system. Many uses — ideal for Parties, or as a Baby Alarm, Intercom, Telephone or Record Player Amplifier, etc. Attractive rexine covered cabinet, size 12 × 9 × 4in., with powerful 7 × 4in. speaker and four transistor one watt power amplifier. Uses PP9 battery. Brand new in Makers' carton with full makers' guarantee. World famous make.

Only **75/-** Post 5/-

### WEYRAD P50 — TRANSISTOR COILS

| | |
|---|---|
| RA2W Ferrite Aerial .. 12/6 | Spare Cores ..... 6d. |
| Osc. P50/1AC ..... 5/4 | Driver Trans. LFDT4 .. 9/6 |
| I.F. P50/2CC 470 kc/s .. 5/7 | Printed Circuit, PCA1 .. 9/6 |
| 3rd I.F. P50/3CC ..... 6/- | J.B. Tuning Gang .... 10/6 |
| P51/1 or P51/2 ..... 5/7 | Weyrad Booklet ..... 2/- |
| P51/3 ..... 6/- | OPT1 ..... 10/6 |
| Ferrite Rod 8 × ⅜in. 4/-. 6 × ½in. 5/- | |

## VOLUME CONTROLS

Long spindles. Midget Size 5 K. ohms to 2 Meg. LOG or LIN. L/S 3/-. D.P. 5/- STEREO L/S 11/-. D.P. 15/- Edge 5K. S.P. Transistor, 5/-.

## 80ohm Coax 9d. yd.

BRITISH AERIALITE AERAXIAL-AIR SPACED FRINGE LOW LOSS **2/-** yd. Ideal 625 lines

WIRE-WOUND 3-WATT POTS. Small type with small knob. Values 10 Ω to 30 K., Carbon 30 K to 2 meg. **5/-**

WIRE-WOUND 3-WATT STANDARD SIZE POTS. LONG SPINDLE 10 OHMS to 100 K. **8/-**

VEROBOARD 0·15 MATRIX
2½ × 5in. 3/8. 2½ × 3½in. 3/2. 3½ × 3½in. 3/8. 3½ × 5in. 5/2.
EDGE CONNECTORS 16 way 5/-; 24 way 7/6.
PINS 36 per packet 3/4. FACE CUTTERS 7/6.
S.R.B.P. Board 0·15 MATRIX 2½in. wide 6d. per 1in., 3½in. wide 9d. per 1in.; 5in. wide 1/- per 1in. (up to 17in.).
S.R.B.P. undrilled ½in. Board 10 × 8in. 3/-.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2½in. sides, 7 × 4in., 6/-; 11 × 3in., 7/6; 11 × 7in. 9/6; 13 × 9in., 10/6; 15 × 14in., 15/-; 9 × 7 × 2in., 8/6; 14 × 11 × 2in., 14/6.

ALUMINIUM PANELS 18 s.w.g. 12 × 12in. 6/6; 14 × 9in. 5/6; 12 × 8in. 4/6; 10 × 7in. 3/6; 8 × 6in. 2/6; 6 × 4in., 1/6.

1½inch DIAMETER WAVE-CHANGE SWITCHES. 2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way 4/6 each. 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way 4/6 each.
¼ inch DIAMETER Wavechange "MAKITS" 1 p. 12-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 6 p. 2-way. 1 wafer 12/-, 2 wafer 18/-, 3 wafer 24/-, 4 wafer 30/-, 5 wafer 36/-.
TOGGLE SWITCHES, sp. 2/6; sp. dt. 3/6; dp. 3/6; dp. dt. 4/6

### ALL PURPOSE HEADPHONES

| | |
|---|---|
| H.R. HEADPHONES 2000 ohms Super Sensitive .. | 35/- |
| LOW RESISTANCE HEADPHONES 3-5 ohms .... | 39/6 |
| DE LUXE PADDED STEREO PHONES 8 ohms .. | 79/6 |

## "THE INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER



**42/6** Post 2/6

200/250 v. A.C. Leaflet S.A.E.

*Minimum Post and Packing 2/6.*

★ GENERAL PURPOSE TRANSISTOR PRE AMPLIFIER BRITISH MADE ★

for Mike, Tape, P.U., Guitar.

Battery 9-12v. or H.T. line 200-300v. D.C. operation. Size 1¾" × 1¼" × ¾". Response 25 c.p.s. to 25 Kc/s, 26 db gain. For use with valve or transistor equipment. Full instructions. Brand new. Guaranteed. Details S.A.E. **17/6 each**

| NEW TUBULAR ELECTROLYTICS | | CAN TYPES | |
|---|---|---|---|
| 2/350V .. 2/6 | 100/25V .. 2/- | 16+16/500V | 11/- |
| 4/350V .. 2/6 | 250/25V .. 2/6 | 50+50/350V | 7/- |
| 8/450V .. 2/6 | 500/25V .. 3/- | 60+100/350V | 11/6 |
| 16/450V .. 3/- | 8+8/450V 3/6 | 32+32/250V | 3/6 |
| 32/450V .. 4/- | 8+16/450V 4/- | 32+32/450V | 6/6 |
| 25/25V .. 2/- | 16+16/450V 5/- | 32+32+32/350v. | 8/6 |
| 50/50V .. 2/- | 32+32/350V 5/- | 100+50+50/350v. | 9/6 |

SUB-MIN. ELECTROLYTICS. 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 2/-; 500, 1000mF 12V 3/6; 2000mF 25V 7/-.
CERAMIC. 1pF to 0.01mF, 9d. Silver Mica 2 to 5000pF, 9d.
PAPER 350V-0·1 9d. 0·5 2/6; 1mF 3/-; 2mF 150V 3/-.
500V-0·001 to 0·05 9d; 0·1 1/-; 0·25 1/6; 0·47 5/-.
1,000V-0·001, 0·0022, 0·0047, 0·01, 0·02, 1/6; 0·047, 0·1, 2/6.
SILVER MICA. Close tolerance 1%. 2·2-500pF 1/6; 560-2,200pF 2/-; 2,700-5,600pF 4/-; 6,800pF-0·01, mfd 6/-; each.
TWIN GANG. "0-0" 208pF+176pF, 11/-. Slow motion drive 365pF+385pF with 25pF+25pF, 11/-; 500pF slow motion, standard 9/-; small 3-gang 500pF 22/-.
SHORT WAVE. 25pF, 11/-.
CHROME TELESCOPIC AERIALS 23in. 5/-.
TUNING. Solid dielectric. 100pF, 300pF, 500pF, 7/- each.
TRIMMERS. Compression 30, 50, 70pF, 1/-; 100pF, 150pF, 1/6; 250pF, 1/6; 800pF, 750pF, 2/-; 1000pF, 2/6.
RECTIFIERS CONTACT COOLED ½wave 60mA 7/6; 85mA 9/6. SILICON BYZ13 6/-; BY100 10/-.
Full wave Bridge 75mA 10/-; 150mA 19/6; TV rects. 10/-.
NEON PANEL INDICATORS 250v. AC/DC Red. Amber 4/-.
RESISTORS. Preferred values, 10 ohms to 10 meg. ¼ w., ½ w., 1 w., 20% 3d.; 1½ w. 8d.; 2 w. 1/-; ½ w. 10% 6d.
HIGH STABILITY. ½ w. 1% 10 ohms to 10 meg., 2/-. Ditto 5%. Preferred values 10 ohms to 22 meg., 9d.
WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K. 2/- each; 2½ watt. 1 ohm to 8·2 ohms. 2/-

## Q MAX CHASSIS CUTTER

Complete: a die, a punch, an Allen screw and key
⅛in. 16/- ¼in. 17/6 1¼in. 19/6 1½in. 24/- 2⅜in. 44/3
¼in. 16/- 1in. 19/6 1¼in. 20/6 1½in. 29/- 2½in. 57/3
⅛in. 16/9 1⅛in. 19/6 1¼in. 21/6 2in. 39/- 1in. sq. 36/6

TRANSISTOR MAINS POWER PACKS. FULL WAVE 9 volt 500mA. Size 4½ × 2½ × 2in. Metal case. Crackle finish. Output terminals. On/off switch. Half Wave 9 volt 50mA. Size 2½ × 1¼in. Snap terminals **49/6** 32/6

## MAINS TRANSFORMERS

| | Post 5/- each |
|---|---|
| 250-0-250 50 mA. 6.3 v. 2 amps, centre tapped | 19/6 |
| 250-0-250 80 mA. 6.3 v. 4 amp. | 28/- |
| 250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a, or 5 v. 2 a. | 38/- |
| 350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a, or 5 v. 2 a. | 38/- |
| 300-0-300 v. 120 mA., 6.3 v. 4 a. C.T.; 6.3 v. 2 a. | 45/- |
| MINIATURE 200 v. 20 mA., 6.3 v. 1 a. 2½ × 2 × 1¼in. | 15/- |
| MIDGET 220 v. 45 mA., 6.3 v. 2 a. 2½ × 2½ × 2in. .. | 17/6 |
| HEATER TRANS. 6.3 v. 1½ a., 10/6; .. 6.3 v. 4 a. | 15/6 |
| Ditto tapped sec. 1.4 v., 2, 3, 4, 5, 6.3 v. 1½ amp. .. | 15/6 |
| GENERAL PURPOSE LOW VOLTAGE. Outputs 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. at 2 a. ..... | 38/- |
| 1 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60. | 38/- |
| AUTO TRANSFORMERS 0-115-230 v. Input/Output, 60w. 18/6; 150w. 38/-; 500w. £5; 1000w. £12. | |
| CHARGER TRANSFORMERS. Input 200/250v for 6 or 12v., 1½ amp., 24/-; 4 amp., 38/-. | |
| FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v. outputs. 1½ amp. 8/-; 2 amp. 11/-; 4 amp. 17/-. | |

COAXIAL PLUG 1/3, PANEL SOCKETS 1/3. LINE 3/6. OUTLET BOXES. SURFACE OR FLUSH 5/-.
BALANCED TWIN FEEDERS 1/- yd. 80 ohms or 300 ohms.
JACK SOCKET Std. open-circuit 2/6, closed circuit 4/6; Chrome Lead Socket 7/6. Phono Plugs 1/-. Phono Socket 1/-.
JACK PLUGS Std. Chrome 3/-; 3·5mm Chrome 2/6. DIN SOCKETS Chassis 3-pin 1/6; 5-pin 2/-. DIN SOCKETS Lead 3-pin 3/6; 5-pin 5/-. DIN PLUGS 3-pin 3/6; 5-pin 5/-.
VALVE HOLDERS, 9d.; CERAMIC 1/-; CANS 1/-.



## E.M.I. 13½ × 8in. LOUDSPEAKERS

With flared tweeter cone and ceramic magnet. 10 watts. Bass res. 45-60 cps. Flux 10,000 gauss. Speech coil, 3 or 15 ohm. **45/-**

Also with twin tweeters. Complete with crossover. 3 or 8 or 15 ohms. 10 watt. **£4**

Recommended Teak Cabinet Size 16 × 10 × 9in. **£5**

## MINI-MODULE LOUDSPEAKER KIT


10 WATT **65/-** CARRIAGE 5/-

Triple speaker system combining on ready cut baffle. ⅛ in. chipboard 15 in. × 8½ in. Separate Bass, Middle and Treble loudspeakers and crossover condenser. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The Mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 8 ohm.

TEAK VENEERED BOOKSHELF ENCLOSURE. 16 × 10 × 9 in. Modern Scandinavian fluted front design for Mini-Module. **£5** Post 5/-

ALL MODELS "BAKER SPEAKERS" IN STOCK

## BAKER 12in MAJOR £8

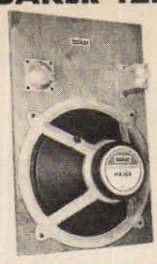

30-14,500 c.p.s., 12in double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 45 c.p.s. Rated 20 watts. Voice coils 3 or 8 or 15 ohms.

Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. **£10.19.6**

BAKER "GROUP SOUND" SPEAKERS POST FREE

| 'Group 25' | 'Group 35' | 'Group 50' |
|---|---|---|
| 12in 25 watt **6gns.** | 12in 35 watt **8½gns.** | 15in 50 watt **18gns.** |

TEAK HI-FI SPEAKER CABINETS. Fluted wood front.
For 10 or 12in round Loudspeaker ..... £9.0.0.
For 13 × 8in or 8in round Loudspeaker ..... £5.0.0.
For 10 × 6in or 6½in round Loudspeaker ..... £4.0.0.
LOUDSPEAKER CABINET WADDING 18in wide. 3/- ft

Horn Tweeters 2-16kc/s, 10W 8 ohm 29/6.
De Luxe Horn Tweeters 2-18 Kc/s, 15W, 16 ohm 59/6.
Moving Coil Cone Tweeter 8 ohm 19/-.
3000 c.p.s. CROSSOVERS 3 or 8 or 15 ohm 19/-.
SPECIAL OFFER! 80 ohm. 2½in, 2½in. dia.; 35 ohm, 3 in. 25 ohm, 3in. dia.; 6 × 4in; 8 × 3in; 8 × 5in. **17/6** EACH TYPE
15 ohm, 7 × 4in; 8 × 5in.
8 ohm 6 × 4in; 3 ohm, 2½in, 3in, 5in, 5 × 3in, 7 × 4in.
LOUDSPEAKERS P.M. 3 OHMS. 6½in 22/6; 8 × 5in. 21/-; 8 × 2½in 21/-; 8in 35/-; 10 × 6in 30/-.
5 in. WOOFER. 8 watts max. 20-10,000 cps. 8 or 15 ohm. 39/6.
ELAC 8 in. De Luxe Ceramic 3 ohm or 15 ohm 50/-.
8in LOUDSPEAKER. TWIN CONE 15 ohm 35/-.
RICH ALLAN 8 or 10 or 12in Twin cone 3 or 15 ohm 39/6.
OUTPUT TRANS. EL84 etc. 5/-; MIKE TRANS. 50:1 5/-.
SPEAKER COVERING MATERIALS. Samples Large S.A.E.

## SOUND ACTIVATED PSYCHEDELIC LIGHT BOX




Fascinating light patterns of Green, Blue, Red and Amber.

Works with any mono or stereo amplifier. Input required 0.2 watts. A.C. mains operated. Size 13 × 13 × 4in.

**£12.10.0**

## ALL EAGLE PRODUCTS

SUPPLIED AT LOWEST PRICES.
ILLUSTRATED EAGLE CATALOGUE 5/-. Post free.

BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. **79/6**

BARGAIN DE LUXE TAPE SPLICER Cuts, trims, joins for editing and repairs. With 3 blades. **22/6**

BARGAIN 4 CHANNEL TRANSISTOR MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. **59/6**

BARGAIN FM TUNER 88-108 Mc/s Six Transistor. 9 volt. Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 × 5 × 4in. Chassis only, less cabinet £7.10.0 **£9.10.0**

FM STEREO MULTIPLEX ADAPTOR for above or general use. Ready made with 4 transistors, 6 diodes **99/6**

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. **69/6**

★ RADIO BOOKS ★ (Postage 9d.)

| | |
|---|---|
| Practical Radio Inside Out | 4/6 |
| Practical Stereo Handbook | 3/6 |
| Supersensitive Transistor Pocket Radio | 3/6 |
| Radio Valve Guide, Books 1, 2, 3, or 4 ea. 5/- No. 5 ea. | 6/- |
| T.V. Fault Finding 405/625 lines | 8/6 |
| Transistor Communication Sets | 6/- |
| Wireless World Radio Valve Data | 10/- |
| Transistor Circuits for Radio Controlled Models | 7/6 |
| Valves, Transistors and Diodes equivalents Manual | 10/6 |
| Coil Design and Construction | 5/- |
| Hartley on Hi-Fi Radio Tuners | 5/- |
| 22 Circuits for Micro-Alloy Transistors | 5/- |
| Practical Car Radio Installation | 6/- |

3 inch MOVING COIL METERS BRITISH MADE
Various calibrations/movements. 500 Microamp; 1 Milliamp; 50-0-50 Microamp. etc. S.A.E. for list. **37/6**



## MAINS ELECTRIC MOTORS

(120v. or 240v. AC). Size 2½ × 2½ × 1½in. Clockwise 1,200 r.p.m. off load. Heavy duty 4 pole 50mA. Spindle ¼ × 3/20. BARGAIN PRICE **17/6** EACH Post 2/6

3 for 50/-; 6 for 90/-.

*Minimum Post and Packing 2/6.* RETURN OF POST DESPATCH. HI-FI STOCKISTS. CUSTOMERS FREE CAR PARK. CALLERS WELCOME.

# RADIO COMPONENT SPECIALISTS

337 WHITEHORSE ROAD, CROYDON
Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.)

*List 1/-.* **Written guarantee with every purchase.** (*Export: Remit cash and extra postage.*) *Buses 133, 68 pass door. S.R. Stn. Selhurst.* **Tel. 01-684-1665**

# L S T ELECTRONIC COMPONENTS LTD

## =BETTER QUALITY, SERVICE, PRICES & LARGEST STOCKS

| | | | | | | | | | | | | | | | | | | | |
|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|
| AAY30 | 1/7 | ASY29 | 6/- | BF185 | 8/- | CG86 | 2/6 | NKT103 | 6/- | NKT231 | 6/- | NKT0013 | 6/8 | OC203 | 7/6 | 40324 | 9/8 | 2N1711 | 5/1 | 2N4058 | 3/4 |
| AAZ13 | 3/2 | ASZ21 | 7/6 | BF194 | 3/6 | CG94 | 2/6 | NKT104 | 6/- | NKT232 | 6/- | NKT10419 | | OC204 | 8/- | 40326 | 7/8 | 2N2147 | 18/3 | 2N4059 | 5/- |
| AC107 | 7/7 | AUY10 | 30/- | BFX13 | 5/- | CR1-051C | 8/- | NKT105 | 6/- | NKT237 | 5/9 | | 3/10 | OC205 | 9/- | 40329 | 4/9 | 2N2148 | 12/6 | 2N4060 | 5/- |
| AC126 | 5/- | B2M | 12/6 | BFX29 | 6/2 | CR1-401C | 10/- | NKT106 | 6/- | NKT238 | 4/- | NKT10519 | 4/5 | OC206 | 10/6 | 40344 | 5/3 | 2N2160 | 14/9 | 2N4061 | 4/- |
| AC127 | 4/- | B3M | 15/- | BFX44 | 8/- | D13T1 | 10/- | NKT107 | 6/- | NKT239 | 4/- | NKT10339 | 4/7 | OC207 | 7/6 | 40347 | 7/6 | 2N2368 | 3/4 | 2N4062 | 4/6 |
| AC127Z | 9/6 | B108 | 2/6 | BFX84 | 5/2 | FCH111 | 16/- | NKT108 | 6/- | NKT240 | 3/10 | NKT10439 | 5/5 | OC209 | 12/- | 40348 | 10/8 | 2N2369 | 3/4 | 2N4284 | 3/- |
| AC128 | 4/- | BA111 | 6/- | BFX85 | 6/9 | FCH141 | 16/- | NKT109 | 6/- | NKT241 | 3/9 | NKT12329 | 8/5 | OC470 | 10/- | 40360 | 8/6 | 2N2369A | 3/11 | 2N4287 | 3/- |
| AC176 | 5/- | BAX13 | 1/6 | BFX86 | 4/11 | FCH151 | 16/- | NKT121 | 10/6 | NKT242 | 2/11 | NKT12429 | | OCP71 | 19/6 | 40361 | 9/6 | 2N2613 | 7/6 | 2N4288 | 3/- |
| AC187 | 12/- | BC113 | 5/- | BFX87 | 5/11 | FCH201 | 21/7 | NKT122 | 10/- | NKT243 | 12/- | | 10/6 | ORP12 | 9/6 | 40362 | 11/6 | 2N2614 | 4/- | 2N4289 | 3/- |
| AC188 | 12/- | BC116 | 8/- | BFX88 | 5/8 | FCH221 | 21/4 | NKT123 | 9/6 | NKT244 | 3/1 | NKT13329 | | ORP60 | 8/- | 40370 | 6/- | 2N2646 | 10/- | 2N4290 | 3/- |
| ACY17 | 5/4 | BC118 | 5/- | BFY18 | 15/- | FST3/8AF | 5/- | NKT124 | 6/5 | NKT245 | 3/- | | 3/11 | ORP61 | 8/- | 40406 | 11/3 | 2N2904 | 8/10 | 2N4291 | 3/- |
| ACY18 | 4/- | BC125 | 12/- | BFY50 | 4/6 | GET16 | 12/6 | NKT125 | 4/6 | NKT262 | 4/8 | NKT13429 | | ORP63 | 9/- | 40408 | 10/3 | 2N2904A | 9/9 | 2N4871 | 6/9 |
| ACY19 | 4/- | BC126 | 11/- | BFY51 | 3/9 | GET102 | 6/- | NKT126 | 4/- | NKT263 | 4/8 | | 3/11 | P346A | 3/9 | 40462 | 11/3 | 2N2905 | 12/11 | 2S104 | 12/6 |
| ACY20 | 3/10 | BC147 | 2/9 | BFY52 | 4/6 | GET103 | 5/- | NKT127 | 10/6 | NKT284 | 4/3 | NKT16229 | 8/5 | RAS310AF | 8/- | 40467 | 16/6 | 2N2905A | 15/1 | 2S711 | 26/6 |
| ACY21 | 3/10 | BC148 | 3/8 | BFY53 | 3/2 | GET113 | 4/- | NKT128 | 10/- | NKT265 | 5/6 | NKT20329 | 6/8 | RAS508AF | | 40468A | 7/- | 2N2906 | 8/10 | 3N128 | 13/9 |
| ACY22 | 3/9 | BC149 | 3/- | BFY90 | 24/6 | GET114 | 4/- | NKT129 | 8/6 | NKT270 | 6/- | NKT20339 | 6/4 | | 15/- | 40602 | 8/- | 2N2906A | 10/10 | 3N140 | 15/3 |
| ACY27 | 3/6 | BC154 | 12/- | BFW57 | 6/- | GET120 | 6/6 | NKT135 | 6/1 | NKT271 | 2/10 | NKT35219 | | RS220F | 4/- | 1Z20 | 10/- | 2N2924 | 4/- | 3N141 | 14/6 |
| ACY28 | 3/8 | BC167 | 3/6 | BFW58 | 5/6 | GET872 | 5/- | NKT137 | 6/1 | NKT272 | 2/10 | | 15/9 | S1M | 19/- | 2G302 | 3/9 | 2N2925 | 3/8 | BA111 | 6/- |
| ACY29 | 7/6 | BC168 | 3/9 | BFW59 | 5/- | GET880 | 9/- | NKT141 | 10/6 | NKT273 | 3/8 | OC19 | 5/- | S4M | 33/6 | 2G306 | 8/6 | 2N3053 | 4/5 | BYX36/150 | |
| ACY30 | 7/6 | BC169 | 3/9 | BFW60 | 4/6 | GET887 | 4/- | NKT142 | 10/- | NKT274 | 2/10 | OC20, | 19/6 | ST140 | 3/- | 2G339A | 5/- | 2N3054 | 12/6 | | 2/6 |
| ACY31 | 4/7 | BC171 | 2/- | BLY47 | 31/3 | GET889 | 6/- | NKT143 | 9/6 | NKT275 | 3/4 | OC22 | 8/- | ST141 | 5/- | 2G371 | 3/- | 2N3235 | 28/6 | BYX36/300 | |
| ACY34 | 3/5 | BC182L | 2/3 | BSX19 | 3/3 | GET890 | 6/6 | NKT144 | 8/- | NKT276 | 3/6 | OC23 | 8/- | ST2 | 9/9 | 2G371B | 3/- | 2N3234 | 27/6 | | 2/10 |
| ACY35 | 3/6 | BC183L | 1/10 | BSX20 | 3/3 | GET896 | 4/6 | NKT151 | 6/- | NKT279A | 2/6 | OC24 | 8/- | T1407 | 9/8 | 2G374 | 5/- | 2N3242 | 7/9 | BYX36/600 | |
| ACY36 | 2/9 | BC184L | 3/- | BSX21 | 7/6 | GET897 | 4/6 | NKT153 | 6/- | NKT281 | 5/- | OC25 | 7/6 | TIS34 | 17/6 | 2G381 | 5/- | 2N3391A | 6/- | | 3/- |
| ACY39 | 12/- | BC212L | 3/4 | BSX60 | 12/7 | GET898 | 6/- | NKT154 | 6/- | NKT301 | 18/- | OC26 | 6/6 | TIS44 | 1/9 | 2N174 | 16/- | 2N3392 | 5/- | BYZ10 | 9/9 |
| ACY40 | 3/- | BCY30 | 5/- | BSX61 | 7/1 | GEX45/1 | 3/- | NKT161 | 6/- | NKT302 | 12/5 | OC28 | 12/- | TIS45 | 3/3 | 2N385A/ | | 2N3393 | 5/- | BYZ12 | 6/- |
| AD140 | 11/- | BCY31 | 5/6 | BSX76 | 4/- | GJ6M | 4/- | NKT162 | 6/- | NKT303 | 17/6 | OC29 | 15/- | TIS46 | 3/3 | 2N388A | 15/- | 2N3394 | 4/9 | BYZ13 | 5/- |
| AD149 | 11/6 | BCY32 | 10/- | BSX77 | 6/- | GP297/1 | 8/- | NKT163 | 6/- | NKT304 | 9/10 | OC35 | 9/- | TIS47 | 3/3 | 2N404 | 4/6 | 2N3402 | 5/6 | EA403 | 3/6 |
| AD161 | 6/- | BCY33 | 4/- | BSX78 | 6/6 | GP826 | 20/- | NKT164 | 6/- | NKT351 | 10/- | OC36 | 12/6 | TIS48 | 3/3 | 2N696 | 3/7 | 2N3403 | 5/6 | EC401 | 5/- |
| AD162 | 6/- | BCY34 | 5/- | BSY27 | 4/- | KB82 | 5/- | NKT165 | 6/- | NKT352 | 17/6 | OC41 | 4/6 | TIS49 | 3/6 | 2N697 | 3/10 | 2N3404 | 7/6 | OA5 | 3/8 |
| ADT140 | 12/6 | BCY38 | 6/- | BSY29 | 5/- | MAT100 | 5/- | NKT201 | 6/- | NKT361 | 20/- | OC42 | 4/6 | TIS50 | 5/6 | 2N698 | 6/- | 2N3414 | 5/6 | OA10 | 6/- |
| ADZ11 | 32/- | BCY40 | 10/- | BSY32 | 5/- | MAT101 | 5/6 | NKT202 | 6/- | NKT362 | 20/- | OC43 | 4/6 | TIS51 | 4/- | 2N706 | 2/4 | 2N3415 | 6/- | OA47 | 1/8 |
| AF102 | 12/6 | BCY42 | 4/- | BSY36 | 5/- | MAT120 | 5/- | NKT204 | 6/- | NKT401 | 14/6 | OC44 | 3/- | TIS52 | 4/- | 2N706A | 2/6 | 2N3416 | 7/6 | OA70 | 1/8 |
| AF106 | 7/6 | BCY43 | 4/- | BSY37 | 5/- | MAT121 | 5/6 | NKT205 | 6/- | NKT402 | 15/- | OC45 | 3/- | TIS53 | 6/6 | 2N708 | 3/3 | 2N3436 | 15/- | OA73 | 1/8 |
| AF114 | 5/- | BCY70 | 3/10 | BSY38 | 4/- | ME1100 | 6/- | NKT206 | 6/- | NKT403 | 14/9 | OC70 | 2/6 | TIS60 | 6/6 | 2N709 | 8/6 | 2N3525 | 21/9 | OA79 | 1/8 |
| AF115 | 5/- | BCU71 | 7/8 | BSY95 | 3/2 | MJ400 | 21/6 | NKT208 | 6/- | NKT404 | 11/- | OC71 | 3/- | TIS61 | 7/- | 2N711 | 7/6 | 2N3528 | 19/- | OA81 | 1/8 |
| AF116 | 5/- | BCY72 | 3/2 | BSY95A | 2/11 | MJ420 | 22/6 | NKT210 | 4/2 | NKT405 | 11/- | OC72 | 4/6 | TIP31A | 12/4 | 2N711A | 7/6 | 2N3702 | 2/6 | OA85 | 1/8 |
| AF117 | 5/- | BCY87 | 86/9 | BYZ14 | 33/3 | MJ421 | 22/6 | NKT211 | 3/9 | NKT406 | 9/11 | OC74 | 8/- | TIP32A | 14/10 | 2N743 | 4/6 | 2N3703 | 2/5 | OA90 | 1/8 |
| AF118 | 8/10 | BD119 | 15/- | BYZ15 | 33/3 | MJ480 | 20/6 | NKT212 | 3/9 | NKT420 | 8/11 | OC75 | 4/6 | U23AAA | 5/- | 2N744 | 6/- | 2N3704 | 3/2 | OA91 | 1/8 |
| AF124 | 4/2 | BD121 | 18/- | C106F | 9/- | MJ481 | 27/- | NKT213 | 4/7 | NKT451 | 9/11 | OC76 | 2/6 | V205 | 20/- | 2N929 | 5/3 | 2N3705 | 2/8 | OA95 | 1/8 |
| AF125 | 4/2 | BD123 | 21/6 | C111 | 18/- | MJ490 | 22/6 | NKT214 | 3/5 | NKT452 | 9/6 | OC77 | 5/6 | V405A | 9/3 | 2N930 | 6/- | 2N3706 | 2/3 | OA200 | 2/- |
| AF126 | 3/6 | BD124 | 12/- | C111E | 12/- | MJ491 | 29/6 | NKT215 | 3/7 | NKT453 | 6/6 | OC81 | 4/6 | XB113 | 6/- | 2N1090 | 6/6 | 2N3707 | 2/10 | OA202 | 2/- |
| AF127 | 3/6 | BDY20 | 20/8 | C400 | 9/- | MPF102 | 8/6 | NKT216 | 7/6 | NKT603F | 4/8 | OC81D | 3/- | XK508 | 20/- | 2N1131 | 6/11 | 2N3708 | 1/10 | SD19 | 7d |
| AF178 | 9/6 | BF115 | 5/- | C426 | 3/3 | MPF103 | 7/6 | NKT217 | 9/- | NKT613F | 5/2 | OC82 | 5/- | 40250 | 10/9 | 2N1132 | 7/9 | 2N3709 | 2/- | TD716 | 12/- |
| AF179 | 11/6 | BF152 | 13/6 | C444 | 9/8 | MPF104 | 7/6 | NKT218 | 6/- | NKT654F | 4/2 | OC82D | 3/- | 40309 | 6/6 | 2N1302 | 3/7 | 2N3710 | 2/3 | 1N34A | 4/- |
| AF180 | 12/6 | BF154 | 9/- | CG50 | 2/6 | MPF105 | 8/- | NKT219 | 4/7 | NKT675 | 6/8 | OC82 | 4/6 | 40310 | 9/- | 2N1303 | 3/7 | 2N3711 | 2/6 | 1N82A | 9/6 |
| AF181 | 8/6 | BF159 | 15/- | CG61 | 2/6 | NKT11 | 7/6 | NKT221 | 7/- | NKT676 | 5/- | OC84 | 5/- | 40311 | 6/9 | 2N1304 | 4/11 | 2N3819 | 7/- | 1N914 | 1/9 |
| AF186W | 9/- | BF163 | 9/- | CG62 | 2/6 | NKT12 | 5/5 | NKT222 | 6/- | NKT677F | 3/10 | OC123 | 7/- | 40312 | 9/8 | 2N1305 | 4/11 | 2N3820 | 18/9 | 1N4148 | 1/9 |
| AF186G | 9/- | BF167 | 5/- | CG62H | 2/6 | NKT32 | 6/2 | NKT223 | 5/- | NKT703 | 8/- | OC139 | 5/- | 40314 | 7/3 | 2N1306 | 6/- | 2N3826 | 6/- | IS44 | 1/9 |
| AF239 | 7/6 | BF173 | 6/- | CG63 | 2/6 | NKT42 | 6/- | NKT224 | 3/7 | NKT713 | 3/10 | OC140 | 7/- | 40315 | 7/3 | 2N1307 | 6/- | 2N3866 | 25/- | IS113 | 4/6 |
| AFY19 | 22/6 | BF178 | 10/6 | CG64 | 2/6 | NKT43 | 6/- | NKT225 | 3/6 | NKT717 | 5/10 | OC170 | 5/- | 40316 | 9/3 | 2N1308 | 6/9 | 2N3903 | 7/- | IS130 | 2/- |
| AFZ11 | 8/- | BF179 | 12/6 | CG6E | 2/6 | NKT72 | 3/9 | NKT226 | 11/- | NKT734 | 4/11 | OC171 | 6/- | 40317 | 7/3 | 2N1309 | 6/3 | 2N3904 | 7/- | | |
| ASY26 | 4/5 | BF180 | 6/- | CG83 | 2/6 | NKT73 | 3/7 | NKT227 | 9/6 | NKT736 | 6/2 | OC200 | 6/3 | 40319 | 10/9 | 2N1496 | 34/- | 2N3905 | 7/6 | | |
| ASY27 | 6/- | BF181 | 6/6 | CG84 | 2/6 | NKT101 | 6/- | NKT228 | 6/6 | NKT773 | 3/7 | OC201 | 9/6 | 40320 | 7/3 | 2N1613 | 4/5 | 2N3906 | 7/6 | | |
| ASY28 | 4/5 | BF184 | 7/- | CG85 | 2/6 | NKT102 | 6/- | NKT229 | 3/11 | NKT774 | 6/- | OC202 | 18/- | 40323 | 6/6 | 2N1617A | 29/6 | 2N4037 | 15/- | | |

**BC107/8/9 2/9**
NPN Planar transistors
BC107 & 9
25 + 2/5 100 + 2/2
BC108 25 + 2/3 100 + 2/-

**2N4871 6/9**
Motorola unijunction
25 + 5/9 100 + 4/9

**2N3055 15/-**
115 watt silicon power transistor
25 + 13/- 100 + 11/-

**IRC 20 7/-**
Int. Rectifier thyristor
200 piv 1·2 amp
(similar C106B1)
25 + 6/- 100 + 5/-

**2N2926 2/-**
NPN Planar transistors
25 + 1/8 100 + 1/6

**BY 127 4/-**
Mullard Plastic
HV rectifier 800 piv.
1 amp. (similar BY100, etc.)
25 + 3/3 100 + 3/-

**2N3819 7/-**
Texas FET
25 + 6/- 100 + 5/3

**MGA 100 35/-**

**31F2 28/6**
Infra-red devices

**OCP71 19/6**
Mullard phototransistor
25 + 17/3 100 + 14/9

### NE560B PHASE LOCKED LOOP

The Phase locked loop is a circuit concept similar to a receiver in that one signal can be selected from many and information derived from the signal *all without tuned circuits*. The PLL can Detect tones, Decode or Demodulate FM, Synchronize signals, Track unstable signals, and Reconstitute signals.

A complete system in one 16 lead DIL package. The NE560B PLL costs £12.0.10 in small quantities. We don't expect you to pay without knowing what the PLL can do—write now for free data.

### SILICON RECTIFIERS

1 amp Miniature Moulded Junction Rectifiers.

| | P.I.V. | 1-24 | 25-99 | 100+ |
|---|---|---|---|---|
| 1N4001 | 50 | 1/10 | 1/8 | 1/5 |
| 1N4002 | 100 | 2/2 | 1/10 | 1/7 |
| 1N4003 | 200 | 2/11 | 2/7 | 2/2 |
| 1N4004 | 400 | 3/9 | 3/4 | 2/10 |
| 1N4005 | 600 | 4/- | 3/9 | 3/2 |
| 1N4006 | 800 | 4/9 | 4/4 | 3/8 |
| 1N4007 | 1000 | 5/- | 4/8 | 4/2 |

DISCOUNT: Quantities of different 1N4000 series may be combined to qualify for the quantity discount prices quoted, example: 10/1N4001, 1/8; 10/1N4002, 1/10; 5/1N4007, 4/9 (25 total pieces).
(In the event of any 1N4000 series going temporarily out of stock we reserve the right to send higher voltage types at no extra charge.
1000+ and over prices on application.

### ZENER DIODES

400mW 10% GLASS CASE.
TEXAS Mfr.

| | | | |
|---|---|---|---|
| IS2036 | 3·6 volt | IS2082 | 8·2 volt |
| IS2039 | 3·9 volt | IS2100 | 10 volt |
| IS2043 | 4·3 volt | IS2110 | 11 volt |
| IS2047 | 4·7 volt | IS2120 | 12 volt |
| IS2056 | 5·6 volt | IS2160 | 16 volt |
| IS2062 | 6·2 volt | IS2180 | 18 volt |
| IS2068 | 6·8 volt | IS2270 | 27 volt |
| IS2075 | 7·5 volt | IS2300 | 30 volt |

PRICES: 1-24 3/6
25-99 2/9 100+ 2/3

### NEWS NEWS NEWS NEWS.....

L.S.T. Electronic Components Limited are proud to announce their official appointment by Newmarket Transistors Ltd.—All Newmarket products now available at *Industrial User prices*. All R.C.A. Semiconductors and Integrated circuits now also available from L.S.T. at *Industrial User prices*. Many Mullard, General Electric, Texas types also ex stock at L.S.T. at *Industrial User prices and better*. And what's more our Retail catalogue is free to all. Iskra resistors, Mullard Capacitors, Veroboard, Repanco coils and other misc. components stocked in large quantities. Official International Rectifier Semiconductor Centre stockists.

### INTEGRATED CIRCUITS

Some R.C.A. Linear types

| | | | | | | | |
|---|---|---|---|---|---|---|---|
| CA3005 | 23/6 | CA3020 | 25/3 | CA3020SB | 21/- | CA3043 | 27/6 |
| CA3011 | 14/9 | CA3021 | 31/3 | CA3035 | 24/6 | CA3044 | 24/- |
| CA3012 | 17/9 | CA3022 | 26/- | CA3036 | 14/6 | CA3045 | 24/6 |
| CA3013 | 21/- | CA3023 | 25/3 | CA3039 | 16/9 | CA3046 | 45/2 |
| CA3014 | 24/9 | CA3026 | 20/- | CA3041 | 21/9 | CA3048 | 10/9 |
| CA3018 | 16/9 | CA3028A | 14/9 | CA3042 | 21/9 | CA3051 | 28/9 |

Application notes for CA series 2/6 per copy.

| | |
|---|---|
| IC10 Sinclair Audio Amp | 59/6 |
| PA230 GE IC Preamplifier | 20/- |
| PA234 GE IC 1W Amp | 20/- |
| PA237 GE IC 2W Amp | 32/6 |
| PA246 GE IC 5W Amp | 52/6 |
| PA424 GE IC Zero Voltage Switch | 43/- |
| SL403A Plessy 3W Amp | 42/6 |
| SL720C Plessy Linear | 29/6 |
| TAA263 Mullard Linear | 15/- |
| TAA293 Mullard Gen. Purp. Amp | 20/- |
| TAA310 Record/Playback Amp | 30/- |
| TAA320 MOS LF Amplifier | 13/- |
| TAD100 Mullard IC receiver | 45/- |
| 3N84 GE Silicon controlled switch | 26/- |

Data sheets 1/- (SL403A 2/6. IC10 data not sold separately)

| | 1-6 | 7-11 | 12+ |
|---|---|---|---|
| UL900 | 9/9 | 9/- | 8/- |
| UL914 | 9/9 | 9/- | 8/- |
| UL923 | 12/6 | 11/9 | 11/- |

Data and circuits (5 pages) 2/6 DIL adaptors/spreaders 1/6 each.

*Prices* quoted are current at time of going to press, E. & O. E, and may be subject to variation without notice—Items listed not in current production will be withdrawn when stocks advertised are sold. Semiconductors offered carry full Manufacturers' *guarantee* where applicable. *Data* sheets will be supplied on request 1/- per copy.
*Price breaks* apply at 25+ and 100+. Please contact Sales Dept. for Price and availability.
*Terms* of Business: Retail Mail orders—cash with order only please. Trade: Nett Monthly Account on receipt of satisfactory references.
*Despatch*: Goods quoted ex stock are normally despatched within one working day by first class post.
*Export* orders and enquiries particularly welcome. Cables: LESTROCO BRENTWOOD.
*Post and Packing* allow 1/- per order inland: 4/- Europe; 12/- Commonwealth.

Address your Order to:

**L.S.T. ELECTRONIC COMPONENTS LTD.**
**7 COPTFOLD ROAD**
**BRENTWOOD, ESSEX**

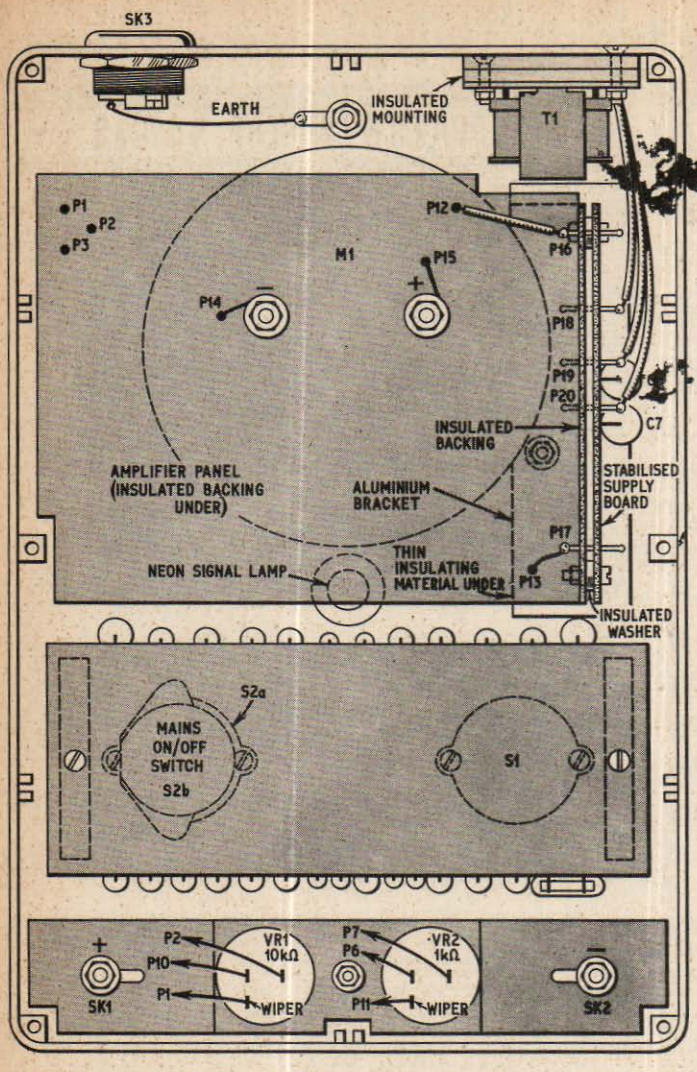



*Fig. 14. Interior of the multimeter showing component positioning and potentiometer wiring*

## COMPONENTS . . .

**Potentiometers**
VR1 10kΩ miniature carbon
VR2 1kΩ miniature carbon

**Sockets**
SK1 Red insulated screw terminal
SK2 Black insulated screw terminal
SK3 Miniature three pin mains connector

**Transformer**
T1 Miniature mains, primary 0–220/240V, secondary 12–0–12V, 40mA, type P9005 (Electroniques)

**Meter**
M1 Moving coil milliammeter, B.P.L. type S40–V1 (1mA f.s.d.) *or* SEW type MR-65P

**Miscellaneous**
LP1 Neon signal lamp type SGF9/A (Electroniques)
Knobs pointer (2 off)
Diecast case $8\frac{3}{4}$in × $5\frac{3}{4}$in × $2\frac{5}{32}$in
Bakelite; $\frac{1}{8}$in thickness, $5\frac{7}{16}$in × $3\frac{1}{8}$in, $\frac{1}{16}$in thickness 4in × $1\frac{1}{2}$in, $\frac{1}{8}$in thickness black $2\frac{1}{16}$in × $\frac{1}{2}$in
Perspex $3\frac{1}{8}$in × $5\frac{5}{16}$in × $\frac{1}{8}$in thickness
6B.A. and 8B.A. fixings

## CONNECTING UP

The Veropins on the amplifier board are connected up with reference to the pin numbers on the circuit diagram (Fig. 2), the switch connection diagram (Fig. 8), and Fig. 14, the plan of the interior of the multimeter. The two Veropins adjacent to the meter terminals are connected to the terminals by short leads, and the Veropins nearest to the stabilised voltage supply, are connected to the two on the vertical panel as shown in Fig. 14. The row of Veropins on the left of the amplifier board are connected by flexible p.v.c. covered wires to the range switching assembly, and to the two potentiometers that are mounted as shown in Fig. 15 by means of strips of $\frac{1}{8}$in insulating material.

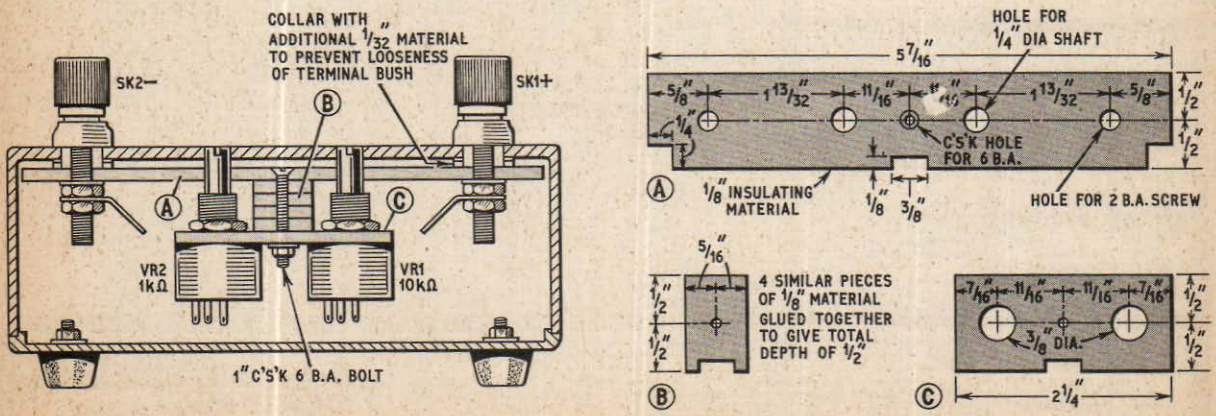



*Fig. 15. Potentiometer mounting details, the ends of the spindles should be flush with the top of the case when fitted*

*continued from page 630*

The three secondary connections from the mains transformer are joined to the terminal pins on the voltage stabiliser panel.

Positioning of all components is shown in Fig. 14 and once the various sections have been mounted and wired up as described previously the meter can be connected to the mains supply ready for setting up and testing.

## OFFSET ADJUSTMENT

A high gain differential d.c. amplifier needs pre-set adjustments to take up the mismatch in transistors and other components; adjustment is at the input stage where the sensitivity is greatest.

In the absence of an applied input, the terminals of the testmeter should be at the same potential. A small difference of potential at the input is called offset voltage, and arises from mismatch in the base-emitter potentials of the two input transistors. It can be balanced out by adjusting VR2, thus bringing the two input terminals to the same potential.


There is also an offset in the bias current of the two input transistors. The bias currents—less than a microampere—flow through the two 1MΩ feedback resistors and produce a small potential drop between output and input. The bias current adjustment is carried out indirectly by VR1 in the collector circuit of the input stage. When both offsets have been balanced out, there will be no potential difference, either at the input or at the output.

## METER ZEROING

The two adjustments are not independent of each other. Each potentiometer has to be adjusted in turn to bring the pointer of the meter exactly to zero. A short insulated wire is connected between the input terminals each time that VR2 is adjusted, and temporarily disconnected when adjusting VR1. The potentiometer VR1 is thus the open circuit adjustment, and VR2 the short circuit adjustment, and the two are marked "O.C." and "S.C." respectively on the Perspex escutcheon.

Successive adjustments become smaller and should be continued on the most sensitive 2mV range until the pointer is at zero under both input conditions. The short circuit adjustment (VR2) is rather critical on the 2mV range, and it is probably advisable to solder a 470 ohm carbon film resistor permanently across it to make adjustment easier, providing that the narrower range of adjustment contains the required setting.

Once the above adjustments have been made and the meter has been tested on all ranges it is ready for use. ★

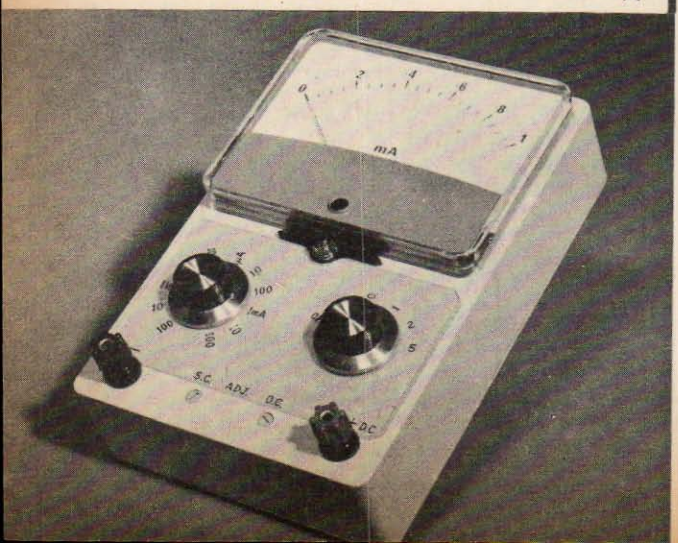

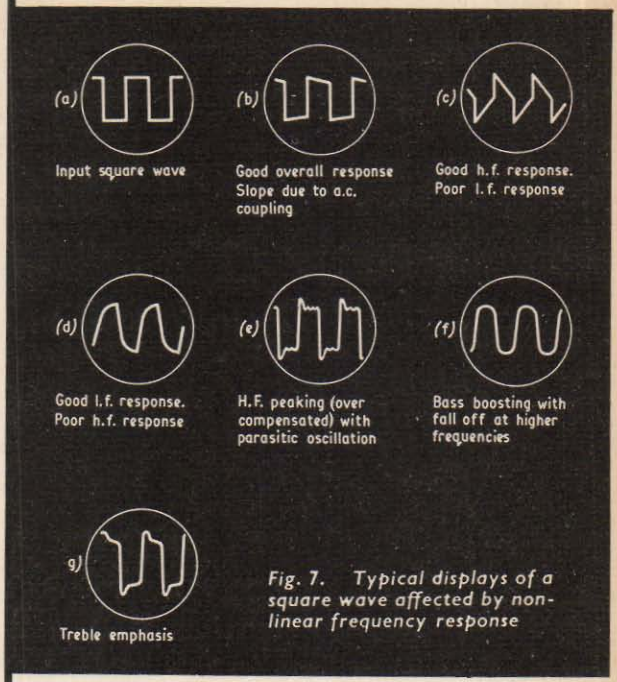




*Fig. 7. Typical displays of a square wave affected by non-linear frequency response*

maximum amplitude is 1 unit the average is 0·637 and this is what the meter will read.

However, we are usually more interested in the r.m.s. value which is, for sine waves, 0·707. If we divide the r.m.s. value by the average, we find the form factor, in this case 1·11. This is the amount by which the meter is scaled or calibrated. So the meter is known as average reading, r.m.s. calibrated. The form factor is obviously different for other waveforms, this calibration is therefore true only for sine waves.

## AMPLIFIER TESTING

Square wave testing of amplifiers has the advantage of time saving. Plotting a frequency response curve is a tedious business. It involves changing the frequency of the signal generator point by point along the frequency base, and noting the amplifier's output reading. From this the output voltage versus frequency graph is drawn.

It is obvious that examining the effects of tone controls of an audio amplifier can be a long and dreary process. But, by applying a square wave to the amplifier input, and monitoring the output on an oscilloscope, the effects of tone controls and filters can be seen by the alteration to the wave shape. See Fig. 7.

Treble boost will show up as overshoot of the leading edge and treble cut as a rounding off. Bass boost will tilt the flat top left to right and bass cut right to left.

Checking a pre-amplifier with a square wave for the first time you may be dismayed to find that the output appears to be distorted. Even at the mid-point of the controls, the leading edge will probably display a slight kink and the top a slight curve. This is due to the type of tone control circuit which is common to many pre-amplifiers. However, the basic square shape, and the variation as the tone controls are adjusted is quite clear. ★

# ELECTRONIC BROKERS

## LOW COST ELECTRONIC & SCIENTIFIC EQUIPMENT AND COMPONENTS

### MOTORS

**HIGH PRECISION MAINS MOTOR**
230V 50Hz ¼ h.p. continuously rated. 3,000 r.p.m. Made by Croydon Engineering Model KA 60 JFB. Suitable for capstan motor. Size 8in long, 4¼in diameter with 6in diameter flange and 4 fixing holes. These motors are Capacitor Start, Capacitor Run, supplied less Capacitor. Also available 3 Phase. **£4.10.0.** each. £1.5.0. P. & P.

**SHADED POLE MOTORS 120V 50Hz**
Precision made as used in record decks and tape recorders. Suitable many other applications. **10/-** each. P. & P. 3/-.

**PRECISION MOTORS by PULLIN**
28V, 3,000 r.p.m., 0·0016 h.p.; 28V, 5,000 r.p.m., 0·0014 h.p.; each **£4.10.0.** P. & P. 5/-.

**HYSTERESIS REVERSIBLE MOTOR**
Incorporating two coils. Each coil when energised will produce opposite rotation of output shaft. 120V 60Hz. 1/10 r.p.m. **30/-** each. P. & P. 3/-.

**LOW TORQUE HYSTERESIS MOTOR MA23**



Ideal for instrument chart drives. Extremely quiet, useful in areas where ambient noise levels are low. High starting torque enables relative high inertia loads to be driven up to 6oz/in. Available in the following speeds and ranges: 240V 50Hz, 4 r.p.m., ½ r.p.m., 1½ r.p.m., 1 r.p.m., ¾ r.p.m., ½ r.p.m., ¼ r.p.m., ½ r.p.m., 1/10 r.p.m., 1/12 r.p.m., 1/20 r.p.m., 1/45 r.p.m., 1/60 r.p.m., 1/360 r.p.m. **25/-** each. P. & P. 3/-.

**HYSTERESIS CLUTCH MOTOR**




With integral clutch allowing the motor to drop out of engagement with the gear train, thereby facilitating easy resetting when used in timers or in conjunction with a light spring. 6 oz torque at 240V 50Hz, 1/12 r.p.m., 1/10 r.p.m., ¼ r.p.m., ½ r.p.m., ¾ r.p.m., 1 r.p.m., 15 r.p.m. 120V 50Hz, 1/12 r.p.m., 1/10 r.p.m., ¼ r.p.m., 5/12 r.p.m., 4/11 r.p.m., 2 r.p.m. 120V 60Hz, ½ r.p.m., 1 r.p.m. 24V 50Hz, 1/20 r.p.m., 4 r.p.m. **25/-** each. P. & P. 3/-.

**D.C. MOTORS**
Similar to above type MD 83. 28V 1/20 r.p.m., 1/60 r.p.m., 1 r.p.m. 12V 1/20 r.p.m. 24V 1/15 r.p.m. 30V 1/12 r.p.m. **30/-**. P. & P. 3/-.

**SYNCHRONOUS MOTORS**
200/250V 50Hz. New condition, ex-equipment. S-1 RPH. Self starting, complete with gearing shaft ⅛in dia., ½in long. **30/-**. P. & P. 3/-.

**OSCILLOSCOPE TYPE CT 52**

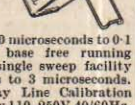

A very handy miniature portable instrument for general purpose applications. 2¼in diam. tube. Wave form investigation from 10Hz-20MHz. Pulse monitoring duration 50 microseconds to 0·1 microsecond. Time base free running 10Hz-40kHz. Also single sweep facility from 50 microseconds to 3 microseconds. "Y" Amplifier. Delay Line Calibration Voltage. Power supply 110-250V 40/60Hz. 50W. Supplied with metal carrying case. L. 13in. H. 8in. W. 5½in. Weight 14½lb. Price **£22.** P. & P. 10/-.

**AVO TRANSISTOR ANALYSER CT 446**
In V. G. condition. Current instrument. Battery powered. Size 15½" × 9½" × 5". Weight 15lb. Price **£42.10.0.** Carr. £1.

**ELECTRIC CLOCK MOTOR**
NEW 200-250V, 50Hz, 2W. Synchronous induction motor. 2 revs. per hour. O/P shaft. ¼in dia × ⅝in long. Clockwise rotation. Three-holed mounting at 120° on 2in PCD. Price **20/-**. P. & P. 5/-.

**DELAY LINE**
2 microsecond, 4,000 ohm, Type MON 2484D. Length 2½in × ⅜in × ⅜in. Encapsulated module. Price **30/-**. P. & P. 5/-.

**NEW FRACTIONAL HP SINGLE PHASE INDUCTION MOTORS**
230V, 50Hz. Continuously rated. Impedance protected type. Available as follows:

| r.p.m. | Amp. | Approx. H.P. |
|---|---|---|
| 875 | 0·83 | 1/16 |
| 875 | 1·8 | 1/8 |
| 875 | 1·19 | 1/12 |
| 1,275 | 0·82 | 1/16 |
| 1,300 | 0·25 | 1/50 |
| 1,300 | 1·27 | 1/25 |
| 1,300 | 0·44 | 1/30 |
| 1,300 | 0·27 | 1/50 |
| 1,300 | 0·25 | 1/50 |
| 1,300 | 0·91 | 1/20 |
| 1,500 | 1·47 | 1/7 |
| 2,500 | 0·72 | 1/20 |
| 2,600 | 0·45 | 1/30 |

Price **35/-**. P. & P. 7/6.

**MINIATURE UNISELECTORS**



3 bank, 12 way, 250 ohm, 24V. Type 2200A. Supplied complete with plug-in base. Size 3in × 1in × 2in. A very neat precision component. Price **£4.19.6.** P. & P. 5/-.

**AVOMETERS**
These well-known portable test instruments have been overhauled and are offered complete with leads, crocodile clips and prods.

| | | |
|---|---|---|
| Model 9 8X | **£24.10.0** | P. & P. 7/6 |
| Model 8 | **£18. 0.0** | P. & P. 7/6 |
| Model 7 | **£14.10.0** | P. & P. 7/6 |
| Model 7 Mk.II | **£15. 0.0** | P. & P. 7/6 |
| Model 7X | **£15.10.0** | P. & P. 7/6 |
| Model 48A | **£11. 0.0** | P. & P. 7/6 |
| Model 47A | **£10. 0.0** | P. & P. 7/6 |
| Model 40 | **£10. 0.0** | P. & P. 7/6 |

Model 48A complete with voltage multiplier for 480V and 3600V. Current shunts for 120A and 480A. A.C. Current transformer for 20A and 60A. In special wooden box. **£14.10.0.** P. & P. 10/-.

**SET OF MEASURING INSTRUMENTS**



Brand new high grade moving coil meters. Ideal auto-electrics and other general d.c. applications. Supplied with 3 shunts in neat attache type metal carrying case. Specifications: Voltmeter 0-15V, 0-150V, 0-450V. D.C. Linear mirror scale 3mA FSD. Ammeter unshunted 7·5mA FSD. Used with 3 shunts to give ranges of 0-3A, 0-7·5A, 0-15A, 0-7·5A, 0-15A, 0-30A. The ammeter can also be used as a 0-75 mV Voltmeter. Scale length 83 mm. Accuracy 1%. Case moulded plastic. Meter size 4¼in × 4¼in. List price £30. Our price **£5.19.6.** P. & P. 30/-.

**HIGH VALUE DECADE RESISTANCE BOX**



Ranges from 0·01MΩ to 111MΩ. Accuracy 0·05%. Maximum Power Rating 0·1W per step. Price **£22.10.0.** P. & P. £1.0.0.

**PORTABLE WHEATSTONE BRIDGE**
Specification. Type: Moving Coil Galvanometer. Ranges: 1. 0-05 to 5 ohms. 2. 0-5 to 50 ohms. 3. 5 to 500 ohms. 4. 50 to 5,000 ohms. 5. 500 to 50,000 ohms. Scales: Switched. Slidewire: 0-5 to 50. Galvanometer Scale: 10-0-10. Case: Moulded plastic. Internal Source: 4V Dry battery. Dimensions: 200 × 110 × 65mm. Weight: 0·9kg. List price **£25.** Our price **£9.19.6.**

### OSCILLOSCOPES

| | |
|---|---|
| Cossor 1035 | **£19.10.0** |
| Cossor 1049 | **£25. 0.0** |
| Solartron 513 | **£39.10.0** |
| Solartron D300 | **£20. 0.0** |
| Furzehill 0100 | **£19.10.0** |
| Furzehill 0110 | **£19.10.0** |
| Furzehill 1684B | **£19.10.0** |
| Airmec 249 | **£15. 0.0** |
| Airmec 723 | **£15. 0.0** |

Carriage extra.

### COUNTERS

**ELECTRO MAGNETIC COUNTER** 300 ohm 24V. Slow impulse counter of 10 impulses per second. **6/6.** P. & P. 3/-.



**6 DIGIT ELECTRICAL IMPULSE COUNTER** with electrical and mechanical reset counter driven by 110 V DC 4400 ohms coil. Reset 110 V DC 800 ohms coil. Housed in plastic-alloy case. The units can be interlocked with each other to give vertical or horizontal displays. Price **79/6.** P. & P. 5/-.

**VEEDER ROOT 6 DIGIT COUNTER**
Suitable for counting all kinds of production runs, business machine operation. Mechanically driven. Reset type KA1337, manual knob. Ex-equipt. but new condition. Special price **25/-** plus 5/- P. & P.

**3 DIGIT RESETTABLE COUNTER**
Totalising 48V d.c. at 48mA; 10 impulses/sec. Length 4in × ⅜in × 1in. Price **£3.15.0.** P. & P. 5/-.

**4 DIGIT NON-RESETTABLE COUNTER**
Totalising 10 impulses per second. Length 3⅛in × 1⅜in × 1⅜in. 24V d.c., 300 ohm. Price **6/6.** P. & P. 5/-.

**6 DIGIT RESETTABLE COUNTER**
Totalising 240V 50Hz. Viewing window 2in × ⅜in. Ex-equipment. Price **55/-**. P. & P. 5/-.

**6 DIGIT TOTALISING NON-RESETTABLE COUNTER**
Mechanical operation. Chromium finish. Length 1⅛in × ⅜in × ⅜in with viewing window ⅜in × ⅛in. Ex-equipment. Price **9/6.** P. & P. 2/6.


**BERKELEY DECIMAL COUNTING UNIT 0-9**
4 valves double triode type 5965 special quality Unit plugs into standard octal base. Modular construction with 10 miniature neon lamps on display panel. Power supplies 6·3V, a.c., 150V d.c. Cut-on or Cut-off—15V. Size 5⅛in × 5⅛in × ⅜in. Price **65/-**. P. & P. 5/-.

**MINIATURE DIGITAL DISPLAY**



Operates on a rear projection 6·3 pilot lamp. The lamp projects the corresponding digit on the condensing lens through a projector lens, on to the viewing screen at the front of the unit. 1in width. 3⅛in deep. 1⅝in high. Weight 3½oz. Character size ⅜in high, 0·9 with 8 right hand decimal point and degree. List price 6 gns. Our price **49/6.** P. & P. 5/-.

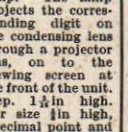**EAC DIGIVISOR Mk. II DIGITAL READ-OUT DISPLAY**



Ideally suitable for use in conjunction with transistorised decade counting devices. The DIGIVISOR incorporates a moving coil movement which moves a translucent scale through an optical system and the resultant single plane image is projected on a screen. The translucent scale is made to represent digits 0-9. Specifications: 6·3V 250 microamp. Image height ⅜in. Size 4 9/16 × 2 39/64 × 1⅛in. **Our price 3½ gns.** List price 8½ gns. P. & P. 5/-.

**LAMPS**
250V, 15W, MBC. Panel lamps. Ideal making up displays, etc. Length 2⅜in × 1⅛in dia. Special offer, **10 for £1.** P. & P. 5/-.

**MICROSWITCHES**
Assorted miniature types. Special offer, **15 for £1.** P. & P. 5/-.

**MINIATURE MOVING COIL RELAY S115**



By Sangamo Weston, suitable for D.C. circuit. A high sensitivity relay more sensitive than the electromagnetic type. Single Coil Resistance 310 micro amps. 315Ω. List price £4.10. Our price **20/-**. P. & P. 3/-.

**NUMICATORS**



Fig. size 16mm.
Cold cathode gas filled in line 0-9 digital display tubes. Long life expectancy. Minimum striking voltage 180V. Side reading Type XN 13 and XN 3, amber. Price **18/6** each. P. & P. 2/6.
Fig. size 20 mm.
Type NI 1. End reading. Price **£1** each. P. & P. 2/6.

**DOUBLE AUDIO FADERS**



These hard to get, professional recording studio units are ideal for audio signal mixing, fading programmes in and out, etc. Two bank 1,000 + 1,000 ohm wire-wound parallel connection to give 500 ohm 1W. Independent tracks fitted scale makings, with red and blue control knobs. Panel mounting. Ex-equipment. Price **£3.19.6.** P. & P. 7/6.

**LINEAR THYRISTOR CONTROLLED LIGHT DIMMER—BRAND NEW**



High grade full wave bridge circuit gives linear control of light brightness. Ideal for controlling room lighting and a.c./d.c. commutator motors fitted to portable electric hand drills. Fits standard 2in conduit box. 240V, 50Hz, 600W. Price **59/6.** P. & P. 2/6.

**POCKET CALCULATOR**



Save time and solve all your multiplication, division, percentage, cube and squareroot problems. Easy to use pocket calculator with no errors. Invaluable daily aid, should last a lifetime, offered complete in black wallet with full instructions, 3¼in diam. **12/6** each, P. & P. 1/6.

New complete telephone dial assemblies Clear perspex dial — no markings **20/-** each, P. & P. 5/-.

**RAPID HEAT SOURCE . . .**



from brand new **Infra Red Tubular Quartz Lamps.** Ideally suited as heat source for Drying Ovens, Egg Hatching, Incubators, etc. 240V, 1,440V, 20,000 Angstroms. Length 12in × ⅜in dia. Price **15/-**. P. & P. 5/-.

**SOLENOIDS**
High quality solidly constructed solenoids. Actuated by 48V 300Ω coil. Overall length 3" × 1" square with a ½" travel of the ¼" dia. shaft. **8/6.** P. & P. 3/-.

**INDICATOR LAMPS**
Panel-mounting. Various colours and types. Press to test facility. Prices from **5/-** each. P. & P. 1/6.

**ELECTRONIC BROKERS LTD., 49-53 PANCRAS RD., LONDON, N.W.1 Tel. 01-837 7781/2 Cables: SELELECTRO**

**CARRIAGE EXTRA**

# TRANSISTOR RADIOS TO BUILD YOURSELF

Backed by after sales service




## *NEW!* roamer eight mk 1

### WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, S.W.1, S.W.2, S.W.3, and Trawler Band. Built in ferrite rod aerial for Medium and Long Waves. 5 section 22in chrome plated telescopic aerial for Short Waves can be angled and rotated for maximum performance. Push-pull output using 600Mw type transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. 8 transistors plus 3 diodes. Famous make 7 × 4in speaker. Air spaced ganged tuning condenser. On/off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9 × 7 × 4in approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build. Parts price list and easy build plans 5/- (FREE with parts).

**Total building costs** **£6.19.6** P. & P. 7/6

## roamer seven mk IV



7 FULLY TUNABLE WAVE BANDS—M.W.1, M.W.2, L.W., S.W.1, S.W.2, S.W.3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. 5 Section 22in chrome plated telescopic aerial for Short Waves—can be angled and rotated for peak S.W. listening. Socket for Car Aerial. Powerful push-pull output. 7 transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7 × 4in P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9 × 7 × 4in approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 3/- (FREE with parts).

**Total building costs**

**£5.19.6** P. & P. 7/6

Personal Earpiece with switched socket for private listening, 5/- extra.

## *NEW!* transeight



### SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case in black with red grille and cream knobs and dial with polished brass inserts. Size 9 × 5½ × 2¾in. approx. Tunable on Medium and Long Waves, 3 Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 8 improved type transistors plus 3 diodes. Push-pull output. Ample power to drive a larger speaker. Parts price list and easy build plans 5/- (FREE with parts).


**Total building costs**

**89/6** P. & P. 5/6

Earpiece with switched socket for private listening 5/- extra.

## pocket five
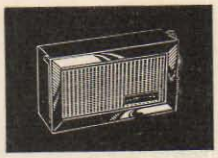
### MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER AND EARPIECE



Attractive black and gold case. Size 5½ × 1½ × 5¾in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker, also Personal Earpiece with switched socket for private listening. Easy build plans and parts price list 1/6 (FREE with parts).

**Total building costs**

**44/6** P. & P. 3/6

## transona five

### MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER



Attractive case with red speaker grille. Size 6½ × 4¼in × 1¾in. 7 stages—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Easy build plans and parts price list 1/6 (FREE with parts).

**Total building costs**

**47/6** P. & P. 3/9

## roamer six

### SIX WAVEBAND PORTABLE WITH 3in. SPEAKER



Attractive case with gilt fittings. Size 7½ × 5½ × 1¾in. Tunable on Medium and Long Waves, two Short Waves, Trawler Band plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. (Carrying strap 1/6 extra). Easy build plans and parts price list 2/- (FREE with parts).

**Total building costs**

**79/6** P. & P. 4/6

* *Callers side entrance Stylo Shoe Shop*

* *Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.*

## RADIO EXCHANGE LTD

61a, HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

| | | | |
|---|---|---|---|
| ROAMER EIGHT | ☐ | ROAMER SEVEN | ☐ |
| TRANSEIGHT | ☐ | POCKET FIVE | ☐ |
| TRANSONA FIVE | ☐ | ROAMER SIX | ☐ |

Parts price list and plans for.....

Name.....

Address.....

.....

..... PE 20


# MARKET PLACE

**Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned.**
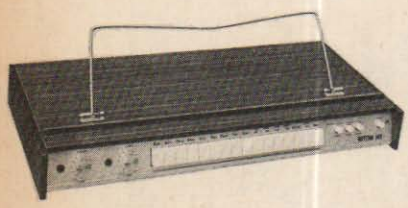
## RHYTHM UNIT

To interest our musically minded readers this month is a versatile automatic rhythm unit to add complete accompaniment to an organ or other solo instruments.

Known as the Rhythm Ace it gives a choice of 10 different percussion tones: bass drum; small drum; conga (high and low); brush; claves;



***Rhythm Ace from Severn Musical Industries***

cow bell; cymbal, maraccas, and bongo. There are 16 different rhythm patterns ranging from waltzes to samba and cha-cha.

The required performance is selected by push-buttons and there are four separate cancel buttons for cutting out the cymbal, cow bell, bass drum and claves. The unit is operated by manual start or foot-switch operation and a tempo or speed control, mounted on the front panel, is also incorporated.

The rythm unit is designed to play through any high impedance amplifier, retails at £147 and is available from any branch of **Selmer Musical Instruments Ltd.**, or for nearest stockist write to **Severn Musical Instruments Ltd.**, Woodchester, Stroud, Gloucester.

Another sound effect in vogue at the present time is that of reverberation. Readers who are experimenting in this field may be interested in the range of Gibbs Spring Line units from **Hammond Organ (U.K.) Ltd.** These units range from a delay time of 0·027sec large spring, 0·022sec small spring to 0·038sec large spring, 0·025sec small spring. The delay times vary from 2sec to 1·5sec

Prices and further particulars can be obtained from Hammond Organ (U.K.) Ltd., Deansbrook Road, Edgware, Middlesex.

## SPEED SENTRY

The fear of prosecution for speeding and the inevitable licence endorsement which accompanies this offence is always a threat to the person who is dependent on his licence for his livelihood. The Speedset Audible Speed Indicator from **Automents Ltd.** is a worthwhile fitment for the car as it removes the necessity for constantly looking down at the speedometer to check the speed, and enables the driver to give full attention to the road.

The Speedset gives an audible alarm instantly a preselected road speed is exceeded. The selection of the required road speed is accomplished by depressing push buttons, the range available is 30, 40, 50, 60 and 70 m.p.h. or for continental use 50, 65, 80, 100 and 120 k.p.h.

The speed alarm consists of two main units, the control unit which is fitted beneath the dashboard, and a self-adhesive transducer which fixes to the back of the vehicle's speedometer and plugs into the control unit. The transducer detects the rotor speed within the speedometer and transmits this to the control unit where the actual road speed is computed and triggers the alarm if the selected speed is exceeded.

An adjustable volume control is fitted and preset potentiometers are accessible from the front panel of the control unit enabling a certain amount of speed setting variations, i.e. 30 m.p.h. can be set between 28 and 38 m.p.h.

Designed to fit any 12V positive or negative earth vehicle the current consumption is claimed to be less than a car parking light. The prize of the Speedset is £19 15s and further particulars can be obtained from Automents Ltd., New Street, Oadby, Leicester.


## STROBOSCOPE

The latest version of the **Dawe** transistor stroboflash, type 1209C, is ideal for educational and industrial laboratories (not psychedelic).

The new model has internal modifications and additional facilities and is intended for the measurement of the repetition rate of cyclical events, or for observing such events in slow motion.

The instrument has a basic operating range from 300 to 18,000 flashes per minute in three switchable ranges. Speeds up to 180,000 rev/min can be measured by using harmonics by virtue of the very short flash duration of 5–10 microseconds, depending on flash rate. The Xenon tube used gives high-intensity white light and provides a mean illumination at 1 metre distance which increases from 50 lux on the 18,000 flashes/min range to 100 lux on the 1,800 flashes/min range. Mean flash tube power is 6W maximum.

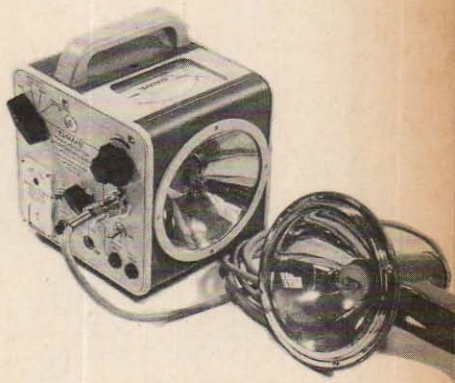The flash rate is controlled by a variable transistorised oscillator, which also drives the anologue frequency meter calibrated directly in flashes/min. Alternatively, an external mechanical contactor or photoelectric pick-up can be used; in both cases the flash rate is indicated on the meter.



***Dawe Stroboflash type 1209C***

An extension lamp can be plugged in and there is now a selector switch which enables the output to be switched between the built-in and extension lamps.

Further specifications and application details can be obtained from Dawe Instruments Ltd., Concord Road, Western Avenue, London, W.3.



***Speedset audible speed indicator marketed by Automents Ltd.***

## LOGIC TESTER

A new logic tester, designed to ease the problem of checking a digital system is being manufactured by **Southern Techniques (Electronics) Ltd.**, Waldeck House, Waldeck Road, Maidenhead, Berks.

The tester emits an audible tone, the pitch of which is high when its probes are connected to a logical "1" level, and low when its probes are connected to a logical "0" level. An open circuit condition between the probes is indicated by the absence of tones. An earphone jack is provided which disconnects the internal loudspeaker when the earphone plug is inserted.

A particularly useful feature is a built-in transient detector. With the tester switched to transient detection and the probes connected to a circuit under test, then the arrival of a logical "1" pulse causes the tester to emit a continuous tone until reset.




***Logic Tester from Southern Techniques (Electronics) Ltd.***

Models of this tester are available for operation from internal batteries or mains supply, and suitable for high or low voltage logic systems, prices range from £15 to £20.

## DIGITAL CLOCK INDICATOR

Readers experimenting with their own designs for constructing digital clocks may be interested in the recent product introduced to the U.K. market by **ITT Component Group Europe.** It is a synchronous motor-driven digital time indicator incorporating an alarm setting mechanism. The alarm operates a changeover microswitch which permits any desired warning device to be triggered at the selected time.

The standard model operates from 240V a.c. 50Hz. Time indication is for a 12-hour clock, divided into minute intervals and the alarm graduation is for 24 hours at 10 minute intervals. The indicating numerals are white on black.


Full particulars are available from ITT Components Group Europe, Trading Services, Edinburgh Way, Harlow, Essex.

## INTEGRATED CIRCUITS

A 250mW low power audio i.c. amplifier, type MFC 4000, is the first of a new range of low cost integrated circuits designed specifically for the consumer market by **Motorola Semiconductors.**

The special feature of this i.c. is that the pin spacing is wider, uses smaller chips, fewer circuit elements and is designed so that it will easily mount on the standard perforated boards. Built in a four-lead package, it is the equivalent to six transistors, three diodes and five resistors.

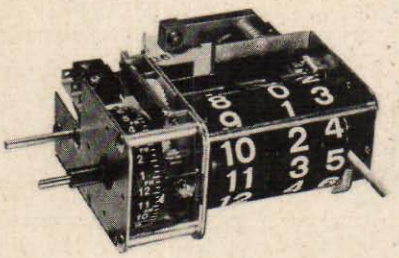The transformerless output is suitable for loads up to 16 ohms and a typical harmonic distortion figure at 50mW is 0·7 per cent. The input sensitivity is 15mV r.m.s. for 50mW



***ITT Synchronous motordriven digital time indicator***

output. Powered by a 9V d.c. supply the quiescent current is 3·5mA.

The type MFC 4000 is designed mainly for small radios but can be used for any low power amplifier output stages.

Also in the same range is the type MFC 4010 which is a high gain wide-band amplifier that could be used either as a general purpose a.f. amplifier or as an i.f. amplifier at 465kHz.

This i.c. contains three transistors and five resistors. Typical output noise is 1mV r.m.s. and with a 18V supply the current drain is 3mA.


Another integrated circuit for use either as a television intercarrier sound limiter-amplifier, detector and a.f. pre-amplifier, or for a similar function in high quality f.m. stereo radio receivers and tuner units is the TAA661 from **SGS (United Kingdom) Ltd.**

At an input level of 1mV the a.m. rejection is better than 40dB. It is claimed to give good performance from a supply voltage ranging from 4·5 to 15V, with a typical quiescent current of 15mA at 12V. The limiting threshold voltage is about 100$\mu$V and remains independent of the supply voltage.

Designed to replace the conventional complementary-symmetry audio output stage, driver and pre-amplifier stages in 9V or 12V battery-operated radio receivers, record players and tape recorders, the TAA661 is capable of delivering 1W r.m.s. from a 9V supply without a heat sink.

The integrated amplifier can be directly driven from a diode detector circuit or crystal pick-up with negligible distortion. Few external components are required and bias conditions are stabilised; no pre-set resistor or setting-up procedure is necessary. Feedback is available if required by the use of one external resistor.

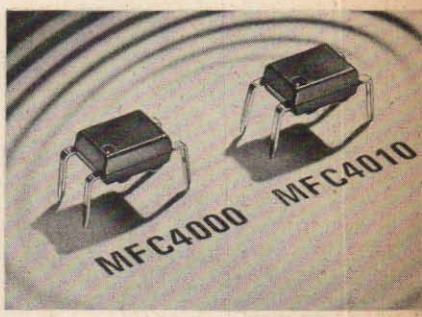A 3 watt 24V version is available and is designated TAA621.




***Integrated circuits from Motorola Semiconductors***

## LITERATURE

The new edition of the excellent **Henry's Radio** components catalogue has a new companion in the form of a special audio catalogue. Like their other catalogue the same high standard is maintained throughout and separate sections deal with amplifiers, tuners, tape recorders, record decks and accessories.

The catalogues are to be revised every three months in future.

Henry's are now expanding their business to further premises and the electronic components and equipment section is moving to 354 Edgware Road, London, W.2. The high fidelity section, with four demonstration rooms, to 356 Edgware Road, and the store at 309 Edgware Road is to become the electronic organ department coupled with public address and discotheque equipment.

*The existing premises at 303 Edgware Road will handle all mail order and identical sales for the time being.*

## MICRO SWITCH



5 amp. changeover contacts, 1/9 each, 18/- doz. 15 amp. model 2/- each or £1/- doz.



## TOGGLE SWITCH

3 amp. 250V with fixing ring. 1/6 each, 15/- doz.

## CONSTRUCTORS' PARCEL

1. Plessey miniature 2 gang tuning condenser with built-in trimmers and wave gang switch. 2. Ferrite slab aerial with coils to suit the above tuning condenser. 3. Circuit diagram giving all component values for 6 transistor circuit covering full medium wave and the long wave band around radio 2. The three items for only 7/6 which is half of the price of the tuning condenser alone.

## 10 AMP 24V BATTERY CHARGER

Ideal unit for garage, boat station, etc., £22.10.0 each plus carriage and cost.

## BEHIND THE EAR DEAF-AID

Made by a very famous maker. Thoroughly overhauled, cleaned and reconditioned. Guaranteed 6 months. Regular price around £50. Our price £10.

## ISOLATION TRANSFORMERS 200–250 MAINS

A must if you work on mains equipment. Prevents accidents and shocks even in damp conditions. Input and output separately screened by connection block. 100 watt £3.10.0. 250 watt £5.

## SLOW MOTION DRIVES

For coupling to tuning condensers, etc. One end ¼in shaft, the other end fits to a ¼in shaft with grub screws. Price 4/6 each, 48/- dozen.

## LARGE PANEL MOUNTING MOVING COIL METERS

Size 5in × 4in Centre zero 200-0-200 micro amp. made by Sangamo Weston. Regular price probably £8. Our price 59/6. Ditto but 100-0-100 79/6.

## A.C. AMMETER

0–5 amps. flush mounting—moving iron. Ex equipment but guaranteed perfect 29/6.

## CIRCUIT BOARDS

Heavy copper on 3/32 paxolin sheet ideal for making power packs, etc., as sheet is very strong and thick enough to allow copper to be cut away with hacksaw blade. 5in × 5in 1/6 each. 15in × 5in, 4/6 each.

## 6kVA AUTO-TRANSFORMER

In ventilated sheet steel case—tapped 110V–140V–170V–200V–230V. Ex equipment but guaranteed perfect £19.10.0, carriage at cost.

## PP3 BATTERY ELIMINATOR



Run your small transistor radio from the mains—full wave circuit. Made up ready to wire into your set and adjustable high or low current. 8/6 each.

## REED SWITCHES



Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types:

**Miniature.** 1in long × approximately ¼in diameter. Will make and break up to ½A up to 300 volts. Price 2/6 each, 24/- dozen.

**Standard.** 2in long × ⅝in diameter. This will break currents of up to 1A, voltages up to 250 volts. Price 2/- each, 18/- per dozen.

**Flat.** Flat type, 2in long, just over ⅛in thick, flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1 amp 200 volts. Price 6/- each. £3 per dozen.

Small ceramic magnets to operate these reed switches 1/9 each. 18/- dozen.

## 0·005mFd TUNING CONDENSER



Proved design, ideal for straight or reflex circuits 2/6 each, 24/- dozen.

## SUB-MINIATURE MOVING COIL MICROPHONE

**as used in behind the ear deaf-aids**

Acts also as earphone size only ¼in × ⅜in × ¼in. Regular price probably £3 or more. Our price 19/6. Note these are ex equipment but if not in perfect working order they will be exchanged.

## CHART RECORDER MOTOR

Small (2in diameter approx.) instrument motor with fixing flange and spindle (⅛in long, ¼in diameter) integral gear box gives 1 rev. per 24 hours. 19/6.

## IGNITION (E.H.T.) TRANSFORMER

Made by Parmeko Ltd., Primary 240V 50Hz. Secondary 5kV at 23mA. Size approx. 4¼in × 3¼in × 2¼in thick. 29/6 plus 4/6 P. & P.



## 12 VOLT EXTRACTOR FAN BY DELCO

Ideal for ventilation in Caravan, Car or Boat. 6 Bladed 5in diameter fan inside heavy duty cylinder with 3 point fixing flange. 5¼in diameter fixing hole. Length approx. 8¼in. Exceptional bargain 27/6 plus 5/6 post and insurance.

## INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A once-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade device, definitely not sub-standard or seconds. The ICs are all single silicon chip General Purpose Amplifiers. Regular price of which is well over £1 each. Full circuit details of the ICs are included and in addition you will receive a list of 50 different ICs available at bargain prices 5/- upwards with circuits and technical data of each. Complete parcel only £1 post paid; or List and all data 10/- post free. Credited when you order ICs value 30/- and upwards.



## 24-HOUR TIME SWITCH

Mains operated. Adjustable Contacts give 2 on/offs per 24 hours. Contracts rated 15 amps. repeating mechanism so ideal for shop window control, or to switch hall lights (anti-burglar precaution) while you are on holiday. Made by the famous Smiths Company. This month only 39/6 with Perspex cover, plus 3/6 postage and insurance, a real snip which should not be missed.

## DISTRIBUTION PANELS



Just what you need for work bench or lab. 4 × 13 amp sockets and on/off switch with neon warning light in metal box. Takes standard 13 amp fused plugs. Supplied complete with 7 feet of heavy cable.
39/6 wired up, ready to work plus 4/6 post and insurance.
5 amp 3 pin model 35/-. 15 amp 3 pin model 45/-.

## BARGAIN OF THE YEAR

## MICROSONIC RADIOS




7 transistor Key chain Radio in very pretty case, size 2¼ × 2½ × 1¼in—complete with soft leather zipped bag. Specification:—Circuit: 7 transistor superheterodyne. Frequency range: 530 to 1,600 Kc/s. Sensitivity: 5 mv/m. Intermediate frequency: 465Kc/s, or 455Kc/s. Power output: 40mW. Antenna: ferrite rod. Loudspeaker: Permanent magnet type. In transit from the East these sets suffered slight corrosion as the batteries were left in them but when this corrosion is cleared away they should work perfectly—offered without guarantee except that they are new. Price only 24/6 plus 2/6 post and insurance, less batteries. 6 for £7, post free.

## THE 5-5 WATT STEREO AMPLIFIER

Made by one of our most famous makers for a de-luxe player. This amplifier has a quality of reproduction much better than average. Using a total 16 transistors and a generously sized mains power pack. Controls include bass, treble, balance and volume. Suitable for 8–16 ohms impedance speakers with crossovers for tweeter mid-range and bass thus giving option of 1, 2 or 3 speakers per channel. Offered at about one third of its original price only £9.19.6 plus 6/6 post and insurance.

## OUT OF SEASON BARGAIN

## 3 kW TANGENTIAL HEATER UNIT

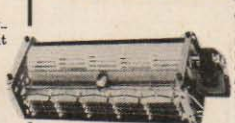

This heater unit is the very latest type, most efficient and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW element and 1kW element allowing switching 1, 2 and 3kW and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only need control switch. 59/6. 2kW Model as above except 2 kilowatts 39/6. Postage and insurance 6/6. Don't miss this.

## THIS MONTH'S SNIP

## AUTO ELECTRIC CAR AERIAL



With dash board control switch—fully extendable to 40" or fully retracted. Suitable for 12V positive or Neg. earth—supplied complete with fitting instructions and ready wired dash board switch £5.18.6 plus 5/-. p. & p.

## RECORD CHANGER BARGAIN



The "Princess" 4-speed automatic record changer and player for beauty, long-life. Will take up to ten records which may be mixed, stylus brush cleans stylus after each playing—other features include pick-up height adjustment and stylus pressure adjustment. This truly is a fine instrument which is a cancelled export order. Therefore they have travelled back and forth and may need mechanical re-adjustment. We offer these at less than the price of a single player—only 49/6 plus 8/6 p. & p. 200-240V.

## STANDARD WAFER SWITCHES



Standard size 1½ wafer—silver-plated 5-amp contact, standard ¼in spindle 2in long—with locking washer and nut.

No. of Poles 2 way 3 way 4 way 5 way 6 way 8 way 9 way 10 way 12 way

| | | | | | | | | | |
|---|---|---|---|---|---|---|---|---|---|
| 1 pole | 6/6 | 6/6 | 6/6 | 6/6 | 6/6 | 6/6 | 6/6 | 6/6 | 6/6 |
| 2 poles | 6/6 | 6/6 | 6/6 | 6/6 | 6/6 | 6/6 | 6/6 | 10/6 | 10/6 |
| 3 poles | 6/6 | 6/6 | 6/6 | 6/6 | 10/6 | 10/6 | 10/6 | 14/6 | 14/6 |
| 4 poles | 6/6 | 6/6 | 6/6 | 10/6 | 10/6 | 10/6 | 10/6 | 18/6 | 18/6 |
| 5 poles | 6/6 | 6/6 | 10/6 | 10/6 | 14/6 | 14/6 | 14/6 | 22/6 | 22/6 |
| 6 poles | 6/6 | 10/6 | 10/6 | 10/6 | 14/6 | 14/6 | 14/6 | 26/6 | 26/6 |
| 7 poles | 10/6 | 10/6 | 10/6 | 14/6 | 18/6 | 18/6 | 18/6 | 30/6 | 30/6 |
| 8 poles | 10/6 | 10/6 | 10/6 | 14/6 | 18/6 | 18/6 | 18/6 | 34/6 | 34/6 |
| 9 poles | 10/6 | 10/6 | 14/6 | 14/6 | 22/6 | 22/6 | 22/6 | 38/6 | 38/6 |
| 10 poles | 10/6 | 10/6 | 14/6 | 18/6 | 22/6 | 22/6 | 22/6 | 42/6 | 42/6 |
| 11 poles | 10/6 | 14/6 | 14/6 | 18/6 | 26/6 | 26/6 | 26/6 | 46/6 | 46/6 |
| 12 poles | 10/6 | 14/6 | 14/6 | 18/6 | 26/6 | 26/6 | 26/6 | 50/6 | 50/6 |

Where postage is not stated then orders over £5 are post free. Below £5 add 2/9. Semiconductors add 1/- post. Over £1 ost free. S.A.E. with enquiries please.

## NEED A SPECIAL SWITCH?

## Double Leaf Contact



Very slight pressure closes both contacts, 1/6 each, 12/- doz. Plastic push-rod suitable for operating, 1/- each, 9/- doz.

## COMPUTER MULTI-CORE CABLES

12, 14/0076 copper cores, each one insulated by coloured P.V.C. then separately screened, the 12 metal braided cores laid together and P.V.C. covered overall making a cable just under ½ in. dia. but quite pliable. Price 7/6 per ft. Any length cut. Other sizes available 7 core 5/- ft., 6 core 4/- ft., 4 core 3/6 ft.

## INSULATED TERMINAL HEADS

Make your own terminal and save half the cost. 2BA 6d each, 5/- doz. 4BA 5d each, 4/- doz.

## MAINS TRANSFORMER BARGAIN

Normal mains primary 250V tapped 230V—four secondaries 350–0–350 @ 150MA, 100V @ 20MA, 6·3V @ 3A, 4V @ 2A—upright mounting size 5 × 4½ × 3½ in approx. Price 35/- plus 7/6 post, etc.

## RING MAIN (13 AMP) SPUR BOX

for joining water heaters—clocks and all auto devices to ring main—white bakelite, fused, made by G.E.C. 2/- each, 18/- doz.


## 250V 15 AMP CHANGEOVER SWITCH

Double pole with centre off—suitable reversing or series parallel circuits—useful for heating control and to prolong life of floodlamps—2/6 each, 24/- doz.


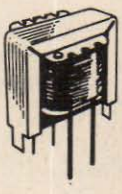
## Instrument Knobs

½in dia. head with ¼in shank for flatted ¼in spindle, 9d each, 8/- dozen. Ditto but with metal disc, 1/- each, 11/- dozen.




## Midget Output Transformer

Ratio 140 : 1. Size approx. 1in × ⅞in × ⅞in, primary impedance 450Ω. Connection by flying leads. 4/6 each, 48/- doz.
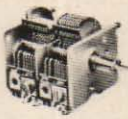
## Midget Output Transformer

Ratio 80 : 1. Size approx. 1¼in × 1in × ⅞in. Primary impedance 132Ω. Printed circuit board connection. 5/6 each, £3 doz.



## 4-Gang Air Spaced Tuning Condenser

For AM/FM circuits. AM rf section 200 pf osc section 80 pf both with trimmers.—FM rf section 9·5 pf osc section 11·2 pf—integral slow-motion drive. 9/6 each.

## Mains Connector



A quick way to connect equipment to the mains safely and firmly—L., N. and E. coded to new colour scheme; disconnection by plugs prevents accidental switching on; has sockets which allow insertion of meter without disconnection; cable inlets firmly hold one hair wire on up to four 7.029 cables. 12/6 each.




## DRILL CONTROLLER

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. 19/6 plus 2/6 post and insurance. Made up model also available, 37/6 plus 2/6 p. & p.

## ELECTRIC CLOCK WITH 25 AMP SWITCH



Made by Smith's, these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only 39/6, less than the value of the clock alone—post and insurance 2/9.

# ELECTRONICS (CROYDON) LTD

**Dept. PE, 266 London Road, Croydon CRO 2TH**

**Also 102/3 Tamworth Road, Croydon**

# BOOKS BY G.A. BRIGGS

OVER A QUARTER OF A MILLION COPIES SOLD SINCE 1948

**AERIAL HANDBOOK**
**(second edition)**
176 pages, 144 illustrations.
PRICE (semi-stiff cover) 15/- (16/6 post free).
Cloth bound 22/6 (24/- post free).



**CABINET HANDBOOK**
112 pages, 90 illustrations.
PRICE 7/6 (8/6 post free). Semi-stiff cover.
Cloth bound 15/- (16/6 post free).



**AUDIO BIOGRAPHIES**
344 pages, 64 contributions from pioneers and leaders in Audio. Cloth bound.
PRICE 25/- (27/- post free).



**MUSICAL INSTRUMENTS AND AUDIO**
240 pages, 212 illustrations. Cloth bound.
PRICE 32/6 (34/6 post free).



**LOUDSPEAKERS**
Fifth edition—336 pages, 230 illustrations.
Cloth bound. PRICE 30/- (32/6 post free).



**A TO Z IN AUDIO**
224 pages, 160 illustrations. Cloth bound.
PRICE 15/6 (17/- post free).



**PIANOS, PIANISTS AND SONICS**
190 pages, 102 illustrations. Cloth bound.
PRICE 18/6 (20/- post free).



**ABOUT YOUR HEARING**
132 pages, 112 illustrations.
PRICE (semi-stiff cover) 15/6 (16/6 post free).
Cloth bound 22/6 (24/- post free).



## READERS OPINIONS

I have recently been going through eight of your books and they have been a feast of information. I have been like a dog with eight tasty dishes, not knowing which one to tackle first but nipping about and sampling each one.
Somerset, Sept. 69

Having read the majority of your "Bibles on Hi Fi", of such a remarkably "hi" standard, I eagerly await a copy of your Cabinet Handbook.
London N22, Nov. 69

*Please send orders and enquiries to:—*

**RANK WHARFEDALE BOOK DEPT. B.W.S.**
**13 WELLS ROAD ILKLEY YORKS**
**Telephone: ILKLEY 4246**

**Published by**
**RANK WHARFEDALE LIMITED IDLE BRADFORD YORKSHIRE**



# XCELITE

Precision made hand tools for the professional



74CG

**PLIERS**




69CG

69CG Radio-TV Pliers
70CG Flat Nose Pliers
71CG Round Nose Pliers
72CG Chain Nose Pliers
73CG Tip Cutting Pliers
74CG Diagonal Close Cutting Pliers

A complete range of miniature lightweight pliers especially designed for holding, bending, shaping and cutting of fine wires in electronic, Radio/TV, electrical and jewellery work.

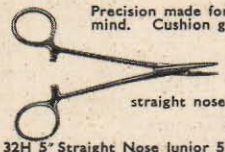Precision made for the expert with miniatures in mind. Cushion grip handle, coil spring openers.



straight nose



curved nose

**SEIZERS**

32H 5" Straight Nose Junior 5" Seizer
35H 5" Curved Nose Junior 5" Seizer
42H 6" Straight Nose Seizer
43H 6" Curved Nose Seizer

Box joint construction, two position snap on lock. Precision machined from perfectly tempered steel.
Holds like surgical clamp and acts as heat sink.
Straight or curved nose, in 5" and 6" sizes.

*Distributed by*

Special Products Distributors Limited
81 Piccadilly, London, W.1
Tel. 01-629 9556 Cables: SPECIPROD, London, W.1
*Full details an request* *Made in U.S.A.*



# VALVES

**SAME DAY SERVICE**
**NEW! TESTED! GUARANTEED!**

**SETS** 1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94. Set of 4 for 18/6. DAF96, DF96, DK96, DL96, 4 for 27/-

| | | | | | | | | | | | |
|---|---|---|---|---|---|---|---|---|---|---|---|
| OZ4 | 4/6 | 20P3 | 11/9 | DK96 | 7/3 | EL38 | 17/6 | PCL82 | 7/3 | UBC41 | 9/- |
| 1A7GT | 7/6 | 20P4 | 18/6 | DL35 | 5/- | EL41 | 11/- | PCL83 | 12/- | UBF80 | 5/9 |
| 1H5GT | 7/3 | 25L6GT | 5/- | DL92 | 5/9 | EL84 | 4/9 | PCL84 | 7/6 | UBF89 | 6/9 |
| 1N5GT | 7/9 | 25U4GT | 11/6 | DL94 | 6/3 | EL90 | 4/6 | PCL85 | 9/- | UCC84 | 7/- |
| 1R5 | 5/9 | 30C1 | 6/6 | DL96 | 7/3 | EL500 | 12/6 | PCL86 | 8/3 | UCC85 | 7/3 |
| 1S5 | 4/3 | 30C15 | 13/- | DY86 | 5/9 | EM80 | 8/3 | PCL88 | 14/6 | UCF80 | 7/3 |
| 1T4 | 2/9 | 30C17 | 16/- | DY87 | 5/9 | EM81 | 8/3 | PCL800 | 15/6 | UCH42 | 12/6 |
| 3S4 | 5/9 | 30C18 | 13/6 | EABC80 | 6/6 | EM84 | 6/9 | PENA4 | 8/6 | UCH81 | 6/6 |
| 3V4 | 6/3 | 30F5 | 16/- | EAF42 | 10/- | EM87 | 7/6 | PFL200 | 11/9 | UCL82 | 7/- |
| 5Y3GT | 5/9 | 30FL1 | 12/9 | EB91 | 2/3 | EY51 | 7/3 | PL36 | 9/9 | UCL83 | 11/9 |
| 5Z4G | 7/6 | 30FL12 | 14/6 | EBC33 | 8/- | EY86 | 6/6 | PL81 | 9/3 | UF41 | 10/6 |
| 6/30L2 | 12/- | 30FL14 | 14/6 | EBC41 | 9/6 | EZ40 | 8/- | PL82 | 6/6 | UF85 | 6/9 |
| 6AL5 | 2/3 | 30L1 | 6/6 | EBF80 | 6/9 | EZ41 | 8/- | PL83 | 6/6 | UF89 | 6/9 |
| 6AM6 | 2/9 | 30L15 | 13/- | EBF89 | 6/3 | EZ80 | 4/6 | PL84 | 6/6 | UL41 | 12/- |
| 6AQ5 | 4/6 | 30L17 | 15/6 | ECC81 | 3/9 | EZ81 | 4/9 | PL500 | 18/- | UL44 | 20/- |
| 6AT6 | 4/- | 30P4 | 12/- | ECC82 | 4/9 | GZ32 | 8/9 | PL504 | 13/6 | UL84 | 7/- |
| 6AU6 | 4/6 | 30P12 | 13/9 | ECC83 | 7/- | KT41 | 15/6 | PL508 | 23/6 | UM80 | 5/- |
| 6BA6 | 4/6 | 30P19 | 12/- | ECC85 | 5/- | KT61 | 9/9 | PM84 | 7/6 | UM84 | 4/6 |
| 6BE6 | 4/9 | 30PL1 | 13/9 | ECC804 | 12/- | KT66 | 16/9 | PX25 | 23/6 | UY41 | 7/6 |
| 6BJ6 | 8/6 | 30PL13 | 15/6 | ECF80 | 6/6 | LN329 | 14/6 | PY32 | 10/- | UY85 | 5/9 |
| 6C5G | 4/9 | 30PL14 | 14/6 | ECF82 | 6/6 | N78 | 17/6 | PY33 | 10/- | VP4B | 15/6 |
| 6F13 | 3/6 | 35L6GT | 8/9 | ECH35 | 6/- | P61 | 10/- | PY81 | 5/3 | W77 | 3/6 |
| 6F14 | 9/- | 35W4 | 4/6 | ECH42 | 13/6 | PABC80 | 7/- | PY82 | 5/3 | W119 | 7/- |
| 6F23 | 14/3 | 35Z4GT | 5/- | ECH81 | 5/9 | PC86 | 10/3 | PY83 | 5/9 | Z77 | 2/9 |
| 6F25 | 13/- | 807 | 9/- | ECH83 | 8/3 | PC88 | 10/3 | PY88 | 6/9 | AC107 | 3/6 |
| 6J5G | 4/9 | 6063 | 12/6 | ECH84 | 7/6 | PC96 | 8/6 | PY800 | 7/6 | AC127 | 2/6 |
| 6K7G | 2/6 | AC/VP2 | 15/6 | ECL80 | 7/- | PC97 | 8/- | PY801 | 7/6 | AD140 | 7/6 |
| 6K8G | 2/9 | AZ31 | 9/6 | ECL82 | 6/9 | PC900 | 7/6 | R19 | 6/6 | AF115 | 3/- |
| 6SN7GT | 4/3 | B349 | 13/- | ECL86 | 8/- | PCC84 | 6/6 | R20 | 12/6 | AF116 | 3/- |
| 6V6G | 3/3 | B729 | 12/6 | EF37A | 6/6 | PCC85 | 6/- | U25 | 13/- | AF117 | 4/- |
| 6V6GT | 6/6 | CCH35 | 13/6 | EF39 | 4/9 | PCC88 | 9/- | U26 | 12/- | AF125 | 3/6 |
| 6X4 | 4/3 | CL33 | 18/6 | EF41 | 11/9 | PCC89 | 10/6 | U47 | 13/6 | AF127 | 3/6 |
| 0X5GT | 5/9 | CY31 | 6/9 | EF80 | 4/6 | PCC189 | 10/6 | U49 | 13/6 | OC26 | 5/- |
| 10F1 | 14/- | DAC32 | 7/3 | EF85 | 6/3 | PCC805 | 13/- | U78 | 4/3 | OC44 | 2/6 |
| 10F18 | 7/- | DAF91 | 4/3 | EF86 | 6/3 | PCF80 | 6/6 | U191 | 12/6 | OC45 | 2/6 |
| 10P13 | 12/- | DAF96 | 7/3 | EF89 | 5/3 | PCF82 | 6/6 | U193 | 8/6 | OC71 | 2/6 |
| 12AT7 | 3/9 | DF33 | 7/9 | EF91 | 2/9 | PCF86 | 10/- | U251 | 14/6 | OC72 | 2/6 |
| 12AU6 | 4/9 | DF91 | 2/9 | EF94 | 4/6 | PCF800 | 13/6 | U301 | 10/6 | OC75 | 2/6 |
| 12AU7 | 4/9 | DF96 | 7/3 | EF183 | 5/9 | PCF801 | 6/9 | U329 | 14/6 | OC81 | 2/6 |
| 12AX7 | 4/9 | DH77 | 4/- | EF184 | 6/6 | PCF802 | 9/- | U801 | 19/6 | OC81D | 2/6 |
| 12K8GT | 7/3 | DK32 | 7/6 | EH90 | 6/3 | PCF805 | 13/6 | | | OC82 | 2/6 |
| 19BG6G | 17/6 | DK91 | 5/9 | EL33 | 9/9 | PCF806 | 12/9 | UABC80 | 6/6 | OC82D | 2/6 |
| 20F2 | 13/6 | DK92 | 8/6 | EL34 | 9/6 | PCF808 | 14/6 | UAF42 | 10/3 | OC170 | 4/6 |

# READERS RADIO (P.E.)

**85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441**

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.

# ELECTROVALUE

## EVERYTHING BRAND NEW AND TO SPECIFICATION • LARGE STOCKS

## BARGAINS IN NEW SEMICONDUCTORS

All power types supplied with free insulating sets

| | | | | | | | | | |
|---|---|---|---|---|---|---|---|---|---|
| 1N914 | 1/3 | 2N3706 | 3/3 | 40512 | 45/6 | BC147 | 3/6 | BFY51 | 4/3 |
| 1N3754 | 4/– | 2N3707 | 4/– | 40602 | 9/6 | BC148 | 3/3 | BSX20 | 3/9 |
| 1N4148 | 1/9 | 2N3708 | 3/– | AC107 | 14/6 | BC149 | 3/6 | BY164 | 10/– |
| 1N5054 | 4/– | 2N3709 | 3/– | AC126 | 6/6 | BC153 | 10/– | BY238 | 3/6 |
| 18940 | 1/– | 2N3710 | 3/6 | AC127 | 6/– | BC154 | 11/– | C106B1 | 14/6 |
| 2N696 | 5/6 | 2N3711 | 3/11 | AC128 | 6/– | BC157 | 3/9 | MC140 | 5/– |
| 2N697 | 5/6 | 2N3731 | 24/– | AC176 | 11/– | BC158 | 3/6 | MJ480 | 21/– |
| 2N706 | 2/9 | 2N3794 | 3/3 | ACY22 | 3/9 | BC159 | 3/9 | MJ481 | 27/– |
| 2N1302 | 4/– | 2N3819 | 8/6 | ACY40 | 4/– | BC167 | 2/6 | MJ491 | 30/– |
| 2N1303 | 4/– | 2N3820 | 25/6 | ACY41 | 5/– | BC168 | 2/3 | MPF102 | 7/6 |
| 2N1304 | 4/6 | 2N3904 | 7/6 | AD142 | 14/3 | BC169 | 2/6 | NKT403 | 15/6 |
| 2N1305 | 4/6 | 2N3906 | 7/6 | AD149 | 17/6 | BC177 | 6/3 | NKT405 | 15/– |
| 2N1306 | 6/9 | 2N4058 | 5/3 | AD161/AD162 | | BC178 | 5/8 | OA47 | 1/9 |
| 2N1307 | 6/9 | 2N4059 | 4/– | (matched) | 16/– pr. | BC179 | 6/– | OA90 | 1/3 |
| 2N1308 | 8/9 | 2N4060 | 4/3 | AF114 | 7/– | BC182L | 4/3 | OA91 | 1/3 |
| 2N1309 | 8/9 | 2N4061 | 4/3 | AF115 | 7/– | BC183L | 2/3 | OA95 | 1/3 |
| 2N1613 | 6/– | 2N4062 | 4/3 | AF116 | 6/6 | BC184L | 2/6 | OA99 | 3/– |
| 2N1711 | 7/– | 2N4284 | 3/3 | AF117 | 6/6 | BC186 | 8/6 | OA200 | 1/11 |
| 2N2147 | 18/9 | 2N4286 | 3/3 | AF124 | 7/6 | BC212L | 5/– | OA202 | 2/– |
| 2N2218 | 9/3 | 2N4289 | 3/3 | AF127 | 7/– | BC213L | 5/– | OC71 | 5/6 |
| 2N2270 | 12/9 | 2N4291 | 3/3 | AF139 | 9/6 | BC214L | 5/3 | TIP31A | 17/6 |
| 2N2484 | 13/6 | 2N4292 | 3/3 | AF180 | 18/6 | BCY70 | 5/6 | TIP32A | 23/9 |
| 2N2646 | 10/9 | 2N4410 | 4/9 | AF239 | 9/9 | BD121 | 18/– | TIS43 | 10/6 |
| 2N2904 | 11/– | 2N5062 | 12/3 | ASY26 | 6/6 | BD123 | 24/3 | ZTX300 | 3/6 |
| 2N2924 | 4/– | 2N5163 | 5/– | ASY27 | 8/3 | BD124 | 16/– | ZTX301 | 3/6 |
| 2N2925 | 4/6 | 2N5192 | 25/– | ASY28 | 6/6 | BF167 | 8/6 | ZTX302 | 4/6 |
| 2N2926 | 2/3 | 2N5195 | 28/3 | B5041 | 15/– | BF178 | 10/6 | ZTX303 | 4/6 |
| 2N3053 | 5/6 | 2N5457 | 9/9 | BA102 | 9/– | BF180 | 12/– | ZTX304 | 6/9 |
| 2N3054 | 14/3 | 2N5458 | 9/9 | BA156 | 4/– | BF194 | 7/– | ZTX500 | 5/– |
| 2N3055 | 16/– | 2N5459 | 9/9 | BA130 | 4/6 | BF195 | 7/6 | ZTX501 | 5/– |
| 2N3325 | 10/9 | 40250 | 14/3 | BA145 | 5/6 | BFX29 | 10/9 | ZTX502 | 6/– |
| 2N3663 | 11/6 | 40361 | 12/6 | BC107 | 2/9 | BFX84 | 7/5 | ZTX503 | 5/– |
| 2N3702 | 3/6 | 40362 | 16/– | BC108 | 2/6 | BFX85 | 8/3 | ZTX504 | 12/– |
| 2N3703 | 3/3 | 40406 | 16/3 | BC109 | 2/9 | BFX87 | 8/6 | ZTX530 | 5/5 |
| 2N3704 | 3/9 | 40408 | 14/6 | BC125 | 12/– | BFX88 | 6/9 | ZTX531 | 6/9 |
| 2N3705 | 3/5 | 40430 | 37/– | BC126 | 12/– | BFY50 | 4/6 | | |

## RESISTORS

| Code | Power | Tolerance | Range | Values available | 1 to 9 | 10 to 99 (see note below) | 100 up |
|---|---|---|---|---|---|---|---|
| C | 1/20W | 5% | 82Ω–220kΩ | E12 | 18d | 16d | 15d |
| C | ¼W | 5% | 4·7Ω–330kΩ | E24 | 2·5d | 2d | 1·75d |
| C | ¼W | 10% | 4·7Ω–10MΩ | E12 | 2·5d | 2d | 1·75d |
| C | ½W | 5% | 4·7Ω–10MΩ | E24 | 3d | 2·5d | 2·25d |
| C | 1W | 10% | 4·7Ω–10MΩ | E12 | 6d | 5d | 4·5d |
| MO | ½W | 2% | 10Ω–1MΩ | E24 | 9d | 8d | 7d |
| WW | 1W | 10% ± 1/20Ω | 0·22Ω–3·9Ω | E12 | 15d all quantities | | |
| WW | 3W | 5% | 12Ω–10kΩ | E12 | 15d all quantities | | |
| WW | 7W | 5% | 12Ω–10kΩ | E12 | 18d all quantities | | |

**CODES:** C = carbon film high stability low noise. MO = metal oxide Electrosil TR5 ultra low noise. WW = wire wound Plessey.
**VALUES:** E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

*Prices are in pence each for same ohmic value and power rating, NOT mixed values. (Ignore fractions of 1d on total resistor order.)*

### INTEGRATED CIRCUIT AMPLIFIERS

**SINCLAIR IC.10** complete with instruction book giving amplifier circuit details and range of applications. **59/6** nett.

**PLESSEY SL403A.** Only **48/6** each. 3W into 7·5Ω for 18V supply. Application data with two or more.

### WAVECHANGE SWITCHES LONG SPINDLES

1P 12W; 2P 6W; 3P 4W; 4P 3W .. .. **4/9** each

**SLIDER SWITCHES** D.P.D.T. .. .. .. **3/–** each

### NEON INDICATOR LAMPS all 200/250V

Square bezel, red only .. .. .. .. **3/9**
Round chrome bezel red, amber, clear .. .. **4/9** each
Toggle switches, 250V a.c. 1·5A. Chrome dolly and chrome milled nut S.P.S.T. **3/9**; S.P.D.T. **4/6**; D.P.D.T. **5/9**; S.P.D.T. centre off **5/–**.

**S-DeC's** put an end to "birdsnesting". Components just plug in. Saves valuable time. Use components again and again. S-DeC only **30/–** post free. Compact T-DeC, increased capacity, may be temperature-cycled. T-DeC only **50/–** post free. Full range stocked.

### MULLARD POLYESTER C280 series

250V 20%: 0·01, 0·022, 0·033, 0·047, **8d** ea.; 0·068, 0·1, **9d** ea.; 0·15, **11d**; 0·22, **1/–**. 10%: 0·33, **1/5**; 0·47, **1/8**; 0·68, **2/3**; 1μF, **2/9**; 1·5μF, **4/2**; 2·2μF, **4/9**.

### MULLARD SUB-MIN ELECTROLYTIC

C426 range axial lead **1/3** each
Values (μF/V): 0·64/64, 1/40, 1·6/25, 2·5/16, 2·5/64, 4/10, 4/40, 5/64, 6·4/6·4, 6·4/25, 8/4, 8/40, 10/2·5, 10/16, 10/64, 12·5/25, 16/40, 20/16, 20/16, 20/64, 25/6·4, 25/25, 32/4, 32/10, 32/40, 32/64, 40/16, 40/2·5, 50/6·4, 50/25, 50/40, 64/4, 64/10, 80/2·5, 80/16, 80/25, 100/6·4, 125/4, 125/10, 125/16, 160/2·5, 200/6·4, 200/10, 250/4, 320/2·5, 320/6·4, 400/4, 500/2·5.

### LARGE CAPACITORS

High ripple current types: 1000/25 **5/6**; 1000/50 **8/2**; 1000/100 **16/3**; 2000/25 **7/4**; 2000/50 **11/4**; 2000/100 **28/9**; 2500/64 **15/5**; 2500/70 **19/6**; 5000/25 **12/6**; 5000/50 **21/11**; 5000/100 **58/3**; 10000/15 **17/–**; 10000/25 **24/6**; 10000/50 **44/–**; 10000/70 **61/–**.

### MEDIUM RANGE ELECTROLYTICS

Axial leads: 50/50 **2/–**; 100/25 **2/–**; 100/50 **2/6**; 250/25 **2/6**; 330/25 **2/6**; 250/50 **3/9**; 500/25 **3/9**; 500/50 **4/6**; 1000/25 **4/–**; 1000/50 **6/–**; 2000/25 **6/–**.

### SMALL ELECTROLYTICS

Axial leads: 4·7/10, 4·7/25, 5/50, 1/– ea. 10/10, 10/25, 10/50, 33/10, 50/10, 1/– ea. 25/25, 25/50, 47/25, 100/10, 220/10, **1/3** ea.

### PEAK SOUND PRODUCTS ENGLEFIELD AMPLIFIER



**Build it 12 + 12 or 25 + 25**

Stereo amplifier in modular kit form (including cabinet) 12 watts per channel **£38.9.0**; 25 watts **£58.15.0**. Cabinet kit only **£6**. These prices nett. As recently reviewed in Hi Fi Sound.

### BAXANDALL SPEAKER SYSTEM



Designed by Peter Baxandall. Superb reproduction for its size. Handles 10 watts with ease. Uses ELAC 15Ω 59RM109 speaker unit. Kit **£13.12.0** nett.; built **£19.8.6** nett.

### STEREO AMPLIFIER SA.10-10



Developed from the very successful SA.8-8 amplifier giving first class stereo amplification featuring separate volume controls for each channel, bass and treble controls. 10 watts per channel into 5 to 8Ω. Kit **£19.7.6** nett.; built **£24.16.8** nett. Suitable 8Ω wide range speakers available **£13.15.0** each nett.

### MAINLINE AMPLIFIER KITS

RCA/SGS designed main amplifier kits. Input sensitivity 500–700mV for full output into 8Ω.

| Power | Kit price including components | Suitable unreg. power supply kit |
|---|---|---|
| 12W | 140/– nett | 92/– |
| 25W | 165/– nett | N/A |
| 40W | 195/– nett | 115/1 |
| 70W | 210/– nett | 138/10 |

### 30 WATT BAILEY AMPLIFIER KIT

Special summer reduction (to Sept. 30th, 1970, only). Sensitivity 1·2V for full output into 8Ω. Transistors for one channel **£7.5.6** list, **£6** only nett. Transistors for two channels **£14.11.0** list **£11** only nett. Capacitors and resistors (metal oxide) **30/–** per channel nett. Complete unregulated power supply kit **87/6** nett.

### ZENER DIODES

5% full range E24 values: 400mW: 2·7V to 30V **4/6** ea. 1W: 6·8V to 82V **9/–** ea. 1·5W: 4·7V to 75V **12/–** ea. Clip to increase 1·5W rating to 3 watts (type 266F) **9d.**

### CARBON TRACK POTENTIOMETERS, long spindles.

Double wiper ensures minimum noise level.

| | | |
|---|---|---|
| Single gang linear | 220Ω to 2·2MΩ | 2/6 |
| Single gang log | 4·7KΩ to 2·2MΩ | 2/6 |
| Dual gang linear | 4·7KΩ to 2·2MΩ | 8/6 |
| Dual gang log | 4·7KΩ to 2·2MΩ | 8/6 |
| Log/antilog | 10K, 47K, 1MΩ only | 8/6 |
| Dual antilog | 10K only | 8/6 |

Any type with ¼A D.P. mains switch, extra **2/6**. Please note: only decades of 10, 22 and 47 are available within ranges quoted.

### CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only 100Ω, 220Ω, 470Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10MΩ. Vertical or horizontal mounting **1/–** each.

### COMPONENT DISCOUNTS

10% on orders for components for £5 or more. 15% on orders for components for £15 or more (No discount on nett items).

### POSTAGE AND PACKING

Free on orders over **£2**. Please add 1/6 if under. Overseas orders welcome: carriage charged at cost.

**ELECTROVALUE** **Dept. PE8, 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY**
Hours: 9—5.30; Sat. 1 p.m. Tel.: Egham 5533 (STD 0784-3). Telex 264475

# COMPLETE STEREO SYSTEM

FOR ONLY **39 GNS**

CARRIAGE 35/-



PREMIER STEREO SYSTEM "ONE" Consists of an all transistor stereo amplifier. Garrard 2025 T/C auto/manual record player unit fitted stereo/mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor amplifier has an output of 5 watts per channel with inputs for pick-up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector. Power on/off, stereo/mono switch. Brushed aluminium front panel. Black metal case with teakwood ends: Size 12 × 5½ × 3½in. high (Amplifier available separately if required **£14.19.6.** Carr. 7/6).

**PREMIER STEREO SYSTEM "TWO"**

As system "ONE" above but with Garrard SP25.

**PREMIER PRICE** **45 Gns.** Carr. 35/-




## "VERITONE" RECORDING TAPE

**SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED.**

TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

| | | | | | | | |
|---|---|---|---|---|---|---|---|
| LP3 | 3" | 250' | P.V.C. | 5/6 | LP6 | 5½" 1200' | P.V.C. 12/6 |
| TT3 | 3" | 450' | POLYESTER | 7/6 | DT6 | 5½" 1800' | POLYESTER 22/6 |
| DT3 | 3½" | 600' | POLYESTER | 11/6 | TT6 | 5½" 2400' | POLYESTER 37/6 |
| SP5 | 5" | 600' | P.V.C. | 8/6 | SP7 | 7" 1200' | P.V.C. 12/6 |
| LP5 | 5" | 900' | P.V.C. | 10/- | LP7 | 7" 1800' | P.V.C. 15/- |
| DT5 | 5" | 1200' | POLYESTER | 15/- | DT7 | 7" 2400' | POLYESTER 25/- |
| | | | | | TT7 | 7" 3600' | POLYESTER 50/- |

**TAPE SPOOLS** 3" 1/-, 5", 5½", 7" 1/9.

Post and Packing 3" 1/-, 5", 5½" 1/6, 7" 2/-. (3 reels and over Post Free.)




## TAPE CASSETTES

C60 (60 min.) 7/6 3 for 21/-

C90 (90 min.) 12/6 3 for 36/-

C120 (120 min.) 17/6 3 for 51/-

P. & P. 1/-.

**CASSETTE HEAD CLEANER**

Removes unwanted deposits from delicate tape heads.

Fits all cassette recorders. **11/6** P. & P. 1/-

***All cassettes can be supplied with library cases at 6d extra each.***


# PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1 Tel: 01-636 3451




# And NOW . . . . A NEW KIT
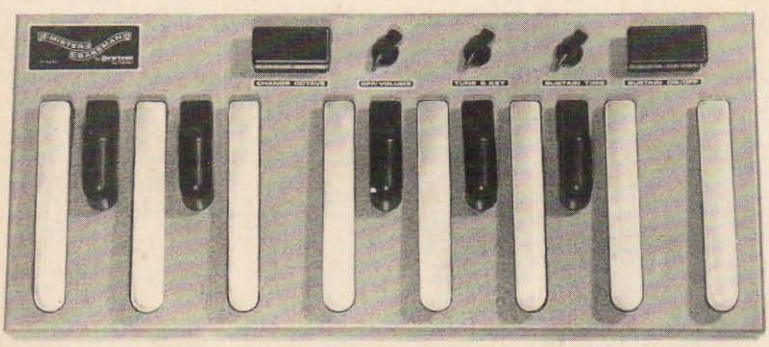
## The famous "MISTER BASSMAN" Model B2M by **Dewtron**



IN NEW COMPLETE "DEW-IT-YOURSELF" **KIT** FORM!

Kit contains steel cabinet, finished hammer-blue, and ALL PARTS and PANEL LABELS. MASTER CIRCUIT MODULE supplied BUILT! Printed wiring mounting board ensures quick and simple assembly in 2–3 hours by average-talent technician. CLEAR CONCISE INSTRUCTIONS, step-by-step.

Direct from makers. **£25** complete kit of parts less batteries. Post paid.

**D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset BH22 9AR**

★ Specially designed to allow use with the Philips Philicorda. Can be connected to Organ Gram socket and used without additional amplifier.

★ Adds effective bass when used with a piano.

★ The versatile tuning feature makes the instrument ideal as accompaniment for guitars, clarinets and many other solo instruments, including one-man bands!

Weight: Approx. 8½lb unboxed.
Dimensions: 50cm × 27·5cm × 9cm (approx).
Output impedance nominally high, but will match wide range of amplifier inputs without distortion.

★ 13-Note Pedal board giving full chromatic scale, nominally C to C, but adjustable by Key control to play in any key desired.

★ Octave Jump switch, giving instant change from 8ft to 16ft pitches and vice-versa at the touch of a foot-switch.

★ Sustain On/Off switch, enabling Sustain to be switched in or out at the touch of a foot-switch.

★ Variable Sustain Time control giving adjustment of sustain from 0 to 3 seconds after any pedal is released, with realistic string-bass effect.

★ Fully adjustable playing key giving a half-octave adjustment in either direction up or down scale, allowing instrument to be played in any key without the need for difficult transposing!

★ Fully adjustable volume control enabling best level to be set to suit any normal amplifier. Very high signal output is possible making the use of additional pre-amplifiers unnecessary.

★ Completely self-contained and independent of mains. Requires only to be plugged into an amplifier. Runs on its own internal batteries, 2 × type PP6. Low current consumption giving months of life with normal playing.

# SEMICONDUCTORS & COMPONENTS

**BRAND NEW** (Saturday callers only 5% Discount) **GUARANTEED**

## TRANSISTORS

| | | | | | | | | | | | |
|---|---|---|---|---|---|---|---|---|---|---|---|
| 2G301 | 4/– | 2N3394 | 4/– | 3N142 | 19/6 | BC160 | 12/6 | BFY52 | 4/6 | NKT225 | 4/6 |
| 2G302 | 4/– | 2N3402 | 4/6 | 3N143 | 19/6 | BC167 | 3/– | BFY53 | 5/6 | NKT229 | 6/– |
| 2G303 | 4/– | 2N3403 | 4/6 | 3N152 | 22/6 | BC168 | 3/6 | BFY56A | 11/– | NKT237 | 7/– |
| 2G306 | 8/6 | 2N3404 | 7/6 | R.C.A.:— | | BC168B | 2/9 | BFY75 | 6/– | NKT238 | 5/– |
| 2G308 | 6/– | 2N3405 | 9/– | 40050 | 13/6 | BC168C | 3/– | BFY76 | 8/– | NKT240 | 5/6 |
| 2G309 | 6/– | 2N3414 | 5/6 | 40250 | 10/– | BC169 | 3/6 | BFY77 | 11/6 | NKT241 | 5/6 |
| 2G371 | 3/– | 2N3415 | 6/6 | 40251 | 19/6 | BC169B | 2/9 | BFY85 | 9/– | NKT10419 | |
| 2G374 | 4/– | 2N3416 | 7/6 | 40309 | 8/– | BC169C | 3/6 | BFY90 | 13/6 | | 6/– |
| 2G381 | 4/6 | 2N3417 | 7/6 | 40310 | 11/6 | BC170 | 3/6 | BFW58 | 5/6 | NKT10439 | |
| 2N404 | 4/6 | 2N3570 | 17/6 | 40311 | 9/6 | BC171 | 3/6 | BFW59 | 5/– | | 7/6 |
| 2N696 | 4/– | 2N3572 | 17/6 | 40312 | 12/6 | BC172 | 3/6 | BFW60 | 5/– | NKT10519 | |
| 2N697 | 4/– | 2N3605 | 5/6 | 40314 | 9/6 | BC175 | 5/6 | BPX25 | 37/– | | 6/6 |
| 2N698 | 5/– | 2N3606 | 5/6 | 40315 | 9/6 | BC182 | 4/6 | BPX29 | 36/– | NKT20329 | |
| 2N706 | 2/6 | 2N3607 | 4/6 | 40316 | 12/6 | BC182L | 4/– | BPY10 | 29/– | | 9/6 |
| 2N706A | 2/6 | 2N3662 | 7/6 | 40317 | 9/6 | BC183 | 4/6 | BRY39 | 9/6 | NKT20339 | |
| 2N708 | 3/– | 2N3663 | 7/6 | 40319 | 13/6 | BC184 | 4/6 | BSX19 | 3/6 | | 7/6 |
| 2N709 | 12/6 | 2N3702 | 3/6 | 40344 | 7/– | BC212L | 4/6 | BSX20 | 3/6 | NKT80111 | |
| 2N718 | 5/– | 2N3703 | 4/6 | 40347 | 8/6 | BCY30 | 5/6 | BSX21 | 7/6 | | 15/6 |
| 2N726 | 6/– | 2N3704 | 4/6 | 40348 | 12/6 | BCY31 | 5/6 | BSX26 | 9/– | NKT80112 | |
| 2N727 | 6/– | 2N3705 | 4/– | 40360 | 11/– | BCY32 | 7/6 | BSX27 | 9/6 | | 19/6 |
| 2N914 | 3/6 | 2N3706 | 4/6 | 40361 | 12/6 | BCY33 | 4/– | BSX28 | 6/6 | NKT80113 | |
| 2N916 | 3/6 | 2N3707 | 4/– | 40362 | 13/6 | BCY34 | 4/6 | BSX60 | 16/6 | | 22/6 |
| 2N918 | 6/– | 2N3708 | 3/6 | 40370 | 7/6 | BCY38 | 4/6 | BSX61 | 12/6 | NKT80211 | |
| 2N929 | 4/6 | 2N3709 | 3/6 | 40406 | 14/6 | BCY39 | 8/6 | BSX76 | 4/6 | | 18/6 |
| 2N930 | 5/6 | 2N3710 | 4/– | 40407 | 11/6 | BCY40 | 7/6 | BSX77 | 5/6 | NKT80212 | |
| 2N987 | 10/6 | 2N3711 | 4/– | 40408 | 12/6 | BCY42 | 3/– | BSX78 | 5/6 | | 18/6 |
| 2N1090 | 6/6 | 2N3819 | 7/– | 40409 | 14/– | BCY43 | 3/– | BSY24 | 3/– | NKT80213 | |
| 2N1091 | 6/6 | 2N3823 | 22/6 | 40410 | 16/– | BCY54 | 6/6 | BSY25 | 3/– | | 18/6 |
| 2N1131 | 5/6 | 2N3854 | 5/6 | 40467 | 14/6 | BCY58 | 4/6 | BSY26 | 3/6 | NKT80214 | |
| 2N1132 | 6/6 | 2N3854A | 5/6 | 40468A | 14/6 | BCY59 | 4/6 | BSY27 | 3/6 | | 18/6 |
| 2N1302 | 3/6 | 2N3855 | 5/6 | 40600 | 14/6 | BCY60 | 19/6 | BSY28 | 3/6 | NKT80215 | |
| 2N1303 | 3/6 | 2N3855A | 6/– | AC107 | 6/– | BCY70 | 4/– | BSY29 | 3/6 | | 18/6 |
| 2N1304 | 4/6 | 2N3856 | 6/– | AC126 | 4/– | BCY71 | 8/6 | BSY32 | 5/– | NKT80216 | |
| 2N1305 | 4/6 | 2N3856A | 7/– | AC127 | 5/– | BCY72 | 3/6 | BSY36 | 5/– | | 18/6 |
| 2N1306 | 5/– | 2N3858 | 5/– | AC128 | 4/– | BCZ10 | 5/6 | BSY37 | 5/– | OC20 | 15/– |
| 2N1307 | 5/– | 2N3858A | 6/– | AC154 | 4/6 | BCZ11 | 7/6 | BSY38 | 4/6 | OC22 | 10/– |
| 2N1308 | 6/– | 2N3859 | 5/6 | AC176 | 5/– | BD116 | 22/6 | BSY39 | 4/6 | OC23 | 10/– |
| 2N1309 | 6/– | 2N3859A | 6/6 | AC187 | 12/– | BD121 | 13/– | BSY40 | 6/6 | OC24 | 11/6 |
| 2N1507 | 5/6 | 2N3860 | 6/– | AC188 | 7/6 | BD123 | 16/6 | BSY51 | 6/6 | OC25 | 10/– |
| 2N1613 | 5/– | 2N3866 | 30/– | ACY17 | 5/– | BD124 | 12/– | BSY52 | 6/6 | OC26 | 6/6 |
| 2N1631 | 8/6 | 2N3877 | 8/– | ACY18 | 5/– | BD131 | 24/– | BSY53 | 7/6 | OC28 | 12/6 |
| 2N1632 | 8/6 | 2N3877A | 8/– | ACY19 | 5/– | BD132 | 24/– | BSY54 | 8/– | OC29 | 15/– |
| 2N1637 | 8/6 | 2N388A | 12/6 | ACY20 | 5/– | BDY10 | 27/6 | BSY56 | 18/– | OC30 | 8/– |
| 2N1638 | 7/6 | 2N3900 | 7/6 | ACY21 | 5/– | BDY11 | 37/6 | BSY79 | 9/– | OC35 | 8/– |
| 2N1639 | 7/6 | 2N3900A | 8/– | ACY22 | 4/– | BDY17 | 37/6 | BSY82 | 10/6 | OC36 | 12/6 |
| 2N1711 | 5/– | 2N3901 | 19/6 | ACY28 | 4/– | BDY18 | 49/6 | BSY90 | 11/6 | OC38 | 10/6 |
| 2N1889 | 6/6 | 2N3903 | 7/– | ACY40 | 4/– | BDY19 | 62/6 | BSY95A | 2/6 | OC41 | 4/6 |
| 2N1893 | 8/6 | 2N3904 | 7/– | ACY41 | 5/– | BDY20 | 22/6 | BSW41 | 8/6 | OC42 | 5/– |
| 2N2147 | 14/6 | 2N3905 | 7/6 | ACY44 | 8/– | BDY38 | 19/6 | BSW70 | 5/6 | OC44 | 4/– |
| 2N2148 | 12/6 | 2N3906 | 7/6 | ADI40 | 8/– | BDY60 | 36/– | D16P1 | 7/6 | OC45 | 2/6 |
| 2N2160 | 11/6 | 2N4058 | 5/6 | ADI49 | 11/6 | BDY61 | 36/– | D16P2 | 8/– | OC46 | 3/– |
| 2N2193 | 9/6 | 2N4059 | 5/– | ADI50 | 12/6 | BDY62 | 27/6 | D16P3 | 7/6 | OC70 | 3/– |
| 2N2193A | 10/– | 2N4060 | 5/– | ADI61 | 7/6 | BFI15 | 5/– | D16P4 | 8/– | OC71 | 2/6 |
| 2N2194A | 4/6 | 2N4061 | 4/6 | ADI62 | 7/6 | BFI17 | 9/6 | GET102 | 6/– | OC72 | 2/6 |
| 2N2217 | 5/6 | 2N4062 | 4/6 | AFI06 | 8/6 | BFI63 | 7/6 | GET113 | 4/– | OC74 | 6/6 |
| 2N2218 | 6/– | 2N4244 | 9/6 | AFI14 | 5/– | BFI67 | 5/– | GET114 | 4/– | OC75 | 4/6 |
| 2N2219 | 6/– | 2N4255 | 8/6 | AFI15 | 6/– | BFI73 | 6/6 | GET118 | 4/– | OC76 | 4/6 |
| 2N2220 | 5/– | 2N4285 | 3/6 | AFI16 | 5/– | BFI77 | 6/6 | GET119 | 4/– | OC77 | 6/– |
| 2N2221 | 5/– | 2N4286 | 3/6 | AFI17 | 5/– | BFI78 | 12/6 | GET120 | 6/6 | OC81 | 4/– |
| 2N2222 | 5/– | 2N4287 | 3/6 | AFI18 | 12/6 | BFI79 | 14/6 | GET873 | 3/– | OC81D | 4/6 |
| 2N2287 | 21/6 | 2N4288 | 3/6 | AFI19 | 4/– | BFI80 | 7/– | GET880 | 6/– | OC83 | 5/– |
| 2N2297 | 6/– | 2N4289 | 3/6 | AFI24 | 4/6 | BFI81 | 6/6 | GET887 | 4/– | OC84 | 5/– |
| 2N2303 | 5/– | 2N4290 | 3/6 | AFI25 | 4/– | BFI84 | 6/6 | GET889 | 4/6 | OC139 | 6/6 |
| 2N2368 | 5/– | 2N4291 | 3/6 | AFI26 | 4/– | BFI85 | 8/6 | GET890 | 4/6 | OC140 | 6/6 |
| 2N2369 | 3/– | 2N4292 | 3/6 | AFI27 | 3/6 | BFI94 | 4/6 | GET896 | 4/6 | OC170 | 6/– |
| 2N2369A | 5/6 | 2N5027 | 10/6 | AFI39 | 7/6 | BFI95 | 5/6 | GET897 | 4/6 | OC171 | 6/– |
| 2N2410 | 8/6 | 2N5028 | 11/6 | AFI78 | 11/– | BFI96 | 8/6 | GET898 | 4/6 | OC200 | 6/6 |
| 2N2483 | 5/6 | 2N5029 | 9/6 | AFI79 | 14/6 | BFI97 | 8/6 | MAT100 | 6/– | OC201 | 9/6 |
| 2N2484 | 6/6 | 2N5030 | 8/6 | AFI80 | 10/6 | BFI98 | 8/6 | MAT101 | 6/– | OC202 | 12/6 |
| 2N2539 | 4/6 | 2N5172 | 3/– | AFI81 | 8/6 | BF200 | 10/6 | MAT120 | 6/– | OC203 | 8/6 |
| 2N2540 | 4/6 | 2N5174 | 10/6 | AF239 | 8/6 | BF224 | 6/– | MAT121 | 6/– | OC204 | 8/6 |
| 2N2613 | 7/– | 2N5175 | 10/6 | AF279 | 9/6 | BF225 | 6/– | MC140 | 6/6 | OC205 | 8/6 |
| 2N2614 | 6/– | 2N5176 | 9/– | AF280 | 12/6 | BF237 | 6/6 | MJ400 | 21/6 | OC207 | 7/6 |
| 2N2646 | 11/6 | 2N5232 | 5/6 | AFZ11 | 6/6 | BF238 | 6/6 | MJ420 | 22/6 | OCP71 | 8/6 |
| 2N2696 | 6/6 | 2N5232A | 6/– | ASY26 | 5/– | BF244 | 9/6 | MJ421 | 22/6 | ORP12 | 12/6 |
| 2N2711 | 6/– | 2N5245 | 12/6 | ASY27 | 7/6 | BFX12 | 4/6 | MJ430 | 20/6 | ORP60 | 10/– |
| 2N2712 | 6/– | 2N5246 | 12/6 | ASY28 | 5/6 | BFW61 | 136 | MJ440 | 19/6 | ORP61 | 10/– |
| 2N2713 | 5/6 | 2N5249 | 13/6 | ASY29 | 5/6 | BFX12 | 4/6 | MJ480 | 19/6 | P346A | 4/6 |
| 2N2714 | 6/– | 2N5249A | 13/6 | ASY36 | 5/– | BFX13 | 4/6 | MJ481 | 25/– | TIP31A | 16/6 |
| 2N2865 | 12/6 | 2N5265 | 62/6 | ASY50 | 5/– | BFX29 | 7/– | MJ490 | 20/– | TIP32A | 19/6 |
| 2N2904 | 7/– | 2N5266 | 55/– | ASY54 | 5/– | BFX30 | 9/– | MJ491 | 27/6 | TIS34 | 12/6 |
| 2N2904A | 8/– | 2N5267 | 52/6 | ASY86 | 6/6 | BFX43 | 7/6 | MJ1800 | 43/6 | TIS43 | 8/– |
| 2N2905 | 8/– | 2N5305 | 7/6 | ASZ20 | 7/6 | BFX44 | 7/6 | MJE340 | 12/6 | TIS44 | 2/6 |
| 2N2905A | 9/– | 2N5306 | 8/– | ASZ21 | 7/6 | BFX68 | 13/6 | MJE520 | 17/6 | TIS45 | 3/6 |
| 2N2906 | 6/– | 2N5307 | 7/6 | AUY10 | 30/– | BFX68A | 13/6 | MJE521 | 17/6 | TIS46 | 3/6 |
| 2N2906A | 6/6 | 2N5308 | 7/6 | BC107 | 3/– | BFX84 | 6/– | MPF102 | 8/6 | TIS47 | 3/6 |
| 2N2907 | 6/6 | 2N5309 | 12/6 | BC108 | 3/– | BFX85 | 7/– | MPF103 | 7/6 | TIS48 | 3/6 |
| 2N2923 | 3/6 | 2N5310 | 8/6 | BC109 | 3/– | BFX86 | 6/– | MPF104 | 7/6 | TIS49 | 3/6 |
| 2N2924 | 3/6 | 2N5354 | 5/6 | BC113 | 5/6 | BFX87 | 10/– | MPF105 | 7/6 | TIS50 | 4/6 |
| 2N2925 | 3/6 | 2N5355 | 5/6 | BC115 | 6/6 | BFX88 | 5/– | MPS3638 | 6/6 | TIS51 | 3/6 |
| 2N2926 | | 2N5356 | 6/6 | BC116A | 7/6 | BFX89 | 12/6 | NKT0013 | 9/6 | TIS52 | 3/6 |
| ,, Green | 2/9 | 2N5365 | 9/6 | BC118 | 6/6 | BFX92A | 12/6 | NKT124 | 8/6 | TIS53 | 6/– |
| ,, Yellow | 2/6 | 2N5366 | 6/6 | BC121 | 4/– | BFY10 | 6/6 | NKT125 | 5/6 | TIS60 | 6/– |
| ,, Orange | 2/6 | 2N5367 | 11/6 | BC122 | 4/– | BFY11 | 8/6 | NKT126 | 5/6 | TIS61 | 6/– |
| 2N3011 | 6/– | 2N5457 | 7/6 | BC125 | 11/– | BFY12 | 4/6 | NKT128 | 5/6 | ZTX107 | 3/6 |
| 2N3014 | 6/6 | 2N718A | 6/– | BC126 | 11/– | BFY13 | 4/6 | NKT135 | 5/6 | ZTX108 | 3/6 |
| 2N3053 | 5/6 | 2S005 | 15/– | BC134 | 6/6 | BFY17 | 4/6 | NKT137 | 6/6 | ZTX109 | 3/6 |
| 2N3054 | 11/– | 2S020 | 37/6 | BC135 | 8/6 | BFY18 | 6/6 | NKT210 | 6/– | ZTX300 | 3/6 |
| 2N3055 | 15/– | 2S102 | 6/6 | BC136 | 7/6 | BFY19 | 6/6 | NKT211 | 6/– | ZTX301 | 3/6 |
| 2N3133 | 6/– | 2S103 | 6/6 | BC140 | 7/6 | BFY20 | 12/6 | NKT212 | 6/– | ZTX302 | 4/6 |
| 2N3134 | 6/– | 2S104 | 6/6 | BC147 | 3/6 | BFY21 | 8/6 | NKT213 | 6/– | ZTX303 | 4/6 |
| 2N3135 | 5/– | 2S501 | 5/6 | BC148 | 3/– | BFY24 | 9/– | NKT214 | 4/6 | ZTX304 | 6/6 |
| 2N3136 | 5/– | 2S502 | 5/6 | BC149 | 3/6 | BFY29 | 10/– | NKT215 | 4/6 | ZTX500 | 4/6 |
| 2N3390 | 7/6 | 2S503 | 5/6 | BC152 | 3/6 | BFY30 | 10/– | NKT216 | 7/6 | ZTX501 | 5/– |
| 2N3391 | 4/– | 3N83 | 37/6 | BC154 | 8/6 | BFY41 | 10/– | NKT217 | 8/6 | ZTX502 | 5/– |
| 2N3391A | 6/– | 3N128 | 18/6 | BC157 | 4/– | BFY43 | 12/6 | NKT219 | 6/– | ZTX503 | 5/– |
| 2N3392 | 4/– | 3N140 | 19/6 | BC158 | 3/6 | BFY50 | 4/6 | NKT223 | 5/6 | ZTX504 | 12/6 |
| 2N3393 | 4/– | 3N141 | 19/6 | BC159 | 4/– | BFY51 | 4/6 | NKT224 | 5/– | | |

Post & Packing 1/6d per order. Europe 5/–. Commonwealth (Air) 13/–.
Send 6d. stamp for price list.

## PANEL METERS

38 Series—FACE SIZE 42 × 42mm. All prices for 1-9 pieces. 50μA, 37/6; 100μA, 35/–; 200μA, 32/6; 500μA, 27/6; 50-0-50μA, 35/–; 100-0-100μA, 32/6; 500-0-500μA, 25/–; 1MA, 25/–; 5MA, 25/–; 10MA, 25/–; 50MA, 25/–; 100MA, 25/–; 500MA, 25/–; 1A, 25/–; 5A, 25/–; 10V, 25/–; 20V, 25/–; 50V, 25/–; 300V, 25/–; 500V, 25/–

## SILICON RECTIFIERS

| PIV | 50 | 100 | 200 | 400 | 600 | 800 | 1000 | 1200 |
|---|---|---|---|---|---|---|---|---|
| 1A | 2/9 | 3/– | 3/3 | 3/6 | 3/9 | 4/– | 4/6 | — |
| 3A | 3/– | — | — | 4/6 | — | 6/– | — | — |
| 6A | — | — | 5/– | 6/– | 6/6 | 7/– | 10/–* | — |
| 10A | 10/6 | 11/6 | 13/– | 15/6 | 17/6 | 19/6 | 25/– | 32/– |
| 17A | 11/6 | 12/6 | 15/6 | 18/– | 19/6 | 24/– | 31/6 | 37/6 |

*5A only 1A Types are plastic

## DIODES & RECTIFIERS

| | | | | | | | | | |
|---|---|---|---|---|---|---|---|---|---|
| IN461 | 4/6 | IS131 | 2/6 | BA144 | 2/6 | BYX10 | 4/6 | OA73 | 1/9 |
| IN914 | 1/6 | IS132 | 3/– | BAX13 | 1/6 | BYZ10 | 7/– | OA79 | 1/6 |
| IN916 | 1/6 | IS940 | 1/6 | BAX16 | 1/9 | BYZ11 | 6/6 | OA81 | 1/6 |
| IN4007 | 4/6 | AA119 | 2/6 | BAY18 | 3/3 | BYZ12 | 6/– | OA85 | 1/6 |
| IS010 | 3/– | AA213 | 4/6 | BAY31 | 1/6 | BYZ13 | 5/– | OA90 | 1/6 |
| IS021 | 4/– | AAZ13 | 4/– | BAY38 | 3/9 | FST3/4 | 3/– | OA91 | 1/6 |
| IS025 | 5/– | AAZ15 | 2/6 | BY100 | 4/6 | FST3/8 | 4/– | OA95 | 1/6 |
| IS44 | 2/– | AAZ17 | 2/– | BY103 | 4/6 | OA5 | 3/6 | OA200 | 2/– |
| IS113 | 3/– | BA100 | 3/– | BY122 | 7/6 | OA9 | 2/– | OA202 | 2/– |
| IS120 | 3/– | BA102 | 4/6 | BY124 | 3/– | OA10 | 2/6 | | |
| IS121 | 3/6 | BA110 | 7/– | BY126 | 3/6 | OA47 | 1/6 | | |
| IS130 | 2/6 | BA115 | 1/6 | BY127 | 4/6 | OA70 | 1/6 | | |

## INTEGRATED CIRCUITS

**RCA**

| | | | | | |
|---|---|---|---|---|---|
| CA3000 | 39/6 | CA3020A | | CA2029A | |
| CA3005 | 25/6 | | 37/– | | 38/6 |
| CA3007 | 57/6 | CA3021 | 34/– | CA3035 | 27/6 |
| CA3012 | 19/6 | CA3023 | 26/– | CA3036 | 16/6 |
| CA3014 | 27/– | CA3026 | 21/– | CA3039 | 19/6 |
| CA3018 | 19/– | CA3028A | | CA3041 | 25/– |
| CA3018A | | | 16/6 | CA3042 | 25/– |
| | 25/– | CA3028B | | CA3043 | 29/– |
| CA3019 | 19/– | | 24/– | CA3044 | 27/– |

| | | | |
|---|---|---|---|
| CA3046 | 19/6 | | |
| CA3048 | 45/– | | |
| CA3050 | 39/6 | | |
| CA3051 | 28/– | | |
| CA3052 | 36/6 | | |
| CA3053 | 12/– | | |
| CA3054 | 24/– | | |
| CA3055 | 50/– | | |
| CA3059 | 27/– | | |
| CA3064 | 35/– | | |

Data and application sheets 2/– per type

**Motorola**

| | | | |
|---|---|---|---|
| MC724P | 17/6 | MC799P | 17/6 |
| MC780P | 57/6 | MC838P | 130/– |
| MC788P | 19/6 | MCI303P | 57/9 |
| MC789P | 17/6 | MCI304P | 79/6 |
| MC790P | 27/6 | MCI552G | 89/6 |
| MC792P | 17/6 | | |

**Fairchild**

| | 1–6 | 7–11 | 12+ |
|---|---|---|---|
| L900 Buffer | 9/9 | 9/– | 8/– |
| L914 Dual Gate | 9/9 | 9/– | 8/– |
| L923 JK Flip Flop | 12/6 | 11/9 | 11/– |
| L709 Operational Amplifier | 21/– | 19/6 | 18/– |

Quantity Prices on Application

**General Electric**

| | | | |
|---|---|---|---|
| PA230 | Low Level Amplifier | | 22/6 |
| PA234 | 1 watt Audio Amplifier | | 21/6 |
| PA237 | 2 watt Audio Amplifier | | 37/6 |
| PA246 | 5 watt Audio Amplifier | | 57/6 |

**Mullard**

| | | | | | |
|---|---|---|---|---|---|
| TAA241 | 32/6 | FJH101 | 17/6 | | |
| TAA243 | 30/– | FJH121 | 17/6 | | |
| TAA263 | 15/6 | FJH141 | 17/6 | | |
| TAA300 | 35/– | FJH161 | 17/6 | | |
| TAA310 | 25/– | FJH171 | 18/3 | | |
| TAA320 | 14/6 | FJH221 | 17/6 | | |
| TAA350 | 35/– | FJJ101 | 27/6 | | |
| TAB101 | 19/6 | FJJ121 | 37/6 | | |
| TAD100 | 39/6 | FJJ141 | 62/6 | | |

**Plessey**

| | | | | |
|---|---|---|---|---|
| SL402A | 42/6 | SL403A | 42/6 | Data and App. Sheets 2/6 |

## TRIACS

SC41D, 6A 400V 25/–

SC41B, 6A 200V 22/–

40512 6A 400V 33/–

## THYRISTORS

| PIV | 50 | 100 | 200 | 300 | 400 |
|---|---|---|---|---|---|
| 1A | 5/– | 5/6 | 7/6 | 8/– | 9/6 |
| 3A | 6/– | 7/6 | 8/– | 9/– | 10/6 |
| 5A | — | 11/– | 13/– | — | 15/– |
| 7A | — | 11/– | 13/– | 14/– | 19/6 |
| 25A | 27/6 | 30/– | 33/– | — | 37/6 |

Also 12A, 100 PIV, 15/–; 600 PIV, 35/6; 25A, 400 PIV 37/6

## VEROBOARD

| | 0·15 Matrix | 0·1 Matrix |
|---|---|---|
| 2½ × 3¾in | 3/6 | 4/– |
| 2½ × 5in | 4/3 | 4/9 |
| 3¾ × 3¾in | 4/3 | 4/9 |
| 3¾ × 5in | 5/6 | 5/6 |
| 3¾ × 17in | 16/– | 21/6 |
| 3¾ × 17in (plain) | — | 11/6 |
| 5 × 17in (plain) | 15/6 | — |
| Vero Pins (bags of 50) | 5/– | 5/– |
| Vero Cutter, 9/– | | |

## HEAT SINKS

4·8 × 4 × 1in Finned for Two TO-3 Trans., 9/6. 4·8 × 2 × 1in Finned, for One TO-3 Trans., 6/6. For SO-1, 6d. For TO-5, 1/– Finned. For TO-18, 1/– Finned. For TO-18, 1/– Finned.

## RESISTORS

**Carbon Film**

¼ watt 5%, 3d.
½ watt 5%, 4d.
½ watt 5%, 5d.
1 watt 10%, 6d.
2 watt 10%, 1/3

## CAPACITORS

A large and comprehensive range available: Electrolytic, Polyester, Ceramic, Polystyrene, Silver Mica, Tantalum, Trimmers

Examples:
2,000mF 25V, 8/6
2,500mF 50V, 13/6
3,000mF 25V, 10/6
5,000mF 50V, 19/6

## WIRE-WOUND

2·5 watt 5% (up to 270 ohms only), 1/6
5 watt 5% (upto 8·2k Ω only), 2/–
10 watt 5% (up to 25k Ω only), 2/6

## POTENTIOMETERS

**Carbon:**
Log. and Lin., less switch, 3/–. Log. and Lin., with switch, 4/6. Wire-wound Pots (3W), 5/6. Twin Ganged Stereo Pots, Log. and Lin., 7/6.

## PRESETS (CARBON)

0·1 Watt 1/–
0·2 Watt 1/3
0·3 Watt 1/6

## THERMISTORS


R53 (STC) 25/6
K151 (Ik) 2/6
Mullard Thermistors also in stock. Please enquire.


Tel. 01-452 0161/2/3
Telex 21492

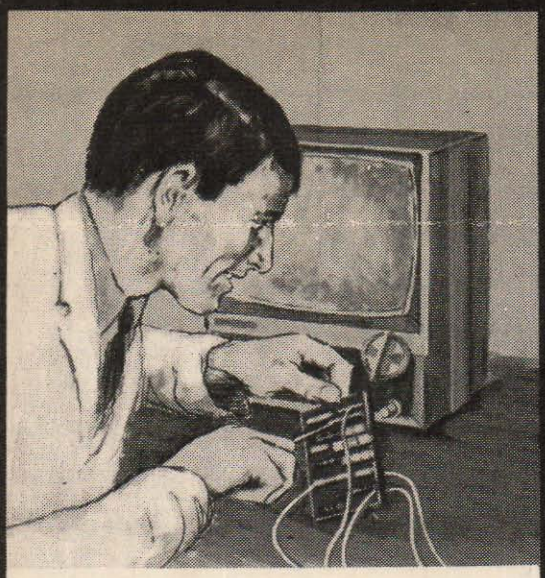**A. MARSHALL & SON**
**28 CRICKLEWOOD BROADWAY, LONDON, N.W.2**


Send 2/6 for our New Comprehensive Catalogue containing Vouchers worth 6/–

**CALLERS WELCOME**
**HRS. 9-5.30 Mon-Sat**



# Train for tomorrow's world in Radio and Television at The Pembridge College of Electronics.

**The next full-time 2 year College Diploma Course which gives a thorough fundamental training for radio and television engineers starts on 2nd September, 1970.**

The course includes theoretical and practical instruction on Colour Television receivers and is designed to cover the syllabus of the new City and Guilds Radio, Television and Electronics Technicians' Course. Pembridge College diplomas are awarded to successful students.

The way to get ahead in this fast growing industry—an industry that gives you many far-reaching opportunities—is to enrol now. Minimum entrance requirements: "O" Level, Senior Cambridge or equivalent in Mathematics and English.

**To : The Pembridge College of Electronics (Dept. PE4), 34a Hereford Road, London, W.2.**

Please send, without obligation, details of the Full-time Course in Radio, Television and Electronics.

NAME .....

ADDRESS .....

.....

# BI-PAK = LOW COST I.C's



BI-PAK Semiconductors now offer you the largest and most popular range of I.C's available at these **EXCLUSIVE LOW PRICES.** TTL Digital SN74N Series fully coded, brand new to manufacturers' specifications. Dual in-line plastic 14 and 16 pin packages.

| BI-PAK Order No. | Description | Price and qty. prices 1–24 | 25–99 | 100 up |
|---|---|---|---|---|
| BP00 = SN7400N | Quad 2-Input NAND GATE | 6/6 | 5/6 | 4/6 |
| BP01 = SN7401N | Quad 2-Input NAND Gate—OPEN COLLECTOR | 6/6 | 5/6 | 4/6 |
| BP04 = SN7404N | HEX INVERTER | 6/6 | 5/6 | 4/6 |
| BP10 = SN7410N | Triple 3-Input NAND GATE | 6/6 | 5/6 | 4/6 |
| BP20 = SN7420N | Dual 4-Input NAND GATE | 6/6 | 5/6 | 4/6 |
| BP30 = SN7430N | Single 8-Input NAND GATE | 6/6 | 5/6 | 4/6 |
| BP40 = SN7440N | Dual 4-Input BUFFER GATE | 6/6 | 5/6 | 4/6 |
| BP41 = SN7441AN | BCD to decimal decoder and NIT Driver | 22/6 | 20/– | 17/6 |
| BP42 = SN7442N | BCD to decimal decode (TTL O/P) | 22/6 | 20/– | 17/6 |
| BP50 = SN7450N | Dual 2-Input AND/OR/NOT GATE —expandable | 6/6 | 5/6 | 4/6 |
| BP53 = SN7453N | Single 8-Input AND/OR/NOT GATE—expandable | 6/6 | 5/6 | 4/6 |
| BP60 = SN7460N | Dual 4-Input—expandable | 6/6 | 5/6 | 4/6 |
| BP70 = SN7470N | Single JK Flip-Flop—edge triggered | 9/– | 8/– | 7/– |
| BP72 = SN7472N | Single Master Slave JK Flip-flop | 9/– | 8/– | 7/– |
| BP73 = SN7473N | Dual Master Slave JK Flip-flop | 10/– | 9/– | 8/6 |
| BP74 = SN7474N | Dual D Flip-flop | 10/– | 9/– | 8/6 |
| BP75 = SN7475N | Quad Bistable Latch | 11/– | 10/– | 9/6 |
| BP76 = SN7476N | Dual Master Slave Flip-flop with preset and clear | 11/– | 10/– | 9/6 |
| BP83 = SN7483N | Four Bit Binary Adder | 26/– | 22/6 | 20/– |
| BP90 = SN7490N | BCD Decade Counter | 22/6 | 20/– | 17/6 |
| BP92 = SN7492N | Divide by 12 4 Bit binary counter | 22/6 | 20/– | 17/6 |
| BP93 = SN7493N | Divide by 16 4 Bit binary counter | 22/6 | 20/– | 17/6 |
| BP94 = SN7494N | Dual Entry 4 Bit Shift Register | 22/6 | 20/– | 17/6 |
| BP95 = SN7495N | 4 Bit Up-Down Shift Register | 22/6 | 20/– | 17/6 |
| BP96 = SN7496N | 5 Bit shift register | 24/– | 21/– | 18/6 |

Data is available for the SN74N Series of Integrated circuits in booklet form, price 2/6.

| BRAND NEW. FULL TO MANUFACTURERS' SPECIFICATION | Price each 1–24 | 25–99 | 100 up |
|---|---|---|---|
| BP709 Operational Amplifier, dual-in-line 14 pin package = SN72709 and similar to MIC709 and ZLD709C. | 10/6 | 9/– | 8/– |

This is a high performance operational amplifier with high impedance differential inputs and low impedance output.

## INTEGRATED CIRCUITS

Manufacturers' "Fall outs"—out of spec. devices including functional units and part functional but classed as out of spec. from the manufacturers very rigid specifications. Ideal for learning about I.C's and experimental work, on testing, some will be found perfect.

| PAK No. | | PAK No. | |
|---|---|---|---|
| UIC00 = 5 × 7400N ..... | 10/– | UIC73 = 5 × 7473N ..... | 10/– |
| UIC01 = 5 × 7401N ..... | 10/– | UIC74 = 5 × 7474N ..... | 10/– |
| UIC02 = 5 × 7402N ..... | 10/– | UIC75 = 5 × 7475N ..... | 10/– |
| UIC03 = 5 × 7403N ..... | 10/– | UIC76 = 5 × 7476N ..... | 10/– |
| UIC04 = 5 × 7404N ..... | 10/– | UIC80 = 5 × 7480N ..... | 10/– |
| UIC05 = 5 × 7405N ..... | 10/– | UIC82 = 5 × 7482N ..... | 10/– |
| UIC10 = 5 × 7410N ..... | 10/– | UIC83 = 5 × 7483N ..... | 10/– |
| UIC20 = 5 × 7420N ..... | 10/– | UIC86 = 5 × 7486N ..... | 10/– |
| UIC40 = 5 × 7440N ..... | 10/– | UIC90 = 5 × 7490N ..... | 10/– |
| UIC41 = 5 × 7441AN ..... | 10/– | UIC92 = 5 × 7492N ..... | 10/– |
| UIC42 = 5 × 7442N ..... | 10/– | UIC93 = 5 × 7493N ..... | 10/– |
| UIC50 = 5 × 7450N ..... | 10/– | UIC94 = 5 × 7494N ..... | 10/– |
| UIC51 = 5 × 7451N ..... | 10/– | UIC95 = 5 × 7495N ..... | 10/– |
| UIC60 = 5 × 7460N ..... | 10/– | UIC96 = 5 × 7496N ..... | 10/– |
| UIC70 = 5 × 7470N ..... | 10/– | UICX1 = 20 × ASST'D 74's | 30/– |
| UIC72 = 5 × 7472N ..... | 10/– | | |

Packs cannot be split but 20 assorted pieces (our mix) is available as PAK UICX1.
Every PAK carries our BI-PAK Satisfaction or money back GUARANTEE.

## DUAL-IN-LINE DOW PROFILE SOCKETS

14 and 16 lead sockets for use with Dual-in-Line Integrated Circuits.

| Order No. | | Price each 1–24 | 25–99 | 100 up |
|---|---|---|---|---|
| TS014 | 14 pin type | 7/6 | 6/– | 5/3 |
| TS016 | 16 pin type | 10/– | 8/6 | 7/9 |

## FAIRCHILD (U.S.A.) I.C's

| RTL Micrologic Circuits | | Qty. prices each 1–11 | 12–24 | 25–99 | 100 up |
|---|---|---|---|---|---|
| Epoxy case To-5 temp range 15°C to 55°C | | 9/9 | 8/– | 7/6 | 6/6 |
| μL 900 Buffer | | 9/9 | 8/– | 7/6 | 6/6 |
| μL 914 Dual two-input GATE | | 9/9 | 8/– | 7/6 | 6/6 |
| μL 923 J-K Flip-flop | | 12/6 | 11/– | 10/6 | 9/6 |

Full data and circuits for IC's in Booklet form price 1/6 each.

| | | | |
|---|---|---|---|
| μA703E Linear RF-IF AMPLIFIER | 11/– | 10/– | 9/– 8/3 |

PLASTIC CASE To-5 6 lead up to 100 m/cs.

## MOTOROLA DIGITAL I.C's

| MDTL dual in-line package. | Price |
|---|---|
| Type MC844P expandable dual 4-input NAND Power Gate | 10/– each |
| Type MC845P Clocked Flip-flop | 15/– each |

FULL DATA SUPPLIED WITH UNITS

Please send all orders direct to our warehouse and despatch department.

**BI-PAK SEMICONDUCTORS**

**P.O. BOX 6, WARE, HERTS.**

Postage and packing add 1/–. Overseas add extra for Airmail. Minimum order 10/–. Cash with order please.

# VALUE ALL THE WAY

## LINEAR INTEGRATED CIRCUITS

**BI-PAK MONOLITHIC AMPLIFIERS (TO-5 8 lead)**

BP709C, Operational amplifier, 15/- each.
BP701C, Operational amplifier (with Zener output), 12/6 each.
BP702C, Operational amplifier (with direct output), 12/6 each.
BP501, Wide band amplifier, 18/- each.
BP521, Logarithmic wide band amp., 14/- each.
BP20/C, General purpose amplifier (TO-5 8 lead), (voltage or current amp.), 12/6 each.
I.C. Operational Amplifier with Zener output.
Type 701C. Ideal for P.E. Projects. 8 Lead TO-5 case. Full data.

**Our price 12/6 each**

5 off 11/- each. Large Qty. Prices quoted for.

## IC AMPLIFIER



Identical encapsulation and pin configuration to the following: SL402-3, IC10 and IC403. Each circuit incorporates a pre-amp and class A.B. Power amp stage capable of delivering up to 3 watts RMS. Fully tested and guaranteed. Supplied complete with circuit details and data. CODED BP.1010. OUR LOWEST PRICE 30/- each. 10 up 25/- each.

**MULLARD I.C. AMPLIFIERS**

TAA243, Operational amplifier, 70/- each.
TAA263, Linear AF amplifier, 15/9 each.
TAA293, General purpose amplifier, 21/- each.

**CA3020 RCA (U.S.A.) LINEAR INTEGRATED CIRCUITS**

Audio Power Amplifier, 30/- each.

**OTHER MONOLITHIC DEVICES**

D13D1 Silicon Unilateral switch 10/- each.
A Silicon Planar, monolithic integrated circuit having thyristor electrical characteristics, but with an anode gate and a built-in "Zener" diode between gate and cathode. Full data and application circuits available on request.

**Silicon Microwave Diodes—Sylvania (U.S.A.)**

IN218 and IN218R matched pair S. Band mixer. Max. overall noise faction 13·7dB at 3,000m/cs Brand new and boxed. Clearance Price 6/- pair.

**EX-EQUIPMENT MULLARD**

AF117 transistors. Large can 4 lead type. Leads cut short but still usable, real value at 15 for 10/-.

## AD161 *NPN*
## AD162 *PNP*

MATCHED COMPLEMENTARY PAIRS OF GERM. POWER TRANSISTORS.

For mains driven output stages of Amplifiers and Radio receivers.

OUR LOWEST PRICE OF 12/6 *PER PAIR*

HIGH POWER SILICON PLANAR TRANSISTORS. TO-3.

FERRANTI ZT1487 NPN

VCB60 1c 6A ft. 1M/cs
VCE40 Ptot. 75W
VEB8 hFE15-45

PRICE 15/- EACH

**2N3055 115 WATT SIL. POWER NPN**

OUR PRICE 12/6 EACH

**FULL RANGE OF ZENER DIODES VOLTAGE RANGE 2-16V.** 400mV (DO-7 Case) 2/6 ea. 1½W (Top-Hat) 3/6 ea. 10W (SO-10 Stud) 5/- ea. All fully tested 5% tol. and marked. State voltage required.

**BRAND NEW TEXAS GERM. TRANSISTORS Coded and Guaranteed**

| Pak No. | | EQVT |
|---|---|---|
| T1 | 8 2G371A | OC71 |
| T2 | 8 2G374 | OC76 |
| T3 | 8 2G744A | OC81D |
| T4 | 8 2G381A | OC81 |
| T5 | 8 2G382T | OC82 |
| T6 | 8 2G344A | OC44 |
| T7 | 8 2G345A | OC45 |
| T8 | 8 2G378 | OC78 |
| T9 | 8 2G399A | 2N1302 |
| T10 | 8 2G417 | AF117 |

All 10/- each pack

**2N2060 NPN SIL. DUAL TRANS.** CODE D1699 TEXAS. Our price 5/- each.

**120 VCB NIXIE DRIVER TRANSISTOR.** Sim. BSX21 & C407. 2N1893 FULLY TESTED AND CODED ND120. 1-24 3/6 each. To-5 N.P.N. 25 up 3/- each.

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqvt. ZTX300 1/- each. Any Qty.

## FREE

One 10/- Pack of your own choice free with orders valued £4 or over.

NPN DIFFUSED SILICON PHOTO-DUO-DIODE TYPE IS701 (2N2175) for Tape Readout, high switching and measurement indicators. 50V, 250mW. OUR PRICE 10/- EACH, 50 OR OVER 8/6 EACH, FULL DETAILS.

**FET'S**

2N 3819 ..... 10/-
2N 3820 ..... 25/-
MPF105 ..... 8/-

**LOW COST F.E.T.s**

Fully Tested, Guaranteed Parameters equit. to 2N3819, MPF102, 2N5459. 1-24 7/6 each; 25-99 6/3 each; 100 up 5/6 each. Coded FE19. Full data sent. TO-72 case.

## CADMIUM CELLS

ORP12 8/6
ORP60, ORP61 8/- each

## PHOTO TRANS.

OCP71 Type. 8/6

## KING OF THE PAKS — Unequalled Value and Quality

# SUPER PAKS

**NEW BI-PAK UNTESTED SEMICONDUCTORS**

Satisfaction GUARANTEED in Every Pak, or money back.

| Pak No. | | |
|---|---|---|
| U1 | 120 Glass Sub-min. General Purpose Germanium Diodes | 10/- |
| U2 | 60 Mixed Germanium Transistors AF/RF | 10/- |
| U3 | 75 Germanium Gold Bonded Diodes sim. OA5, OA47 | 10/- |
| U4 | 40 Germanium Transistors like OC81, AC128 | 10/- |
| U5 | 60 200mA Sub-min. Sil. Diodes | 10/- |
| U6 | 30 Silicon Planar Transistors NPN sim. BSY95A, 2N706 | 10/- |
| U7 | 16 Silicon Rectifiers Top-Hat 750mA up to 1,000V | 10/- |
| U8 | 50 Sil. Planar Diodes 250mA OA/200/202 | 10/- |
| U9 | 20 Mixed Volts 1 watt Zener Diodes | 10/- |
| U11 | 30 PNP Silicon Planar Transistors TO-5 sim. 2N1132 | 10/- |
| U13 | 30 PNP-NPN Sil. Transistors OC200 & 2S104 | 10/- |
| U14 | 150 Mixed Silicon and Germanium Diodes | 10/- |
| U15 | 25 NPN Silicon Planar Transistors TO-5 sim. 2N697 | 10/- |
| U16 | 10 3-Amp Silicon Rectifiers Stud Type up to 1000 PIV | 10/- |
| U17 | 30 Germanium PNP AF Transistors TO-5 like ACY 17-22 | 10/- |
| U18 | 8 6-Amp Silicon Rectifiers BYZ13 Type up to 600 PIV | 10/- |
| U19 | 25 Silicon NPN Transistors like BC108 | 10/- |
| U20 | 12 1·5-amp Silicon Rectifiers Top-Hat up to 1,000 PIV | 10/- |
| U21 | 30 A.F. Germanium alloy Transistors 2G300 Series & OC71 | 10/- |
| U23 | 30 Madt's like MAT Series PNP Transistors | 10/- |
| U24 | 20 Germanium 1-amp Rectifiers GJM up to 300 PIV | 10/- |
| U25 | 25 300Mc/s NPN Silicon Transistors 2N708, BSY27 | 10/- |
| U26 | 30 Fast Switching Silicon Diodes like IN914 Micro-min | 10/- |
| U28 | Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip-Flops, Registers, etc., 8 Assorted Pieces | 20/- |
| U29 | 10 1 amp SCR's T0-5 can up to 600 PIV CR81/25-600 | 20/- |
| U31 | 20 Sil. Planar NPN trans. low noise Amp 2N3707 | 10/- |
| U32 | 25 Zener diodes 400mW D07 case mixed Volts, 3-18 | 10/- |
| U33 | 15 Plastic case 1 amp Silicon rectifiers 1N4000 series | 10/- |
| U34 | 30 Sil. PNP alloy trans. TO-5 BCY26, 2S302/4 | 10/- |
| U35 | 25 Sil. Planar trans. PNP TO-18 2N2906 | 10/- |
| U36 | 25 Sil. Planar NPN trans. TO-5 BFY50/51/52 | 10/- |
| U37 | 30 Sil. alloy trans. SO-2 PNP, OC200 2S322 | 10/- |
| U38 | 20 Fast Switching Sil. trans. NPN, 400Mc/s 2N3011 | 10/- |
| U39 | 30 RF Germ. PNP trans. 2N1303/5 TO-5 | 10/- |
| U40 | 10 Dual trans. 6 lead TO-5 2N2060 | 10/- |
| U41 | 25 RF Germ. trans. TO-1 OC45 NKT72 | 10/- |
| U42 | 10 VHF Germ. PNP trans. TO-1 NKT667 AF117 | 10/- |

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked

## NEW LOW PRICE TESTED S.C.R.'s

| | 1A (TO-5 case) | 3A (TO-66 case) | 7A (TO-48 case) | 16A (TO-48 case) | | 30A |
|---|---|---|---|---|---|---|
| PIV | each | each | each | each | PIV | each |
| 50 | 4/6 | 5/- | 9/6 | 10/6 | 25 | 20/- |
| 100 | 5/- | 6/6 | 10/6 | 12/6 | 50 | 23/- |
| 200 | 7/- | 7/6 | 11/6 | 15/- | 100 | 28/- |
| 400 | 8/6 | 9/6 | 13/6 | 18/6 | 200 | 32/- |
| 600 | 10/6 | 11/6 | 15/6 | 25/- | 400 | 35/- |
| 800 | 12/6 | 14/- | 18/- | 30/- | 600 | 80/- |

**2A POTTED BRIDGE RECTIFIERS.**
200V 10/-.

**TRANSISTOR EQVT. AND SPECIFICATION BOOK.** (German Publication.) A complete cross reference and equivalent book for European, American and Japanese Transistors. Exclusive to BI-PAK. 15/- each.

**PRINTED CIRCUITS EX-COMPUTER**

Packed with semiconductors and components, 10 boards give a guaranteed 30 trans and 30 diodes. Our price 10 boards 10/-. Plus 2/- P. & P.

**PLEASE NOTE.** To avoid any further Increased Postal Charges to our Customers and enable us to keep our "By Return Postal service" which is second to none, we have re-organised and streamlined our Despatch Order Department and we now request you to send all your orders together with your remittance, direct to our Warehouse and Despatch Department, postal address: **BI-PAK SEMICONDUCTORS, Despatch Dept., P.O. BOX 6, WARE, HERTS.** Postage and packing still 1/- per order. Minimum order 10/-.

## SIL. RECTS. TESTED

| PIV | 750mA | 3A | 10A | 30A |
|---|---|---|---|---|
| 50 | 1/- | 2/9 | 4/3 | 9/6 |
| 100 | 1/3 | 3/3 | 4/6 | 15/- |
| 200 | 1/9 | 4/- | 4/9 | 20/- |
| 300 | 2/3 | 4/6 | 6/6 | 22/- |
| 400 | 2/6 | 5/6 | 7/6 | 25/- |
| 500 | 3/- | 6/- | 8/6 | 30/- |
| 600 | 3/3 | 6/9 | 9/- | 37/- |
| 800 | 3/6 | 7/6 | 11/- | 40/- |
| 1000 | 5/- | 9/3 | 12/6 | 50/- |
| 1200 | 6/6 | 11/6 | 15/- | |

**TRIACS**

| VBOM | 2A (TO-1) | 6A (TO-66) | 10A (TO-48) |
|---|---|---|---|
| 100 | 14/- | 15/- | 22/6 |
| 200 | 17/6 | 20/- | 28/- |
| 400 | 20/- | 24/- | 35/- |

VBOM = Blocking voltage in either direction.

**LUCAS 35A SIL. RECTS.**

Branded. 400 PIV. Special Price, stud type, flying lead, 22/6 each.

**UNIJUNCTION**

**UT46.** Eqvt. 2N2646, Eqvt. TI843. BEN3000 5/6 each, 25-99 5/-. 100 UP 4/-.

**NPN SILICON PLANAR**

BC107/8/9, 2/- each; 50-99, 1/10; 100 up, 1/8 each; 1,000 off, 1/6 each. Fully tested and coded TO-18 case.

**SILICON HIGH VOLTAGE RECTIFIERS**

10-Amp 3-K.V. (3000 P.I.V.) Stud Type with Flying Leads, 16/- each.

## QUALITY-TESTED PAKS

| | | |
|---|---|---|
| 6 | Matched Trans. OC44/45/81/81D | 10/- |
| 20 | Red Spot AF Trans. PNP | 10/- |
| 16 | White Spot RF Trans. PNP | 10/- |
| 5 | Silicon Rects. 3 A 100-400 PIV | 10/- |
| 2 | 10 A Silicon Rects. 100 PIV | 10/- |
| 2 | OC1 140 Trans. NPN Switching | 10/- |
| 1 | 12 A SCR 100 PIV | 10/- |
| 3 | Sil. Trans. 2S303 PNP | 10/- |
| 3 | 200 Mc/s Sil. Trans. NPN BSY26/27 | 10/- |
| 3 | Zener Diodes 1W 33V 5% Tol. | 10/- |
| 4 | High Current Trans. OC42 Eqvt. | 10/- |
| 2 | Power Transistors 1 OC26 1 OC35 | 10/- |
| 5 | Silicon Rects, 400 PIV 250mA | 10/- |
| 4 | OC75 Transistors | 10/- |
| 1 | Power Trans. OC29 100V | 10/- |
| 10 | OA202 Sil. Diodes Sub-min. | 10/- |
| 2 | Low Noise Trans. NPN 2N929/30 | 10/- |
| 1 | Sil. Trans. NPN VCB 100 ZT86 | 10/- |
| 8 | OA81 Diodes | 10/- |
| 4 | OC72 Transistors | 10/- |
| 4 | OC77 Transistors | 10/- |
| 4 | Sil. Rects. 400 PIV 500mA | 10/- |
| 5 | GET884 Trans. Eqvt. OC44 | 10/- |
| 5 | GET883 Trans. Eqvt. OC45 | 10/- |
| 2 | 2N708 Sil. Trans. 300Mc/s NPN | 10/- |
| 3 | GT31 LF Low Noise Germ Trans. | 10/- |
| 6 | 1N914 Sil. Diodes 75 PIV 75mA | 10/- |
| 8 | OA95 Germ. Diodes Sub-min. 1N69 | 10/- |
| 3 | NPN Germ. Trans. NKT773 Eqvt. | 10/- |
| 2 | OC22 Power Trans. Germ. | 10/- |
| 2 | OC25 Power Trans. Germ. | 10/- |
| 4 | AC128 Trans. PNP High Gain | 10/- |
| 4 | AC127/128 Comp. pair PNP/NPN | 10/- |
| 3 | 2N1307 PNP Switching Trans. | 10/- |
| 7 | CG62H Germ. Diodes Eqvt. OA71 | 10/- |
| 3 | AF116 Type Trans. | 10/- |
| 12 | Assorted Germ. Diodes Marked | 10/- |
| 4 | AC126 Germ. PNP Trans. | 10/- |
| 4 | Silicon Rects. 100 PIV 750mA | 10/- |
| 3 | AF117 Trans. | 10/- |
| 7 | OC81 Type Trans. | 10/- |
| 3 | OC171 Trans. | 10/- |
| 5 | 2N2926 Sil. Epoxy Trans. | 10/- |
| 7 | OC71 Type Trans. | 10/- |
| 2 | 28701 Sil. Trans. Texas | 10/- |
| 2 | 10 A 600 PIV Sil. Rects. 1S46R | 10/- |
| 3 | BC108 Sil. NPN High Gain Trans. | 10/- |
| 1 | 2N910 NPN Sil. Trans. VCB 100 | 10/- |
| 2 | 1000 PIV Sil. Rect. 1·5 A R53310 AF | 10/- |
| 3 | BSY95A Sil. Trans. NPN 200Mc/s | 10/- |
| 3 | OC200 Sil. Trans. | 10/- |
| 2 | GET880 Low Noise Germ. Trans. | 10/- |
| 1 | AF139 PNP High Freq. Trans. | 10/- |
| 3 | NPN Trans. 1 ST141 & 2ST140 | 10/- |
| 4 | Madt's 2 MAT100 & 2MAT120 | 10/- |
| 3 | Madt's 2 MAT101 & 1 MAT121 | 10/- |
| 4 | OC44 Germ. Trans. AF | 10/- |
| 3 | AC127 NPN Germ. Trans. | 10/- |
| 1 | 2N3906 Sil. PNP Trans. Motorola | 10/- |
| 2 | Sil. Power Rects. BYZ13 | 15/- |
| 1 | Sil. Power Trans. NPN 100Mc/s. TK201A | 15/- |
| 2 | 2N1132 PNP Epitaxial Planar Sil. | 10/- |
| 3 | 2N697 Epitaxial Planar Trans. Sil. | 15/- |
| 4 | Germ. Power Trans. Eqvt. OC16 | 15/- |
| 1 | Unijunction Trans. 2N2646 | 15/- |
| 2 | Sil. Trans. 200Mc/s 60Vcb ZT83/84 | 15/- |
| 20 | NKT Trans. AF, RF, VHF. Coded + Eqvt. List | 10/- |
| 2 | 2N2712 Sil. Epoxy Planar HFE225 | 15/- |
| 8 | BY100 Type Sil. Rects. | 20/- |
| 25 | Sil. and Germ. Trans. Mixed, all marked, New | 30/- |

**SEMICONDUCTORS FOR "P.E." 50+50AMP.**

| TYPE | EACH | TYPE | EACH |
|---|---|---|---|
| 2N1613 | 4/6 | 1N914 | 1/- |
| 2N3055 | 12/6 | OA200 | 1/- |
| 2N3703 | 3/- | BFY51 | 3/6 |
| 2N3704 | 3/6 | BYZ13 | 4/6 |
| 2N3707 | 3/9 | 40362 | 14/- |
| 2N3819 | 8/- | 22V 1½W Zener | 3/6 |

GIRO No. 388-7006


**BI-PAK**

63A High Street WARE Herts.

KING OF THE PAKS **BI-PAK** GUARANTEE SATISFACTION OR **MONEY BACK**

## MONO TRANSISTOR AMPLIFIER

**HSL.700**

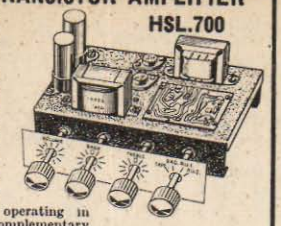

A really high fidelity monaural amplifier with performance characteristics to suit the most discriminating listener. 6 transistor circuit with integrated preamplifier assembled on special printed sub panel. AD161-AD162 operating in symmetrical complementary pair. Output transformer coupled to 3 ohm and 15 ohm speaker sockets. Standard phono input sockets. Full wave bridge rectifier power supply for a.c. mains 200–240v. Controls: bass, treble, volume/on/off. Function selector for PU1, PU2, tape, radio. The HSL.700 is strongly constructed on rigid steel chassis bronze hammer enamel finish, size 9½ × 5 × 4½in. high.

Sensitivity—PU1—50m/v, 56K input impedance.
PU2—110m/v, 1 meg input impedance.
Tape—110m/v, 1 meg input impedance.
Radio—110m/v, 1 meg input impedance.

Output power measured at 1Kc—6·2 watts RMS into 3 ohms, 5·8 watts RMS into 15 ohm. Overall frequency response 30c/s–18Kc/s: Continuously variable tone controls: Bass, +8db to —12db at 100c/s. Treble, +10db to —10db at 10Kc/s.

The HSL.700 has been designed for true high fidelity reproduction from radio tuner, gramophone deck and tape recorder preamp. Supplied ready built and tested, complete with knobs, attractive anodised aluminium front escutcheon panel, long spindles (can be cut to suit your housing requirements) full circuit diagram and operating instructions.

**OUR SPECIAL PRICE £7.19.6.** P. & P. 7/6.

### LOUDSPEAKER BARGAINS

3in 4 ohm **10/-**, P. & P. 1/6. 5in 3 ohm **16/-**, P. & P. 3/–. 7 × 4in 3 ohm **21/-**, P. & P. 4/–. 10 × 6in 3 ohm **27/6**, P. & P. 6/-. E.M.I. 8 × 3in 3 ohm with high flux magnet **26/-**, P. & P. 4/–. E.M.I. 13½ × 8in 3 ohm with high flux ceramic magnet **42/-**, (15 ohm **45/-**), P. & P. 6/–. E.M.I. 13 × 8in, 3 or 15 ohm with two inbuilt tweeters and crossover network **4 gns**, P. & P. 6/–.

**BRAND NEW.** 12in 15w H/D Speakers, 3 or 15 ohm. Current production by well-known British maker. Now with Hiflux ceramic ferrobar magnet assembly **£5.10.0**, P. & P. 7/6. Guitar models: 25w **£6.0.0**. 35w **£8.0.0**.

**E.M.I. 3½in HEAVY DUTY TWEETERS.** Powerful ceramic magnet. Available in 3 or 8 ohm **15/-** each; 15 ohm **16/6** each. P. & P. 2/6.

**12in "RA" TWIN CONE LOUDSPEAKER**
10 watts peak handling. 3 or 15 ohm, **37/6**, P. & P. 6/–.

**35 OHM SPEAKERS**
3½in **14/-**, P. & P. 2/6; 7 × 4in **21/-**, P. & P. 4/–.

**MAGNAVOX DESK TYPE MOVING COIL MICROPHONE.** Medium impedance. Brand New — Special Price **42/-**. P. & P. 2/-.

**BALANCED ARMATURE EARPHONE**
Approx. 70 ohm impedance. Can be used as ultra sensitive mike or speaker. ONLY **3/6**. P. & P. 1/6

**CRYSTAL MIKES.** High imp. for desk or hand use. High sensitivity, **18/6**. P. & P. 1/6.

**HIGH IMPEDANCE CRYSTAL STICK MIKES.** OUR PRICE **21/-**. P. & P. 1/6.

**HIGH IMPEDANCE DYNAMIC STICK MIKES.** High sensitivity. **39/6**. P. & P. 2/6.

**SPECIAL OFFER! PLESSEY TYPE 29 TWIN TUNING GANG.** 400pF + 146pF. Fitted with trimmers and 5:1 integral slow motion. Suitable for nominal 470 kc/s I.F. Size approx. 2 × 1 × 1½ in. Only **8/6**. P. & P. 2/6.

**HONEYWELL MICROSWITCHES S/P. C/O.** Push-button action. Rating 250v. AC at 15 amps. Size approx. 1½" × ½" × ½". 5/- each. P. & P. 1/- (6 or more post free).

**TELESCOPIC AERIALS WITH SWIVEL JOINT.** Can be angled and rotated in any direction. 12 section Heavy Chrome. Extends from 7" to approx. 56". Maximum diameter ½". **10/-** each. P. & P. 1/6. 6 section Lacquered Brass. Extends from 6" to approx. 22½". Maximum diameter ¼". 5/- each. P. & P. 1/-.

## TRANSFORMER BARGAINS!

**BRAND NEW MULTI-RATIO MAINS TRANSFORMERS.** Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations: 0-5-10-15-20-25-30-35-40-60V half wave at 1 amp or 10-0-10, 20-0-20, 30-0-30V. at 2 amps full wave. Size 3inL × 3½inW × 3inD. Price **35/-**. P. & P. 6/-.

**MAINS TRANSFORMER.** For transistor power supplies. Pri. 200/240V. Sec. 9–0–9 at 500mA. **14/-**. P. & P. 2/6. Pri. 200/240V. Sec. 12–0–12 at 1 amp. **17/6**. P. & P. 2/6. Pri. 200/240V. Sec. 10–0–10 at 2 amp. **27/6**. P. & P. 3/6. Tapped Primary 200–220–240V. Sec. 21·5V at 500mA. **12/6**. P. & P. 2/6.

**BATTERY CHARGER TRANSFORMERS.** 200/240V. input. Nominal output for 6 or 12V. batteries 3 amps. Size approx. 3 × 2½ × 2½in. Brand New. Price **21/-**. P. & P. 5/-.

**HIGH GRADE COPPER LAMINATE BOARDS**
8 × 6 × ⅛in. FIVE for **10/-**. P. & P. 2/-.

**STOCKISTS OF SINCLAIR EQUIPMENT**
Z.30 Amplifier **89/6**. P. & P. 2/6. Stereo 60 Pre-Amplifier **£9.19.6**. P. & P. 5/-. PZ5 Power Supply **£4.19.6**. P. & P. 3/6. PZ6 Power Supply **£7.19.6**. P. & P. 3/6. IC.10 Integrated Circuit **59/6**. P. & P. 2/-.

## SPECIAL OFFER!!

**HI-FI LOUDSPEAKER SYSTEM. Beautifully made teak finish enclosure with most attractive Tygan front. Size 16½" high × 10½" wide × 6" deep. Fitted with E.M.I. Ceramic Magnet 13" × 8" bass unit, two H.F. tweeter units and crossover. Power handling 10 watts. Available 3 or 15 ohm impedance. 8 Gns.** Carriage 10/-

## TRANSISTOR STEREO 8 + 8 MK II

Now using Silicon Transistors in first five stages on each channel resulting in even lower noise level with improved sensitivity. A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors giving 8 watts push pull output per channel (16W mono). Integrated pre-amp. with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 3 to 15 ohms. Compact design, all parts supplied including drilled metal work. Cir-Kit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Freq. response ±3dB. 20–20,000c/s. Bass boost approx. to +12dB. Treble cut approx. to —16dB. Negative feedback 18dB over main amp. Power requirements 25V at 0·6 amp.

**PRICES:** AMPLIFIER KIT **£10.10.0**; POWER PACK KIT **£3.0.0**; CABINET **£3.0.0**. All Post Free.

Also available STEREO 10+10. As above but 10 watts per channel. **PRICES:** AMPLIFIER KIT **£12**. POWER PACK KIT £3.10.0.

Circuit diagram, construction details and parts list (free with kit) **1/6**. (8.A.E.).

**GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER.** For P.U. Tape, Mike, Guitar, etc., and suitable for use with valve or transistor equipment. 9–18V. Battery or from H.T. line 200/300V. Frequency response 15Hz–25KHz. Gain 26dB. Solid encapsulation size 1½ × 1½ × ½in. Brand new — complete with instructions. Price **17/6**. P. & P. 2/6.



**SPECIAL PURCHASE!**
**E.M.I. 4-SPEED PLAYER**
Heavy 8½in. metal turntable. Low flutter performance 200/250 V shaded motor (90 V tap). Complete with latest type lightweight pick-up arm and mono cartridge with t/o stylii for LP/78. ONLY **63/-**. P. & P. 6/6.

**QUALITY RECORD PLAYER AMPLIFIER MK II**
A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, EZ80 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. × 3 d. × 6 h. Ready built and tested. PRICE **75/-**. P. & P. 6/-. ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE **97/6**. P. & P. 7/6.

**DE LUXE QUALITY PORTABLE R/P CABINET MK II**
Uncut motor board size 14½ × 12in., clearance 2in. below, 5½in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 × 15 × 8in. PRICE **79/6**. P. & P. 9/6.



**3-VALVE AUDIO AMPLIFIER HA34 MK II**
Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7½in w. × 4in. d. × 4½in. h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4½ watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only **£4.15.0**. P. & P. 6/-.


**HSL "FOUR" AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. **79/6**. P. & P. 6/–.

## HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound mains transformer, EZ80 rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3·5 watts. Volume and tone controls. Chassis size only 7in. wide × 3in. deep × 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New completely wired and tested with valves and good quality output transformer. FEW ONLY.

**OUR ROCK BOTTOM BARGAIN PRICE 55/-** P. & P. 6/-

## DE LUXE STEREO AMPLIFIER

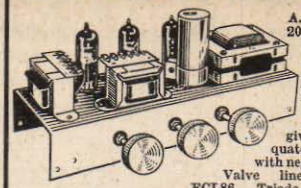

A.c. mains 200–240 volts. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up:—2 × ECL86 Triode Pentodes. 1 × EZ80 as full wave rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300m/v for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11in. w × 4in. x. Overall height including valves 5in. Ready built and tested to a high standard. **Price 8 gns.** P. & P. 8/-.

### 4-SPEED RECORD PLAYER BARGAINS

**Mains models. All brand new in maker's packing.**

**LATEST B.S.R. C109/A21 4-SPEED AUTOCHANGER.** With latest mono compatible cartridge **£6.19.6**. Carr. 6/6. With stereo cartridge **£7.19.6**. Carr. 6/6.

**LATEST GARRARD MODELS. All types available 1025, 2025, SP25, 3000, AT60 etc. Send S.A.E. for Latest Prices!**

**PLINTH UNITS** cut out for Garrard Models 1025, 2025, 2000, 3000, AT60, SP25. With rigid transparent plastic cover. Special design enables unit to be used with cover in position. OUR PRICE **£5.15.0** complete. P. & P. 8/6.

**LATEST ACOS GP91/1SC Mono Compatible Cartridge** with t/o stylus for LP/EP/78. Universal mounting bracket. **30/-**. P. & P. 1/6.

**SONOTONE 2539** High output Stereo Cartridge. T/O stylus for Stereo/LP/78. Complete with universal mounting bracket. List Price **48/7**.
OUR PRICE **25/-**. P. & P. 1/6.

**SONOTONE 9TAHC** compatible Stereo Cartridge with diamond stylus **50/-**. P. & P. 2/-.

**LATEST RONETTE T/O Stereo Compatible Cartridge** for EP/LP/Stereo/78. **32/6**. P. & P. 2/-.

**LATEST RONETTE T/O Mono Compatible Cartridge** for EP/LP/78 mono or stereo records on mono equipment. **30/-**. P. & P. 2/-.

**HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT Type TA1**



Peak output in excess of 1½ watts. All standard British components. Built on printed circuit panel size 6 × 3in. Generous size Driver and Output Transformers. Output transformer tapped for 3 ohm and 15 ohm speakers. Transistors (GET114 or S1 Mullard AC 128D and matched pair of AC128-o/p). 9 volt operation. Everything supplied, wire, battery clips, solder, etc. Comprehensive easy to follow instructions and circuit diagram **2/6** (Free with Kit). All parts sold separately. **SPECIAL PRICE 45/-**. P. & P. 3/-. Also ready built and tested, **52/6**. P. & P. 3/-.

**10/14 WATT HI-FI AMPLIFIER KIT**



A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3–15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet **2/6** (Free with parts). **All parts sold separately.** ONLY **£7.9.6**. P. & P. 8/6. Also available ready built and tested complete with std. input sockets, **£9.5.0**. P. & P. 8/6.

**BRAND NEW TRANSISTOR BARGAINS.** GET 15 (Matched Pair) **15/-**; V15/10p, **10/-**; OC71 **5/-**; OC76 **6/-**; AF117 **3/6**; 2G339 (NPN) **3/-**.
Set of Mullard 6 transistors OC44, 2—OC45, AC128D, matched pair AC128 **25/-**; ORP12 Cadmium Sulphide Cell **10/6**. All post free.

**VYNAIR AND REXINE SPEAKERS AND CABINET FABRICS** app. 54in. wide. Usually 35/- yd., our price **15/-** yd. length. P. & P. 2/6 (min. 1 yd.). S.A.E. for samples.

*Open 9-5.30 Monday to Saturday*
*Early closing Wed. 1 p.m.*
*A few minutes from South Wimbledon Tube Station*

# HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19 Tel. 01-540 3985

*SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES*

*(Please write clearly)*

**PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.**

## Brand New Fully Guaranteed
# TRANSISTORS & DEVICES

| | | | | | |
|---|---|---|---|---|---|
| 1N4001 | 2/- | AAZ13 | 2/6 | BPY10 | 19/6 |
| 1N4002 | 2/3 | AAZ17 | 2/- | BSX20 | 4/- |
| 1N4003 | 2/6 | AC126 | 5/- | BSX21 | 5/- |
| 1N4004 | 3/- | AC127 | 5/6 | BSX76 | 4/- |
| 1N4005 | 3/6 | AC127Z | 12/6 | BSY27 | 4/- |
| 1N4006 | 4/- | AC128 | 5/- | BSY28 | 5/- |
| 1N4007 | 5/- | AC153 | 4/- | BSY29 | 5/- |
| 1N4009 | 1/6 | AC154 | 3/- | BSY50 | 5/- |
| 1N4148 | 1/9 | AC169 | 3/- | BSY53 | 5/- |
| 2G301 | 4/- | AC176 | 5/- | BSY66 | 5/- |
| 2G302 | 4/6 | AC187 | 5/- | BSY67 | 5/- |
| 2G303 | 5/- | AC188 | 6/- | BSY95 | 3/- |
| 2G306 | 7/6 | ACY17 | 6/- | BSY95A | 4/6 |
| 2G308 | 7/6 | ACY18 | 4/- | BY100 | 3/6 |
| 2G309 | 6/- | ACY19 | 5/- | BY103 | 4/6 |
| 2G371 | 4/6 | ACY20 | 4/- | BY114 | 5/- |
| 2G374 | 5/6 | ACY21 | 4/6 | BY126 | 5/- |
| 2G381 | 5/- | ACY22 | 3/6 | BYZ10 | 10/- |
| 2G382 | 6/- | ACY28 | 3/6 | BYZ11 | 9/- |
| 2G383 | 5/- | ACY34 | 4/- | BYZ12 | 8/- |
| 2N404 | 4/6 | ACY36 | 5/- | BYZ13 | 5/- |
| 2N696 | 4/6 | ACY39 | 9/6 | BYZ15 | 20/- |
| 2N697 | 5/- | ACY40 | 3/- | BYZ16 | 12/6 |
| 2N698 | 8/6 | AD140 | 11/- | GET102 | 8/- |
| 2N706 | 1/6 | AD149 | 12/6 | GET103 | 4/6 |
| 2N706A | 2/6 | AD161 | 7/6 | MPF102 | 8/6 |
| 2N707 | 12/6 | AD162 | 7/6 | MPF103 | 7/- |
| 2N708 | 3/- | AF102 | 15/- | MPF104 | 7/6 |
| 2N914 | 4/6 | AF114 | 6/6 | MPF105 | 8/- |
| 2N916 | 4/6 | AF115 | 6/- | OA5 | 3/- |
| 2N918 | 7/6 | AF116 | 6/6 | OA7 | 4/- |
| 2N919 | 4/- | AF117 | 5/- | OA9 | 3/- |
| 2N920 | 5/- | AF118 | 12/6 | OA10 | 4/- |
| 2N922 | 8/6 | AF124 | 6/- | OA47 | 2/- |
| 2N930 | 7/6 | AF125 | 5/- | OA70 | 2/- |
| 2N1131 | 6/- | AF126 | 4/- | OA71 | 2/- |
| 2N1132 | 8/- | AF127 | 4/- | OA73 | 2/- |
| 2N1303 | 4/6 | AF139 | 6/- | OA74 | 2/- |
| 2N1304 | 5/- | AF178 | 9/6 | OA79 | 2/- |
| 2N1305 | 5/- | AF181 | 8/6 | OA81 | 2/- |
| 2N1306 | 5/- | AF186 | 9/- | OA85 | 2/6 |
| 2N1307 | 5/- | AF239 | 8/- | OA86 | 4/- |
| 2N1308 | 6/- | AFY19 | 22/6 | OA90 | 2/- |
| 2N1309 | 5/- | AFZ11 | 8/- | OA91 | 1/6 |
| 2N1613 | 5/- | AFZ12 | 10/- | OA95 | 1/6 |
| 2N2147 | 17/6 | ASY26 | 6/6 | OA200 | 1/9 |
| 2N2160 | 15/- | ASY27 | 7/6 | OA202 | 2/- |
| 2N2287 | 25/- | ASY28 | 6/6 | OA210 | 6/- |
| 2N2646 | 10/6 | ASY29 | 6/- | OA211 | 9/6 |
| 2N2904 | 8/6 | ASY67 | 9/6 | OAZ226 | 7/6 |
| 2N2905 | 10/- | ASZ21 | 8/6 | OAZ228 | 7/6 |
| 2N2925 | 4/- | AUY10 | 19/6 | OAZ229 | 9/6 |
| 2N2926 | 2/6 | B3M | 19/6 | OAZ231 | 9/6 |
| 2N3011 | 7/6 | BA110 | 5/- | OAZ234 | 7/6 |
| 2N3053 | 5/- | BAY31 | 2/- | OAZ238 | 9/6 |
| 2N3054 | 12/6 | BC107 | 3/- | OC16 | 10/- |
| 2N3055 | 15/- | BC108 | 2/9 | OC19 | 7/6 |
| 2N3702 | 3/6 | BC109 | 3/- | OC20 | 19/6 |
| 2N3703 | 3/6 | BC113 | 6/- | OC22 | 9/6 |
| 2N3704 | 4/- | BC116 | 9/- | OC23 | 12/6 |
| 2N3705 | 3/6 | BC118 | 7/6 | OC24 | 12/6 |
| 2N3707 | 4/- | BC134 | 7/6 | OC25 | 7/6 |
| 2N3709 | 3/6 | BC135 | 6/- | OC26 | 5/- |
| 2N3710 | 3/- | BC136 | 7/- | OC28 | 12/6 |
| 2N3794 | 2/6 | BC137 | 8/- | OC29 | 12/6 |
| 2N3711 | 3/6 | BC138 | 8/- | OC35 | 10/- |
| 2N3730 | 10/- | BC147 | 3/9 | OC36 | 12/6 |
| 2N3731 | 12/6 | BC148 | 2/9 | OC41 | 5/- |
| 2N3819 | 8/- | BC149 | 4/- | OC42 | 6/- |
| 2N3820 | 19/6 | BCY30 | 5/6 | OC43 | 8/- |
| 2N3823 | 17/6 | BCY31 | 8/6 | OC44 | 4/- |
| 2N4058 | 5/6 | BCY32 | 10/- | OC45 | 3/6 |
| 2N4061 | 4/- | BCY33 | 5/- | OC46 | 5/6 |
| 2N4286 | 3/- | BCY34 | 6/- | OC70 | 3/- |
| 2N4288 | 3/- | BCY38 | 7/- | OC71 | 3/- |
| 2N4289 | 3/6 | BCY39 | 8/6 | OC72 | 5/- |
| 2N4290 | 3/- | BCY40 | 10/- | OC73 | 6/- |
| 2N4291 | 3/- | BCY42 | 5/- | OC74 | 6/- |
| 2N4292 | 3/- | BCY43 | 5/- | OC75 | 5/- |
| 40361 | 12/- | BCY70 | 4/- | OC76 | 5/- |
| 40362 | 13/6 | BCZ11 | 7/6 | OC77 | 8/- |
| 28001 | 10/- | BD124 | 12/6 | OC78 | 5/- |
| 28002 | 10/6 | BEN3000 | 5/- | OC81 | 5/- |
| 28003 | 9/6 | BF115 | 5/- | OC81D | 4/- |
| 28004 | 9/6 | BF152 | 6/- | OC82 | 5/- |
| 28005 | 15/- | BF154 | 8/- | OC83 | 5/- |
| 28012 | 25/- | BF158 | 6/- | OC84 | 5/- |
| 28013 | 20/- | BF159 | 12/- | OC122 | 10/- |
| 28017 | 15/- | BF163 | 8/- | OC123 | 10/- |
| 28034 | 12/6 | BF167 | 5/- | OC139 | 5/- |
| 28036 | 25/- | BF173 | 6/- | OC140 | 7/6 |
| 28320 | 9/- | BF180 | 7/6 | OC141 | 15/- |
| 28321 | 6/- | BF181 | 7/6 | OC169 | 5/- |
| 28322 | 7/6 | BF194 | 3/6 | OC170 | 5/- |
| 28323 | 10/- | BF195 | 3/- | OC171 | 6/- |
| 28324 | 12/6 | BFX30 | 6/- | OC200 | 5/- |
| 28512 | 9/6 | BFX88 | 5/- | OC201 | 9/6 |
| 28701 | 8/6 | BFY20 | 12/6 | OC202 | 18/6 |
| 28702 | 11/- | BFY50 | 5/- | OC203 | 7/6 |
| 28731 | 8/6 | BFY51 | 4/6 | OC204 | 8/- |
| 28732 | 8/6 | BFY52 | 5/- | OC205 | 12/6 |
| 28733 | 9/6 | BFY53 | 4/- | OC206 | 15/- |
| AA178 | 8/6 | BFY64 | 8/6 | OC207 | 15/- |
| AAY12 | 5/- | BLY10 | 20/- | OCP71 | 19/6 |
| AAZ12 | 4/- | BLY11 | 22/6 | ORP12 | 12/6 |
| | | | | ORP60 | 8/- |

### INTEGRATED CIRCUITS

| Type | 1 | 12+ | 25+ | 100+ | 500+ |
|---|---|---|---|---|---|
| UL914 | 9/9 | 9/- | 8/- | 7/3 | 6/6 |
| UL923 | 12/6 | 11/9 | 11/- | 10/- | 9/3 |
| SL403A | 49/6 | 45/- | 40/- | 37/6 | 35/- |
| MC1303 | 52/6 | 48/ | 45/- | 40/- | 35/- |
| MC1304 | 55/- | 50/- | 47/6 | 42/6 | 37/6 |
| PA246 | 52/6 | 48/- | 45/- | 40/- | 35/- |

**2N3055** 15/- Mullard 115 watt Silicon power
25+ 13/- 100+ 11/-

**2N3819** 8/- Texas F.E.T.
25+ 6/9 100+ 5/9 500+ 5/-

**2N2926** 2/- NPN planar all colours
25+ 1/8 100+ 1/6

**2N2646** 10/6 Motorola Unijunction
25+ 8/9 100+ 7/6 500+ 6/9

**AF139** 6/- Siemens V.H.F.
25+ 5/3 100+ 4/6 500+ 3/9

**AF186** 9/- Mullard V.H.F.
25+ 8/- 100+ 7/- 500+ 6/-

**AD161/AD162** 6/6 ea. Mullard NPN/PNP
25+ 5/- 100+ 4/3

**BY126** 3/6 Mullard 800V 1 amp plastic
25+ 2/9 100+ 2/6

**BY127** 4/- Mullard 800V 1 amp plastic
25+ 3/3 100+ 3/-

**BYZ13** 5/- Mullard 6A 200V
25+ 4/- 100+ 3/4 500+ 3/-

**BT102/500R** 12/6 Mullard thyristor 500 p.i.v. 6·5 amp
25+ 11/- 100+ 10/3

**BC107/8/9** 2/9 I.T.T. planars
25+ 2/5 100+ 2/- 500+ 1/10

**OA200/OA202** 1/9 Silicon diodes
25+ 1/6 100+ 1/3 500+ 1/1

**OCP71** 19/6 Mullard photo
25+ 17/3 100+14/9 500+ 13/6

**OC42** 6/- Mullard
25+ 5/3 100+ 4/9 500+ 4/3

**OC44** 4/- Mullard
25+ 3/3 100+ 2/9 500+ 2/4

**OC45** 3/6 Mullard
25+ 3/- 100+ 2/6 500+ 2/-

**OC71** 3/- Mullard
25+ 2/3 100+ 2/- 500+ 1/9

**OC75** 5/- Mullard
25+ 4/3 100+ 3/6 500+ 3/-

**BCY34** 6/- Mullard
25+ 5/- 100+ 4/3 500+ 4/-

**OC20** 19/6 Mullard 100V
25+ 15/9 100+ 14/6 500+ 13/3

**IN4001/2/3** 2/3 1 amp 100–300V
25+ 1/10 100+ 1/6 500+ 1/4

**IN4004/5** 3/- 400–600V 1 amp
25+ 2/6 100+ 2/- 500+ 1/10

**ZENER DIODES** 400MW 5% BZY88 range all voltages 3·3V–33V 4/-
25+ 2/6 100+ 2/- 500+ 1/9 1,000+ 1/7 any one type

**IN4006/7** 4/- 800–1000V 1 amp
25+ 3/4 100+ 3/- 500+ 2/6

**OC139** 5/- Mullard
25+ 4/- 100+ 3/3 500+ 3/-

**OC140** 7/6 Mullard
25+ 6/- 100+ 5/- 500+4/-

**SEND FOR YOUR FREE COPY OF 1970 LIST NO. 36 OF OVER 1,000 DEVICES TODAY!**
**Discounts** 10% on 12+ any one type
15% on 25+ any one type

Quantity prices 100+ phone (01) 723 0401 Ex. 4
All listed devices are from stock. Please add 1/6 post and packing to your order. Please note minimum order value 10/-.

**HENRY'S RADIO** 303 EDGWARE ROAD LONDON, W.2 (01) 723 1008/9
OPEN MON-SAT 9am-6pm THURS 9am-1pm



# If you can put a 'Yes' in every box, you might just make a RADIO TECHNICIAN in Air Traffic Control

An all-consuming interest in telecommunications ☐

At least one year's practical experience in telecommunications, preferably with 'ONC' or 'C and G' technical qualifications ☐

A highly developed sense of responsibility ☐

Willingness to undergo a rigorous programme of training ☐

Aged 19 or over ☐

**To the right man, the National Air Traffic Control Service offers the prospect of an interesting and steadily developing career as a Radio Technician in air traffic control.**

The work involves the installation and maintenance of some of the very latest electronic equipment at civil airports, radar stations and other specialist establishments all over the country. Important today, the job will become increasingly vital as Britain's air traffic continues to grow, and prospects for promotion are excellent. Starting salary varies from £1044 (at 19) to £1373 (at 25 or over). Scale maximum £1590 (higher rates at Heathrow). The annual leave allowance is good, and there is a non-contributory pension for established staff.

If you feel you can meet the demands of this rather special job—and you have a strong determination to succeed—you are invited to complete the coupon below.

Send this coupon for full details and application form
**To: A J Edwards, C Eng, MIEE, The Adelphi, Room 705, John Adam Street, London WC2,**
marking your envelope "Recruitment".

Name .....

Address .....

PET/G1

Not applicable to residents outside the United Kingdom

**NATCS**
**National Air Traffic Control Service**

# Practical Electronics Classified Advertisements

RATES: 1/6 per word (minimum 12 words). Box No. 1/6 extra. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London, E.C.4

## MISCELLANEOUS

### MORE ROBOTS

Synthetic Animals with "BRAINS" of their own. The LATEST range of projects include: an electronic 'animal' which "LEARNS", and an Electro Chemical device capable of "REPRODUCING" itself! Other projects SURE TO INTRIGUE YOU are a transmitter/receiver which radiates without using r.f. so there's NO NEED TO WORRY ABOUT A LICENCE, also TEN new projects, one of which is an electronic dice machine. HOSTS OF EASY-TO-CONSTRUCT projects, for anyone with a basic knowledge of Electronics. DON'T WAIT. SEND 3/- for your list—NOW!

To: 'BOFFIN PROJECTS'
4 CUNLIFFE ROAD
STONELEIGH, EWELL, SURREY
Designed by GERRY BROWN and JOHN SALMON and presented on T.V.

### TOP TRANSISTORS

| | | |
|---|---|---|
| ACY22 1/9 | OC45 1/9 | ZTX300 1/9 |
| BFY51 1/9 | OC71 1/9 | 2N706 1/9 |
| BFY52 1/9 | OC201 1/9 | 2N2926 1/9 |
| BSY27 1/9 | OC202 1/9 | 2N3708 1/9 |

All the above items are available at 16 for £1. Brand new. Individually tested.

### ANTEX SOLDER IRON

This is a lightweight iron fitted with a 15 watt nickel plated bit. It has been designed to enable you to weld reliable joints quickly and accurately.

Special low price. Model CN240 volts.

**ACT NOW 29/11**

MONEY BACK GUARANTEE—P. & P. 1/-

**J. M. KING (S), 17 Buckridge Portpool Lane, London, E.C.1**

**A CORNUCOPIA OF COMPONENTS!** Scarce valves, selected TV components, speakers and cabinets. Computer panels—long leads, NOT printed circuits. Transistors, resistors—new and recovered. State your requirements. S.A.E. for details MAIL-MART, 6 Eastbourne Road, Pevensey Bay, Sussex.

**BUILD IT** in a DEWBOX quality cabinet 2in × 2½in × any length. DEW LTD., Ringwood Road, Ferndown, Dorset. S.A.E. for leaflet. Write now—right now.

### POWER SUPPLIES

**Professional grade silicon transistor power supply modules.** Units consist of p.c. board assembly size 6" × 3½". 240 Volts AC input. DC Voltage adjustable from 9-13 Volts at max 250mA. No load to full load voltage change less than 1%. Ripple less than 2mV. **£5. 2. 6d.** each.
Also available PEAC Op. Amps. **34**/- each.
**WESTEK**
**P.O. BOX 7, RICKMANSWORTH, HERTS**

**ENAMELLED COPPER WIRE**

| S.W.G. | Per ¼lb reel | Per 1lb reel |
|---|---|---|
| 18–22 | **11/3** | **16/6** |
| 23–30 | **11/9** | **17/6** |
| 31–35 | **12/3** | **18/6** |
| 36–40 | **13/6** | **21/-** |
| 41–44 | **16/3** | **26/6** |

Orders despatched by return of post. Please add 1/- per item P. & P. Supplied by: BANNER TRANSFORMERS, 84 Old Lansdowne Road, West Didsbury, Manchester, 20. TRADE ENQUIRIES INVITED.

**PARAPHYSICAL LABORATORY,** Downton, Wilts. Telekinetic photographs/data. S.A.E. for list. Samples **20s.**

## MISCELLANEOUS *(continued)*

**PHOTO ELECTRIC SWITCH KIT**
Light cell transistor, relay etc. Elegant case in hammer blue 5¾" × 2¾" × 4¼" fitted with light hood, ideal counter alarm, dawn/dusk switch, etc. **35**/- post paid.

### 6 OR 12 VOLT FLUORESCENT LIGHTS

12 ins. 8 Watt tube ample light for caravan, tent, etc. Fully transistorised, low battery drain
Unbeatable at **65/6** post paid.
or in kit form **57/6**

### 4 WATT GRAM AMPS.

Volume and tone controls, mains operation, 3Ω output, new and boxed **72/6** POST PAID
**SALOP ELECTRONICS** Callers welcome
**23 Wyle Cop**
**Shrewsbury, Shropshire** *S.A.E. for lists*

**CLEARING LABORATORY,** scopes, V.T.V.M's, V.O.M's, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, M/C relays, components, etc. Lower Beeding 236.

**MUSICAL MIRACLES!** Drum, Cymbals, Waa-waa and Fuzz modules. New unique effects units, Percussion, etc. Good waa-waa kits **49/-.** Famous "Mister Bassman" bass pedal unit. Also bargain components list of reed switches, etc. Send S.A.E. NOW! D.E.W. LTD., 254 Ringwood Road, Ferndown, Dorset.

## FOR SALE

**NEW CATALOGUE** No. 18, containing credit vouchers value 10/-, now available. Manufacturers' new and surplus electronic and mechanical components, price **4/6,** post free. ARTHUR SALLIS RADIO CONTROL LTD., 28 Gardner Street, Brighton, Sussex.

### MORSE MADE EASY !!

**FACT NOT FICTION.** If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected).
Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.
For details and course C.O.D. ring S.T.D. 01-660 2896 or send 8d. stamp for explanatory booklet to:
**G3HSC (Box 19), 45 GREEN LANE, PURLEY SURREY**

**ALL KINDS OF EVERYTHING** for sale to Irish readers. Write for price list, plus Bargain page. TONER ELECTRONICS, Lismore Park, Waterford. Phone 3048.

**FOR SALE.** Crystal Microphone and Stand. New unused. JOHNSON, Stalham, Norfolk.

**LOUDSPEAKER CABINETS LIMITED.** Number of quality made Speaker Cabinets For Sale size 23¼in high, 10in deep, 15in wide. Available in teak or walnut. C.W.O. Price **£10** + P. & P. 10/-. Callers welcome. ELECTRONIC SOUND, 31 Newberries Parade, Radlett, Herts. Tel. 5440.

## HI-FI EQUIPMENT

**SHURE GOLDRING** Cartridges. Post Free. G800, M44/5/7 **£7.17.6.** M3D **£5.5.0.** M44E **£8.19.6.** M55E **£9.19.6.** M75E/2 **£16.10.0.** Garrard SP25/2 **£10.17.6.** AP.75 **£16.17.6.** P. & P. 7/6. ULTIMATE ELECTRONICS, 38 Achilles Road, London, N.W.6. Mail Order Only.

## WANTED

**CASH PAID** for New Valves. Payment by return. WILLOW VALE ELECTRONICS, 4 The Broadway, Hanwell, London, W.7. 01-567 5400/2971.

## SERVICE SHEETS

### LARGE SUPPLIER OF SERVICE SHEETS

T.V., RADIO, TRANSISTORS, TAPES, CAR RADIOS
5/- EACH, MANUALS FROM 10/- PLUS LARGE S.A.E.
(Uncrossed P.O.'s please, original returned if service sheets not available.)
FREE TV FAULT TRACING CHART OR TV LIST ON REQUEST WITH ORDER
**C. CARANNA**
**71 BEAUFORT PARK, LONDON, N.W.11**
***MAIL ORDER ONLY***

**SERVICE SHEETS.** Radio, TV, etc., 8,000 models. List **2**/-. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

**SERVICE SHEETS** (1925–1970) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from **1**/-. Over 8,000 models available. Catalogue **2/6.** Please send S.A.E. with all orders/enquiries. HAMILTON RADIO, 54 London Road, Bexhill, Sussex.

**RADIO TELEVISION,** over 8,000 Models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Rd., London, W.6. SHE 8441.

## BOOKS AND PUBLICATIONS

### SURPLUS HANDBOOKS

| | |
|---|---|
| **19 set** Circuit and Notes ..... | **7**/- P.P. 9d |
| **1155 set** Circuit and Notes .... | **7**/- P.P. 9d |
| **H.R.O.** Technical Instructions .. | **6**/- P.P. 9d |
| **38 set** Technical Instructions.... | **6**/- P.P. 9d |
| **46 set** Working Instructions.... | **6**/- P.P. 9d |
| **88 set** Technical Instructions.... | **7/6** P.P. 9d |
| **BC. 221** Circuit and Notes ..... | **6**/- P.P. 9d |
| **Wavemeter Class D** Tech. Instr | **6**/- P.P. 9d |
| **18 set** Circuit and Notes ..... | **6**/- P.P. 9d |
| **BC.1000 (31 set)** Circuit & Notes | **6**/- P.P. 9d |
| **CR.100/B.28** Circuit and Notes | **10/6** P.P. 1/- |
| **R.107** Circuit and Notes..... | **7/6** P.P. 9d |
| **A.R.88D.** Instruction Manual.... | **18/6** P.P. 9d |
| **62 set** Circuit and Notes ..... | **7**/- P.P. 9d |
| **52 set** Sender & Receiver Circuits | **8**/- post free |

**Circuit Diagrams 5/6** each post free. R.1116/A, R.1224/A, R.1355, R.F. 24, 25, & 26. A.1134, T.1154, CR.300, BC.342. BC.312. BC.348.J.E.M.P. BC.624. 22 set.
**Colour Code Indicator 2/6** P.P. 6d.
S.A.E. with all enquiries please
Postage rates apply to U.K. only.
Mail order only to:
**Instructional Handbook Supplies**
**Dept. P.E., Talbot House, 28 Talbot Gardens Leeds 8**

## EDUCATIONAL

**ENGINEERS.** A technical certificate or qualification will bring you security and much better pay. Elem. and adv. private postal courses for C.Eng., A.M.I.E.R.E., A.M.S.E. (Mech. & Elec.), City & Guilds, A.M.I.M.I., A.I.O.B. and G.C.E. exams. Diploma courses in all branches of Engineering—Mech., Elec., Auto, Electronics, Radio, Computers, Draughts., Building, etc. For full details write for FREE 132-page guide. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Dept. 125K), Aldermaston Court, Aldermaston, Berks.

**GET INTO ELECTRONICS**—big opportunities for trained men. Learn the practical way with low-cost Postal Training, complete with equipment. A.M.I.E.R.E., R.T.E.B., City & Guilds, Radio, T/V, Telecoms., etc. For FREE 100-page book, write Dept. 856K, CHAMBERS COLLEGE, College House, 29-31 Wrights Lane, Kensington, London, W.8.

## COURSES

**FULL TIME COURSES** in (*a*) Basic Electronics, (*b*) Television Servicing. Nine month courses starting September 21 next, leading to City and Guilds certificates. Extensive laboratory work included. Full details from: Section 47/48, SOUTHALL COLLEGE OF TECHNOLOGY, Beaconsfield Road, Southall, Middx.

**ISLEWORTH POLYTECHNIC**

FULL-TIME COURSES IN ELECTRONICS FOR SCHOOL-LEAVERS

**ARE YOU:** between 16 and 18 years old? aiming at a career in electronics?

**HAVE YOU:** completed 5 years secondary education (preferably taking C.S.E's in Maths and Physics?)
lived in the U.K. for 3 years or more?

**DID YOU KNOW:** further education, for you, is free?

One year full-time courses at Isleworth Polytechnic prepare students for the Part I Radio Television and Electronics Technician's Certificate and the Part I Telecommunication Technician's Certificate (C. and G. 434 and 49). (Also courses available for Electronics Mechanics (Part I C. and G. 433).

Write for details and application forms

**The Head of Science and Electrical Engineering Department, Isleworth Polytechnic, St. John's Road, Isleworth, Middx.**

## OFFICIAL APPOINTMENTS

**LONDON BOROUGH OF EALING EDUCATION DEPARTMENT**

LABORATORY TECHNICIAN required at Southall College of Technology as soon as possible to work in the Electronics and Television Servicing Laboratories. Experience in television/electronics servicing essential. Good trade or other relevant qualifications will be an advantage. Salary £1,055 – £1,220 inclusive (under review).

Application forms obtainable from the Registrar of the College, Beaconsfield Road, Southall, Middlesex, returnable within 14 days of appearance of this advertisement.

**P. J. COOMBER**
**Town Clerk and Chief Executive Officer**

## SITUATIONS VACANT

A.M.I.E.R.E., A.M.S.E. (Elec.), City & Guilds, G.C.E., etc., on "Satisfaction or Refund of Fee" terms. Wide range of Home Study Courses in Electronics, Computers, Radio, T.V., etc. 132-page Guide—FREE. Please state subject of interest. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Dept. 124K), Aldermaston Court, Aldermaston Berks.

## RECEIVERS AND COMPONENTS

**GUARANTEED TUBES AT REDUCED PRICES**

We are the area stockists for Display Electronics Re-manufactured Tubes. These tubes have a complete new gun assembly, the glass is the only reconditioned part and that cannot wear out.
We invite enquiries from the trade or the public.
*Daily* 9.30-5.30. *Fri.* 9.30-8, *closed Wednesday.*
**TELEVISION CITY**
50 Richmond Road, Kingston, Surrey
Telephone 01-546 3961 (100 yards from station)

**BRAND NEW ELECTROLYTICS** 15/16V 0·5, 1, 2, 5, 8, 10, 20, 30, 40, 50, 100mF, **8·5d.** E12 series 5% resistors, Carbon Film ¼W 10Ω to 1MΩ. **1·5d.** Wirewound 5W 15Ω to 15KΩ, **10d.** Postage 1/-. The C.R. SUPPLY CO., 127, Chesterfield Rd., Sheffield, S8 0RN.

**ALIVE AND WELL** and living in Croydon. Amatronix Ltd. still going strong. Ceramic filters, transistors, amplifier packs. 2N3819 **7/6,** BC169 **2/6.** List 6d. Mail order only. 396 Seisdon Road, S. Croydon, Surrey CR2 0DE.

**BIRD ORGAN SPARES**

We hold large stocks having purchased manufacturers' entire stock.
6 watt amplifier. Black cloth finish. 6" × 10" speaker. 2 inputs. Tone volume controls. Size 14" × 6½" × 24". Price £14 C.W.O.
100 watts solid state amplifiers. 2, 4 and 6 input. Separate volume. Treble, bass, master controls from £83.9.6.
Mini-Lez "Leslie" type cabinet. Teak finish. Size 15" × 13½" × 17½" from £39.
Stop Tab units. Pedal Boards, Swell Pedals, etc. Send S.A.E. for brochures and price lists:
**E.M.C. P.E.2**
**22 Norwich Road**
**Bournemouth BH2 5QZ**

## SITUATIONS VACANT

**UNIVERSITY OF SOUTHAMPTON INSTITUTE OF SOUND AND VIBRATION RESEARCH**

Person required to help with development and operation of instrumentation systems for noise and vibration measurement, including analysis of data and routine maintenance of equipment. Salary on scale — either – £456 – £771 or £905 – £1,273 with supplementary allowances for qualifications. Please write stating date of birth, experience and qualifications and giving the names of two referees to the

**Deputy Secretary**
**The University**
**Southampton SO9 5NH**
quoting Ref.: PE

**JUNIOR TECHNICAL OFFICER or TECHNICIAN**

required at our Hampstead Laboratories, Holly Hill, N.W.3, to assist scientists engaged on new concept of medical research of 'Human Aerodynamics'. Suitable for applicant in early 20's with some experience of workshop practice and interest in electronic instrumentation. Salary according to experience and qualifications (O.N.C./H.N.C.) on scale £759 – £1,508 p.a. Please apply quoting our reference PE 51/1 to:

**Mr. J. H. WOODCOCK**
National Institute For Medical Research
The Ridgeway, Mill Hill
London, N.W.7
Telephone 959 3666

ICS
Established 1891

**TECHNICAL TRAINING IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING**

First-class opportunities in Radio and Electronics await the **I C S trained man.** Let I C S train YOU for a well-paid post in this expanding field.
I C S courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma courses in Radio/TV Engineering and Servicing, Electronics, Computers, etc. Expert coaching for:

* **C. & G. TELECOMMUNICATION TECHNICIANS' CERTS.**
* **C. & G. ELECTRONIC SERVICING.**
* **R.T.E.B. RADIO AND TV SERVICING CERTIFICATE.**
* **RADIO AMATEURS' EXAMINATION.**
* **P.M.G. CERTIFICATES IN RADIOTELEGRAPHY.**

Examination Students coached until successful.

**NEW SELF-BUILD RADIO AND ELECTRONIC COURSES**
Build your own 5-valve receiver, transistor portable, signal generator, multimeter and valve volt meter—**all under expert guidance.**

POST THIS COUPON TODAY and find out how I C S can help YOU in your career. Full details of I C S courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF THE ASSOCIATION OF BRITISH CORRESPONDENCE COLLEGES

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

**A WHOLE WORLD OF KNOWLEDGE AWAITS YOU!**

International Correspondence Schools
(Dept. 152), Intertext House, Stewarts Road,
London, S.W.8.

**NAME** .....
Block Capitals Please

**ADDRESS** .....

.....

..... 8.70

# INSTRUMENTAL AUDIO EFFECTS

**SUPER "FUZZ" UNIT.** Connects between guitar and amplifier. Operates from 9V battery. Complete printed-circuit board assembly, built and tested. Size 3½in × 2½in × ⅞in. **65/–** plus 2/6 carriage.

**"WAA-WAA" UNIT.** Connects between guitar and amplifier. Operates from 9V battery. Complete printed-circuit board assembly, built and tested. Size 3½in × 2½in × ⅞in. **65/–** plus 2/6 carriage.

**CREATE "PHASE"** on your tape recordings, records, etc., unique electronic circuitry enables you to create "phase" at the turn of a knob. Just connect between pre-amp. and power-amp.

This is not waa-waa, white-noise or swish but genuine phase-shift created electronically. Input and output impedances match to 10–50k Ω. Operates from 9V battery. Complete printed-circuit assembly, built and tested. Size 4in × 2½in × 1⅜in. **65/–** plus 2/6 carriage.

**"AUTO-WAA".** The basic "waa-waa" type amplifier concept has been made more sophisticated by automatically generating this effect with an oscillator. This removes the need for a potentiometer or foot pedal and replaces this with two controls to alter the repetition rate and duty cycle of the oscillator.

This unit can be connected between a guitar and an amplifier to provide continuous "waa-waa" effect; or between an organ keyboard and amplifier. To provide an effect similar to a "Leslie" speaker with variable speed from chorale to fast rate. Operates from 2 × 9V batteries. Complete printed-circuit assembly, built and tested. Size 4½in × 3½in × 1½in. **£5** plus 2/6 carriage.

*Trade Enquiries Invited* *Mail Order Only*

S.a.e. for all enquiries

## DABAR ELECTRONIC PRODUCTS

**98a LICHFIELD STREET**

**WALSALL, STAFFS.**

---

**POLYESTER CAPACITORS**

400V, 0·0068, 0·0047, 0·0033, 0·0022μF, **7d.** 160V, 0·01, 0·015, 0·022, 0·033, 0·047, **7d;** 0·068, 0·1, **8d;** 0·15, 0·22, **10d;** 0·33, **1/-;** 0·47, **1/4;** 0·68, **2/-.**

Mica: 350pF, 2kV, 600pF, 240pF, 160pF, 150pF, 100pF, 62pF, 30pF, 27pF, 22pF, 10pF, 8·2pF, 3·3pF, **6d.**

Printed circuit type: 470pF, 220pF, 50pF, **6d.**

**ELECTROLYTIC CAPACITORS**

500μF can, 6V; 400μF, 6·4V; 320μF, 10V; 30μF, 6V; 20μF, 6V; 8μF, 6V; 4μF, 4V, **1/-.**

**RESISTORS**

¼W 200Ω 2·7k, 22k, 30k, 62k, 83k, 150k, 430k; ½W 1k, 1·5k, 3·6k, 5·6k, 27k, 47k, 68k, 560k, **2½d.**

**TRANSISTORS**

OC200, **6/-:** OC201, **7/6;** BCY30, **6/-;** BCY31, **7/6.**

Tested Silicon TO5 and SO2, Audio: high gain, **4/-;** medium, **2/-,** low, **1/-.**

Diode IN914, **1/6.** Connecting Wire, 25yd, **2/6.**

C.W.O. Post and Packing 1/6

**VALECTRON**

LINKS ROAD, LOWESTOFT

---

**CONNOR SIGNAL TESTER** for testing Radios, Record Player, Amplifiers, and T/Vs. Tester consists of Audio Amplifier, Multivibrator, a Dectector (AM), and Test Speaker (25z). Speed up your service with a Connor Tester. Battery operated, **£15,** with probe leads, less battery, Post free. C.W.O. CONNOR ELECTRONICS, 43 Wade Reach, Kirby Road, Walton on Naze, Essex.

---

**AUDIOSCAN-HI-FI** loudspeaker systems for the home constructor, cabinet kits, new range of Peerless speakers, speaker kit systems and cross-over networks. BAF wadding and all necessary components. Free speaker fabric samples on request. Send **9d** in stamps to: AUDIOSCAN, Dept. PE, 4 Princes Square, Harrogate, Yorks.

---

**POLYSTYRENE CAPACITORS:** 125/350V 150, 180, 330, 390, 560, 680, 820, 1,800, 2,200, 2,700, 5,600, 6,800, 8,200: 125V 18, 22, 120, 220, 1,200, 1,500, 3,300, 3,900, 0.01, 0.012, 0.015. Paper: 100V 0.0001, 0.001, 0.002, 0.005, **3/-** doz. **Computer Panels:** 5-BC108, Diodes, **3/-, 4-10/-;** 8-OC76, 8-OA10, **5/-;** 4-OC42, **3/-;** 8-OC43/GET875, 24-OA81, **7/6;** 24-A1678, 550 MEE pnp. 24 Diodes **10/-;** 3-OC23, 8 Diodes **10/-.** Mixed Transistors on Panels 100 **20/-. Brand New Chassis:** 2-OC35, 2-OC29, 12-W.W. Resistors, **25/-. Electrolytics:** 4,000, 60V, **7/6.** Post 1/6 order. J.W.B. RADIO, 75, Hayfield Road, Salford, 6, Lancs.

---

## R & R RADIO

**51 Burnley Road, Rawtenstall**

**Rossendale, Lancs**

**Tel.: Rossendale 3152**

**VALVES BOXED, TESTED & GUARANTEED**

| | | | | | |
|---|---|---|---|---|---|
| EBF80 | 3/- | PCC84 | 3/- | PY81 | 3/6 |
| EBF89 | 3/6 | PCF80 | 3/- | PY82 | 3/- |
| ECC82 | 3/- | PCF82 | 3/6 | PY800 | 3/6 |
| ECL80 | 3/- | PCL82 | 4/- | PY801 | 3/6 |
| EF80 | 1/6 | PCL83 | 4/- | UI91 | 4/6 |
| EF85 | 3/- | PL36 | 5/- | 30F5 | 2/6 |
| EY86 | 4/- | PL81 | 4/- | 30P12 | 4/6 |
| EZ40 | 4/6 | PL83 | 4/- | 30C15 | 5/- |
| EBC41 | 4/6 | PY33 | 5/- | 50CD6G | 7/6 |

POST, ONE VALVE **9d.** TWO TO SIX **6d.** OVER SIX POST PAID.

---

**BRAND NEW FULL SPECIFICATION COMPONENTS**

2N706 3/-; 2N1711 6/8; 2N2906 12/-; 2N3456 30/-; 2N3703 3/3; BF117 10/-; SL403A 46/-; SL702C 21/-. Sub-min. polyester capacitors: 250V: 0·0047 and 0·01 μF. 11d ea., 0·022 1/- ea., 0·047 1/1 ea. High stab ¼W 5% resistors 47 ohm to 10 MΩ 1/4 per 5; 5/3 per 25; 19/- per 100— your selection. Catalogues 1/-. P. & P. on all orders under £2; 2/-.

**SPECIALIST ELECTRONICS CO.**
26 York Road, Crosby, Liverpool L23 5TS

---

**PRINTED CIRCUIT BOARDS for P.E. PROJECTS**

All boards drilled and roller tinned complete with layout drawing.

**EXAMPLES**

Marine Tachometer (May 1970) 5/- ea. Musical Stave (May 1970) 8/- ea.

Waa-Waa pedal Vol. 4 No. 7 **2/9** ea. Audio Sig. Gen. (Sine and Square on one board) Vol. 5 No. 10 **8/6** ea.

S.A.E. for List of over 36 Boards. Trade enquiries welcomed.

**P.H. ELECTRONICS, Industrial Estate, Sandwich, Kent.** Tel. 2517

---

**PRINTED CIRCUITS.** Capacity now available Send artwork for quote. S.A.E. Sample 1 off. Artwork, reduction, negative, **4d.** per. sq in. 1/10in Fibreglass. **1/6** per sq in. including tinning. Drilling extra. FREEMANTLE, 18 Pennine Road, Millbrook, Southampton.

---

**OFFER.** Copper laminated 1/16in fibreglass. Board single-sided **4d.** per sq in. Double-sided **5d.** per sq in. Any size cut. Minimum order **10/-.** P. & P. plus 10%. FREEMANTLE, 18 Pennine Road, Millbrook, Southampton.

---

*CONSTRUCTOR UNITS*

*R.F. Generator.* Supplied with coils, tuning cap., switch and details for wiring and calibration. Covers 150KH/z to 30MH/z. **89/6** + 3/6 p.p.

*A.F. Unit.* Osc. operates at 2 freq's. for A.F. R.F. checks, connects as amp. for continuity checks. Dual freq. square wave o/p for audio/HiFi tests. Provides modulation for R.F unit. **39/6** + 3/6 p.p. S.A.E. for details.

Tweed Electronics (PE), 9 The Green, Hatfield Peverel, Chelmsford, Essex

---

## NEW MODEL V.H.F. KIT MK2

Our latest Kit, improved design and performance plus extra Amplifier Stage, receives Aircraft, Amateurs, Mobile, Radio 2, 3, 4, etc.

This novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 Volt Battery, complete with easy to follow instructions and built in Jack Socket for use with Earphones or Amplifier.

**Only 68/-. P. & P. Free U.K. only**

Postal Orders, Cheques to:
Dept. P.E.
Galleon Trading Co., 298A Lodge Lane
Romford, Essex

---

# SILICON TRANSISTORS 1,000,000 FOR SALE

Clearance of *pnp* Silicon Alloy Transistors from the 2S300 (TO-5) and 2S320 (SO-2) range and similar to the OC200-205 and BCY30-34 series. Available only from us at a fraction of the manufacturing cost. All these devices would normally be subject to re-selection for industrial use but owing to company policy change have been made available to us surplus to requirements. Offering these transistors in varied quantities make them ideal for *Amateur Electronics, Radio Hams and for experimental use in Schools, Colleges and Industry.*

Supplied uncoded (no warranty by the manufacturers). But our assurance given that a minimum of 80% will be found to be good usable Silicon Alloy Transistors. Please state preference of type, i.e., TO-5 2S300 or SO-2 2S320.

Approximate count by weight:
100 off—**15s.** (plus p. & p. 2s.)
300 off—**£1 15s.** (plus p. & p. 3s.)
500 off—**£2 10s.** (plus p. & p. 3s. 6d.)
1,000 off—**£4** (plus p. & p. 5s.)
10,000 off—**£35** (plus p. & p. 11s.)

Large quantities quoted for on request.

EXPORT ENQUIRIES WELCOME

All correspondence, cheques, postal orders, etc., to:

**DIOTRAN SALES**
**P.O. BOX 5**
**63a High Street, Ware, Herts.**
**Tel.: WARE 3442**

---

*AMAZING VALUE*

**NEW BRANDED FULL SPECIFICATION DEVICES**

**Integrated Circuits complete with data:**
GE PA234 1W Audio Amplifier **17/6**
GE PA237 2W Audio Amplifier **32/6**
Plessey SL402A Preamp. and 2W Amp. (equiv. IC10) with instructions **40/–**
GE D40C1 4W Darlington Amplifier. Very High Gain 10,000 min. **13/6**
MEL 11 Photo Darlington Amp. **9/6**
Connectors for DIL I.C.s **7/–**

**High Quality low cost transistors:**

| | | | |
|---|---|---|---|
| GE 2N5172 | 1/9 | MUL BFX86 | 6/– |
| ME 0412 | 3/9 | MUL BD124 | 12/– |
| TI 2N4059 | 3/6 | S 2N3055 | 14/– |

**Triacs for full wave power control:**
RCA 40669 8A 400V **24/–**
RCA 40583 Trigger Diode **5/3**

**Plastic Rectifiers for power supplies:**
ITT 1 Amp. 4000 series

| | |
|---|---|
| IN4001, 50V 1/9 | IN4004, 400V 2/5 |
| IN4002, 100V 2/– | IN4005, 600V 2/9 |
| IN4003, 200V 2/2 | IN4006, 800V 3/5 |
| IN4007, 1000V 4/– | |

IN4820 1·5A 400V Si Rectifier **2/6**
W005 1A 50V full wave bridge Si **7/6**
PD40 2A 400V full wave bridge Si **12/6**

**JEF ELECTRONICS (P.E.8)**
**York House, 12 York Drive, Grappenhall**
**Warrington, Lancs.** Mail Order Only
C.W.O. P. & P. 1/- per order. Overseas 7/6.
Money back if not satisfied.

---

**TOP PRICES PAID**

for new valves and components

Write:

**KENSINGTON SUPPLIES**
**(B) 367 Kensington Street**
**Bradford 8, Yorks.**

---

9V 3A Transformers, suitable P.E. Model Train Controller (June). New, impregnated, **19/-** including postage. F. C. STAIRS, 97a High Street, Edgware, Middx.

## 240 VOLT ELECTRICITY ANYWHERE



**BEST EVER 200/240 VOLT "MAINS" SUPPLY FROM 12 VOLT CAR BATTERY**

Exclusive World Scoop Purchase. The fabulous **Mk. 12D American Heavy Duty Dynamotor Unit** with a **Massive** 220 watt output and giving the most **Brilliant** 200/240 volt performance of all time. Marvellous for **Television, Drills, Power Tools, Mains Lighting, AC Fluorescent Lighting** and all 200/240 volt Universal AC/DC mains equipment. Made at tremendous cost for U.S.A. Govt. by Delco-Remy. This magnificent machine is unobtainable elsewhere. **Brand New** and **Fully Tested. Only £5.9.6** + 10/6 postage. C.O.D. with pleasure, refund guarantee. Please send S.A.E. for illustrated details.

**Dept. PE, SCIENTIFIC PRODUCTS**
**Rear Derby Road, North Promenade**
**Blackpool, Lancashire**

## NEW RANGE U.H.F. TV AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.

**Loft Mounting Arrays.** 7 element, **40/-**; 11 element, **47/6**; 14 element, **55/-**; 18 element, **62/6. Wall Mounting** with **Cranked Arm,** 7 element, **60/-**; 11 element, **67/6**; 14 element, **75/-**; 18 element, **82/6. Mast Mounting** with 2in. clamp. 7 element, **42/6**; 11 element, **55/-**; 14 element, **62/-**; 18 element, **70/-. Chimney Mounting Arrays, Complete,** 7 element, **72/6**; 11 element, **80/-**; 14 element, **87/6**; 18 element, **95/-.** Complete assembly instructions with every unit. **Low Loss Cable, 1/6** yd. **U.H.F. Pre-amps** from **75/-.** State clearly channel number required on all orders.

### BBC · ITV AERIALS



**BBC (Band 1).** Loft, **25/-.** External S/D, **30/-.** "H", **£2.15.0.**
**ITV (Band 3).** 3 element loft array, **30/-.** 5 element, **40/-.** 7 element, **50/-.** Wall mounting, 3 element, **50/-.** 5 element, **55/-.**
**Combined BBC/ITV.** Loft 1 + 3, **40/-**; 1 + 5, **50/-**; 1 + 7, **60/-**; Wall mounting 1 + 3, **60/-**; 1 + 5, **70/-**; Chimney 1 + 3, **70/-**; 1 + 5, **80/-.**
**VHF** transistor pre-amps, **75/-.**

**COMBINED BBC1—ITV—BBC2 AERIALS**
1 + 3 + 9, **70/-.** 1 + 5 + 9, **80/-.** 1 + 5 + 14, **90/-.** 1 + 7 + 14, **100/-.** Loft mounting only.

**F.M. (Band 2).** Loft S.D. **17.6.** "H", **35/-.** 3 element, **57.6.** External units available. Co-ax. cable, **8d.** yd. Co-ax. plugs, **1/6.** Outlet boxes, **5/-.** Diplexer Crossover Boxes, **17/6.** C.W.O. or C.O.D. P. & P. 6/6. Send 6d. stamps for illustrated lists.

*CALLERS WELCOME*

OPEN ALL DAY SATURDAY

**K.V.A. ELECTRONICS (Dept. P.E.)**
**40-41 Monarch Parade**
**London Road, Mitcham, Surrey**
**01-648 4884**

## 4-STATION INTERCOM




**£7.5.0**

Solve your communication problems with this **4-Station Transistor Intercom** system (**1 master** and **3 Subs**), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from **Master** to **Subs** and **Subs** to **Master.** Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 7/6.

### MAINS INTERCOM

**No batteries—no wires.** Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. **Price £11.19.6.** P. & P. 8/6 extra.

## INTERCOM/BABY ALARM




**3 Gns.**

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 2/6. P. & P. 4/6.




**59/6**

Why not boost business efficiency with this incredible De-Luxe **Telephone Amplifier.** Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Battery 2/6 extra. P. & P. 3/6. Full price refunded if not satisfied in 7 days.

**WEST LONDON DIRECT SUPPLIES (PE/3)**
**169 KENSINGTON HIGH STREET, LONDON, W.8**

R.C.A. 40669 8A. 400 p.i.v. Plastic Triac **21/-** only.

BC184L **2/6**; BC169C **3/-**; 2N4058 **3/6**; 2N4302 **11/-.**

Carbon Film Resistors E12 Series 10Ω–1MΩ 5% ½W. Your Selection 1–12, **3d** each 13 and over, **2·5d** each.

Dulci 207 Stereo Amp. 7+7W o.p. **£19.10s** few only.

MAIL ORDER ONLY. P. & P. 1/-.

## SPECTRUM AUDIO

**45 SELBORNE ROAD, LONDON, N.22**

## AUDIO EFFECTS

**5 SHAW LANE, HALIFAX, YORKS.**

Buy with confidence and obtain the right results. Refunds without question if any of our products fail to give 100% satisfaction.

**AMATEUR BANDS ALL TRANSISTOR SUPERHET RECEIVER KIT.** No fuss, no drilling. Just fit the components on our printed circuit. Slow Motion tuning. Simple IF alignment. Perspex front panel. Push pull AF amp drives your 8 –15 ohm speaker. Amp can be used separately. Designed to accept a BFO signal. Uses Denco plug in coils
2T. 0·5 to 1·54 Mhz 3T. 1·67 to 5·3 Mhz
4T. 5·0 to 15 Mhz 5T. 10·5 to 31·5 Mhz
Range 3T normally supplied with kit. Uses 9 Volt battery. Easy step by step instructions. Complete Kit. **£8.19.6** plus 5/6 P.P. & Ins. Extra ranges **12/-** per range.

**POWER CONTROLLER.** Power at your finger tips. Not merely half wave control but full wave. A single variable control gives zero to full power. Uses latest 15 amp 3kW triac and special triggering device. Ideal for all types of lighting, fires, motors, drills, etc. Complete with box, power socket, cables, etc. In kit form with easy to follow instructions **£6.9.6.** Ready built **£9.4.6** plus 5/6 P. P. & Ins.

**REVERBERATION AMPLIFIER.** Self contained transistorised, battery operated. An entirely different approach to sound reproduction. Normally, sound reproduction from a single source, has a flat one dimensional effect. With this unit, proper sound delay through reverberation, tones, are created with a truly third dimension for concert hall originality. Two controls adjust volume and reverberation. Simply plug microphone, guitar, etc., in, and the output into your amplifier. Supplied in a beautiful walnut cabinet 7¼in × 3in × 4¼in. **£10.4.0.** P. P. & Ins. 6/-.

**VOX SWITCH.** This sound operated switch is ideal for mobile TX work, tape recorder switching, etc. You speak, it switches. High and medium imp. inputs. AF take off point. Drives your 12 volt relay. In kit form with full instructions **42/6.** Ready built, tested and guaranteed. **69/6** post paid.

**METRONOME UNIT.** Variable beat. Listen while you play and keep in time. Easily built, pocket size with personal mini earphone. In kit form **27/6,** post paid. Ready built in an attractive polythene case, **37/6** post paid.

**MORSE OSCILLATOR.** PC board, transistors, high stab. components, battery carrier, ear piece. Adjustable tone. Just attach your key. Drives phones or speaker. In kit form **17/6** post paid. Ready built in similar case as above **27/6** post paid.

**STRAIGHT FROM THE PRESS.** Latest Mullard manual: Audio Amps, FM tuners, Stereo decoder, Receiver circuits, Hi Fi, Tape, etc., etc. **32/6** post paid.

**TEXAS TRANSISTORS.** Complementary symmetry. Driver, NPN, PNP output. The set of three **ONLY 6/6** post paid.

## BATTERY ELIMINATORS

The ideal way of running your TRANSISTOR RADIO, RECORD PLAYER, TAPE RECORDER, AMPLIFIER, etc. Types available: 6v, 9v, 12v, 18v (single output) 39/6 each. P. & P. 2/9. 9v + 9v; 6v + 6v; or 4½v + 4½v (two separate outputs) 42/6 each. P. & P. 2/9. Please state output required. All the above units are completely isolated from mains by double wound transformer ensuring 100% safety.

**R.C.S. PRODUCTS (RADIO) LTD.**
**(Dept. P.E.), 31 Oliver Road, London, E.17**

## YUKAN SELF-SPRAY

*SO PROFESSIONAL THE YUKAN AEROSOL WAY-*

*Get these NOW! air drying GREY HAMMER OR BLACK WRINKLE (CRACKLE) finishes*

Yukan Aerosol spraykit contains 16 ozs. fine quality, durable easy instant spray. No stove baking required. Hammers available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 15/11 at our counter or 16/11, carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Matt finish (12 ozs. self-spray cans only) 13/11 carriage paid.
SPECIAL OFFER: 1 can plus optional transferable snap-on trigger handle (value 5/-) for 18/11, carriage paid. Choice of 13 self-spray plain colours and primer (Motor car quality) also available.

*Other Yukan Air Drying Aerosols, 16 ozs. at 16/11 carr. paid include: Zinc Chromate Clear Lacquer Metallics: Grey, Blue, Bronze and Gold.*

Please enclose cheque or crossed P.O. for total amount direct to:

**DEPT: K/6 YUKAN, 307a, EDGWARE ROAD, LONDON, W.2.**

We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations—We can supply you too.

Open all day Saturday. Closed Thursday afternoons.

## BUILD YOUR CIRCUITS on VEROBOARD



—the Universal Wiring Board—
obtainable from your local Retailer

*Trade enquiries to:*
**NORMAN ROSE (ELECTRICAL) LTD.**
**8 St. Chad's Place, Gray's Inn Road, London, W.C.1**

*Technical enquiries to:*
**VERO ELECTRONICS LTD.**
**Industrial Estate, Chandler's Ford, Hants**

# R.S.T. VALVE MAIL ORDER CO.

**BLACKWOOD HALL, WELLFIELD RD., S.W.16**

***SPECIAL EXPRESS MAIL ORDER SERVICE***

| | | | | | | | | | |
|---|---|---|---|---|---|---|---|---|---|
| 1N21 | 3/6 | 2S308 | 9/– | BCY54 | 7/3 | GET116 | 6/– | OC20 | 20/– |
| 1N21B | 5/– | 2S501 | 5/– | BCY60 | 19/– | GET118 | 4/– | OC22 | 8/– |
| 1N23 | 4/– | 2S703 | 12/6 | BCY70 | 6/– | GET119 | 4/– | OC23 | 8/6 |
| 1N85 | 17/6 | 3N143 | 19/– | BCZ11 | 6/– | GET120 | 6/6 | OC24 | 9/– |
| 1N253 | 10/– | A13759 | 4/– | BD121 | 19/– | GET587 | 8/6 | OC25 | 7/6 |
| 1N256 | 10/– | AA129 | 5/– | BD123 | 22/6 | GET872B | 6/– | OC26 | 6/– |
| 1N645 | 5/– | AAZ12 | 3/6 | BD124 | 12/– | GET873 | 3/– | OC28 | 12/6 |
| 1N725A | 4/– | AAZ13 | 3/– | BDY11 | 5/6 | GET875 | 6/– | OC29 | 14/6 |
| 1N4007 | 4/6 | AC107 | 5/6 | BF115 | 5/6 | GET880 | 8/9 | OC30 | 5/– |
| 18021 | 4/– | AC126 | 4/– | BF117 | 10/– | GET882 | 6/– | OC35 | 6/3 |
| 18113 | 3/– | AC127 | 5/– | BF167 | 6/6 | GET885 | 10/– | OC36 | 8/6 |
| 18130 | 2/6 | AC128 | 4/6 | BF173 | 7/3 | GEX35 | 4/6 | OC38 | 10/3 |
| 18131 | 2/6 | AC129 | 7/6 | BF181 | 6/– | GEX44 | 1/6 | OC41 | 4/6 |
| 2G220 | 12/6 | AC187 | 11/– | BF184 | 7/6 | GEX941 | 4/– | OC42 | 5/– |
| 2G240 | 3/6 | AC188 | 11/– | BF185 | 6/– | GJ3M | 7/6 | OC43 | 9/– |
| 2G301 | 3/6 | ACY17 | 4/6 | BF194 | 6/3 | GJ4M | 7/6 | OC44 | 4/– |
| 2G306 | 8/– | ACY18 | 4/– | BF195 | 5/6 | GJ5M | 7/6 | OC45 | 3/3 |
| 2G371B | 4/– | ACY19 | 5/– | BF196 | 5/6 | HG1005 | 10/– | OC46 | 3/– |
| 2G381A | 4/6 | ACY20 | 5/– | BF197 | 5/6 | MAT100 | 6/– | OC58 | 12/6 |
| 2G403 | 10/– | ACY21 | 4/6 | BFX12 | 5/6 | MAT101 | 8/3 | OC59 | 17/– |
| 2G414 | 6/– | ACY22 | 4/– | BFX13 | 5/6 | MAT120 | 5/9 | OC70 | 3/6 |
| 2G417 | 6/– | ACY27 | 5/– | BFX29 | 12/– | MAT121 | 6/– | OC71 | 3/– |
| 2N214 | 8/6 | ACY28 | 4/– | BFX30 | 8/6 | MJ420 | 22/– | OC72 | 4/– |
| 2N404 | 6/– | ACY39 | 12/6 | BFX35 | 19/6 | MJ421 | 22/– | OC73 | 7/3 |
| 2N247 | 9/6 | ACY40 | 4/– | BFX43 | 8/3 | NKT128 | 6/– | OC74 | 4/6 |
| 2N697 | 4/– | ACY41 | 5/– | BFX44 | 8/3 | NKT129 | 6/– | OC75 | 4/6 |
| 2N698 | 4/6 | ACY44 | 7/6 | BFX68 | 13/– | NKT135 | 5/3 | OC76 | 3/– |
| 2N706 | 3/– | AD140 | 8/– | BFX68A | 13/6 | NKT210 | 6/– | OC77 | 8/– |
| 2N706A | 3/6 | AD149 | 12/– | BFX85 | 10/– | NKT211 | 6/6 | OC78 | 3/– |
| 2N708 | 4/– | AD150 | 15/– | BFX86 | 9/6 | NKT212 | 5/4 | OC78D | 3/3 |
| 2N709 | 12/6 | AD161 | 7/6 | BFX87 | 9/6 | NKT213 | 6/4 | OC79 | 5/– |
| 2N711 | 7/6 | AD162 | 7/– | BFX88 | 5/– | NKT214 | 4/4 | OC81 | 4/– |
| 2N987 | 10/6 | AF106 | 10/6 | BFY20 | 12/– | NKT215 | 4/6 | OC81D | 3/– |
| 2N1090 | 6/6 | AF114 | 5/– | BFY21 | 8/6 | NKT216 | 6/4 | OC81DM | 3/– |
| 2N1091 | 6/6 | AF115 | 5/9 | BFY24 | 9/– | NKT217 | 8/4 | OC81M | 5/– |
| 2N1131 | 8/6 | AF116 | 4/6 | BFY41 | 9/6 | NKT218 | 22/6 | OC82 | 3/– |
| 2N1132 | 7/6 | AF117 | 4/6 | BFY43 | 12/6 | NKT219 | 6/6 | OC82D | 3/– |
| 2N1302 | 4/– | AF118 | 12/– | BFY50 | 5/– | NKT221 | 5/6 | OC83 | 4/6 |
| 2N1303 | 4/3 | AF119 | 4/– | BFY51 | 6/– | NKT223 | 6/6 | OC84 | 4/9 |
| 2N1304 | 4/9 | AF124 | 5/– | BFY53 | 5/6 | NKT224 | 4/9 | OC114 | 7/6 |
| 2N1305 | 5/– | AF125 | 5/– | BFY77 | 12/– | NKT225 | 4/9 | OC122 | 12/6 |
| 2N1306 | 5/– | AF126 | 5/– | BFY90 | 12/6 | NKT226 | 5/6 | OC123 | 4/4 |
| 2N1307 | 5/– | AF127 | 4/6 | BSX27 | 10/– | NKT227 | 5/6 | OC139 | 7/6 |
| 2N1308 | 6/– | AF139 | 7/6 | BSX60 | 18/6 | NKT229 | 5/9 | OC140 | 6/6 |
| 2N1309 | 6/– | AF178 | 12/6 | BSX61 | 12/– | NKT237 | 7/9 | OC141 | 12/3 |
| 2N1420 | 7/3 | AF179 | 11/– | BSY26 | 3/6 | NKT238 | 5/9 | OC169 | 6/– |
| 2N1507 | 5/6 | AF180 | 12/– | BSY27 | 4/– | NKT240 | 6/6 | OC170 | 5/6 |
| 2N1526 | 7/6 | AF181 | 8/– | BSY51 | 10/– | NKT241 | 6/6 | OC171 | 6/– |
| 2N1909 | 45/– | AF186 | 11/– | BSY78 | 9/3 | NKT251 | 4/9 | OC172 | 7/– |
| 2N2147 | 16/6 | AFY19 | 22/6 | BSY79 | 9/3 | NKT261 | 4/6 | OC200 | 5/6 |
| 2N2148 | 12/– | AFZ11 | 6/– | BSY82 | 10/– | NKT274 | 4/9 | OC201 | 8/6 |
| 2N2160 | 14/– | AFZ12 | 6/6 | BSY83 | 11/– | NKT275 | 5/– | OC202 | 8/6 |
| 2N2193 | 5/6 | ASY26 | 5/6 | BSY84 | 12/– | NKT277 | 4/9 | OC203 | 6/– |
| 2N2287 | 20/6 | ASY27 | 7/6 | BSY95A | 3/6 | NKT403 | 9/9 | OC204 | 5/6 |
| 2N2297 | 6/– | ASY28 | 5/3 | BY100 | 4/6 | NKT404 | 12/6 | OC205 | 9/– |
| 2N2369A | 5/– | ASY29 | 5/– | BY213 | 5/– | NKT678 | 6/– | OC206 | 14/6 |
| 2N2410 | 10/6 | ASY36 | 5/6 | BYZ11 | 5/– | NKT713 | 7/6 | OC207 | 7/6 |
| 2N2411 | 6/6 | ASY50 | 5/– | BYZ11N | 7/6 | NKT773 | 6/– | OC450 | 6/– |
| 2N2412 | 6/6 | ASY51 | 7/6 | BYZ12 | 6/– | NKT777 | 7/6 | OC470 | 6/– |
| 2N2483 | 5/6 | ASY53 | 4/9 | BYZ14 | 27/6 | NKT80113 | 20/– | OCP71 | 20/– |
| 2N2484 | 7/6 | ASY54 | 4/9 | BYZ15 | 35/– | O78B | 7/6 | PS144 | 4/– |
| 2N2646 | 11/6 | ASY55 | 6/– | BYZ16 | 17/6 | OA5 | 3/6 | S19T | 6/– |
| 2N2696 | 6/3 | ASY62 | 5/– | C111 | 13/– | OA10 | 3/– | SAC40 | 5/– |
| 2N2865 | 12/– | ASY86 | 6/6 | C20A | 12/6 | OA47 | 2/– | SFT308 | 7/6 |
| 2N2904 | 7/6 | ASZ17 | 13/6 | CRS1/05 | 5/– | OA70 | 1/6 | SJ052F | 7/6 |
| 2N2904A | 8/– | ASZ20 | 7/3 | CS4B | 37/6 | OA71 | 2/– | ST222A | 5/– |
| 2N2906 | 8/– | ASZ21 | 7/6 | CS10B | 67/6 | OA73 | 2/– | ST7231 | 12/6 |
| 2N2907 | 7/6 | ASZ23 | 19/6 | CV101 | 5/– | OA74 | 4/– | SX68 | 4/– |
| 2N2926 | 3/– | AUY10 | 19/6 | CV253 | 20/– | OA79 | 1/9 | SX68UH | 4/6 |
| 2N2924 | 4/6 | BC107 | 3/6 | CV2154 | 32/6 | OA81 | 1/6 | SX631 | 7/6 |
| 2N3014 | 7/6 | BC108 | 3/6 | CV2155 | 32/6 | OA85 | 1/6 | SX631UC | 10/– |
| 2N3054 | 11/– | BC109 | 3/6 | CV2279 | 10/6 | OA86 | 4/– | SX680T | 4/– |
| 2N3055 | 14/6 | BC113 | 6/3 | CV2923 | 4/6 | OA90 | 1/6 | SX634WK | 8/– |
| 2N3705 | 4/– | BC115 | 6/6 | CV4073 | 3/– | OA91 | 1/6 | SX753 | 15/– |
| 2N3706 | 4/6 | BC116 | 11/6 | CV4074 | 3/6 | OA95 | 1/6 | SZ33C | 12/– |
| 2N3707 | 4/– | BC118 | 6/6 | CV7108 | 80/– | OA200 | 2/– | V15/10P | 15/– |
| 2N3708 | 4/– | BC121 | 4/– | CV7109 | 75/– | OA202 | 2/– | V15/30P | 15/– |
| 2N3709 | 4/– | BC122 | 4/– | CV7183 | 30/– | OA210 | 6/6 | V30/201P | 9/6 |
| 2N3710 | 4/– | BC125 | 13/6 | CV7312 | 10/– | OA211 | 10/– | XA122 | 6/– |
| 2N3819 | 8/– | BC126 | 13/– | CV7324 | 10/– | OAZ200 | 11/– | XA124 | 4/– |
| 2N3820 | 20/– | BC140 | 11/– | CV7341 | 6/– | OAZ201 | 10/– | XA142 | 5/– |
| 2N3823 | 17/– | BC145 | 15/– | CV7347 | 4/– | OAZ202 | 7/6 | XA143 | 5/– |
| 2N3900 | 10/6 | BC147 | 4/9 | CV7361 | 12/6 | OAZ203 | 8/– | XA152 | 5/– |
| 2N3900A | 11/– | BC148 | 4/6 | D246 | 7/6 | OAZ204 | 8/– | XA162 | 8/6 |
| 2N5027 | 10/6 | BC149 | 5/– | DD006 | 6/6 | OAZ207 | 10/– | XB101 | 8/6 |
| 2N5028 | 11/6 | BC157 | 4/– | DD007 | 8/– | OAZ208 | 6/6 | XB121 | 8/6 |
| 2N5307 | 7/6 | BC160 | 12/6 | DD008 | 7/6 | OAZ210 | 6/6 | XK505 | 5/– |
| 2N5308 | 7/6 | BCY31 | 6/– | GD3 | 6/6 | OAZ222 | 9/6 | XK518 | 6/– |
| 2N5309 | 11/– | BCY32 | 7/6 | GD4 | 7/– | OAZ224 | 9/6 | Z2A82CR | 5/– |
| 28005 | 14/– | BCY33 | 5/– | GD5 | 6/6 | OAZ241 | 7/6 | ZR24 | 12/6 |
| 28013 | 15/– | BCY34 | 5/– | GD6 | 6/– | OAZ242 | 4/6 | ZS32A | 6/– |
| 28013A | 16/6 | BCY38 | 5/6 | GD8 | 5/– | OAZ246 | 4/6 | ZT21 | 6/– |
| 28301 | 12/6 | BCY39 | 7/– | GET102 | 5/– | OAZ290 | 9/– | ZT43 | 5/– |
| 28304 | 9/– | BCY40 | 7/6 | GET113 | 5/– | OC16 | 15/– | | |
| | | BCY42 | 3/– | GET114 | 4/– | OC16T | 16/6 | | |
| | | | | | | OC19 | 8/6 | | |

**TRANSISTORS (POSTAGE, PACKING & INSURANCE) 1/3 PER ORDER**

## SEND S.A.E. FOR LIST OF 3,000 TYPES— VALVES, TUBES AND TRANSISTORS

| TERMS | OPEN DAILY TO CALLERS |
|---|---|
| C.W.O. | Mon.–Sat. 9 a.m.–5.30 p.m. Closed Sat. 1.30 p.m.–2.30 p.m. |
| no C.O.D. | Tel. 01-769 0199/1649 |




# newbury SOUND EQUIPMENT
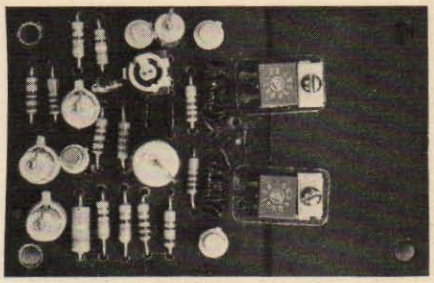
## 20 Watts RMS for 86/-

+2/6 p.p. FREE ON TWO MODULES

**THE 6T2 POWER AMPLIFIER** WITH INTEGRAL PRE-AMPLIFIER USES THE LATEST R.C.A. PLASTIC OUTPUT TRANSISTORS—ENABLING OUTPUTS OF 25 WATTS MUSIC TO BE OBTAINED FROM A 3½" × 2½" (9·5cm × 6·6cm) CIRCUIT BOARD—RECOMMENDED FOR ECONOMY HI-FI, P.A. APPLICATION OR GUITAR AMPLIFIERS.



- 10-30,000 Hz @ 10 Watts ± 1dB.
- Distortion 0.25% typical at 15 Watts.
- Power gain 80dB.
- 35 Volt operation.
- Load Impedances 3-15 ohms.
- Six Transistor, two Diodes.
- Top quality components throughout.

**POWER AMPLIFIER 3T1 19/6**
50 0mW for 40mV input 35-45,000 Hz
**ORGAN MODULE 3TN 17/6**
Will act as Oscillator or Divider up to 6,000 Hz
**MULTI-PURPOSE PRE-AMPLIFIER 19/6**
9-24V gain variable to 40 dB
**DUAL VOLTAGE PRE-AMPLIFIER 17/6**
9-24V, 200-500V 26 dB gain.
**TACHOMETER MODULE** (any car at all) **18/9**

POST & PACKAGE 1/-


ALL THESE MODULES ARE ENCAPSULATED AND WILL MOUNT ON VEROBOARD

**ALL NEWBURY MODULES ARE DESIGNED TO BE INTER-CONNECTED WITH EASE**

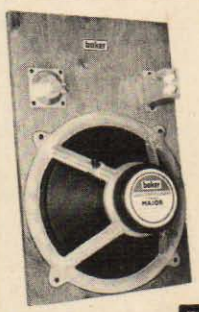**NEWBURY SOUND EQUIPMENT, 21 LANCASTER CT. LANCASTER AVENUE, S.E.27**

**We welcome** your application problems, but **please send an S.A.E.** with your enquiry.





## BAKER 12in. MAJOR £9

The remarkable quality and performance of the "Major" makes possible truly brilliant and rich sound from a single loudspeaker. It recreates the entire musical spectrum from 30 to 14,500 c.p.s. The unit consists of the latest double cone, woofer and tweeter cone together with a special **Baker CERAMIC** magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 45 c.p.s. For Hi-Fi or P.A. Rated 20 watts. Voice coils available 3 or 8 or 15 ohms.

**Major Module** 30-17,000 cps with tweeter, crossover, baffle 19 × 12½in. and instructions. **£11.10.0**

Send 4d Stamp for Further Details

**Baker Reproducers Ltd**

**Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684-1665**



## Build the 'COLT' in only 15 hours

**By using our factory-made, fully tested units**

- ★ Suited to all kinds of music
- ★ Internal 10 watt amplifier and loudspeaker
- ★ Uses latest integrated circuits
- ★ 49-notes, 8 stops, glide, vibrato, etc.
- ★ All units available separately



Price **£82.10.0** complete
(terms available)
Other models out shortly

## Harmonics

**(Bromley) Ltd.**

**Clarion Works, Napier Road, Bromley, Kent. 01-460 2122**

# VALUABLE NEW HANDBOOK

# FREE TO AMBITIOUS ENGINEERS

## Have you had *your* copy of "Engineering Opportunities"?

The new edition of **"ENGINEERING OPPORTUNITIES"** is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new **"ENGINEERING OPPORTUNITIES"** should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

### On 'SATISFACTION OR REFUND OF FEE' terms

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

### WHICH OF THESE IS YOUR PET SUBJECT?

**ELECTRONIC ENG.**
*Advanced Electronic Eng.— Gen. Electronic Eng.— Applied Electronics — Practical Electronics — Radar Tech.— Frequency Modulation — Transistors.*

**ELECTRICAL ENG.**
*Advanced Electrical Eng.— General Electrical Eng. — Installations — Draughtsmanship — Illuminating Eng. — Refrigeration — Elem. Elec. Science — Elec. Supply — Mining Elec. Eng.*

**CIVIL ENG.**
*Advanced Civil Eng.— General Civil Eng. — Municipal Eng. — Structural Eng. —Sanitary Eng.—Road Eng. — Hydraulics — Mining — Water Supply — Petrol Tech.*

**RADIO & T.V. ENG.**
*Advanced Radio — General Radio—Radio & TV Servicing — TV Engineering — Telecommunications — Sound Recording — Automation — Practical Radio — Radio Amateurs' Examination.*

**MECHANICAL ENG.**
*Advanced Mechanical Eng.— Gen. Mech. Eng.—Maintenance Eng. — Diesel Eng. — Press Tool Design — Sheet Metal Work — Welding — Eng. Pattern Making — Inspection - Draughtsmanship — Metallurgy — Production Eng.*

**AUTOMOBILE ENG.**
*Advanced Automobile Eng.— General Auto. Eng. — Auto. Maintenance — Repair — Auto. Diesel Maintenance — Auto. Electrical Equipment— Garage Management.*

**WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS INCLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRUMENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.**

**Which qualification would increase your earning power?** A.M.I.E.R.E., B.Sc.(Eng.), A.M.S.E., A.M.I.P.E., A.M.I.M.I., A.R.I.B.A., A.I.O.B., A.M.I.Ex., A.R.I.C.S., M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., C.ENG., CITY & GUILDS, GEN. CERT. OF EDUCATION, ETC.

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**
316A, ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

### THIS BOOK TELLS YOU

- ★ *HOW to get a better paid, more interesting job.*
- ★ *HOW to qualify for rapid promotion.*
- ★ *HOW to put some letters after your name and become a key man . . . quickly and easily.*
- ★ *HOW to benefit from our free Advisory and Appointments Depts.*
- ★ *HOW you can take advantage of the chances you are now missing.*
- ★ *HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.*

*164 PAGES OF EXPERT CAREER - GUIDANCE*

**PRACTICAL EQUIPMENT**

Basic Practical and Theoretic Courses for beginners in Electronics, Radio, T.V., Etc., A.M.I.E.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Electronics Electronics Engineering Practical Radio Radio & Television Servicing Automation

**INCLUDING TOOLS**

*The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.*

**B.I.E.T.**




You are bound to benefit from reading **"ENGINEERING OPPORTUNITIES"** — send for your copy *now*— FREE and without obligation.

**POST COUPON NOW!**

TO B.I.E.T. 316A, ALDERMASTON COURT, ALDERMASTON, BERKSHIRE.

*Please send me a FREE copy of "ENGINEERING OPPORTUNITIES." I am interested in (state subject, exam., or career).*

.....

**NAME** .....

**ADDRESS** .....

.....

.....

WRITE IF YOU PREFER NOT TO CUT THIS PAGE

**THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD**



Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by The Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/sia) Ltd. : South Africa—Central News Agency Ltd. : Rhodesia and Zambia—Kingstons Ltd. : East Africa—Stationery and Office Supplies Ltd. Subscription Rate (including postage) : For one year to any part of the world £2 5s. 0d.

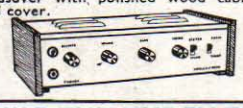

Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

# HENRY'S RADIO LTD. ENGLAND'S LEADING COMPONENT AND EQUIPMENT CENTRES

## COMPLETE STEREO SYSTEM FOR £39.10.0

HENELEC 5-5 STEREO AMPLIFIER. Inputs for ceramic cartridge, AUX/Tuner. Output for 8 to 15 ohms speakers. Silver with black and wood finish. British made. Size 12¾in × 3¼in × 6¼in. Fitted headphone socket.

Complete system comprises 5-5 amplifier, Garrard 3000 or model 50 with 9TAHC diamond cartridge. Pair E.M.I. 10W speakers, twin tweeters and crossover with polished wood cabinets 18in × 11in × 7in. Also plinth and cover.



- Complete stereo system (Rec. Price £50), **£39.10.0**, p.p. 20/-.
- Amplifier only, **£13.19.6**, p.p. 7/6.
- TE1035 recommended stereo phones, 39/6.

## BUILD THIS VHF FM TUNER

5 MULLARD TRANSISTORS 300kc/s BANDWIDTH. PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it —VHF FM gives the REAL sound. All parts sold separately.



PARTS TOTAL COST **£6.19.6.** ASK FOR BROCHURE No. 3. P.P. 3/6.

DECODER **£5.19.6.** (FOR STEREO) P.P. 3/-.

## BUILD YOURSELF A QUALITY RADIO

New printed circuit design with full power output. Fully tuneable on both MW/LW bands. 7 Mullard transistors. Fitted 5in speaker. Room filling power. Easy to build with terrific results. Two colour leathercloth cabinet with silvered front. All local and continental stations. Complete detailed instructions.



Total cost **£6.19.6.** p.p. 6/6. Ask for Leaflet No. 1.

## SINCLAIR EQUIPMENT

## SPECIAL OFFER

Z30, 75/- each; stereo 60, **£8.10.0**; PZ5, 79/6; PZ6, **£6.19.6**; Z50, **£5.9.6**; PZ8, **£5.19.6**. Two of Z30, stereo 60, PZ5 (usually £23.10.0) **£19,** or with PZ6 in place of PZ5, **£21.**

Complete range of amplifiers and preamplifiers in stock. All detailed in catalogue above.

## TEST EQUIPMENT FOR YOUR HOME



AF105 50kV multimeter (Illus.), price **£8.10.0**, p.p. 3/6; leather case, **28/6.**

200H 20k/V multimeter, price **£3.17.6**, p.p. 3/-; case, **12/6.**

TE20D R.F. Generator (Illus.), price **£15**, p.p. 7/6.

TE22D Matching Audio Generator, price **£17**, p.p. 7/6.

TE65 Valve Voltmeter, price **£17.10.0**, p.p. 7/6.

Full details and complete range in catalogue.





## SLIM POCKET TEST GEAR

- SIGNAL INJECTOR 35/-, p.p. 1/6
- SIGNAL TRACER **29/6**, p.p. 1/6

**NEW** World's lowest cost Stereo Magnetic Cartridge. O/P ·7mV. 20c/s-20kc/s. Diamond Stylus—Recommended. **79/6** p.p. 2/6

## HI-FI equipment to suit EVERY POCKET



**FREE**—STOCK LIST NO. 16/17 ON REQUEST

Choose from 100 complete stereo systems—complete range of individual units also in stock. Demonstrations all day.

**100 STEREO SYSTEMS**

**LOW CASH AND CREDIT/HP PRICES**

(Credit terms from £30 purchase—callers only)



## HENRY'S LATEST CATALOGUE

NEW PRINT—NOW 350 PAGES

★ **COMPONENTS, TESTGEAR**

★ **EQUIPMENT, MODULES**

★ **SPECIAL OFFERS, ETC.**

***EVERYTHING FOR THE CONSTRUCTOR***

Complete with 10/- value discount vouchers for use with purchase. Price **7/6**, p.p. 2/-.


WHY NOT SEND AWAY TODAY?




## *NEW!* 25W and 50W RMS SILICON AMPLIFIERS

LOOK AT THE SPECIFICATIONS:

- 0·3% distortion at full power.
- —1dB 11c/s to 40kc/s at full power.
- Response —1dB 11c/s–100kc/s.

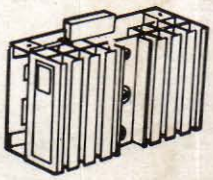

**PA25**—10 silicon transistors; differential input; 25W r.m.s. into 8 ohms, 400mV input. Size only 5in × 3in × 2in. Four-hole fixing. Supplied with edge connector and harness.

**PA50**—12 transistor version, 50W r.m.s. into 3–4 ohms.

MU442—power supply for one or two PA25 or one PA50.

● PA25, **£7.10.0.** ● PA50, **£9.10.0.** ● MU442, **£6.**

## *NEW!* STEREO FET SELF POWERED PREAMPLIFIER

MODEL FET 154 STEREO

Inputs for pickup (mag. etc). Tuner/Aux. Tape in and out. Response 20c/s to 30kc/s. Output adjustable up to 1 volt. Mains operated stabilised supply. Slim design. Size 12″×5¼″×1¾″. Price **£16.10.0.**

NO SOLDERING—JUST PLUG CONNECTORS

## YOU CAN SAVE 25% brand new GARRARD (post 7/6).


SP25 Mk. II **£11.9.6**; AP75, **£16.19.6**; SL65B **£14.19.6**; SL72B, **£25**; A70 Mk. II, **£11.19.6.** SPECIAL—Above with sonotone 9TAHC diam., add **£2**; with magnetic, add **70/–**; with Goldring G800, add **£8.10.0.**



**Also**—Fitted with 9TAHC diamond, Model 50, **£8.10.0**; 3000LM, **£9.15.0.** Plinths/covers; Standard, **99/6**, p.p. 4/6; Deluxe, **£8.10.0**, p.p. 6/–; SL72B type, **£8.10.0**, p.p. 6/– (Not for A70).
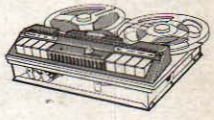
## SCOOP— New ¼″ TRACK TAPE DECKS

British made 3-speed mains-operated tape machine. Fitted Marriott XRPS17 and XES11 ¼in track heads. Piano key operation. Designed for the home constructor. Operates with up to 7in spools vertically or horizontally. Size 13in × 10in × 5¼in.



**PRICE £13.19.6,** p.p. 10/6.

## ELECTRONIC ORGANS


★ MODERN ALL BRITISH TRANSISTORISED DESIGNS AVAILABLE AS KITS OR READY BUILT

★ TEAK VENEERED CABINETS FOR ALL MODELS

★ 49 NOTE, 61 NOTE SINGLE MANUAL DESIGNS ALSO TWO 49 MANUAL NOTE

★ KITS AVAILABLE IN SECTIONS AS REQUIRED

★ HP and CREDIT SALE FACILITIES.

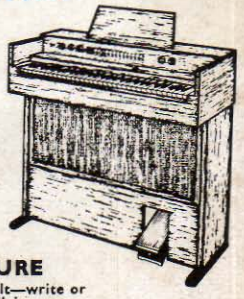

★ **FREE 16-PAGE BROCHURE**

Covering organs in kit form and ready built—write or phone to ORGAN DEPT. Ask for Peter Elvins.

# HENRY'S RADIO LTD.

Mail Order Dept, Electronic Components and Equipment, and Electronic Organ Dept.
303 EDGWARE ROAD, LONDON W2.
Telephone: 01-723 1008/9
Open Mon-Sat. 9am—6pm. Thurs. 9am-1pm

High Fidelity and Audio Centre
309 EDGWARE ROAD, LONDON W2.
Telephone: 01-723 6963
Open all day Saturday.