
PRACTICAL

ELECTRONICS


JULY 1973

20p

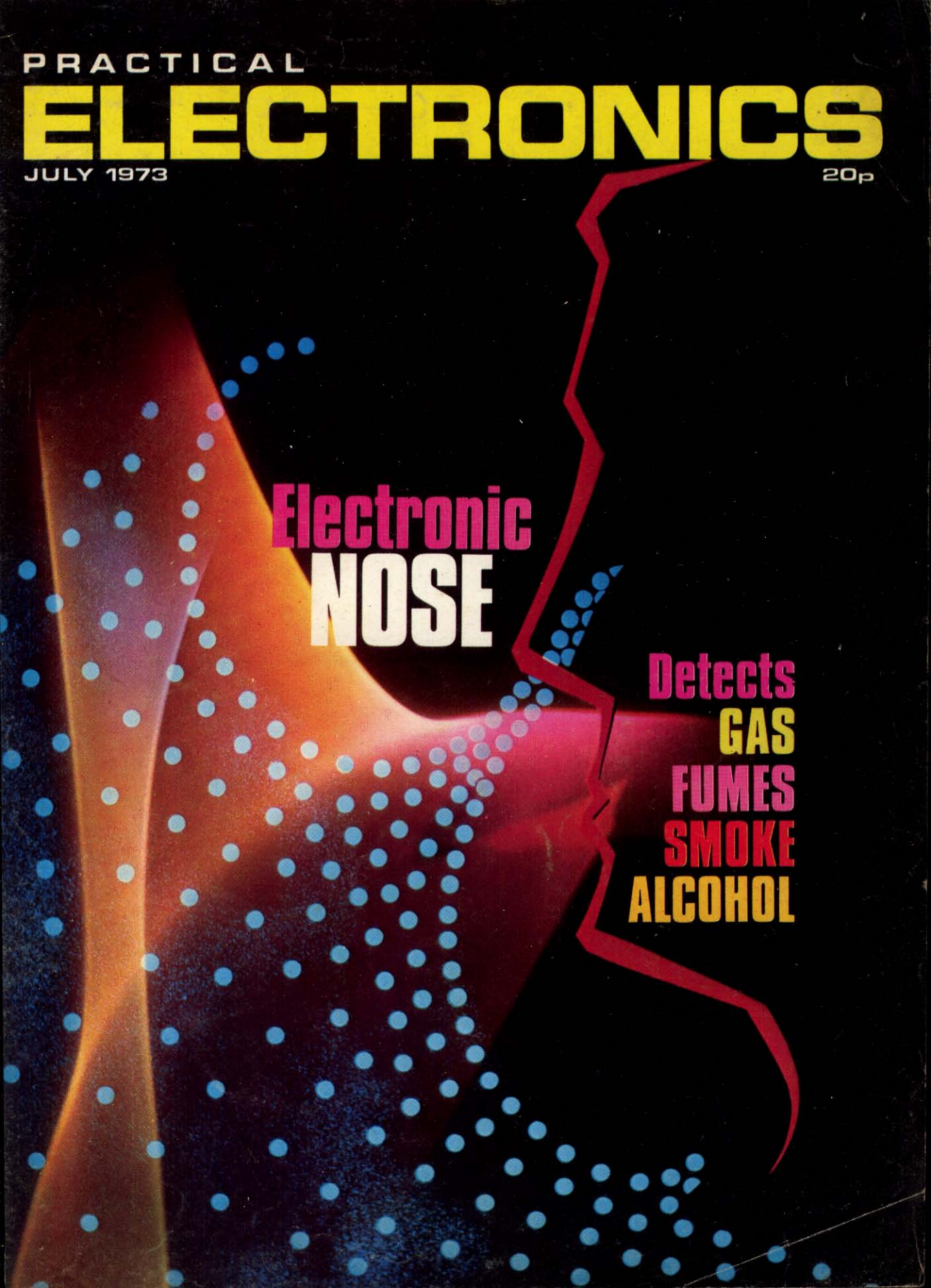

The X25

Why two shafts?

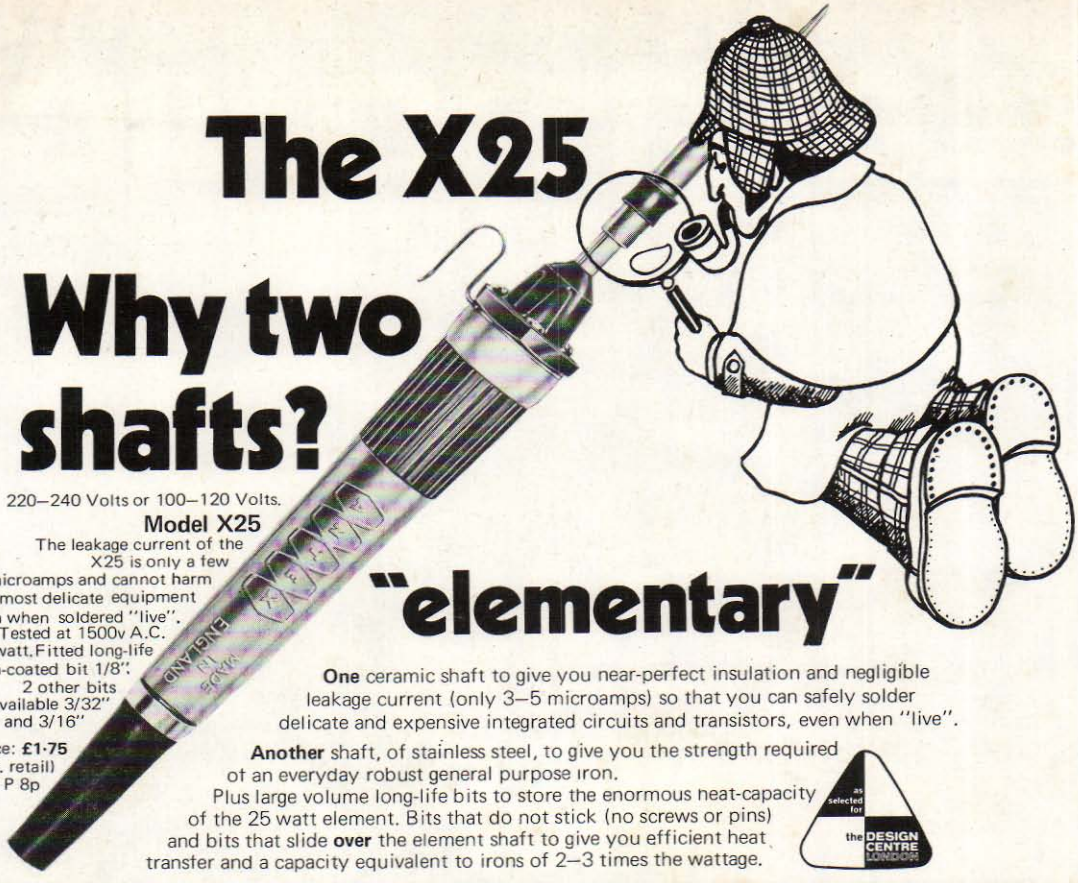

220–240 Volts or 100–120 Volts.

Model X25

The leakage current of the X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live". Tested at 1500v A.C. 25 watt. Fitted long-life iron-coated bit 1/8". 2 other bits available 3/32" and 3/16"

Price: **£1·75** (rec. retail) P & P 8p

"elementary"

One ceramic shaft to give you near-perfect insulation and negligible leakage current (only 3–5 microamps) so that you can safely solder delicate and expensive integrated circuits and transistors, even when "live".

Another shaft, of stainless steel, to give you the strength required of an everyday robust general purpose iron.

Plus large volume long-life bits to store the enormous heat-capacity of the 25 watt element. Bits that do not stick (no screws or pins) and bits that slide **over** the element shaft to give you efficient heat transfer and a capacity equivalent to irons of 2–3 times the wattage.

as selected for the DESIGN CENTRE LONDON



MODEL CCN

220 volts or 240 volts. The 15 watt miniature model CCN also has negligible leakage.
Test voltage 4000v A.C. Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32". 4 other bits available 1/8", 3/16", 1/4" and 3/64".
PRICE: £1·80 P&P 5p

MODEL G

18 watt miniature iron, fitted with long life iron-coated bit 3/32". Voltages 240, 220 or 110.
PRICE: £1·83 (rec. retail). P&P5p



All prices mentioned are exclusive of V.A.T.



MODEL CN

Miniature 15 watt soldering iron fitted 3/32" iron-coated bit. Many other bits available from 3/64", to 3/16". Voltages 240, 220, 110, 50 or 24.
PRICE: £1·70 (rec. retail). P&P5p

MODEL CN2

Miniature 15 watt soldering iron fitted with nickel plated bit 3/32". Voltages 240 or 220.
PRICE: £1·70 (rec. retail). P&P5p



MODEL MLX. KIT

Battery-operated 12v. 25 watt iron fitted with 15' lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet with booklet "How to Solder"
PRICE: £1·95 (rec. retail). P&P 12p



MODEL SK.1 KIT

Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.
PRICE: £2·75 (rec. retail). P&P 12p

MODEL SK.2 KIT

Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32" heat sink, solder, and "How to Solder" booklet.
PRICE: £2·40 (rec. retail). P&P 8p



ANTEX

From radio or electrical dealers, car accessory shops or in case of difficulty direct from:–
ANTEX LTD. FREEPOST (no stamp required) **PLYMOUTH PL1 1BR.** Tel: 0752 67377.

☐ Please send the ANTEX colour catalogue.

☐ Please send the following:

.....

.....

.....

I enclose cheque/P.O./Cash (Giro No. 2581000) Reg. No: 393594

.....

NAME .....

ADDRESS.....

PE7

.....

PRACTICAL
ELECTRONICS
VOLUME 9 No. 7 JULY 1973

CONSTRUCTIONAL PROJECTS

ELECTRONIC NOSE *by D. Bollen*
A portable gas and vapour detector 574

SWITCHED GAIN PREAMPLIFIER *by D. Crocker*
A wide band general purpose instrument 580

P.E. SOUND SYNTHESISER—6 *by G. D. Shaw*
Ramp generator and sound studio set-up 596

TWIN POWER SUPPLY *by G. S. Schajer*
Constant current/constant voltage up to one amp 604

LIGHTING CONTROL UNIT *by G. A. Davies*
Single knob control for multiple effects 611

GENERAL FEATURES

NEW DEVICES . . . APPLICATIONS
The latest in circuit ideas for the experimenter 584

INGENUITY UNLIMITED
Tape Motor Controller—I.C. Lamp Flasher—Windscreen Wiper Control —Engine Temperature Controller—Brake Light Monitor 587

25 YEARS OF SEMICONDUCTORS—1 *by M. J. Rose*
Transistors and small signal diodes 591

LOGIC TUTOR EXPERIMENTS—3 *by M. Hughes*
NAND gates 603

NEWS AND COMMENT

EDITORIAL—Another Sense 573

SPACEWATCH *by Frank W. Hyde*
Outer Hebrides Activity—Soviet Satellites 579

BOOK REVIEWS
Selected new books we have received 583

POINTS ARISING
Pushbutton Varicap Stereo Tuner 583

PHYSICS EXHIBITION
Electronics in science at the Phys. Soc. 594

ON THE FRINGE *by Gerry Brown*
The more unusual aspects of electronics 595

NEWS BRIEFS
Telephone Scrambler—Commercial Radio—Data Transmission—Golden Jubilee 602

INDUSTRY NOTEBOOK *by Nexus*
What's happening inside industry 617

PATENTS REVIEW
Thought provoking ideas on file at the British Patents Office 618

MARKET PLACE
Workshop aids and new products available 621

READOUT
Readers letters and back number requests 622

Our August issue will be published on Friday, July 13, 1973

© IPC Magazines Limited 1973. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Subscription Rates including postage for one year, to any part of the world, £2·65.

G. F. MILWARD 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

TRANSISTORS

Output Transistors
BD 112 ... 25p
OC 36 ... 50p
BD 145 ... 25p

Small Signal N.P.N.
BC 108 ... 10p
BC 109 ... 10p
BF 194 ... 10p

Transmitting Types
BFR 64 ... £1
BKY 89A ... £5
BLY 93A ... £9

Microwave Varactor Diodes
BXY 27/28/32/35/36/37/38/39/40/41 ... £1

Microwave Detector
CAY 10 ... £5

Microwave Mixer
CL 7331 ... £20

Microwave Gunn Effect Oscillator
CL 8370 ... £10
CL 8380 ... £10
CL 8390 ... £10
CL 8470 ... £40

Microwave Tunnel Diodes
AEY 13 ... £5
AEY 16 ... £10

R.F. Transistors
BF 180 ... 20p
BF 194 ... 10p
AF 124 ... 20p

Field Effect Transistors
BFW 12/13/14 ... 25p

Micro-miniature N.P.N.
BFS 18R ... 10p
LDA 400/403/450/452 ... 10p

Ir.fra-red Transmitters
CQY 11A ... £4
CQY 12A ... £10

Light-sensitive Trans
OCP 70 ... 20p

Complementary Drivers, 2 watts (per matched pair)

INTEGRATED CIRCUITS
TBA 500 Luminance I.C. ... £1
TBA 510 Chrominance I.C. ... £1
FEQ 101 64bit Memory ... £1
7400 ... 12p
7401 ... 12p
7410 ... 12p
7420 ... 12p
7440 ... 12p
7453 ... 12p
7470 ... 24p
7472 ... 24p
7473 ... 32p
7474 ... 32p
7482 ... 88p
7483 ... 95p
7490 ... 58p
7491 ... 78p
7492 ... 58p
7493 ... 58p
7495 ... 68p
5400 ... 10p
6404 ... 10p

NEW! NEW! NEW! NEW!

An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.
Method: Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner.
Light sensitive aerosol spray ... £1·00 plus
Developer and Etchant ... 50p postage

NEWER THAN NEW! !

Fibre Glass Board pre-treated with light-sensitive lacquer enabling you to produce prototype printed circuits within five minutes.
75mm × 100mm ... 33p
150mm × 100mm ... 66p
150mm × 200mm ... £1·32

Epoxy-Resin
75mm × 100mm ... 22p
100mm × 150mm ... 44p
150mm × 200mm ... 88p

Copper-clad Fibre Board
12in × 6in ... 45p

Copper-clad Epoxy Resin Board
12in × 6in ... 25p

VEROBOARD
2½in × 1in × 0·15in ... 6p
3¾in × 2½in × 0·15in ... 16p
3¾in × 3¾in × 0·15in ... 20p
5in × 2½in × 0·15in ... 20p
5in × 3¾in × 0·15in ... 28p
17in × 2½in × 0·15in ... 55p
17in × 3¾in × 0·15in ... 74p
3¾in × 2½in × 0·1in ... 21p
3¾in × 3¾in × 0·1in ... 24p
5in × 2½in × 0·1in ... 23p
5in × 3¾in × 0·1in ... 28p

Spot Face Cutter 38p. Pin Insert Tool 48p. Terminal Pins (0·1 or 0·15) 36 for 18p. Special Offer Pack consisting of 5 2½in × 1in boards and a Spot Face Cutter—50p. "ODDS & ENDS"—1p sq in.

MULLARD POLYESTER CAPACITORS
500,000 in STOCK!!!
0·001µF 0·0018µF 0·0056µF 0·015µF
0·0012µF 0·0022µF 0·01µF 0·033µF
0·0015µF 0·0027µF 0·012µF 0·082µF
20p dozen; 75p—100; £5–1,000; £40–10,000
0·15µF 0·18µF 0·22µF 0·39µF 0·68µF
20p dozen; £1–100; £6·50–1,000; £50–10,000

ERIE MONOLITHIC CERAMIC CAPACITORS
3p each; 20p dozen; £1·75 per 100

10pF	68pF	560pF
15pF	100pF	620pF
22pF	150pF	680pF
33pF	220pF	1,000pF
39pF	330pF	
47pF	470pF	

£1 100 ¼-1 WATT RESISTORS, 100 CERAMIC CAPACITORS, 100 DIODES — POSTAGE 15p — PACK No. 1

£1 1 VEROBOARD CUTTER, 5 2½in x 0·15 BOARDS, 50 SQ.IN "ODD PIECES" VERO — POSTAGE 15p — PACK No. 3

£1 20 ASSORTED UNUSED MARKED, TESTED TRANSISTORS BC108, ETC. — POSTAGE 15p — PACK No. 5

£1 6 COMPUTER PANELS CONTAINING MASSES OF DIODES, TRANSISTORS, INDUCTORS, RESISTORS AND CAPACITORS — POSTAGE 25P — PACK No. 7

£1 100 RESISTORS, 100 CERAMIC CAPACITORS, 100 POLYSTYRENE CAPACITORS — POSTAGE 15p — PACK No. 2

£1 100 RESISTORS, 100 CERAMIC CAPACITORS, 50 MULLARD POLYESTER CAPACITORS — POSTAGE 15p — PACK No. 4

£1 1 TRANSISTORISED SIGNAL TRACER KIT, 1 TRANSISTORISED SIGNAL INJECTOR KIT — POSTAGE 15p — PACK No. 6

£1 100 RESISTORS, 100 CAPACITORS (ASSORTED TYPES) — POSTAGE 15P — PACK No. 8

POSTAGE (MINIMUM) 15P PER ORDER — **ALL GOODS PLUS 10% V.A.T.**



Lasky's Audio-Tronics Catalogue 1973

The new 1973 VAT edition of Lasky's famous Audio-Tronics Catalogue will be available in early April—FREE on request. The 48 tabloid size pages—many in full colour—have been reprinted with VAT price changes for your convenience, together with many new items. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals), Tape Recording and Audio Accessories. Send for your copy now and see for yourself that VAT can mean a saving on many of the 1000's of items we offer.

FREE Send this coupon with 15p for post and inclusion on our regular mailing list.

NAME .....

ADDRESS .....

.....

.....PE13

LASKY'S RADIO LIMITED, 3-15 CAVELL STREET, LONDON E.1.

GUNTON ELECTRONIC IGNITION KIT £9·35 INC. VAT

READY BUILT UNIT GUARANTEED 5 YEARS £11·55 INC. VAT

Patents Pending. 12 volt only—state pos. or neg. earth.
Capacitive discharge ignition is recognised as being the most efficient system and will give you:



★ Continual Peak-Tuned Performance
★ Up to 20% reduced fuel consumption
★ Easier All-weather Starting
★ Increased Acceleration and Top Speed
★ Longer Spark Plug Life
★ Increased Battery Life
★ Elimination of Contact Breaker Burn
★ Purer Exhaust Gas Emission

Kit includes absolutely everything for assembly: Ready drilled Case and Hardware Printed Circuit Board, Cables, Coil Connectors, Silicon Grease Nuts and Bolts, etc. 8 page illustrated instructions cover fitting of all types of tachometers. Call in for a workshop demonstration. S.A.E. all enquiries please, or Phone 33652. (Many letters from satisfied customers.)

SCORPIO: Transformer £2·42. Printed Circuit Board 83p

All prices include carriage and V.A.T.

ALUMINIUM BOXES

Complete with baseplate and screws

AT DIRECT FROM MANUFACTURERS' PRICES WITH RETURN OF POST SERVICE

Type No	L	W	D	Price
7*	5¼	2¾	1½	44p
8*	4	4	1½	44p
9*	4	2¾	1½	44p
10*	5¼	4	1½	53p
11	4	2½	2	44p
12	3	2	1	39p
13	6	4	2	59p
14	7	5	2½	68p
15	8	6	3	88p
16	10	7	3	96p

* These sizes accept standard veroboard range.
All prices include carriage and V.A.T. 20% discount on 10 or more boxes. 30% discount on orders over £10.

Dept. PE7, ELECTRONICS DESIGN ASSOCIATES
82 BATH STREET, WALSALL WS1 3DE

SAXON ENTERTAINMENTS

STANDARD and CUSTOM-BUILT AUDIO and ELECTRONIC EQUIPMENT
NEW and SECONDHAND MUSICAL INSTRUMENTS. MAIN DISTRIBUTORS
FOR A.K.G. HIGH QUALITY MICROPHONES

SA25-SA35-SA100

LOW-PRICED AUDIO MODULES FOR DOMESTIC and COMMERCIAL USE

New versions using 3A "Plastic Power" Driver Transistors now available



THESE THREE MODULES HAVE ENJOYED UNPARALLELED SUCCESS DURING THE FIRST FEW MONTHS OF THEIR BEING MADE AVAILABLE TO THE GENERAL PUBLIC. WE ARE PLEASED TO ANNOUNCE THAT WE CAN NOW OFFER FAST DISPATCH ON MOST OF OUR ADVERTISED ITEMS, INCLUDING THESE THREE MODULES.

SA25 £2·95 carr. free
25 WATTS R.M.S. 7 transistors, 7 diodes

SA35 £4·45 carr. free
35 WATTS R.M.S. 7 transistors, 7 diodes

SA100 £10·90 carr. free
100 WATTS R.M.S. 11 transistors, 6 diodes

ALL THREE MODULES HAVE OPEN AND SHORT CIRCUIT PROTECTION, AND THE SA100 IS PROOF AGAINST OVER-DISSIPATION AND FAULTY INDUCTIVE LOADS.

ONLY ADVANCED DESIGN TECHNIQUES MAKE THESE EXTRAORDINARILY LOW PRICES POSSIBLE.

BRIEF SPEC. FOR ALL THREE MODULES

Freq. response	20–40,000Hz ± 1dB
Distortion	0·2% at 1kHz
Loads	4 to 16 ohms
Quiescent current	15mA
Noise	Better than −75dB
Supply voltage	25–45V, SA25/35 40–70V, SA100
Size	4½in × 4in × 1in (SA100) 4in × 3in × 1in (SA25, SA35)

Circuits, connecting instructions and application data are supplied free with all modules.

POWER SUPPLIES FOR THE SA25/35 and SA100 AUDIO MODULES

PU45	Unstabilised supply for 2 SA25/35's, **£4·90**.
PU70	Unstabilised supply for one or two SA100's, **£7·75**, carr. 40p
PS45	Stabilised module for 2 SA25's or two SA35's, **£3·50**, carr. free
MT45	Transformer for above, heavy duty, **£2·85**, carr. 20p
MT30	Transformer for unstabilised supply complete with rectifier diodes mounted **£3·50**, carr. 20p
PS70	Stabilised supply module for one or two SA100's, **£4·90**, carr. free
MT70	Transformer for PS70, **£4·90**, carr. 40p

ALL MODULES ARE BUILT ON GLASS FIBRE P.C. BOARD
AND ARE SUPPLIED FULLY TESTED

OTHER SAXON PRODUCTS . . .

120 WATT HEAVY DUTY MODULE

£13·90 + 20p carr. or with supply **£18·95** + 40p carr.

Featuring a rugged class A driver stage, this module will run from all our mixers etc., and most other makes of mixer. It delivers 120W into an eight ohm load and employs 4 TO3 can (115W) output transistors.



SPECIFICATION

Power output	120W into 8 ohms
Freq. response	20–20,000Hz ± 2dB
Input sensitivity	200mV into 10K
Construction	Fibreglass board
Size	8in × 4in × 4in (5in with supply)

Low distortion parallel push–pull output stage.

NEW: 160 Watt version & supply **£27·90**

SINGLE CHANNEL SOUND/LIGHT CONVERTER


This compact and reliable unit operates from amplifiers with outputs from 5–100W. Does not impose a heavy load on the amplifier, or, if connected in the wrong polarity, cause any damage, as with some units.

Operation is simplicity itself and the unit is fully fused. The unit is supplied to function from bass notes but may easily be converted to respond only to treble or mid-range notes by the addition of components costing less than 5p.



£8·90 carr. free

THREE CHANNEL SOUND TO LIGHT UNIT

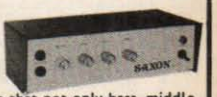

Handling the total of 3,000W (3kW) this unit is unique for its price in that not only bass middle and treble but also master controls are provided. Two amplifier sockets eliminate the need for split leads, etc. Supplied in tough steel case for free-mounting or panel fixing. Fully guaranteed.

£19·75 carr. 30p

MONO VERSION £6·50, carr. 20p

(As illustrated below. S.A.E. details. 9V operation)
OUTPUTS UP TO 1V RMS


£15·80 carr. 30p
SAXON STEREO CONTROL UNIT



Two decks, and full headphone monitoring. The unit is mains operated and measures 17½in × 3in × 4in deep and is finished with a smart white on black facia. The controls are: Left/Right deck fader, volume, bass, treble, headphone selector and volume, microphone volume, bass, treble, mains on/off. **THIS IS A MUST FOR THE HOME BUILT HIGH QUALITY DISCOTHEQUE AND IS COMPARABLE TO UNITS AT OVER TWICE THE PRICE.**
(N.B.—Stereo only has mic. input.)

COMPLETE AMPLIFIERS

THE CSE 100. £34·90 carr. free

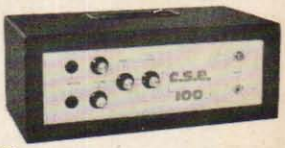

This versatile unit is now available in a black vynide case and so represents even better value than ever, delivering speech and music powers of up to 100W R.M.S. and continuous signal outputs of 70W.
Two individually controlled inputs with wide range bass and treble controls. Ideal for small groups, D.J's, etc.



The SAXON 100. £48·50, carr. free.

With an R.M.S. output of 120W speech and music, 100W continuous power, four individually controlled F.E.T. input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

LOUDSPEAKERS British made bargains!!!

12in 25W 8/15 ohms **£5·95**, carr. 30p. 15in 50W 8/15 ohm, **£14·50**, carr. 50p. 12in 40W 15,000 gauss magnet system 8/15 ohm, **£11·50**, carr. 40p.

A.K.G. MICROPHONES suitable for disco, group or general P.A. use D11DHL ideal disco mike, only **£9·45** (r.r.p. £11).

600W 3 colour light boxes, smart rexine finish.
£15 carr. free

ALL PRICES SUBJECT TO VAT AT STANDARD RATE

SEND S.A.E. FOR OUR A.K.G. PRICE LIST. DISCOUNTS ON ALL MICS.

Mail Orders to Dept. P.E.7

SAXON ENTERTAINMENTS LTD., 327-331 WHITEHORSE RD., W. CROYDON, SURREY CR0 2HS

Telephone 01-684 6385 — Hours of Business 9.30 a.m. — 5.30 p.m.

TERMS OF BUSINESS C.W.O.: C.O.D. 35p extra: Cash by registered post, please.

TRADE AND EXPORT ENQUIRIES INVITED

NOW! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS

Build as you learn with the exciting new TECHNATRON Outfit! No mathematics. No soldering—you learn the *practical* way.

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical "know-how"—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.'s simplified study method and the remarkable TECHNATRON Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

. . . and what's more, you will understand exactly what you are doing. The TECHNATRON Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

You LEARN—but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a "non-technical" type. And, if you want to make it a career, B.I.E.T. has a fine range of courses up to City and Guilds standards.

Specialist Booklet

If you wish to make a career in Electronics, send for your FREE copy of "NEW OPPORTUNITIES". This brand new booklet—just out—tells you all about TECHNATRON and B.I.E.T.'s full range of courses.



FREE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. BPE17, ALDERMASTON COURT, READING RG7 4PF

Accredited by the Council for the Accreditation of Correspondence Colleges.

POST THIS COUPON FOR FREE BOOK

CL | BPE17

NAME (BLOCK CAPITALS)..... AGE.....

ADDRESS.....

.....

.....

SUBJECT OF INTEREST.....

ERSIN Multicore 5 CORE SOLDER

for fast, easy reliable soldering

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

EASY-TO-USE DISPENSERS



Size 5 Savbit alloy 18 swg, **18p** (illustrated).
Size 19A 60/40 alloy 18 swg, **18p**
Size 15 60/40 alloy 22 swg, **22p**

IDEAL FOR HOME CONSTRUCTORS

Size 1 cartons in 40/60, 60/40 and Savbit alloys in 7 gauges **25p**



Size 12 for Service Engineers and Electricians. 75ft of 18 swg Savbit alloy. **75p**



NEW! BIB WIRE STRIPPER AND CUTTER



Deluxe Model 9 Automatic opening spring, locking catch, plastic-covered handles. Case hardened and precision ground. Adjusts to most wire sizes. Cuts and strips flex, splits plastic twin flex. **75p**

Prices shown are recommended retail, excluding V.A.T.
From Electrical and Hardware Shops. If unobtainable, send 10p p&p direct to:
Multicore Solders Ltd., Hemel Hempstead, Hertfordshire HP2 7EP

AMAZING MINI-DRILL



FOR PRECISION MODEL WORK



+ 6 TOOLS

ONLY £2.20 P. & P. 10p

Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4½ volt external battery. So much more scope with MINI-DRILL. Super Kit (extra power, interchangeable chuck) **£5·44** p.p. 13p.
De Luxe Professional Kit with 17 tools **£8·41** p.p. 23p.
Money Ref. Guarantee.

MERLIN SUPPLY CO.

Dept. PE7D, Nailsea, Bristol BS19 2LP

AUTOMATIC EMERGENCY SUPPLY

250v 50 Hz—150 watt Inverter. Full kit of parts excluding meter. Circuit as appeared in December P.W. Complete kit—**£16·95** + 80p. P. & P.

OTHER INVERTERS AVAILABLE IN KIT FORM

150 Watt—**£13·50** + 60p P. & P. 75 Watt—**£7·80** + 60p P. & P.
300 Watt—**£17·90** + 85p P. & P. 40 Watt—**£5·20** + 40p P. & P.
25 Watt—**£2·60** + 20p P. & P.

All above operate from 12v. battery and give 250v.-50Hz. Output. 24 volt types are also available, alternative outputs or taps can be supplied. Transformers and/or Transistors can be supplied separately.

SPECIAL OFFER

12v. Fluorescent lights, suitable for tents, caravans, houses or secondary lighting for factories, hotels, etc. 12 inch—8 watt—**£3·40** post paid. 21 inch—13 watt—**£4·20** post paid. Large discounts available for quantities.

BATTERY CHARGER KIT

10 amp charge current—**£5·50** + 40p P. & P.
(consists of Transformer and Rectifiers)

ASTRO ELECTRONICS

6 BARNES ROAD, CHESTERFIELD, DERBYSHIRE

THIS IS THE FIRST PAGE OF THE GREAT BI-PAK SECTION

BRAND NEW FULLY GUARANTEED DEVICES

AC107	0·22	AD162	0·37	BC148	0·11	BD137	0·50	BF188	0·44	OC19	0·39	2G371	0·18	2N2219	0·22
AC113	0·22	AD161 &		BC149	0·13	BD138	0·55	BF194	0·13	OC20	0·70	2G371B	0·13	2N2220	0·24
AC115	0·26	AD162(MP)		BC150	0·20	BD139	0·61	BF195	0·13	OC22	0·42	2G373	0·19	2N2221	0·22
AC117K	0·22		0·61	BC151	0·22	BD140	0·66	BF196	0·16	OC23	0·46	2G374	0·19	2N2222	0·22
AC122	0·13	ADT140	0·55	BC152	0·19	BD155	0·88	BF197	0·16	OC24	0·62	2G377	0·33	2N2368	0·19
AC125	0·19	AF114	0·27	BC153	0·31	BD175	0·66	BF200	0·50	OC25	0·42	2G378	0·18	2N2369	0·16
AC126	0·19	AF115	0·27	BC154	0·33	BD176	0·66	BF222	1·05	OC26	0·25	2G381	0·18	2N2369A	0·16
AC127	0·19	AF116	0·27	BC157	0·20	BD177	0·72	BF257	0·50	OC28	0·55	2G382	0·18	2N2411	0·27
AC128	0·19	AF117	0·27	BC158	0·13	BD178	0·72	BF258	0·66	OC29	0·55	2G401	0·33	2N2412	0·27
AC132	0·16	AF118	0·39	BC159	0·13	BD179	0·77	BF259	0·94	OC35	0·46	2G414	0·33	2N2646	0·52
AC134	0·16	AF124	0·33	BC160	0·50	BD180	0·77	BF262	0·61	OC36	0·55	2G417	0·28	2N2711	0·23
AC137	0·16	AF125	0·28	BC161	0·55	BD185	0·72	BF263	0·61	OC41	0·22	2N388	0·39	2N2712	0·23
AC141	0·16	AF126	0·31	BC167	0·13	BD186	0·72	BF270	0·39	OC42	0·27	2N388A	0·61	2N2714	0·23
AC141K	0·19	AF127	0·31	BC168	0·13	BD187	0·77	BF271	0·33	OC44	0·17	2N404	0·22	2N2904	0·19
AC142	0·16	AF139	0·33	BC169	0·13	BD188	0·77	BF272	0·88	OC45	0·14	2N404A	0·31	2N2904A	0·23
AC142K	0·19	AF178	0·33	BC170	0·13	BD189	0·83	BF273	0·39	OC70	0·11	2N524	0·46	2N2905	0·23
AC151	0·17	AF179	0·55	BC171	0·16	BD190	0·83	BF274	0·39	OC71	0·11	2N527	0·54	2N2905A	0·23
AC154	0·22	AF180	0·55	BC172	0·16	BD195	0·94	BFW10	0·66	OC72	0·16	2N598	0·46	2N2906	0·17
AC155	0·22	AF181	0·50	BC173	0·16	BD196	0·94	BFX29	0·30	OC74	0·16	2N599	0·50	2N2906A	0·20
AC156	0·22	AF186	0·50	BC174	0·16	BD197	0·99	BFX84	0·24	OC75	0·17	2N696	0·14	2N2907	0·22
AC157	0·27	AF239	0·41	BC175	0·24	BD198	0·99	BFX85	0·33	OC76	0·17	2N697	0·15	2N2907A	0·24
AC165	0·22	AL102	0·72	BC177	0·21	BD199	1·05	BFX86	0·24	OC77	0·28	2N698	0·27	2N2923	0·16
AC166	0·22	AL103	0·72	BC178	0·21	BD200	1·05	BFX87	0·27	OC81	0·17	2N699	0·39	2N2924	0·16
AC167	0·22	ASY26	0·28	BC179	0·21	BD205	0·88	BFX88	0·24	OC81D	0·17	2N706	0·09	2N2925	0·16
AC168	0·27	ASY27	0·33	BC180	0·27	BD206	0·88	BFY50	0·22	OC82	0·17	2N706A	0·10	2N2926 (G)	
AC169	0·16	ASY28	0·28	BC181	0·27	BD207	1·05	BFY51	0·22	OC82D	0·17	2N708	0·13		0·14
AC176	0·22	ASY29	0·28	BC182	0·11	BD208	1·05	BFY52	0·22	OC83	0·22	2N711	0·33	2N2926 (Y)	
AC177	0·27	ASY50	0·28	BC182L	0·11	BDY20	1·10	BFY53	0·19	OC84	0·22	2N717	0·39		0·12
AC178	0·31	ASY51	0·28	BC183	0·11	BF115	0·27	BPX25	0·94	OC139	0·22	2N718	0·27	2N2926 (O)	
AC179	0·31	ASY52	0·28	BC183L	0·11	BF117	0·50	BSX19	0·17	OC140	0·22	2N718A	0·55		0·11
AC180	0·19	ASY54	0·28	BC184	0·13	BF118	0·77	BSX20	0·17	OC169	0·28	2N726	0·31	2N2926 (R)	
AC180K	0·22	ASY55	0·28	BC184L	0·13	BF119	0·77	BSY25	0·17	OC170	0·28	2N727	0·31		0·11
AC181	0·19	ASY56	0·28	BC186	0·31	BF121	0·50	BSY26	0·17	OC171	0·28	2N743	0·22	2N2926 (B)	
AC181K	0·22	ASY57	0·28	BC187	0·31	BF123	0·55	BSY27	0·17	OC200	0·28	2N744	0·22		0·11
AC187	0·24	ASY58	0·28	BC207	0·12	BF125	0·50	BSY28	0·17	OC201	0·31	2N914	0·16	2N3010	0·77
AC187K	0·22	ASZ21	0·44	BC208	0·12	BF127	0·55	BSY29	0·17	OC202	0·31	2N918	0·33	2N3011	0·16
AC188	0·24	BC107	0·10	BC209	0·13	BF152	0·61	BSY38	0·20	OC203	0·28	2N929	0·23	2N3053	0·19
AC188K	0·22	BC108	0·10	BC212L	0·12	BF153	0·50	BSY39	0·20	OC204	0·28	2N930	0·23		
ACY17	0·28	BC109	0·11	BC213L	0·12	BF154	0·50	BSY40	0·31	OC205	0·39	2N1131	0·22		
ACY18	0·22	BC113	0·11	BC214L	0·16	BF155	0·77	BSY41	0·31	OC309	0·44	2N1132	0·24		
ACY19	0·22	BC114	0·17	BC225	0·28	BF156	0·53	BSY95	0·14	OCP71	0·48	2N1302	0·16		
ACY20	0·22	BC115	0·17	BC226	0·39	BF157	0·61	BSY95A	0·14	ORP12	0·48	2N1303	0·16	AA119	0·09
ACY21	0·22	BC116	0·17	BCY30	0·27	BF158	0·61	Bu105	2·20	ORP60	0·44	2N1304	0·19	AA120	0·09
ACY22	0·18	BC117	0·17	BCY31	0·29	BF159	0·66	C111E	0·55	ORP61	0·44	2N1305	0·19	AA129	0·09
ACY27	0·20	BC118	0·11	BCY32	0·33	BF160	0·44	C400	0·33	P346A	0·22	2N1306	0·23	AAY30	0·10
ACY28	0·21	BC119	0·33	BCY33	0·24	BF162	0·44	C407	0·28	P397	0·46	2N1307	0·23	AAZ13	0·11
ACY29	0·39	BC120	0·88	BCY34	0·28	BF163	0·44	C424	0·22	ST140	0·14	2N1308	0·26	BA100	0·11
ACY30	0·31	BC125	0·13	BCY70	0·16	BF164	0·44	C425	0·55	ST141	0·19	2N1309	0·26	BA116	0·23
ACY31	0·31	BC126	0·20	BCY71	0·20	BF165	0·44	C426	0·39	TIS43	0·33	2N1613	0·22	BA126	0·24
ACY34	0·23	BC132	0·13	BCY72	0·16	BF167	0·24	C428	0·22	UT46	0·30	2N1711	0·22	BA148	0·16
ACY35	0·23	BC134	0·20	BCZ10	0·22	BF173	0·24	C441	0·33	2G301	0·21	2N1889	0·35	BA154	0·13
ACY36	0·31	BC135	0·13	BCZ11	0·28	BF176	0·39	C442	0·33	2G302	0·21	2N1890	0·50	BA155	0·16
ACY40	0·19	BC136	0·17	BCZ12	0·28	BF177	0·39	C444	0·39	2G303	0·21	2N1893	0·41	BA156	0·15
ACY41	0·20	BC137	0·17	BD121	0·66	BF178	0·33	C450	0·24	2G304	0·27	2N2147	0·79	BY100	0·17
ACY44	0·39	BC139	0·44	BD123	0·72	BF179	0·33	MAT100	0·21	2G306	0·44	2N2148	0·63	BY101	0·13
AD130	0·42	BC140	0·33	BD124	0·66	BF180	0·33	MAT101	0·22	2G308	0·39	2N2160	0·66	BY105	0·19
AD140	0·53	BC141	0·33	BD131	0·55	BF181	0·33	MAT120	0·21	2G309	0·39	2N2192	0·39	BY114	0·13
AD142	0·53	BC142	0·33	BD132	0·66	BF182	0·44	MAT121	0·22	2G339	0·22	2N2193	0·39	BY126	0·16
AD143	0·42	BC143	0·33	BD133	0·72	BF183	0·44	MPF102	0·46	2G339A	0·18	2N2194	0·39	BY127	0·17
AD149	0·55	BC145	0·50	BD135	0·44	BF184	0·28	MPF104	0·41	2G344	0·20	2N2217	0·24	BY128	0·17
AD161	0·37	BC147	0·11	BD136	0·44	BF185	0·33	MPF105	0·41	2G345	0·18	2N2218	0·22	BY130	0·18

2N3054	0·51	2N4059	0·11												
2N3055	0·55	2N4060	0·13												
2N3391	0·16	2N4061	0·13												
2N3391A	0·18	2N4062	0·13												
2N3392	0·16	2N4284	0·19												
2N3393	0·16	2N4285	0·19												
2N3394	0·16	2N4286	0·19												
2N3395	0·19	2N4287	0·19												
2N3402	0·23	2N4288	0·19												
2N3403	0·23	2N4289	0·19												
2N3404	0·31	2N4290	0·19												
2N3405	0·46	2N4291	0·19												
2N3414	0·17	2N4292	0·19												
2N3415	0·17	2N4293	0·19												
2N3416	0·31	2N5172	0·13												
2N3417	0·31	2N5457	0·35												
2N3525	0·83	2N5458	0·35												
2N3646	0·10	2N5459	0·44												
2N3702	0·11	2S301	0·55												
2N3703	0·11	2S302A	0·46												
2N3704	0·12	2S302	0·46												
2N3705	0·11	2S303	0·81												
2N3706	0·10	2S034	0·77												
2N3707	0·12	2S305	0·93												
2N3708	0·08	2S306	0·93												
2N3709	0·10	2S307	0·93												
2N3710	0·10	2S321	0·62												
2N3711	0·10	2S322	0·46												
2N3819	0·31	2S322A	0·46												
2N3820	0·55	2S323	0·62												
2N3821	0·39	2S324	0·77												
2N3823	0·31	2S325	0·77												
2N3903	0·31	2S326	0·77												
2N3904	0·33	2S327	0·77												
2N3905	0·31	2S701	0·46												
2N3906	0·30	40361	0·44												
2N4058	0·13	40362	0·50												

DIODES AND RECTIFIERS

AA119	0·09	BY133	0·23	OA10	0·39
AA120	0·09	BY164	0·55	OA47	0·08
AA129	0·09	BYX38/300		OA70	0·08
AAY30	0·10		0·46	OA79	0·08
AAZ13	0·11	BYZ10	0·39	OA81	0·08
BA100	0·11	BYZ11	0·33	OA85	0·10
BA116	0·23	BYZ12	0·33	OA90	0·07
BA126	0·24	BYZ13	0·28	OA91	0·07
BA148	0·16	BYZ16	0·44	OA95	0·08
BA154	0·13	BYZ17	0·39	OA200	0·07
BA155	0·16	BYZ18	0·39	OA202	0·08
BA156	0·15	BYZ19	0·31	SD10	0·06
BY100	0·17	CG62		SD19	0·06
BY101	0·13	(OA91 Eq.)		1N34	0·08
BY105	0·19		0·06	1N34A	0·08
BY114	0·13	CG651—		1N914	0·07
BY126	0·16	(OA70–OA79)		1N916	0·07
BY127	0·17		0·07	1N414B	0·07
BY128	0·17	OA5	0·39	18021	0·11
BY130	0·18	OA85L	0·23	18951	0·07

NEW COMPONENT PAK BARGAINS

Pak No.	Qty.	Description	Price
C 1	250	Resistors mixed values approx. (count by weight)	0·55
C 2	200	Capacitors mixed values approx. (count by weight)	0·55
C 3	50	Precision Resistors ·1%, and ·01% mixed values	0·55
C 4	75	¼th W Resistors mixed preferred values	0·55
C 5	5	Pieces assorted Ferrite Rods	0·55
C 6	2	Tuning Gangs, MW/LW VHF	0·55
C 7	1	Pack Wire 50 meters assorted colours	0·55
C 8	10	Reed Switches	0·55
C 9	3	Micro Switches	0·55
C10	15	Assorted Pots & Pre-Sets	0·55
C11	5	Jack Sockets 3 × 3·5m 2 × Standard Switch Types	0·55
C12	40	Paper Condensers preferred types mixed values	0·55
C13	20	Electrolytics Trans. types	0·55
C14	1	Pack assorted Hardware—Nuts/Bolts, Gromets, etc.	0·55
C15	4	Mains Toggle Switches, 2 Amp D/P	0·55
C16	20	Assorted Tag Strips & Panels	0·55
C17	10	Assorted Control Knobs	0·55
C18	4	Rotary Wave Change Switches	0·55
C19	3	Relays 6—24V Operating	0·55
C20	4	Sheets Copper Laminate approx. 10in × 7in	0·55

Please add 10p post and packing on all component packs, plus a further 10p on pack Nos. C1, C2, C19 and C20.

Component Lists for mail order available on request.

Plus-much more-
SEND NOW FOR THE
BI-PAK *"Component Catalogue"*
5p to cover postage, etc.

INTERESTED IN ELECTRONICS?
then give us a ring, we need staff—fast!
0920-3442

JUMBO COMPONENT PAKS
Mixed Electronic Components

Resistors, capacitors, pots, electrolytics and coils plus many other useful items. Approximately 3lb in weight. Price including P. & P. £1·65.

EXCEPTIONALLY GOOD VALUE



BRAND NEW POST OFFICE TYPE TELE-PHONE DIALS ONLY 83p each

THE NEW S.G.S. EA 1000 AUDIO AMP MODULE *Guarantee

3 Watts R.M.S. ONLY £2·89 each



Module Tested and Guaranteed.
Qty. 1—9 £2·89; 10—25 £2·51 Price each. Larger quantities quoted on request. Full hook-up diagrams and complete technical data supplied free with each module or available separately at 10p each.

SYSTEM 12 STEREO

Each Kit contains two Amplifier Modules, 3 watts RMS, two loudspeakers, 15 ohms, the pre-amplifier, transformer, power supply module, front panel and other accessories, as well as an illustrated stage-by-stage instruction booklet designed for the beginner.
Further details available on request.



ONLY £18·64 FREE P. & P.

NOW-TURN OVER FOR MORE FANTASTIC OFFERS

Cut these 3 pages out and keep for reference

The largest selection

NEW LOW PRICED TESTED S.C.R.'S

	PIV 50	100	200	400	600	800
	£p	£p	£p	£p	£p	£p
1A TO5	0·28	0·28	0·34	0·48	0·59	0·70
3A TO66	0·28	0·37	0·41	0·52	0·63	0·77
5A TO66	0·34	0·52	0·54	0·62	0·75	0·88
5A TO64	0·34	0·52	0·54	0·62	0·75	0·88
7A TO48	0·52	0·55	0·63	0·74	0·85	0·99
10A TO48	0·56	0·64	0·67	0·83	1·07	1·32
16A TO48	0·59	0·70	0·83	1·03	1·38	1·65
30A TO48	1·27	1·54	1·76	1·93	—	4·40

SIL. RECTS. TESTED

PIV	300mA DO7	750mA SO16	1A Plastic	1·5A SO16	3A SO10	10A SO10	30A SO32A
50	0·04	0·06	0·06	0·08	0·16	0·23	0·66
100	0·04	0·07	0·06	0·15	0·18	0·26	0·83
200	0·06	0·10	0·07	0·16	0·22	0·27	1·10
400	0·07	0·15	0·08	0·22	0·30	0·41	1·38
600	0·08	0·18	0·11	0·26	0·38	0·50	2·05
800	0·11	0·19	0·12	0·28	0·41	0·61	2·20
1000	0·12	0·30	0·16	0·33	0·51	0·70	2·75
1200	—	0·37	—	0·42	0·63	0·83	—

TRIACS

VBOM	2A TO-66	6A TO-66	10A TO-48
	£p	£p	£p
100V	33	55	83
200V	55	66	99
400V	77	83	1·21

DIACS

FOR USE WITH TRIACS
BR100 (D32) 41p each

FREE

One 50p Pak of your own choice free with orders valued £4 or over.

BRAND NEW TEXAS GERM. TRANSISTORS Coded and Guaranteed

Pak No.		EQVT
T1	8	2G373 OC71
T2	8	D1374 OC75
T3	8	D1216 OC81D
T4	8	2G381T OC81
T5	8	2G382T OC82
T6	8	2G344B OC44
T7	8	2G345B OC45
T8	8	2G378 OC78
T9	8	2G399A 2N1302
T10	8	2G417 AF117

All 55p each pak

2N2060 NPN SIL. DUAL TRANS. CODE D1699 TEXAS. Our price 28p each.

120 VCB NIXIE DRIVER TRANSISTOR. Sim. BSX21 & C407, 2N1893 FULLY TESTED AND CODED ND 120. 1-24 19p each. TO-5 N.P.N. 25 up 17p each.

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqvt. ZTX300 6p each. Any Quantity.

ZENER DIODES

400mW (DO-7 Case), range 2–33V, 15p each. 1·5W (Top-Hat), range 2–33V, 20p each. 10W (SO-10 Stud), range 2–33V, 33p each.

10 amp POTTED BRIDGE RECTIFIER on heat sink. 100PIV. 99p each

NEW LINE Plastic Encapsulated 2 Amp. BRIDGE RECTS.

50V RMS	35p each
100V RMS	41p each
400V RMS	51p each

Size 15mm × 6mm.

UNIJUNCTION TRANSISTORS

Direct replacement for TIS43 and BEN3000 also electrically equivalent to 2N2646 Qty.: 1–24 30p each, 25–99 28p each, 100+ 22p each.

CADMIUM CELLS

ORP12 48p
ORP60, ORP61 44p each

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N706/8. BSY-27/28/95A. All usable devices no open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

		£p
20	For	0·55
50	For	1·10
100	For	1·92
500	For	8·25
1000	For	14·30

SIL. G.P. DIODES £p

300mW	30	0·55
40PIV(Min.)	100	1·65
Sub-Min.	500	5·50
Full Tested	1,000	9·90

Ideal for Organ Builders.

POWER TRANS BONANZA!

GENERAL PURPOSE GERM. PNP

Coded GP100. BRAND NEW TO-3 CASE. POSS. REPLACE:—OC25–28–29–30–35–36. NKT 401–403–404–405–406–430–451–452–453. T13027–3028, 2N250A, 2N456A–457A–458A, 2N511 A & B. 2G220–222, ETC. VCBO 80V VCEO 50V IC 10A PT. 30 WATTS Hfe 30–170.

PRICE 1–24	25–99	100 up
47p each	44p each	40p each

SILICON High Voltage 250V NPN TO-3 case. G.P. Switching & Amplifier Applications. Brand new Coded R 2400 VCBO 250/VCEO 100/IC 6A/30 Watts. HFE type 20/ft 5MHZ.
OUR PRICE EACH:

1–24	25–99	100 up
55p	50p	44p

2N3055

115 WATT SIL POWER NPN
55p EACH

AD161/162 PNP

M/P COMP GERM TRANS.
OUR LOWEST PRICE OF 60p PER PAIR

SILICON 50 WATTS MATCHED NPN/PNP
BIP 19 NPN TO-3 Plastic. BIP 20 PNP. Brand new. VCBO 100/VCEO 50/IC 10A. HFE type 100/ft 3mHZ.
OUR PRICE PER PAIR:
1–24 prs: 66p 25–99 prs. 61p 100 prs. 55p

KING OF THE PAKS Unequalled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.		Description	Price
U 1	120	Glass Sub-Min. General Purpose Germanium Diodes	0·55
U 2	60	Mixed Germanium Transistors AF/RF	0·55
U 3	75	Germanium Gold Bonded Sub-Min. like OA5, OA47	0·55
U 4	40	Germanium Transistors like OC81, AC128	0·55
U 5	60	200mA Sub-Min. Silicon Diodes	0·55
U 6	30	Sil. Planar Trans. NPN like BSY95A. 2N706	0·55
U 7	16	Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000	0·55
U 8	50	Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0·55
U 9	20	Mixed Voltages, 1 Watt Zener Diodes	0·55
U10	20	BAY50 charge storage Diodes DO-7 Glass	0·55
U11	25	PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	0·55
U12	12	Silicon Rectifiers Epoxy 500mA up to 800 PIV	0·55
U13	30	PNP-NPN Sil. Transistors OC200 & 2S 104	0·55
U14	150	Mixed Silicon and Germanium Diodes	0·55
U15	25	NPN Sil. Planar Trans. TO-5 like BFY51, 2N697	0·55
U16	10	3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0·55
U17	30	Germanium PNP AF Transistors TO-5 like ACY 17-22	0·55
U18	8	6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0·55
U19	25	Silicon NPN Transistors like BC108	0·55
U20	12	1·5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0·55
U21	30	AF. Germanium Alloy Transistors 2G300 Series & OC71	0·55
U23	30	MADT's like MHz Series PNP Transistors	0·55
U24	20	Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0·55
U25	25	300MHz NPN Silicon Transistors 2N708, BSY27	0·55
U26	30	Fast Switching Silicon Diodes like IN914 Micro-Min.	0·55
U27	12	NPN Germanium AF Transistors TO-1 like AC127	0·50
U29	10	1 Amp SCR's TO-5 can, up to 600 PIV CR81/25-600	1·15
U30	15	Plastic Silicon Planar Trans. NPN 2N2926	0·55
U31	20	Silicon Planar Plastic NPN Trans. Low Noise Amp 2N3707	0·55
U32	25	Zener Diodes 400mW DO-7 case 3–18 volts mixed	0·55
U33	15	Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0·55
U34	30	Silicon PNP Alloy Trans. TO-5 BCY26 2S302/4	0·55
U35	25	Silicon Planar Transistors PNP TO-18 2N2906	0·55
U36	25	Silicon Planar NPN Transistors TO-5 BFY50/51/52	0·55
U37	30	Silicon Alloy Transistors SO-2 PNP OC200, 2S322	0·55
U38	20	Fast Switching Silicon Trans. NPN 400MHz 2N3011	0·55
U39	30	RF. Germ. PNP Transistors 2N1303/5 TO-5	0·55
U40	10	Dual Transistors 6 lead TO-5 2N2060	0·55
U41	25	RF Germanium Transistors TO-5, OC45, NKT72	0·55
U42	10	VHF Germanium PNP Transistors TO-1 NKT667, AF117	0·55
U43	25	Sil. Trans. Plastic TO-18 A.F. BC113/114	0·55
U44	20	Sil. Trans. Plastic TO-5 BC115/NPN	0·55
U45	7	3A SCR. TO66 up to 600PIV	1·10

Code Nos. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

QUALITY TESTED SEMICONDUCTORS

Pak No.			Price £p
Q 1	20	Red spot transistors *pnp*	0·55
Q 2	16	White spot R.F. transistors *pnp*	0·55
Q 3	4	OC77 type transistors	0·55
Q 4	6	Matched transistors OC44/45/81/81D	0·55
Q 5	4	OC75 transistors	0·55
Q 6	5	OC72 transistors	0·55
Q 7	4	AC128 transistors *pnp* high gain	0·55
Q 8	4	AC126 transistors *pnp*	0·55
Q 9	7	OC81 type transistors	0·55
Q10	7	OC71 type transistors	0·55
Q11	2	AC127/128 Complementary pairs *pnp/npn*	0·55
Q12	3	AF116 type transistors	0·55
Q13	3	AF117 type transistors	0·55
Q14	3	OC171 H.F. type transistors	0·55
Q15	7	2N2926 Sil. Epoxy transistors mixed colours	0·55
Q16	2	GET880 low noise Germanium transistors	0·55
Q17	5	*npn* 2 × ST.141 & 3 × ST.140	0·55
Q18	4	MADT'S 2 × MAT 100 & 2 × MAT 120	0·55
Q19	3	MADT'S 2 × MAT 101 & 1 × MAT 121	0·55
Q20	4	OC44 Germanium transistors A.F.	0·55
Q21	4	AC127 *npn* Germanium transistors	0·55
Q22	20	NKT transistors A.F. R.F. coded	0·55
Q23	10	OA202 Silicon diodes sub-min.	0·55
Q24	8	OA81 diodes	0·55
Q25	15	IN914 Silicon diodes 75PIV 75mA	0·55
Q26	8	OA95 Germanium diodes sub-min IN69	0·55
Q27	2	10A 600 PIV Silicon rectifiers IS425R	0·55
Q28	2	Silicon power rectifiers BYZ13	0·55
Q29	4	Silicon transistors 2 × 2N696, 1 × 2N697, 1 × 2N698	0·55
Q30	7	Silicon switch transistors 2N706 *npn*	0·55
Q31	6	Silicon switch transistors 2N708, *npn*	0·55
Q32	3	*pnp* Silicon transistors 2 × 2N1131, 1 × 2N1132	0·55
Q33	3	Silicon *npn* transistors 2N1711	0·55
Q34	7	Silicon *npn* transistors 2N2369, 500MHz (code P397)	0·55
Q35	3	Silicon *pnp* TO-5. 2 × 2N2904 & 1 × 2N2905	0·55
Q36	7	2N3646 TO-18 plastic 300MHz *npn*	0·55
Q37	3	2N3053 *npn* Silicon transistors	0·55
Q38	7	*pnp* transistors 4 × 2N3703, 3 × 2N3702	0·55

ELECTRONIC SLIDE-RULE

The MK Slide Rule, designed to simplify Electronic calculations features the following scales:—Conversion of Frequency and Wavelength. Calculation of L, C and fo of Tuned Circuits. Reactance and Self Inductance. Area of Circles. Volume of Cylinders. Resistance of Conductors. Weight of Conductors. Decibel Calculations. Angle Functions. Natural Logs and "e" Functions. Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and Hp. A must for every electronic engineer and enthusiast. Size: 2cm × 4cm. Complete with case and instructions. Price each: £3·69

SILICON PHOTO TRANSISTOR. TO-18 Lens end NPN Sim. to BP × 25 and P21. BRAND NEW. Full data available. Fully guaranteed. Qty. 1·24 25·99 100 up Price each 69p 44p 38p

F.E.T.'S

2N3819	31p	2N5458	35p
2N3820	55p	2N5459	44p
2N3821	34p	BFW10	66p
2N3823	31p	MPF105	41p

NEW 6TH EDITION

TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 99p each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX STOCK. SEND FOR FREE LIST.

INTEGRATED CIRCUIT PAKS

Manufacturers' "Fall Outs" which include Functional and Part-Functional Units. These are classed as 'out-of-spec' from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	=12×7400	0·55	UIC46	=5×7446	0·55	UIC86	=5×7486	0·55
UIC01	=12×7401	0·55	UIC47	=5×7447	0·55	UIC90	=5×7490	0·55
UIC02	=12×7402	0·55	UIC48	=5×7448	0·55	UIC91	=5×7491	0·55
UIC03	=12×7403	0·55	UIC50	=12×7450	0·55	UIC92	=5×7492	0·55
UIC04	=12×7404	0·55	UIC51	=12×7451	0·55	UIC93	=5×7493	0·55
UIC05	=12×7405	0·55	UIC53	=12×7453	0·55	UIC94	=5×7494	0·55
UIC06	=8×7406	0·55	UIC54	=12×7454	0·55	UIC95	=5×7495	0·55
UIC07	=8×7407	0·55	UIC60	=12×7460	0·55	UIC96	=5×7496	0·55
UIC10	=12×7410	0·55	UIC70	=8×7470	0·55	UIC100	=5×74100	0·55
UIC13	=8×7413	0·55	UIC72	=8×7472	0·55	UIC121	=5×74121	0·55
UIC20	=12×7420	0·55	UIC73	=8×7473	0·55	UIC141	=5×74141	0·55
UIC30	=12×7430	0·55	UIC74	=8×7474	0·55	UIC151	=5×74151	0·55
UIC40	=12×7440	0·55	UIC75	=8×7475	0·55	UIC154	=5×74154	0·55
UIC41	=5×7441	0·55	UIC76	=8×7476	0·55	UIC193	=5×74193	0·55
UIC42	=5×7442	0·55	UIC80	=5×7480	0·55	UIC199	=5×74199	0·55
UIC43	=5×7443	0·55	UIC81	=5×7481	0·55			
UIC44	=5×7444	0·55	UIC82	=5×7482	0·55	UICXI	=25 Assorted	74's 1·65
UIC45	=5×7445	0·55	UIC83	=5×7483	0·55			

Paks cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC X1.

BI–PAKS NEW COMPONENT SHOP NOW OPEN WITH A WIDE RANGE OF ELECTRONIC COMPONENTS AND ACCESSORIES AT COMPETITIVE PRICES—

18 BALDOCK STREET (A10), WARE, HERTS.
TEL. (STD 0920) 61593
open MON.-SAT. 9.15 a.m. to 6 p.m., FRIDAY until 8 p.m.

All mail orders please add 10p post and packing.
Send all orders to BI-PAK, P.O. BOX 6, WARE, HERTS.

-the lowest prices!

74 Series T.T.L. I.C's

BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS



	1	25	100+
SN7400	0·17	0·16	0·13
SN7401	0·17	0·16	0·13
SN7402	0·17	0·16	0·13
SN7403	0·17	0·16	0·13
SN7404	0·17	0·16	0·13
SN7405	0·17	0·16	0·13
SN7406	0·39	0·34	0·31
SN7407	0·39	0·34	0·31
SN7408	0·20	0·14	0·18
SN7409	0·20	0·19	0·18
SN7410	0·17	0·16	0·13
SN7411	0·28	0·24	0·26
SN7412	0·39	0·34	0·31
SN7413	0·32	0·29	0·27
SN7416	0·48	0·44	0·42
SN7417	0·48	0·44	0·42
SN7420	0·17	0·16	0·13
SN7422	0·55	0·53	0·50
SN7423	0·55	0·53	0·50
SN7425	0·55	0·53	0·50
SN7426	0·50	0·46	0·44
SN7427	0·50	0·46	0·44
SN7428	0·77	0·72	0·66
SN7430	0·17	0·16	0·13
SN7432	0·50	0·46	0·44
SN7433	0·88	0·83	0·77
SN7437	0·71	0·68	0·66
SN7438	0·71	0·68	0·66
SN7440	0·17	0·16	0·13
SN7441	0·74	0·71	0·64
SN7442	0·74	0·71	0·64
SN7443	1·43	1·88	1·32
SN7444	1·43	1·88	1·32
SN7445	1·98	1·95	1·93
SN7446	1·07	1·04	0·97
SN7447	1·10	1·07	1·05
SN7448	1·10	1·07	1·05
SN7450	0·17	0·16	0·13
SN7451	0·17	0·16	0·13
SN7453	0·17	0·16	0·13
SN7454	0·17	0·16	0·13
SN7460	0·17	0·16	0·13
SN7470	0·32	0·29	0·27
SN7472	0·32	0·29	0·27
SN7473	0·41	0·39	0·35
SN7474	0·41	0·39	0·35
SN7475	0·50	0·48	0·46
SN7476	0·44	0·43	0·43
SN7480	0·74	0·71	0·64
SN7481	1·32	1·27	1·21
SN7482	0·96	0·95	0·94
SN7483	1·21	1·16	1·05
SN7484	1·10	1·05	0·99
SN7485	3·98	3·85	3·74

	1	25	100+
SN7486	0·35	0·34	0·33
SN7489	6·05	5·78	5·50
SN7490	0·74	0·71	0·64
SN7491	1·10	1·05	0·99
SN7492	0·74	0·71	0·64
SN7493	0·74	0·71	0·64
SN7494	0·85	0·82	0·75
SN7495	0·35	0·82	0·75
SN7496	0·86	0·93	0·86
SN74100	1·82	1·76	1·71
SN74104	1·07	1·04	0·97
SN74105	1·07	1·04	0·97
SN74107	0·44	0·42	0·40
SN74110	0·51	0·59	0·55
SN74111	1·38	1·27	1·21
SN74118	1·10	1·05	0·99
SN74119	1·40	1·38	1·21
SN74121	0·44	0·41	0·38
SN74122	1·54	1·43	1·21
SN74123	3·08	2·97	2·86
SN74141	0·74	0·71	0·64
SN74145	1·65	1·54	1·43
SN74150	3·30	2·97	2·75
SN74151	1·10	1·05	0·99
SN74153	1·32	1·21	1·05
SN74154	1·98	1·87	1·76
SN74155	1·54	1·43	1·32
SN74156	1·54	1·43	1·32
SN74157	2·09	1·98	1·87
SN74160	1·98	1·87	1·76
SN74161	1·98	1·87	1·76
SN74162	4·40	4·13	3·85
SN74163	4·40	4·13	3·85
SN74164	2·42	2·37	2·31
SN74165	2·48	2·42	2·37
SN74166	3·85	3·58	3·30
SN74174	2·53	2·42	2·31
SN74175	1·76	1·65	1·54
SN74176	2·75	2·64	2·53
SN74177	2·75	2·64	2·53
SN74180	2·20	1·76	1·54
SN74181	6·05	5·50	5·23
SN74182	2·20	1·98	1·76
SN74184	3·85	3·58	3·30
SN74190	2·15	2·09	2·04
SN74191	2·09	2·04	1·98
SN74192	2·15	2·09	2·04
SN74193	2·20	1·98	1·93
SN74194	2·97	2·86	2·75
SN74195	2·20	2·09	1·98
SN74196	1·98	1·87	1·76
SN74197	1·98	1·87	1·76
SN74198	6·05	5·50	4·95
SN74199	6·05	5·50	4·95

LINEAR I.C.'s—FULL SPEC.

Type No.	Price 1–24	25–99	100+
BP201C—SL201C	0·70	0·59	0·50
BP710C—SL701C	0·70	0·55	0·50
BP702C—SL702C	0·70	0·55	0·50
BP702—72702	0·59	0·50	0·44
BP709—72709	0·40	0·39	0·33
BP709P—μA709C	0·40	0·38	0·33
BP710—72710	0·40	0·46	0·44
BP711—μA711	0·40	0·48	0·44
BP741—72741	0·55	0·50	0·45
μA703C	0·31	0·29	0·27
TAA263	0·77	0·66	0·61
TAA293	0·99	0·83	0·77
TAA350	1·87	1·74	1·65
EA1000	2·90		

ROCK BOTTOM PRICES
LOGIC DTL 930 Series I.C's

Type No.	Price 1–24	25–99	100 up
BP930	0·13	0·12	0·11
BP932	0·14	0·13	0·12
BP933	0·14	0·13	0·12
BP935	0·14	0·13	0·12
BP936	0·14	0·13	0·12
BP944	0·14	0·13	0·12
BP945	0·28	0·27	0·24
BP946	0·13	0·12	0·11
BP948	0·28	0·27	0·24
BP951	0·72	0·66	0·61
BP962	0·13	0·12	0·11
BP9093	0·44	0·42	0·39
BP9094	0·44	0·42	0·39
BP9097	0·44	0·42	0·39
BP9099	0·44	0·42	0·39

NUMERICAL INDICATOR TUBES



MODEL	CD66	GR116	3015F Minitron
Anode Voltage (Vdc)	170min	175min	5
Cathode Current (mA)	2·3	14	8
Numerical Height (mm)	16	13	9
Tube Height (mm)	47	32	22
Tube Diameter (mm)	19	13	12 wide
I.C. Driver Rec.	BP41 or 141	BP41 or 141	BP47
PRICE EACH	£1·87	£1·70	£2·09

All indicators 0·9 + Decimal point. All side viewing. Full data for all types available on request.

RTL MICROLOGIC CIRCUITS

	Price each 1–24	25–99	100 up
Epoxy TO-5 case μL900 Buffer	38p	36p	29p
μL914 Dual 2i/p gate	38p	36p	29p
μL923 J-K flip-flop	55p	51p	49p

Date and Circuits Booklet for IC's Price 8p.

DUAL IN LINE SOCKETS

(14 & 16 Lead)	1–24	25–99	100+
TSO14	0·33	0·30	0·28
TSO16 16 pin type	0·34	0·35	0·33
BPS14 14 pin type (low cost)	0·17	0·15	0·12
BPS16 16 pin type (low cost)	0·16½	0·16	0·13

BI-PAK DO IT AGAIN!

50W pk 25w (RMS)

0·1% DISTORTION!
HI-FI AUDIO AMPLIFIER



THE AL50

ONLY **£3·58 each**

* Frequency Response 15Hz to 100,000—1dB.
* Load—3, 4, 8 or 16 ohms.
* Distortion—better than ·1% at 1KHz.
* Signal to noise ratio 80dB.
* Supply voltage 10–35 Volts.
* Overall size 63mm × 105mm × 13mm.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and AL50 was conceived to fill the need for all your A.F. amplification needs.
FULLY BUILT—TESTED—GUARANTEED.

STABILISED POWER MODULE SPM80



AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1·5 amps at 35 volts. Size: 68mm × 105mm × 30mm.
These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Disco Systems, Public Address, Intercom Units, etc. Handbook available, 10p **PRICE £3·25**

TRANSFORMER BMT80 £2·15 p. & p. 28p

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages.
Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.



SPECIFICATION

Frequency Response	20Hz — 20kHz ± 1dB
Harmonic Distortion	better than 0·1%
Inputs: 1. Tape Head	1·25mV into 50K Ω
2. Radio, Tuner	35mV into 50K Ω
3. Magnetic P.U.	1·5mV into 50K Ω
All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB from 20Hz to 20kHz.	
Bass Control	±15dB at 20Hz
Treble Control	±15dB at 20kHz
Filters: Rumble (High Pass)	100Hz
Scratch (Low Pass)	8kHz
Signal/Noise Ratio	better than —65dB
Input overload	+26dB
Supply	+35 volts at 20mA
Dimensions	292mm × 82mm × 35m

ONLY £13·15

SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £25·30 FREE p. & p.

All prices quoted in new pence *Giro No. 388-7006*
Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 10p. Overseas add extra for airmail
Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

parts for PRACTICAL ELECTRONICS projects

After many requests, Electro Spares are now supplying lists of components for **all** the projects featured in "Practical Electronics", commencing with May 1973 issue. Just forward an S.A.E. (preferably 9" × 4" minimum), and state which project is of interest to you—we will forward an individually priced list of the components required.

No need to buy a full kit—you need only purchase the parts you require at any one time.

All Electro Spares supplied components are new, branded products of reputable manufacturers, and carry full makers' guarantee.

We regret we cannot supply lists for projects published **before** May 1973 issue.

"ONE SOURCE" BUYING MAKES SENSE—
IT CAN SAVE YOU TIME, MONEY AND POSTAGE

"p.e." f.m. varicap stereo tuner

Electro Spares offer a kit of high quality parts to the published specification for this remarkable tuner, featured in "Practical Electronics", May 1973.

Features include pushbutton "Spot On" tuning, with up to 5 pre-set stations (no difficult tuning dial and drive cord). Easy, "no problem" construction, requiring only a few simple setting up adjustments with a D.C. Voltmeter. Uses **NEW** pre-set modules for R.F. and I.F. circuits—no circuit alignment. High efficiency integrated circuit Phase Lock Loop Decoder for perfect stereo reception, with stereo lamp indicator.

Fibre Glass P.C. Board, neat slim line cabinet, with brushed aluminium front panel, push buttons, etc., etc.

IDEAL FOR USE WITH THE "TEXAN", "P.E. GEMINI" AND ANY GOOD QUALITY STEREO AMPLIFIER.

Please send S.A.E. for full details.

"p.e. gemini" stereo amplifier

QUALITY HI-FI FOR THE HOME CONSTRUCTOR

30 Watts (R.M.S.) per Channel into 8 ohms!

Total Harmonic Distortion 0.02%!

Frequency Response (−3 dB) 20Hz — 100kHz!

We are still continuing to supply components for this fabulous amplifier, which is now recognised as practically the ultimate in High Fidelity. We know of no better unit for the home constructor, and can supply a booklet, containing full specification, complete constructional information, wiring diagrams, fault finding guide, etc., etc., price 55p plus 4p postage.

Our **new, low** comprehensive price list is supplied with each booklet, or supplied separately on receipt of large S.A.E.

FOR PEOPLE WHO REQUIRE THE **BEST**—
IT HAS TO BE THE **"p.e. gemini"**

NOTE OUR NEW ADDRESS—WITH NEW MAIL ORDER DEPARTMENT FOR QUICK EFFICIENT SERVICE.

PLEASE PAY US A CALL—VISITORS WELCOME—EASY PARKING.


Electro-Spares

288 Ecclesall Road
Sheffield S11 8PE
Tel.: Sheffield 668888

"THE COMPONENT CENTRE OF THE NORTH"

PSYCHEDELIC LIGHTING UNIT IN KIT FORM

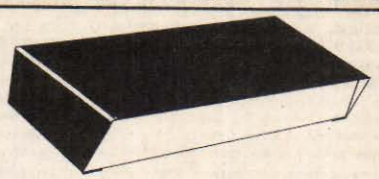Make this fascinating three-channel unit from a kit which contains all components needed to produce a reliable and entertaining display. Takes its drive from the speaker terminals of a record player, tape recorder or portable radio. Will provide a brilliant 2kW of light, using normal 240 volt coloured lamps. Price per kit, **£10·40**



METAL CABINETS

These attractive steel cabinets are PVC covered in a range of colours, and offer an economically priced unit for the home constructor. The chassis, which has a white satin PVC finish, provides an easily accessible building area, with an integral fascia panel. The cabinet is supplied complete with stick-on feet.

Colours available include Green, Grey, Black, White and Blue. Every effort will be made to supply a selected colour, but please give alternatives if possible.

Approximate size in inches			Price
l.	*w.*	*d.*	
8	6	3	**£1·60**
11	6¼	3	**£2·04**

Other sizes to special order. Please send S.A.E. for quotation.

FIXED VOLTAGE REGULATORS

TO3 case. Gives stabilised supply. MVR 5 V, MVR 12 V, MVR15 V. All priced at **£1·65**

VEROBOARD

	0·1	0·15
2½ × 1in	7p	7p
2½ × 3¾in	27p	20p
2½ × 5in	29p	29p
3¾ × 3¾in	29p	29p
3¾ × 5in	31p	32p

PRINTED CIRCUIT CAPACITORS

Electrolytic, low voltage, small size. Available in the following uF/V. 0·47/63, 1/63, 2·2/63, 4·7/40, 10/63, 22/40, 100/10, **9p** each; 47/40, 100/63, 220/40, 470/16, **15p** each; 1,000/16, **18p** each.

Our CATALOGUE, priced at 25p post free, shows the majority of the R.S. range of professional components. Most are available by return of post. Prices include VAT. All orders over 50p POST FREE. S.A.E. with all queries please.

CELECTRON-E

P.O. Box No. 1, Llantwit Major, Glamorgan, Wales CF6 9YN



become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

RAPY

free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
P.O. BOX 156, JERSEY

NAME : _____

ADDRESS : _____ EB73

_____ BLOCK CAPS please

Build yourself a TRANSISTOR RADIO

WITH AFTER SALES SERVICE

ROAMER 10 WITH VHF INCLUDING AIRCRAFT



10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS ALSO AIRCRAFT BAND.

Built-in ferrite rod aerial for MW/LW. Retractable, chrome plated 7 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Fine tone moving coil speaker. Ganged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in × 7in × 4in.

Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts).

TOTAL BUILDING COSTS **£9·35** P.P. & INS. 52p (OVERSEAS P. & P. £1·05)

ROAMER EIGHT Mk. I

NOW WITH VARIABLE TONE CONTROL



7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Retractable chrome plated telescopic aerial for short waves. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in × 7in × 4in approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£7·68** P. P. & INS. 47p (OVERSEAS P. & P. £1·05)


ROAMER SEVEN Mk. IV



7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Extra medium waveband provides easier tuning of Radio Luxembourg, etc. Built-in ferrite rod aerial for MW and LW. Retractable 4 section 24in chrome plated telescopic aerial for SW. Socket for car aerial. Powerful push-pull output. 7 transistors and 2 diodes, including micro-alloy R.F. transistors. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9in × 7in × 4in approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£6·58** P. P. & INS. 47p (OVERSEAS P. & P. £1·05)

ROAMER SIX

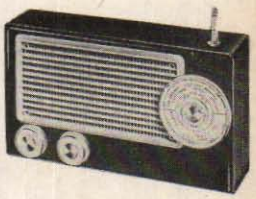

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 9 stages—6 transistors and 2 diodes including micro-alloy R.F. transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9in × 5¼in × 2¼in approx. Easy build plans and parts price list 25p (FREE with parts).

TOTAL BUILDING COSTS **£4·38** P. P. & INS. 31p (OVERSEAS P. & P. £1·05)

POCKET FIVE



3 TUNABLE WAVEBANDS: MW, LW, TRAWLER BAND WITH EXTENDED MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5¼in × 1¾in × 3¾in. Easy build plans and parts price list 10p (FREE with parts).

TOTAL BUILDING COSTS **£2·50** P. P. & INS. 24p (OVERSEAS P. & P. 65p)

TRANSONA FIVE




5 TRANSISTORS AND 2 DIODES

3 TUNABLE WAVE BANDS: MW, LW AND TRAWLER BAND. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6¼in × 4¼in × 1¼in. Easy build plans and parts price list 10p (FREE with parts).

TOTAL BUILDING COSTS **£2·75** P. P. & INS. 25p (OVERSEAS P. & P. 65p)

TRANS EIGHT

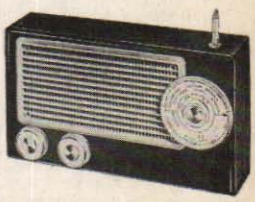

8 TRANSISTORS AND 3 DIODES

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in × 5¼in × 2¼in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£4·95** P. P. & INS. 33p (OVERSEAS P. & P. £1·05)

"EDU-KIT"



BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT. Components include: Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine tone moving coil Speaker: Terminal Strip: Ferrite Rod Aerial: 2 Plugs and Sockets: Battery Clips: 4 Tag Boards Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three ¼in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and easy build plans 25p (FREE with parts).

ALL PARTS INCLUDING CASE AND PLANS **£6·05** P. P. & INS. 33p (OVERSEAS P.&P. £1·05)

FULL AFTER SALES SERVICE

★ Callers side entrance "Lavell" Shop
★ Open 10-1, 2.30-4.30 Monday-Friday, 9-12 Saturday
★ PLEASE NOTE: ALL PRICES INCLUDE V.A.T.

RADIO EXCHANGE LTD

61a HIGH ST., BEDFORD MK40 1SA. Tel. 0234 52367

Reg. no. 788372

I enclose £..... please send items marked

ROAMER TEN	☐	ROAMER SEVEN	☐
ROAMER EIGHT	☐	TRANS EIGHT	☐
TRANSONA FIVE	☐	ROAMER SIX	☐
POCKET FIVE	☐	EDU-KIT	☐

Parts price list and plans for.....

Name .....

Address .....

..... P.E. 55

UNISOUND FOR THE NEW SOUN



AT **£26·12** INC. VAT

It's the RT-VC system that screws together to save you pounds! Unisound comprises two superb speakers and an amplifier/record deck plinth—all beautifully finished in simulated teak. The stereo amplifier (4 watts per channel into 8 ohms) is based on the famous Mullard Unilex system brought up-to-date by RTVC using integrated circuits. Turntable is the proven Garrard 2025TC complete with stereo cartridge and tinted acrylic cover. Speakers are big EMI Twin-cone units all ready for mounting in their elegant cabinets, which simply need screwing and glueing together. Easy step-by-step instructions. **£26·12 complete plus £1·40 packing + £1·40 post.** Diamond Stylus £1·37 extra. Stereo headphones with adaptor £4·40 extra. Send for leaflet.

AN RTVC EXCLUSIVE DESIGN



UNISOUND MODULES ONLY £7·64 + 55p. p. & p.
For the man who wants to design his own stereo—here's your chance to start, with Unisound—pre-amp, power amplifier and control panel. No soldering—just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum.

VISCOUNT III—NOW 20 W

If you can sol
on printed circuit boa
you can build this push-butt
car radio kit. It's simple—j
follow the step-by-step instructio

THE TOURIST PUSH-BUTTON CAR RADIO KIT

AN INCREDIBLE BUY

ONLY FROM RTVC




The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles. It covers the full medium and long wave bands. It is permeability tuned and sturdily constructed. Output is a full 2·5 watts into an 8 ohms speaker. But the Tourist PB will operate into any loudspeaker from 8 to 15 ohms.
Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modulised IF stages which are pre-aligned before despatch. As well as electronic components this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire.
The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale. Chassis size is: 7in wide, 2in high and 4½ in deep.

* Circuit diagram and comprehensive instructions 55p free with parts.

* Fully retractable and lockable car aerial £1 post paid.

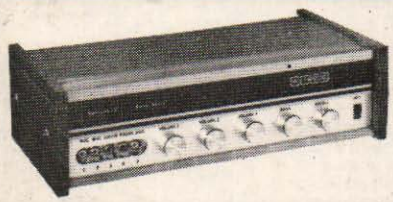CAR RADIO KIT £6·60 p. and p. 55p.
Speaker with baffle and fixing strips £1·
27p p. & p., post free if bought with the
Send stamped addressed envelope
leaflet.



RELIANT MkIV

*5 Electrically Mixed inputs. *3 Individual Mixing controls. *Separate bass and treble contro common to all 5 inputs. *Mixer employing F.E.T. (Field Effect Transistors). *Solid State Circuitr *Attractive Styling. INPUTS 1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic. or Guitar 8m Inputs. 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram. Tuner, Monitor, Organ, etc.) All 250mV sensitivity. Output 20 watts into 8 ohms (suitable for 15 ohms). Size approx. 12¼ × 6 × 3¼ ins.

£13·50 p. & p. 60p

SOUND 50



45 WATT MONO AMPLIFIER. Ideal for Disco. Output Power: 45 watts R.M.S. (Sine Wave) Frequency Response 3dB points 30Hz and 18KHz. Total Distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K. Size: 19¼ × 10¼ × 8ins. Amplifier £31·35 plus £1·65 p. and p. **£31·35** (inc. VAT)



PE TAPE LINK CONSTRUCTORS
Suitable 3 speed deck, less heads. Ca up to 7ins. spools. 2 AC mains. Unused store soiled hence warranty. £1 p. & p. £4·

ALL PRICES INCLUDE VAT

ts per channel RMS

VISCOUNT III AUDIO SYSTEM £49 COMPLETE

20 + 20W r.m.s. 40Hz to 40kHz ± 3dB. Total distortion at 10W at 1kHz–0·1%. This is real value for money! We have designed 2 systems and the heart of them both is the Viscount III amplifier. A unit of great eye appeal with teak finished cabinet. FET's (Field effect, transistors) are incorporated on the input stages, just like top priced units. FET's give you more of the signal you want and almost none of the hiss you don't. Both units have output sockets for headphones and tape recorder.

For both systems we have chosen the famous Garrard SP25 Mk. III deck, with fitted magnetic cartridge, which comes complete with simulated teak plinth and tinted acrylic cover.

The exclusive Duo loudspeaker systems are incomparable for quality within their price range. Large speakers in extremely substantial cabinets. There's a choice of the Duo II's for the smaller room or the big Duo III's for real bass response.

PRICES: SYSTEM 1

Viscount III R 101 amplifier	£24·20 + £1 p & p
2 Duo Type II speakers	£14·00 + £2·20 p & p
Garrard SP25 Mk. III with MAG. cartridge plinth & cover	£18·00 + £1·75 p & p
total	£56·20

Available complete for only £49·00 £3·50 p. & p.

PRICES: SYSTEM 2

Viscount R 101 amplifier	£24·20 + £1 p & p
2 Duo Type III speakers	£32·00 + £3·30 p & p
Garrard SP25 Mk. III with MAG. cartridge plinth & cover	£18·00 + £1·75 p & p
total	£74·20

Available complete for £65·00 £4 p. & p.





EAKERS: Duo Type II Size approx. 17in × 10¾in × 6¾in. Drive unit 13in × 8in with parasitic eeter. Max. power 10 watts 8 ohms. Simulated Teak cabinet. **£14·00** a pair (inc. VAT), £2·20 p. & p. o Type III Size approx. 23¾in × 11¾in × 9¾in. Drive unit 13¾in × 8¾in with HF speaker. Max. power watts, 8 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. **£32·00** a pair (inc. VAT) + £3·30 p. & p.
ECIFICATION R102: 20 watts per channel into 8 ohms (suitable 8–16 ohms.) Total distortion at V 1kHz at 0·1%. P.U.1 (for ceramic cartridges) 180mV into 3 Meg. P.U.2 (for magnetic cartridges) V at 1kHz into 47K equalised within 1dB R.I.A.A. *Radio* 180mV into 220K. (Sensitivities given at full wer.) Tape out facilities: headphone socket, power out 250mW per channel. Signal-to-noise ratio: controls at max.) 58dB. Cross talk better than —40dB on all inputs. Size approx. 13¾in × 9in × n. Send S.A.E. for fully illustrated brochure. 12 months' written guarantee.

NLY FROM US

ES OF OPENING: Acton—Mon.–Sat. 9.30–5.
ed all day Wed.
ware Rd.—Mon.–Sat. 9.30–5. Closed all day Thurs.

VISIT OUR SHOWROOMS


R T V C

Radio and TV Components (Acton) Ltd.
21d High Street, Acton, London W3 6NG
323 Edgware Road, London W2
Mail orders to Acton. Terms C.W.O.
Goods not despatched outside U.K.
All enquiries S.A.E.

TERMS Retail mail order subject to £1·00 minimum order.
Cash with order only. Trade and educational establishments M/AC on application (minimum £5·00).
Postage 10p inland, 25p, Europe.
GUARANTEE: All goods carry full manufacturer's warranty. Get in touch today for a complete run-down of devices available from SCS (include SAE).

SCS COMPONENTS, P.O. Box 26, Wembley, Middlesex HA0 1YY
The 'Professional' Amateur Supplier

device of the month ZN414

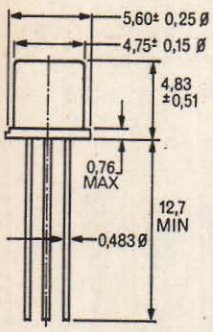

The Ferranti ZN414 is a complete a.m. radio circuit which operates from 1.1 to 1.8 volts and requires only battery, earphones and antenna plus a tuning capacitor and two decoupling capacitors. The ZN414 features: medium and long waveband, good stability on assembly, no setting up of IF coils, plus much more.

a complete a.m radio circuit for just £1·20 + VAT

compatible device MFC 4000B



The Motorola ¼-Watt Audio Amplifier is designed for the output stage of battery powered portable radios.

* 250 mW of Audio Output Power
* Low Standby Current— 3·5 mA typical
* Low Harmonic Distortion
* Reduces Component Count in Portable Radios by Two Transformers and Two Transistors
* Eliminates Costly Component Matching Requirements

motorola 1/4 watt audio amplifier MFC4000 — **50p + VAT**

FIRST TIME EVER at £42·50. Solartron CD7115S2 Double Beam Oscilloscope d.c.—9MHz; 3mV/cm; trigger delay; crystal calibrator; 4in flat faced tube. In good working condition. Carriage £1·50.

HARTLEY TYPE 13A. ONLY **£18.** Double Beam Oscilloscope. TB2Hz–750kHz. Band width 5·5MHz. Sensitivity 33Mv/cm. Calibration markers 100kHz and 1MHz. A completely reliable general purpose oscilloscope. Supplied with CIRCUIT DIAGRAM and Mains lead. Carr. **£1·50.**
As above. Complete with all accessories. **£25.** Carr. £1·50.
Many other oscilloscopes available.

GRATICULES. 12cm × 14cm in High Quality plastic. **30p** each. P. & P. 5p.

MODERN TELEPHONES type 706. Two tone grey, **£3·75** each. The same but black, **£2·75** each. P. & P. 25p each.
Also **TOPAZ YELLOW £4·50** each. P. & P. 25p.

STANDARD GPO DIAL TELEPHONE (black) with internal bell, **87p** each. P. & P. 50p. Two for **£1·50.** P. & P. 75p. All telephones complete with bell and dial.

20Hz to 200kHz WB SINE AND SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use. 9V supply required. **£6·85** each. P. & P. 25p. (Not cased, not calibrated.)

WOBBULATOR. Sweeps 8 to 45MHz ready to use. 6·3V a.c. required. **£9** each. P. & P. 25p. (Not cased, not calibrated.)

CAPACITOR PACK. 50 Brand new components only **50p.** P. & P. 17p.

5 MOVING COIL METERS various. **£2.** P. & P. 37p.

POTS—10 different values. Brand new—**50p.** P. & P. 17p.

COMPONENT PACK consisting of 2·2 pole 2 amp push on/off switches; 4 pots, various, brand new; 250 resistors ¼ and ½ watt, many high stabs, etc. Fine value at **50p** per pack. P. & P. 17p.

P.C.B. PACKS S & D. Quantity 2sqft —no tiny pieces. **50p** plus P. & P. 20p.

FIBRE GLASS as above **£1** plus P. & P. 20p.

5 CRYSTALS 70 to 90kHz. Our choice, **50p.** P. & P. 15p.

Matched pairs, **50p** per pair. P. & P. 15p.

TRIMMER PACK. 2 Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min. strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW, **25p** the lot. P. & P. 10p.

ELECTRONIC TIMER UNITS —wall or bench mounting—2 Hybrid timer boards may be removed leaving excellent 12V battery charger; d.c. Power supply, etc. Price only **£2·50** incl. carriage.

LIGHT EMITTING DIODES (Red) from Hewlett-Packard. Brand New **38p** each. Holder 1p each. Information 5p.

PHOTOCELL equ. OCP71, **13p** each.

PHOTO-RESIST type Clare 703. Two for **50p.**

AMERICAN OSCILLOSCOPE type USM24. A 10 meg scope—all min. valves complete with circuit diagram. Mains input 115 volt 50 cycles therefore **£20.** Carr. £1·50.

MOTOR MIN. SYNCHRONOUS. Size 1⅞" × 2" × ⅞", 240V operation, 3·6 RPM, **25p** each. P & P 5p.

DELIVERED TO YOUR DOOR 1 cwt of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY **£3·50.**

PLEASE ADD 10% V.A.T.

OPEN 9 a.m. to 7.30 p.m. ANY DAY

CHILTMEAD LTD
7/9 ARTHUR ROAD, READING, BERKS.
(rear Tech. College) Tel.: Reading 582605/65916

P.E. SOUND SYNTHESISER

Access
Buy it with Access

SIMPLY SEND EXACT DETAILS OF NAME AND NUMBER COPIED FROM THE FACE OF YOUR ACCESS CARD AND LEAVE THE REST TO US.

mini D.I.L.
741's
32p each

MAINS TRANSFORMER
2 × 30v SEC
WINDINGS @ 750mA
£3·75 each

We stock a full range of professional quality components as specified for this exciting project and many prices are **down.**
2% M.O. resistors now **3·2p** ea. 5% low noise carbon film **1·8p** ea. Cermet presets now **37·5p** ea. Full range of capacitors—Ceramic, Electrolytic, Polyester, 'Styrene, 'Carbonate, Silver Mica, etc. Modular hardware kits; Dual-Rail Regulated Power Supplies; Individual component/module kits from date of publication. P.C.B. for the exciting 'Hutchinson' Tone Control Module. Suppliers of 'Maxview' aerials.
Send **4p** stamp for up-to-date lists.
Attractive discounts on quantity purchases.

EATON AUDIO **P.O Box No. 3, ST. NEOTS HUNTINGDON PE19 3JB**

TERMS: MAIL ORDER ONLY. C.W.O. Cheques or crossed P.O. payable to Eaton Audio. Minimum order £2.
Where P. & P. charges are not shown please add 10p in the £1 to orders under £5. Orders over £5 will be sent free of P. & P.
All prices subject to V.A.T.

MAIL ORDERS: Some items have a postage and handling charge shown against them. Where p. & p. is not shown the charge is 13p for any selection. When both classes of goods are ordered the charge is 13p plus any p. & p. charges shown. (Overseas extra). Telephone 01-692 4412.

GARLAND BROS. LTD.

DEPTFORD BROADWAY, LONDON, SE8 4QN

ALL PRICES SHOWN INCLUDE V.A.T.

SWITCHES

Standard toggle switches: SW20—S.P.S.T., **20p**; SW21—D.P.D.T., **25½p.**

Miniature toggle switches: SW18—S.P.S.T., **51p**; SW19—D.P.D.T., **64p.**

Slider switches: SW3—D.P.D.T., **15½p.**

Miniature push button: SW1—S.P., **14½p.**

Foot operated switch: SW12—S.P.S.T., **46p.**

Door switch: SW14—S.P. Press for off, **20p.**


Wafer switches (rotary)—**26½p** each.
SW4—1 pole, 12 way.
SW5—2 pole, 6 way.
SW6—3 pole, 4 way.
SW7—4 pole, 2 way.
SW8—4 pole, 3 way.





GROOV-KLEEN

de luxe model 42, **£1·83.**

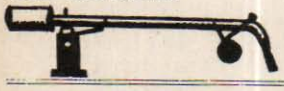

CRYSTAL MICROPHONE



A very neat, sensitive microphone for hand or table use. Complete with lead and 3·5 mm plug. **£1·00.**

PRE-AMPLIFIER

for mics. or guitars. On printed panel complete with standard jack socket. 9V d.c. Input 50 kΩ. Connection data supplied, **70p.**

LAMP FLASHERS 240V

Connect in series with lamp supply to flash approx. once per second.



Type B: 100W, **44p.**
Type C: 500W, **£1·36.**

EA 1000 BARGAIN

This popular **3W amplifier** complete with comprehensive data book showing circuits for mono., stereo, tone controls, power supply, etc. **Our price only £2·35,** plus 13p P. & P.



10 WATT AMPLIFIER module



Input: 30mV into 10k Ω for 10W, 40 — 16,000 Hz. Output: 3-8-16 Ω Power Supply 12V **£4·70** plus 24p P. & P.

PANEL NEON INDICATORS 240V

N1—Round, 9mm diameter, **33p.**
N2—Round, 18mm diameter, **28½p.**
N3—Oblong, 31 × 7mm, **32p.**

CASSETTE ACCESSORIES

Head cleaning tape, in library case, **54p.**

Cassette rack with teak ends, holds 10 cassettes in library cases. **72p,** plus 12p P. & P.

CONNECTING WIRE PACK

Contains 30 feet of stranded wire, 5 colours per pack. **11p.**


RESISTORS

Carbon film
All 5%, high-stability, E12 values. ¼W, 1p; ½W, 1½p; 1W, 4½p; 2W, 6½p.
Wire-wound
5W, 11p; 10W, 13p.

CONSOLE CASES

In plain aluminium, ideal for mixers, instruments, etc.

Type	W. in	A in	B in	C in	D in	Price	P.P.
GB20	8	9	3½	2	3	£1·56	33p
GB21	10	9	3½	2	3	£1·74	33p
GB22	12	9	3½	2	3	£1·89	33p

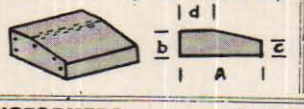

CAR-CASSETTE VOLTAGE STABILISERS

PU12 for Philips and similar cassette recorders. Gives 7½V stabilised output when connected to 12V + or— E car circuit. Fitted with 5 pin, 240° plug, **£3·55** plus 16p P. & P.



PU126, as above, but for 6V recorders. Fitted with coaxial power connector, **£3·55,** plus 16p P. & P.

MAINS POWER SUPPLY

PP75 for Philips and similar *cassette recorders.* Input 240V a.c.; output 7½V d.c. Fitted with 5 pin, 240° plug, **£2·15,** plus 16p P. & P.




ALUMINIUM BOXES

with lids and screws


Type	L.	W.	D.	Price	P. & P.
GB7*	5¼in	2¼in	1¼in	42p	16p
GB8*	4in	4in	1¼in	42p	16p
GB9*	4in	2¼in	1¼in	42p	14p
GB10*	5¼in	4in	1¼in	49p	19p
GB11	4in	2¼in	2in	42p	14p
GB12	3in	2in	1in	36p	15p
GB13	6in	4in	2in	57p	20p
GB14	7in	5in	2¼in	69p	21p
GB15	8in	6in	3in	89p	29p
GB16	10in	7in	3in	£1·00	29p

* These sizes fit standard veroboards

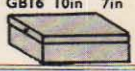

DYNAMIC MICROPHONE UD 130HL

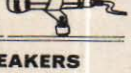This sensitive, quality microphone is uni-directional and is complete with mute switch and 20 feet of cable and plug. 100–12,000Hz. Dual impedance 600 Ω and 50k Ω.



£6·60, plus 24p P. & P.

SPEAKERS



2½in 8 Ω
2½in 8 Ω
2½in 80 Ω
All at **71p** each.

TAPE ERASER




erases a whole reel of tape in seconds. 240V a.c. Full instructions. **£2·20,** plus 22p P. & P.

SCREENED CABLES

Single for mics, audio leads, etc. **5½p** yd.
Twin, as above, common screen **10p** yd.
Stereo, two cores, individually screened **11p** yd.
Four core with common screen **23p** yd.
Four core, individually screened **30p** yd.
Coiled screened leads, 20 feet long **£1·05** each.

PLUGS

Car aerial	15½p
Co-axial	10p
D.I.N. 2 pin (speaker)	11p
D.I.N. 3 pin	15p
D.I.N. 4 pin	15½p
D.I.N. 5 pin, 180°	14½p
D.I.N. 5 pin, 240°	16½p
D.I.N. 6 pin	16½p
Jack, 2½mm unscreened	10p
Jack, 2½mm screened	11p
Jack, 3½mm unscreened	9p
Jack, 3½mm screened	13p
Jack, ¼in unscreened	13p
Jack, ¼in screened	22p
Jack, stereo, unscreened	22p
Jack, stereo, screened	38p
Phono, plastic top	5½p
Phono, plated metal	13p
Wander, red or black	3½p
Banana 4mm, red or black	6½p

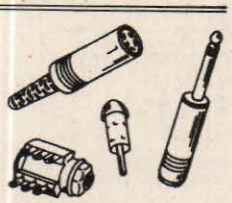


SOCKETS

Car aerial	9p
Co-axial, surface	9p
Co-axial, flush	10p
D.I.N. 2 pin (speaker)	11p
D.I.N. 3 pin	10p
D.I.N. 5 pin, 180°	10p
D.I.N. 5 pin, 240°	10p
Jack, 2½mm	11p
Jack, 3½mm	11p
Jack, ¼in unswitched	16½p
Jack, ¼in switched	18½p
Jack, stereo, switched	26p
Phono, single	5½p
Phono, 2 on a strip	7½p
Phono, 3 on a strip	10p
Phono, 4 on a strip	11p
Wander, single, red or black	3½p
Wander, twin strip	7½p
Banana 4mm red, or black	6½p

LINE SOCKETS

Car aerial	15½p
Co-axial	19p
D.I.N. 2 pin (speaker)	16½p
D.I.N. 3 pin	17½p
D.I.N. 5 pin, 180°	17½p
D.I.N. 5 pin, 240°	17½p
Jack, 3½mm	16½p
Jack, ¼in screened	54p
Jack, stereo, screened	37p
Phono, plated metal	15½p

PLASTIC BOXES

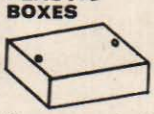

for constructional projects. White, with lid and screws.
BP1 4¼ins × 3ins × 1¼ins—**37p.**
BP2 6ins × 4ins × 2¼ins—**37p.**

CATALOGUE

15p

POST FREE

TRANSFORMERS

all with 0-250 Volt primaries.

Miniature
MM6 6V, 500mA + 6V, 500mA.
MM12 12V, 250mA + 12V, 250mA.
MM20 20V, 150mA + 20V, 150mA.
£1·42, plus 14p P. & P.

L.T.
LT1 6·3V, 1·5V—**82p,** plus 20p P. & P.
LT2 6·3V, 3A—**96p,** plus 28p P. & P.
LT3 12V, 1·5A—**96p,** plus 28p P. & P.
LT4 12V, 3A—**£1·45,** plus 33p P. & P.
LT5 9-0-9V, 0·5A—**83p,** plus 23p P. & P.
LT6 12-0-12V, 1A—**£1·04,** plus 29p P. & P.

Multi-tapped
MT30/2 0-12-15-20-24-30V, 2A—**£2·15,** plus 33p P. & P.
MT60/1 0-5-20-30-40-60V, 1A—**£2·31,** plus 33p P. & P.
MT60/2 0-5-20-30-40-60V, 2A—**£3·25,** plus 37p P. & P.

Charger
CT/01 1A—**£1·16,** plus 28p P. & P.
CT/02 2A—**£1·43,** plus 33p P. & P.
CT/03 4A—**£1·76,** plus 33p P. & P.
Secondaries 0-5-11-17V.

Speaker Matching 3-8-16 Ω
Example: 16 Ω speaker to 8 Ω amplifier. 8Ω amplifier to 3 Ω speaker, etc. **99p,** plus 22p P. & P.

MINIATURE ELECTROLYTICS

1·0μF	63V	7p	150μF	25V	8p
1·5μF	63V	7p	150μF	40V	13p
2·2μF	63V	7p	150μF	63V	15p
3·3μF	63V	7p	220μF	4V	7p
4·7μF	63V	7p	220μF	10V	7p
6·8μF	40V	7p	220μF	16V	8p
6·8μF	63V	7p	220μF	25V	13p
10μF	25V	7p	220μF	40V	15p
10μF	63V	7p	220μF	63V	22p
15μF	16V	7p	330μF	4V	7p
15μF	40V	7p	330μF	10V	8p
15μF	63V	7p	330μF	16V	13p
22μF	10V	7p	330μF	63V	26p
22μF	25V	7p	470μF	6·3V	8p
22μF	63V	7p	470μF	10V	13p
33μF	6·3V	7p	470μF	25V	15p
33μF	16V	7p	470μF	40V	22p
33μF	40V	7p	680μF	6·3V	13p
47μF	4V	7p	680μF	16V	15p
47μF	10V	7p	680μF	25V	22p
47μF	25V	7p	680μF	40V	26p
47μF	40V	7p	1000μF	4V	13p
47μF	63V	8p	1000μF	10V	15p
68μF	6·3V	7p	1000μF	16V	22p
68μF	16V	7p	1000μF	25V	26p
68μF	63V	13p	1500μF	6·3V	15p
100μF	4V	7p	1500μF	10V	22p
100μF	10V	7p	1500μF	16V	26p
100μF	25V	7p	2200μF	6·3V	22p
100μF	40V	8p	2200μF	10V	26p
100μF	63V	15p	3300μF	6·3V	26p
150μF	6·3V	7p	4700μF	4V	26p
150μF	16V	7p			

VEROBOARD

Size	0·1 Matrix	0·15 Matrix
2½in × 3¾in	25½p	18½p
2½in × 5in	28½p	28½p
3¾in × 3¾in	28½p	28½p
3¾in × 5in	32p	35p
17in × 2½in	87p	66p
17in × 3¾in	£1·18	94p

Spot face cutter—**44p**
Pins, either size, pack of 36—**21p**
Edge connectors:
24 way, 0·1—**37½p** 36 way, 0·1—**48½p**
24 way, 0·15—**37½p** 16 way, 0·15—**25p**

BONDED ACRYLIC FIBRE

B.A.F. wadding, 18in wide, 1in thick. The ideal lining for speaker enclosures, **33p** per yard. P. & P. 1yd 14p; each extra yard 4p.

CONTROLS

Log. or Lin.
Single, less switch, **15p**
Single, D.P. switch, **26p**
Tandem, less switch, **44p**
5k Ω, 10k Ω, 25k Ω, 50k Ω, 100k Ω, 250k Ω, 500k Ω, 1M Ω, 2M Ω.

BATTERY ELIMINATORS

suitable for transistor radios and similar light current equipment. Input 240V a.c.
Output: PP6—6V d.c.; PP9—9V d.c.
Price **£1·65,** plus 15p P. & P.

RESISTOR BARGAIN PACK

of **100** ¼W resistors. Tolerance 5% or better, E24 values. Good assortment; our selection, **only 50p.**

MAGNETIC COUNTERS

Brand new, neat, 48 volt, 5 digit counters. **66p.**



CASSETTE MICROPHONE

Low impedance dynamic with remote control switch. Fitted 2½mm and 3½mm plugs. **£2·34,** plus 15p P. & P.



ELECTROLYTICS

1μF	450V	21p	1000μF	50V	46p
2μF	450V	22p	2000μF	25V	43p
4μF	350V	15½p	2000μF	50V	58p
8μF	450V	18½p	2500μF	25V	50p
16μF	450V	20p	2500μF	50V	66p
25μF	25V	7½p	3000μF	25V	53p
25μF	50V	11p	5000μF	25V	66p
32μF	450V	30p	5000μF	50V	£1·21
50μF	50V	11p	8–8μF	450V	20p
100μF	50V	12p	8–16μF	450V	22p
250μF	25V	15½p	16–16μF	450V	30p
250μF	50V	19p	16–32μF	450V	69p
500μF	25V	20p	32–32μF	450V	54p
500μF	50V	27½p	50–50μF	350V	42p
1000μF	25V	30p			

TE-20D RF SIGNAL GENERATOR



Accurate wide range signal generator covering 120 kHz-500 MHz on 6 bands. Directly calibrated. Variable R.F. attenuator audio output, Xtal socket for calibration. 220/240V a.c. Brand new with instructions. **£15.** Carr. 37p. Size 140mm × 215mm × 170mm.

TE22 SINE SQUARE WAVE AUDIO GENERATORS



Sine: 20c/s to 200 kc/s on 4 bands. Square: 20c/s to 30 kc/s. Output impedance 5,000 ohms. 200/250V a.c. Supplied brand new and guaranteed with instruction manual and leads. **£17·50.** Carr. 37½p.


"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. All models—Input 230v. 50/60 c/s. Variable output 0-260v.



MODEL S-260 GENERAL PURPOSE BENCH MOUNTING

1 amp.	£7·00
2·5 amp.	£8·05
5 amp.	£11·75
8 amp.	£15·90
10 amp.	£22·50
12 amp.	£23·60
20 amp.	£49·00
25 amp.	£58·00
40 amp.	£82·50

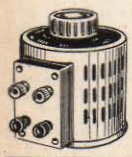

MODEL S-260B

Panel mounting

1 amp	£7·00
2·5 amp	£8·05


Carriage and Packing Extra

AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded.


80W	£2·10	P. & P. 18p
150W	£2·70	P. & P. 18p
300W	£3·60	P. & P. 23p
500W	£5·25	P. & P. 33p
1000W	£7·50	P. & P. 38p
1500W	£10·20	P. & P. 43p
2250W	£17·25	P. & P. 50p
5000W	£35·00	P. & P. £1

MCA.220 AUTOMATIC VOLTAGE STABILISER

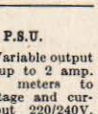

Input 88–125V a.c. or 176–250V a.c. Output 120V a.c. or 240V a.c. 200VA rating. **£11·97.** Post 50p.

PS.200 REGULATED P.S.U.

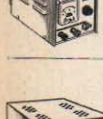


Solid state. Variable output 5–20V d.c. up to 2 amp. Independent meters to monitor voltage and current. Output 220/240V. a.c. Size 7½in. × 5½in. × 3½in. **£19·95.** Post 25p.

PS.1000B REGULATED POWER SUPPLY



Solid state. Output 6, 9 or 12V d.c. up to 3 amps. Meter to monitor current. Input 220/240V a.c. Size 4in. × 3½in. × 6½in. **£11·97.** Post 25p.

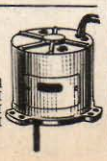230V/240V SMITHS SYNCHRONOUS GEARED MOTORS



Built in gearbox. All brand new and boxed. 30 RPH CW; 2 RPH CW; 20 RPH CW; 2 RPH ACW; 30 RRH CW. **50p each,** Post 12p.

SEW CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVT. DEPTS., EDUCATIONAL AUTHORITIES, ETC.

Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

TYPE SW.100 100mm × 80mm Fronts



50μA	£4·15	5 amp. d.c. ...	£3·60
50-0-50μA ...	£3·95	300V a.c. ...	£3·70
100μA	£3·95	VU Meter ...	£4·30
100-0-100μA .	£3·90		
500μA	£3·70		
1mA	£3·60		
20V d.c.	£3·60		
50V d.c.	£3·60		
300V a.c. ...	£3·60		
1 amp. d.c. ..	£3·60		

Type SD.830 82·5mm × 110mm Fronts




50μA	£3·40	10mA	£3·10
50-0-50μA ...	£3·40	50mA	£3·10
100μA	£3·35	100mA	£3·10
100-0-100μA .	£3·35	500mA	£3·10
200μA	£3·30	1 amp.	£3·10
500μA	£3·15	5 amp.	£3·10
1mA	£3·10	10 amp.	£3·10
5mA	£3·10	5V d.c.	£3·10
		10V d.c.	£3·10
		20V d.c.	£3·10
		50V d.c.	£3·10
		300V d.c.	£3·10
		15V a.c.	£3·30
		300V a.c.	£3·30
		VU Meter ..	£3·50

Type SD.640 63·5mm × 85mm Fronts

50μA	£3·05	500mA	£2·90
50-0-50μA ...	£3·05	1 amp.	£2·90
100μA	£3·00	5 amp.	£2·90
100-0-100μA .	£3·00	10 amp.	£2·90
200μA	£3·00	5V d.c.	£2·90
500μA	£2·95	20V d.c.	£2·90
1mA	£2·90	50V d.c.	£2·90
5mA	£2·90	300V d.c. ...	£2·90
10mA	£2·90	15V a.c.	£3·00
50mA	£2·90	300V a.c. ...	£3·00
100mA	£2·90	VU Meter ..	£3·15

Type SD.460 46mm × 59·5mm Fronts

50μA	£2·80	1 amp.	£2·60
50-0-50μA ...	£2·80	5 amp.	£2·60
100μA	£2·75	10 amp.	£2·60
100-0-100μA .	£2·75	5V d.c.	£2·60
200μA	£2·70	10V d.c.	£2·60
500μA	£2·55	20V d.c.	£2·60
1mA	£2·60	50V d.c.	£2·60
5mA	£2·60	300V d.c. ...	£2·60
10mA	£2·60	1 amp.	£2·70
50mA	£2·60	15V a.c.	£2·70
100mA	£2·60	300V a.c. ...	£2·70
500mA	£2·60	VU Meter ...	£2·90

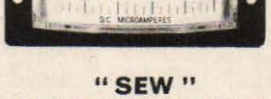

"SEW" EDGEWISE METERS


Type PE.70. 3 17/32in. × 1 15/32in. × 2¼in. deep.

50μA	£3·75	500μA	£3·20
50-0-50μA ...	£3·60	1mA	£3·20
100μA	£3·60	300V a.c. ...	£3·25
100-0-100μA .	£3·50	VU Meter ...	£3·85
200μA	£3·40		

***MOVING IRON— ALL OTHERS MOVING COIL**

Please add postage

Type MR.85P. 4¼in. × 4¼in. Fronts

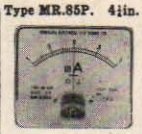

50μA	£3·95	50mA	£3·10
50-0-50μA ...	£3·40	100mA	£3·10
100μA	£3·40	500mA	£3·10
100-0-100μA .	£3·30	1 amp.	£3·10
200μA	£3·30	5 amp.	£3·10
500μA	£3·20	15 amp.	£3·10
5000-500μA .	£3·10	30 amp.	£3·20
1mA	£3·10	20V d.c.	£3·10
1-0-1mA	£3·10	50V d.c.	£3·10
5mA	£3·10	150V d.c. ...	£3·10
10mA	£3·10	300V d.c. ...	£3·10
		15V a.c.	£3·10
		300V a.c. ...	£3·10
		S Meter 1mA.	£3·15
		VU Meter ...	£3·95
		1 amp. a.c.* .	£3·10
		5 amp. a.c.* .	£3·10
		10 amp. a.c.*	£3·10
		20 amp. a.c.*	£3·10
		30 amp. a.c.*	£3·10

Type MR.52P. 2½in. square Fronts.

50μA	£3·50	10V d.c.	£2·50
50-0-50μA ...	£3·05	20V d.c.	£2·50
100μA	£3·00	50V d.c.	£2·50
100-0-100μA .	£2·95	300V d.c. ...	£2·50
500μA	£2·85	15V a.c.	£2·60
1mA	£2·50	300V a.c. ...	£2·60
5mA	£2·50	S Meter 1mA.	£2·60
10mA	£2·50	VU Meter ...	£3·60
50mA	£2·50	1 amp. a.c.* .	£2·50
100mA	£2·50	5 amp. a.c.* .	£2·50
1 amp.	£2·50	10 amp. a.c.*	£2·50
5 amp.	£2·50	20 amp. a.c.*	£2·50
		30 amp. a.c.*	£2·50

Type MR.65P. 3¼in. × 3¼in. Fronts

50μA	£3·70	10V d.c.	£2·60
50-0-50μA ...	£3·15	20V d.c.	£2·60
100μA	£3·15	50V d.c.	£2·60
100-0-100μA .	£3·10	150V d.c. ...	£2·60
200μA	£3·05	300V d.c. ...	£2·60
500μA	£2·75	15V a.c.	£2·80
500-0500μA .	£2·60	50V a.c.	£2·80
1mA	£2·60	150V a.c. ...	£2·80
5mA	£2·60	300V a.c. ...	£2·80
10mA	£2·60	500V a.c. ...	£2·80
50mA	£2·60	S Meter 1mA.	£2·85
100mA	£2·60	VU Meter ...	£3·70
500mA	£2·60	50mA a.c.* ..	£2·60
1 amp.	£2·60	100mA a.c.* .	£2·60
5 amp.	£2·60	200mA a.c.* .	£2·60
10 amp.	£2·60	500mA a.c.* .	£2·60
15 amp.	£2·60	1 amp. a.c.* .	£2·60
20 amp.	£2·60	5 amp. a.c.* .	£2·60
30 amp.	£2·60	10 amp. a.c.*	£2·60
50 amp.	£2·90	20 amp. a.c.*	£2·60
5V d.c.	£2·60	30 amp. a.c.*	£2·60

Type MR.88P. 1 21/32in. square Fronts.



50μA	£2·55	200mA	£2·25
50-0-50μA ...	£2·50	300mA	£2·25
100μA	£2·45	500mA	£2·25
100-0-100μA .	£2·40	750mA	£2·25
200μA	£2·25	1 amp.	£2·25
500μA	£2·25	2 amp.	£2·25
500-0-500μA .	£2·25	5 amp.	£2·25
1mA	£2·25	10 amp.	£2·25
1-0-1mA	£2·25	3V d.c.	£2·25
2mA	£2·25	10V d.c.	£2·25
5mA	£2·25	15V d.c.	£2·25
10mA	£2·25	20V d.c.	£2·25
20mA	£2·25	50V d.c.	£2·25
50mA	£2·25	100V d.c. ...	£2·25
100mA	£2·25	150V d.c. ...	£2·25
150mA	£2·25	300V d.c. ...	£2·25
		500V d.c. ...	£2·25
		750V d.c. ...	£2·25
		15V a.c.	£2·35
		50V d.c.	£2·30
		150V a.c. ...	£2·30
		300V a.c. ...	£2·30
		500V a.c. ...	£2·30
		S Meter 1mA.	£2·30
		VU Meter ...	£2·65

Type MR.45P. 2in. square Fronts.

50μA	£2·70	5 amp.	£2·40
50-0-50μA ...	£2·65	10V d.c.	£2·40
100μA	£2·60	20V d.c.	£2·40
100-0-100μA .	£2·50	50V d.c.	£2·40
200μA	£2·50	300V d.c. ...	£2·40
500μA	£2·45	15V d.c.	£2·40
500-0-500μA .	£2·40	300V d.c. ...	£2·40
1mA	£2·40	S Meter 1mA.	£2·50
5mA	£2·40	VU Meter ...	£2·70
10mA	£2·40	1 amp. a.c.* .	£2·40
50mA	£2·40	5 amp. a.c.* .	£2·40
100mA	£2·40	10 amp. a.c.*	£2·40
500mA	£2·40	20 amp. a.c.*	£2·40
1 amp.	£2·40	30 amp. a.c.*	£2·40

"SEW" BAKELITE PANEL METERS

Type MR.65. 3¼in. square Fronts.



25μA	£4·80	1 amp.	£2·60
50μA	£3·55	5 amp.	£2·60
50-0-50μA ...	£3·05	15 amp.	£2·60
100μA	£3·00	30 amp.	£2·60
100-0-100μA .	£3·00	50 amp.	£2·60
500μA	£2·70	5V d.c.	£2·60
500-0-500μA .	£2·70	10V d.c.	£2·60
1mA	£2·60	20V d.c.	£2·60
1-0-1mA	£2·60	50V d.c.	£2·60
5mA	£2·60	150V d.c. ...	£2·60
10mA	£2·60	300V d.c. ...	£2·60
5mA	£2·60	30V a.c.* ...	£2·65
50mA	£2·60	50V a.c.* ...	£2·65
100mA	£2·60	150V a.c.* ..	£2·65
1-0-1mA	£2·60	300V a.c.* ..	£2·65
2mA	£2·60	500mA a.c.* .	£2·60
5mA	£2·60	1 amp. a.c.* .	£2·60
10mA	£2·60	5 amp. a.c.* .	£2·60
20mA	£2·60	10 amp. a.c.*	£2·60
50mA	£2·60	20 amp. a.c.*	£2·60
100mA	£2·60	50 amp. a.c.*	£2·60
500mA	£2·60	VU Meter ...	£3·65
		50mV d.c. ...	£2·90
		100mV d.c. ..	£2·90

"SEW" EDUCATIONAL METERS



Type ED.107. Size overall 100mm × 90mm × 108mm.

A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3in. mirror scale. The meter movement is easily accessible to demonstrate internal working. Available in the following ranges:

50μA	£5·50	10V d.c.	£4·85
100μA	£5·10	20V d.c.	£4·84
1mA	£4·85	50V d.c.	£4·85
50-0-50μA ...	£5·10	300V d.c. ...	£4·85
10-0-1mA	£4·85	Dual range	
1A d.c.	£4·85	500mA/5A d.c.	£5·10
5A d.c.	£4·85	5V/50V d.c. .	£5·10

Type S-80 80mm square Fronts



50μA	£3·50	1mA	£3·00
50-0-50μA ...	£3·40	20V d.c.	£3·00
100μA	£3·40	50V d.c.	£3·00
100-0-100μA .	£3·30	300V d.c. ...	£3·00
500μA	£3·05	1 amp. d.c. ..	£3·00
		5 amp. d.c. ..	£3·00
		300V a.c. ...	£3·00
		VU Meter ..	£3·70

POWER RHEOSTATS



High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fixing, ¼in dia. shafts. Bulk quantities available.

25 WATT. 10/25/50/100/250/500/1000/1500 2500 or 5000 ohms. **95p.** P. & P. 10p.

50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. **£1·35.** P. & P. 10p.

100 WATT. 1·5/10/25/50/100/250/500/1000 or 2500 ohms. **£1·95.** P. & P. 15p.



240° Wide Angle 1mA Meters

MW1-6 60mm square	£3·97
MW1-8 80mm square	£4·97

Post extra



230 VOLT A.C. 50 CYCLES RELAYS

Brand new. 3 sets of changeover contacts at 5 amp. rating. **50p** each. Post 10p (100 lots £40) Quantities available.

Send S.A.E. for list of Semiconductors and Valves

ALL PRICES ARE EXCLUSIVE OF 10% V.A.T.

ALSO SEE FOLLOWING PAGES

G.W.SMITH & CO (RADIO) LTD

TS60 POCKET MULTIMETER
High-precision at low-cost. Ranges: D.c. 15V, 150V, 1,000V (10,000 O.P.V.). A.c. 15V, 150V, 100V (1,000 O.P.V.).
D.c. Current 150mA. Resistance 100k ohms.
£1·85. Post 15p.




AUDIOTRONIC MODEL ATM.1
Top value 1,000 o.p.v. pocket multimeter.
Ranges: 0/10/50/250/1,000V. A.C. and D.C.
D.C. Current 0–1mA/100mA.
Resistance: 0/150 K ohms.
Decibels: –10 to +22dB.
Size: 90 × 60 × 28mm.
Complete with test leads.
£2·50. Post 15p.



MODEL 1092 Testmeter
5,000 O.P.V.
0/3/15/150/300/1,200V d.c.
0/6/30/300/500 V a.c.
0/300μA/300MA
0/10K/1 meg Ω
Decibels — 10 to + 16 dB
£2·75 each. Post 15p.



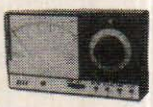LT 601 MULTIMETER
New style 20,000 O.P.V. pocket multimeter. 5/25/50/250/500/2,500V d.c. 10/50/100/500/1,000V a.c. 50μA/250A. 6K/6 meg ohms. —20 to +22dB.
£3·75. Post 20p.



MODEL TH-12
20,000 O.P.V. Overload protection. Slide switch selector. 0/0·25/2·5/10/50/250/1,000V d.c. 0/10/50/250/1,000V a.c. 0/50μA/25/250mA d.c. 0/3K/30K/300K/3 meg. —20 to +50dB.
£4·97. Post 15p.




RUSSIAN 22 RANGE MULTIMETER
Model U437 10,000 O.P.V. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2·5/10/50/250/500/1,000V d.c. 2·5/10/50/250/500/1,000V a.c. D.c. current 100wA/1/10/100mA/1A. Resistance 300 ohms/3/30/300K/3m Ω. Complete with batteries, test leads, instructions and sturdy steel carrying case.
OUR PRICE **£5·97.** Post 25p.



HIOKI MODEL 730X
30,000 O.P.V. Overload protection. 6/30/60/300/600/1,200V d.c. 12/60/120/600/1,200V a.c. 60μA/30mA/300 mA. 2K/200K/2 meg. ohm. —10 to +63dB.
£6·50. Post 15p.



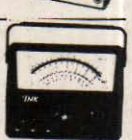MODEL PL436
20k Ω/V d.c. 8k Ω/V a.c. Mirror scale.
0-6/3/12/30/120/600V d.c. 3/30/120/600V a.c. 50/600μA/60/600mA. 10/100K/1 Meg/10 Meg Ω.
—20 to +46dB. **£6·97.** Post 12p.



MODEL 500 30,000 O.P.V. with overload protection mirror scale 0/0·5/2·5/20/25/100/250/500/1,000V d.c. 0/2·5/10/25/100/250/500/1,000V a.c. 0/50μA/5/50/500mA. 12 amp. d.c. 0/60/K/6 Meg./60 Meg Ω.
£8·87. Post paid.



HIOKI MODEL 750X
50,000 O.P.V.
43 ranges 0·0·3 to 1,200V d.c.
0·3 to 1,200V a.c.
0·30μA/300mA.
0·3K/30 meg ohms. —10 to +17dB.
£8·97. Post 20p.



U4312 MULTIMETER
Extremely sturdy instrument for general electrical use, 667 O.P.V.
0/0·3/1·5/7·5/30/60/150/300/600/900V d.c. and 75mV.
0/0·3/1·5/7·5/30/60/150/300/600/900V a.c.
0/300μA/1·5/6/15/60/150
600MA/1·5/6 amp. d.c.
0/1·5/15/60/150/600MA/1·5/6 amp. a.c. 0/200 Ω/3k/30k Ω. Accuracy Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. **£9·50.** Post 25p.



HIOKI MODEL 700X
100,000 O.P.V. Overload protection. Mirror scale. 0·3/0·6/1·2/1·5/3/6/12/30/60/120/300/600/1,200V d.c. 1·5/3/6/12/30/60/150/300/600/1,200V a.c.
15/30μA/3/6/30/60/150/300mA 6/12 amp. d.c. 2K/200K/2 Meg/20 Meg ohm —20 to +63dB. **£13·50.** Post 20p.



MODEL C-7080 EN
Giant 6in mirror scale. 20,000 O.P.V.
0/0·25/1/2·5/10/50/250/1,000/5,000V d.c. 0/2·5/10/50/250/1,000/5,000V a.c.
0/50μA/1/10/100/500mA/10 amp. d.c. 0/2K/200K/20 meg.
—20 to +50dB.
£13·95. Post 35p.



870 WTR MULTIMETER
Features a.c. current ranges. 20,000 O.P.V.
0/0·5/2·5/10/50/250/500/1,000V d.c.
0/2·5/10/50/250/500/1,000V a.c.
0/50μA/1/10/100mA/1/10 amp. d.c.
0/100mA/1/10 amp. a.c.
0/5K/50K/500K/5MEG/50MEG.
—20 +62dB. **£15.** Post 25p.



HT100B4 MULTI-METER
Features a.c. current ranges. 100,000 O.P.V. Mirror Scale. Overload protection.
0/0·5/2·5/10/50/250/500/1,000V d.c.
0/2·5/10/50/250/500/1,000V a.c.
0/10/250μA/2·5/25/250MA
10 amp. d.c.
10 amp. a.c. 0/20K/200K/2MEG/20 MEG.
—20 +62dB. **£15.** Post. 25p.



KAMODEN 72.200 MULTITESTER
High sensitivity tester. 200,000 o.p.v. Overload protection. Mirror scale. Ranges: 0/0·06/0·3/3/30/120/600/1,200V d.c., 0/3/12/60/300/11,200V a.c. 0/6μA/1·2mA/120mA/600mA/12A d.c. 0/12A a.c. —20 to +63dB. 0/2k Ω/200k Ω/2M Ω/200 M Ω. **£16·95.** Post 30p.



TMK LAB TESTER
100,000 O.P.V.
6½in scale buzzer short circuit check.
Sensitivity: 100,000 OPV d.c. 5/Volt a.c.
D.c. volts: 0·5, 2·5, 10, 50, 250, 1,000V.
A.c. volts: 3, 10, 50, 250, 500, 1,000V. D.c. current: 10, 100μA, 10, 100, 500mA, 2·5, 10A. Resistance: 1K, 10K, 100K, 10 meg. 100 meg. Decibels: —10 to +49dB. Plastic case with carrying handle, size 7½in × 6½in × 3½in. **£18·95.** P. & P. 25p.



Model 3-100TR MULTIMETER/TRANSISTOR TESTER. 100,000 O.P.V. mirror scale/overload protection. 0/0·12/0·6/3/12/30/120/600V d.c. 0/6/30/120/600V a.c. 0/12/600μA/12/300mA/12 amp. d.c. 0/10 K/1 MEG/100 MEG. —20 to +50dB. 0·01–2 MFD. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads.
£13·50. Post 25p.



LB3 TRANSISTOR TESTER
Tests ICO and B. *Pnp/npn*. Operates from 9V battery. Complete with all instructions, etc.
£3·95. Post 20p.



LB4 TRANSISTOR TESTER
Tests PNP or NPN transistors, Audio indication. Operates on two 1·5V batteries. Complete with all instructions, etc.
£4·50. Post 20p.



KAMODEN HM-350 TRANSISTOR TESTER
High quality instrument to test Reverse Leak current and D.C. current. Amplification factor of NPN, PNP, transistors, diodes, SCR's, etc. 4" × 4½" clear scale meter. Operates from internal batteries. Complete with instructions, leads and carrying handle. **£12·50.** Post 30p.



MODEL 449A IN CIRCUIT TRANSISTOR TESTER
Checks true a.c. beta in/out. Checks Icbo. Checks diodes in/out. Checks SCR, etc. Beta HI 10—500 LO 2—50 Ibco 0·5000μA. 220/240V a.c. operation. **£17·50.** Post 25p.



MODEL U4311 SUB-STANDARD MULTI-RANGE VOLT AMMETER
Sensitivity 330 ohms/Volt a.c. and d.c. Accuracy 0·5% d.c. 1% a.c. Scale length 165mm.
0/300/750μA/1·5/3/7·5/15/30/75/150/300/750mA/1·5/3/7·5 amp.
d.c. 0/3/7·5/15/30/75/150/300/750mA/1·5/3/7·5 amp. a.c. 0/75/150/300/750mV/1·5/3/7·5·15·30/75/150/300/750V d.c. 0/750mV/1·5/3/7·5/15/30/75/150/300/750V a.c.
Automatic cut out. Supplied complete with test leads, manual and test certificates.
£49. Post 50p.



TE-65 VALVE VOLTMETER
28 ranges. D.c. volts 1·5–1,500V a.c. volts 1·5–1,500V. Resistance up to 1,000 megohms. 200/240V r a.c. operation. Complete with probe and instructions.
£17·50. Post 30p. Additional probes available: R.F. **£2·12**; H.V. **£2·50.**



KAMODEN HM720B F.E.T. V.O.M.
Input impedance 10M Ω. Ranges: 0/0·25/1/2·5/10/50/250/1,000V d.c. 0/2·5/10/50/250/1,000V a.c. 0/25μA/2·5/25/250MA d.c. —20 to +62dB. 0/5k/50k/500k/5M Ω/500M Ω.
£14·95. Post 30p.



TE-40 HIGH SENSITIVITY A.C. VOLTMETER
10 meg. input 10 ranges: 01/·003/·1/·3/1/3/10/30/100/300V. R.M.S. 4cps.-1·2 Mc/s. Decibels —40 to +50dB
Supplied brand new complete with leads and instructions. Operation 230V. a.c. **£17·50.** Carr. 25p.



TMK MODEL 117 F.E.T. ELECTRONIC VOLTMETER
Battery-operated, 11 meg input. 26 ranges. Large 4½in mirror scale. Size 5½in × 4½in × 2½in. D.c. volts 0·3–1,200V. A.c. volts 3–300V R.M.S. 8·0·800V P-P. D.c. Current 0·12·12MA. Resistance up to 2,000M ohm. Decibels —20 to +51dB. Complete with leads/instructions.
£17·50. P. & P. 20p.



MODEL L-55 FET V.O.M.
Input impedance 10 meg ohms. 0/0·3/1·2/6/30/120/600V d.c. 0/3/12/60/120/600V a.c. 0/120μA/120mA d.c. 0/1K/100K/10 meg/100 meg ohms.
£15·97. Post 25p.



KAMODEN HMG-500 INSULATION RESISTANCE TESTER
Range 0–1,000 Megohms, 500 Volt. Battery operated. Wide range clear meter 4½" × 4". Complete with deluxe carrying case, batteries, instructions.
£19·95. Post 30p.



BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR
Sine 18-200,000 Hz: Square 18-50,000 Hz. Output max. +10dB (10 K ohms) Operation internal batteries. Attractive 2-tone case 7½in × 5in × 2in. Price **£17·50.** Carr. 17p.



CI-5 PULSE OSCILLOSCOPE
For display of pulsed and periodic waveforms in electronic circuits VERT. AMP. Bandwidth 10MHz. Sensitivity at 100kHz V RMS/mm. 0·1-25; HOR. AMP. Bandwidth 500kHz. Sensitivity at 100kHz, V RMS/mm. 0·3-25; Pre-set triggered sweep 1-3,000μsec.; free running 20-200,000Hz in nine ranges. Calibrator pips. 220mm × 360mm × 430mm, 115-230V a.c. operation.
£39. Carr. paid.




TO-3 PORTABLE OSCILLOSCOPE
8in tube, Y amp. Sensitivity 0·1V p-p/CM. Bandwidth 1·5cps-1·5MHz. Input imp. 2 meg Ω 25pF X amp. sensitivity 0·9V. p-p/CM. Bandwidth 1·5cps-800kHz. Input imp. 2 meg Ω 20pF Time base. 5 ranges 10cps-300kHz. Synchronisation. Internal/external. Illuminated scale 140mm × 215mm × 330mm. Weight 15½lb. 220/240V a.c. Supplied brand new with handbook. **£47·50.** Carr. 50p.



RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPE
5MHz Pass Band. Separate Y1 and Y2 amplifiers. Rectangular 5in × 4in C.R.T. Calibrated triggered sweep from 0·2μsec to 100 milli-sec per cm. Free running time base 50 Hz-1MHz. Built-in time base calibrator and amplitude calibrator. Supplied complete with all accessories and instruction manual.
£87. Carr. paid.



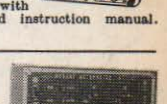MODEL AT201 DECADE ATTENUATOR
Frequency range 0-200kHz. Attenuator 0-111dB, 0·1dB step. Impedance 600 ohms. Max. Input power 30dBm. Size 180mm × 90mm × 55mm.
£12·50. Post 37p.



ARF-300 AF/RF SIGNAL GENERATOR
All transistorised, compact, fully portable. AF sine wave 18 Hz to 220 KHz. AF square wave 18 Hz to 100 KHz. Output sine/square 10v. P-P. RF 100 KHz to 200 MHz. Output 1v. maximum. Operation 220/240v. AC. Complete with instructions and leads. **£29·95.** Post 50p.



G.W.SMITH & CO (RADIO) LTD

UNR 30 RECEIVER



4 Bands covering 550kHz-30MHz. BFO Built-in Speaker 220/240V a.c. Brand new with instructions.

OUR PRICE **£15·75** Carr. 37p

UR-1A RECEIVER



4 Bands covering 550kHz-30MHz. FET, S Meter. Variable BFO for SSB. Built-in Speaker. Bandspread. Sensitivity Control. 220/240V a.c. or 12V d.c. 12½ × 4½in × 7in. Brand new with instructions.

OUR PRICE **£25·00** Carr. 37p

SKYWOOD CX203 RECEIVER



Solid state. 5 bands covering 200-420kHz and 0·55 to 30MHz. Illuminated slide rule dial. Bandspread. Aerial tuning. BFO, AVC, ANL, "S" meter. AM/CW/SSB. Integrated speaker and phone socket, 220/240V a.c. or 12V d.c. Size 325 × 266 × 150mm. Complete with instructions and circuit.

OUR PRICE **£32·50** Carr. 50p

LAFAYETTE HA-600 RECEIVER



General coverage 150-400kHz, 550kHz-30MHz. FET front end, 2 mech. filters, product detector, variable BFO, noise limiter, S Meter Bandspread. RF Gain. 15in × 9½in × 8½in. 18 lb. 220/240V a.c. or 12V d.c. Brand new with instructions.

OUR PRICE **£50·00** Carr. 50p

TRIO 9R59DS RECEIVER



4 bands covering 550kHz-30MHz continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. SSB-CW. ANL. Variable BFO. S meter. Sep. bandspread dial. IF frequency 445kHz audio output 1·5W. Variable RF and AF gain controls 115/250V a.c. Size: 7in × 13in × 10in with instruction manual.

OUR PRICE **£49·50** Carr. Paid

FULL RANGE OF TRIO STOCKED

ALSO SEE PREVIOUS PAGES

EMI LOUDSPEAKERS



Model 350. 13in × 8in with single tweeter /crossover. 20-20,000 Hz. 15W RMS. Available 8 or 15 ohms. **£7·25** each. P. & P. 37p.

Model 450. 13in × 8in with twin tweeters/ crossover. 55-13,000 Hz. 8W RMS.

Available 8 or 15 ohms. **£8·62** each. P. & P. 25p.

SPECIAL OFFER!

STEREO SPEAKERS



Matched pair of bookshelf speakers. De luxe teak veneered finish. Size 14½ in × 9in × 7½ in. 8 ohms, 8W RMS 16W peak. Complete with DIN lead.

OUR PRICE **£12·95** Carr. 50p

HA-10 STEREO HEADPHONE AMPLIFIER



All silicon transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. Inputs 5MU/100MU. Output 50MW.

OUR PRICE **£5·97** P. & P. 20p

MP7 MIXER PREAMPLIFIER



5 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9½in × 5in × 3in. Inputs Mics: 3 × 3mV 50K; 2 × 3mV 600 ohm. Phono meg. 4mV 50K. Phono ceramic 100mV 1 meg. Output 250mV 100K.

OUR PRICE **£8·97** P. & P. 20p

1021 STEREO LISTENING STATION



For balancing and gain selection of loudspks. with additional facility for stereo headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets 6in × 4in × 2½in.

OUR PRICE **£2·25** P. & P. 20p

HAND HELD 2-WAY WALKIE TALKIES

Industrial quality in robust metal cases. Battery operation. Volume and squelch controls. Call button and press to talk button. Telescopic aerial. Complete carrying cases.

2 channel 300mW

£52·50 Pair. Post 50p.

3 channel 2W.

£79·50 Pair. Post 50p.

(Note: Licence required for operation in U.K.)


HOMER INTERCOMS



Ideal for home, office, stores, factories, etc. Supplied complete with batteries, cable and free instructions.

2 Station **£12·97**. P. & P. 15p.
3 Station **£5·25**. P. & P. 15p.
4 Station **£6·62**. P. & P. 17p.

FM TUNER CHASSIS

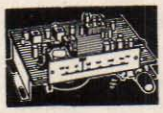

6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6in × 4in × 2½in 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108MHz. Ready built ready for use. Fantastic value for money.

OUR PRICE **£5·95** P. & P. 20p

SH628 STEREO HEADPHONES



Outstanding value. Soft earpads, adjustable headband. 8-16 ohms. 20-20,000 Hz. Complete with lead and stereo plug.

OUR PRICE **£1·87** P. & P. 30p

TE1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET



Sensitive magnetic headset with soft earpads. Impedance 2,600 ohms (d.c. 600 ohms). Frequency response 200-4,000 Hz.

OUR PRICE **£1·97** P. & P. 30p

LH02S STEREO HEADPHONES



Lightweight headphones with padded earpieces. 4-16 ohms. 20-20,000 Hz. Complete with 6 ft cord and plug.

OUR PRICE **£1·95** P. & P. 30p

BH001 HEADSET AND BOOM MICROPHONE



Moving coil. Headphone imp. 16 ohms. Mike imp. 200 ohms. Ideal for language teaching, communications etc. Complete with leads and plugs.

OUR PRICE **£4·95** P. & P. 30p

DH.08S STEREO HEADPHONES



De luxe model with unique 2 waymechanical units and volume controls. 8 ohms. 20-20,000 Hz. Complete with coil lead and stereo jack plug.

OUR PRICE **£7·97** P. & P. 30p

ROTEL BARGAIN!

RH700 STEREO PHONES



Soft leather ear cushions. Impedance 8-16 ohms. 20-20,000 Hz. 15ft coiled lead. Brand New and boxed. (List £9·95).

OUR PRICE **£6·75** P. & P. 30p

4-CHANNEL STEREO HEADPHONES



T T C G3600 — Soft vinyl covered head cushion and earphones Each earpiece incorporates two 2in speaker units. Fitted 2/4 channel changeover switch. Impedance 4-16 ohm. Frequency response 20-20,000 Hz. Complete with 15ft coiled lead fitted two stereo plugs.

OUR PRICE **£9·95** P. & P. 30p

ROTEL BARGAINS!



STEREO AMPLIFIERS

RA310 15 + 15 watt	£34·95
RA610 32 + 32 watt	£51·95
RA810 40 + 40 watt	£72·95
RA1210 60 + 60 watt	£89·95

P. & P. 50p extra.

AM/FM STEREO RECEIVERS

RX150 7½ + 7½ watt	£38·95
RX200 10 + 10 watt	£46·50
RX400 20 + 20 watt	£57·50

P. & P. 75p

UNREPEATABLE OFFER!



NIKKO TRM50 STEREO AMPLIFIER

17 + 17 watts rms. Inputs for magnetic and crystal phono, tuner, tape etc. Dual stereo speaker outputs. Headphone socket. Full range of controls. (Rec. List Price £59·50.)

OUR PRICE **£39·95** P.&P. 50p

AKAI BARGAINS



CASSETTE, P. & P. 50p.

CS35D Deck	£44·45
CS35 Recorder	£57·75
CS35/CS88 Speakers	£67·95
GXC40D Deck	£57·20
GXC40 Recorder	£67·20
GXC40T Deck/Receiver	£99·05
GXC45 Deck	£78·25
GXC46D Dolby Deck	£83·55
GXC46 Recorder	£89·95
GXC60D Deck	£87·65
GXC65D Dolby Deck	£92·65

CARTRIDGE (P. & P. 50p)

CR81 Deck with amps.	£65·40
CR81D Deck	£53·50
CR81T Recorder/Receiver	£92·75
CR80S8 4 channel Recorder	£114·25
CR80DS8 4 chan. Recorder	£93·65

TAPE (P. & P. 75p)

4000DS Deck	£59·95
4000DS Dust Cover	£3·95
1721L Recorder	£60·35
X5000 Recorder	£82·50
X201D Deck	£108·20
GX220D Deck	£123·95
GX221D	£138·40
GX280D Deck	£196·50
GX370 Deck	£211·50

TAPE CASSETTE (P. & P. 75p)

GX1900D Deck	£144·50

TAPE CARTRIDGE (P. & P. 75p)

X1810D Deck	£138·40

TAPE/CASSETTE/CARTRIDGE (P. & P. 75p)

X2000SD Recorder	£180·75

MICROPHONES (P. & P. 50p)

ADM.11 Dynamic (pair)	£7·50

STEREO RECEIVERS (P. & P. 75p)

AA6300 20+20 watt	£61·95
AA8030 25+25 watt	£92·50
AA8080 40+40 watt	£117·50
AA8100S 2×36 or 4×18 watt	£175·00
AA8500 65+65 watt	£150·50

STEREO AMPLIFIERS (P. & P. 50p)

AA5200 20+20 watt	£61·75
AA5500 30+30 watt	£78·50
AA5800 45+45 watt	£117·50

STEREO TUNERS (P. & P. 50p)

AT550 AM/FM	£60·50
AT580 AM/FM	£94·50

4-CHANNEL UNIT (P. & P. 50p)

881 Synthesiser	£89·95

SPEAKERS

CS88 (pair)	£10.20
SW155 (each)	£51·00

STEREO HEADPHONES

ASE11	£4·75
ASE20	£7·30
ASE22	£8·25

FERGUSON EXPORT MODELS

SPECIAL PURCHASE!



FERGUSON 3408 STEREO TUNER AMPLIFIER

Covers FM 88-108 MHz. Five push button tuning scales. 8+8 watts rms. Inputs for stereo ceramic cartridge and tape, etc. Separate bass, treble, balance and volume controls.

OUR PRICE **£31·50** Carr. 50p



FERGUSON 3416 STEREO TAPE DECK

4 track. 7½, 3¾, 1⅞ i.p.s. Stereo/mono record/play. 7in reels. Inputs for dynamic mikes, radio, gram. Complete with cover.

OUR PRICE **£41·95** Carr. 75p

SAVE UP TO 33⅓% OR MORE! GWS

RECORD DECK PACKAGES



Carriage and Packing 75p

Complete units with Stereo cartridge ready wired in plinth cover.

GARRARD

2025 TC/9TAHCD	£10·65
SP25 111/G800	£15·00
SP25 111/M44E	£16·45
SP25 111/M44-7	£16·10
SP25 111/M55E	£16·90
SP25 111 Module/M75-6	£18·99
AP76/G800	£23·50
AP76/G800E	£25·95
AP76/M44E	£24·95
AP76/M55E	£25·65
AP76/M75ED	£31·70
AP76/M75EJ	£27·85
AP76 Module M75–6	£26·95
AP96 Module M75–6	£30·40
ZERO 100S Module/M93E	£41·85

B.S.R. McDONALD

210/SC7M	£6·85
MP60/G800	£15·00
MP60/TPD1/G800	£15·20
MP60/M44-7	£16·60
HT70/TPD1/G800	£18·60

GOLDRING

GL72/G800	£30·90
GL75/G800	£33·60
GL75/G800E	£36·75

GOODMANS

TD100/G800 Teak	£46·85
TD100/G800 White	£48·60

LEAK

Delta/M75-6	£43·95

PHILIPS

GA105/GP200	£13·80
GA160/GP200 Teak	£20·00
GA212/GP400	£45·25
GA308 (less cartridge)	£23·95
GA308 P.U.	£32·75

PIONEER

PL12D (Less cartridge)	£31·75
PL15C (Less cartridge)	£44·25
PL41D (Less cartridge)	£104·75
PL50 (Less cartridge)	£98·90
PL61	£110·30
PLA35	£61·55

THORENS

TD160C/Ortofon M15E Super	£62·50
TD125 AB/II/Ortofon M15 E Super	£96·95

WHARFEDALE

Linton/M44-7	£23·70

SINCLAIR PROJECT 60 PACKAGE DEALS



2 × Z30/Stereo 60/PZ5 **£15·95.** P. & P. 37p.

2 × Z30/Stereo 69/PZ6 **£18·00.** P. & P. 37p.

2 × Z50/Stereo 60/PZ8 **£20·25.** P. & P. 37p.

Transformer for PZ8 **£3** extra.

Active Filter Unit **£4·45.**

Project 60 FM Tuner **£14·95.**

Pair of Q16 Speakers **£10·70.**

Sinclair Project 605 **£20·97.** P. & P. 37p.

All Sinclair Products in stock: 2000 Stereo Amplifier, **£22·95**; 3000 Stereo Amplifier, **£28·95**; 2000/3000 Stereo Tuner, **£26·30.**

Q830 Speakers, **£23·95** pair, P. & P. 50p extra on above items.

RECORD DECKS



Carriage & Packing 50p

B.S.R. McDONALD

C114 Mini	£3·95
C129 Mono	£5·50
C137	£7·00
510/TPD1	£13·95
610	£9·90
610/TPD1	£14·85
710	£19·20
810	£24·50
710/810 Plinth and Cover	£8·35
MP60	£7·65
MP60/G800	£10·25
MP60/TPD1	£12·60
MP60/TPD2	£11·25
HT70	£10·97
HT70/G800	£13·60
HT70/TPD1	£15·95

GONNOISSEUR

BD1 Kit	£9·10
BD1 Chassis	£11·35
BD1/SAU2/Plinth/Cover	£27·60
BD2/SAU2/Chassis	£22·70
BD2/SAU2/Plinth/Cover	£28·50

GARRARD

2025 T/C Stereo	£6·40
SP25 III	£8·50
SP25 III/Acos GP104 Ceramic	£8·50
SP25/M75–6	£13·90
AP76	£15·55
SL65B	£11·15
SL72B	£17·75
SL95B	£25·25
401	£33·50
ZERO 100A	£30·30
ZERO 100S	£27·95

GOLDRING

G99	£16·85
G101P/C	£16·85
GL69/2	£15·75
GL72	£17·85
GL72/P	£23·20
Plinth 69/72	£5·35
LID 72	£2·70
GL75	£23·75
GL75P	£29·30
Plinth 75	£5·55
LID 75	£2·97
GL85/P/C	£49·50

THORENS

TD125/H	£52·15
TD125AB/II	£78·55
TX25	£5·60
TD150A/II	£29·25
TD160C	£43·95

PLINTHS AND COVERS

Carriage and Packing 50p

Budget B.S.R.	£2·95
Budget SP25 etc.	£2·95
Budget AP76/Zero 100S	£3·95
Budget 401/arm	£11·95
Garrard WB1	£2·20
Garrard SPC1	£2·20
Garrard WB4	£3·25
Garrard SPC4	£3·55
SME2000 System	£26·40

SPECIAL GARRARD OFFERS!



STEREO 1025T

4 speed autochanger unit fitted with stereo ceramic cartridge.

OUR PRICE **£4·95** Carr. & Ins. 50p

SP25 III WITH ACOS GP 104



4 speed single record player fitted with Acos GP104 stereo ceramic cartridge.

OUR PRICE **£8·50** Carr. & Ins. 50p

AUDIOTRONIC RANGE OF HIGH QUALITY EQUIPMENT



ACP-8 8 TRACK CAR PLAYER

Attractive black and silver finish. 12V neg. earth. Slider controls for Volume, Tone and Balance. Channel selector button with red pilot lamp. Complete with speakers, mounting brackets and instructions.

ONLY £12·50 P. & P. 40p



ACR1 PUSH BUTTON CAR RADIO

Push button tuning of one LW and five MW stations of your choice. 12V pos. or neg. earth. Complete with speaker, mounting brackets and instructions.

OUR PRICE **£8·95** P. & P. 50p




ACR 3500 CAR RADIO

Manual tuning of Medium and Long waves. 12V pos. or neg. earth. Complete with speaker, mounting brackets and instructions

OUR PRICE **£6·50** P. & P. 50p

ACA 5SE ELECTRIC CAR AERIAL

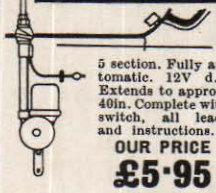

5 section. Fully automatic. 12V d.c. Extends to approx. 40in. Complete with switch, all leads and instructions.

OUR PRICE **£5·95**

P. & P. 50p

AUDIOTRONIC DOLBY 'B' NOISE REDUCTION UNITS



OUTSTANDING VALUE!

Reduce tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Size 16½in × 8in × 3½in. a.c. 00/250V2.

PROCESS TWO

For use with cassette and tape recorders. Freq. res. 30Hz—20kHz—2dB. Off tape monitoring. Switchable multiplex filter. Two Dolby calibration meters. S/N better than 70dB. Supplied with test cassette or tape as required.

OUR PRICE **£34·50** P.&P. 50p

PROCESS FOUR

For use with semi professional tape recorders. Freq. res. 30Hz—20kHz ±2dB. S/N better than 70dB. Full source tape monitoring. Record/Replay metering. Switchable multiplex filter. Supplied with test tape.

OUR PRICE **£50·00** P.&P. 50p



LOW NOISE TAPE CASSETTES

Top Hi-Fi quality in library cases

TYPE	5	10	25
C60	£1·29	£2·53	£5·99
C90	£1·85	£3·62	£8·59
C120	£2·29	£4·48	£10·63

P. & P. 15p Post Free

CASSETTE TAPE HEAD CLEANER 30p each. P. & P 5p.

MONATONE 6750 SYSTEM



AM/FM 4+4 watt stereo tuner amplifier, Garrard 2025 T/C, plinth and cover, stereo cartridge, pair of matching speakers.

OUR PRICE **£30·50**

Carriage and Packing £1·00

ALBANY HOUSE AM 108 SYSTEM



8+8 watt amplifier Garrard SP25, plinth and cover, G800 cartridge, pair of Medway T138 speakers.

OUR PRICE **£52·75**

Carriage and Packing £1·25

VAT

All prices are subject to **10% VAT** (10p in the £)

Order with confidence by post – but remember to add 10% VAT (10p in the £) to total value of goods including carriage/packing and send cash with order. PLEASE PRINT NAME & ADDRESS CLEARLY.

SEND LARGE S.A.E. FOR FULL HI-FI DISCOUNT LIST

G.W.SMITH & CO (RADIO) LTD

ALL MAIL ORDERS TO:

11-12, PADDINGTON GREEN, LONDON W2 1LG. Tel: 01-262 6562

PERSONAL CALLERS WELCOME AT ANY OF OUR RETAIL BRANCHES

CENTRAL LONDON

257/8, Tottenham Court Rd. W.1.	Tel: 01-580 0670
10, Tottenham Court Rd, W.1.	Tel: 01-637 2232
27, Tottenham Court Rd, W.1.	Tel: 01-636 3715
87, Tottenham Court Rd, W.1.	Tel: 01-580 3739
21, Old Compton Street, W.1.	Tel: 01-437 9369
3, Lisle Street, W.C.2.	Tel: 01-437 8204
34, Lisle Street, W.C.2.	Tel: 01-437 9155
118, Edgware Road, W.2.	Tel: 01-723 9789
193, Edgware Road, W.2.	Tel: 01-723 6211
311, Edgware Road, W.2.	Tel: 01-262 0387
382, Edgware Road, W.2.	Tel: 01-723 4194
152/3, Fleet Street, E.C.4.	Tel: 01-353 2833
378, Harrow Road, W.9.	Tel: 01-286 9530

ESSEX

86, South Street, Romford.	Tel: Romford 20218

SURREY

1046, Whitgift Centre, Croydon.	Tel: 01-681 3027
27 & 21, Eden Street, Kingston.	Tel: 01-546 7845
32, Hill Street, Richmond.	Tel: 01-948 1441

ALL BRANCHES OPEN 9 a.m.–6 p.m. MONDAY TO SATURDAY

Buy it with Access — BARCLAYCARD with some here

CREDIT TERMS FOR CALLERS (£50 and over)

ALL EQUIPMENT IS BRAND NEW, FULLY GUARANTEED AND OFFERED WITH FULL AFTER SALES SERVICE

All items and prices are correct at **22-5-73** but subject to change without notice. E. & O. E.

PART OF THE AUDIOTRONIC GROUP OF COMPANIES

RST VALVE MAIL ORDER CO.

16a WELLFIELD ROAD, LONDON SW16 2BS

SPECIAL EXPRESS MAIL ORDER SERVICE

Express postage 1p per transistor, over ten post free
INTEGRATED CIRCUITS 5p + 1p each added

	£p		£p		£p		£p		£p
1N21	0·17	AFZ12	1·00	BYZ10	0·35	OAZ211	0·32	Z8170	0·10
1N23	0·20	ASY26	0·25	BYZ11	0·32	OAZ222	0·45	Z8271	0·18
1N85	0·38	ASY27	0·32	BYZ12	0·30	OAZ223	0·45	ZT21	0·25
1N253	0·50	ASY28	0·25	BYZ13	0·25	OAZ224	0·45	ZT43	0·25
1N256	0·50	ASY29	0·30	BYZ15	1·00	OAZ241	0·22	ZTX107	0·15
1N645	0·25	ASY36	0·25	BYZ16	0·62	OAZ242	0·22	ZTX108	0·12
1N725A	0·20	ASY50	0·17	BYZ88C3V3		OAZ244	0·22	ZTX300	0·12
1N914	0·07	ASY61	0·40			OAZ246	0·23	ZTX304	0·25
1N4007	0·20	ASY63	0·20		0·15	OAZ290	0·38	ZTX500	0·16
18113	0·15	ASY65	0·20	C111	0·65	OC16	0·50	ZTX503	0·17
18130	0·13	ASY62	0·25	CR81/05	0·25	OC16T	0·38	ZTX531	0·25
18131	0·13	ASY86	0·33	CR81/40	0·45	OC19	0·37		
18202	0·23	ASZ21	0·42	C84B	2·50	OC20	0·85		
2G371	0·22	ASZ23	0·75	C810B	3·13	OC22	0·50		
2G381	0·25	AUY10	0·98	DD000	0·15	OC23	0·60	**INTEGRATED CIRCUITS**	
2G414	0·30	AU101	1·50	DD003	0·15	OC24	0·60		
2G417	0·22	BC107	0·10	DD006	0·18	OC25	0·37	7400	0·20
2N404	0·20	BC108	0·10	DD007	0·40	OC26	0·25	7401	0·20
2N697	0·15	BC109	0·10	DD008	0·38	OC28	0·60	7402	0·20
2N698	0·40	BC113	0·15	GD3	0·33	OC29	0·60	7403	0·20
2N706	0·10	BC115	0·20	GD4	0·05	OC30	0·40	7404	0·20
2N706A	0·12	BC116	0·25	GD5	0·33	OC35	0·50	7405	0·20
2N708	0·15	BC116A	0·30	GD8	0·25	OC36	0·60	7406	0·30
2N709	0·63	BC118	0·25	GD12	0·05	OC41	0·25	7407	0·30
2N1091	0·33	BC121	0·20	GET102	0·30	OC42	0·30	7408	0·20
2N1131	0·25	BC122	0·20	GET103	0·22	OC43	0·40	7409	0·45
2N1132	0·25	BC125	0·68	GET113	0·20	OC44	0·17	7410	0·20
2N1302	0·18	BC126	0·65	GET114	0·15	OC44M	0·17	7411	0·23
2N1303	0·18	BC140	0·55	GET115	0·45	OC45	0·12	7412	0·42
2N1304	0·22	BC147	0·15	GET116	0·50	OC45M	0·18	7413	0·30
2N1305	0·22	BC148	0·13	GET120	0·25	OC46	0·27	7416	0·30
2N1306	0·25	BC149	0·15	GET872	0·30	OC57	0·60	7417	0·30
2N1307	0·25	BC157	0·15	GET875	0·25	OC58	0·60	7420	0·20
2N1308	0·25	BC158	0·12	GET880	0·37	OC59	0·65	7422	0·48
2N2147	0·75	BC160	0·63	GET881	0·25	OC66	0·50	7423	0·48
2N2148	0·60	BC169	0·13	GET882	0·25	OC70	0·12	7425	0·48
2N2160	0·60	BCY31	0·35	GET885	0·25	OC71	0·12	7427	0·42
2N2218	0·20	BCY32	0·55	GEX44	0·08	OC72	0·20	7428	0·50
2N2219	0·20			GEX45/1	0·10	OC73	0·30	7430	0·20
2N2369A	0·15	BCY33	0·25	GEX941	0·15	OC74	0·30	7432	0·42
2N2444	1·99	BCY34	0·30	GJ3M	0·25	OC75	0·25	7433	0·70
2N2613	0·28	BCY38	0·40	GJ4M	0·38	OC76	0·25	7437	0·65
2N2646	0·45	BCY39	1·00	GJ5M	0·25	OC77	0·40	7438	0·65
2N2904	0·20	BCY40	0·50	GJ7M	0·37	OC78	0·20	7440	0·20
2N2904A	0·25	BCY42	0·25	HG1005	0·50	OC81	0·20	7441AN	0·75
2N2906	0·20	BCY70	0·15	HS100A	0·20	OC81D	0·20	7442	0·75
2N2907	0·23	BCY71	0·20	MAT100	0·25	OC81M	0·20	7450	0·20
2N2924	0·23	BCZ10	0·35	MAT101	0·30	OC81DM	0·18	7451	0·20
2N2925	0·15	BCZ11	0·50	MAT120	0·25	OC81Z	0·40	7453	0·20
2N2926	0·10	BD121	0·65	MAT121	0·30	OC82	0·25	7454	0·20
2N3054	0·50	BD123	0·80	MJE520	0·87	OC82D	0·20	7460	0·20
2N3055	0·75	BD124	0·75	MJE2955	1·37	OC83	0·25	7470	0·30
2N3702	0·10	BDY11	1·62	MJE3055	0·87	OC84	0·25	7472	0·30
2N3705	0·10	BF115	0·25	NKT128	0·35	OC114	0·38	7473	0·40
2N3706	0·23	BF117	0·50	NKT129	0·30	OC122	0·60	7474	0·40
2N3707	0·12	BF167	0·25	NKT211	0·25	OC123	0·65	7475	0·55
2N3709	0·10	BF173	0·25	NKT213	0·25	OC139	0·25	7476	0·45
2N3710	0·10	BF181	0·35	NKT214	0·15	OC140	0·35	7480	0·80
2N3711	0·10	BF184	0·20	NKT216	0·37	OC141	0·60	7482	0·87
2N3819	0·35	BF185	0·20	NKT217	0·35	OC169	0·20	7483	1·00
2N5027	0·53	BF194	0·17	NKT218	1·13	OC170	0·25	7484	0·90
2N5088	0·33	BF195	0·15	NKT219	0·33	OC171	0·30	7486	0·45
28301	0·50	BF196	0·15	NKT222	0·20	OC200	0·40	7490	0·75
28304	0·75	BF197	0·15	NKT224	0·22	OC201	0·70	7491AN	1·00
28501	0·37	BF861	0·28	NKT251	0·24	OC202	0·80	7492	0·75
28702	0·62	BF898	0·28	NKT271	0·25	OC203	0·40	7493	0·75
AA129	0·20	BFX12	0·20	NKT272	0·25	OC204	0·40	7494	0·80
AAZ12	0·30	BFX13	0·25	NKT273	0·15	OC205	0·75	7495	0·80
AAZ13	0·12	BFX29	0·25	NKT274	0·20	OC206	0·90	7496	1·00
AC107	0·37	BFX30	0·25	NKT275	0·25	OC207	0·90	7497	6·25
AC126	0·20	BFX35	0·98	NKT277	0·20	OC209	0·90	74100	2·50
AC127	0·25	BFX63	0·50	NKT278	0·25	OC410	0·80	74107	0·50
AC128	0·20	BFX84	0·25	NKT301	0·40	OC460	0·20	74110	0·80
AC187	0·25	BFX85	0·30	NKT304	0·75	OC470	0·30	74111	1·45
AC188	0·25	BFX86	0·25	NKT403	0·75	OCP71	0·87	74118	1·00
ACY17	0·30	BFX87	0·25	NKT404	0·55	ORP12	0·50	74119	1·90
ACY18	0·25	BFX88	0·20	NKT678	0·30	ORP60	0·40	74121	0·60
ACY19	0·25	BFY10	1·00	NKT713	0·25	ORP61	0·42	74122	1·35
ACY20	0·20	BFY11	1·25	NKT773	0·25	S19T	0·80	74123	2·70
ACY21	0·20	BFY17	0·25	NKT777	0·38	SAC40	0·25	74141	1·00
ACY22	0·10	BYF18	0·25	O78B	0·38	SFT308	0·38	74145	1·50
ACY27	0·25	BFY19	0·25			ST222	0·38	74150	3·35
ACY28	0·17	BFY24	0·45	OA6	0·12	ST2231	0·63	74151	1·10
ACY39	0·50	BFY44	1·00	OA47	0·10	SX68	0·20	74154	2·00
ACY40	0·15	BFY50	0·22	OA70	0·10	SX631	0·30	74155	1·55
ACY41	0·15	BFY51	0·20	OA71	0·10	SX635	0·40	74156	1·55
ACY44	0·25	BFY52	0·22	OA73	0·10	SX640	0·50	74157	1·80
AD140	0·50	BFY53	0·17	OA74	0·10	SX641	0·55	74170	4·10
AD149	0·50	BFY64	0·42	OA79	0·10	SX642	0·60	74174	2·00
AD161	0·37	BFY90	0·65	OA81	0·08	SX644	0·75	74175	1·35
AD162	0·37	BSX27	0·50	OA85	0·12	SX645	0·75	74176	1·60
AF106	0·30	BSX60	0·93	OA86	0·15	V15/30P	0·50	74190	1·95
AF114	0·25	BSX76	0·15	OA90	0·08	V30/201P	0·75	74191	1·95
AF115	0·25	BSY26	0·18	OA91	0·07	V60/201	0·50	74192	2·00
AF116	0·25	BSY27	0·17	OA95	0·07	V60/201P	0·75	74193	2·00
AF117	0·25	BSY51	0·50	OA200	0·07	XA101	0·10	74194	2·50
AF118	0·62	BSY95A	0·12	OA202	0·10	XA102	0·18	74195	1·85
AF119	0·20	BSY95	0·12	OA210	0·25	XA151	0·15	74196	1·50
AF124	0·25	BT102/500R		OA211	0·30	XA152	0·15	74197	1·50
AF125	0·20		0·75	OAZ200	0·55	XA161	0·25	74198	4·60
AF126	0·17	BTY42	0·92	OAZ201	0·50	XA162	0·25	74199	4·60
AF127	0·17	BTY79/100R		OAZ202	0·42	XB101	0·43		
AF139	0·30		0·75	OAZ203	0·42	XB102	0·10	Plug in sockets —low profile	
AF178	0·55	BTY79/400R		OAZ204	0·30	XB103	0·25	14 pin DIL	0·15
AF179	0·65		1·25	OAZ205	0·42	XB113	0·12	16 pin DIL	0·17
AF180	0·52	BY100	0·15	OAZ206	0·42	XB121	0·43		
AF181	0·42	BY126	0·15	OAZ207	0·47	ZR24	0·63		
AF186	0·40	BY127	0·17	OAZ208	0·32				
AFY19	1·13	BY182	0·85	OAZ209	0·32				
AFZ11	0·60	BYZ13	0·25	OAZ210	0·32				

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.
Valves, Tubes and Transistors • Closed Sat. 1 p.m.-3 p.m.
Terms C.W.O. only Tel. 01-677 2424-7
All orders subject to V.A.T. at 10% rate. This must be added to the total order including postage.

FM TUNER THOUSANDS NOW IN USE

NELSON-JONES

Approved parts of this outstanding design (W.W. April 1971). Featuring 0·75μV sensitivity. Mosfet front end. Ceramic I.F. strip. Triple gang tuning, ¼V r.m.s. output level, suitable for phase locked decoder. Designer's own PCB S.A.E. please for lists.

Solid State Tuning Indicator.

High Performance Decoder also available.

PUSH BUTTON VARICAP

Tuning now available.

Six Position push button unit with individual frequency scales. Teak case and full metalwork matches the **Texan** amp. Please send for details.

LIGHT EMITTING DIODES (Red)

Improved Type panel or PCB mounting with free mounting clip—clear or black. Order LEDIA. Please add postage.

Monsanto miniature PCB mounting with radial leads. Order LED2. Please add postage.

NOW ONLY 35p each with connection data + V.A.T.

7 SEGMENT LED DISPLAY


0·325in Characters 0–9 and nine letters. TTL, DTL compatible. ONLY **£2·46** each, p.p. 10p. BCD–7Seg Dec Driver, **£1·30** (+ V.A.T.)

INTEGREX LIMITED, DEPT. P.E.

P.O. BOX 45, DERBY DE1 1TW

Tel.: Repton (0283 89) 3580

SINCLAIR IC12 £2·00

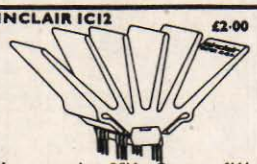

Max. supply 28V. Power 6W RMS. Complete with free printed circuit board and 44-page instruction booklet.

SWANLEY IC TOMORROW— £2·50

The World's most powerful IC amplifier. Similar to the above but operates at 35V max. supply and gives 12W RMS output. Manufactured for us by a leading semiconductor company. Supplied with our instructions and a 6-month guarantee, but no printed circuit.

SINCLAIR EQUIPMENT



Z30	£3·50	Stereo 60	£7·80
PZ5	£3·97	Z50	£4·25
PZ8	£6·60	PZ6	£6·40
AFU	£4·50		

Transformer for PZ8 £2·95.
Project 60 tuner £16·80.

EXECUTIVE CALCULATOR £50·00

PROJECT 60 KIT £2·50
Our extremely popular kit contains the extra capacitors, din plugs and sockets, cables and fuseholder needed to complete Project 60.

KITS FOR IC12 AND IC TOMORROW
Except for the power kits and speakers all items suit both integrated circuits.

DELUXE KIT
Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version **£1·45**. Stereo version with balance control **£3·30**.

POWER KIT FOR IC12
A set of components to construct a 28V 0·5A power supply **£2·27**. Also suitable Sinclair PZ5 **£3·97**.

POWER KIT FOR IC TOMORROW
A set of components to construct a 35V 1A power supply **£2·97**.

LOUDSPEAKERS FOR IC12
8 ohm types. 5" **£1·00**. 5" × 8" **£1·45**.

PREAMPLIFIER KITS
Type 1 for magnetic pickups, mics. and tuners with 3 position equalisation switch. Mono model **£1·20**. Stereo model **£2·20**. Type 2 for ceramic or crystal pickups. Mono 60p. Stereo **£1·20**.
SEND S.A.E. FOR FREE LEAFLET ON KITS AND TBA651.

S-DECS AND T-DECS



S-Decs	£1·44
T-Decs	£2·88
μ-Decs A	£3·00
16 dil IC carriers	£1·20

IC RADIO CHIP TBA651 £2·10
The world's most advanced IC radio chip. Contains RF Amp, oscillator, mixer, IF Amps, wide range AGC circuitry and voltage stabiliser. With data **£2·10**. Send S.A.E. for free leaflet. Kit of resistors, capacitors and IF filters **£1·75** extra.

SWANLEY ELECTRONICS

32 Goldsel Road • Swanley • Kent BR8 8EZ

Postage 10p per item. Please add 10% extra to total cost of order for VAT. Official credit orders from schools, etc., welcome. Full lists 10p post free. Send S.A.E. for free 8-page book on IC TOMORROW, IC12 kits and TBA651.

ANOTHER GREAT SHOPERTUNITIES SCOOP!

YES, "YOU'VE GOT THE WHOLE WIDE WORLD IN YOUR HANDS"! ALMOST UNBELIEVABLE! Think of the year 1984 and what might be produced then—now get the fantastic **ASTRAD 17** and **SEE** for yourself that the incredible Russians have done it all **NOW!** It's the radio perfectionist's dream come true! **THIS ONE SUPERSEDES ALL EARLIER MODELS!** It will probably make your present radio seem like a "crystal set"! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only **£18·50—a mere fraction of even today's Russian miracle price!** We challenge you to compare performance and value with **£80** radios! **★Send quickly, test on 7 day mail order appro. from receipt of goods—refund if not delighted. Elegant black and chrome finish facia, set in fabulous Cabinet built case—constructed of fine Russian hardwood in beautiful Teak Veneer finish—prevents vibration, ensures purer and sweeter tone than ever!** Volume controlled from a whisper to a roar that would fill a hall! **Much wider band spread, for absolute "pin-point" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity!** Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of space communications. **Yes, EVERY WAVEBAND** instantly at your fingertips **including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the earth during 24 hours a day including all normal transmissions. VHF: FM/USW, AM: LW, MW, SW, gets, locally, local and new stations not yet operational, and messages from all over the world! Expensive TURRET TUNER** side control waveband selection unit (as used on expensive T.V.'s!) Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output! ON/OFF volume and separate Treble and Bass tone controls for utter perfection of reproduction and tone! **Press-button dial illumination! Take it anywhere**—runs economically on standard batteries or direct through battery eliminator from 220/240V AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39in approx. **It's also a fabulous CAR RADIO. Can also be used through extension amplifier, tape recorder or public address system. SIZE** 14in × 10½in × 4½in overall approx. Magnificently designed, made to give **years of perfect service.** (U.K. service facilities and spares available for years and years to come, if ever necessary!). With WRITTEN GUARANTEE, manual with simple operating instructions and circuit diagram. PLUS Ultra sensitive earphone for personal listening. **ONLY £18·50** (with mains/battery eliminator **£2·25 extra). BOX, POST, ETC. 45p—NO MORE TO PAY! ★BUT WAIT, for only 75p extra** you get the sensational **"COMPUTERISED" WORLD TUNING GUIDE** (it enables you to time, pinpoint and get transmissions the whole world over—even a child can do it in a flash—**it even lets you know when to tune into the U.K., when abroad. NO GUESSING! NO MESSING! PLUS Standard "longlife" batteries.** (Sorry—We cannot change these new radios for any earlier model purchased.)

THOUSANDS of MILES REDUCED to INCHES?

1973 RUSSIAN RADIO TECHNOLOGY SHRINKS THE WORLD! *COMPUTERISED?

THIS FANTASTIC **EARTH SHRINKER**

YES, 24,901 miles SHRUNK TO ONLY 14" x 10½" x 4½" inches approx?

BRAND NEW FABULOUS **ASTRAD 17** PORTABLE RADIO & COMMUNICATIONS RECEIVER

WORLD WIDE RECEPTION THOUSANDS OF TRANSMISSIONS A STATIONS POUR IN FROM THE FOUR CORNERS OF THE EARTH!



28 TRANSISTORS AND DIODES! **WAVEBANDS:** STANDARD LONG and MEDIUM Plus 5 SHORT WAVEBANDS Plus ULTRA SHORT WAVES (V.H.F. AM. FM. MW. LW. USW.)

*MUST YOU PAY UP TO £80?

BATTERY MODEL **£18·50** BOX POST ETC. 45p

MAINS/BATTERY ELIMINATOR -£2·25 extra

FIRST TIME EVER! *NOW AVAILABLE WITH fabulous COMPUTERISED" WORLD TUNING GUIDE! NO MORE GUESSWORK— INSTANT DATA at your fingertips — enables you to TUNE IN A FLASH to transmissions the world over!

THIS OFFER ONLY FROM US!

BUY ONE FROM US! SAVE £21·60 NOW!

fabulous BRAND NEW **SOLID STATE** BATTERY/MAINS AC Combined V.H.F AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER

This equipment's got EVERYTHING!



WITH REMOTE CONTROL MICROPHONE

RECOMMENDED RETAIL PRICE £44

OUR PRICE **£22·40** CARR. ETC. 39p

Shopertunities "thunder" ahead with an offer that's FANTASTIC (even by our standards!). We've snapped up 500 magnificent machines. **Latest sensation in the world of sound!** First-class makers! Fabulous **VHF, AM/FM Radio AND Cassette Tape Recorder & Player combined & it also runs off standard batteries or mains.** (Simply plug in the 220/240V AC line cord.) **Record and play back anything, anywhere! RECOMMENDED RETAIL PRICE GENUINELY £44! WE OFFER AT ALMOST HALF PRICE!** Wonderful features: **★ Press-button Keyboard Control Panel or latest MASTER SWITCH CONTROL! ★ "MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic Leveller! ★ Separate ON/OFF and HI-LO volume controls! ★ Heavy duty built-in speaker! ★ Earphone** (for personal listening or "monitoring") **and extension speaker sockets! ★ Remote control microphone! ★ Built-in swivel telescopic extension aerial (24in approx.)! Magnificently made case with carry handle. (DESIGNS VARY SLIGHTLY.)** Takes standard 30, 60, 90 or 120-minute Cassette Tapes, obtainable everywhere. **AND the amazing built-in full circuit VHF, AM/FM Radio** gives you superb clarity of tone, incredible station **selection.** Unique rotating Station Selector Dial—gets, locally, city and regional stations in every part of the country, plus B.B.C. National, VHF. Picks up dozens of foreign stations. **Fabulous in your car!** You could pay £ £ £'s more for a Car Radio or Car Cassette player ALONE! **£22·40, carr. etc., 39p. —NO MORE TO PAY! Complete with simple instructions, remote control microphone with on/off switch and microphone stand. WITH WRITTEN GUARANTEE.** Send quickly, test on 7 day mail order appro. from receipt of goods—refund if not delighted. Or call.

BONUS OFFER: Batteries and Cassette Tape 28p extra if required.

CALLERS: ACCESS & BARCLAYCARDS ACCEPTED AT BOTH STORES

FIRST TIME EVER! *SAVE £15·21!

BRAND NEW **AC/DC BATTERY/MAINS Cassette TAPE RECORDER & PLAYER**

With remote control microphone.



FIRST CLASS MAKERS

WE COULD CHARGE UP TO £26·97!

OUR PRICE **£11·76** POST ETC. 34p

THE ONE STEP FORWARD EVERYONE HAS WAITED FOR! **NOW** a superb de-luxe portable **BATTERY/MAINS** tape recorder and player—and incredible **Shopertunities** bring it to you for **ONLY £11·76!** Due to our cut price we cannot name first-class makers—but rest assured **you're getting one of the BEST!** Expensive **"PIANO KEYBOARD" CONTROL PANEL** (or latest **MASTER SWITCH control) AND AUTOMATIC LEVEL CONTROL.** No fiddling with awkward tape and reels, **just "slap-in" a cassette and off you go!** (Takes 30, 60, or 90 minute standard cassette tapes obtainable everywhere). **Amazing** performance ensures perfect tapings and superb reproduction! Remote control microphone. Rapid Rewind! Fast forward! Beautiful tone from a whisper to a roar! Completely self contained—**record anywhere,** indoors or out! **Runs on standard batteries AND 220/240V AC mains.** Separate jacks for remote control microphone, etc. Size 9½in × 5in × 2½in approx. Design can vary slightly. With carry handle. WRITTEN GUARANTEE and full instructions. (Recommended selling price £26·97!) **OUR PRICE ONLY £11·76, post, etc. 34p—NO MORE TO PAY! ★Send quickly, test on 7 day mail order appro. from receipt of goods—refund if not delighted.** Or call at either of our stores.

BONUS OFFER:—Cassette tape, standard batteries AND Microphone stand 55p extra if required.

Order by post to Uxbridge Road address or call at either store.

Bargains galore at both stores.—**(COMMERCIAL TRAVELLERS PLEASE NOTE:** Merchandising office at Holborn Store.)

SHOPERTUNITIES LTD.

Dept. PE/30, 164 UXBRIDGE RD. (facing Shepherds Bush Green), **LONDON W12 8AQ. (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN** (opposite Chancery Lane), **LONDON, W.C.1. (Thurs. 7 p.m.) BOTH OPEN MON. TO SAT. 9 A.M. TILL 6 P.M.**

I.L.P. (Electronics) Ltd

100 WATTS!



* NO EXTERNAL COMPONENTS
* MECHANICALLY & ELECTRICALLY ROBUST
* INTEGRAL HEATSINK
* HERMETICALLY SEALED UNIT
* ATTRACTIVE APPEARANCE
* LOW COST
* BRITISH BUILT

With the development of the HY200, ILP bring you the first **COMPLETE** Hybrid Power Amplifier.

COMPLETE: because the HY200 uses no external components!

COMPLETE: because the HY200 is its own heatsink!

By the use of integrated circuit technique, using 27 transistors, the HY200 achieves total component integration. The use of specially developed high thermally conductive alloy and encapsulant is responsible for its compact size and robust nature.

The module is protected by the generous design of the output circuit, incorporating 25amp transistors. A fuse in the speaker line completes protection.

Only 5 connections are provided, input, output, power lines and earth.

OUTPUT POWER: 100 watts RMS; 200 watts peak music power. **INPUT IMPEDANCE:** 10kΩ. **INPUT SENSITIVITY:** 0Dbm (0·775volt RMS). **LOAD IMPEDANCE:** 4–16Ω. **TOTAL HARMONIC DISTORTION:** less than 0·1% at 100 watts, typically 0·05%. **SIGNAL : NOISE:** better than 75Db relative to 100 watts. **FREQUENCY RESPONSE:** 10Hz–50KHz ±1Db. **SUPPLY VOLTAGE:** ±45volts. **APPLICATIONS:** P.A., Disco, Groups, Hi-Fi, Industrial. **PRICE: £14·90** inc. VAT & P&P. Trade applications welcomed.

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

Please note we reserve the right to substitute at our discretion updated versions of advertised designs where applicable.

PE

ANOTHER SENSE

THIS month we break new ground in applied electronics. Most of the characteristic human senses can be simulated in some fashion by electronic means, but smell and taste are much more difficult for non-biological systems to imitate. Only just recently has it become possible to simulate in some degree the sense of smell without complex and costly chemical devices. This is due to a newly developed semiconductor transducer which responds to the presence of molecules carried in the air.

This particular kind of transducer is a valuable and timely addition to the field of instrumentation and control. Its appearance is especially relevant in these days of public consciousness about the environment and concern for a curb on all objectionable and harmful pollution of the atmosphere. Electronics is now equipped to wage an increasingly effective part in the battle of the environment.

Considering the actual trandsucer itself: now that it has been realised, the gas and vapour detector seems quite simple and rudimentary in its practical form. This apparent simplicity (a common enough outward characteristic of many solid state devices) should not give cause to underestimate the technical achievement it represents. Although the powers of discrimination between different vapours and odours are limited, this transducer is obviously but the first in a series of devices of ever increasing sensitivity and selectivity that will appear in due course. In a wider context the emergence of such a device must be recognised as but one reward from a continuing process of exploration into semiconductor materials which has followed in the wake of the original transistor breakthrough of 25 years ago. This research, conducted on a world wide basis, frequently gives birth to new devices and these largely constitute the power and strength behind electronics, particularly when they enable this technology to penetrate and influence other fields.

With the creation of a kind of electronic nose, interest is likely to be directed towards a simulation of the human taste buds. This, we are given to understand, is a rather more formidable problem. But problems involving electronics usually do find their solution, as suggested in the previous paragraph.

Finally, a slight digression in order to discuss a (not too serious) question of terminology. There are some who might question the propriety of applying biological descriptions to inanimate devices or equipments. True, we have the outstanding example of the poor old computer which has long suffered from the over-generous honour accorded it by the popular title "electronic brain". We could be strictly objective and refer to this month's feature project as simply a gas and vapour detector. However, "electronic nose" seems a rather apt and certainly more colourful description for this unusual innovation in the home constructor field. Its applications are serious enough, however, as will soon be appreciated.—F.E.B.

Editor
F. E. BENNETT

Editorial
D. BARRINGTON
G. GODBOLD
S. R. LEWIS B.Sc.


Art Dept.
J. D. POUNTNEY *Art Editor*
J. A. HADLEY
R. J. GOODMAN

Advertisement Manager
D. W. B. TILLEARD (*Manager*)
Phone: 01-634 4202

P. J. MEW
Phone: 01-634 4210

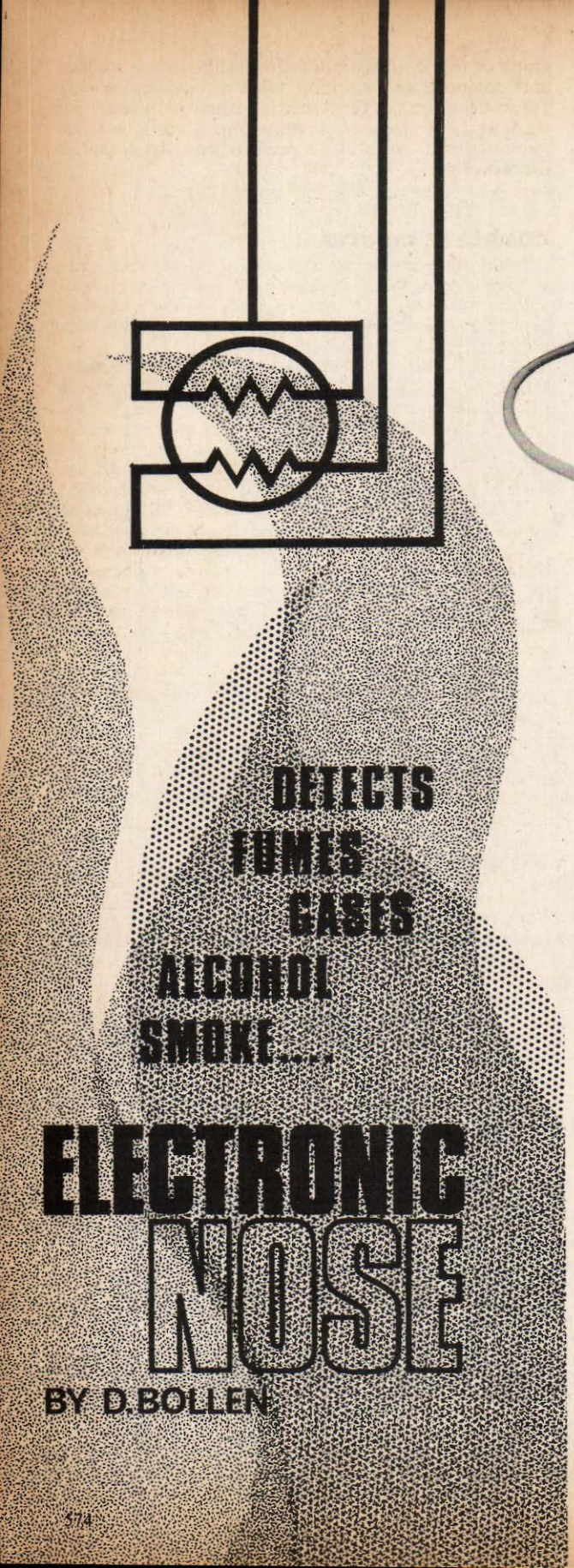C. R. BROWN, *Classified*
Phone: 01-634 4301


Editorial & Advertising Offices:
Fleetway House, Farringdon St.,
London EC4A 4AD
Phone: *Editorial* 01-634 4452
Advertisements 01-634 4202



DETECTS FUMES GASES ALCOHOL SMOKE....

ELECTRONIC NOSE

BY D.BOLLEN

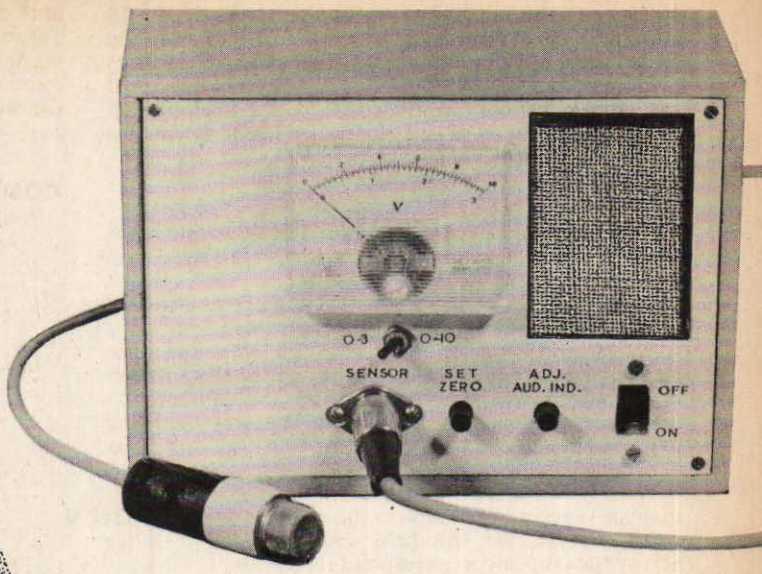

THIS battery operated instrument is designed around a new type of semiconductor sensor which responds to certain gases, vapours, and smoke particles. The sensor cannot distinguish between different smells but it does allow an assessment to be made of the relative concentration of a contaminant in air. Applications include breathalyser, fuel vapour and firedamp detector, air pollution meter, paint dryness indicator, and gas leak locator.

The electronic nose has a meter readout scaled in arbitrary units of 0–3 and 0–10, as well as an audible indicator giving a note of rising pitch proportional to gas or smoke intake. As a rough indication of sensitivity, a measurable response is obtained from 1 cubic millimetre of alcohol evaporated in a volume of air the size of a tea-chest, this is approximately 10,000 times less than the concentration needed to form an explosive mixture.

SEMICONDUCTOR GAS SENSOR (SGS)

The gas sensor consists of two heating filaments embedded in an *n*-type semiconductor chip, see Fig. 1. Only one filament is used for heating the chip, the other merely serving as an ohmic contact. Gas or smoke impurities reduce the intrinsic resistance of the chip, as measured between the two heating filaments, and chip heat determines the rate at which an impurity is absorbed and deabsorbed.

The Japanese manufacturers of the gas sensing device used in this article are not very informative on the working principle involved, but an educated guess is that the semiconductor chip undergoes temporary doping in the presence of air impurities, and this lowers intrinsic resistance in the same way as it does with other types of semiconductor. Heat is required to convect the impurity through the porous structure of the chip, and for deabsorption when the source of contamination is removed.

Heater requirements are around 1·2V maximum at 750 milliamps, and the device runs warm to the touch.

The chip is non-polarised and will conduct in either direction. Chip resistance is in the range 10 to 50 kilohms in clean air, falling to less than 1 kilohm in the presence of moderate concentrations of gases such as hydrogen, carbon monoxide, methane, propane, coal gas, and the vapours from alcohol, petrol, acetone, etc. A whiff of tobacco smoke is also sufficient to cause a similar resistance change.

BASIC CIRCUIT

Fig. 2 shows the basic circuit of the electronic nose, where the voltage across the SGS chip is compared with a fixed voltage at the junction of R1 and R2. In the absence of an air contaminant, VR1 is adjusted so that both voltages are equal and the meter reads zero.

When gas or smoke is detected, the chip resistance decreases and "pulls down" the voltage at the junction of H2 and VR1 slider, thus causing the voltmeter to display a reading. Tests indicate that the resulting meter reading is linearly related to contaminant concentration.

With its balanced configuration, the Fig. 2 circuit is insensitive to small changes in the voltage of battery B2; when the reference voltage drops, so does the voltage across the chip, by a corresponding amount.

RESPONSE TIME

The response of the Fig. 2 circuit, to the sudden application and removal of a "smell", is shown by the graph of Fig. 3. Absorption time is about two seconds and complete deabsorption takes about 80 seconds. However, when the instrument is employed merely for tracing the source of a contaminant, and not for measurements, there is no need to wait for complete deabsorption.

COMPLETE CIRCUIT

In the complete circuit of the nose, Fig. 4, a reference voltage is provided, as before, by R1 and R2, and VR1 adjusts meter zero. The sensor is contained in a small probe and leads connecting to the measuring circuit *via* plug and socket PL1 and SK1.

A 100μA meter movement, with two switch selected series resistors R3 and R4, is used as a voltmeter in Fig. 4. Because the voltmeter places a significant load on the circuit, particularly when switched to the 0–3 range, the values of R3 and R4 are compensated to give a true relationship between ranges. In the 0–10 S1 position, meter full scale is represented by 4V.

Voltage controlled oscillator TR1 and TR2 gives an audible indication of changes in SGS resistance. VR2 sets the oscillator frequency to zero when the meter reading is zero. When SGS resistance decreases, the voltage across VR2 slider and the positive supply rail increases, thus applying a bias current to TR1 base. C1 charges up via TR1 and R5 at a rate dependent on the TR1 bias current.

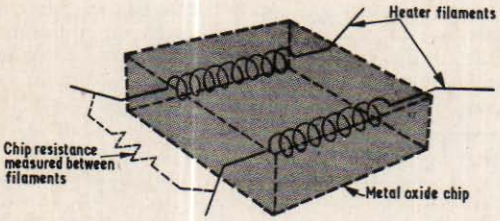


Fig. 1. Construction of the semiconductor gas sensor

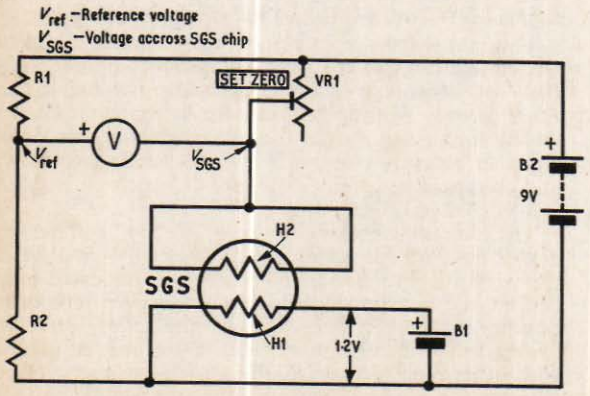


Fig. 2. Basic circuit of the electronic nose


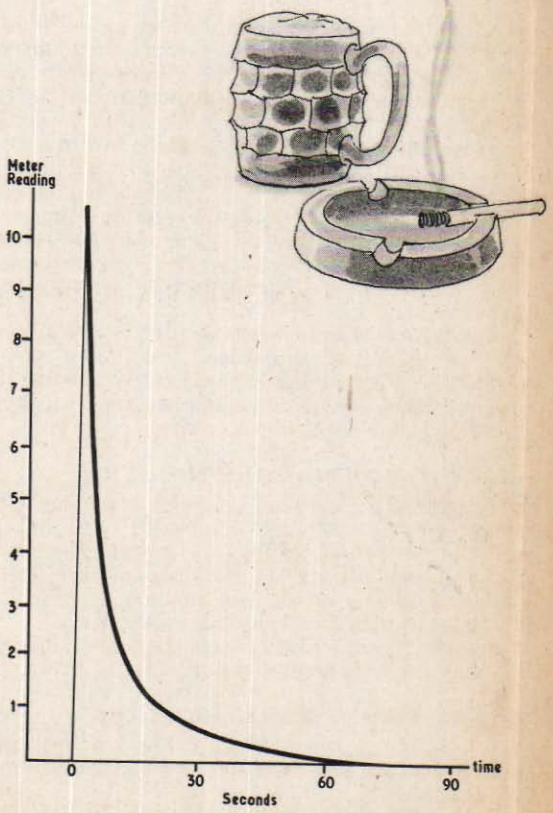


Fig. 3. Gas sensor response time graph

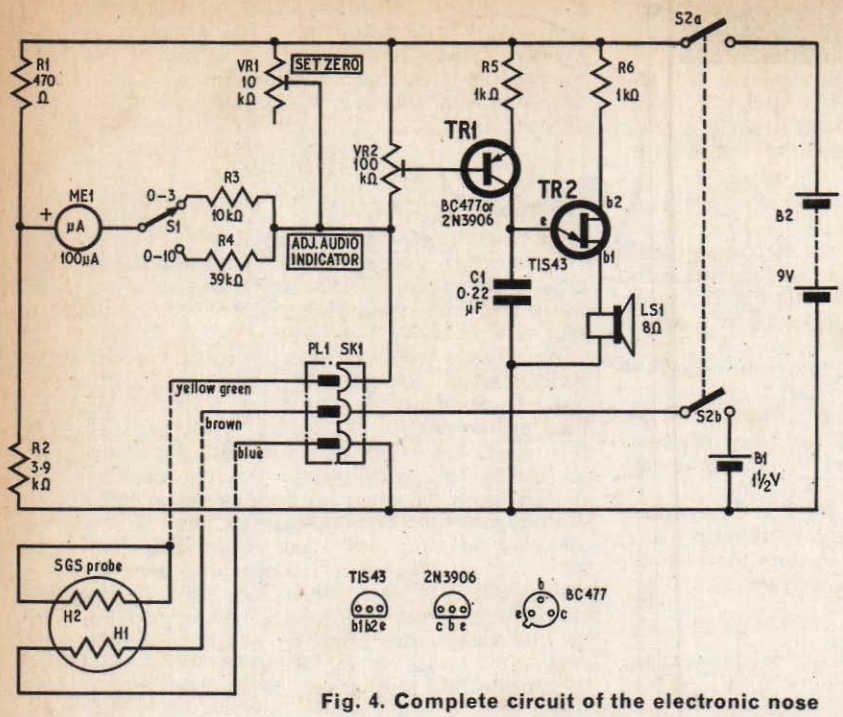

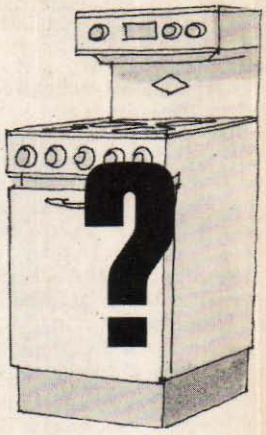


Fig. 4. Complete circuit of the electronic nose

At the threshold voltage of the unijunction transistor TR2, C1 is rapidly discharged through the loudspeaker LS1 to give an audible "click". For a small decrease in chip resistance, the audible indicator clicks like a Geiger counter, but if the chip resistance continues to decrease the clicks will run together to form a note of rising pitch which is related to the meter reading.

Battery B1 in Fig. 4 is a U14 gas lighter cell of nominal 1·5V. When loaded by the SGS heater, the internal resistance of the cell, plus the small resistance presented by interconnecting wiring, will give a voltage drop of around 0·3V, thus only 1·2V is finally applied to heater H1.

A reduction of heater voltage as B1 ages will increase absorption and deabsorption times, but will not materially affect calibration accuracy. Life of a U14 will be approximately 1 week when the instrument is used for two to three hours per day.

CIRCUIT BOARD CONSTRUCTION

Transistors, fixed resistors, and capacitor C1 are mounted on a 1·9in by 1·5in piece of 0·1in matrix plain circuit board, see Fig. 5. Insert terminal pins in the positions shown, so that they project from the underside of the board, then component leads can be pushed through and soldered to the pins, or other component leads. The unused portion of the circuit board is used for mounting purposes.

FRONT PANEL CONSTRUCTION

Front panel layout is shown in Fig. 6, and the photographs, but this will depend to some extent on the size of meter used.

Position the loudspeaker in the top left-hand corner at the back of the panel and draw round it with a pencil. Find the best position for ME1, to clear LS1 and B1, and mark this out. Next draw in hole centres for the controls, leaving a clear space above VR1 and VR2 for a short section cut from a plastic clip of the type used to hang posters, this makes an ideal circuit board mount.

Drill and cut all holes, including a loudspeaker aperture shaped to suit the space available, and apply lettering to the front of the panel. If VR1 and VR2 are miniature printed circuit mounting knob pre-sets, these can be glued to the front panel, along with the circuit board mounting clip, loudspeaker gauze, and loudspeaker. It is best to employ a semi-flexible glue as this will allow components to be prised off for replacement.

BOX AND BATTERY MOUNT

The U14 cell for B1 is held by a spring steel clip which is bolted to the back of the box and serves as the negative connection. A strip of brass makes contact with the positive battery pole. If the box is made of metal, the brass strip should, of course, be insulated from the box. A simple metal clip serves to hold B2 in position.

PROBE DETAILS

Details of the sensor probe are given in Fig. 7. The probe lead should not be more than 1 metre long, and all solder connections should be really secure, to minimise heater voltage drop. Try to avoid contaminating the SGS gauze with any material which might influence chip resistance, such as glue or paint. H1 and H2 heater pins are interchangeable.

ADJUSTMENT AND TESTING

Set VR1 and VR2 to the mid-position, S1 to the 0–10 range, and switch on. The meter pointer should

COMPONENTS . . .

Resistors
R1 470Ω
R2 3·9kΩ
R3 10kΩ 2% metal oxide
R4 39kΩ 2% metal oxide
R5 1kΩ
R6 1kΩ
All 10% ½W except where stated

Potentiometers
VR1 10kΩ } miniature knob presets
VR2 100kΩ }

Capacitor
C1 0·22μF

Transistors
TR1 BC477 *or* 2N3906
TR2 TIS43

Sensor
SGS1 Semiconductor gas sensor (available from Trampus Electronix, P.O. Box 29, Bracknell, Berks.)

Meter
ME1 100μA f.s.d.

Batteries
B1 U14 1·5V gaslighter
B2 PP6 9V

Loudspeaker
LS1 2½in dia, 8Ω

Switches
S1 Miniature single pole toggle
S2 D.P.D.T. slide

Plug and Socket
PL1 3-way DIN
SK1 3-way DIN

Miscellaneous
Plain 0·1in matrix board 1·9in × 1·5in. Terminal pins. 2A 3-core mains cable, 1 metre. Connecting wire.

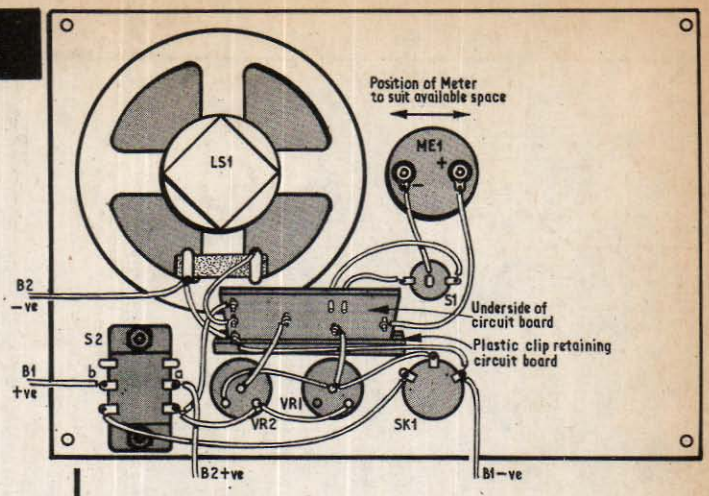


Fig. 6. Front panel interwiring details

touch the zero stop and then rise quickly to beyond full scale, accompanied by a note of rising pitch from the loudspeaker. After about a minute, the meter reading and audio note will begin to decline as the SGS decontaminates. Because absorption takes place when the SGS is not in use, and reaches a high level, five minutes should be allowed for initial warm up and complete deabsorption when the instrument is first switched on.

Now trim VR1 for a reading of 0·2 on the 0–3 range and adjust VR2 for a series of slowly repeated clicks from the loudspeaker, these should cease when the meter is zeroed.

After the initial warm up period the meter zero reading should remain reasonably stable, but remember that the SGS can detect slight traces of smoke and other contaminants in an ordinary room so some fluctuation just above zero will occur. In the event of erratic meter readings, the wiring between B1 and H1 should be suspected.

Out of doors, and in strong draughts, the meter reading may drop below zero due to cooling of the semiconductor chip, this effect can be minimised by enclosing the probe in a simple windshield.

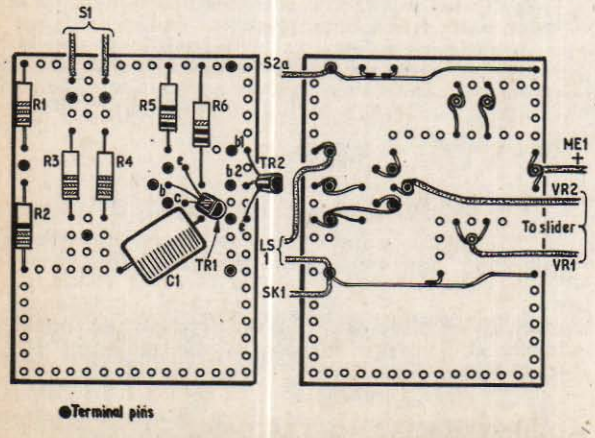


Fig. 5. Layout of the components on the perforated board


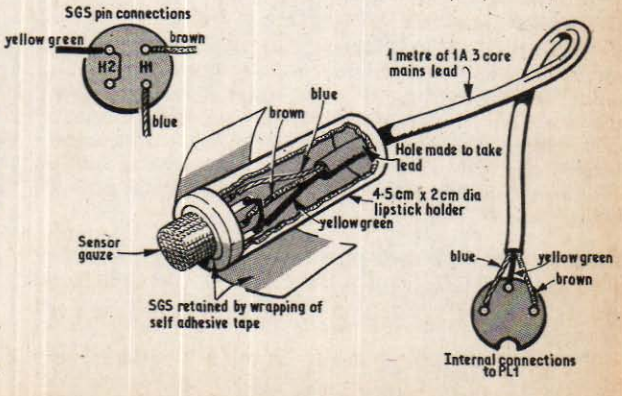


Fig. 7. Details of the sensor probe

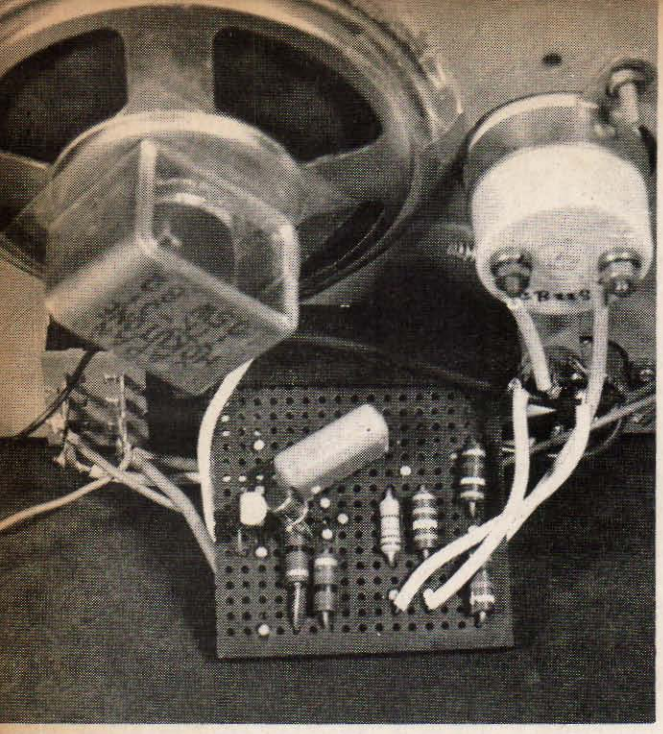

Photograph of the rear of the front panel showing Veroboard and meter connections

To test the nose, move the probe near to an open bottle of methylated spirits or blow smoke at the sensor gauze.

APPLICATIONS

If the probe is gently breathed upon one or two hours after drinking a pint of beer, this should be sufficient to cause a reading of 10. The nose can therefore act as an ultra-sensitive breathalyser. Similarly, it may be possible to assess the alcoholic content of drinks by placing the sensor at a fixed distance from a sample of given volume and temperature.

Minor gas leaks from cigarette lighters, camping stoves, and domestic cookers are readily detected, with the aid of the audible indicator, as are fumes from storage batteries and many volatile chemicals. The electronic nose is particularly useful for detecting odourless gases.

When placed near the exhaust of an internal combustion engine, the SGS will respond to carbon monoxide, as well as oil fumes and unburnt fuel, so the reading obtained can be taken as a general measure of engine tune and condition. However, for really accurate results, the exhaust gases should be captured in a bottle or can, the contents of which are "sniffed" in a draught free environment.

For air pollution measurements, the instrument should first be zeroed in a clean air zone, preferably out in the country, and then be taken to the area to be tested. Alternatively, comparative readings can be taken in a city environment by adjusting the meter to read 1 unit instead of zero. A high reading does not necessarily suggest serious pollution as this could be caused by a wide range of harmless volatiles, such as perfumes and deodorants! ★



NEXT MONTH

....BATTLE CHESS

Expand your concept of Chess by introducing realistic "Battle" conditions into the game. Using simple electronic concepts Battle Chess avoids the boredom of Chess played as a court intrigue and takes it into the realms of the military struggle, where factors such as the strength of a piece, its distance from its fellows, morale of a side, are all considered in each individual conflict

AUDIO COMPRESSOR...

The Audio Compressor is a unit which gives a constant output level for a wide range of input levels. It eliminates the need for constant level adjustment when using a microphone with a tape recorder and can also be used with amateur transmitting equipment to avoid the possibility of overmodulation

MEGOHMMETER...

Both the home electrician and the electronics experimenter will find uses for this simple to build high voltage megohmmeter.

Around the home it can be used to check wiring systems, or to detect dampness in walls. In electronics it can be used to locate poor insulation which could cause trouble in high impedance circuits

SYNTHESISER-7

Ring Modulator and Spring Line Amplifier

The ring modulator enables you to create unique exciting space-age sounds within the range of 25Hz–20kHz.

PRACTICAL ELECTRONICS

AUGUST ISSUE ON SALE JULY 13, 1973



BY FRANK W. HYDE

OUTER HEBRIDES ACTIVITY

In aerospace activities the more glamorous and spectacular events command most attention. The fact is that other very important projects are proceeding which seldom appear in the news. One is the work that goes on at South Uist in the outer Hebrides.

In one day during April this year seven British *Petrel* rockets were launched. This is the first time that more than three launches a day have been made. Each rocket carried a payload constructed at the Science Research Council's Radio and Space Research Station at Slough.

The object of the launchings was to study the ionisation of the atmosphere above 60km (40 miles) altitude. The experimental data gained will demonstrate the development of the D-region of the ionosphere through a day which will assist the checking of the theoretical work in progress at the research station.

Each payload carried a number of experiments dealing with:—

1. Measurements of the electron concentration and the collision frequency of the electrons due to Faraday rotation and differential absorption at three radio frequencies.
   These frequencies are transmitted from the ground to the rocket.

2. Measurements of electron concentration fine structure using a Langmuir probe designed for this special purpose.

3. Measurement of the intensity of the solar ultraviolet radiation at 1216Å (the Lyman alpha region) and the concentration of molecular oxygen as a result of the atmospheric absorption of this frequency of radiation.

4. The measurement of X-rays from the Sun in the range 2–8 Ångstrom units.

5. A new experiment which was developed in collaboration with the Max Planck institute at Lindau, West Germany and the University College of Wales at Aberystwyth, to measure the concentration of atomic oxygen in the ionosphere by the manner in which corrosion takes place of thin silver film..

6. The housekeeping functions of the vehicle, that is, the attitude of the rocket to the Sun, the slant range of the rocket from the launching site, the instrumentation of temperature etc.

EXERCISE ACHIEVED

The rockets all reached altitudes of some 140km (90 miles) and measurements were transmitted by each rocket to the ground station on South Uist and recorded on tape.

The data shows that the objects of the exercise have been achieved although some problems were met, such as postponements due to gale force winds and spectacular, though from the project point of view unwanted, aurora displays. The performance of this rocket, which is 7½ inches in diameter and nine feet long, has shown that it can be safely launched in near gale force winds.

The project scientist Dr P. H. G. Dickinson of RSRS has praised the support he has received from the U.K. Atomic Energy Authority and from the Army which was responsible for the safety of the range and the surveillance radar on St Kilda. The *Skylark* rocket was designed and made by Bristol Aerojet.

ARGENTINA AND THE SKYLARK

Two test firings have been carried out by a British team for the Argentine government. This is an attempt to use *Skylark* as an Earth resources rocket with the aim at finding a cheaper method of carrying out such surveys.

A combined team from the British Aircraft Corporation and the Royal Aircraft Establishment, Farnborough, launched the rockets from a transportable launcher to a height in excess of 240km. The payloads consisted of four cameras with different lenses and different films. The descent of the payload was by parachute.

Recovery was very rapid as helicopters were used.

Some 640 photographs were obtained taking in a large part of Argentina. The pictures will be analysed by teams from Reading University and the Instituto Nacional de Technologia Agropechuaria of Argentina.

The valuation made will be in terms of land use and crop inventory.

SOVIET SATELLITES

The Soviet Union launched more than three times the number of *Cosmos* photo-reconnaissance satellites than the United States during 1972. In spite of this only 25 per cent more time was logged by the U.S.S.R. amounting to 366 days, compared with 295 days for the United States, which used only eight satellites.

It would appear that there was some acceleration of effort after the international agreement was signed. Eighty per cent of the satellites were of an advanced design with the provision of a rocket that can be vernier controlled which makes it possible to direct the satellite over a specific target.


The cameras used are probably of high resolution and narrow angle to get greater detail.

The satellites are not just used for mapping strategical situated industrial plants. There is a more practical use for them. Two of the satellites were launched at 81 degree orbits and used to check ice packs and sea lanes. Another satellite enabled information about the conditions to be applied to the sea routes with the result that a flotilla of ice breakers and cargo vessels were able to make a safe trip from the Yenisei river to Murmansk. The U.S.S.R. attribute the success to the availability of accurate information from the satellites.

PIONEER

The second Jupiter probe, *Pioneer G*, is now on its way. It will take over from *Pioneer 10* if that vehicle should have difficulty when in the vicinity of Jupiter.

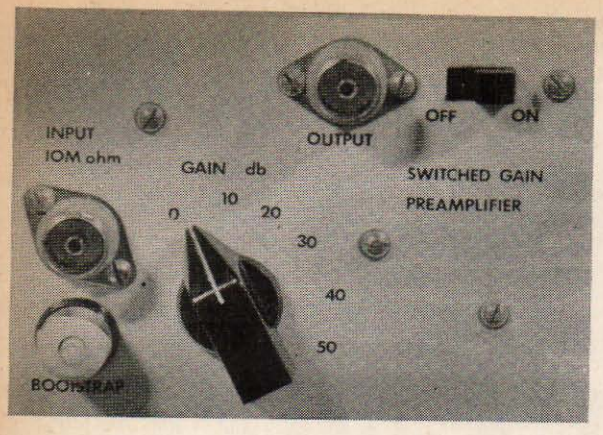The conditions there could be such that high level radiation could damage the spacecraft. If however, the fly-by is successful the second vehicle will have a slightly different programme. *Pioneer G* or *Pioneer 11* as it will be known will approach within 27,000 miles of the giant planet.



Switched Gain Preamplifier

By D. Crocker

THE amplifier to be described was designed to serve as a general purpose unit for a wide range of applications. It may be used, for example, between a signal source and a power amplifier to increase sensitivity, as an a.c. coupled oscilloscope preamplifier, a monitor amplifier to feed a crystal earpiece directly, or as an impedance matching device for coupling a crystal or ceramic pickup or a crystal microphone to an amplifier having a low input impedance.

In order to make the amplifier as versatile as possible, it was decided that a variable gain of up to 50dB was required together with a wide band width and high input and low output impedances. It should also have a low power consumption so that it may be run from batteries, making it self contained.

CIRCUIT DESCRIPTION

The complete circuit is shown in Fig. 1. In order to obtain a high input resistance, use of a field effect transistor is made in the first stage. Unlike a bipolar (conventional) transistor, that is a voltage operated device drawing very little current from the input signal. The current flowing between the source and drain terminals is varied by the voltage between the gate (the third terminal) and the source.

This varying current is fed to the base of a *p-n-p* transistor, TR2, comprising the second stage.

Since it is desirable to apply negative feedback to the source of TR1 in order to accurately determine the gain and widen the frequency response, the open loop gain (i.e. the gain before feedback is applied) should be above 3,000 for a closed loop gain of 50dB. Although the phase shift between TR1 source and TR2 collector is the required 180 degrees (TR2 having provided this), the gain provided would be much less than 1,000 if TR2 was given a simple resistor as a collector load. Another common emitter stage cannot be used as it would provide an extra 180 degree phase shift, making the feedback positive; an emitter follower, TR3, has therefore been used.

As this can provide no voltage gain by itself, R9, the collector load of TR2, has been bootstrapped by C4. This makes R9 appear to be in parallel with TR3 emitter-base junction, and since the effective resistance of this is lower than R9, most of TR2 collector signal current flows through TR3, giving rise to an amplified collector/emitter current in TR3 which flows through R12, developing an output voltage across it.

SPECIFICATION

Gain
Switched gains of 0, 10, 20, 30, 40, and 50dB

Bandwidth
Low frequency: —3dB at 10Hz
High frequency: —3dB at:
200kHz (50dB gain)
500kHz (40dB gain)
800kHz (30dB gain)
>800kHz (0, 10 or 20dB gain)

Maximum output
12V p-p (no load)
7V p-p (10kΩ load)
1·5V p-p (1kΩ load)

Slewing rate
Approximately 10V/μS minimum

Noise
Referred to input: approx. 150μV p-p (input open)
approx. 25μV p-p (input shorted)

Supply current
Approximately 1·2mA

Input resistance
12MΩ with S3 out.

The overall effect of the emitter follower TR3 and bootstrapped resistor R9 is to make the collector load resistance of TR2 very high, so that TR2 gives a high voltage gain.

FEEDBACK

Negative feedback is applied from the output to TR1 source through R11. As well as enabling the gain to be varied, this stabilises d.c. conditions throughout the amplifier and reduces its output impedance. When S1 is set for unity gain (0dB), full negative feedback is applied; for higher gains resistors R4 to R8 are switched in to reduce the amount of feedback.

For an amplifier of this sort, the gain is given by the formula

$$G = \frac{A(Rs + Rf)}{Rf + Rs.A} \qquad \text{if } A \gg 1$$

or

$$G = 1 + \frac{Rf}{Rs} \qquad \text{if } A \gg G$$

In this circuit A, the open loop gain, is between 3,000 and 7,000 depending on the load. Rf is R11 of Fig. 1 and Rs is the resistor switched in by S1. This resistor is connected in series with C3 in order not to disturb the d.c. conditions.

The current consumption of the amplifier has been reduced to about 1·2mA by giving R12 the rather high value of 10kΩ. This limits the maximum output available when a low impedance is used to the figures given in the specification. Whilst this has proved to be satisfactory, any constructor requiring a higher output current capability can decrease the value of R12 (but not below about 2kΩ) at the expense of reduced battery life.

an open loop gain of over 6,000, so that over 67dB of feedback is applied when the amplifier is set for unity gain, this form of instability has not occurred in the prototype.

CONSTRUCTION

In order to avoid hum pick-up at the high impedance input, the amplifier is constructed in an aluminium box which provides screening. Most of the circuitry is constructed on a piece of 0·1in matrix Veroboard measuring 25·4mm × 50·8mm.

Before mounting the components, breaks are made in the copper strips as shown in Fig. 2 and terminal pins are inserted from the copper side of the board. These should then be soldered in place and tinned.

The pins in row 7 support the screens; these are made from 2 pieces cut from tin measuring about 9mm × 33mm and 17mm × 33mm. They are flattened, cleaned, and one side of each is coated with solder. After placing small pieces of p.v.c. insulating tape between the 5 terminal pins over rows B, D and F, the

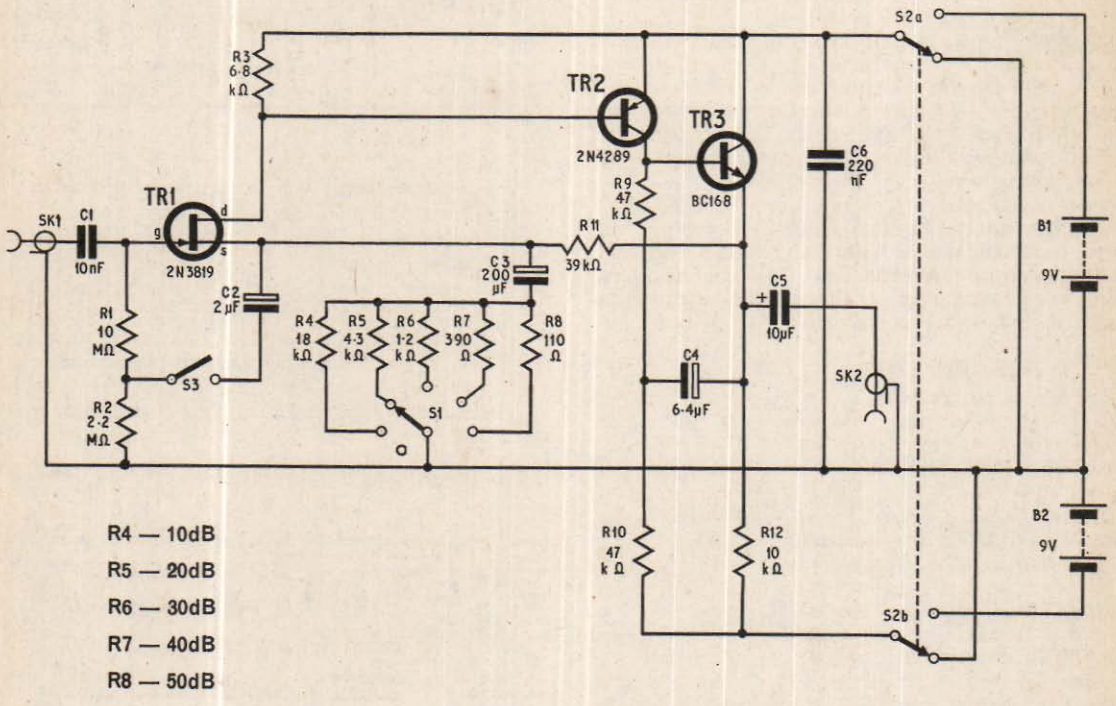


Fig. 1. Circuit diagram of preamplifier.

Since the output offset voltage may be positive or negative, the output capacitor C5 is a tantalum type; these can withstand small reverse voltages.

STABILITY

There are two ways in which an amplifier of this sort might be unstable. First, since the amplifier has a high, non-inverting gain and a high input impedance, feedback from the output to the input can easily occur causing oscillation. This is prevented by placing an earthed metal screen on the circuit board and using co-axial input and output connectors.

Secondly, due to extra phase shift in the amplifier, the feedback through R11 could become positive at high frequencies. In spite of the fact that the amplifier has

screens are soldered in place on the terminal pins in the position shown in Fig. 2. The smaller piece of tin is fitted on the copper side of the board. The components may then be wired in the positions shown in Fig. 3. Component wires should be sleeved where appropriate. An aluminium box measuring 4in × 2¾in × 1¼in with lid is required. The lid is drilled to accommodate the switches and sockets and these fitted.

MOUNTING THE BOARD

In order to mount the circuit board, one face of a ¾in 6 B.A. tapped hexagonal pillar is tinned and soldered to the screen on the copper side of the board, placing it approximately below hole F8 (see Fig. 2), without allowing the screen to part from the pins. The pillar



COMPONENTS . . .

Resistors

R1	10MΩ
R2	2·2MΩ
R3	6·8kΩ
R4	18kΩ
R5	4·3kΩ
R6	1·2kΩ
R7	390Ω
R8	110Ω
R9	47kΩ
R10	47kΩ
R11	39kΩ
R12	10kΩ

All ⅛W 5% carbon

Capacitors

C1	0·01μF miniature polyester
C2	2μF 16V miniature electrolytic
C3	200μF 6·4V miniature electrolytic
C4	6·4μF 25V miniature electrolytic
C5	10μF 25V tantalum bead electrolytic
C6	0·22μF miniature polyester

Transistors

TR1	2N3819
TR2	2N4289
TR3	BC168B *or* BC169

Switches

S1	2 pole 6 way miniature wavechange switch (only 1 pole used)
S2	d.p.d.t. slider switch
S3	s.p.s.t. push on/push off switch (see text)

Miscellaneous

SK1, SK2 Surface mounting co-axial sockets (2 off). B1, B2 9V PP3 batteries (2 off). Aluminium box 4in × 2¾in × 1½in with lid 0·1in matrix Veroboard 2in × 1in. Veropins for 0·1in matrix Veroboard (12). 6BA bolts (¼in), nuts and washers ⅜in or ¼in. Terry clips (2). PP3 battery connectors (2)

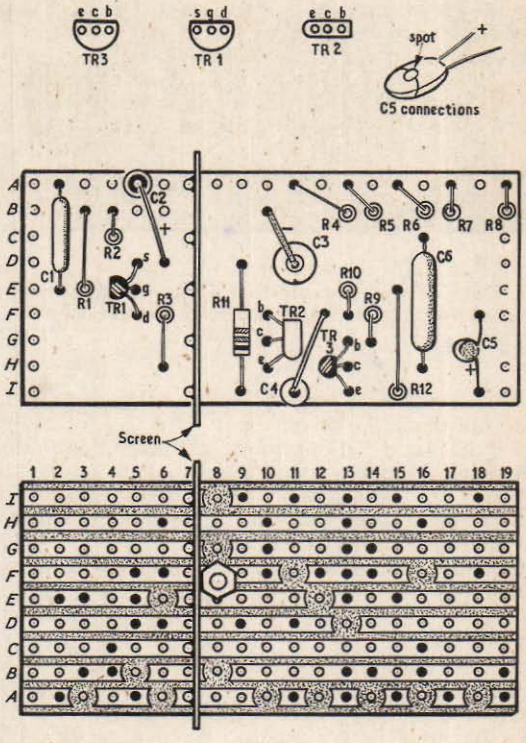


Fig. 2. Component assembly and wiring details.


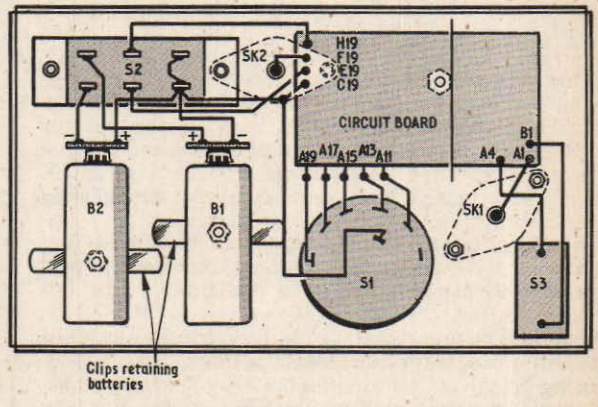


Fig. 3. Total component assembly within the aluminium box.

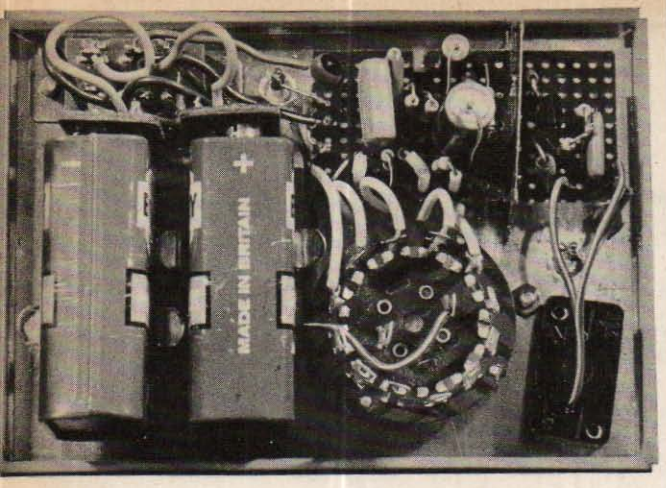

Rear view of the preamplifier front panel showing layout of components and position of circuit board

should not touch the board itself. It is then necessary to see if the board can be screwed into place by a 6 B.A. bolt passing through the appropriate hole in the lid into the pillar; check that the box will still fit inside the lid, and if necessary desolder and re-position the pillar. This pillar also earths the case.

Once the circuit board has been mounted the components may be wired up as in Fig. 3.

TESTING

When the wiring has been completed and checked the batteries may be inserted. If a milliammeter is available, it may be connected in series with B1. When the circuit is switched on it should read about 1mA (ensure that S3 is out when measuring this). The amplifier can be tested using a signal generator or other signal source and an oscilloscope, power amplifier or crystal earpiece.

USING THE AMPLIFIER

This preamplifier has many uses in the workshop. As an audio preamplifier when a power amplifier has insufficient sensitivity or an input impedance too low for the signal source, as an audio signal tracer (using a crystal earpiece or a small power amplifier), as an i.f. signal tracer (using a detector diode at the output) or as a general purpose oscilloscope pre-amplifier.

In normal use a screened input lead should be used to prevent feedback or hum pick-up, this is not always necessary when the amplifier is fed from a low impedance source.

It should be noted that a very low frequency damped oscillation occurs for several seconds after S3 is closed. Closing S3 gives the amplifier a very high input resistance due to the bootstrapping effect on R1; this may be several hundred megohms when a low gain is being used. However, since the 12 megohm input impedance obtained when S3 is out is usually quite sufficient, some constructors may prefer to omit this facility.

Due to the low current drain the batteries should give several months of operation. The use of silicon planar transistors should make this unit very reliable. ★



BOOK REVIEWS

HANDBOOK OF I.C. CIRCUIT PROJECTS

By Jim Ashe
Published by Tab Books
224 pages, 5½in × 8½in. Price $4·95 paperback, $7·95 hardbound

APART from the very obvious disadvantage over American sourcing and prices, this book forms a useful addition to the shelves where one is comparatively new to work with integrated circuits.

Indeed, the fast reducing prices of i.c.s makes some sort of volume of this type almost mandatory for the experimenter.

The current book deals with the subject from start to finish taking the reader through the basics of i.c.s and their handling and then gently introduces him to various projects. These range from audio equipment through various "novelty" items such as touch-plates to instrumentation and security devices.

Readers of all conversions are catered for from the scientist to the Ham and indeed the author has taken the precaution of supplying a good deal of additional data on specific components, the sources of these and of data and so on. It is unfortunate that much of the source data is not valid here but most readers will be able to find products in the columns of PRACTICAL ELECTRONICS.

R.D.R.

UNDERSTANDING ELECTRONIC CIRCUITS

By Ian R. Sinclair
Published by Fountain Press M.A.P. Book Division
205 pages, 8¾in × 5½in. Price £3·50

LIKE Ian Sinclair's earlier book "Understanding Electronic Components", this volume is directed to the reader with some basic understanding of electronics, certainly to the extent of the properties of electronic components and the elementary laws of electrical circuits.

The author has directed his attention to the enthusiast who wishes to extend his understanding of the subject as well as to the undergraduate who wishes a wider understanding of electronics in an overall sense.

It should perhaps be emphasised that this volume does not set out to tell the reader how to construct something so much as how many of the circuits he will meet in electronics actually operate.

R.D.R.

POINTS ARISING

PUSHBUTTON VARICAP STEREO TUNER

(May 1973)

Some constructors have experienced oscillation of the voltage regulator i.c. This may be cured by placing a 0·1μF capacitor in parallel with C13. Also some constructors have reported hum picked up by the tuner. This may be cured by increasing C1 from 0·1μF to 1·5μF or 2μF.

NEW DEVICES ...APPLICATIONS

A Schmitt Trigger With Variable Hysteresis

As materials are evolved so new devices appear on the market at prices the experimenter can afford. In addition, existing devices come under scrutiny and are adapted to more and more applications.

In this section we present a selection of both new devices and applications, with news of applications developed for existing devices.

Generally only basic circuit details will be given sufficient for the experimenter to create his own equipment.

THE Schmitt trigger is a two-state device which changes state each time a given input voltage is exceeded. It is one of the most widely used building blocks in electronics today, serving as a pulse shaper, voltage level monitor and voltage controlled switch.

All Schmitt triggers exhibit hysteresis, that is the input voltage at which they trigger is higher than the voltage below which they return to their initial state after being triggered. A typical hysteresis curve is shown in solid lines in Fig. 1 (b).

The application of currently available logic circuitry to form Schmitt triggers has been investigated and one useful solution has been developed by Jim Halligan of Motorola. Using CMOS gates he has created a trigger which exhibits variable hysteresis. That is, in the curve of Fig. 1 (b) the voltage at which the trigger returns to the untriggered state can be varied.

First of all, the CMOS gate as a trigger. Fig. 1 (a) shows a Motorola MC14023 triple, three input, NAND gate from the CMOS family.

The voltage measurement function of the trigger is performed by gate *A*, the point at which triggering occurs being determined by the threshold voltage of this gate.

The regenerative switching function in which the trigger returns from the triggered to the untriggered state is provided by gates *B* and *C* which are cross-connected to form a simple bistable.

The threshold depends on the number of gate inputs which are driven, for example with a power supply V_{DD} at 15 volts if two inputs of a three-input gate are held high the threshold of the third gate is about 5 volts. With all three inputs driven in parallel the threshold is 8·5 volts.

Thus in Fig. 1 (a) gate *A* has a threshold of 8·5 volts and *B* a threshold of 5 volts when the output of gate *C* is high.

In addition, with V_{in} at 0 volts the outputs of gates *A* and *B* will be high and, due to bistable action, output of *C* will be low.

Increasing the value of V_{in} will have no direct effect on gate *B* as all its inputs must go high if it is to change state. The truth table in Table 1 shows the various operations of the gates.

When V_{in} reaches 8·5 volts the output of gate *A* will go low as all its inputs are driven in parallel. Thus the input of gate *C* is 11 from gate *B* and 0 from gate *A*. So the output of gate *C* goes high.

As a result gate *B* is presented with a 1 (the V_{in} above 8·5 volts) and 11 from gate *C*. Thus its output goes low.

Hysteresis is created because the gate *B* now has two inputs high from gate *C* and one which is driven by V_{in}. The threshold becomes 5 volts.

As V_{in} falls below 8·5 volts gate *A* output goes high but from Table 1 it can be seen that there will be no change elsewhere following this.

But, as the value of V_{in} falls below 5 volts the outputs of gate *B* goes high and that of *C* falls. Thus the circuit resumes its quiescent untriggered state. The transfer characteristics are shown in Fig. 1 (b) and the output waveform at 1 (c).

VARIATION OF TRIGGER

If one of the inputs of gate *A* is connected to V_{DD} the upper threshold is reduced as shown in dashed in Fig. 1 (b) to 7·5 volts.

The circuit of Fig. 1 (d) uses an MC14011 quad two-input CMOS gate to give true variation of the hysteresis. The value of the potentiometer is not too critical and allows the hysteresis to be set anywhere between 0 and 50 per cent V_{DD} by adjustment of the upper level.

A small value of potentiometer will increase current consumption and a larger one will cause the sensitivity of adjustment to suffer.

Prices of the components are:—14011, £0·52, 14023, £0·52, one off from distributors.

Table 1: NAND Gate Truth Table

Input	Output
000	1
001	1
010	1
011	1
100	1
101	1
110	1
111	0

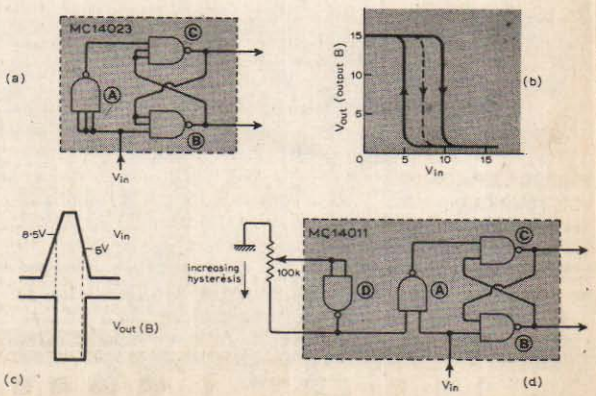


Fig. 1.

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD

COMPLETE TELEPHONES



EX G.P.O. NORMAL HOUSEHOLD TYPE

ONLY £1·05

POST & PACKING 45p EACH



TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

ONLY 27½p

POST & PACKING 16½p

TESTED AND GUARANTEED PAKS

B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV 1 amp. plastic	55p
B81	10	Reed Switches, 1" long ⅛" dia. Highspeed P.O. type	55p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	55p
H4	250	Mixed Resistors. Approx. quantity counted by weight	55p
H7	40	Wirewound Resistors. Mixed types and values	55p
H9	2	OCP71 Light Sensitive Photo Transistor	55p
H28	20	OC200/1/2/3 PNP Silicon uncoded TO-5 can	55p
H30	20	1 Watt Zener Diodes, Mixed Voltages 6·8–43V	55p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked	55p
H38	30	Short lead Transistors, NPN Silicon Planar types	55p
H39	10	Integrated circuits 6 gates BMC 962, 4 flip flops BMC 945	55p
H40	20	BFY 50/2, 2N696, 2N1613, NPN Silicon uncoded TO-5	55p
H41	2	BD131/BD132 Complementary Plastic Transistors	55p

UNMARKED UNTESTED PAKS

B1	50	Germanium Transistors PNP, AF and RF	55p
B66	150	Germanium Diodes Min. glass type	55p
B83	200	Trans. manufacturers' rejects all types NPN; PNP, Sil. and Germ.	55p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	55p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	55p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1 2N706A, BSY95A, etc.	55p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	55p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	55p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied	55p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	55p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed volts	55p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO–3 Can	55p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1·10 each



OVER

1,000,000

TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

600,000 Silicon planar plastic transistors. Unmarked, untested, factory clearance. A random sampling showed these to be of remarkably high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BCY70, etc.

Audio NPN, similar to ZTX300, 2N3708/9 BC107/8/9, BC168/9, etc.

Please state Audio NPN or Audio PNP when ordering.

ALL AT 500 for **£3·30**, 1,000 for **£5·50**, 10,000 for **£44.**

P & P 11p per 1,000

OUR VERY POPULAR 4p TRANSISTORS

TYPE "A" PNP Silicon Alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.
TYPE "G" NPN Silicon, similar ZTX300 range.
TYPE "H" PNP Silicon, similar ZTX500 range.

8 RELAYS FOR VARIOUS TYPES P & P 27½p **£1·10**

Our famous P1 Pak is still leading in value for money



Full of Short Lead Semiconductors and Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and a host of Diodes and Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.1. Only 55p. 11p P & P on this Pak.

A CROSS HATCH GENERATOR FOR £3·85 ! ! !

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This is a project in the September edition of Television.

This complete kit of parts costs £3·85, post paid.

A MUST for Colour T.V. Alignment.

STEREO DECODER £4·95

A ready built unit, ready for connection to the I.F. stages of your existing FM Radio or Tuner Unit. A tell tale light can be connected to show the presence of a Stereo transmission and correct operation of the Unit.

The Unit is in the form of a small printed circuit, and no further alignment is necessary, as all preset adjustments have already been carried out at the factory.

It is recommended that a L.E.D. is used as the indicating light and a suitable device is available from us at 36½p.

Supplied with necessary instructions and written guarantee.

FREE CATALOGUE FOR

TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS



100,000 Plastic Power Transistors

in stock, more on way!

NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1

	VCE Min. 15	HFE Min. 15	
	1–12	13–25	26–50
40 watt	22p	20p	18p
90 watt	26½p	24½p	22p

Range 2

	VCE Min. 40	HFE Min. 40	
	1–12	13–25	26–50
40 watt	33p	31p	29p
90 watt	38½p	36½p	33p

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

INTEGRATED CIRCUITS. We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available. This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights, etc. Pocket Size, 15p, Wall Chart, 18p.

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 16½p each } Now new low
16 pin type at 18p each } profile type.

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:

B.P.I. Transistor Equivalents and Substitutes: **40p**
This includes many thousands of British, U.S.A., European and C.V. equivalents.

The Iliffe Radio Valve & Transistor Data Book 9th Edition: P & P 23½p. **75p**
Characteristics of 3,000 valves and tubes. 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.

Send for lists of publications.

N.B.—Books are void of V.A.T.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME.....

ADDRESS .....

.....


ALL PRICES INCLUDE 10% V.A.T.

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 11p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE.

BI-PRE-PAK LTD


Co. Regn No. 820919

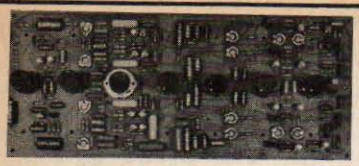DEPT. A. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344



PHONOSONICS P. C. BOARDS

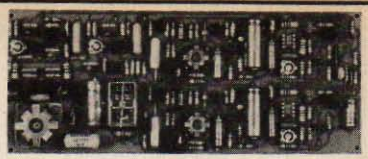All PCBs Fibreglass, Drilled, Roller-Tinned. Layout and Circuit Diagrams Free with each PCB. Unless stated "as published", PCBs are designed by Phonosonics. Pots are rotary unless stated as slider.



AURORA
Multichannel Sound Controlled Light (PE Apr./Aug. 71). S/c's (excl. SCRs), Rs, Cs, Pots, Cores—8 ch. **£17·75**; 4 ch. **£10·15**. Reg. PSU **£3·65**. PCB—4 ch. control (4¼in × 10⅜in) Mk. 2—also holds rotary or slider pots **£2·35**. PCB (4¼in × 5in) Mk. 2—for PSU, Sync Gen. 8 cores, 8 SCRs, **£1·35**. SCRs—1A, **50p**, 3A, **55p**.

A.F. SIGNAL GENERATOR
(PE Nov. 72). S/c's, Rs, Cs, Pots, Sw's, PCB (2¼in × 4in) also holds Sw's, **£3·15**.

AUDIO MIXER
(PE Jan. 72). Rs, Cs, Pots, PCB (1¼in × 2in) (i.c. excl.), **£1·55**.

DOOR BELL YODELLER
(PE Apr. 71). S/c's, Rs, Cs, Pots, PCB (3in × 3¼in), **£5·10**. T/fmr **£1·30**. L/spkr **£1·30**.

BIOLOGICAL AMPLIFIER
(PE Jan./Feb. 73). P/A Set—S/c's, i.c.'s, Rs, Cs, Pots, PCB (1¼in × 3⅜in), **£3·70**. O/P Stages (S/c's, Rs, Cs, Pots and Sw's as reqd.). Alphaphone **60p**, Cardiophone **75p**, Freq. Meter **£1·90**, Vis-Feedback **60p**. Audio Amp PC7 avail. to order **£4·75**.

ELECTRONIC PIANO
(PE Sep. 72/Jan. 73)—Details in lists

GEMINI STEREO AMPLIFIER
(PE Nov. 70/Mar. 71) Stereo Sets and PCBs. Pre-amp—S/c's **£1·85**. Rs, Cs, Pots, Maka-Sw's—with ¼W MO Rs, **£11·60**—with ¼W CF Rs, **£9·35**—with ½W CF Rs, **£8·90**. PCB (3¼in × 10⅜in) for sets with MO and ¼W Rs, also holds rotary or slider pots and Maka-Sw's, **£2·10**. Main Amp—Rs, Cs, Pots, **£5·40**. PCB (3¼in × 5in), **£1·40**. PSU—Rs, Cs, Pot, **£3·70**. PCB (2in × 4in), **75p**.

LOGICAL RADIO CONTROL
(PE Apr./Jun. 72)—Details in lists

GEMINI STEREO TUNER
(PE Apr./Jun. 72). Rs, Cs, Pot, **£3·80**. PCB as publ., **£1·80**.

MICROPHONE MIXER
(PE Apr. 69). S/c's, Rs, Cs, Pots, **£2·90**. PCB (3¾in × 4¼in) also holds 6 rotary or 4 slider pots, **£1·20**.

MODEL SERVO CONTROL
(PE Feb./Mar. 72)—Details in lists

8 WATT AMPLIFIER
(PW Nov./Dec. 72). Pre-amp—S/c's, Rs, Cs, Pots, Sw—Mono, **£2·50**; Stereo, **£5·20**. PCB (3¼in × 7¼in) (Stereo) also holds rotary or slider pots and Sw, **£1·50**. Main Amp—S/c's, Rs, Cs, Pot—Mono, **£3·90**; Stereo, **£7·70**. PCB (2¼in × 3in) Mono), **60p**.

POST AND PACKING
U.K. 10p per order. EXPORT at cost—please allow for this when ordering and also state whether air or surface postage required.

HI-FI TAPE LINK
(PE Mar./Apr. 73). S/c's, i.c.'s, Rs, Cs, Relay and pc-base, Pot Cores and pc-bases, Sw's, Pots, Panel Lamp—Mono, **£11·80**; Stereo, **£18·70**. PSU, **£2·50**. PCB—Main Assy. (3¼in × 9in) (Stereo) also holds relay and cores, **£1·85**. PCB—Sub-Assy. (2¼in × 6¼in) (Stereo) holds Sw-assoc. Rs, Cs, Presets and mounts on Sw's, **80p**.

REVERBERATION UNIT
(PW Nov./Dec. 72). S/c's, Rs, Cs, Slider Pots, T/fmr, **£6·80**. PCB (2in × 11¼in) also holds sliders, **£1·20**. 9in Spring Unit avail. to order, **£3·75**.

VIBRASONIC GUITAR PRE-AMP
(PW Sept. 70). Incl. Mic P/A, 2-Guitar P/A, Trem and Tone Controls, Master Volume. S/c's, Rs, Cs, LDR, Rotary Pots, Lamp, Coupling T/fmr, **£7·75**. PSU, **£2·80**. PCB (3¼in × 10⅜in) Mk. 2, also holds 7 rotary or slider pots, **£2·30**.

ULTRASONIC TRANSMITTER-RECEIVER
(PE May 72). S/c's, Rs, Cs, Pot, Relay, Dual PCB (2in × 5¼in), **£3·90**. T/ducers avail. to order, **£7·30** per pair.

ALSO
PCBs as published (while stocks last) for:
DIGICAL PSU (PE Aug. 72), **60p**
OSCILLOSCOPE P/A (PE Aug. 72), **40p**
SCORPIO (PE Nov./Dec. 71), **70p**
TRIFFID (PE Feb. 73), **60p**

AND
DIGITRONIC (PW Mar. 73). Read-out PCB (1¼in × 3¼in), **60p**.

V.A.T.
U.K. Orders only—add 10% to total cost of order.

TAPE NOISE LIMITER
(PE Feb. 72). S/c's, Rs, Cs, Pot, PCB (1¼in × 3in), **£2·20**. Reg. PSU and PCB (1¼in × 2¼in), **£3·20**.

VERSATILE LIGHT EFFECTS UNIT
Single Channel Sound Controlled Light with built-in variable strobe. (PE June 72). S/c's, Rs, Cs, Pots, T/fmrs, Keyswitch, **£8·85**. PCB (3¼in × 7¼in) Mk. 2, also holds pots, Sw, T/T7 T/fmr, **£1·50**. SCRs—1A, **50p**, 3A, **55p**.

PHOTOPRINT PROCESS CONTROL
(PE Jan./Feb. 72). Finds exposures, controls timing, stabs. mains voltage. S/c's, SCR, LDR, Rs, Cs, Pots, Relay, Keyswitch, T/fmr, **£7·60**. PCB (3¼in × 5¼in) also holds pots, Sw, relay, **£1·20**.

SOUND SYNTHESISER (PE Current Series)
Details of PCBs and Components in list. Free mailing list service available for further information about PCBs and Sets for this project.

LIST
S.A.E. for free list and with all enquiries please.

PHONOSONICS, DEPT. PE7, 25 KENTISH ROAD, BELVEDERE, KENT DA17 5BW **MAIL ORDER ONLY**



Ever had Component Problems?

1. Problems of choosing your components?
2. Problems of getting them quickly?
3. Problems of locating a supplier?



HOME RADIO (COMPONENTS) **LTD**
have created a catalogue and an organisation that between them solve your problems simply & economically

PUT US TO THE TEST

FIRST YOU'LL NEED THE CATALOGUE.
SEND COUPON with 77p CHEQUE or P.O.

The price of 77p applies only to catalogues purchased by customers in the UK and to BFPO addresses.

Please write your Name and Address in block capitals

Name _____

Address _____

_____

_____

_____

HOME RADIO (Components) LTD. Regd. No. 912966 London
Dept. PE, 234-240 London Road, Mitcham CR4 3HD

INGENUITY UNLIMITED

A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.
This is YOUR page and any idea published will be awarded payment according to its merits.

TAPE MOTOR CONTROLLER

THE mechanical governor provided on a recently acquired portable tape recorder motor posed problems of electrical noise and mechanical wear. Thus it was decided to replace it with an electronic system to control motor speed both within a given speed setting as did the original governor and from speed to speed as is often achieved using different sized pulleys.

The circuit of the system is shown in Fig. 1 where current supply to the motor is controlled by TR3, itself controlled by the base voltage of TR1. A basic d.c. bias is applied to the base of TR1 from the Zener circuit and chain, R1, VR1/VR2. This sets the main motor speed.

Regulation of the speed about the selected value is supplied by detecting motor shaft speed using a pick-up coil and magnet assembly as shown in Fig. 2. The coil provides an a.c. voltage to D2 which thus gives a d.c. bias at the base of TR1. As the voltage fed back depends on the rotational speed of the motor speed control over a wide range is possible.

Under normal operating conditions the voltage from emitter follower TR1 appearing across R2 is about 2V. An increase in speed raises this value making D3 conduct through R3 and TR2 conducts heavily. This cuts the bias on TR3 to slow the motor.

Similarly, a decrease in motor speed reverses the process.

Supply voltages from 8 to 15V are acceptable and in addition to exhibiting good quick-start properties, the equipment provides almost twice motor voltage on full stall condition.

Colin Anderson,
Wanganui, New Zealand

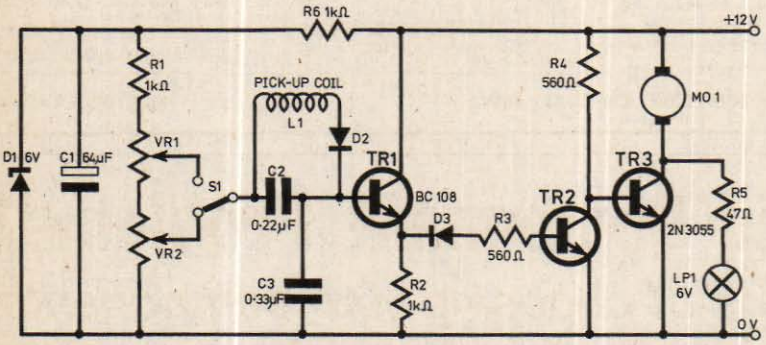


Fig. 1. Circuit diagram for the tape motor controller

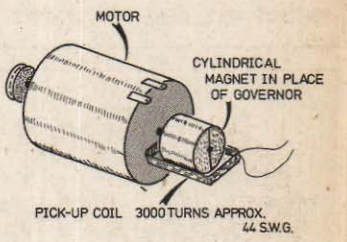


Fig. 2. Pick-up coil and magnet arrangement

I.C. LAMP FLASHER

THE DTL integrated circuit type 9944 is a cheap dual buffer amplifier in one dual-in-line package and can be used to make a reliable, economical lamp flasher.

In the circuit, diagram Fig 1, the two amplifiers are cross-connected with capacitors C1 and C2, the values of which determine the frequency. The circuit becomes a multivibrator with the lamp LP1 in one collector.

Numbers in the circuit are the i.c. pin numbers.

If C1 and C2 are 100μF (over 8V rating), a flashing rate of 30 per minute is obtained. Any 6V low current bulb may be used or the circuit could be used to operate a relay.

The Mullard equivalent i.c. is the DTL FCH 121, but the pin numbering is different. On this device, pins 1 and 8 are 6 and 8. Cross-connect pins 8 with 13 and pins 1 with 6, using the capacitors C1 and C2. Also pin 7 is +6V and pin 14 is ground (neg).

A. M. May,
Weybridge.

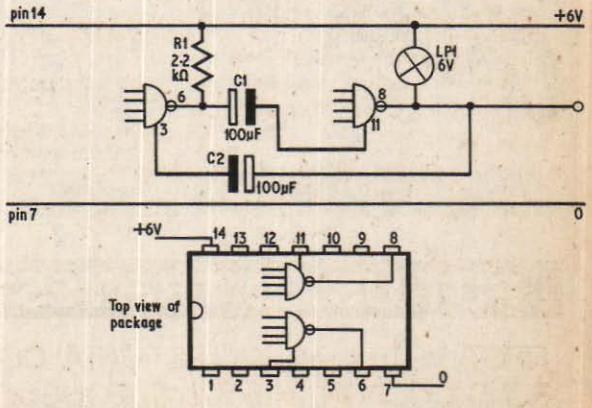


Fig. 1. Circuit diagram and i.c. connections for the simple flasher

WINDSCREEN WIPER CONTROL



THIS device, which can only be used with those windscreen wiper motors having a self-parking system since the system serves to turn-off the thyristor, can provide sweep delays of from 2 to 35 seconds.

The circuit is very simple, see Fig. 1, and uses few components. The original was constructed in a 35mm film can with switch S1 mounted on the variable resistor VR1. The control transistor is a UT46 or equivalent (2N2646) and the thyristor uses the can as a heatsink.

If the vehicle is negative earth with the windscreen wiper motor switched in the earth lead then the can may be earthed and only two leads are needed. One for positive supply and one for the positive supply to the wiper motor. As the thyristor is in parallel with the wiper motor polarity must be observed with care or triggering will not occur.

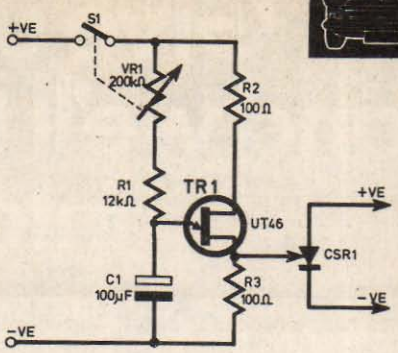


Fig. 1. Windscreen wiper delay circuit

The thyristor should be a high p.i.v. version, in the original a 7A 50V p.i.v. type was used.

C. M. Calver,
Melton Mowbray

ENGINE TEMPERATURE CONTROLLER

The circuit of Fig. 1 includes a stabiliser section, TR1, R1, R3, C1 and D1. This supplies power for the remainder which is basically a Wheatstone bridge circuit in which the thermistor TH1 forms one arm.

Balance of the bridge determines when the transistor TR2 cuts off. The vehicle fan is switched by RLA1.

For operation the normal "Temperature High" warning indicator is replaced with a thermistor. In practice the circuit is fail safe in that if TR2 goes open circuit for any reason then the fan is automatically switched on.

When the engine is cool the thermistor has a high resistance which puts TR2 in the ON condition. As temperature increases and resistance decreases the bias voltage across the transistor decreases until TR1 cuts OFF. The level of cut-off is determined by VR1. The value of R3 is determined by measuring the bridge circuit resistance and making R3 equal it. R1 may need adjusting if R3 is high.

Manual over-ride and a form of test facility may be provided by replacing the link by a switch.

If required a temperature indicator can be added as shown in Fig. 2. The voltmeter must have a high resistance with respect to R2. The 6 volt Zener is used to hold the zero down by 6 volts. In practice the "normal" temperature will probably show as about 1 volt.

R. K. Todd,
Albrighton

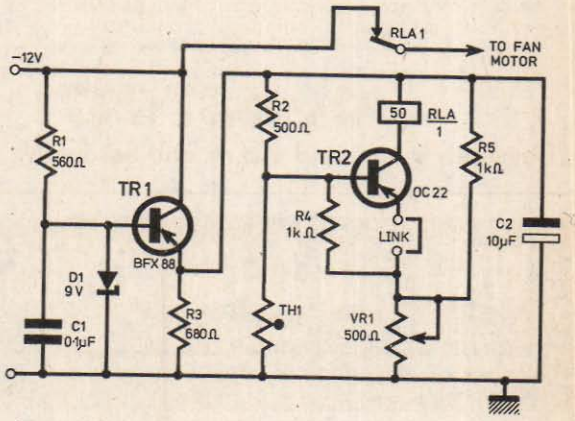


Fig. 1. Circuit for the temperature controller

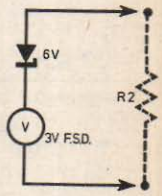


Fig. 2. Adding a temperature gauge


BRAKE LIGHT MONITOR

INDICATION of the state of the brake lights on a vehicle may be obtained without inserting extra lamp bulbs in the brake light circuit by using a reed switch actuated by a specially wound double coil to actuate a panel indicator lamp.

The circuit shown in Fig. 1 indicates the simplicity of the idea. Two coils serve to actuate the one reed but they are counter-wound so that as long as the pair of brake lights operate the reed remains quiescent. If one or other bulb fails then the reed is operated to give an indication at the dash board.

S. W. F. Morum
Chislehurst

Fig. 1. Brake light monitor

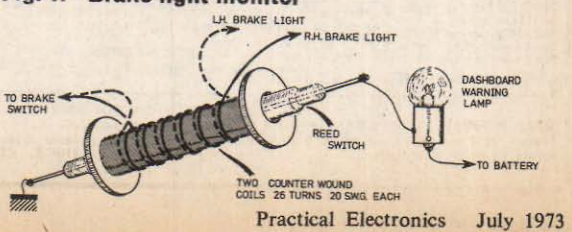

Give us six months, and we'll turn your hobby into a career.

You have a hobby for a very good reason. It gives you a lot of pleasure.

So if you can find a job that involves your hobby, chances are you'll enjoy your work more, and you'll do better work.

Now CDI can help you find such a job. A job where you'll be responsible for the maintenance of a computer installation. A job that pays well too. If you're interested in mechanics or electronics (without necessarily being a mathematical genius), have a clear, logical mind and a will to work, then we can train you to be a Computer Engineer inside six months.

So give us a call. CDI. We're the Training Division of one of the world's largest computer manufacturers. And we have the experience to know if you can make it. A ten minute talk with us, and you could be on the way to spending the rest of your life with your hobby.

Ring

01-637 2171

between 9 a.m. and 9 p.m. and ask for Mr PLUMMER

It's quicker and easier to phone, but if you prefer, send this coupon to: Control Data Institute, Wells House, 77 Wells Street, London, W.1.

Please give me further information.

Name

Address

Age Phone PE7

CONTROL DATA INSTITUTE — CONTROL DATA LIMITED

The Training Division of one of the world's largest Computer manufacturers.

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND

C.W.O. Please. P. & P. please add 10p to orders under £2

MAIL ORDER. CALLERS SATURDAYS ONLY

TRANSISTORS

AC125	12p	AFI14	12p	OC44	10p	BC149	12p	2N2926G	10p
AC126	12p	AFI15	12p	OC45	10p	BD131	49p	2N2218A	13p
AC127	12p	AFI16	12p	OC70	10p	BD132	49p	2N2220	10p
AC128	12p	AFI17	12p	OC71	10p	BF194	15p	2N2221	10p
AC187	12p	OC26	40p	OC72	10p	BF195	15p	2N2483	10p
AC188	12p	OC28	40p	BC107	8p	BFY50	22p	2N2484	10p
AD161	30p	OC35	40p	BC108	8p	BFY51	22p	2N3014	10p
AD162	30p	OC42	10p	BC109	8p	2N2926R	9p	2N3055	55p
				BC147	12p	2N2926O	9p		
				BC148	12p	2N2926V	9p		

DIODES AND RECTIFIERS

OA85	7p	IN4004	7p
OA91	5p	IN4007	8p
OA200	8p	IN914	5p
OA202	8p	IN4148	5p
IN4001	6p	BZY10	20p

BYZ13 16p | WO1 Bridge Rect. 1A 30p

ZENER DIODE. BYZ 88, 400mW Range, 3·3V–30V. Price 12p each.

LINEAR IC's. DIL PACKAGING. 709C 30p, 741C 32p, 723C 80p. **DIL SOCKETS:** 8 pin 23p; 14 and 16 pin 15p.

VEROBOARD

	0·1	0·15
2½ × 3¾in	20p	18p
2½ × 5in	24p	22p
3¾ × 3¾in	24p	22p
3¾ × 5in	27p	30p
2½ × 17in	75p	60p
3¾ × 17in	97p	84p
5 × 17in	128p	—
2½ × 17in (plain)		40p
3¾ × 17in (plain)		60p
5 × 17in (plain)		80p
Pkt. 50 pins		20p
Spot face cutter		42p
Pin insertion tool		52p

JACK PLUGS AND SOCKETS

Standard Screened, 12p | Stereo Screened, 30p | Standard Socket, 12p | Stereo Screened, 15p | 2·5mm Screened, 8p | 3·5mm Screened, 10p | 2·5mm Socket, 7p | 3·5mm Socket, 7p

DIN PLUGS & SOCKETS Pin: 2, 3, 4, 5 (180° or 240°) Plugs, 12p. Socket 8p.

COMPACT CASSETTES C60 40p; C90 55p; C120 75p.

PHONO PLUGS AND SOCKETS: PLUGS assorted colours 5p. Socket: Single 5p, Double 7p, Triple 10p

SWITCHES Toggle SPST 18p, DPDT 22p. **SLIDE SWITCH** 1A 10p

D.C. POWER SUPPLY: Current 500mA. O/P Voltage: 3, 4·5, 6, 7·5, 9, 12. Price: £3·60 P. & P. 15p.

STEREO HEADPHONES. HOSIDEN DH-02V-S. 8 ohm: Individual vol. control. Soft ear padding. Light wt. PRICE: £2·85. P & P. 15p.

RESISTORS

High stability low noise carbon film. Miniature wire wound.

Power Watts	Tol.	Range	Values Available	PRICE 1–9	10–99	100+
‡	5%	2·2–2·2M	E12	1p	0·8p	0·7p
½	5%	2·2–4·7M	E12	1p	0·8p	0·7p
1	5%	2·2–10M	E12	2p	1·6p	1·4p
4	10%	1–10 ohm	E12	6p	5p	—

Do not mix ohmic values to obtain quantity prices. Ignore fraction

POLYESTER CAPACITORS. Axial lead type:

400V: 0·001μF, 0·0015μF, 0·0022μF, 0·0033μF, 0·0047μF, 0·0068μF, 2½p; 0·01μF, 0·015μF, 0·022μF, 0·047μF, 3p; 0·068μF, 0·1μF, 0·15μF, 4p; 0·22μF, 7p; 0·33μF, 10p; 0·47μF, 13p.

160V: 0·1μF, 0·15μF, 4p; 0·22μF, 5p; 0·33, 6p; 0·47μF, 7p; 0·68μF, 10p; 1μF, 13p.

Radial lead P.C. type:

250V: 0·01μF, 0·015μF, 0·022μF, 3p; 0·033μF, 0·047μF, 0·068μF, 3½p; 0·1μF, 4p; 0·15μF, 4p; 0·22μF, 0·33μF, 5p; 0·47μF, 7p; 0·68μF, 10p; 1·0μF, 11p.

ELECTROLYTIC CAPACITORS. Miniature axial lead type.

63V: 1μF, 1·5μF, 2·2μF, 3·3μF, 4·7μF, 6·8μF, 10μF, 15μF, 22μF, 47μF, 68μF, 6p each. 40V: 100μF, 6p; 150μF 25V, 6p; 25V: 220μF, 11p; 470μF, 13p; 680μF, 20p; 1,000μF, 25p.

CERAMIC CAPACITORS: 50V d.c. Plaquette body 25mm leads. Range: 22pF–10,000pF. Price 2p each.

POTENTIOMETERS: Carbon Track 0·25W, Log and linear values

5k Ω — 2M Ω Single Gang	12p
5k Ω — 2M Ω s/gang W/switch	24p
5k Ω — 2M Ω Dual gang	37p
1K linear single gang	12p
Knobs Pointer type	8p
Small Aluminium	10p
Black chrome rim	15p

SLIDER POTENTIOMETERS 0·25W log and linear values

10k Ω — 100k Ω Single gang	35p
10k Ω — 100k Ω Dual gang	50p
Knobs	10p

PRESET POTENTIOMETERS 0·25W 1k Ω — 1M, Hor. and Vert. 5p; 0·1W Vert. only 3p

WATFORD ELECTRONICS. 35 CARDIFF RD., WATFORD Herts. England. Enclose 10p stamps for our comprehensive catalogue

Name.....

Address.....

.....

ZN414 £1.25 POST FREE

The I.C. Radio in a TO18 can. Supplied complete with data sheet No. 10 which contains specification, circuit and details and prices of components such as ferrite rods, compression trimmers etc.

I.C. Sockets

Dual-in-line or Zig-Zag (Quil). 14 and 16 pin
Our Price 1p per pin

Slider Pots

Single	Dual	log or lin
10K	10 + 10K	
25K	25 + 25K	
50K	50 + 50K	
100K	100 + 100K	Knobs
30p	50p	10p.

NEW LISTS
LOUDSPEAKERS — No. 4
COILS AND INDUCTORS — No. 5
TRANSFORMERS — No. 6
(postage 5p)

Diodes & Rectifiers

AA119	9p	BA156	15p	BY176	£1·50
AA120	9p	BA243	56p	BY182	£1·50
AA129	9p	OA47	10p	BY250	23p
BA102	25p	OA79	9p	IN4001	6p
BA115	17p	OA90	7p	IN4002	7p
BA130	10p	OA91	7p	IN4003	8p
BA145	20p	OA200	10p	IN4004	8p
BA148	20p	BY100	15p	IN4005	10p
BA154	13p	BY126	15p	IN4006	12p
BA155	14p	BY127	15p	IN4007	15p

VDR's & Thermistors

A15B	75p	GL23	£1·00	VA1005	15p
CZ1	15p	R53	£1·32	VA1026	13p
CZ4	13p	R54	£1·46	VA1033	13p
CZ13A	13p			VA1040	10p
E298 ED/A258	10p			VA1053	10p
E298 ZZ/06	10p			VA1055S	10p
GL16	£1			VA1034	10p

Resistors

¼ watt 5% Carbon Film – low noise Hi-Stabs
All E24 values **1p** each plus p. & p. 7p for up to 50 Resistors and a further 2p for each additional 50. Deduct **33⅓%** for 100 of one type or **25%** for mixed orders over £1 in value.

1 W	10% Carbon Composition	3p each
2 W	10% Carbon Composition	6p each
2½ W	5% Wire wound	9p each
5 W	Wire wound	9p each
10 W	Wire wound	10p each

plus p. & p. 7p for up to 25 resistors plus 1p for each additional 25.



SGS
EA1000
3 Watt Audio Amplifier
Our Price Inc. handbook £2·49.



FM TUNER chassis fully transistorised 9 volt operation. OUR PRICE £6·25
Matching stereo decoder £4·97
Ask for model list No. 11.



10+ less 15%
25+ less 25%
100+ less 33⅓%
5 Watt Audio Amplifier
Our Price £3·99
Less quantity discount.


Potentiometers



5KΩ	50KΩ	500KΩ
10KΩ	100KΩ	1MΩ
25KΩ	250KΩ	2MΩ

log or lin less switch (& 1KΩ lin) — 12p
log or lin with switch — 24p
dual less switch — 40p
dual with switch 10K, 100K & 1M log only — 52p
10K log + 10K antilog less switch — 40p

Eliminators

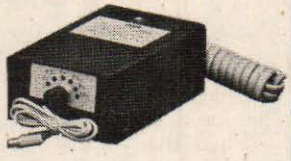

6 volt @ 50mA	£1.50
9 volt @ 50mA	£1.50
6 + 6 volt, 50mA	£2.50
9 + 9 volt, 50mA	£2.50
7½ volt for cassette recorders	£2.00
6, 7½ or 9 volt	£3.00
3, 4½, 6, 7½, 9, 12 @ 500mA (illus.)	£3.99

Car Battery Converter fully stabilised to provide 6, 7½ or 9 volts — £4.99
(p. & p. 15p on all types)

Presets



Vertical or Horizontal

0·1 watt 5p	0·25 watt 7p			
100	1K Ω	10K Ω	100K Ω	1M Ω
250	2·5K Ω	25K Ω	250K Ω	2·5M Ω
500	5K Ω	50K Ω	500K Ω	5M Ω

Capacitors

disc ceramic — 5p
·01µF 18v, ·022µF 18v, ·047µF 12v

low voltage — 5p
0·1µF 30v, 0·22µF 6v, 0·47µF 3v

ceramic plate 30V

1000pf	10p
2200pf	10p
4700pf	10p
10,000pf	10p

Ceramic – plate (all 5p. each)

1·8pf	8·2pf	33pf	120pf
2·2pf	10pf	39pf	150pf
3·3pf	12pf	47pf	180pf
3·9pf	15pf	56pf	220pf
4·7pf	18pf	68pf	270pf
5·6pf	22pf	82pf	330pf
6·8pf	27pf	100pf	

63V (C333)

mylar film 100V

1000pf	2p	·01µF	3p	·068µF	4p
2000pf	2p	·02µF	3p	·1µF	4p
5000pf	2p	·04µF	3p	·2µF	5p
		·05µF	3p		

polystyrene 160V
10pf to 10,000pf in multiples of 10, 15, 22, 33, 47 & 68. **3p each**

metallised polyester 250V (C280)

·01µF	3p	·068µF	3½p	·47µF	8p
·015µF	3p	·1µF	4p	·68µF	11p
·022µF	3p	·15µF	4p	1µF	13p
·033µF	3p	·22µF	5p	1·5µF	20p
·047µF	3p	·33µF	6½p	2·2µF	24p

metallised polyester 400V (C281)

·01µF	4½p	·047µF	6p	·22µF	10p
·015µF	4½p	·068µF	6p	·33µF	14p
·022µF	4½p	·1µF	7p	·47µF	15p
·033µF	5½p	·15µF	8p		

silvered mica 1% (>50pf) 500V

2·2pf—820pf	7p	4·7nF—5600pf	19p
1nF—2·2nf	9p	6800pf—·01µF	29p
2·7nF—3·6nF	16p		

mixed dielectric 600V

·01µF	7p	·047µF	7p	·22µF	16p
·022µF	7p	·068µF	8p	·47µF	24p
·033µF	7p	·1µF	8p	1µF	33p

mixed dielectric 1000V

1000pf	6p	6800pf	9p	·1µF	12p
2200pf	6p	·01µF	9p	·22µF	22p
3300pf	6p	·022µF	9p	·47µF	30p
4700pf	6p	·047µF	12p		

Ceramic 12KV.d.c. — 10pf 9p, 15pf 9p, 22pf 9p, 68pf 9p, 82pf 9p, 100pf 9p, 120pf 9p, 140pf 9p, 150pf 9p, 180pf 9p

8KV.d.c. — 200pf 9p, 220pf 9p, 250pf 9p, 270pf 9p, 300pf 9p

750V DISC — 470pf 5p, 1000pf 5p, 5000pf 5p, 10,000pf 5p

HI-K 750V. — 1000pf 5p, 1500pf 5p, 2000pf 5p, 3000pf 5p, 5000pf 5p, 10,000pf 5p


feed-through — 1000pf 5p

CHROMASONIC electronics

Please add 10% V.A.T. to your total order

MAIL ORDERS: Where no p. & p. charge is shown, a minimum of 7p applies. p. & p. on overseas orders is charged at cost.
ADDRESS TO: **M. O. Dept.**
56, Fortis Green Road, London, N10 3HN.
Telephone 01-883 3705

Heat Sinks

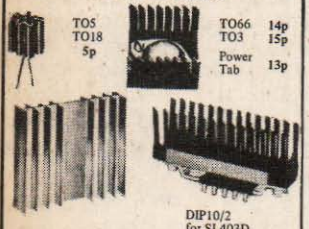

TO5 TO18 5p
TO66 TO3 14p 15p
Power Tab 13p
DIP10/2 for SL403D
10D 50p 15p

Veroboard

	Copperclad 0.1"	Copperclad 0.15"	Plain 0.15"
2½" x 1"	6p	6p	–
2½" x 3⅜"	20p	16p (9)	10p
2½" x 5"	24p	21p (7)	12p
3⅜" x 3⅜"	24p	21p (8)	–
3⅜" x 5"	27p	27p (10)	17p
17" x 2½"	67p	50p	37p
17" x 3⅜"	90p	70p	52p
17" x 5"	–	–	75p

Spot-face Cutter 36p
Pin Insertion Tool 47p
Terminal Pins 18p per pack of 36

NEW LISTS
BOXES, CHASSIS, etc. — No. 7
TRANSISTORS, I.C.'s, etc. — (soon)
(postage 5p)


Aluminium Boxes

Including baseplate and screws

No.	L.	W.	D.	Price	p. & p.
(7)	2¾"	x 5¼"	x 1½"	35p	8p
(8)	4"	x 4"	x 1½"	35p	8p
(9)	4"	x 2¾"	x 1½"	35p	8p
(10)	4"	x 5¼"	x 1½"	40p	8p
11	4"	x 2½"	x 2"	35p	8p
12	3"	x 2"	x 1"	32p	9p
13	6"	x 4"	x 2"	50p	10p
14	7"	x 5"	x 2½"	58p	12p
15	8"	x 6"	x 3"	75p	18p
16	10"	x 7"	x 3"	85p	20p

Transistors & Integrated Circuits

AC107	25p	BC147	10p	BF196	15p	OC81	19p	2N1304	22p	2N5172	15p
AC126	17p	BC148	10p	BF197	15p	OC140	20p	2N1711	25p	BZY88 ZENERS SERIES	10p ea.
AC127	15p	BC149	10p	BF272	53p	OC170	23p	2N1893	30p		
AC128	15p	BC157	12p	BFY50	24p	OC171	30p	2N2926	all 10p	LO05TI	£1.50
AC176	15p	BC158	10p	BFY51	21p	ZTX107	15p	2N3053	23p	LO36TI	£1.50
AC187	25p	BC159	12p	BRY39	36p	ZTX108	12p	2N3054	50p	LO37TI	£1.50
AC187K	25p	BC169	15p	BSX21	26p	ZTX109	15p	2N3055	49p	MC1303L	£1.75
AC188	25p	BC268	15p	BSY95A	14p	ZTX300	12p	2N3702	12p	MC1330	80p
AC188K	25p	BD115	67p	BU105/02	£1.75	ZTX301	15p	2N3703	12p	MC1350	75p
ACY20	20p	BD131	70p	MJE340	67p	ZTX302	20p	2N3704	10p	MC1351	£1.00
AD140	40p	BD132	70p	MPF192	40p	ZTX303	20p	2N3705	10p	MC1352	£1.00
AD149	40p	BD131/2M.P.		MPF103	37p	ZTX304	25p	2N3706	10p	MFC4000B	49p
AD161 AD162	60p		149p	MPF104	37p	ZTX341	20p	2N3707	15p	MFC4010A	55p
		BF160	21p	MPF105	40p	ZTX500	15p	2N3708	12p	LM380	£1.45
AF114	18p	BF167	20p	MPF106	45p	ZTX501	15p	2N3709	12p	SL403D	£1.50
AF115	18p	BF173	20p	OC28	40p	ZTX502	20p	2N3710	12p	TAD100	£1.50
AF116	18p	BF180	25p	OC35	40p	ZTX503	17p	2N3711	12p	FILTER LP1175	£1.50
AF117	18p	BF181	30p	OC44	15p	ZTX504	50p	2N3819	35p		
AF139	28p	BF184	25p	OC45	15p	ZTX531	25p	2N3903	15p	µA709C	34p
BC107	10p	BF185	25p	OC71	11p	2N697	18p	2N3904	17p	µA710	45p
BC108	10p	BF194	15p	OC72	17p	2N706	12p	2N3905	21p	µA723C	95p
BC109	10p	BF195	15p	OC76	15p	2N708	15p	2N3906	12p	µA741C	47p

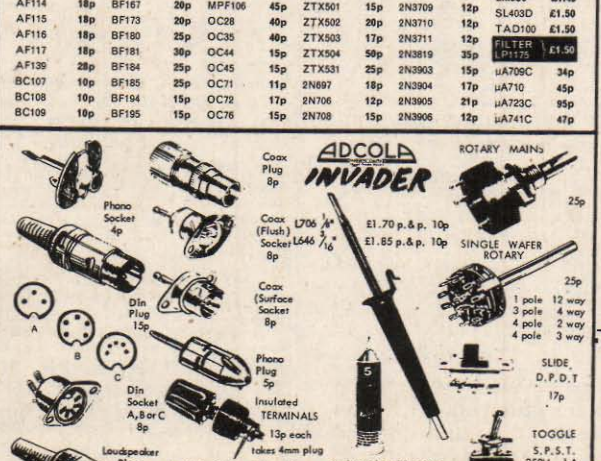

Mullard & Siemens Electrolytics

CAP µF	VOLTAGE 4	6.3	10	16	25	40	63
1	—	—	—	—	—	—	6p
1·5	—	—	—	—	—	—	6p
2·2	—	—	—	—	—	—	6p
3·3	—	—	—	—	—	—	6p
4·7	—	—	—	—	—	—	6p
6·8	—	—	—	—	—	8p	6p
10	—	—	—	—	8p	—	6p
15	—	—	—	8p	—	6p	6p
22	—	—	6p	—	6p	—	6p
33	—	6p	—	8p	—	6p	—
47	6p	—	8p	—	6p	6p	—
68	—	8p	—	6p	—	—	10p
100	6p	—	6p	—	6p	8p	12p
150	—	8p	—	6p	6p	10p	12p
220	8p	—	6p	6p	10p	12p	18p
330	8p	—	8p	10p	—	—	21p
470	—	8p	10p	—	12p	18p	40p
680	—	10p	—	12p	18p	21p	—
1000	10p	—	12p	18p	21p	40p	60p
1500	—	12p	18p	21p	—	—	—
2200	—	18p	21p	40p	45p	55p	93p
3300	—	21p	—	—	—	—	—
4700	21p	—	—	60p	75p	93p	—

CAP µF	VOLTAGE 16	25	40	64
500			33p	40p
1250			50p	—
1600			—	75p
2000		40p	50p	—
2500		—	75p	93p
3200		50p	—	—
4000		75p	93p	—
6400		75p	93p	—

Quantity Prices on application.

Hi-Volt Electrolytics

1; 2; 4; 8µF	450V	14p	32µF	450V	20p
16µF	450V	15p	50µF	350V	20p
8 + 8µF; 450 V.W		18p	32 + 32µF; 350 V.W		25p
8 + 16µF; 450 V.W		20p	32 + 32µF; 450 V.W		43p
16 + 16µF; 450 V.W		25p	50 + 50µF; 350 V.W		35p

25 YEARS OF SEMICONDUCTORS

PART 1 TRANSISTORS AND SMALL-SIGNAL DIODES

By M. J. Rose (MULLARD LTD.)

THE FIRST transistor emerged from Bell Telephone Laboratories twenty-five years ago. Since then, the whole electronics industry has been transformed. Perhaps the most important change the transistor brought about was the introduction of new technologies of manufacture.

It is from the development of these technologies that the many types of present-day semiconductor device have come. These two articles present an overall, and necessarily brief, survey of these devices.

THE FIRST TRANSISTORS

In 1948 John Bardeen and Walter Brattain of Bell Telephone Laboratories invented the point-contact transistor.

The point-contact transistor had two fine wires placed close together on a semiconductor wafer. It was shown that not only was the current flowing between one of the wires and the semiconductor wafer affected by the current between the other wire and the wafer, but under certain conditions amplification could be obtained.

Perhaps the most important result of the point-contact transistor was that it provided experimental verification of the previous theoretical work. It paved the way for the junction transistor, a much more practicable device, invented by William Shockley also of Bell Telephone Laboratories in 1950.

JUNCTION TRANSISTOR

The junction transistor is essentially a sandwich of *p*-type and *n*-type semiconductor material containing two *pn* junctions. The first transistors were literally sandwiches, being made by the alloy-junction method.

A simplified cross-section of an alloy-junction transistor is shown in Fig. 1. This method of manufacture is still used for some audio-frequency transistors today.

Restrictions in minimum base width achievable with this technology gave the early alloy-junction transistors a cut-off frequency of approximately 1MHz, although refinements of the manufacturing technique raised this to approximately 5MHz.

ALLOY-DIFFUSED AND MESA TRANSISTORS

Other types of transistor were developed during the 1950's to overcome the limitations of the alloy-junction type. One of these types was the alloy-diffused transistor. The base layer of the alloy-diffused transistor was very thin, giving a cut-off frequency of approximately 800MHz.

Another type of transistor was the mesa transistor, originally developed to improve the switching characteristics. Its construction is shown in Fig. 2. The mesa transistor could operate with switching waveforms with rise times in the region of 1μs.

The technique of mesa etching is still used today in some types of transistor.

PLANAR TRANSISTORS

The introduction of the planar transistor in 1960 marked several important changes in transistor manufacture. Silicon rather than germanium was used as the semiconductor material with considerable advantages. Silicon transistors will withstand higher junction temperatures than germanium ones, and have higher voltage ratings and lower leakage currents.

Diffusion from vapour into clearly-defined areas of the silicon wafer enabled close control to be exercised, and the diffusion areas could be constructed by photographic techniques. For the first time in transistor manufacture, true mass-production techniques could be applied, with a consequent drop in price.

In the manufacture of silicon transistors an oxide layer is grown over a wafer of *n*-type silicon. Windows can be cut in this oxide by etching in areas defined by exposure through a mask, and *p*-type silicon formed by a boron diffusion. A second oxide layer is formed, selectively etched, and *n*-type silicon formed by a phosphorus diffusion. In this way a transistor is built up, as shown in Fig. 3.

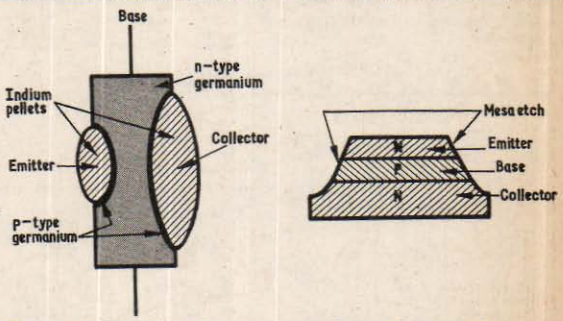


Fig. 1. Simplified cross-section of an alloy-junction transistor (left)

Fig. 2. Cross-section of mesa transistor (right)

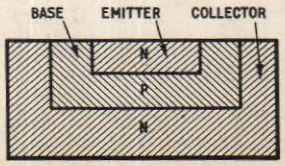


Fig. 3. Cross-section of planar transistor

Because the area of diffusion defined by a mask is the same for each transistor, the whole of a silicon wafer can be exposed at the same time. Thus up to 10,000 transistors can be manufactured on a silicon wafer 5cm in diameter in one manufacturing sequence.

Planar transistors can operate at frequencies up to the microwave region, well above 1GHz.

PLANAR EPITAXIAL TRANSISTORS

A development of the planar transistor that improves the performance is the planar epitaxial transistor. In this type, the transistor is formed in an epitaxial layer which is simply a layer of silicon with a near-perfect crystal structure. The silicon wafer on which the layer is grown forms a substrate as shown in Fig. 4.

By forming the epitaxial layer of high resistivity material but making the collector in the layer very thin, a transistor with high breakdown voltage and high collector current can be obtained.

FIELD-EFFECT TRANSISTORS

The transistors described so far are bipolar types, the current being conducted by two types of carriers (electrons and holes). The field-effect transistor (f.e.t.) is a unipolar transistor, the current being conducted by one type of carrier only.

A current-carrying channel of *n*-type silicon is surrounded by the *p*-type gate, as shown in Fig. 5. When a positive voltage is applied between drain and source, a current flows through the channel. A depletion layer is formed at the *p-n* junction of the gate and channel, and by applying a negative bias between the gate and source the depletion layer moves into the channel to restrict the area available for current flow. As the bias increases, a value is reached, the pinch-off voltage, at which no current flows. Thus the current through the f.e.t. can be controlled by the gate voltage, as in a triode valve.

The f.e.t. described is a junction f.e.t. or j.f.e.t. Another type can be constructed, the insulated-gate f.e.t., MOSFET or MOST. The initials MOS strictly speaking stand for Metal Oxide Semiconductor.

MOS refers to the construction of the transistor formed, a metal gate (aluminium or polysilicon) insulated from the silicon substrate by a layer of silicon oxide, as shown in Fig. 6.

By applying a voltage of the correct polarity to the gate, a current-carrying channel can be formed between the source and the drain, and when a voltage is applied across the source and the drain, a current flows.

The current-carrying channel in a *p*-type substrate is an *n*-type inversion layer. Similarly, a *p*-channel is formed in an *n*-type substrate. In addition, the *p*-channel and *n*-channels MOSTs can be enhancement or depletion types. Enhancement MOSTs are normally off, and require a gate voltage greater than the threshold voltage before conduction can occur. Depletion MOSTs are normally on, and require a pinch-off voltage on the gate to stop conduction.

Thus the circuit designer has four types of MOST to choose from for his application. All types of f.e.t. have very high input impedances, and so form a useful complement to bipolar transistors.

UNIJUNCTION TRANSISTOR

A unijunction transistor consists of a bar-shaped silicon slice with contacts either end and a *p-n* junction (the emitter) at some point along the length, see Fig. 7. It is therefore a three-terminal device but with only one junction.

With no emitter current flowing, the bar acts as a simple voltage divider with a fraction of the interbase voltage providing a reverse bias across the emitter junction. As the emitter voltage is increased, no appreciable current flows until the emitter voltage is greater than the reverse bias when there is a sudden increase in current. The unijunction transistor can therefore be used as a voltage-triggered device, in oscillators and sensors.

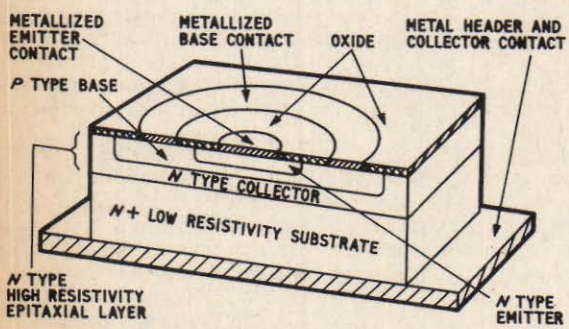


Fig. 4. Cross-section of planar epitaxial transistor

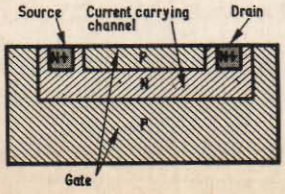


Fig. 5. Structure of junction FET

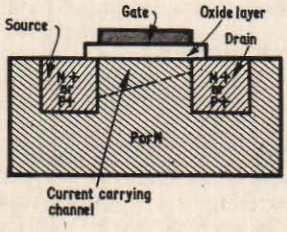


Fig. 6. Structure of MOSFET

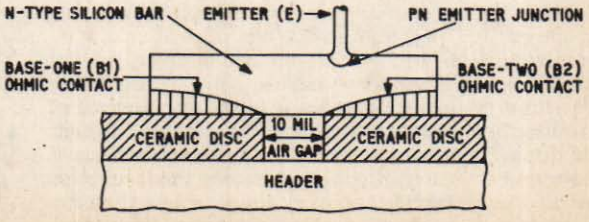


Fig. 7. Cross-section of a typical unijunction transistor

HIGHER POWER, HIGHER FREQUENCY

The development of the planar technology during the 1960's enabled the operating frequency of small-signal transistors to be raised so that by the end of the decade transistors with cut-off frequencies of 6GHz and capable of switching waveforms with rise times of 1ns were available.

Germanium power transistors could handle about 10W with a suitable heatsink. This power level was increased with the introduction of silicon power transistors. Today, silicon power transistors for low-frequency operation are manufactured by the single-diffused method, or, where high voltages are to be encountered (1kV or more), by the triple-diffused method. Powers of up to 150W typically can be handled.

The planar epitaxial technology enabled the operating frequency of power transistors to be raised considerably. More complex base-emitter configurations were developed to take operation high into the radio frequencies. A typical configuration is the interdigital one where fingers of the emitter layer interleave fingers of the base layer. Typical performance figures of present-day r.f. power transistors are 100W at 50MHz and 10W at 2GHz.

OTHER TYPES OF TRANSISTOR

The mexa transistor has an epitaxial base layer. The lightly-doped base is grown on a heavily-doped collector, the emitter layer diffused, and the complete structure mesa etched. The resulting transistor is rugged and has a low collector resistance.

Hometaxial transistors are made by simultaneously diffusing impurities on both sides of a homogeneous base layer, followed by a mesa etch of the emitter. Because of the homogeneous base, the risk of hot spots is reduced, and the transistor has good second-breakdown properties. The wide base width also gives good voltage breakdown properties.

Triple-diffused transistors are also manufactured in this way; the base and emitter are diffused on one side of the collector wafer as usual, but a third diffusion is used to form another collector layer. The technique can be used on planar or non-planar devices, and gives an improved value of collector saturation voltage.

SMALL-SIGNAL DIODES

The modern point-contact diode uses a germanium wafer to which a fine wire contact is welded. Because the current rating is very low (only a few milliamps) these diodes are only used for applications where junction diodes cannot be used efficiently, for example, as detector and mixer diodes at microwave frequencies.

Besides the low current rating, germanium point-contact diodes have a low inverse voltage and a high reverse current. These disadvantages were overcome by the introduction of the silicon junction diode in the mid-1950s. The junctions were made first by alloying with aluminium pellets, and later by diffusion. With the introduction of the planar technology, planar epitaxial diodes became available.

The limit of operating speed is set by the lifetime of the minority carriers formed by the reverse voltage. Gold doping reduces the lifetime of minority carriers in silicon, and by using silicon diodes with small junction areas and gold doping, recovery times of less than 5ns are obtained, making the diodes suitable for use in high speed computers.

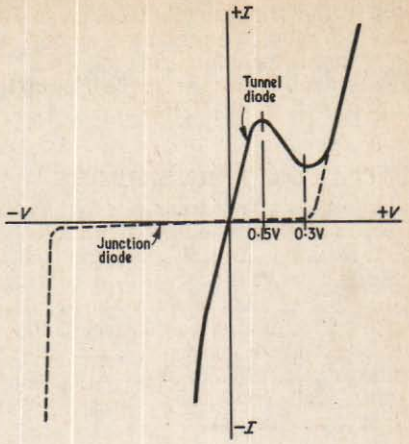


Fig. 8. Voltage/current characteristic of tunnel diode compared with junction diode

Faster switching diodes can be made by using gallium arsenide instead of silicon as the semiconductor material.

"ZENER" DIODES

As the reverse voltage across a junction diode is increased, a point is reached where the small leakage currently suddenly increases. This "breakdown" may be caused by electrons breaking from their bonds (the Zener effect), or more usually by avalanche breakdown.

In this type of breakdown, the electron minority carriers gain sufficient velocity to dislodge other electrons which in turn are accelerated sufficiently to dislodge further electrons. There is therefore a sudden build-up of current, and this may destroy the diode.

If the breakdown can be controlled, however, a useful range of devices, generally called (incorrectly) Zener diodes but more accurately voltage regulator diodes, is obtained. The value of breakdown voltage is determined by the doping level of the impurities in the diode.

Voltage regulator diodes are incorporated into supply lines to provide a simple method of stabilisation. Special types with very low temperature coefficients are called voltage reference diodes, and provide a simple form of voltage standard. If the voltage regulator diode is made rugged enough to withstand the dissipation, then it can be used to suppress voltage transient surges. Such range suppression diodes can withstand surges as high as 10kV provided the duration is only a few microseconds.

TUNNEL DIODES AND VARACTOR DIODES

Two types of diode use the properties of *pn* junctions to give special characteristics. The tunnel diode uses a normal *pn* junction in which both regions are heavily doped. With a reverse bias such a large number of electrons are present at the junction that some "tunnel" their way across the junction. Similarly, with a small forward bias below that required for conduction in a

normal diode, tunnelling occurs. The forward tunnel current reaches a peak at approximately 0·15V, then decreases until normal forward conduction occurs at approximately 0·3V.

The V/I characteristic of a tunnel diode is shown by the full line in Fig. 8 with, for comparison, the characteristic of a normal diode in broken lines. The negative resistance part of the tunnel diode characteristic can be used in oscillators.

The varactor diode uses the capacitance of a reverse-biased *pn* junction. The reverse bias causes a depletion layer between the *p* and *n* regions, the width of the layer being proportional to the voltage. The junction area is made large to exploit this effect and to provide a reasonable change in capacitance with voltage.

Varactor diodes can be used as tuning elements to replace such devices as the parallel-plate tuning capacitor. They also have application as frequency multipliers. A string of varactor diodes and tuned circuits can be used to generate power efficiently at microwave frequencies from a lower-frequency source.

MICROWAVE DIODES

Some types of diode have properties that make them especially useful at microwave frequencies. Such types are the backward diode, PIN diode, Schottky barrier diode, and Gunn diode.

The backward diode, as the name implies, is a reverse-biased junction diode but one in which the breakdown voltage occurs very near the zero voltage point. Thus the resistance with reverse bias is lower than the forward resistance. Backward diodes can therefore be used as microwave detectors.

The PIN diode is also a *pn* junction but with a layer of intrinsic silicon between the *p* and *n* regions. With a forward bias, the PIN diode presents a low resistance because the bias injects carriers into the intrinsic region. With a reverse bias, however, the resistance remains very high. The PIN diode can therefore be used as a detector and also as a switch.

The Schottky barrier diode uses a metal-semiconductor junction as the rectifying element. Like the point-contact diode, the Schottky diode has the advantage of not suffering from minority carrier storage effects that limit the performance of junction diodes. Thus Schottky diodes can be used for higher-frequency applications, and also for very fast switching.

GUNN DIODE

The Gunn diode is not, strictly, a diode at all as it does not contain a rectifying element. It is formed by a thin layer of *n*-type gallium arsenide grown on a gallium arsenide substrate. The substrate forms the "anode" of the Gunn diode, while a "cathode" contact is formed on the face of the *n*-type layer.

When a low d.c. voltage is applied across the diode, high field regions called domains are formed at the cathode and rapidly cross to the anode. Current pulses are superimposed on the steady current through the diode, the frequency of the pulses depending on the transit time and therefore the thickness of the layer. For a thickness of 10μm, the frequency is 10GHz.

The Gunn diode can be mounted in a tuned cavity to form a simple microwave oscillator with advantages in space and cost over such devices as klystrons. Maximum output powers up to 3W can be obtained from Gunn diode oscillators.

The second article will describe power devices, photo devices, and integrated circuits.

PHYSICS EXHIBITION

IT IS interesting to see that, in the issue in which PRACTICAL ELECTRONICS publishes an article on an "Electronic Nose", we are also able to describe an electronic alcohol meter which will probably replace the so-called Breathalyser in drinking-and-driving cases and prove useful in many fields of research.

BREATHALYSER?

The Alcolmeter, as the latter is called, is an electronic instrument capable of indicating the presence and concentration of certain chemicals in air. It was on show at the Physics Exhibition, Earls Court, in April together with several other interesting items which show the steady movement of electronics into the important field of measurement and control.

The Alcolmeter uses a "fuel cell" developed to detect only alcohol unlike the one used in the P.E. Electronic Nose, which is capable of much wider application. In operation the Alcolmeter cell gives an output in millivolts dependent on the alcohol content of air drawn into a cell chamber by a small single-stroke pump. This is amplified and applied to a meter calibrated in milligrams of alcohol per 100 millilitre of blood. It is understood that accuracy is up to the requirements for normal police operation here so we can perhaps expect to see the instrument in use on the roads soon.

Of course, such an instrument has many applications in research and, using somewhat different cells, can be made to detect other types of chemical.

Light detection in the operation of power stations was well in hand on the CEGB stands with a demonstration of the Nordust smoke monitor, used to identify the presence of dust in smokestack gases. This instrument uses light scattered back to a photocell from dust particles in the airstream. Here electronics not only makes the operation possible in terms of sensitivity, as the amount of light available is very small, but also in terms of removal of anomalies due to cell variables by using balanced input operational amplifiers.

LOOKING AT FIRE

Similarly, it is only because electronic techniques such as correlation between two signals exists that the CEGB have been able to develop a flame monitor capable of identifying one flame in a furnace using perhaps 20 burners. This is effected by looking at the flame in question from two different directions, correlating the outputs of the viewing cells and indicating the amount of correlation present. Where there is a high percentage, say 80 or more, the flame is alight. Under any other conditions the amount of correlation is much lower. Such equipment can be used to initiate some form of "flame-out" warning.

On the signal generation front it looks as if there are some interesting developments afoot. The Royal Radar Establishment at Malvern have developed some devices called Surface Acoustic Wave Oscillators using an excess gain amplifier and a SAW delay line.

As both devices are very small and can be made using photoetching techniques, samples have been prepared capable of oscillation up to 490MHz as a fundamental frequency and mounted in a single TO8 can. It is envisaged that frequencies up to 1GHz are well within the bounds of possibility with this device. But first of all some problems over temperature variations have to be overcome.

Gerry Brown . . .

ON THE FRINGE



OHM NURSERIES

Gardening is not one of my personal predilections, although there are times when the subject manages to stir a glimmer of interest in me, as when, a few months ago, someone employed electronic means to accelerate crop-shedding (which you will, no doubt, recall) in orchards. Then there's the subject, requiring a lot more scrutiny (and perhaps something to which we shall return) called "Electrology" claiming an ability to reproduce whole outlines of leaves by previous photography of incomplete or damaged specimens!

However, the subject taking interest with a number of nurserymen in Canada right now is the result of some researches recently conducted by Professor D. S. Fenson and Dr G. Craig for their department of agriculture. Apparently, too much guesswork is associated with assessing the right time to lift plants for storage during the winter, following a hardening-off period in the autumn.

Measurement of the plants (in this case the strawberry) resistance, electrical that is, they have established a direct correlation with the fittest time to dig 'em up. This resistance changes (they don't say how) with the sudden drop in temperature immediately preceeding the winter, thus permitting early removal of the less hardy plants before frost damage can occur.—Do I hear an "ohm groan" from the non-gardeners?

GETTING THROUGH

Would you believe, communication-without-wires (apart from jungle drums, semaphore, and heliographs) was "old hat" before either Marconi, or, that great Russian, Popof, "invented" radio? Actually, it was about 1866, even prior to the invention of the electric lamp, that a dentist, one Mahlon Loomis, demonstarted a workable electric wire-less set-up over a distance exceeding 14 miles. Just how this worked is not terribly clear, but in essence it consisted of a pair of kites, one at each station, carrying some several hundred feet of wire "line". This, at the "transmitter" was grounded to earth, while at the "receiver" it was terminated to earth via a sensitive galvanometer.

The principle of operation seems to have been one which relied upon charged air currents and, presumably, a stiff breeze to boot. But credit where it is due, he *did* manage in some way (by, probably, making and breaking the transmitter earth connection) to interfere with the static charge in the vicinity of the wire and so influence the overall electrical equilibrium; sufficient, certainly, to be detected well over ten miles away.

Obviously, there must have been both considerable delays, and uncertainty about the reception (particularly for changes in wind direction and speed) but his idea at the time carried enough conviction for two fair sized companies to be formed; unfortunately, poor old Loomis died without ever fully realising his ambitions and with him too did the "atmospheric communicator".

RADIO VACUUM

You might be interested to hear that even today people are experimenting with methods foreign to normal transmission techniques to overcome the many disadvantages, to name poor penetration of the walls of buildings as a typical one. Just the other day I learnt that Dr Richard Arnold of Argonne National Laboratories in Illinois managed to achieve success with the transmission of a pulse-coded signal along a muon beam of all things! Since muons are atomic particles, detection consisted of a scintilation counter arrangement.


If this were not enough, my colleague, inspired by all this chat about particulate transmitters, assures me that once he has overcome the teething troubles with the bag size of the laboratory vacuum cleaner, he is entirely convinced that we will be able to announce the birth of the worlds first dust'n'soot scatter propagation system; what do you think?

NASTY TASTE?

Apart from the ferry, Gosport now seems to be in the position to capture our hearts with yet another singularly cunning piece of wizardry; a firm there has brought into being an electronic (more accurately, ionic) water de-bugging device.

Designed to clip into the supply pipe, it works on the principle that bacteria have a common dislike for silver ions, and comprises simply a pair of electrodes which cause ions to go into solution and rapidly interact with the bugs, "doing them in" very quickly. One of these units can comfortably handle as much as 250 litres of brackish aqua in a little over a minute or so.

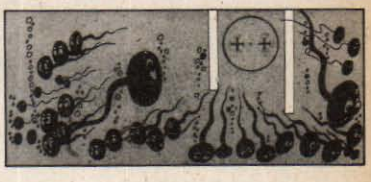Good news for campers, but what happens once it's in the gut, I wonder? Perhaps the stomach's hydrochloric acid converts it to the chloride which ought to be very harmful, except to your pocket; have you seen the price of silver recently?



QUESTION OF FITNESS

Probably because I'm a bit of an "odd-ball" anyway, the Editor and I sometimes have difficulty agreeing about the relevance of subject matter in this column to the field of electronics; and, since this magazine is one which sets out to deal fairly exclusively with the subject, it isn't unreasonable that he should expect there to be some link. But there's the problem. Just what is some link? And by exclusively, do we really mean restrictive?

Each time you buy your copy of P.E. have you ever wondered whether, sooner or later, the "crunch" might come when there will be literally nothing left to invent? Of course, there are the good old standbys like electronic doorbells, burglar alarms, and so forth, plus even more sophisticated ways of doing these same things in miniature. But what then?

In this inventing lark, for whatever the outlet, it seriously looks as if, to survive, we must look upon our particular subject in a less exclusive way. Indeed, to innovate in the real sense of the word must require us to never completely exclude any other discipline, just in case it turns out to be vital!


Once we (and, certainly, industry) accept this maxim, my prediction is that it will only be a matter of time before technology sees the "birth" of Interfacing Engineers capable of performing a sort of inter-disciplinary integration. Henceforth, instead of knowing an awful lot about a little, they will be in the unique position to discover myriads of, previously unheard of, applications from the suddenly limitless number of available permutations.

Let's drink to the daring, the real innovators, and to the possession of minds that never permit us the hollow excuse to be bored stiff!

PE Sound Synthesiser 6

TONE CONTROL & EXPERIMENTAL SOUND STUDIO

By G.D. Shaw

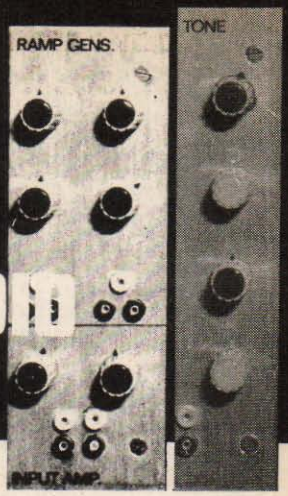

THIS month the Tone Control module will be described together with some notes on the setting up of an experimental sound studio.

HUTCHINSON TONE CONTROL

The tone control circuit used in the Synthesiser is based upon the design by P. B. Hutchinson which appeared in *Wireless World* (November 1970) and which, in turn, was inspired by R. Ambler's design for a "Tone Balance Control" which was published in the March 1970 issue of the same journal. A number of minor changes have been made to the original circuit in order to make it fully compatible with the circuitry in the Synthesiser but the frequency selective network, suggested by Hutchinson have been retained.

The type of tone control usually adopted for the majority of domestic equipments is that in which the greatest effect occurs at the extreme ends of the audio frequency spectrum while the mid-band frequencies remain relatively unchanged. The Baxandall and Siemens designs provide just such a characteristic. In recent years however there has been a tendency towards extending the scope of the tone controls in domestic equipment.

For purely domestic purposes there is no doubt that the ability to manipulate the frequencies over the whole of the audio frequency spectrum can make an enormous difference to the quality and effect of the ensuing sound. The Hutchinson tone control circuit combines many of the advantages of mid-band correction with relatively severe "end of range" effects all of which are extremely useful to the experimenter in sound.

TONE CONTROL RESPONSE CURVES

Fig. 6.1 shows a graphical representation (shown dashed) of the kind of effect obtainable by means of a conventional tone control circuit of the passive kind. Note that there is very little effect on the mid-range frequencies even when the treble and bass controls are adjusted to their maximum value positions.

On the other hand, the designed response of the Hutchinson circuit (shown solid) provides an overlap of bass and treble responses ranging from about 200Hz to 4kHz. The provision of separate boost and cut controls to both the bass and treble ranges therefore means that it is possible to tailor the overall characteristic of the curve to suit many particular applications. It is, for example, possible to build up tonal correction curves to compensate for deficiencies in sound transmission transducers such as pick-ups or loudspeakers.

The basic principle of operation is illustrated graphically in Figs. 6.2 and 6.3. Each potentiometer in the circuit controls the 3dB frequency of a curve having a slope of about 6–7dB/octave, the function of the potentiometers being in accordance with the direction of the slope. In Fig. 6.2 the dashed lines (1) represent the effect on the audio frequencies when all the controls are set flat. Since both the boost and cut selective networks are designed to have a fairly close match a similar result is obtained if all controls are set to their maximum positions.

With all the controls set flat, the effect of advancing any one of them is to bring the related slope further into the audio spectrum. The dotted line (2) shows the result of advancing the treble boost control about halfway. So far, of course, the resultant curve is similar to that obtainable from a conventional tone control circuit but if the treble cut control is now advanced from its flat position the effect is to reduce the

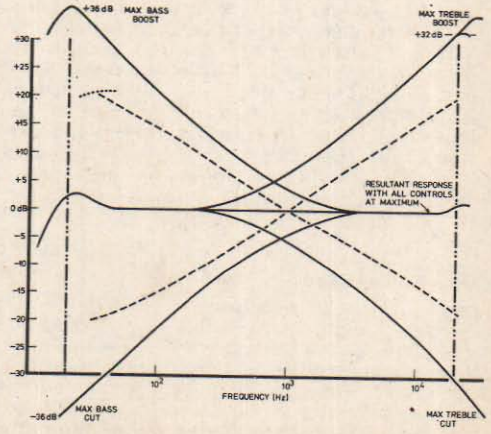


Fig. 6.1. A comparison of characteristic curves obtained from a conventional passive tone control (shown dashed) and those from the Hutchinson circuit (shown solid)

degree of boost to the upper frequencies without affecting the boost applied to the middle frequencies. This is shown as the overall resultant (4) by means of the solid line in Fig. 6.2.

An advantage of this form of control lies in the possibility of combining the effect of boost and cut settings from opposite ends of the spectrum to provide a resultant slope of up to 12–14dB/octave. A typical curve obtainable from such combination is shown in Fig. 6.3.

TONE CONTROL BASICS

The general form of the tone control circuit is shown schematically in Fig. 6.4, from which it will be seen that two frequency selective networks are employed. One lies directly in the signal path to the operational amplifier and acts as the cut network whilst the second lies in the amplifier feedback loop and acts as the boost network.

The design of each network is identical and is shown in Fig. 6.5. C1, R1 and VR1 form a simple first-order high pass filter with a slope of about −6dB/octave. The 3dB frequency is given by 1/CR where C is the value of C1 and R is the value of R1 in series with the value of VR1. With the component values shown the highest 3dB frequency is thus 1·54kHz and the lowest is 28Hz. C2, R2 and VR2 form a simple first-order low pass filter again with a slope of about —6dB/octave. In this case the highest 3dB frequency is 22·6kHz and the lowest is 415Hz.

The same network is able to provide boost characteristics since, in the feedback path of the operational amplifier, it reduces the a.c. feedback thereby increasing the gain of the amplifier.

Depending upon the settings of the potentiometers the input impedance of the frequency selective networks can vary between 470 ohms in parallel with 470 ohms at minimum and 25·5 kilohms in parallel with 25·2 kilohms at maximum. It is thus necessary to provide a driving source having an output impedance of less than 200 ohms.

Similarly, it is necessary to compensate for changes in output impedance of the tone control circuit by driving into a load of 50 kilohms or more.

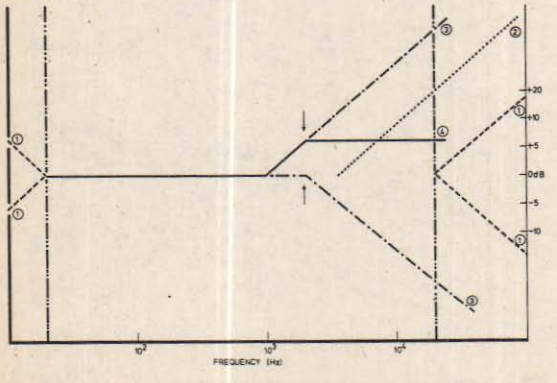


Fig. 6.2. Operation of the Hutchinson Tone Control circuit. Controls set flat ①, treble boost advanced—other controls flat ②, projected treble boost and cut with controls adjusted separately ③, resultant curve resulting from summing the boost and cut curves

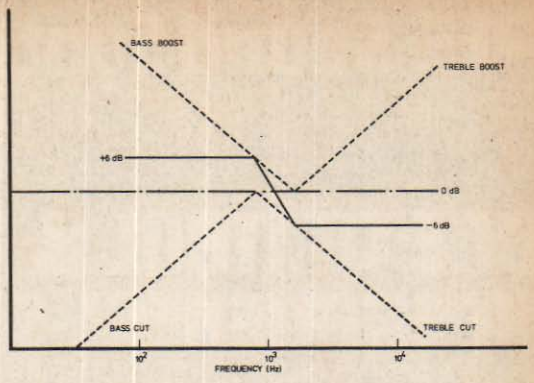


Fig. 6.3. Combining controls to give a 12dB/octave cut-off at mid-band. Dashed curves indicate responses when controls are used separately

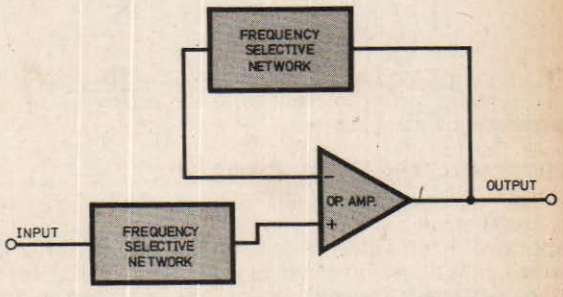


Fig. 6.4. Block diagram of Hutchinson Tone Control

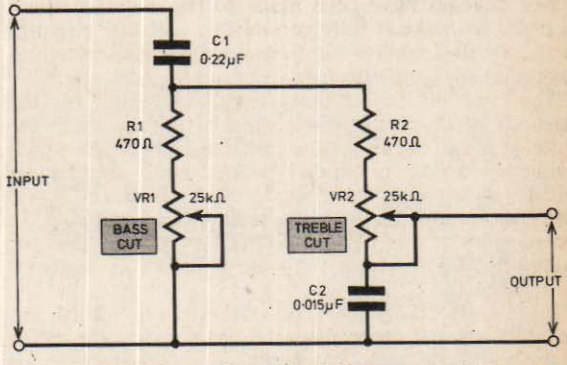


Fig. 6.5. Configuration of high pass and low pass filters used in Hutchinson Tone Control

THE COMPLETE CIRCUIT

The complete circuit of the Tone Control is shown in Fig. 6.6. TR1 is an emitter follower which provides a low impedance drive. R10 and R11 provide d.c. feedback to maintain the output of the amplifier at 0 V. Capacitor C6 decouples audio frequencies from the d.c. feedback loop and R12 provides a limit to this decoupling so that the a.c. closed-loop gain of the amplifier is limited to about +36dB. In the original circuit this was found necessary to avoid resonances at the extreme ends of the audio spectrum under conditions of maximum boost. The resonances were caused by interaction between the boost characteristic and the d.c. feedback loop at the bass end, and the high frequency compensation of the amplifier at the treble end.

TONE CONTROL MODULE

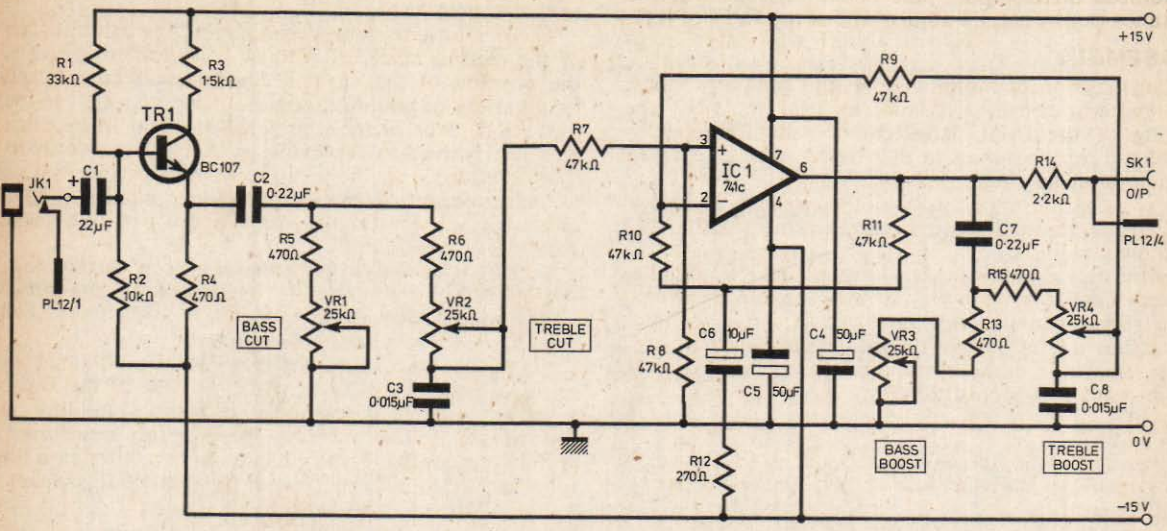


Fig. 6.6. Circuit diagram of the tone control

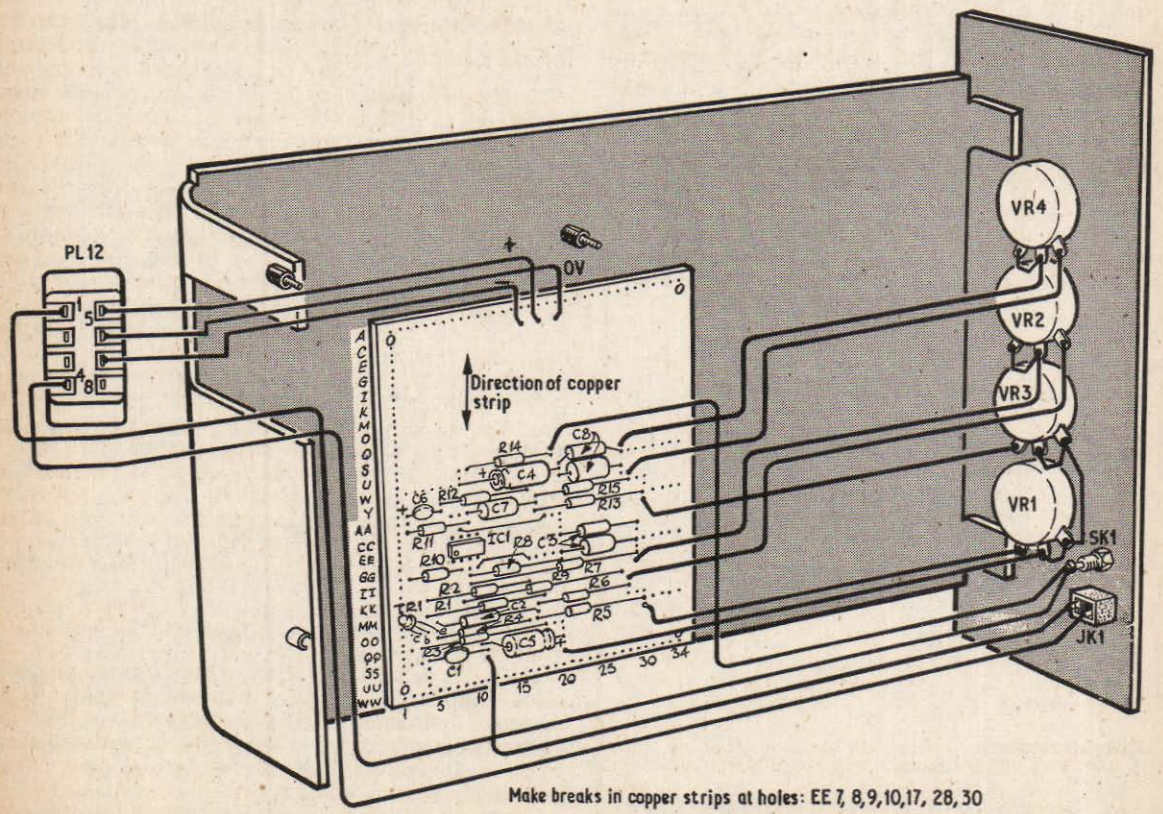


Fig. 6.7. Veroboard component assembly and wiring details for Tone Control module

The original circuit utilised a 709 operational amplifier as the active element and substitution of a 741 has resulted in the virtual elimination of high frequency resonance problems. However there is the possibility that low frequency resonance may remain under conditions of maximum bass boost although this can be tuned out by careful adjustment of the value of R12.

ASSEMBLY

Construction of the module should generally follow the pattern already outlined, that is, assembly and wiring of the front panel components followed by assembly of the module hardware and finally the wiring in of the circuit board.

Layout of the components on the circuit board is not too critical and the recommended circuit board layout is shown in Fig. 6.7.

Some care should be taken in wiring up the potentiometers since it is quite easy to wire these in the wrong way round and this will give rise to some very odd results during testing out the finished module. Fig. 6.7 also shows the component layout and wiring on the front panel and McMurdo plug.

TESTING

Testing the module covers only the establishment of performance characteristics at various points in the audio spectrum and it is recommended that a sine wave oscillator be used for this purpose. Starting with the oscillator at 20Hz the frequency should be advanced in multiples of 20Hz up, to and including 100Hz and thereafter in multiples of 200Hz up to 1,000Hz.

From 1,000Hz the frequency advance should be in steps of 2,000Hz. This procedure will give about 20 points on the graph and should be quite sufficient to establish the circuit characteristics.

COMPONENTS . . .

TONE CONTROL

Resistors

R1	33kΩ	R7–R11	47kΩ (5 off)
R2	10kΩ	R12	270Ω
R3	1·5kΩ	R13	470Ω
R4	470Ω	R14	2·2kΩ
R5–R6	470Ω (2 off)	R15	470Ω

All 2% ½ watt metal oxide

Capacitors

C1	22μF tantalum 16V
C2	0·22μF polyester
C3	0·015μF polystyrene
C4–C5	50μF elect. 25V (2 off)
C6	10μF elect. 25V
C7	0·22μF polyester
C8	0·015μF polystyrene

Integrated Circuit

IC1 741C 8pin d.i.l.

Transistor

TR1 BC107

Potentiometers

VR1–VR4 25kΩ linear min. moulded carbon (4 off)

Miscellaneous

JK1–3·5 mm jack socket, SK1—2 mm miniature socket, 0·1 matrix Veroboard

The measuring procedure should be repeated five times, the first being with all controls set flat and subsequent measurements with each of the individual boost and cut controls set to maximum in turn. If component values have been chosen as specified the resultant graph should bear a very close resemblance to that shown in Fig. 6.1.

There is little to be said concerning the actual usage of the module since, as with all tone control circuits, the position of the various controls will be dictated by a variety of circumstances not least of which is the individual constructor's preference. The little extra trouble involved in the manipulation of four controls is well rewarded by the greater versatility of the system in the provision of exactly the sound required. As a general guide to module usage there are two basic methods of operation.

Tonal correction curves are provided by setting both the boost and cut slopes to the middle of the audio spectrum and then moving one or the other out until the required effect has been achieved.

Simple boost or cut characteristics are obtained by setting all the slopes to the extreme ends of the audio spectrum and then moving the appropriate one in towards the middle until the desired effect is achieved. If only one control is manipulated in this latter case the resultant slope will, of course, be about 6dB/octave.

FORMING A STUDIO

In part four of this series the reader was introduced to the idea that the tape recorder was a very necessary adjunct to the Synthesiser if the full potential of the instrument were to be realised. This idea may be extended by considering the Synthesiser as the central focus around which may be constructed a simple yet versatile sound studio capable of providing a wide range of facilities to the keen experimenter. Thus, in addition to the tape recorder, there are a number of other items of so-called peripheral equipment which may be added to and usefully extend the versatility of the system. Fig. 6.8 illustrates one possible arrangement which utilises a fairly wide range of external apparatus.

In common with the basic concept of modular construction for the Synthesiser, the establishment of a studio may also be considered on the basis of a form of modular growth in which individual pieces of apparatus, including the Synthesiser, are treated as separate modules. In the Synthesiser itself all the modules plug into a bus-bar system which provides power supplies and signal paths for the interconnected, prewired modules. In a similar fashion the studio must have a central signal routing system and this is provided by what is known as the main patch. The power supplies for the studio apparatus are not, however, routed via the main patch, and the provision of a power supply distribution system will be dealt with later in these notes.

THE MAIN PATCH

The main patch in any studio is thus a very important piece of apparatus. Ideally it should provide a rapid means of interconnecting the signal pathways of all the apparatus incorporated in the studio in virtually every possible configuration and do so with a minimum of noise and crosstalk addition.

There are a number of possibilities for the construction of the main patch, the actual method adopted depending largely upon the means and inclination of individual constructors. It is worthwhile stressing,

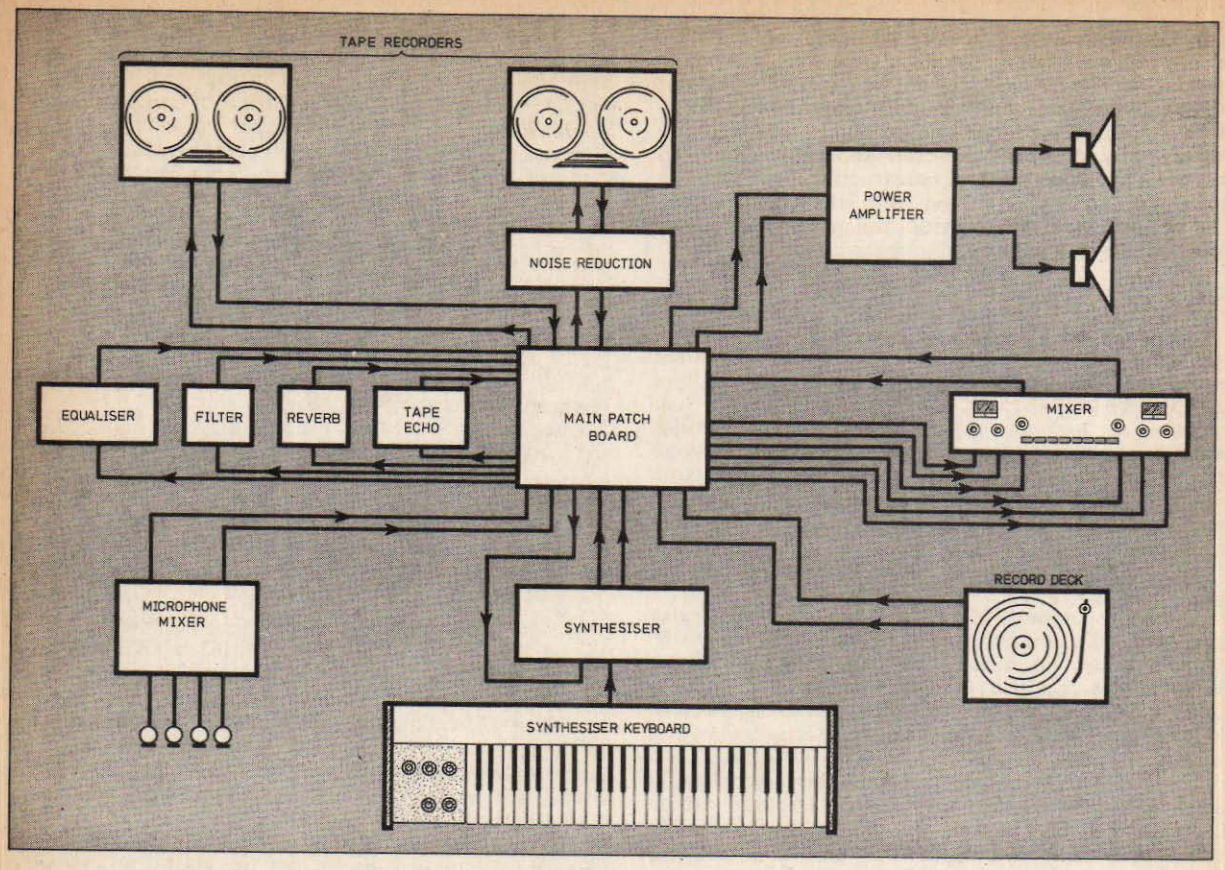


Fig. 6.8. One possible arrangement of apparatus to form an experimental sound studio

however, that a little extra quality in components chosen and effort expended in construction will be amply repaid in terms of reduction in the problems associated with poor contact assemblies.

One method of construction involving very little effort on the part of the constructor lies in the employment of ready-built patching matrices such as those manufactured by Sealectro Ltd. Matrices of a similar type are supplied "built-in" in a number of commercially available synthesisers and have proved to be quite successful in this application. The adoption of a ready-built matrix has the advantage that the patch can be assembled very quickly. In addition, the space taken by the patch is very small indeed although this could perhaps be something of a disadvantage if the screened signal cables for connection to the matrix are of any size at all. Another idea for the construction of a patching system is the use of 3·5mm jack sockets arranged generally as shown in Fig. 6.9. It is important to note that the type of jack sockets employed should be of the open-circuit variety.

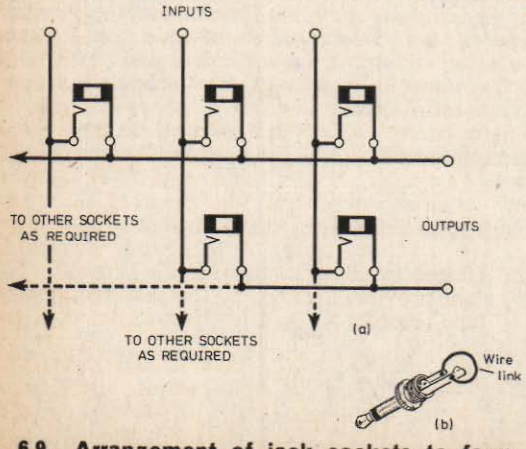


Fig. 6.9. Arrangement of jack sockets to form a patch board

The type of main patch employed in professional circles frequently makes use of a system based upon standard G.P.O. type jacks. Although rather larger than either of the other possibilities mentioned the greater contact area and general robustness of the components involved makes this latter system worthy of consideration if any serious work of high quality is envisaged. In terms of cost the system is not significantly more expensive than those previously mentioned.

OVERCOMING HUM

Perhaps one of the greatest problems associated with the interconnection of a range of apparatus lies in the formation of ground or hum loops within the system. In some circumstances the source of the hum can be quite difficult to trace and it is therefore worthwhile expending a little time in establishing a system which eliminates, from the outset, as many sources of hum as possible.

By far the greatest source of hum lies in the formation of loops through the earthing system of mains powered apparatus. The frequency of the hum can vary between 50Hz and 120Hz depending upon the mains frequency and type of rectification employed. Until quite recently the majority of mains powered apparatus employed the live chassis method of construction in which the signal ground was common with the mains earth. This type of apparatus provides the greatest hazard as far as the formation of hum loops is concerned.

COMMON POINT EARTH

Connection of a number of pieces of mains powered apparatus into the main patch may be accomplished as shown schematically in Fig. 6.10. In this case power supplies are distributed from a panel which has one common earth to the mains. Screened signal cables are used where the screen is disconnected at one end of the cable only. Thus the connections at the main patch are made on high signal levels only while the circuit is completed through the common earth in the power distribution panel.

Although these latter remarks apply particularly to apparatus in which live chassis contruction has been employed, a similar form of interconnection may be employed with apparatus which has a fully floating signal ground, i.e. there is no electrical connection between the signal ground and the mains earth.

In circumstances where *all* the apparatus involved is of this latter form of construction it is necessary to provide a common ground return on all signal lines and this is best done by connecting the screens of all signal cables to a common point at the main patch. This latter point is left floating except in the case where mixed types of apparatus are being used and, in these circumstances, the signal cable screens of apparatus with floating outputs only are commoned at the main patch and this point then returned direct to mains earth.

CHOOSING THE RIGHT CABLE

A second prime source of hum lies in the type of cable used to route signals and its relationship to the impedance of the inputs to which it is connected. It is best to choose a signal cable which is compatible with both low and high signal level inputs and thus one should steer clear of the majority of commercially available so called miniature signal cables which are prewired to a range of plugs and sockets. Unfortunately many of these, whilst perfectly suitable for the transmission of relatively high level signals into high impedance loads, are quite unsuited to low impedance networks due to the relatively high impedance and core/screen capacitance of the cable itself.

A signal cable which should prove suitable for most purposes in the studio will have a nominal impedance of about 50 ohms and a core screen capacitance of not more than 100 picofarads/metre.

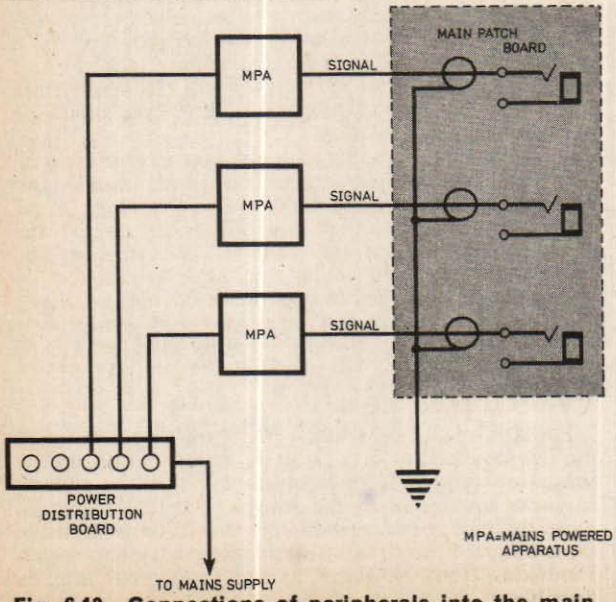


Fig. 6.10. Connections of peripherals into the main patch

CHOICE OF PERIPHERALS

Referring again to Fig. 6.8 the choice of peripherals for the Synthesiser must rest primarily with the individual, the only limiting factor being the compatibility of one unit with another. Although all the equipment shown is available commercially in several different forms a large proportion of it could be constructed at home with the aid of designs published. For example the Synthesiser Reverberation Amplifier (to be published next month) can be employed, without modification, to drive the spring line unit type HR162 available from Henry's Radio Ltd. Commercially available reverberation units include those manufactured by Eagle, Grampian and Sansui ranging in price from about £20 to £70 and offering a variety of facilities.

The choice of mixers is legion and can range from the four channel T.T.C.–B2005 distributed by Adastra at about £4 to the four channel Unimixer by Soundex at prices from about £90. Again, however, the constructor may opt to build his own mixer from a range of published designs.

The choice of filter units is rather more restricted for domestic users but for those with about £200 to spend the Levers-Rich A501 offers full audio spectrum equalisation in seven bands.

THE TAPE RECORDER

As with the case of the mixers, the choice of tape recorder is extremely wide but can be narrowed down by application of a list of specific requirements which are desirable although not absolutely mandatory. In professional circles the production of a Synthesiser recording may entail a mix-down from perhaps as many as twenty-four discrete tracks. In these circumstances the final master tape will have been involved in only one tape to tape transfer and consequently the recorded sound is likely to have suffered only the very slightest loss in quality.

If the amateur attempts to simulate these professional methods (in terms of tracks involved) with the equipment normally available to him there may be as many as fifteen to twenty tape transfers involved in a very complex recording. Thus the quality of sound on the tapes involved in a number of transfers is likely to be much reduced in comparison with the original. This factor alone provides the first and foremost requirement of any tape recorder to be used for creative work and that is quality.

In general terms the purchaser should invest in a machine which offers the best possible specification coupled with a minimum number of features designed to ease the problems entailed in the production of good quality recordings. These may be summarised as follows.

SPECIFICATION AND MACHINES

Three speed machines are preferable with 38cm/sec: 19cm/sec and 9·5cm/sec providing the ideal. Speeds below 9·5cm/sec are unlikely to be very useful. Three or four heads with provision for "on" and "off" tape monitoring. Stereo quarter track machines having sound-with-sound facilities, ideally through the medium of an input mixer, provide the minimum facilities for just about the only form of multitracking available to the average amateur.

There are a number of tape recorders on the market which combine an excellent technical specification with the features listed above. Amongst these are: Akai 1720L and GX220D; Beocord 1600; Ferrograph 702 and 704; Philips N4418 and N4450; Pye 9137; Rovex Series 77 1104; Sony TC630 and TC270; Telefunken M204TS; Uher Royal de Luxe.

As far as sound-with-sound or track transfer is concerned most of the recorders listed employ slightly different methods of providing this facility involving the use of one or more switches and, in some cases, an external signal routing cable. In this respect the Philips N4450 is notable in that, after laying down the first recording, this may then be transferred back and forth between tracks, with or without the addition of further material, by the manipulation of a single switch. This latter recorder also incorporates facilities for the addition of echo/reverberation again at the throw of a switch.

DECK CONVERSION

Recorders offering the facility of more than two tracks, or four tracks if one includes the quadraphonic types that are beginning to make their appearance, would normally be expected to be priced out of the reach of most amateurs. The determined constructor, however, could do worse than consider the conversion of some of the computer decks which become available from time to time. Several of the capstan driven decks now available from about £40 are superbly engineered devices and suitable for conversion. The speed of computer decks is usually quite high but this need not necessarily be a disadvantage since it would be used for record and replay of its own material only.

Heads are available from a number of sources. Gresham, for example, manufacture an eight-track, half-inch head for record/replay purposes at a price of around £70–£80. For the purposes of erasing, economies can be made by stacking a number of stereo erase heads. The electronics for the recorder could be based on the Hi-Fi Tape Link (recently published in this magazine) or, alternatively, on the range of Motorola integrated circuits designed specifically for tape record/replay purposes.

OTHER ADDITIONS

The addition of a Dolby B noise reduction unit should be a prime consideration and for a studio system it is best to choose a discrete unit rather than have the system built-in to a recorder.

Other useful additions to the studio include a separate power amplifier with speakers for monitoring purposes and a suitable turntable unit. These latter items could generally be "borrowed" from the domestic Hi-Fi system as and when required.

Next Month: The Meter Unit; Voltage Controlled Reverberation Amplifier and Ring Modulator.

NEWS BRIEFS

Telephone Scrambler for Commercial Use

FOR businessmen who require absolute security in their communication, EMI have introduced a new electronic scrambler for use with both private and public telephone networks. Known as the Privateer it is suitable for a wide number of applications in business, commercial and industrial organisations.

Once a telephone call has been set up in the conventional manner the Privateer telephone is brought into operation simply by pressing a separate switch. Subsequent conversation is then electronically scrambled as it is transmitted to the telephone line, and only becomes intelligible when it is unscrambled by matching equipment at the receiving end.

Commercial Radio

STUDIO automation is expected to be a major feature in many of the radio stations forming Britain's new commercial network which will start broadcasting within the next 12 months. The trend is being set by London's general entertainment channel Capital Radio, which is aiming for equipment which can automatically select and play a high proportion of the station's daily programme output from material stored on magnetic tapes.

Negotiations are going ahead with EMI to supply equipment from their extensive range of Schafer radio automation systems.

Equipped with a solid-state memory, this system is able if required, to provide a full 24 hours of continuous broadcasts—the memory being programmed to select on a time or sequential basis pre-recorded "events", including entertainment, commercials, and station announcements, from its vast repertoire. Using a keyboard, an operator can insert a complete day's programme in the memory, building up the programme on a minute by minute basis if required.

Data Transmission

MANY different kinds of information, from heartbeats to motorway hazards, can now be transmitted over Britain's public telephone network in a new communications service introduced by the Post Office on June 1.

During trials, the new Datel 400 service has already been used to send heartbeat readings from a small hospital to a large one a mile away, and information on river pollution has been sent to a Government laboratory. The latest development being studied at the moment is the sending of information on motorway hazards and weather conditions to a central monitoring point.

Golden Jubilee

IN April the well-known components manufacturers, A. F. Bulgin & Co. Ltd., celebrated their 50th anniversary with an announcement of unbroken profit figures stretching back over the full 50 years to 1923 when Arthur Bulgin started the company on £100 capital.

It is perhaps indicative of the value of "service" that this organisation who hold as their aim to provide customers with a service through a family company, that they have managed to succeed so well in the face of growing and aggressive international competition.

At the celebrations Arthur Bulgin, managing director, presented three new members of the company's 25 Year Club with gold watches including Albert Ridpath, foreman of the injection moulding section, who becomes the 50th member of this club. Quite a record for a company started on £100 and still running as a family concern.

LOGIC TUTOR EXPERIMENTS..



NAND GATES

TO avoid having to make, and use, three different types of circuit (AND, OR and NOT gates) to provide logic functions; the modern logic designer uses exclusively NAND gates. By suitable arrangement of these it is possible to generate any logic function that is desired and this type of gate is to be used throughout this series.

NAND VARIANTS

A NAND gate is made by inverting after an AND; the simplest possible circuit is shown in detail in Fig. 3.1 and depicts a basic form of DTL (Diode Transistor Logic). The DTL used in the Logic Tutor is only a minor variant of this circuit; do not confuse this with the basic TTL (Transistor Transistor Logic) NAND gate—Fig. 3.2—which, although it carries out the same function, has entirely different input gating and output stages.

Though NAND is a compound of AND with NOT it is so commonly used that it is considered to be yet another fundamental gate and as such has a standard symbol of its own (Fig. 3.3.). It is possible to obtain 1, 2, 3, 4 and 6 input NAND gates as standards and certain DTL gates have facility for the number of inputs to be expanded by adding extra diodes at the expander node.

Select a two input NAND on the Logic Tutor and connect the inputs to two logic level switches monitoring the output level on one of the lamps. The output will be the inverse of AND as shown in the truth table ($Q = \overline{A \cdot B}$) which means that the output will always be level 1 until all the inputs are at level 1 and at that condition the output will fall to 0. Verify this for yourself and then do the same with a 4 input gate.

INVERT FROM NAND

We demonstrated INVERT last month, but now look at the truth table and Fig. 3.4 to see how this came about. Consider a gate with inputs A and B shorted together and the shorted node called X. If X is 1 both A and B will be 1—refer to the truth table and see that two ones on the input of a NAND give an output 0. If X is made 0 both A and B will be 0 and this is shown to give an output of 1. Thus whatever X is the output is the opposite—an INVERT or NOT function.

Another way of obtaining INVERT is to make input B permanently a level 1. Whatever A is, the output will be the opposite.

A point worth noting is that in all forms of current sinking logic (DTL and TTL) a floating input to a NAND gate will be presumed (by the gate) to be at level 1 however it is bad practice to leave spare inputs of a gate disconnected as they are liable to pick up stray signals and cause severe logic ambiguities.

AND FROM NAND

If the NAND function is obtained by inverting AND we can get back to AND by inverting again after a NAND gate as shown in Fig. 3.5. The output is $\overline{A \cdot B}$ inverted—the double negate cancels and we are left with simply $A \cdot B$.

As an exercise try and simulate a six input AND using any of the NAND gates available on the Logic Tutor (expanders are not permitted!). We shall publish an answer next month and at the same time describe De Morgan's Theorem and show how to use this in conjunction with NAND logic to produce OR.

by M. Hughes

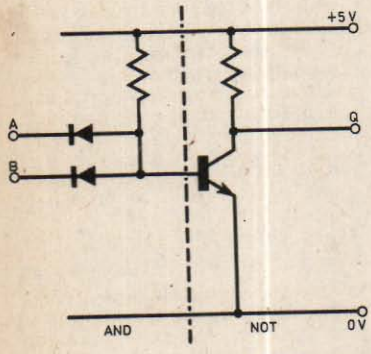


Fig. 3.1. Basic DTL NAND gate

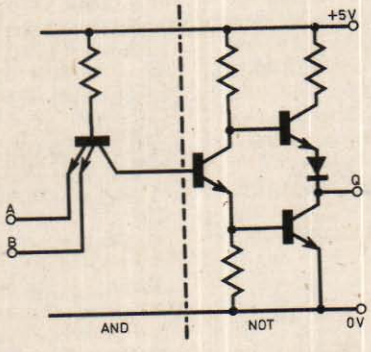


Fig. 3.2. Basic TTL NAND gate

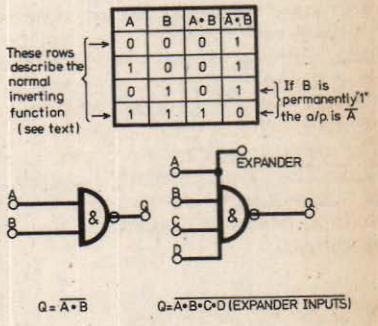


Fig. 3.3. Two forms of NAND gate together with a truth table

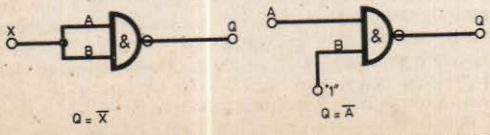


Fig. 3.4. Two ways of getting INVERT from NAND

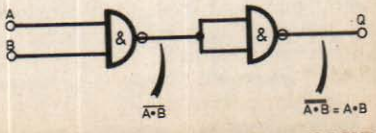


Fig. 3.5. The AND function from NAND gates



TWIN POWER SUPPLY

By G. S. SCHAJER

THE USE of integrated circuits has made it possible to make a high quality regulated supply incorporating a current limit facility using a surprisingly small number of components. Since the supplies are so simple and inexpensive, a twin power supply unit is a practical possibility, and is extremely useful especially in development work.

The current limit facility is one which is not found except in the most expensive power supply units, and it will be found to be extremely useful—sometimes in rather unexpected ways. Apart from its use as an overload protection and as a constant current source, the author has found it to be an excellent way of testing Zener diodes!

The current limit facility is nearly as accurate as the voltage regulator and, if required, the unit may be used as a constant current source.

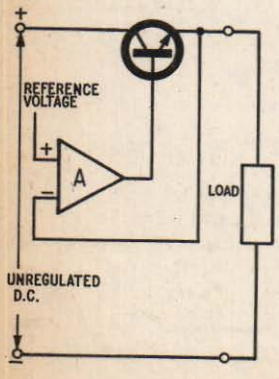


Fig. 1. The basic voltage regulator circuit

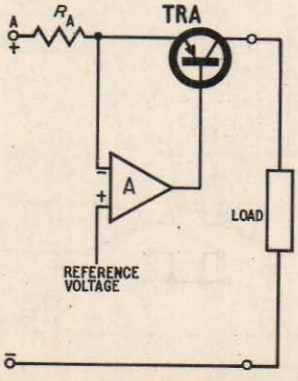


Fig. 2. The basic current limiting circuit

CIRCUIT DESCRIPTION

The integrated circuits used are the 741 operational amplifiers (op amps) which are cheap and readily available. The operational amplifier differs from the ordinary amplifier in as much as that it has two inputs, an inverting one (marked with a minus sign) and a non-inverting one (marked with a plus sign).

If there is a small difference between the voltages applied to these inputs, the output will change according to the magnitude and polarity of the difference. The op amp may therefore be used as a difference amplifier. This is the case in the circuit shown in Fig. 1, which shows a voltage follower circuit.

The output of the op amp is controlling a transistor in the supply rail of an unregulated supply. It is comparing a reference voltage and the output voltage and amplifying the difference. If the output voltage falls, the input to the transistor is increased, tending to restore the output to its original value. Similarly an increase in output will cause less current to the transistor base and thus decrease the output.

Since the op amp has a very high gain, the input need only change by a small amount for it to produce a substantial restorative action. The output thus follows the reference voltage with a high degree of accuracy.

CURRENT LIMITING

Fig. 2 shows a basic current limiting circuit. It functions in exactly the same way as the voltage regulator except that instead of the output voltage, the voltage drop across R_A (and thus the current) is compared with the reference.

The current at which the circuit limits is dependent on the reference voltage and the value of the resistor according to the relationship:

$$\text{Current limit} = \frac{\text{Reference Voltage}}{R_A}$$

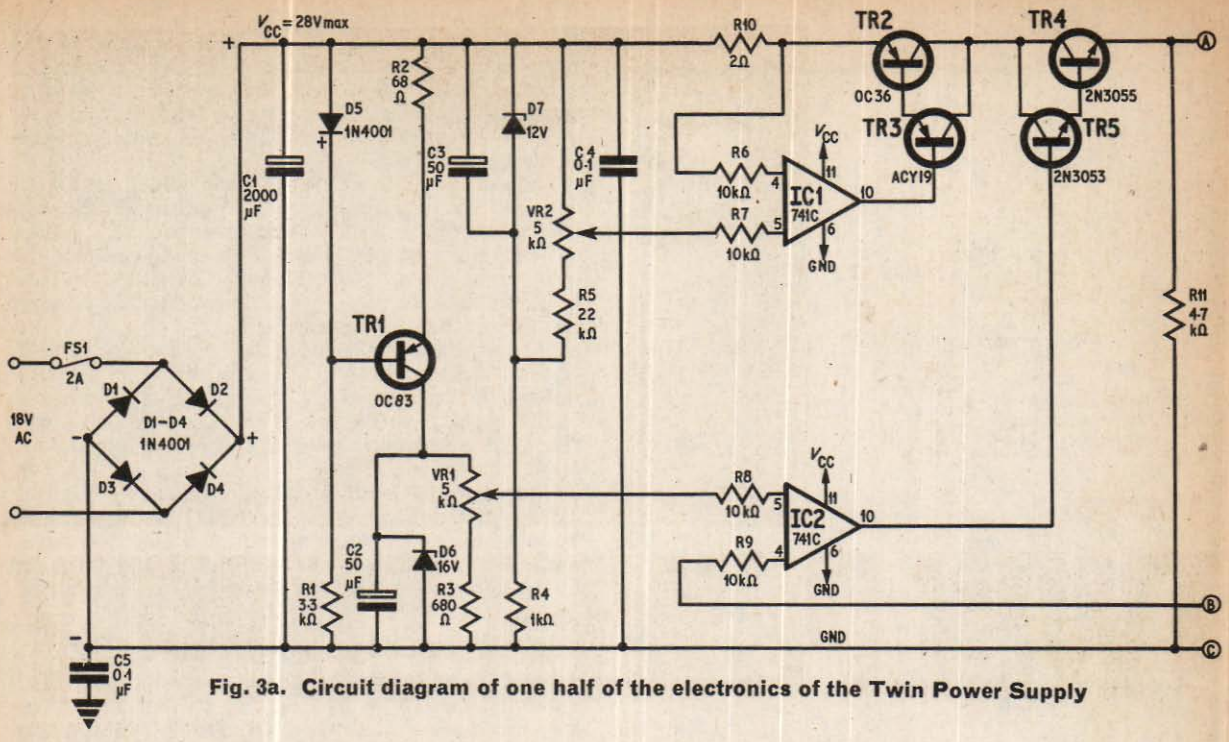


Fig. 3a. Circuit diagram of one half of the electronics of the Twin Power Supply

SPECIFICATION

Two identical supplies with complete isolation	
Fully variable output voltage	2 to 15V
Fully variable current limit	35mA to 1A
Ripple at 15V, 1A	0·4mV
Voltage regulation	0·1%

If the circuit is operated in the region of current limiting it makes a good constant current source. Its accuracy is nearly as good as that of the voltage follower. The slight deterioration is due to the thermal instability of the resistor.

FULL CIRCUIT DIAGRAM

The voltage follower and the current source may be used together as shown in the full circuit diagram, Fig. 3a. The reference voltages are made adjustable so that the output voltage and the current limit may be adjusted.

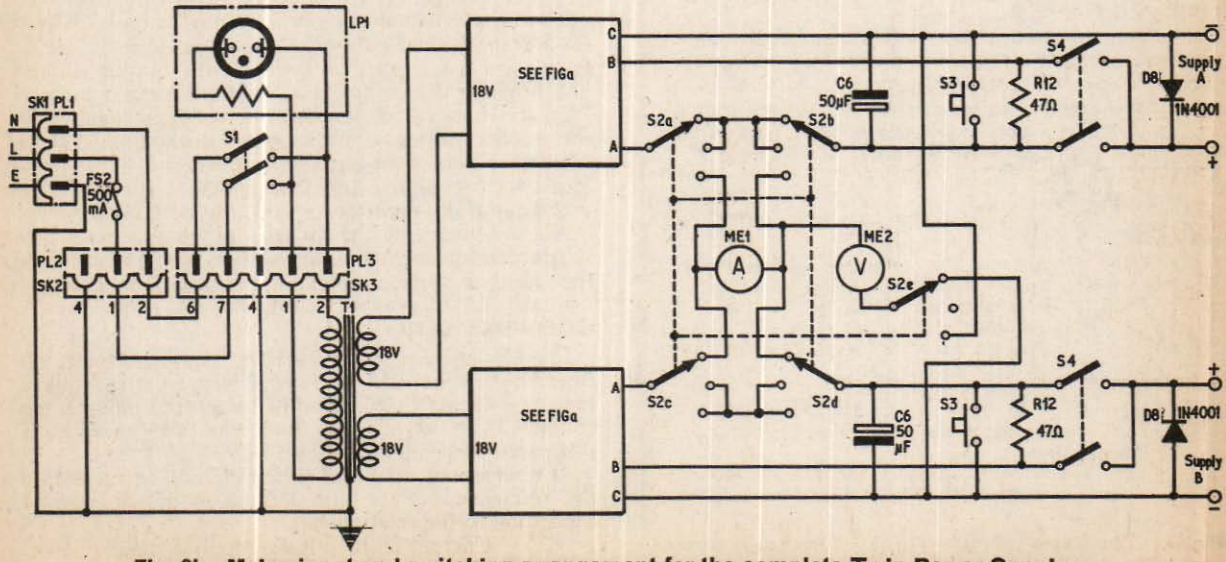


Fig. 3b. Mains input and switching arrangement for the complete Twin Power Supply

COMPONENTS . . .

Resistors

R1	3·3kΩ
R2	68Ω
R3	680Ω
R4	1kΩ
R5	22kΩ
R6–R9	10kΩ (4 off)
R10	2Ω 10W wirewound
R11	4·7kΩ
R12	47Ω

All ±10% ¼W carbon except R10

Potentiometers

VR1	5kΩ linear
VR2	5kΩ linear

Capacitors

C1	2,000μF 50V elect.
C2	50μF 25V elect.
C3	50μF 15V elect.
C4	0·1μF 250V polyester
C5	0·1μF 250V polyester
C6	50μF 25V elect.

Integrated Circuits

IC1, IC2 741C (2 off)

Transistors

TR1	OC83
TR2	OC36
TR3	ACY19
TR4	2N3055
TR5	2N3053

Diodes

D1–4	1N4001 (4 off) *or* 2A bridge rectifier
D5	1N4001
D6	16V 400mW Zener
D7	12V 400mW Zener
D8	1N4001

Switches

S1	D.P.D.T. mains toggle
S2	5 pole 3 way, make before break, rotary wafer
S3	Push to make release to break, pushbutton
S4	D.P.D.T. toggle

All the above components are for one half of the Twin Power Supply except S1 and S2, only one each of these being required

Miscellaneous

T1	Douglas MT127 0–24–30–40–48–60V 2A
ME1	1A f.s.d. 3in meter
ME2	20V f.s.d. 3in meter (or 15V if available)
PL1, SK1	Bulgin P360 mains plug and socket
PL2, SK2	B7G plug and socket
PL3, SK3	B7G plug and socket
LP1	Mains neon with integral resistor
FS1	2A fuse and holder (2 off)
FS2	500mA fuse and holder

Terminals (4 off)

0·15in matrix edge connectors and Veroboard (optional)

Case, plastic feet, paxolin panel, Veroboard, printed circuit board, power transistor insulating set (4 off)

A germanium transistor (TR1) biased by a silicon diode (D5) is used as a constant current source to feed a Zener diode (D6) thus giving a very stable reference voltage. Since the output voltage cannot be taken below 2V a resistor, R3, is connected in series with the potentiometer VR1 to make the minimum reference voltage also 2V.

The current limit reference Zener diode (D7) does not need similar stabilisation as it only operates when the load current is constant and hence the rail voltage is not changing. A maximum of 2V is required for this voltage and this is obtained from a 12V Zener (D7) and a resistor R5 in series with VR2 to produce the required voltage at the potentiometer wiper.

The outputs of the op amps do not run directly to the output transistors but via driver transistors in the super alpha pair configuration. This prevents overloading of the op amp output which can only supply 25mA. The 741 has indefinite short circuit protection which is comforting during testing.

Under extreme conditions one or other of the output transistors is dissipating nearly the full power input of the supply from the transformer, i.e. about 20W. The need for heatsinking is obvious and should be taken into account when deciding the output power required.

OUTPUT VOLTAGE MONITORING

The connection from the inverting input of IC2 is connected directly to S4 (Fig. 3b) so that the voltage drop in meters, switches and wiring does not affect the regulation of the supply. When S4 is closed the input to the op amp is connected to the output terminal and so any voltage drop across the switch due to contact resistance will similarly not affect the regulation.

When the switch is off the supply is disconnected from the output but the high impedance op amp input is still connected to the supply by R12. This enables the supply to operate so that the voltage and current limit may be set when S4 is off. The current limit set switch S3 is independent of S4.

A reverse biased diode D8 is connected across the output terminals to protect the supply from back e.m.f. when disconnecting a reactive load.

Resistor R11 is included so that the supply has a load in the absence of any external load. C6 protects against high frequency oscillation and C5 reduces mains borne interference.

THERMAL EFFECTS

The 2Ω resistor in the current limiting circuit should be a high wattage type to prevent excessive heating which causes resistance variations. A 10W type drifts by about five per cent which is reasonable; a higher wattage should be used for greater stability.

On the prototype the rail voltage off load was 28V. Under no circumstances should this voltage be exceeded by using a higher voltage transformer as this will damage the integrated circuit. On a 1A load the rail voltage drops to 21V.

Meters are provided to measure the voltage and current output of the two supplies. It is possible to switch them from one supply to the other, but without breaking the continuity of either supply, and yet maintaining the isolation between the supplies.

The circuit shows the switching arrangement required. A five pole, three way, make before break switch is used. The centre position is "off". A make-before-break switch is essential, otherwise there will be a break in continuity during switching.

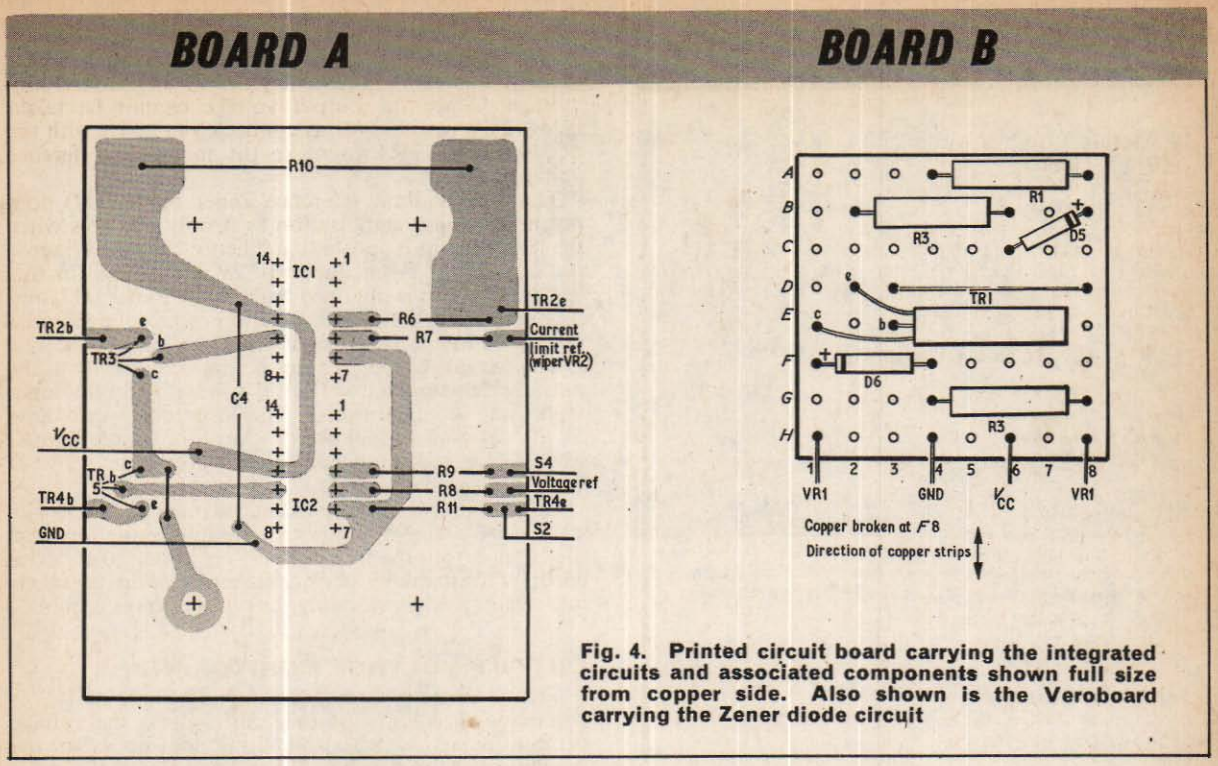


Fig. 4. Printed circuit board carrying the integrated circuits and associated components shown full size from copper side. Also shown is the Veroboard carrying the Zener diode circuit

CONSTRUCTION

The method of construction is a matter of personal choice, dictated to some extent by the materials available. Some thought should be put into planning the layout of the components and a little extra care when making up the unit is well worth the effort.

Some details are given of the construction of the prototype, together with some of the points to remember when building the supply. They are given merely as a guide and need not be adhered to rigidly.

The integrated circuits and associated components are mounted on a printed circuit board which is shown in Fig. 4. The two rows of holes for the i.c.s are easily drilled by clamping a small piece of Veroboard (0·1in matrix) to the printed circuit board and using its holes as a template. Holders for the i.c.s may be used if desired.


The Zener diodes and associated components are mounted on the front panel, attached to the tags of the potentiometers. The stabilisation circuitry for the Zener diode D6 is made on a small piece of Veroboard (0·15in matrix) which is mounted on the back of VR1 by means of its connecting wires. If the potentiometer has a metal case steps should be taken to prevent the Veroboard shorting.

The layout of the front panel is shown in the photograph (Fig. 8). This was made from a piece of white Perspex $\frac{3}{16}$in thick. Detailed drilling details are not given as some of the components will vary according to availability. The meters shown are not generally available but SEW series 65 meters are a suitable type to use.

It is a good idea to connect the spindles of potentiometers VR1 and VR2 to the negative rails of the supplies as this reduces hum pickup. Use thick wire for the current carrying sections of the supply to reduce heating effects.

TRANSFORMER

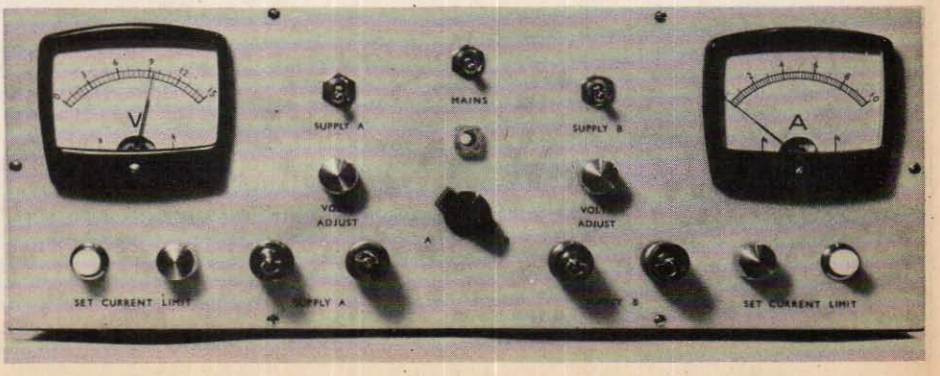The power is supplied by a single transformer with two isolated 18V, 2A secondary windings. This is not



Photograph of the completed Twin Power Supply

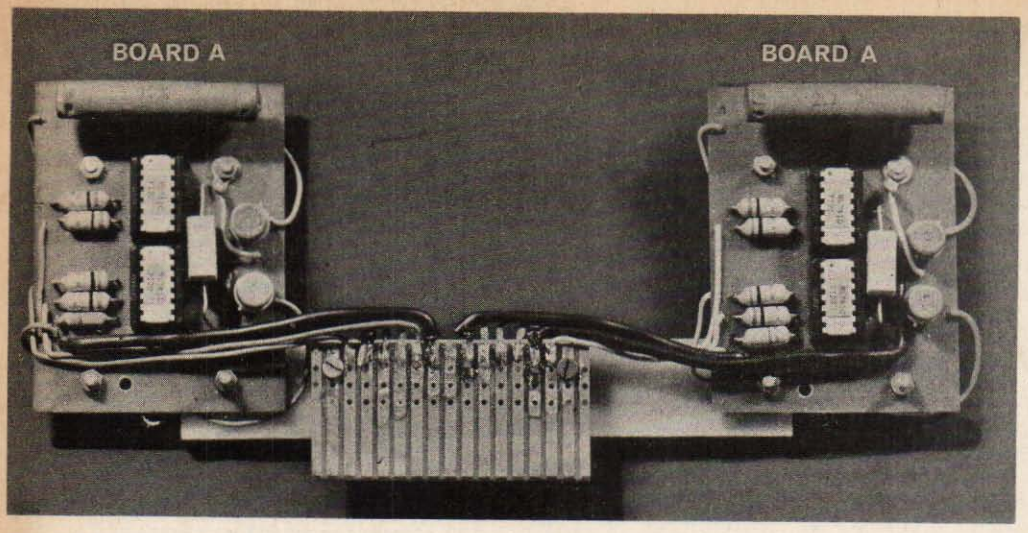


Fig. 5. Layout of the components on the back panel. Details of board A are given in Fig. 4. TR2 and TR4 are mounted under the boards on the panel

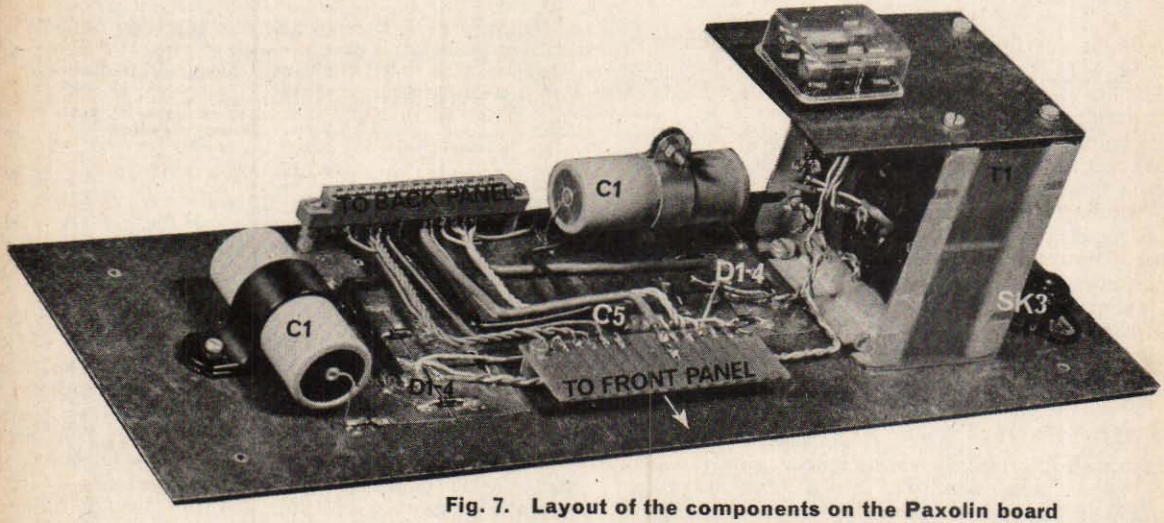


Fig. 7. Layout of the components on the Paxolin board

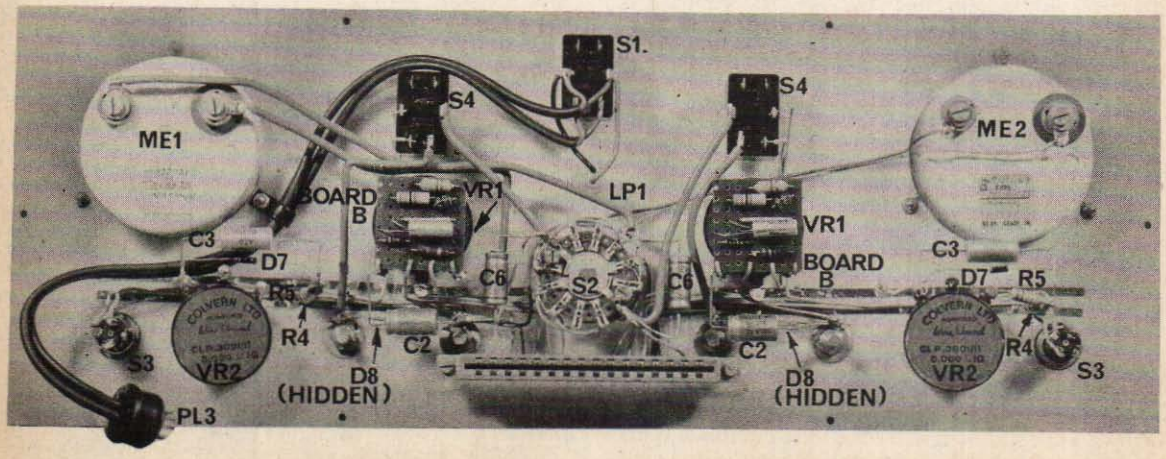


Fig. 8. Layout of the components on the front panel. Board B is shown in Fig. 4

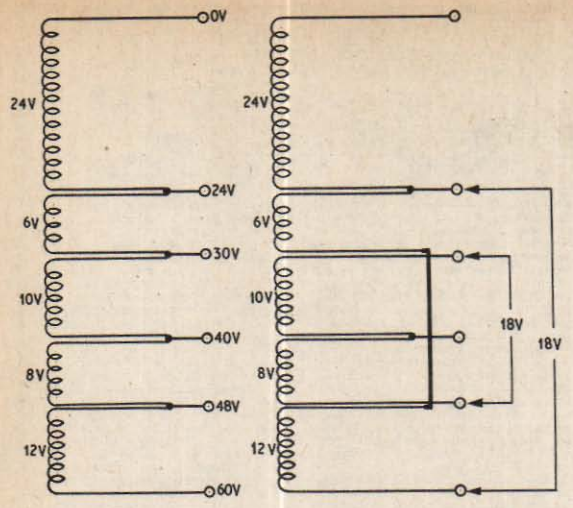


Fig. 6. Diagram showing modification to the Douglas MT127 transformer

available in this form but a simple modification to a Douglas MT127 will give the required result. The MT127 has taps at 0–24–30–40–48–60 volts and these are connected to tags.

The connections to the tags marked 30V and 48V should be carefully unsoldered and the end of the 30V winding should be connected to the beginning of the 48V winding. This is shown diagrammatically in Fig. 6.

One 18V supply is available at the tags of the 30V and 48V and the other at the tags of 24V and 60V. Check that the correct windings are being used with a continuity meter and make sure that there is complete isolation between the two windings. Alternatively two 18V, 2A transformers may be used.

PAXOLIN PANEL

The transformer, rectifiers and capacitors are mounted on a Paxolin panel which fits into the bottom of the case, Fig. 7. Discrete diodes soldered to squares of stick-down copper sheet form the bridge rectifiers but it is probably more convenient to use a ready-made 2A bridge.

The back panel is a piece of 14 s.w.g. aluminium painted matt black and this acts as a heatsink for the four power transistors, Fig. 5. The p.c.b.s carrying the i.c.s are also mounted on this panel. Mica washers to insulate the transistors as well as plastic bushes on the bolts should be used to ensure that the transistors do not make contact with the panel.

On the prototype, both the front and back panels were made removable by using offcuts of Veroboard and edge connectors to form plugs and sockets. The mains input is kept completely separate by using B7G plugs and sockets to make the connections between the front and back panels of the transformer.

TESTING THE SUPPLY

Should the supply not function check the reference voltages as any fault here will be reflected in the output. If they are alright then the fault must lie in the op amps or associated components. ★

TRANSFORMERS

MAINS ISOLATING SERIES
Primary 200-250 Volts Secondary 240 Volts Centre Tapped (120V) and Earth Shielded
ALSO AVAILABLE WITH 115/120V SEC. WINDING

Ref. No.	VA (Watts)	Weight lb	Weight oz	Size cm.	P & P £	P & P p
07	20	1	11	7·0 × 6·0 × 6·5	1·77	30
100	60	3	8	8·9 × 8·0 × 7·7	2·62	36
61	100	5	12	10·2 × 8·9 × 8·3	2·88	52
30	200	9	8	12·0 × 10·3 × 10·0	4·83	52
62	250	12	4	9·5 × 12·7 × 11·4	6·38	67
55	350	15	0	14·0 × 10·8 × 12·4	8·55	82
63	500	27	0	17·1 × 11·4 × 15·9	12·32	*
92	1000	40	0	17·8 × 17·1 × 21·6	22·70	*
128	2000	63	0	24·1 × 21·6 × 15·2	37·50	*

PLEASE NOTE NEW ADDRESS AS BELOW

AUTO SERIES (NOT ISOLATED)

Ref. No.	VA (Watts)	Weight lb	Weight oz	Size cm.	Auto Taps	P & P £	P & P p
113	20		11	7·3 × 4·3 × 4·4	0-115-210-240	0·93	22
64	75	1	14	7·0 × 6·4 × 6·0	0-115-210-240	1·82	30
4	150	3	0	8·9 × 6·4 × 7·6	0-115-200-220-240	2·20	36
66	300	6	0	10·2 × 10·2 × 9·5	" "	4·28	52
67	500	12	8	14·0 × 10·2 × 11·4	" "	6·35	67
84	1000	16	0	11·4 × 14·0 × 14·0	" "	11·54	82
93	1500	28	9	13·5 × 14·9 × 16·5	" "	16·72	*
95	2000	40	0	17·8 × 16·5 × 21·6	" "	21·82	*
73	3000	45	8	17·4 × 18·1 × 21·3	" "	29·70	*

TOTALLY ENCLOSED 115V AUTO TRANSFORMERS
115V 500 Watt totally enclosed auto transformer, complete with mains lead and two 115V outlet sockets, £8·63. P & P 67p.
Also available a 20 Watt version. £1·84. P & P 22p.

LOW VOLTAGE SERIES (ISOLATED)
PRIMARY 200-250 VOLTS 12 AND/OR 24 VOLT RANGE

Ref. No.	Amps. 12V	Amps. 24V	Weight lb	Weight oz	Size cm.	Secondary Windings	P & P £	P & P p
111	0·5	0·25		12	7·6 × 5·7 × 4·4	0-12V at 0·25A × 2	0·93	22
213	1·0	0·5	1	0	8·3 × 5·1 × 5·1	0-12V at 0·5A × 2	1·11	22
71	2	1	1	0	7·0 × 6·4 × 5·7	0-12V at 1A × 2	1·46	22
18	4	2	2	4	8·3 × 7·0 × 7·0	0-12V at 2A × 2	2·04	36
70	6	3	3	12	10·2 × 7·6 × 8·6	0-12V at 3A × 2	2·46	42
108	8	4	5	4	10·0 × 8·3 × 8·2	0-12V at 4A × 2	2·73	52
72	10	5	6	3	7·9 × 10·8 × 10·2	0-12V at 5A × 2	3·23	52
17	16	8	7	8	12·1 × 9·5 × 10·2	0-12V at 8A × 2	4·99	52
115	20	10	11	13	12·1 × 11·4 × 10·2	0-12V at 10A × 2	6·35	67
187	30	15	16	12	13·3 × 12·1 × 12·1	0-12V at 15A × 2	11·73	82
226	60	30	34	0	17·0 × 14·5 × 12·5	0-12V at 30A × 2	21·57	*

30 VOLT RANGE

Ref. No.	Amps.	Weight lb	Weight oz	Size cm.	Secondary Taps	P & P £	P & P p
112	0·5	1	4	8·3 × 3·7 × 4·9	0-12-15-20-24-30V	1·11	22
79	1·0	2	0	7·0 × 6·4 × 6·0	" "	1·48	36
3	2·0	3	2	8·9 × 7·0 × 7·6	" "	2·21	36
20	3·0	4	6	10·2 × 8·9 × 8·6	" "	2·72	42
21	4·0	6	0	10·2 × 10·0 × 8·6	" "	3·23	52
51	5·0	6	8	12·1 × 10·0 × 8·6	" "	4·02	52
117	6·0	7	8	12·1 × 10·0 × 10·2	" "	4·80	52
88	8·0	10	0	14·0 × 11·7 × 10·0	" "	6·20	67
89	10·0	12	2	14·0 × 10·2 × 11·4	" "	7·85	67

50 VOLT RANGE

Ref. No.	Amps.	Weight lb	Weight oz	Size cm.	Secondary Taps	P & P £	P & P p
102	0·5	1	11	7·0 × 7·0 × 5·7	0-19-25-33-40-50V	1·46	30
103	1·0	2	10	8·3 × 7·3 × 7·0	" "	2·13	36
104	2·0	5	0	10·2 × 8·9 × 8·6	" "	2·96	42
105	3·0	6	0	10·2 × 10·2 × 8·3	" "	4·01	52
106	4·0	9	4	12·1 × 11·4 × 10·2	" "	5·31	52
107	6·0	12	4	12·1 × 11·1 × 13·3	" "	7·85	67
118	8·0	18	9	13·3 × 13·3 × 12·1	" "	10·25	97
119	10·0	19	12	16·5 × 11·4 × 15·9	" "	12·85	97

60 VOLT RANGE

Ref. No.	Amps.	Weight lb	Weight oz	Size cm.	Secondary Taps	P & P £	P & P p
124	0·5	2	4	8·3 × 9·5 × 6·7	0-24-30-40-48-60V	1·48	36
126	1·0	3	0	8·9 × 7·6 × 7·6	" "	2·06	36
127	2·0	5	6	10·2 × 8·9 × 8·6	" "	3·23	42
125	3·0	8	8	11·9 × 9·5 × 10·0	" "	4·92	52
123	4·0	10	6	11·4 × 9·5 × 11·4	" "	6·35	67
120	6·0	16	12	13·3 × 12·1 × 12·1	" "	9·20	82
122	10·0	23	2	16·5 × 12·7 × 16·5	" "	15·23	*

LEAD ACID BATTERY CHARGER TYPES

Ref. No.	Amps.	Weight lb	Weight oz	Size cm.		P & P £	P & P p
45	1·5	1	9	7·0 × 6·0 × 6·0	Please note, these units do not include rectifiers	1·47	30
5	4·0	3	11	10·2 × 7·0 × 8·3		2·23	42
86	6·0	5	12	10·2 × 8·9 × 8·3		3·37	52
146	8·0	6	4	8·9 × 10·2 × 10·2		3·84	52
50	12·5	11	14	13·3 × 10·8 × 12·1		5·72	67

All ratings are continuous. Standard construction: open with solder tags and wax impregnation. Enclosed styles to order.

FULL SPEC. TRANSISTORS (E.G.)
BC107/108/109 10p each. | 2N 3055 60p each + mica and bushes | AD161/162 60p pair + mica and bushes

Carriage via B.R.S.

★ Quantity prices on application

ELECTROSIL RESISTORS • AVOMETERS

PLEASE ADD 10% FOR V.A.T. INC. P. & P.

BARRIE electronics
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/8
NEAREST TUBE STATIONS: ALDGATE & ALDGATE EAST

FAULT LOCATION



KONTAKT "Cold Spray 75"

For rapid and effective fault location

Non-toxic, non-inflammable, Cold Spray 75 is a chemically inert coolant capable of producing temperatures of down to —42 centrigrade. It can also be used to prevent heat damage during soldering processes, for the rapid freezing of small articles for biological and technical purposes and the prompt location of hairline cracks and other faults in temperature dependent components.

Other Kontakt products:

Kontakt 60 and Kontakt 61 for relay contact cleaning; Plastic Spray 70, transparent protective lacquer; Insulating Spray 72; Kontakt WL, Spray Wash; Antistatic Spray 100, Antistatic agent for plastics; Politur 80, Polish and cleaner; Fluid 101, Dehydrating Fluid.

Details from U.K. distributors:

Special Products Distributors Ltd.
81 Piccadilly, London W1V 0HL. Tel. 01-629 9556

PRACTICAL ELECTRONICS "SCORPIO" ELECTRONIC IGNITION SYSTEM



This Capacitor-Discharge Electronic Ignition system was described in the November and December issues of Practical Electronics. It is suitable for incorporating in any 12V ignition system in cars, boats, go-karts, etc., of either pos. or neg. earth and up to six cylinders. The original coil, plugs, points and contact-breaker capacitor fitted in the vehicle are used. No extra or special components are required.

Helps to promote easier starting (even under sub-zero conditions), improved acceleration, better high-speed performance, quicker engine warm-up and improved fuel economy. Eliminates excessive contact-breaker point burning and the need to adjust point and spark-plug gaps with precision.

Construction of the unit can easily be completed in an evening and installation should take no longer than half an hour. A complete complement of components is supplied with each kit together with ready-drilled roller-tinned professional quality fibre-glass printed-circuit board, custom-wound transformer and fully-machined die-cast case. All components are available separately. Case size 7¼in × 4½in × 2in. approx.

Complete assembly and wiring manual **25p**, refundable on purchase of kit. Price: **£10·50** plus 50p P. & P.

PSYCHODELIC LIGHTING UNIT Mk. 3



This unit represents a natural progression from our phenomenally successful Mk. 1 and 2 Units. As before the drive voltage is derived directly from the amplifier output or across the speakers. The unit converts the audio frequency signals into a three-coloured light display; the colour depending on the frequency of the signal and the intensity on the loudness of the audio source.

The unit is constructed on professional fibre-glass printed-circuit board material and uses latest full-wave triac circuitry. There is a master-level control, together with independent sensitivity controls for each channel. The original minimum ambient light level controls have been redesigned permitting their use as faders; allowing dimming from max. to zero at the turn of a knob. R.F.I. suppression is now incorporated as standard as well as provision for D.J. "Pulse-Flash" controls. The choice of two inputs enables operation from both high and low power amplifiers. Max. power 1·5kW per channel at 240V a.c.

Complete assembly built and tested. Size 9in × 7in × 3in. Price **£25** carr. paid.


PLEASE NOTE ALL THE ABOVE PRICES ARE SUBJECT TO V.A.T. ADJUSTMENT

DABAR ELECTRONIC PRODUCTS
98a Lichfield Street, Walsall, Staffs. WS1 1UZ
TELEPHONE: WALSALL 34365 TELEGRAMS: DABELEC Walsall Staffs.

We've written this book on kits

You can get a copy free

Below are just a few of the large selection of kits fully illustrated in the NEW HEATHKIT CATALOGUE – kits for every interest, every budget, stereo hi-fi systems and accessories, intercoms, transistor radios, tool kits, electronic calculators, automotive ignition analysers and checkers, electronic testing and measuring equipment, amateur and short-wave radio gear, metal locators – even a powerful battery charger.

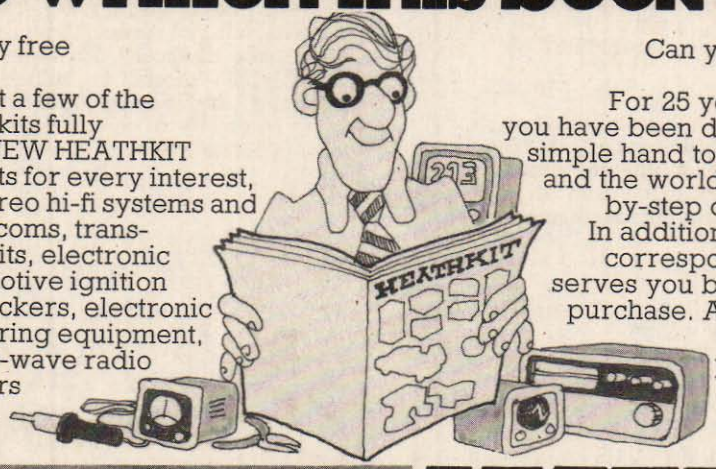

Can you build a Heathkit?

For 25 years people just like you have been doing it – using a few simple hand tools, a soldering iron and the world-famous Heath step-by-step construction manual. In addition, a factory technical correspondence department serves you both before and after purchase. And, finally, building your Heathkit is fun, pure and simple . . .

The coupon gets you started.



Please send me the FREE Heathkit catalogue

Name _____


Address _____

_____

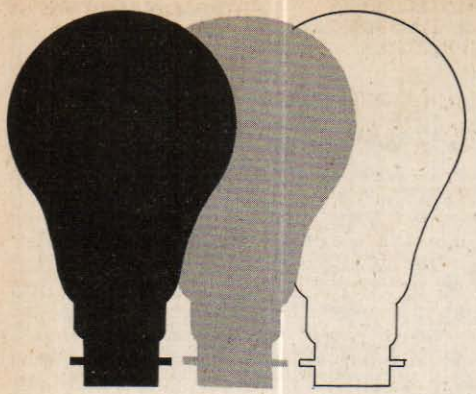_____

HEATH
Schlumberger

Dept. PE/07/73
Heath (Gloucester) Limited
Bristol Road, Gloucester GL2 6EE



LIGHTING CONTROL UNIT

By G. A. Davies

ANYONE who has helped to organise a disco-theque group performance or even put lights on a Christmas tree, must have felt the need for a simple flashing light controller. Many circuits, perhaps using a multivibrator, exist. But these are severely limited in their flashing rates if on and off periods are kept approximately equal, and if strobe-like effects and very slow changes are required from the same unit range switching will be needed, leading to expensive and complex wiring and tedious operation.

The circuit described here uses a similar method but a quite different principle to produce a variety of effects all available from settings of a single control. In place of continual OFF/ON switching, gradual changes enhance the effects, which range from a fast strobe to flashes lasting up to and over one minute.

COSTS

The cost of the unit if all parts including case are purchased new will be a little over £2·70. By making the case and shopping around this may be reduced. An experimental set-up may be made from common items in the spares box with the possible exception of the thyristor.

GENERAL

The circuit of Fig. 1 shows a multivibrator, TR1/TR2 actuating a driver circuit TR3 which in turn actuates a thyristor CSR1.

The components of the multivibrator are selected to give a repetition rate of about 50Hz with TR1 in the ON state for about 1ms and TR2 ON for between 10 and 25ms dependent on the setting of VR1.

THE DRIVER CIRCUIT

Output pulses from the multivibrator are fed to the base of TR3 *via* R5 which is large enough to prevent the following circuit from interfering with the multivibrator. Each pulse turns TR3 ON, allowing an amplified pulse of current through the collector into the gate of the thyristor. R6 limits this pulse to about 30mA which should be sufficient to operate most thyristors. If a low current thyristor is to be used some saving in battery drain can be made by increasing the value of R6 to 390Ω.

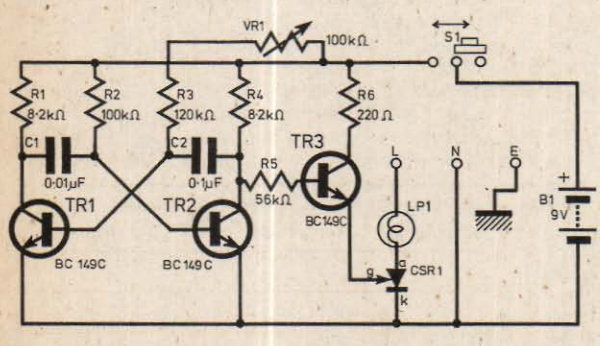


Fig. 1. The circuit diagram of the light controller. TR1/TR2 form a multivibrator driving CSR1 through driver TR3


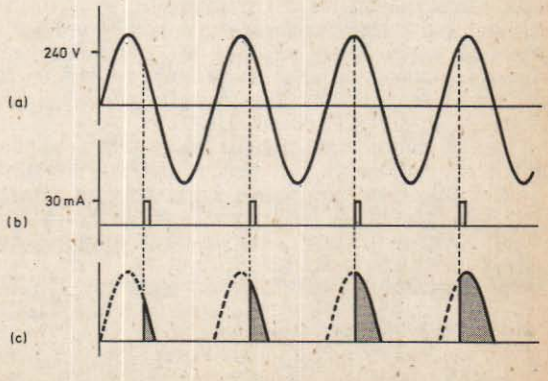


Fig. 2. Graphic representation of the relationship between mains cycles, control pulses and load current, at a given multivibrator frequency

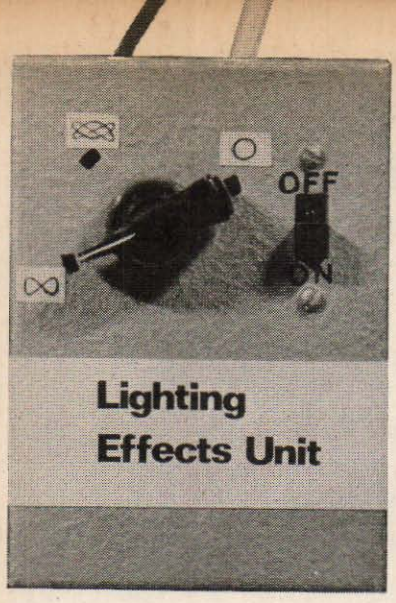

reached when the pulse has finished before the cycle starts. The power then falls to zero until the next pulse arrives at the end of the cycle and power increases slowly again.

If a 100W bulb is used as the load the light will be seen to change intensity as in Fig. 3 (f), the rate of change depending on the frequency difference between the mains and multivibrator pulses. The reversed version, Fig. 3 (g), is obtained by setting the pulse frequency lower than 50Hz.

With large frequency differences a strobe effect is obtained and with careful adjustments an almost constant light output can be set. It must be borne in mind that the maximum light output is only half that given by the bulb connected straight to the mains.

The other effects shown in Fig. 3 can be obtained with the controller remembering that thermal inertia, i.e. the time taken for the lamp filament to heat up and cool down, will slow down some of the faster changes.

CONSTRUCTION

To the inexperienced constructor it is impossible to overstress the need for great care over safety. The whole circuit is connected to the mains, and although

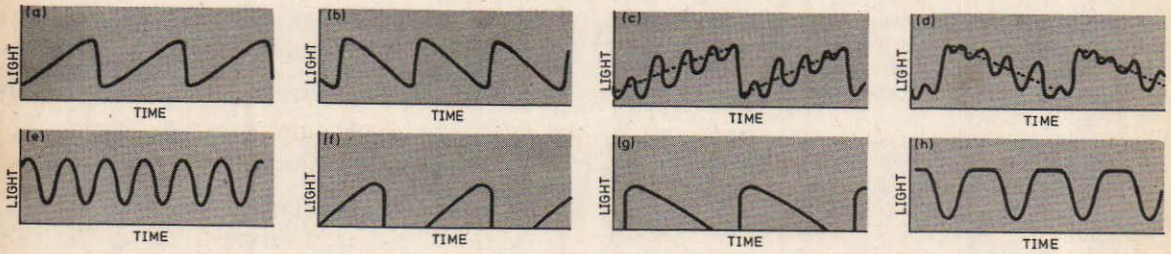


Fig. 3. Variations in light output obtainable with the circuit of Fig. 1

THE THYRISTOR

This semiconductor device can be considered as a combination of a rectifier and a latching relay. It will not under any circumstances (other than breakdown) pass a current from cathode to anode, and also it will not pass a current from anode to cathode unless a sufficiently large current is supplied to the gate. Once triggered in this way, however, the anode current will not stop, even after the gate triggering current has stopped, until the anode voltage is reduced to zero, or changes sign to negative if a.c. is applied.

In this particular application a.c. mains voltage is connected to the anode through the controlled load. When the mains is negative no current can pass due to rectifying action. Thus any current pulses arriving at the gate from TR3 are ignored.

When the mains is positive the thyristor can conduct, but will not do so until a trigger pulse has turned it on.

Fig. 2 (a) shows the mains input voltage. For a given frequency of the multivibrator (b) is the train of current pulses in the gate of the thyristor. All negative half cycles of the a.c. are rectified out and positive half cycles are let through only after an input pulse, so that the voltage supplied to the load looks like Fig. 3 (c).

If the multivibrator is set as shown at a slightly higher frequency than the mains 50Hz, that part of the half cycle allowed through will change. As the drive pulse comes earlier in each cycle, the power in the load slowly rises to a maximum of about half the rated power (all negative half cycles are lost) until a point is

the live is isolated through the lamp and is thus proof against short circuits, great care must be taken over insulation. The isolation of the case from the thyristor poses the greatest problem here and the solution depends upon the component chosen.


The prototype was housed in an aluminium box measuring about 4in × 2¾in × 1½in deep and fitted with an overlapping lid held by a self-tapping screw at either end. The switch and the potentiometer are fixed to the lid and the remaining parts are assembled in the box. Firstly the top and bottom should be drilled to accept the components.

A small aluminium clip shown in Fig. 4 is needed to secure the battery with small blocks of polystyrene stuck to the lid and sides to hold it firmly in place. The clip can be fixed with Araldite.

The circuit board and terminal block are secured by ¼in 6 B.A. tapped pillars screwed or Araldited (preferably both, since the screws will have to be very short) to the case. Countersunk screws are used in the prototype, the heads being filled in with Araldite and painted over but this is of course a matter of individual choice.

COMPONENT BOARD

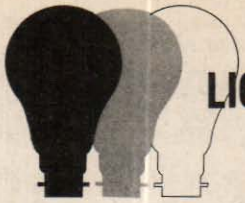Details of this are given in Fig. 4. The six 6 B.A. clearance holes should be drilled carefully first and then the components pushed through and soldered, the transistors being soldered last to avoid overheating.



LIGHTING CONTROL UNIT

COMPONENTS . . .

Resistors

R1	8·2kΩ	R3	120kΩ	R5	56kΩ
R2	100kΩ	R4	8·2kΩ	R6	220Ω

All ¼W 10% carbon

Potentiometer

VR1 100kΩ carbon linear

Capacitors

C1 0·01μF 250V poly.
C2 0·1μF 250V poly.

Thyristor

CSR1 BO226 (see text)

Transistors

TR1, 2, 3 BC149C (or BC169C, BC108C, BC109C)

Miscellaneous

S1 d.p.d.t. slider switch or on/off toggle
B1 9V PP3 or equivalent
2in × 3¾in s.r.b.p. 0·1in matrix, 2A terminal block (5 sections required), 6 ¼in 6BA tapped pillars, Case see text, 6BA screws, 18swg aluminium for battery clip and heatsink, grommets, wire, solder, sleeving.

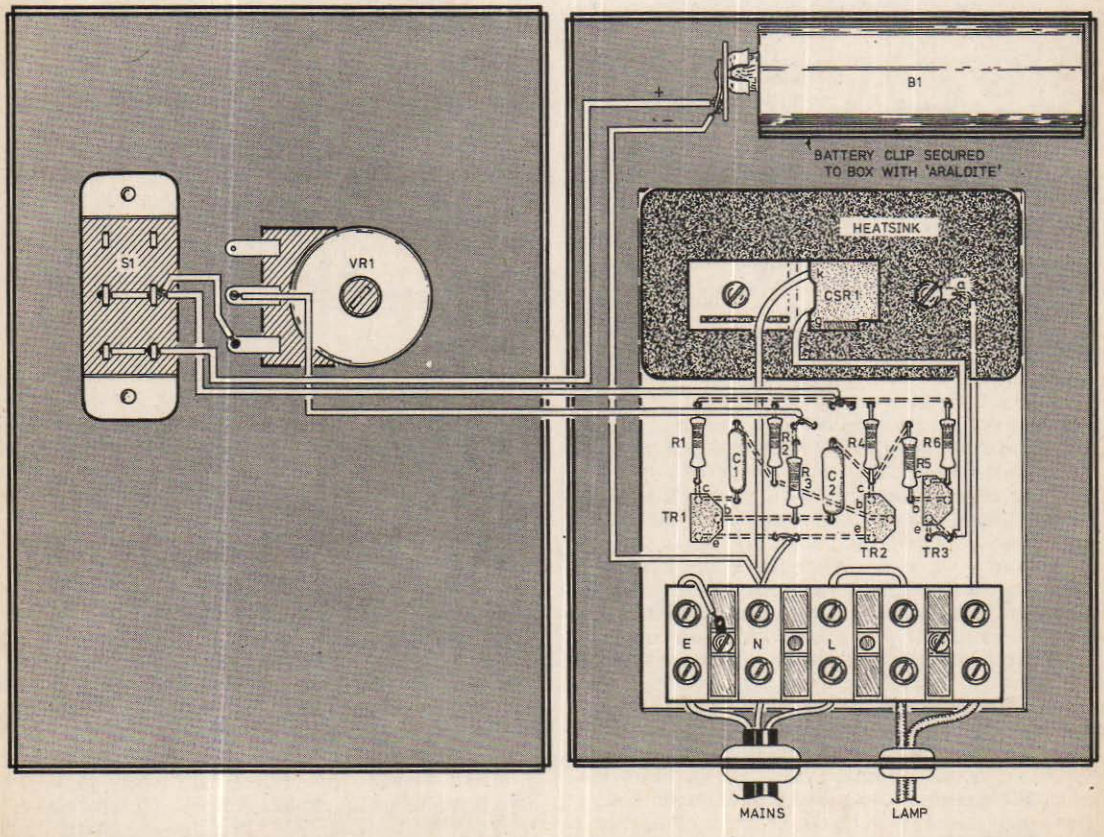


Fig. 4. General layout of the controller showing main wiring board and component positioning. NOTE: Ensure that the heatsink is well isolated from case

Four loops of wire are made on the component side so that connections can be made. Next screw two ¼in pillars to the inside holes; the board can then be bolted down onto the pillars.

The heatsink in Fig. 4 is mounted on the board using two further pillars, the thyristor being fixed down under one screw (a smear of silicone grease will be helpful here under the tab to improve heat transfer). The lead from the terminal block can be soldered to, or clamped by the other screw/pillar to act as the anode connection. Make certain the heatsink mounting is insulated from the case.

The wiring can be completed with p.v.c. insulated stranded wire, colours being chosen to suit. Sleeving the thyristor leads is advisable or tape may be used.

COMPONENTS

The components specified in the list are all quite easily obtainable. The transistors can be any of the listed types, BC 149C being most suited to the mode of construction used and also the cheapest.

If surplus transistors are tried TR3 should be selected for low leakage and high gain. The C suffix on the listed types ensures a gain of over 400.

The thyristor will depend on the application; for mains it must be rated at 400V peak forward and reverse voltage, the current will depend upon the power of the lamps used. At 240V a 3A thyristor with a good heatsink will take a total load of 1000W and give 500W of light. A 0·8A version in a TO5 or similar case will overcome the insulation problem and make the unit possibly smaller but will not take more than 250 to 275W load and give 100 to 150 watts of light.

The 2in × 1in panel used cannot be considered a good heatsink and also it is inside a sealed box. In addition large powered bulbs also complicate things because their high thermal inertia causes large surges on switching ON. The unit should be able to take a 500W lamp at all control settings to give 250W of light. With lower powered lamps in parallel it should be possible to go up to 700 to 800W. However, due to the cost of such a setup this has not been tried. A few hundred watts will be found adequate for most purposes but care should be taken to ensure there is no overheating with the components specified.

TESTING

When the wiring is complete and checked, connect the battery in circuit and, using a meter set to a current range, put this across the switch. A current of about 3mA should register, switch the range down if necessary to read this. Rotate VR1 and the current should change slightly.

Following this or, alternatively if no meter is available, connect the mains lead to a plug fitted with a 3A or 5A fuse and the output lead to a lamp of 40 to 100W power. (In the prototype a cable socket was connected so that lamps could be plugged in and removed freely.) Switch the mains on. If nothing happens all is well; now switch on the unit with S1. The bulb should now light and flash in a pattern depending upon the setting of VR1. Explore the range of the potentiometer and see that it is similar to that indicated in Fig. 4. If this is not so, adjustment of R3 may be necessary.

LAMP HOUSING

For lighting effects the lamps will have to be fitted in some way to achieve the desired effect. Coloured pearl bulbs or bulbs fitted in boxes with coloured filters can be used but these give very directed illumination and an improvement is made with more diffuse lighting. Frosted screens can be tried but an excellent result is given by a box with lamps, reflectors and filters placed at the bottom of a wall so that the light is projected up onto the wall. Car headlamp reflectors can also be adapted to produce a focused beam for special effects.

FAULT FINDING

Three conditions will indicate faults in the unit which might occur.

Firstly the lamp may not light. Check the operation of the multivibrator with a high impedance earpiece or an oscilloscope after first unplugging the unit from the mains and putting S1 to ON. With one side of the earpiece connected to battery negative look for a signal at 40 to 100Hz at TR2 collector. If this is present check for the same at the gate of CSR1. If the signal is also present here the thyristor or the mains wiring is at fault. Look for breaks in the relevant part of the circuit or for faulty components.

Secondly if the lamp lights continually at half brilliance then check for a signal at TR2 collector with a voltmeter. If this reads about 1V then check TR3 and its wiring. If it is 2V or more the multivibrator is the cause of the trouble. Check for correct positioning of C1 and C2.

Finally if the lamp lights at its normal full brilliance this indicates a short circuit in the unit. If none can be found then the thyristor may be shorted. Check that the fuse and bulb are not also shorted before replacing.

THE FINISH

Finishing the unit is left entirely to the constructor, the prototype was painted with a silver "hammer" paint and the words "LIGHTING EFFECTS UNIT" painted in black across a white stripe. The "critical settings" of the control were marked approximately with Lissajous figures corresponding to the ratio of the mains and multivibrator frequencies. Any method of calibration will suffice and as long as you can understand it that is all that really matters.

SUPPRESSION

If the unit interferes with radios or TVs on high power operation a suppressor may have to be fitted. This will consist of inductors in series and/or capacitors in parallel with the power lines. This was not included in the prototype because of space consideration and since no interference has arisen anyway.

USE

Every constructor will rapidly become accustomed to the effects produced by the unit and will soon know how to use its effects to the greatest advantage. Positioning and colouring will follow logically to give the best results.

A word of warning, however. The strobe effects produced should not be used as dominant lighting in an otherwise darkened room as it can have a bad effect on the subconscious mind after prolonged exposure. Headaches can also be caused, probably due to the sensation of rapid blinking. If strobes are used make sure that the other lighting is at least equal in strength to the strobed light.


Finally, when fault finding as described earlier make certain the equipment is not connected to the mains. Also earth the case to mains earth. ★

look! electronics really mastered

... practical
... visual
... exciting!

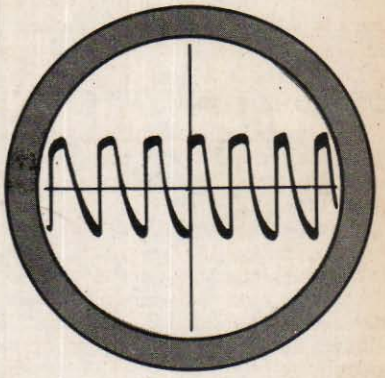no previous knowledge
no unnecessary theory
no "maths"








RAPY

BUILD, SEE AND LEARN
step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

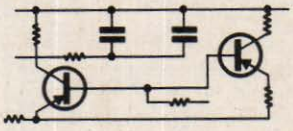2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW for BROCHURE

or write if you prefer not to cut page

To BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, P.O. BOX 156, JERSEY. Please send your free brochure, without obligation, to: *we do not employ representatives*

NAME

ADDRESS


BLOCK CAPS

PLEASE EL73

special free gift also to all our students

PRICES NOW INCLUDE VAT


SUPERSOUND 13 HI-FI MONO AMPLIFIER

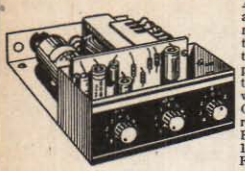

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13W r.m.s. into 8 ohm. Frequency response 12Hz—30KHz ± 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8–15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3in high × 6in wide × 7¼in deep. A.C. 200/250V.

PRICE £11·60 P. & P. 25p.

DE LUXE STEREO AMPLIFIER

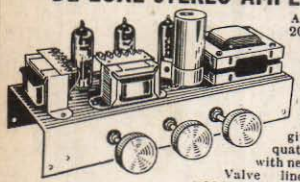

A.c. mains 200–240 volts. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up:—2 × ECL86 Triode Pentodes. 1 × EZ80 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300m/v for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11in. w × 4in. x. Overall height including valves 5in. Ready built and tested to a high standard. **Price £9·90.** P. & P. 45p.

NEW! POWER SUPPLY UNIT

200/240V A.C. input. Four switched fully smoothed D.C. outputs giving 6V and 7½V and 9V and 12V at 1 amp continuous (1½ amp intermittent). Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case, overall size 6" × 3½" × 2½". Suitable for Transistor Radios, Tape Recorders, Amplifiers, etc., etc. Ready built and tested.

PRICE £5 P. & P. 35p.

BLACK ANODISED 16g. ALUMINIUM HEAT SINKS. For TO3, complete with mica's and bushes. Size 2¼in × 3in approx. **28p** pair. P. & P. 5p.

HIGH GRADE COPPER LAMINATE BOARDS. 8" × 6", 5 for **55p**. P. & P. 13p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations: 0-5-10-15-20-25-30-35-40-60V half wave at 1 amp or 10-0-10, 20-0-20, 30-0-30V, at 2 amps full wave. Size 3inL × 3¼inW × 3inD. Price **£2·10**. P. & P. 30p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240V Sec. 9-0-9 at 500mA. **£1** P. & P. 13p. Pri. 200/240V Sec. 12-0-12 at 1 amp. **£1·10** P. & P. 13p. Pri. 200/240V Sec. 10-0-10 at 2 amp. **£1·65** P. & P. 30p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER. For P.U. Tape, Mike, Guitar, etc., and suitable for use with valve or transistor equipment. 9–18V. Battery or from H.T. line 200/300V. Frequency response 15Hz–25KHz. Gain 26dB. Solid encapsulation size 1¾ × 1¼ × ¾in. Brand new — complete with instructions. Price **£1**. P. & P. 13p.

3 REFERENCE ENCYCLOPEDIAS FOR ELECTRONIC ENGINEERS AND DESIGNERS, covering between them, transistor characteristics, diode and transistor equivalents. Many thousands of up-to-date European types listed.

Diode Equivalents	**80p**
Transistor Equivalents	**90p**
Transistor Characteristics	**£1·20**
All three together	**£2·60**

POST FREE

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A., European and Japanese transistors. ONLY **40p**. Post 5p.

CENTRE ZERO MINIATURE MOVING COIL METER. 100μA for balance or tuning. Approx. size 1in × 1in × ¾in. Limited number **88p**. P. & P. 10p.

RECORD PLAYER BARGAINS

Mains models. All brand new in maker's packing.

LATEST B.S.R. C109/C129 AUTOCHANGER UNITS. With latest stereo/mono compatible cartridge **£7·60** plus 50p P. & P.

Garrard SP25 Mk. III with heavy precision machined die cast turntable. **£10·56.** Carr. 50p.

PRECISION ENGINEERED PLINTHS

Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, 5100, SP25 II and III, SL65B, AT60, etc., or B.S.R. C109, C129, A21, etc. Black leatherette finish. Size 12¼in × 14¼in × 3¼in high (approx. 7¼in high, including rigid smoked acrylic cover). P. & P. 35p. **Now only £4·95**

LATEST ACOS GP91/1SC Mono Compatible Cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. **£1·50.** P. & P. 8p.

SONOTONE 9TAHC COMPATIBLE STEREO CARTRIDGE T/O stylus. Diamond Stereo LP and Sapphire 78. ONLY **£2·30.** P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. **£2·90.** P. & P. 10p.

LATEST RONETTE T/O Stereo Compatible Cartridge for EP/LP/Stereo/78. **£1·63.** P. & P. 10p.

LATEST RONETTE T/O Mono Compatible Cartridge for EP/LP/78 mono/stereo records on mono equipment **£1·50.** P. & P 10p.

QUALITY RECORD PLAYER AMPLIFIER MK II

A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. × 3 d. × 5 h. Ready built and tested. PRICE **£4·40.** P. & P. 40p. ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE **£5·85.** P. & P. 50p.

SPECIAL OFFER!!

HI-FI LOUDSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16in high × 10½in wide × 6in deep. Fitted with E.M.I. Ceramic Magnet 13in × 8in bass unit, two H.F. tweeter units and crossover. Max. power handling 10W. Available 3, 8 or 15 ohm impedance.

Our Price £9·25 Carr. 70p.

CABINET AVAILABLE SEPARATELY **£4·95.** Carr. 65p.

Also available in 8 ohm with EMI 13in × 8in. bass speaker with parasitic tweeter. **£7·15.** Carr. 70p.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3·5 watts. Volume and tone controls. Chassis size only 7in. wide × 3in. deep × 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New, completely wired and tested with good quality output transformer.

OUR ROCK BOTTOM BARGAIN PRICE **£3·30** P. & P. 35p

LOUDSPEAKER BARGAINS

5in 3 ohm **£1·05**, P. & P. 15p. 7 × 4in 3 ohm **£1·15**, P. & P. 20p. 10 × 6in 3 or 15 ohm **£1·90**, P. & P. 30p. E.M.I. 8 × 5in 3 ohm with high flux magnet **£1·62**, P. & P. 20p. E.M.I. 13½ × 8in with high flux ceramic magnet with parasitic tweeter 3, 8, or 15 ohm **£3·50**. P. & P. 30p. E.M.I. 13 × 8in, 3 or 8 or 15 ohm with two inbuilt tweeters and crossover network **£4·65**. P. & P. 30p.

EMI CERAMIC MAGNET HEAVY DUTY TWEETER. pprox. 3½in. Av. 3 or 8 or 15 ohms. **£1·25** plus 15p p. & p.

BRAND NEW. 12in 15w H/D Speakers, 3 or 15 ohm. Current production by well-known British maker. Now with Hiflux ceramic ferrobar magnet assembly **£7·50**. Guitar models: 25w **£7·50**, 35w **£9·35**. P. & P. 40p each.



SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUDSPEAKERS. With large ceramic magnet and plasticised cone surround. 8 ohm impedance.

£2·70. P. & P. 25p.

12in "RA" TWIN CONE LOUDSPEAKER

10 watts peak handling. 3, 8 or 15 ohm, **£2·45**. P. & P. 30p. **35 ohm SPEAKERS 3".** ONLY **70p**. P. & P. 13p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11¾in × 14¾in × 1¼in deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz–20kHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only **£6·55** each. P. & P. 25p.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. **Our price 85p yd.** length. P. & P. 15p per yd. (min. 1 yd.). S.A.E. for samples.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam earmuffs. Wired and fitted with standard stereo ¼in jack plug. Frequency response 30–15,000Hz. Matching impedance 8–16 ohms. Easily converted for mono. PRICE **£3·30.** P. & P. 15p.

HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE **£1·15.** P. & P. 10p.

HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED FIBRE GLASS PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EVEN EASIER CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. (Very simple to modify to suit magnetic cartridge—instructions included). Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled fibre glass printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 14W r.m.s. per channel into 5 ohms. Frequency response ± 3dB 12–30,000Hz. Sensitivity better than 80mV into 1MΩ. Full power bandwidth ± 3dB 12–15,000Hz. Bass boost approx. to + 12dB. Treble cut approx. to —16dB. Negative feedback 18dB over main amp. Power requirements 35V at 1·0 amp. Overall size—12" wide × 8" deep × 2½" high.


Fully detailed 7-page construction manual and parts list free with kit or send 18p plus large S.A.E.

PRICES

AMPLIFIER KIT,	**£11·55** P. & P. 18p.
(Magnetic input components 33p extra)	
POWER PACK KIT,	**£3.30** P. & P. 33p.
CABINET,	**£3·30** P. & P 33p.

(Post Free if all units purchased at same time). Full after sales service. Also available ready built and tested, **£23·10.** Post Free.

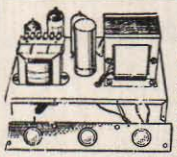Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.



3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7¼in w. × 4in. d. × 4¼in. h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4½ watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only **£5·50.** P. & P. 35p.

BRITISH MADE SOLID STATE ALL SILICON STEREO AMPLIFIER. 15 watts rms per channel output. Frequency response 20Hz to 20KHz. Suitable for magnetic or ceramic pickup tape mic., etc., built-in switchable scratch filter, rumble filter and loudness control. 60 m/m slider controls for bass, treble and volume. 10 way push button function, selector switch. This amplifier has specification and performance usually only found in amplifiers costing twice as much. Each amplifier supplied, tested and fully guaranteed. Finished in the most attractive contemporary style teak cabinet. Size 16½in. × 8½in. × 4½in. Makers' recommended price £46·36. Our price (while stocks last) **£35·75** plus 75p P. & P. Send S.A.E. for full details of specification.

10/14 WATT HI-FI AMPLIFIER KIT



A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3–15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet **15p** plus S.A.E. (Free with parts). **All parts sold separately.** ONLY **£8·80.** P. & P. 55p. Also available ready built and tested **£12·10.** P. & P. 60p.

Open 9-5.30 Mon. to Fri. 9-5 Sat. Early closing Wed. 1p.m.

A few minutes from South Wimbledon Tube Station.


HARVERSON SURPLUS CO. LTD.

Dept. PE, 170 High St., Merton, London, S.W.19 Tel. 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

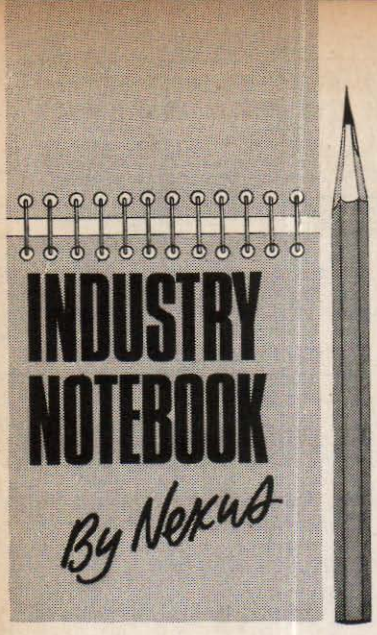PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.



PACE SETTERS

This month I tip two private companies worth watching for future growth. First is Sinclair Radionics currently moving into a strong position with nearly £2 million turnover and a confident forecast of at least £3 million next year. Clive Sinclair at the age of 32 still has the great bulk of his working life ahead of him and now he has the sort of cash flow needed to finance the development of new projects.

The Sinclair "Executive" pocket calculator has proved itself to be the big business breakthrough he had hoped for. It came in a higher price bracket than his previous products and quickly established the volume of production that pushed his company forward, almost overnight, into a new and exciting situation. The "Executive" is now rolling out of final test at the rate of 10,000 per month and 40 per cent of production goes overseas.

Sinclair is investing a lot of his additional turnover in R and D. Expect to see in the next few months or so some new calculators, a range of test instruments to follow up the recently introduced digital multimeter, a pocket-sized TV set, a digital watch and something exciting in digital computers. But he is not going to neglect his army of faithful followers in the audio and hi-fi sector. There will be something new for them too.

Sinclair is clearly widening his market in the consumer sector and starting to move into the professional area, initially through instrumentation. There's nothing that succeeds like success.

My number two tip is Jermyn Manufacturing led by managing director Graham Rattcliff. I last saw him towards the end of April when he was running one of a series of seminars promoting the use of heat pipes, an old idea which has now won a new lease of life as an efficient heat dissipator in modern equipment.

The company's main line is in moulded components and heat pipes are comparatively new. Nonetheless, Rattcliff sees them as an important new line although he confesses that more people want "specials" than from the standard range—always a manufacturer's headache.

I tip both Sinclair Radionics and Jermyn Manufacturing for big growth not only because the products are right but also because both companies are strong on marketing. Sinclair has just established a New York office. Jermyn has sales offices in Munich, Paris and San Francisco.

DISTRIBUTOR NEWS

Component distributors are looking distinctly more cheerful these days now that orders are flowing in faster than supplies rather than the other way round.

Farnell Electronics, among Britain's biggest, has broken through the £1 million pre-tax profit barrier for the first time. Last month SASCO celebrated its 21st Birthday with press advertising wishing founder George ("Stewie") Stewart best wishes.

John Zuber, new chairman and managing director of Guest International has opened a Distribution Division which, if it works as well as his computerised stock control and order system—about the best I've seen—should prosper exceedingly well. And Swift Hardman's new Industrial Electronics and Automation Division, now under the control of ex-TI man Peter Linforth, is aiming at an initial turnover of £1·5 million and was on target when I visited the company a few weeks ago. New franchises include Greenpar (co-axial connectors), Beswick (fuses), and OKI (opto-electronics) bringing the franchise total to 20 in electronics plus 16 in the electro-mechanical sector.

It was rumoured that Motorola Semiconductors might hire or fire one or two distributors this year but the five old faithfuls (Jermyn Distribution, Celdis, Semicomps, A.M. Lock and GDS) all got a nice pat on the back from vice-president Tom Connors at the annual re-appointment ceremony and there were no new appointments.

Leicester-based Atlantic have won a valuable new franchise from National Semiconductors and this should give a big boost to one of our newest distributor companies.

SELLING SERVICES

You don't necessarily have to manufacture or sell goods to make money. Quite a few companies make a good living selling services. Companies like International Aeradio and Cable and Wireless have been doing it for years. A division within Plessey has substantial business on advising and supervising warship re-fits. This outfit works in conjunction with shipyards and although you don't get orders on a daily or even weekly basis, when they come they're big.

Then there is EASAMS which, if my memory serves me correctly, started off in life in 1962 with the name being an acronym for Elliott Automation Space and Military Systems. Since those days there has been some diversification to include consultancy and planning projects in all sorts of fields such as hospitals, transportation and even, recently, an investigation on how best to integrate the coconut industry in Malaya.

FIRST AWARD

EASAMS is the first consultancy firm to win the Queen's Award to Industry for exports with overseas contracts up 300 per cent since 1970. But one of EASAMS toughest jobs must still be the management of the integration of the electronic systems on the European Multi-Role Combat Aircraft (MRCA).

Another unusual Queen's Award winner, again for exports, is four-year-old Racal-Milgo. I write 'unusual' because this company is 50 per cent owned by the Milgo Corporation U.S.A. and I'm wondering (jokingly!) whether Milgo Corp. will be flying the flag and wearing the ties equally with their British partners. Although the equipment comes from the U.S.A. it's the British end of the partnership that provides the international consultancy service, feasibility studies, planning and implementation of some of the most complex data transmission networks in the world today.

Our congratulations go to EASAMS and Racal-Milgo together with English Electric Valve Company who got the only award in the electronics industry for technological innovation, the product being the ceramic hydrogen thyratron.

MOBILE RADIO RATIONALISATION

The long war of attrition in the two-way mobile radio market with lots of little fellows trying to compete with one big one appears to be over following the announcement that Cossor's mobile business has been acquired by Burndept Electronics. This new move follows Burndept's acquisition of the Ultra business in mobile radiotelephones last year, and we must now assume that Burndept will be in a position to seriously start challenging Pye Telecommunications who hold well over 50 per cent of the market.

PATENTS REVIEW...

WATER LEVEL ALARM

BP1 271 654

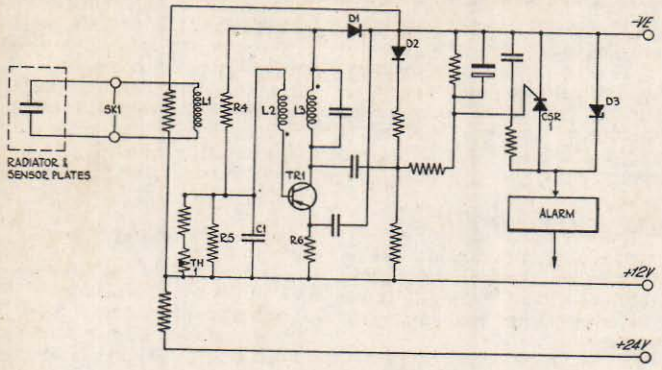


Fig. 1

In BP 1 271 654 Smiths Industries Limited describes circuitry for using an oscillator to sense the loss of cooling water from a car radiator.

A tuned collector oscillator centres round transistor TR1 which has its emitter connected via resistor R6 to a 12 or 24V positive line. The transistor collector connects with the negative line through a transformer winding L3 and diode D1.

The transformer has two further windings L1 and L2, of which winding L2 is connected between the base of TR1 and the junction of R4, R5 and C1. Two electrodes mounted inside the car radiator are connected to L1 through the input socket SK1.

The transformer windings have a turns ratio such that the effective impedance in parallel with L3 is too high to adversely affect oscillation, hence the oscillator will oscillate at audio frequency. But when the radiator water is high enough to short the two electrodes together, the effective impedance in parallel with L3 will drop and so damp down and stop oscillation.

By feeding the oscillator output via a rectification circuit to an alarm system it is possible to sound an alarm or trigger a light when the water level falls and the undamped oscillator starts to produce an audio frequency oscillation.

Various temperature sensitive components, such as a thermistor TH1, provide temperature compensation for the oscillator. This is obviously necessary bearing in mind the high temperature levels encountered in running vehicle engines.

AMPLIFIER PROTECTION

The Marconi Company Limited in BP 1 285 685 has some simple circuitry to offer which, according to some fairly complicated theory, provides protection for transistors against high voltages resulting from generated harmonics.

Fig. 1 shows a well known A-B push-pull wide band amplifier for high frequency working. Transistors TR1 and TR2 are fed by input transformer T1 with a centre-tapped secondary and feed the centre-tapped primary of an output transformer T2. (The circuit is simplified for clarity.)

The amplifier will produce a comparatively high level third harmonic and to eliminate output power at the frequency of this harmonic a filter network (VC1, 2 and L1) is fed via a coaxial cable, the final output being fed to the output terminal. Assuming an applied voltage of 28V, with perfect coupling the voltage on the transistor should never exceed 56 volts. But nothing in this world being perfect, third harmonics produce excessive voltage levels.

The coaxial cable disturbs the ideal phase relationship between the fundamental frequency wave and the third harmonic wave and causes the harmonic to increase the voltage swing in the collector voltage rather than reduce it.

The Marconi invention centres round the provision of a voltage limiting means for modifying the phase of the third harmonic frequency component of the voltage present at the transistor collectors, in relation to the fundamental frequency of the voltage there. But there is no change in amplitude of the fundamental frequency component. Usually a diode clipper is used to limit the voltage wave at the transistor collector so as to produce a flat-topped voltage wave limited to a maximum level such that the fundamental is virtually unaffected by the clipping.

Circuit Fig. 2 shows their novel circuit. This generally resembles the Fig. 1 circuit except that diodes D1 and D2 are used with a d.c. blocking capacitor C1, the diodes receive a d.c. voltage of 60 volts. As a result, the voltage wave form at the collectors of the transistors have a flat top limited to 60 volts.

Although the diodes appear to function as an ordinary amplitude clipper, in fact they operate to clip to a clipping level and merely modify the phase of the third harmonic. Fig. 3a shows the fundamental *Y* and third harmonic *Z* which together make up curve *X* of Fig. 3b. Thus there is no distortion and the clipping is linear.

BP1 285 685

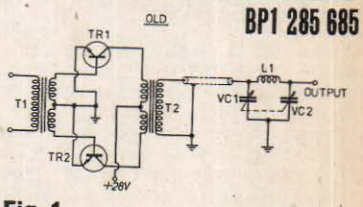


Fig. 1

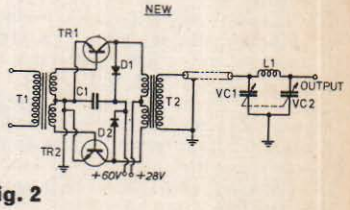


Fig. 2

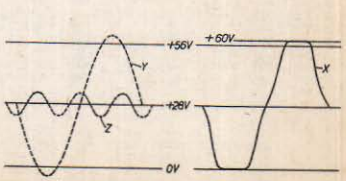


Fig. 3 (a) **(b)**


TRANNIES

I DOCKYARD, STATION ROAD, OLD HARLOW, ESSEX
Phone Harlow 37739

P/P 10p. Price list S.A.E. (Saturday callers welcome)
ALL PRICES INCLUDE VAT

£19.50 ELECTRONIC DIGITAL CLOCK

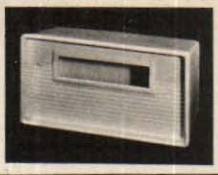(For complete kit of parts including case.)



This 4 digit 24 hour clock is available to readers at this special price for 1 month only. Parts would normally cost over £25. Kit of parts includes twelve IC's, indicators, and a smart white plastic case.

74 Series TTL



	1	25		1	25		1	25		1	25
SN7400	16p	15p	SN7423	55p	50p	SN7450	16p	15p	SN7489	6·05p	5·85p
SN7401	16p	15p	SN7425	55p	50p	SN7451	16p	15p	SN7490	74p	72p
SN7402	16p	15p	SN7427	49p	46p	SN7453	16p	15p	SN7491	1·10p	1·04p
SN7403	16p	15p	SN7428	77p	72p	SN7454	16p	15p	SN7492	74p	72p
SN7404	16p	15p	SN7430	16p	15p	SN7460	16p	15p	SN7493	74p	72p
SN7405	16p	15p	SN7432	49p	46p	SN7470	33p	29p	SN7494	85p	72p
SN7406	38p	35p	SN7433	94p	82p	SN7472	33p	29p	SN7495	85p	72p
SN7407	38p	35p	SN7437	72p	69p	SN7473	41p	39p	SN7496	95p	92p
SN7408	20p	18p	SN7438	72p	69p	SN7474	41p	38p	SN74100	1·80p	1·75p
SN7409	20p	18p	SN7440	16p	15p	SN7475	50p	47p	SN74104	1·09p	1·06p
SN7410	17p	15p	SN7441	74p	70p	SN7476	44p	43p	SN74105	1·09p	1·06p
SN7411	97p	95p	SN7442	74p	70p	SN7480	73p	70p	SN74107	44p	42p
SN7412	38p	35p	SN7443	1·43p	1·37p	SN7481	1·32p	1·26p	SN74110	61p	59p
SN7413	32p	29p	SN7444	1·43p	1·37p	SN7482	97p	95p	SN74111	1·37p	1·27p
SN7416	47p	43p	SN7445	2·00p	1·92p	SN7403	1·20p	1·15p	SN74118	1·10p	1·05p
SN7417	47p	43p	SN7446	1·07p	1·02p	SN7484	1·10p	1·05p	SN74119	1·47p	1·37p
SN7420	16p	15p	SN7447	1·10p	1·03p	SN7485	3·96p	3·85p	SN74121	44p	41p
SN7422	55p	50p	SN7448	1·10p	1·03p	SN7486	36p	35p	SN74122	1·54p	1·43p

* Devices may be mixed to qualify for Price Breaks
* 100 Plus less 10% off 25 plus break

Linear Integrated Circuits



301	DIL	50p	723c	DIL	99p
301	TO99	55p	723c	TO99	95p
301	8 PIN DIL	46p	741c	8 PIN DIL	38p
301A	DIL	69p	741c	14 PIN DIL	39p
301A	TO99	69p	741c	TO99	41p
301A	8 PIN DIL	68p	747c	DIL	46p
307	DIL	69p	748c	DIL	39p
307	TO99	69p	748c	TO99	41p
307	8 PIN DIL	68p	1437	DIL	1·27p
308	TO99	6·45p	1458	TO99	1·27p
308A	TO99	6·40p	3046	DIL	84p
709c	DIL	35p	7503	DIL	1·27p
709c	TO99	31p			

Transistors

								Diodes & Rectifiers	
AC107	16p	BC138	36p	BF260	29p	OC44	14p	1N914	8p
AC126	14p	BC142	33p	BF329	18p	OC45	14p	1N916	8p
AC127	13p	BC143	33p	BF330	18p	OC70	23p	1N4148	8p
AC128	13p	BC144	30p	BF390	37p	OC71	14p	1S44	10p
AC142K	22p	BC145	26p	BFX84	28p	OC72	14p	1N4007	22p
AC141K	20p	BC147	9p	BFX85	35p	OC81	14p	1S113	17p
AC176	15p	BC148	9p	BFX86	22p	OC83	22p	1S120	17p
AC187	13p	BC149	9p	BFX87	28p	OC84	28p	1S121	15p
AC187K	20p	BC153	16p	BFX88	26p	TIP29A	53p	1S130	9p
AC188	13p	BC154	17p	BFY50	21p	TIP30A	64p	1S131	11p
AC188K	20p	BC157	13p	BFY51	17p	TIP31A	64p	1S132	13p
ACY17	24p	BC158	12p	BFY52	17p	TIP32A	78p	1S920	8p
ACY18	21p	BC159	14p	BFY64	39p	TIP33	£1·95	1S922	9p
ACY19	25p	BC167	13p	BFY90	72p	TIP34A		1S923	13p
ACY20	22p	BC168	11p	BSX20	19p		£1·54	1S940	6p
ACY21	23p	BC169	11p	C407	22p	TIP35A		AA119	11p
ACY22	18p	BC177	15p	C426	33p		£2·53	AA129	11p
ACY39	68p	BC179	15p	C428	31p	TIP36A		AA213	11p
AD140	40p	BC182L	9p	C450	17p		£3·19	AAZ15	14p
AD142	44p	BC183L	9p	MP8111	35p	TIP41A	79p	AAZ17	14p
AD143	39p	BC184L	9p	MP8112	42p	TIP42A	91p	BA100	16p
AD149	38p	BC186	33p	MP8113	35p	2N706	18p	BA102	25p
AD150	60p	BC212L	11p	MP8121	33p	2N930	23p	BA115	8p
AD161	29p	BC213L	11p	MP8122	44p	2N1131	22p	BA144	14p
AD162	29p	BC214L	11p	MP8123	50p	2N1132	28p	BA145	22p
AD M/P	50p	BC258	9p	NKT211	28p	2N1613	22p	BA154	14p
AF114	14p	BC259	9p	NKT212	28p	2N1711	26p	BAX13	14p
AF115	14p	BC267	14p	NKT214	25p	2N2904	40p	BAX16	14p
AF116	14p	BC268	15p	NKT217	55p	2N2904A		BAY18	19p
AF117	14p	BC300	40p	NKT261	23p		44p	BAY31	9p
AF118	92p	BC301	32p	NKT271	20p	2N2905	46p	BY100	19p
AF124	27p	BC302	30p	NKT274	20p	2N2924	18p	BY126	16p
AF139	39p	BC303	50p	NKT275	25p	2N2926	10p	BY127	19p
AF239	41p	BC304	40p	NKT403	71p	2N3053	26p	BYX10	24p
AL100	77p	BCY70	17p	NKT405	83p	2N3054	55p	OA5	19p
AL102	66p	BCY71	37p	NKY603F		2N3055	52p	OA9	11p
AL103	55p	BCY72	17p		66p	2N3405	44p	OA10	24p
ASY26	31p	BD123	66p	NKT613G		2N3663	57p	OA47	9p
ASY27	40p	BD130	50p		33p	2N3702	9p	OA70	8p
AU103	99p	BD131	68p	NKT674	26p	2N3703	9p	OA73	11p
AU110	£1·10	BD132	90p	NKT677G		2N3704	9p	OA79	8p
AU111	77p	BD135	42p		24p	2N3705	9p	OA81	9p
BC107	9p	BD136	50p	NKT713	32p	2N3706	9p	OA85	11p
BC108	9p	BD141	£1·87	NKT773	27p	2N3707	9p	OA90	8p
BC109	9p	BD142	50p	OC19	55p	2N3708	9p	OA91	8p
BC113	15½p	BF159	33p	OC20	55p	2N3709	9p	OA95	8p
BC116	16p	BF173	29p	OC23	33p	2N3710	9p	OA200	11p
BC125	16p	BF177	28p	OC25	28p	2N3711	9p		
BC126	25p	BF178	29p	OC28	33p	2N3794	17p		
BC132	16p	BF179	35p	OC29	33p	2N3819	28p		
BC134	16p	BF194	15p	OC35	38p	40361	50p		
BC135	16p	BF195	17p	OC36	38p	40362	50p		
BC137	16p	BF244	27p	OC41	14p	40636	50p		

MULLARD POLYESTER'S

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0·01μF, 0·015μF, 0·022μF, 3½p. 0·33μF, 0·047μF, 0·068μF, 4p. 0·1μF, 4½p. 0·15μF, 0·22μF, 5½p. 0·33μF, 7p. 0·47μF, 9½p. 0·68μF, 12p. 1·0μF, 14p. 1·5μF, 22p. 2·2μF, 27p

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0·001μF, 0·0015μF, 0·0022μF, 0·0033μF, 0·0047μF, 2½p. 0·0068μF, 0·01μF, 0·015μF 0·022μF, 0·033μF, 3½p. 0·047μF, 0·068μF, 0·1μF, 4½p. 0·15μF, 6½p. 0·22μF, 8½p. 0·33μF, 12p. 0·47μF, 14p.
160V: 0·01μF, 0·015μF, 0·22μF, 0·033μF, 0·047μF, 0·068μF, 3p. 0·1μF 3½p. 0·15μF, 4½p. 0·22μF, 5½p. 0·33μF, 6½p. 0·47μF, 8½p. 0·68μF, 12p. 1·0μF, 14½p.

VOLUME CONTROLS

Potentiometers
Carbon track 500 Ω to 2·2M Ω
Log or Linear
Single 13p. Dual gang (stereo) 44p
Single type with D.P. switch 13p extra.

SLIDE POTENTIOMETERS

58mm, TRACK
SINGLE GANGED, LOG or LIN 1k to 1M. 45p each
TWIN GANGED, LOG or LIN 1k to 500k. 66p each.

CARBON SKELETON PRESETS

Small high quality type (linear only).
All valves 100-5 meg ohms.
·1 watt 5½p each
·2-5 watt 6½p each

VEROBOARD

	0·15 Matrix	0·1 Matrix
2½in × 3½in	19p	26p
2½in × 5in	28p	28p
3½in × 3½in	28p	28p
3½in × 5in	38p	32p
5in × 17in (plain)	94p	—

Vero Pins (bag of 36), 22p
Vero cutter, 50p; Pin insertion Tools (0·1 and 0·15 matrix) at 61p.

SLIDE SWITCH

SPST 11p each. D.P.D.T. 13p each.

MINIATURE NEON LAMPS

240V or 110V 1-4 5p, 5 plus 4½p each.

MINITRON DIGITAL INDICATOR TYPE 3015F

Reads 0–9 and decimals
(Data Sheet on request)
ONLY £1·50
16 DIL Socket 33p
Driven by 7447 £1·05

RECTIFIERS

P.I.V.	1 AMP	1·5 AMP
50	IN4001 4½p	PL4001 8p
100	IN4002 4½p	PL4002 9p
200	IN4003 5½p	PL4003 10p
400	IN4004 6½p	PL4004 10p
600	IN4005 8p	PL4005 13p
800	IN4006 9p	PL4006 15p
1000	IN4007 10p	PL4007 20p

BRIDGE RECTIFIERS

P.I.V.	1 AMP	2 AMP	5 AMP	10 AMP
50	33p	53p	£1·76p	£2·20p
100	35p	57p	—	—
200	37p	60p	£1·98p	£2·31p
400	40p	64p	£2·15p	£2·42p
600	44p	66p	£2·42p	£2·75p
800	49p	—	—	—

THYRISTORS

PIV	50	100	200	300	400
1 Amp	28	25	41	44	53
3 Amps	44	50	60	—	66
7 Amps	—	96	1·01	—	1·24

RESISTORS

¼ watt 5% carbon 1p each
¼ watt 10% carbon 1p each
1 watt 10% carbon 2½p each
Range 10 ohms to 4·7 meg.
½ watt m/o 2% 3p each
Range 10—1 meg ohms

Electrolytic Capacitors

4 VOLT

47μF	6½p
100μF	6½p
220μF	6½p
330μF	6½p
1000μF	13p
4700μF	29p

6·3 VOLT

33μF	6½p
68μF	6½p
150μF	6½p
470μF	11p
680μF	13p
1500μF	18p
2200μF	18p
3300μF	26p

10 VOLT

22μF	6½p
47μF	6½p
100μF	6½p
220μF	8p
330μF	10p
470μF	10p
1000μF	11p
1500μF	20p
2200μF	24p

16 VOLT

15μF	6½p
33μF	6½p
68μF	6½p
150μF	8p
220μF	9p
680μF	17p
1000μF	17p
1500μF	25p
2000μF	43p

25 VOLT

10μF	6½p
22μF	6½p
47μF	6½p
100μF	8p
150μF	8p
220μF	10p
470μF	13p
680μF	20p
1000μF	22p
2200μF	39p
5000μF	68p

40 VOLT

6·8μF	6½p
15μF	6½p
33μF	6½p

40 VOLT

47μF	6½p
100μF	9p
150μF	10p
220μF	11p
470μF	19p
680μF	25p
1000μF	25p
2200μF	44p

63 VOLT

1μF	6½p
2·2μF	6½p
4·7μF	6½p
6·8μF	6½p
10μF	6½p
22μF	6½p
68μF	10p
100μF	11p
150μF	13p
220μF	19p
330μF	22p
470μF	26p
1000μF	44p

BARGAIN PACKS

Unmarked Packs
Pack of 25 IN4148 55p

Pack of 10
BC108 55p
BC107 55p
(Plastic can)

Pack of 10 Plastic BC109 55p

Pack of 10
BC169 55p
(unmarked) but tested

2N2646 (unmarked) 33p each

Pack of 10
2N2926G 55p
unbranded but tested

Unmarked but fully tested 2N3055
1–9 33p
10 plus 27p

FULLY MARKED TYPES

AD161, AD162 M/P
1–9 59p
10 plus 53p

BC107–BC108 BC109
1–9 9p
10–99 8p
100 plus 6½p

BC 182L:-3-4-212-4
1–9 9p
10 plus 8p

AC127 or AC128
1–9 13p
10 plus 12p
100 plus 11p

ZENER DIODES

400 M/W 5% Miniature BZY 88 Range
All voltages 3·3—33 Volt 9p each

1 watt 5%
All voltages 6·8—200 Volts 14p each

10 watt 5%
All Voltages 7·5—100 Volts 51p each

CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER DEPT. No. 11 MAYES RD. LONDON N22 6TL

COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY (WE CLOSE ALL DAY THURSDAY)

13 SOUTH MALL, EDMONTON, N.9 803 1685

"CRESCENT" BUBBLE LIGHT SHOW



A new and exciting feature for the professional disc jockey or to give the private party an electric atmosphere, a projected kaleidoscope of colour makes the music you produce more interesting and will appeal to the visual as well as the audio senses.
This budget system compares very favourably with the more sophisticated and much higher priced models.
Specification—Projector: 150W, convection cooled, at 30ft the projected image = 16ft; Motor: 1 rev per 2 min. Liquid Wheel: 6in diameter multicolour.
The Motor is fitted to the Projector and can only be purchased as a single unit. The Liquid Wheel, however, is our very popular standard model & may be purchased separately. A bargain—Projector with Motor ready for instant use, £15; 6in Liquid Wheel, £5=£20 + 75p carr.

TRI-VOLT BATTERY ELIMINATOR



Enables you to work your Transistor Radio, Amplifier or Cassette, etc., from the a.c. mains through this compact Eliminator. Just by moving a plug you can select the voltage you require, 6, 7½ or 9 volt. This means all your transistor power pack applications can be handled by this one unit. Approx. size 2¼in × 2½in × 3¼in. Our Price £2·75 plus 10p P. & P. Same model suitably wired for the Philips Cassette £3 plus 10p P. & P.

DIGITAL CLOCK KIT



24-hr. Nixie dig. clock kit. We supply: a complete set of components; a complete set of easy to follow instructions; printed circuits made to make construction as simple as possible; a cabinet and front panel to give a professional finish. All for the price of the components. £22·50 + 50p P. & P. Please send S.A.E. if you require more information.

AL20 5 WATT AUDIO AMPLIFIER



A low cost high quality 5 watt audio amplifier designed for use in stereo systems, record players and other audio equipment.
Supply Voltage = 9 to 30 volts.
Frequency = 50 to 25 kHz.
Overall Size = 3in × 2½in × 1in approx.
Full technical data and diagrams with each module.
All guaranteed and a bargain at £2·63 plus 5p P. & P.

V.A.T.
From 1st April, 1973, will you please include on your Total (Goods plus Postage and Packing) Value Added Tax at the Standard Stated Rate.

200/250V MAINS RELAY
Heavy duty contacts. 2,500 Ω coil. All new and unused D.P.D.T. mains relays 50p + V.A.T. Carr. Free. Special quantity price: £40 per 100 relays.



MAINS TRANSFORMER
Fused Primary 240V. Secondary 220V @ 50mA. 6·3V @ 1A. This transformer is made to a very high standard and is a small size: 2in × 2¼in × 2½in. 63p plus 15p P. & P.



TRI-VOLT CAR SUPPLY
Enables you to work your Transistor Radio, Amplifier or Cassette, etc. from the 12 volt car supply. Positive or negative earth. Approx. size = 2in. × 3½in. × 1½in. This converter supplies 6, 7½ or 9 volts and is transistor regulated. A real money saving device for £2·50 plus 10p P. & P.

MINI LOUDSPEAKERS



2½in 8 ohm, 50p; 2½in 80 ohm, 50p; 2½in 40 ohm, 50p. Please include 5p P. & P. on each L.S.

ADD LUXURY TO YOUR CAR WITH A MOTOR DRIVEN CAR AERIAL



Spec.: 5 Section
Extended Length 100cm
Length under Fender 40cm
Cable Length 120cm
Supplied complete with Fixing Bracket and Control Switch. £6·75 plus 25p P. & P.

EMI LOUDSPEAKER 450



10W 13in × 8in ± two 2·2½in tweeters and cross-over. All wired and ready for use. This ever-popular 450 in 3–8–15 ohm imp. £3·75 plus 38p P. & P. each.

CRESCENT CASSETTES



Top quality cassettes at unbeatable prices (complete with standard storage case): C60 28p, C90 38p, C120 48p plus 5p P. & P.

"CRESCENT" 100 WATT R.M.S. ALL PURPOSE AMPLIFIER U.BUILD.IT
We supply the three modules for you to build this Disco-Group-P.A. amplifier into the cabinet of your choice.

★ **THE POWER AMP MODULE TP100W**
170W r.m.s. sq. wave 300W instantaneous peak into 8 ohm (60W into 16 ohm). £14·28 carr. 45p

★ **THE PRE-AMP MODULE**
Four control pre-amp, Vol, Bass, Treble. Middle controls. Designed to drive most amplifiers using F.E.T. first stage. £3·96 carr. 25p


★ **THE POWER SUPPLY MODULE PS100**
Is supplied complete with the mains transformer. £9·66 carr. 50p
Complete fixing instructions are supplied and no technical knowledge is required to connect the three ready wired modules.
A fantastic bargain. If you purchase all three modules. £25 carr. 75p
Send S.A.E. for further details on this or our ready built amplifiers.

7in × 4in LOUDSPEAKER



A top quality speaker ideal where small size is important. Manufactured by E.M.I. for a well-known hi-fi set maker. Size: 7in × 4in. Impedance: 8 ohms. Flux: 38,000. Max. Free range: 90Hz to 12kHz. Power handling: 5W. Unbeatable. Price: £1·60. Free postage on this item.

PSYCHEDELIC LIGHT CONTROL UNIT

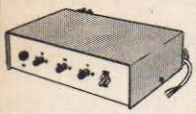

Three Channel: Bass—Middle—Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 500W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed) £18·50 plus 38p P. & P.
If you require more information please send S.A.E.

I-N-T-E-R-L-O-C-K-I-N-G PLASTIC STORAGE DRAWERS



Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/removable space dividers. Build up any size cabinet for wall, bench or table top.

BUY AT TRADE PRICES!

SINGLE UNITS (1D) (5ins × 2½ins × 2½ins). £1·25 DOZEN.

DOUBLE UNITS (2D) (5ins × 4½ins × 2½ins). £2·10 DOZEN.

TREBLE (3D) £2·20 for 8.

DOUBLE TREBLE 2 drawers, in one outer case **(6D2)**, £3·25 for 8, **EXTRA LARGE SIZE (6D1)** £3·10 for 8.

PLUS QUANTITY DISCOUNTS!
Orders £6 and over DEDUCT 5% in the £
Orders £10 and over DEDUCT 7½% in the £
Orders £20 and over DEDUCT 10% in the £

PACKING/POSTAGE/CARRIAGE: Add 35p to all orders under £10. Orders £10 and over, packing/postage/carriage free.

QUOTATIONS FOR LARGER QUANTITIES

Please add 10% V.A.T. to total remittance

IVORYET LIMITED (Dept. PE7) 124 Cricklewood Broadway, London, N.W.2 Tel. 01-450 4844

A DEXTER DIMMASWITCH ALLOWS COMPLETE LIGHTING CONTROL



The DEXTER DIMMASWITCH is an attractive Dimma unit which simply replaces the normal light switch. It is available as a complete "ready to install" unit or "simple to assemble" kit. Two models are available controlling up to 300W or 600W of all lights, except fluorescents, at mains 200-250V, 50Hz. All DEXTER DIMMASWITCH models have built-in radio interference suppression.
600 watt £3.52 Kit form £2.97
300 watt £2.97 Kit form £2.42
All plus 12p post and packing
Prices include VAT. Please send c.w.o. to:

DEXTER & COMPANY
1 ULVER HOUSE
19 KING STREET
CHESTER CH1 2AH
Tel: 0244-25883

AS SUPPLIED TO H.M. GOVERNMENT DEPARTMENTS, HOSPITALS, LOCAL AUTHORITIES, ETC.

RADIO AMATEUR'S HANDBOOK 1973
by THE A.R.R.L.
Price £2·95

UNDERSTANDING ELECTRONIC CIRCUITS by Ian R. Sinclair. Price £3·65.

HOW TO GET THE BEST OUT OF YOUR TAPE RECORDER by P. J. Guy. Price £1·60.

TRANSISTORISED RADIO CONTROL FOR MODELS by D. W. Aldridge. Price £1·60.

HAM RADIO: A BEGINNER'S GUIDE by R. H. Warring. Price £1·70.

PRACTICAL RELAY CIRCUITS by F. J. Oliver. Price £3·40.

110 INTEGRATED CIRCUIT PROJECTS FOR THE HOME CONSTRUCTOR by R. M. Marston. Price £1·25.

TRANSISTOR POCKET BOOK by R. G. Hibberd. Price £1·50.

RADIO HANDBOOK NEW 19th ED. by W. I. Orr. Price £7·75.

ALL PRICES INCLUDE POSTAGE

THE MODERN BOOK CO.
BRITAIN'S LARGEST STOCKIST of British and American Technical Books
19-21 PRAED STREET LONDON W2 1NP
Phone 01-723 4185
Closed Saturday 1 p.m.

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned.

SLIDE RULE CALCULATOR

Electronic calculators of the pocket variety fall generally into two types. The first is the fairly simple device the operation of which is limited to the more normal mathematical operations, and the price of which is steadily falling to around the £40 mark.

The alternative and much more sophisticated device is capable of carrying out complex maths functions such as rooting or calculating to specific laws. Currently there are only one or two of these latter and their price tends to rest in the £200 region.

Predictably, just as the cost of the smaller version has dropped swiftly over the last two years, the more complex device is now showing reduction tendencies.

Thus **Texas Instruments** have just announced a pocket "slide-rule" type of instrument capable of calculating reciprocals, squares and roots, true credit balance and all the more usual functions.

It will also convert an arithmetic entry to scientific notation when the entry exceeds eight digits.

Capable of handling positive and negative numbers over a 200 decade range, the SR-10 is selling at £87·50.

DIGITAL MULTIMETER

Another contender in the low cost digital multimeter field has just been announced by **Advance.** Called the Alpha, it will retail at £55, a price which makes it a real challenge to the analogue meter as well as other digital multimeters.

The Alpha features a total of 24 ranges enabling it to measure d.c. voltages from 1mV to 1kV, a.c. voltages from 1mV to 500V, d.c. and a.c. current from 0·1μV to 1A and resistance from 0·1Ω to 10MΩ. The reading is given on a three digit l.c.d. display which can be adjusted in brightness to conserve power. Accuracy is claimed to be 0·2% ±1 digit on the 1V d.c. range and 0·5% ±1 digit on other d.c. voltage ranges. Input impedance is a high 10MΩ and the instrument can stand overloads of 350V on the 1V range and 1kV on other voltage ranges.

The unit consumes 90mW to 400mW dependent on the setting of the brightness control. It is normally supplied by a 9V dry battery which will last several months in normal use. There is also an optional mains unit at £7 extra and a rechargeable battery unit at £17 extra.

The circuit uses a simple single ramp analogue-to-digital conversion system and all the digital circuitry is contained in a single m.o.s. l.s.i. integrated circuit, custom-designed by Advance.

The unit is available direct from the maker, Advance Electronics Ltd., Raynham Road, Bishop's Stortford, Hertfordshire.

WORKSHOP

Several items for the workshop seem to be worth further consideration this month.

For the work bench there's a new adjustable vice from **W. Greenwood Electronic.** Called the Oryx, the vice is ideal for holding circuit boards during soldering.

The vice has a rotating base which is also part of a steel ball joint in the bench clamp. This arrangement allows the user to position his workpiece in practically any position and the fibre faced jaws of the vice will hold delicate components without damage

Addresses of nearest stockists and price list can be obtained from W. Greenwood Electronic Ltd., 21, Germain Street, Chesham, Bucks.

With the decrease in size of components, tool manufacturers have had to scale down a great number of their tools to meet the demands of handling these components. With this problem in mind **Tele-Productions** are now marketing a range of Swedish Stirex hand tools.


Available as side cutters, pliers and scissors the tools have been designed for close work and the complete tools measure a maximum length of only 175mm, including handle. A feature of the tools are plastics spring-loaded handles which are available in varying colours. This enables particular tools to be colour coded for easy identification.

Full details of tools available and price lists can be obtained from Tele-Production Tools, 28-B, Hamlet Court Road, Westcliff-on-Sea, Essex.

One of the more unusual items is a set of multi-blade screwdriver packs from **F. Parramore and Sons (1924) Ltd.** For electrical requirements the Multi-3 pack comprising wallet, chuck and three blades is recommended. For general purpose use the Multi-5 pack should be able to tackle most jobs.

Complete with a robust 4-jaw chuck handle the cruciform interchangeable blades are suitable for slotted, Pozidriv and Phillips screws.

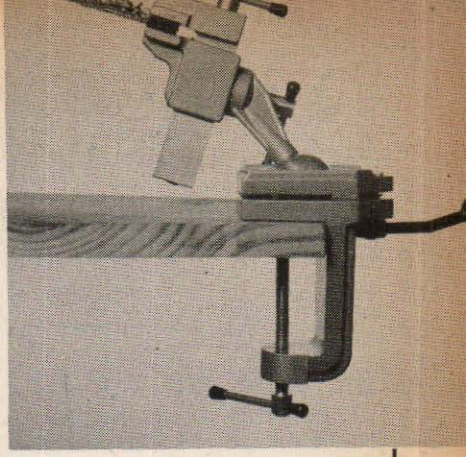One of the reasons for the shape of the blade is that when dealing



Oryx adjustable vice from W. Greenwood Electronic

with over tight screws extra torque can be applied to the blade with a spanner or a special ratchet, available as an extra.

The price of the Multi packs vary from approximately £2·25 to £3·55 and addresses of nearest stockists can be obtained from F. Parramore & Sons (1924) Ltd., Caledonian Works, Chapeltown, Sheffield.

Finally, to help keep the workshop tools tidy readers may be interested in a new range of "Clipco" nylon general purpose clips from **Herbert Terry & Son Ltd.**

Ideal for holding all kinds of tools, the Clipco is made from unbreakable nylon and having a special toothed stem the clips can be easily fixed (no screws or screwing being required) to walls, tiles, wood and pegboard.

Available from most hardware and do-it-yourself stores the clips are sold in packets containing 8, 9 or 10 clips, dependent on size required, and retail at 21p to 23p per pack. The clips can also be purchased in bulk quantity at £2·18 per 100 direct from Herbert Terry & Son Ltd., Redditch, Worcs.



Parramore Paramo screwdriver packs

Alpha digital multimeter from Advance



Readout—

A SELECTION FROM OUR POSTBAG

Correspondents wishing to have a reply must enclose a stamped addressed envelope. We regret we are unable to guarantee a reply on matters not relating to articles published in the magazine. Technical queries cannot be dealt with on the telephone.

Linear or Log Law

Sir—I would like to congratulate your author on the P.E. Sound Synthesiser, on the obviously very impressive results obtained. However, if I might add a few criticisms, I feel that they could prove helpful to your readers, and even Mr Shaw himself. These points are based on a few years' experience in the field of voltage-controlled Synthesiser circuits, and on the successful marketing of such circuits and complete Synthesisers which I have designed.

Firstly, the use of integrated circuits for some applications can be very satisfactory. However, one must remember that one often has to use the most suitable i.c., which is not always (in fact is rarely) exactly made for the job. As a result, one ends up putting the makers' recommended current through the device, say 5 to 10mA, when if one designed a circuit from discrete components one would often find that a few micro-amps is all that is needed for the same job! This means that you can under-run the components at a tiny fraction of the makers' recommended current . . . the life expectancy is thus made infinitely greater.

Secondly, use of most i.c.s involves dual-rail power supply, and also adds dramatically to the overall costs, as i.c.s are going up in price (the Dewtron modules cost, using discrete components, would still be less than £200 for more versatile design than that published, incidentally).

Thirdly, and alas, I feel more importantly, the decision to abandon the use of the proper log-law for the Voltage Controlled Oscillator design. This is really naughty, as it means:

1. No chording facility.
2. No variable keyboard pitch, which is essential if you want the range of use one expects from a synthesiser.
3. Difficulties in tuning the tuning ladder—each note must have its own preset, the adjustment of which will vary vastly from one end of the ladder to the other.
4. Poor frequency stability, because, should voltage or resistance wander, the drift will be concentrated more to one end of the keyboard than the other, due to the non-linearity (or non-log'arity) of the tuning network, whereas, if logarithmic tuning voltage law were used, the variation would be distributed evenly over the whole keyboard, so making it less noticeable, in terms of pitch.
5. Uneven swing in pitch control when driven by a slow-oscillator, unless special (and difficult) compensation is deliberately introduced into the output of the slow oscillator. Imagine a siren that starts climbing in pitch rapidly and then slows down to a slow whine when it reaches the higher frequencies.

Admittedly, the building of a stable, accurate law circuit is difficult, if the effects of temperature are to be minimised, and the circuit shown in the first article is very prone to temperature drift, as matched transistors from a thermal standpoint are virtually impossible to select due to the cycling time involved. None-the-less, circuits are possible (a special unique one is used in the Dewtron-2 module), which will not change even if a hot soldering iron is applied to them! Admittedly, the one in question did take years to perfect, and perhaps Mr Shaw did not have this sort of time at his disposal.

It would be interesting to learn if other readers have further ideas on the above or other points arising from the P.E. Synthesiser design.

B. H. Baily,
Dewtron Design Engineering

Computer Club

Sir—You and your readers may be interested to hear that following my letter in P.E. last year an Amateur Computer Club has been formed.

The club is for those interested in the construction, design or programming of computers as a hobby. At present the main activity of the club is the production of a newsletter which acts as a databus to distribute information on hardware and software techniques of interest to the members.

Any one in joining the club may receive further details from me (SAE appreciated).

M. Lord,
7 Dordells,
Basildon,
Essex

BACK NUMBERS WANTED

Anyone who can supply the undermentioned are asked to communicate directly with the reader.

We regret that back numbers of Practical Electronics can no longer be supplied. We will try to publish announcements of readers' requirements (without a guaranteed date) free of charge.

May-June 1971
Mr. A. V. Barker, 35, Broadwalk, Westhoughton, Nr. Bolton, BL5 2AA.

August 1967
Mr. M. W. Finnemore, 63, Anchorway Road, Green Lane, Coventry, CV3 6JL.

January 1968
Mr. R. Mason, 5 Hope Knowe, Earlston, Berwickshire.

November-December 1971
Mr. K. S. Reehall, 18, Carey Park, Rednnick Lane, Truro, Cornwall.

February 1972
Mr. P. E. North, 33, Windsor Road, Lowestoft, Suffolk.

December 1971, January 1972
Mr. V. G. Dennison, 24, Ledbury Street, Aspley, Brisbane, Australia, 4034.

November 1965, July 1972
Mr. C. H. M. Limb, 68, Westminster Way, North Hinksey, Oxford.

November-December 1971
Mr. D. Griffiths, Deconshire Hall, Cumberland Road, Leeds, LS6 2EQ.

July 1972
Mr. I. Wilson, 8, Cowlarns Road, Barrow-in-Furness, Lancashire.

November-December 1971
Mr. R. A. Eastman, 3, Brookfield Road, Fair Oak, Eastleigh, Hants, SI5 7EX.

April 1971
Mr. D. Wood, 52, Egerton Road, Streetly, Sutton Coldfield, Warks.

February 1967
Mr. C. Calvert, 34, Renwick Road, Blyth, Northumberland.

August 1970
Mr. T. Barclay, Allan Glen's School, 190, Cathedral Street, Glasgow, C.4.

November-December 1968
Mr. B. Russell, 14, Norwood Road, Skegness, Lincs.

January to March 1972
Mr. P. Daswani, 276, Satara Road, Poona—1, India.

February 1969
Mr. P. Couzens, 30, Napier Road, Wembley, Middlesex, HAD 4VA

February 1972
Mr. S. Clements, 17, Sempie Street, Hamilton, Lanarks, ML3 9JL.

September to November 1971
Mr. N. Simmons, 116, Killyglen Road, Larne, Co. Antrim, N. Ireland.

November 1970 to March 1971
Mr. A. Bray, 106, Villiers Street, Stoke, Coventry, CV2 4HL.

Any Copies before April 1971, February to May 1972 and August to October 1972
Mr. F. Murphy, 10, Upton Court, Upton, Wirral, Cheshire, L49 6LS.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0–260V
All Types from ¼ to 50 amp from stock.



SHROUDED TYPE

1 amp, £7·70	20 amp, £53·90
2·5 amp, £8·86	25 amp, £63·80
5 amp, £12·93	37·5 amp, £90·20
10 amp, £24·75	50 amp, £107·80
15 amp, £27·50	

2·5 amp **OPEN TYPE**

(Panel Mounting) ¼ amp, £5·23. 1 amp, £7·70. 2½ amp, £8·86. All carriage paid.

L.T. TRANSFORMERS

All primaries 220–240V

Type No. Sec. Taps	Price
1 30, 32, 34, 36V at 5A	£5·53
2 30, 40, 50V at 5A	£7·95
3 10, 17, 18V at 10A	£5·83
4 6, 12V at 20A	£7·62
5 17, 18, 20V at 20A	£8·56
6 6, 12, 20V at 20A	£8·12
7 24A at 10A	£6·14
8 4, 6, 24, 32V at 12A	£8·42
9 6 and 12V at 10A	£4·51

12 VOLT D.C. MOTOR




Powerful 1 amp. REVERSIBLE motor. Speed 3,750 r.p.m. complete with external gear train (removable) giving approx. final speed of either 125 r.p.m. or 240 r.p.m. Size: 4½in ×2¾in dia. Either type price £1·05.

REVERSIBLE SPLIT PHASE MOTOR

250 r.p.m., 100-115/210-240V A.C., 2in.×1in. Ideal for rim-drive models, display, etc. Extremely powerful for size (including small capacitor). 83p.

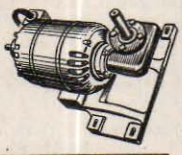PARVALUX TYPE SD19 230/250 VOLT A.C. REVERSIBLE GEARED MOTORS



30 r.p.m. 40 lb. ins. Position of drive spindle adjustable to 3 different angles. Mounted on substantial cast aluminium base. Ex-equipment. Tested and in first-class running order. A really powerful motor offered at a fraction of makers' price. £7·48.

PARVALUX TYPE SD2. 200/250 VOLT A.C./D.C. HIGH SPEED MOTOR



Speed 9,000 r.p.m. approx. or 3,200 r.p.m. if used with built-in governor, or variable speed over a wide range if used in conjunction with our Dimmer Switch, illustrated below. PRICE £2·20.



600 WATT DIMMER SWITCH. Easily fitted. Fully guaranteed by makers. Will control up to 600W of all lights except fluorescent at mains voltage. Complete with simple instructions. £3·30.

240V A.C. SOLENOID FLUID VALVE



Will handle liquids or gases up to 7 p.s.i. Forged brass body, stainless steel core and spring. ¼in b.s.p. inlet/outlet. Precision made, British mfg. PRICE: £2·15.
Special quotation for quantity.
(New in makers' carton)

24-HOUR TIMER



Can be adjusted to give a switching delay of between 2 hrs. to 24 hrs. Driven by 200/250V A.C. synchronous motor. 15 amp c/o contacts. Mfg. Crater Controls Ltd. Supplied with scale calibrated 0-10 (2 hrs. per division). Brand New. £2·20.

HONEYWELL PROGRAMME TIMERS



240V. A.C. 5 r.p.m. motor. Each cam operating a c/o micro switch. Cams are individually variable, allowing inumerable combinations. Ideally suited for machinery control, automation, etc. Also in the field of entertainment, for chaser lights, animated displays, etc.
15 cam model £6·60.
10 cam model £5·50.

SIMPLE 12 CAM PROGRAMMER 240V A.C. 15 RPM MOTOR with 4 adjustable cams and 8 that may be profiled to individual requirements, £4·13.

36V 30 AMP. A.C. or D.C. VARIABLE L.T. SUPPLY UNIT



INPUT 220/240V a.c.
OUTPUT CONTINUOUSLY VARIABLE 0–36V
Fully isolated. Fitted in robust metal case with Voltmeter. Ammeter Panel Indicator and handles. Input and output fully fused. Ideally suited for Lab. or Industrial use. £77.

MOTOROLA MAC 11/6 PLASTIC TRIAC 400 PIV. 10 AMP

Now available EX STOCK. Supplied with full data and applications sheet. Price £1·23.
Suitable DIAC 20p each.

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

EXPERIMENTERS' ECONOMY KIT
Speed adjustable 1 to 30 flash per sec. All electronic components including Xenon Tube and instructions £7·20.

NEW INDUSTRIAL KIT
Ideally suitable for schools, laboratories, etc. Speed adjustable 1-80 f.p.s.
Approx. ½ output of Hy-Lyght. Price £12·10.

HY-LYGHT STROBE MK III
For use in large rooms, halls and utilises a silica tube, printed circuit. Speed adjustable 0-20 f.p.s. Light output greater than many (so called 4 Joule) strobes. £13·75.

THE 'SUPER' HY-LYGHT KIT

Approx. four times the light output of our well proven Hy-Lyght strobe.

- Variable speed from 1-3 flash per sec.
- Reactor control circuit producing an intense white light. ONLY £22·83.

ROBUST, FULLY VENTILATED METAL CASE. For Hy-Lyght Kit including reflector £4·90. Super Hy-Lyght Kit including reflector £8·20.
7-inch POLISHED REFLECTOR
Ideally suited for above Strobe kits. Price 73p.



ELECTRONIC ORGAN KIT

Easy to build. Solid State. Two full octaves (less sharps and flats). Fitted hardwood case. Powered by two penlite 1½V batteries. Complete set of parts including speaker, etc. together with full instructions and 10 tunes. Price £3·50.

RAINBOW STROBE FOUR LIGHT CONTROL MODULE

Will operate four of our Hy-Lyght or Super Hy-Lyght Strobes in either 1, 2, 3, 4 sequence; 2 + 2; or all together. Thoroughly tested and reliable. Complete with full connection instructions. Price: £20·63.
Send S.A.E. for details.

COLOUR WHEEL PROJECTOR



Complete with oil-filled colour wheel. 100 watt lamp. 200/240V A.C. Features extremely efficient optical system. £20·74.

6 INCH COLOUR WHEEL
As used for Disco lighting effects, etc. Price £5·72.

BIG BLACK LIGHT



400Watt. Mercury vapour ultra violet lamp.
Powerful source of u.v. Innumerable industrial applications also ideal for stage, display, discos, etc. P.F. ballast is essential with these bulbs. Price of matched ballast and bulb £18·15.
Spare bulb £8·03.

BLACK LIGHT FLUORESCENT U.V. TUBES

4ft. 40 watt. Price £6·38. (For use in standard bi-pin fluorescent fittings). MINI 9 in. 6 watt black light U.V. tube. £1·60. Complete ballast unit and holders for 9 in. tube. £2·04.

FOOT SWITCH



Suitable for Motors, Drills, Sewing Machines, etc., etc. 5 amp. 250 volt.
Price £1.

ALL PRICES INCLUDE V.A.T. POSTAGE AND PACKING
Overseas orders ask for quote

Superior Quality Precision Made NEW POWER RHEOSTATS



New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.
25 WATT 10/25/50/100/250/500/1k/1·5k ohm £1·10.
50 WATT 1/5/10/25/50/100/250/500/1k/1·5k/2·5k/5k ohm £1·54.
100 WATT 1/5/10/25/50/100/250/500/1k/1·5k/2·5k/3·5k ohm £2·20.
Black Silver Skirted knob calibrated in Nos. 1-9. 1¼in. dia. brass bush. Ideal for above Rheostats, 20p each.

RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS

Col.(1) Coil ohms	1	2	3	4
	52	4–6	6M	70p*
Col. (2)	52	4–6	4 c/o	90p*
Working	150	6–12	4 c/o	90p*
d.c. volts	185	8–12	6M	70p*
Col. 3	410	10–18	4 c/o	80p*
Contracts	600	12–24	4 c/o	80p*
	600	9–18	2 c/o	70p*
Col. (4)	700	16–24	4M 2B	90p*
Price	700	16–24	4 c/o	90p*
	700	15–35	2 c/o HD	80p*
HD=	700	16–24	6M	70p*
Heavy duty	700	6–12	1 c/o HD	60p*
	700	20–30	6 c/o	80p*
*Incl. Base	1,250	24–36	4 c/o	70p*
	2,500	36–45	6M	70p*
All prices	2,400	30–48	4 c/o	60p
incl. P. & P.	9,000	40–70	2 c/o	60p*
	15k	85–110	6M	60p*

12 VOLT D.C. RELAY 140 ohm coil

Type 1: Three sets c/o contacts rated at 5 amps. 88p (Similar to illustration below.)
Type 2: 4-8 volt, 3 c/o HD, 67 ohm coil. 88p.

SPECIAL OFFER
700 ohm 4 c/o. Ex. new equipment. £55 per 100 incl. bases (minimum 100).

230 VOLT A.C. 'DIAMOND H' RELAYS (Unused)



Three sets c/o contacts rated at 5 amps. PRICE: 66p. (100 lots) £44.
24 volt A.C. 3 c/o 66p.

MINIATURE LATCHING RELAY
Manufactured by Clare-Elliott Ltd. Type F. 2 c/o permanent latching in either direction. Coil 1150 ohm, 15-30 Volt D.C. Size ¾" high, ¾" wide, ¾" thick. Complete with 3" leads. New 80p.

BLOWER UNIT



200-240 Volt A.C. Precision German built. Dynamically balanced, quiet, continuously rated, reversible motor. Consumption 60mA. Size 120 mm. dia. ×60 mm. deep. Price £3·50.

UNISELECTOR SWITCHES



NEW **4 Bank 25 Way,** 24V d.c. operation. £6·74. **6 Bank 25 Way,** 24V d.c. £7·43 **8 Bank 25 Way,** 24V d.c. operation. £8·67.

"HONEYWELL" PUSH BUTTON, PANEL MOUNTING MICRO SWITCH ASSEMBLY



Each bank comprises a c/o rated at 10 amps 240V. A.C. Black knob 1in. Fixing hole ¼ in. ONE bank 33p; TWO bank 44p; THREE bank 61p. Quot. for quantity.

'HONEYWELL' LEVER OPERATED MICRO SWITCH



15 amps 250 volt A.C. c/ contacts. Types N100, N101 NEW in maker's carton.
PRICE: 10 for £2·10.

Very special offer



MICRO SWITCH

5 amp c/o contacts. Fitted with removable metal panel assembly. Ex. P.O. 20 for £1·10 (Min. order 20.)

AMMETERS NEW! 2½in. Flush round. Available in D.C. Amps 1, 5, 15, 20 or A.C. Amps 5, 10, 15, 20, both types *£1·93. 0-300V. A.C. £2·09.



INSULATION TESTERS *NEW!*



Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L.8in., W.4in, H.6in, weight 6lb. 1,000V, 1,000 megohms, £37·43. 500V, 500 megohms, £30·80.

All Mail Orders—Callers—Ample Parking
Dept. PE6, 57 BRIDGMAN ROAD CHISWICK, LONDON W4 5BB
Phone 01-995 1560
Showroom open Mon.-Fri.

SERVICE TRADING CO.

Personal callers only. Open Sat.
9 LITTLE NEWPORT STREET LONDON WC2H 7JJ
Phone 01-437 0576

YATES ELECTRONICS

(FLITWICK) LTD.

ELSTOW STORAGE DEPOT
KEMPSTON HARDWICK
BEDFORD

C.W.O. PLEASE. POST AND PACKING PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the components listed will be sent free on request. 10p stamp appreciated.

OPEN ALL DAY SATURDAYS

ALL PRICES SUBJECT TO V.A.T.

RESISTORS

¼W Iskra high stability carbon film—very low noise—capless construction.
¼W Mullard CR25 carbon film—very small body size 7·5 x 2·5mm.
½W 2% ELECTROSIL TR5

Power watts	Tolerance	Range	Values available	Price 1–99	Price 100+
¼	5%	4·7Ω–2·2MΩ	E24	1p	0·8p
¼	10%	3·3MΩ–10MΩ	E12	1p	0·8p
¼	2%	10Ω–1MΩ	E24	3·5p	3p
½	10%	10– 3·9Ω	E12	1p	0·8p
½	5%	4·7Ω–1MΩ	E12	1p	0·8p
4	10%	10–10Ω	E12	6p	5·5p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0·5 watt 5% Iskra resistors 5 off each value 4·7Ω to 1MΩ.
E12 pack 325 resistors **£2·40**. E24 pack 650 resistors **£4·70**.

POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log ¼W, lin ½W).
Single, **12p**. Dual gang (stereo), **40p**. Single D.P. switch **24p**.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C. mounting (0·1 matrix).
Sub-miniature 0·1W, **5p** each. Miniature 0·25W, **6p** each.

TRANSISTORS

AC107	15p	AF125	20p	BD132	75p	OC28	50p
AC126	12p	AF126	20p	BD133	75p	OC35	50p
AC127	12p	AF127	20p	BF115	25p	OC42	12p
AC128	12p	AF139	32p	BF173	20p	OC44	12p
AC131	12p	AF178	32p	BF177	28p	OC45	12p
AC132	12p	AF180	40p	BF178	32p	OC70	12p
AC176	12p	AF181	40p	BF179	32p	OC71	12p
AC187	22p	BC107	9p	BF180	32p	OC72	12p
AC188	22p	BC108	9p	BF181	32p	OC81	12p
AD140	50p	BC109	9p	BF194	15p	OC82D	12p
AD149	45p	BC147	13p	BF195	15p	2N2904	20p
AD161	33p	BC148	13p	BF197	15p	2N2926R	9p
AD162	36p	BC149	13p	BF200	32p	2N2926O	9p
AF114	20p	BC157	14p	BFY50	20p	2N2926Y	9p
AF115	20p	BC158	14p	BFY51	20p	2N2926G	10p
AF116	20p	BC159	14p	BFY52	20p		
AF117	20p	BC187	22p	BU105	225p	2N3054	58p
AF124	22p	BD131	75p	OC26	45p	2N3055	60p

2N3702	13p	ZTX302	15p
2N3703	12p	ZTX500	15p
2N3704	13p	ZTX502	20p
2N3705	12p		
2N3706	11p		
2N3707	12p		
2N3708	10p		
2N3709	11p		
2N3710	11p		
2N3711	11p		
2N4062	12p		
40360	35p		
40361	35p		
40362	40p		
40408	40p		

ZENER DIODES

400mW 5% 3·3V to 30V, **12p**.

WIRE WOUND POTS, 3W, 10, 25, 50Ω and decades to 100kΩ, 35p.

DIODES

RECTIFIER

BY127	1250V	1A	12p
BZY10	800V	6A	25p
BZY13	200V	6A	20p
IN4001	50V	1A	7p
IN4004	400V	1A	8p
IN4007	1000V	1A	10p

SIGNAL

OA85	7p
OA90	5p
OA91	5p
OA202	7p
IN4148	5p
BA114	8p

BRUSHED ALUMINIUM PANELS

12in × 6in=**25p**; 12in × 2½in=**10p**; 9in × 2in=**7p**

SLIDER POTENTIOMETERS

86mm × 9mm × 16mm, length of track 59mm.
SINGLE 10K, 25K, 100K log. or lin. **40p**.
DUAL GANG, 10K + 10K etc. log. or lin. **60p**.
KNOB FOR ABOVE **12p**.
FRONT PANEL **65p**.
18 Gauge panel 12in × 4in with slots cut for use with slider pots. Grey or matt black finish complete with fixings for 4 pots.

THERMISTORS

VA1055S	15p
VA1066S	15p
VA1077	15p
R53	£1·35

THYRISTORS

2N5060 50V 0·8A **30p**, 2N5064 200V 0·8A **47p**, CRS1/40 400V 1A **25p**, 106F 50V 4A **40p**, 106D 400V 4A **55p**.

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0·001μF, 0·0015μF, 0·0022μF, 0·0033μF, 0·0047μF, **2½p**. 0·0068μF, 0·01μF, 0·015μF, 0·022μF, 0·033μF, **3p**. 0·047μF, 0·068μF, 0·1μF, **4p**. 0·15μF, **6p**. 0·22μF, **7½p**. 0·33μF, **11p**. 0·47μF, **13p**.
160V: 0·01μF, 0·015μF, 0·022μF, 0·033μF, 0·047μF, 0·068μF, **3p**. 0·1μF **3½p**. 0·15μF **4½p**. 0·22μF, **5p**. 0·33μF, **6p**. 0·47μF, **7½p**. 0·68μF, **11p**. 1·0μF, **13p**.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0·01μF, 0·015μF, 0·022μF, **3p**. 0·033μF, 0·047μF, 0·068μF, **3½p**. 0·1μF, **4p**. 0·15μF, 0·22μF, **5p**. 0·33μF, **6½p**. 0·47μF, **8½p**. 0·68μF, **11p**. 1·0μF, **13p**. 1·5μF, **20p**. 2·2μF, **24p**.

MYLAR FILM CAPACITORS 100V

0·001μF, 0·002μF, 0·005μF, 0·01μF, 0·02μF, **2½p**. 0·04μF, 0·05μF, 0·068μF, 0·1μF, **3½p**.

CERAMIC DISC CAPACITORS

100pF to 10,000pF, **2p** each.

ELECTROLYTIC CAPACITORS—MULLARD 015/6/7 RANGE REPLACES C426, C457 RANGES.

(μF/v) 1·0/63, 1·5/63, 2·2/63, 3·3/63, 4·7/63, 6·8/40, 10/25, 10/63, 15/16, 15/40, 15/63, 22/10, 22/25, 22/63, 33/6·3, 33/40, 47/4, 47/10, 47/25, 47/40, 47/63, 68/6·3, 68/16, 100/4, 100/10, 100/25, 100/40, 150/6·3, 150/16, 150/25, 220/4, 220/10, 220/16, 330/4, 330/10, 470/6·3, **5p** each. 68/63, 150/40, 220/25, 330/16, 470/10, 680/6·3, 1,000/4, **9p**. 100/63, 150/63, 220/40, 470/25, 680/16, 1,000/10, 1,500/6·3, **12p**. 220/63, 470/40, 680/25, 1,000/16, 1,500/10, 2,200/6·3, **15p**. 330/63, 680/40, 1,000/25, 1,500/16, 2,200/10, 3,300/6·3, 4,700/4, **18p**.

SOLID TANTALUM BEAD CAPACITORS 12p

0·1μF	35V	2·2μF	35V	22μF	16V
0·22μF	35V	4·7μF	35V	33μF	10V
0·47μF	35V	6·8μF	25V	47μF	6·3V
1·0μF	35V	10μF	25V	100μF	3V

VEROBOARD

	0·1	0·15
2½ × 3½	22p	16p
2½ × 5	24p	24p
3½ × 3½	24p	24p
3½ × 5	27p	27p
17 × 2½	75p	57½p
17 × 3½	100p	78p
17 × 5 (plain)	—	82p
17 × 3½ (plain)	—	60p
17 × 2½ (plain)	—	42p
2½ × 5 (plain)	—	12p
2½ × 3½ (plain)	—	11p
Pin insertion tool		52p
Spot face cutter		42p
Pkt. 50 pins		20p

JACK PLUGS AND SOCKETS

Standard screened	18p	2·5mm insulated	8p
Standard insulated	12p	3·5mm insulated	8p
Stereo screened	35p	3·5mm screened	13p
Standard socket	15p	2·5mm socket	8p
Stereo socket	18p	3·5mm socket	8p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°. 6 pin
Plug 12p. Socket 8p.
4 way screened cable, 15p/metre.
6 way screened cable **22p**/metre.

BATTERY ELIMINATOR £1·50

9V mains power supply. Same size as PP9 battery.

LARGE (CAN) ELECTROLYTICS

1600μF	64V	74p	2500μF	64V	80p	4500μF	16V	50p
2500μF	40V	74p	2800μF	100V	£2·60	4500μF	25V	£1·68
2500μF	50V	58p	3200μF	16V	50p	5000μF	50V	£1·10

HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0·01μF	10p	0·047μF	13p	0·22μF	20p
0·022μF	12p	0·1μF	13p	0·47μF	22p

POLYSTYRENE CAPACITORS 160V 2½%

10pF to 1,000pF E12 Series Values **4p each.**

SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs deoxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector.
Detector GDI, **£2**. Kit of parts for detectors including GDI and P.C. board but excluding case. Mains operated detector **£5·20**. 12 or 24V battery operated audible alarm **£7·30**. As above for PP9 battery, **£6·40**.

PRINTED BOARD MARKER 97p

Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to dry, and immerse the board in the etchant. On removal the circuit remains in high relief.

LARGE RANGE ITT/TEXAS IC's NOW IN STOCK

PRICES ARE CALCULATED ON TOTAL NUMBER ORDERED REGARDLESS OF MIX

	1–11 p.	12–24 p	25–99 p	100+ p
7400	18	16	14	13
7401	18	16	14	13
7402	18	16	14	13
7403	18	16	14	13
7404	20	18	16	14
7405	20	18	16	14
7406	50	45	40	35
7407	56	50	44	38
7408	36	30	27	23
7409	36	30	27	33
7410	18	16	14	13
7411	23	21	20	18
7412	36	30	27	23
7413	34	28	26	22
7416	45	43	39	34
7420	18	16	14	13
7421	36	30	27	23
7426	32	29	23	20
7430	20	18	16	14
7432	40	36	32	28
7440	20	18	16	14
7441	80	75	70	65
7442	80	75	70	65
7443	125	120	115	115
7447	175	165	150	120
7448	185	175	170	165
7450	18	16	14	13
7451	18	16	14	13
7453	18	16	14	13
7454	18	16	14	13
7460	18	16	14	13
7470	30	28	25	24
7472	30	28	27	23
7473	40	38	36	30
7474	40	36	32	28
7475	55	52	50	49
7476	40	36	32	30
7480	100	95	90	85
7481	125	115	110	105
7482	100	96	90	85
7483	100	97	95	92
7484	120	115	110	105
7485	250	245	240	230
7486	45	42	37	33
7490	75	67	60	52
7491A	100	92	85	79
7492	75	70	65	60
7493	75	68	60	52
7494	95	90	85	80
7495	105	100	95	90
7496	100	95	90	85
74100	250	240	235	230
74118	100	82	73	64
74121	43	40	38	36
74141	100	95	90	85
74145	150	140	135	130
74150	330	280	250	220
74151	110	100	95	89
74153	120	110	105	95
74154	200	180	170	160
74155	150	120	100	86
74156	130	120	100	96
74180	155	136	112	105
74190	195	190	185	180
74191	195	190	185	180
74192	200	190	180	164
74193	200	180	170	150
74196	200	190	180	170
74197	200	195	180	170

LINEAR IC's

709	14 pin DIL	32p
741	8 pin DIL	34p
741	14 pin DIL	28p
723	14 pin DIL	95p
747	14 pin DIL	85p
748	8 pin DIL	35p
DIL socket,	14 pin and 16 pin	16p



MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at **72p**. Postage 20p for first one then 10p for each one ordered.

MUSIC ON TAPE

A further buy enables us to offer these at an even lower price—namely **65p** each or 5 for **£2·50**. Send for list of titles. We can't repeat when sold out.

BALANCED ARMATURE UNIT



500 ohm, operates as speaker or microphone, so useful in intercom or similar circuits, **37p** each, 10 for **£3·76**.



CAR ELECTRIC PLUG

Fits in place of cigarette lighter. Useful method for making a quick connection into the car electrical system, **38p** each or 10 for **£3·42**.



12 VOLT 1½ AMP POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mF smoothing. Price **£2·20**, plus 20p post & packing.

Heavy Duty Mains Power Pack. Output voltage adjustable from 15·40V in steps—maximum load 250W—that is from 6 amp at 40V to 15amp at 15V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—simply interchange push on leads. Silicon rectifiers and smoothing by 3,000mF. Price **£6·33** plus 65p post.

MAINS RELAY BARGAIN



Special this month are some single, double and treble pole changeover relays. Contacts rated at 15 amps. Operating coil wound for 240V A.C. Good British Make. Unused. Size approx. 1¼" × 1". Open construction.

Single pole **28p** each — 10 for **£2·48**.
Treble pole **39p** each — 10 for **£3·57**.



MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at **22p** each.

CONNECTING WIRE

7·0076 Copper conductors. 500 metre drums available in the following colours: Red/Brown, Yellow, Green/Grey, Blue/Green, Red/Orange, Green/White, Grey/White, Blue/Orange, Brown/Red, Brown/White, Red/Grey, Blue/Grey, Blue/Brown. Price **£2·20** per drum plus 40p post. State alternative colours. *Ditto*—but with 200 metres. Price **£1·38** per drum plus 20p. *Ditto*—but with 100 metres. Price **83p** per drum.

DOOR SWITCH

As fitted to refrigerators, etc. Switches off as door closes. White **17p** each. Black **15p** each.

GOODMANS P.M. SPEAKERS

8in × 5in hi flux 15 ohm coil very suitable for use with Mullard Unilex stereo amplifier or with the EP9000 on its own, **£1·65** plus 20p post each.

7in × 4in also 15 ohm and suitable for use with the EP9000—not quite such good quality of course. Price **£1·05** each.

U.V. LIGHTING

Useful for flaw detection in metals and for looking for water marks, etc., also for fitting over tropical fish tanks—African violets and other indoor plants which must have U.V. for healthy growth. The outfit comprises of a 12in U.V. tube—choke—starter holder and tube ends. Price **£2·20** plus 20p post.

SOIL HEATING KIT



Suitable for garden frame or propogating shelf, etc. Comprises 40W mains transformer, heating wire, connection strip and insulated wire with connection diagram. **£1·65** plus 20p post.

80 WATT TUBULAR ELEMENTS

Brass encased with beaded flex ends. Standard replacements in most absorbtion type refrigerators but also has dozens of other uses. **28p** each or 10 for **£1·48**.

DOUBLE ENDED MAINS MOTOR



This is a very quiet running induction motor, with two special features—one is that it has feet for easy fixing and the other is it has a good length of spindle coming from each end. So it could drive two things at once—or with simple slide attachment could reverse direction. **55p** each or 10 for **£4·95**.




MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied.

Model 1153 500mW power output **73p**.
Model 1172 750mW power output **94p**.
Model EP9000 4 watt power output **£1·60**.
EP9001 twin channel or stereo pre amp. **£1·92**.
10% discount if 10 or more ordered.

CENTRIFUGAL BLOWER

Miniature mains driven blower centrifugal type blower unit by Woods. Powerful but specially built for quiet running—driven by cushioned induction motor with specially built low noise bearings. Overall size 4½" × 4½" × 4". When mounted by flange, air is blown into the equipment but to suck air out, mount it from centre using clamp. Ideal for cooling electrical equipment or fitting into a cooker hood, film drying cabinet or for removing flux smoke when soldering etc. etc. A real bargain at **£2·05**.

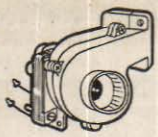



GOOD COMPANION I.C. VERSION

We can now offer these again in I.C. version using Ferranti ZN414 and Mullard AF Module 1172. Cabinet size approx. 11in wide × 8in high × 3in deep. Complete assembly instruction—Excellent tone wood cabinet **£5·75** plus 25p post and insurance.

MIGHTY MIDGET

Probably the tiniest possible radio, as described in Practical Wireless, 4 January 73. All electronic parts **£2·20** post paid.

THIS MONTH'S SNIP


HORSTMANN 24-HOUR TIME SWITCH

With six position programmer. When fitted to hot water systems this could programme as follows:

Programme	Hot Water	Central Heating
0	Off	Off
1	Twice daily	Off
2	All day	Off
3	Twice daily	Twice daily
4	All day	All day
5	Continuously	Continuously




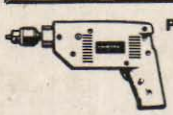Suitable of course, to programme other than central heating and hot water, for instance, programme upstairs and downstairs electric heating or heating and cooling or taped music and radio. In fact there is no limit to the versatility of this Programmer. Mains operated—Size: 3in × 3in × 2in deep. Price **£3·85** each. As illustrated but less case.



PORTABLE ELECTRIC DRILL

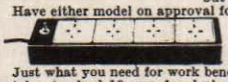Very superior quality made by a famous Dutch Toolmaker. Model No. ASM830. 300W—2 speed 2,200/3,000. With ⅜in chuck and chuck key, also separate side handle and hammer facility for dealing with concrete, etc. An equivalent British made drill would cost **£15**. **£10·90**—similar model but without the hammer attachment **£8·75**. Have either model on approval for 7 days.



DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 × 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work, **£2·50** plus 20p post and insurance.

CAPACITOR DISCHARGE CAR IGNITION



This system which has proved to be amazingly efficient and reliable was first described in the *Wireless World* about a year ago. We can supply kit of parts for an improved and even more efficient version (*Practical Wireless*, June). Price **£6·55** plus 20p post. When ordering please state whether for positive or negative systems. De-luxe model including printed circuit board, etc. **£7·65**.



24-HOUR TIME SWITCH

Made by Smiths, these are A.C. mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable time periods per 24 hours, 5A changeover contacts will switch circuit on or off during these periods. **£2·75** post and ins. 25p. Additional time contacts **55p** pair.

THYRISTOR LIGHT DIMMER



For any lamp up to 1kw. Mounted on switch plate to fit in place of standard switch. Virtually no radio interference. Price **£2·95**, plus 20p post and insurance. Industrial model 5A **£3·30**.



BATTERY CONDITION TESTER

Made by Mallory but suitable for all batteries made by Ever Ready and others, most of which are zinc carbon types but also mercury manganese—nicad—silver oxide and alkaline batteries may be tested. The tester puts a dummy load on the battery and the meter scale indicates the condition depending upon which section the pointer rests. The section reads "replace" "weak" or "good". The tester is complete in its case, size 3½" × 6½" × 2" with leads and prods. Price **£2·48** plus 20p postage.



SPIT MOTOR

200-250V Induction Motor, driving a Carter gear box with 1¼" of output drive shaft running at 5 revs per minute. Intended for roasting chickens also suitable for driving models—windmills, coloured disc lighting effect, etc. etc. **£2·04** plus 20p post and insurance.



DRILL CONTROLLER

NEW IKW MODEL

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. **£1·65**. Made up model also available. **£2·75**.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor condensers and instructions. Real snip only **£1·10**.

SWITCH TRIGGER MATS




So thin is undetectable under carpet but will switch on with slightest pressure. For burglar alarms, shop doors, etc.

24in × 18in **£1·54**.
13in × 10in **£1·10**.

PP3 BATTERY CHARGER

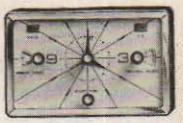Almost 3 times the life can be obtained from PP3 battery if you re-charge it from the mains—this ready to use charger with instructions only **55p**.



15A ELECTRICAL PROGRAMMER

Learn in your sleep: Have radio playing and kettle boiling as you awake—switch on lights to ward off intruders — have a warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp. on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price **£2·15** + 20p p. & p. or with glass front chrome bezel **83p** extra.

BAKELITE INSTRUMENT CASE



Size approx. 6¼"×3¼"×2" deep with brass inserts in four corners and bakelite panel. This is a very strong case suitable to house instruments and special rigs, etc. Price. **50p** each.
Paxolin lid **11p** extra.

ROCKER SWITCH



13 amp self-fixing into an oblong hole. Size approximately 1" × ½" **9p** each, 10 for **81p**.

THERMAL CUTOUT

A miniature device ⅛in dia. on one screw fixing mount—can be used for motor overload protection, fire alarm, soldering iron, switch off, etc., etc. 15 amp contacts open with flame—radiant or conducted heat. **11p** each or 10 for **99p**.

HONEYWELL PUSH BUTTON MICRO SWITCHES

As used in some vending machines, etc. Each switch is a changeover type rated at 15A 250V a.c. Intended for panel mounting with fixing nuts and single black push knob. Single changeover switch **28p**, Double switch **42p**, Triple switch **61p**.

KETTLE ELEMENTS

Made by the famous A.E.I. Co. Complete with washers and combined fixing ring and plug shroud. Normal 2 round pin and flat pin earth connection and overload reset push button. 2 Models—1⅛in (approx.) suitable for 8wan and other similar models—1⅛in (approx.) suitable for G.E.C. Hotpoint, etc. All quick boil 2¾kW elements at 240V. Price **£1·38** each.

MAINS TRANSFORMER BARGAIN

Standard mains 240V input Secondary 2·4V 9A intermittent 5A continuous. Price **55p**.

BULGIN 4 PIN PLUG AND SOCKET

Plug has shielded pin and flex entry and socket for panel mounting. **33p** per pair. *Ditto*—but 3 pin, **22p** per pair.

MACLAREN THERMOSTAT

Make and break 20A a.c. with the sensor probe coupled by 2 feet capillary covering range of 10–100°C—complete with large engraved control knob. Price **83p**.

Where postage is not stated then orders over £5 are post free. Below £5 add 20p. Semiconductors add 5p post. Over £1 post free. S.A.E. with enquiries please.

J. BULL (ELECTRICAL) LTD.

(Dept. P.E.), 7 Park Street, Croydon CRO 1YD

Callers to 102/3 Tamworth Road, Croydon

Sinclair Project 60

Now—the Z.50 Mk.2

with built-in automatic transient overload protection


When originally introduced, the Sinclair Z.50 proved how it was possible to design and produce a popularly priced modular power amplifier having characteristics to challenge the world's costliest amplifiers. Many thousands of Z.50's are now giving excellent service day in, day out. But we have also learned that constructors do not always use their Z.50's ideally. That is why we have introduced modifications whereby risk of damage through mis-use is greatly reduced and performance further enhanced. The Z.50 Mk.2 has improved thermal stability, more accurately regulated D.C. limiting to ensure more symetrical output voltage swing and clipping and still less distortion at lower power. Z.50 Mk.2 is compatible with all other Project 60 modules, and may be incorporated to advantage in existing systems. Eleven silicon epitaxial planar transistors are now used, two more than in the original Z.50; circuitry has been re-designed, making this versatile high performance amplifier better than ever.



with free manual

£5.48

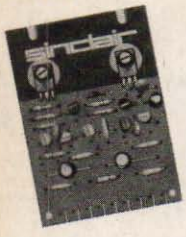Z.30 the power amplifier for quality and economy




with free manual

£4.48

The Z.30 provides excellent facilities for the constructor requiring a high fidelity audio system of less power than that available from Z.50's. Using a power supply of 35 volts, Z.30 will deliver 15 watts RMS into 8 ohms, or 20 watts RMS into 3 ohms using 30 volts. Total harmonic distortion is a fantastically low 0.02% at 15 watts into 8 ohms with signal to noise ratio better than 70 dB unweighted. Input sensitivity 250mV into 100K ohms. Size 80 x 57 x 13 mm ($3\frac{1}{8}$ x $2\frac{1}{4}$ x $\frac{1}{2}$) Z.30, Z.50 and Z.50 MK.2 modules are compatible and interchangeable.

Brilliant new technical specifications

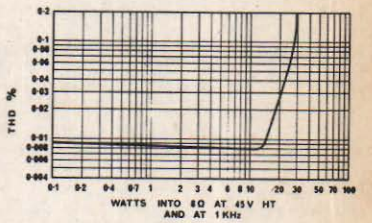Input impedance 100 KΩ
Input (for 30w into 8Ω) 400mV
Signal to noise ratio, referred to full o/p at 30v HT 80dB or better
Distortion 0.02% up to 20W at 8Ω. See curve
Frequency response 10Hz to more than 200 KHz ±1dB
Max. supply voltage 45v (4Ω to 8Ω speakers) (50v 15Ω speakers only)
Min. supply voltage 9v
Load impedance – minimum : 4Ω at 45v HT
Load impedance – maximum : safe on open circuit



Typical Project 60 applications

System	The Units to use	together with	Units cost
Simple battery record player	**Z.30**	Crystal P.U., 12V battery volume control, etc.	**£4.48**
Mains powered record player	**Z.30, PZ.5**	Crystal or ceramic P.U. volume control, etc.	**£9.45**
12W. RMS continuous sine wave stereo amp. for average needs	**2 x Z.30s, Stereo 60; PZ.5**	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	**£23.90**
25W. RMS continuous sine wave stereo amp. using low efficiency (high performance) speakers	**2 x Z.30s, Stereo 60; PZ.6**	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	**£26.90**
80W. (3 ohms) RMS continuous sine wave de luxe stereo amplifier. (60W. RMS into 8 ohms)	**2 x Z.50s, Stereo 60; PZ.8, mains transformer**	As above	**£34.88**
Indoor P.A.	**Z.50, PZ.8, mains transformer**	Mic., guitar, speakers, etc., controls	**£19.43**

F.M. Stereo Tuner **(£25)** & A.F.U. **(£5.98)** may be added as required.

Guarantee

If, within 3 months of purchasing any product direct from Sinclair Radionics Ltd., you are dissatisfied with it, your money will be refunded at once. Many Sinclair appointed Stockists also offer this same guarantee in co-operation with Sinclair Radionics Ltd.

Each Project 60 module is tested before leaving our factory and is guaranteed to work perfectly. Should any defect arise in normal use, we will service it at once and without any charge to you, if it is returned within two years from the date of purchase. Outside this period of guarantee a small charge (typically £1.00) will be made. No charge is made for postage by surface mail. Air Mail is charged at cost.

sinclair

Sinclair Radionics Ltd., R.O. London Rd., St. Ives, Huntingdonshire PE17 4HJ (Phone: St. Ives 64311). Regd. Bus. No. England 699483.

the world's most advanced high fidelity modules

Stereo 60 Pre-amp/control unit



Designed specifically for use on Project 60 systems, the Stereo 60 is equally suitable for use with any high quality power amplifier. Since silicon epitaxial planar transistors are used throughout, a really high signal-to-noise ratio and excellent tracking between channels is achieved. Input selection is by means of press buttons, with accurate equalisation on all input channels. The Stereo 60 is particularly easy to mount.

SPECIFICATIONS—Input sensitivities: Radio – up to 3mV. Mag. p.u. 3mV: correct to R.I.A.A. curve ±1dB :20 to 25,000 Hz. Ceramic p.u. – up to 3mV : Aux – up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE +12 to —12dB at 10KHz : BASS +12 to —12dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.

Built, tested and guaranteed. **£9.98**

Project 60 Stereo F.M. Tuner




The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other advanced features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stero decoder and switchable squelch circuit for silent tuning between stations. In terms of high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with most other high fidelity systems.

SPECIFICATIONS—Number of transistors: 16 plus 20 in I.C. **Tuning range:** 87.5 to 108MHz. **Sensitivity:** 7μV for lock-in over full deviation. **Squelch level:** Typically 20μV. **Signal to noise ratio:** >65dB. **Audio frequency response:** 10Hz – 15KHz (±1dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2μV. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. maximum **Operating voltage:** 25–30VDC. **Indicators:** Stereo on ; tuning. **Size:** 93 x 40 x 207mm.

Built and tested. Post free. **£25**

Super IC.12

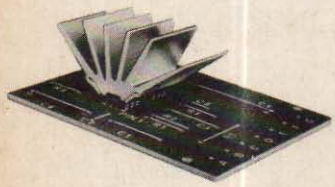Integrated circuit high fidelity amplifier



Having introduced Integrated Circuits to hi-fi constructors with the IC.10, the first time an IC had ever been made available for such purposes, we have followed it with an even more efficient version, the Super IC.12, a most exciting advance over our original unit. This needs very few external resistors and capacitors to make an astonishingly good high fidelity amplifier for use with pick-up, F.M. radio or small P.A. set up, etc. The free 40 page manual supplied, details many other applications which this remarkable IC. make possible. It is the equivalent of a 22 transistor circuit contained within a 16 lead DIL package, and the finned heat sink is sufficient for all requirements. The Super IC.12 is compatible with Project 60 modules which would be used with the Z.50 and Z.30 amplifiers. Complete with free manual and printed circuit board.

SPECIFICATIONS

Output power: 6 watts RMS continuous (12 watts peak). 6–8Ω. **Frequency Response:** 5Hz to 100KHz ±1dB. **Total Harmonic Distortion:** Less than 1%. (Typical 0·1%) at all output powers and frequencies in the audio band (28V). **Load Impedance:** 3 to 15 ohms. **Input Impedance:** 250 Kohms nominal. **Power Gain:** 90dB (1,000,000,000 times) after feedback. **Supply Voltage:** 6 to 28V. **Quiescent current:** 8mA at 28V. **Size:** 22 × 45 × 28mm including pins and heat sink..

Manual available separately 15p post free.

With FREE printed circuit board and 40 page manual.

£2.98 Post free

Power Supply Units
The new PZ.8 Mk.3



The most reliable power supply unit ever made available to constructors. Brilliant circuitry makes failure from over load and even direct shorting of the output impossible. This is due to an ingenious re-entrant current limiting principle which, as far as we know has never before been available in any comparable unit outside the most expensive laboratory equipment. Ripple and residual noise have been reduced to the point of almost total elimination. This is, of course, the perfect unit for Project 60 assemblies, particularly where the new Z.50 MK.2 amplifiers are used. Nominal working voltage – 45.

PZ.8 Mk.3—£7.98
(Mains transformer, if required) £5.98
PZ.5 30v. unstabilised
(not suitable for Project 60 tuner) **£4.98**
PZ.6 35v. stabilised
(not suitable for IC. 12) **£7.98**

Project 605



the easy way to buy and build Project 60 without soldering

Project 605 in one pack contains : one PZ.5, two Z.30's, one Stereo 60 and one Masterlink, which has input sockets and output components grouped on a single module and all necessary leads cut to length and fitted with clips to plug straight on to the modules thus eliminating all soldering.

Complete with comprehensive manual, post free **£29.95**
All you need for a superb 30 watt high fidelity stereo amplifier

Order form

Please send

I enclose cash/cheque/money order.

Name

Address

PE/7/73

SINCLAIR RADIONICS LTD., LONDON ROAD
ST. IVES, HUNTINGDONSHIRE PE17 4HJ

sinclair

Add 10% V.A.T. to all prices quoted on page opposite and above

MAPLIN ELECTRONIC SUPPLIES

★RETURN OF POST SERVICE



This beautifully produced fully illustrated catalogue is yours for the asking. Absolutely free, no obligation. Write now for your copy or phone 037-42 79033 Out of office hours please leave your name and address on our answering machine.

EVERYTHING GUARANTEED BRAND NEW MARKED BY THE MANUFACTURER



MAPLIN: Projected site of London's third airport.

RESISTORS
Carbon film 5% from 1Ω to 1MΩ, 10% from 1·2MΩ to 10MΩ. E12 series, ¼W 1p; ½W 1·2p.
Metal Oxide 2% 10Ω to 1MΩ. E24 series ¼W 4p.
Also 1W, 2½W, 5W, 10W types stocked.

7 SEGMENT DISPLAY
Minitron 3015F
£1·98 each.

POTENTIOMETERS
Miniature carbon track with ¼in. spindles. 5kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, 2MΩ.
Log or lin (and 1kΩ lin), **12p.**
Log or lin with switch **23p.**
Dual gang less switch **38p.**

P.E. SOUND SYNTHESISER

If this project seems expensive YOU HAVEN'T SEEN OUR PRICES!

We shall be stocking all the parts for this exciting project, from the special I.C.'s right down to the nuts, bolts and spacers for mounting the Veroboards.

Send S.A.E. NOW for our detailed price lists.

YOU SIMPLY **MUST** SEE OUR PRICES!

741C
8 pin DIL OP AMP PRICE REDUCED ON THESE TOP QUALITY I.C.s **36p.**

McMURDO
Socket, RS8, **52p**
Plug, RP8, **36p.**
(As used in P.E. Sound Synthesiser.)

SEMI-CONDUCTORS
We stock a large range of transistors and I.C.s, for details please see our free catalogue. LOOK! These popular devices at amazingly low prices. BC107/8/9 10p each. BC169C 12p. BFY51 16p. TIS43 (SS43) 28p. 2N706 10p. 2N2646 45p. 2N3055 49p. 2N3819 24p.

DIN PLUGS. 3 pin, **9p.** 5 pin A (180°), 5 pin B (240°), **10p** each.

DIN SOCKETS. 3 pin, 5 pin A, 5 pin B, **7p** each.

DIN LOUDSPEAKER. 2 pin plug, **8p.** Socket **6p.**

JACK PLUGS standard ¼in plastic barrel, **13p.** Stereo, **25p.** Bright metal barrel, **17p.** Stereo, **29p.**

ROTARY SWITCHES
Adjustable stop. 1 pole 2-12 way, 2 pole 2-6 way, 3 pole 2-4 way, 4 pole 2-3 way. Only **24p** each.

SPECIAL IC, for organ builders, 7 stage frequency divider in one 14 pin DIL package, **£2·63** or special price for pack of 12, **£25.**
Why not ask us to slip a data sheet in with your catalogue.

NUDES!

Clothe those naked projects with our superb instrument cases. We are sole distributors of the

Centurion

range, designed for the professional market, now available to you at special low prices. S.A.E. please for free illustrated leaflet.

HARDWARE
Wide range of nuts and bolts, plated brass and nylon types plus solder tags, shakeproof washers, etc.
SOLDER 10 metres of 22 gauge multicore, **20p.**
Insulating sleeving 3 sizes, 6 colours.

MISCELLANEOUS
LT700 Eagle sub-miniature O/P transformer 1200/5Ω 200mW max., **35p.**
Slide switch DPDT, **12p.**
Silicon grease in special dispenser, 20ml, **38p.**

SEE OUR CATALOGUE for details of how you can obtain £1 worth of components.
ABSOLUTELY FREE

V.A.T. Please add 10% V.A.T. to final total.
Orders and enquiries for catalogues to
MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex SS6 8LR

Postage and packing FREE in U.K. But we have to ask you to send a 10p handling charge with order under 50p.



ELECTRONIC ORGAN KITS

★ Portable—4 octave keyboard with 10 voices, 3 pitches—vibrato, **£145·29.** ★ Console—5 octave keyboard with 10 voices, 3 pitches. Keyboard can be split into solo and accompaniment. Vibrato, built in amplifier and speaker **£250·93.** ★ Console—2 × 4 octave keyboards and 13 note pedal board, 29 voices, Vibrato, Delay Vibrato, Sustain, Reverberation, Precussion, Wah Wah, **£406·00.** ★ Console—2 × 5 octave keyboards and 32 note pedal board, 32 voices. Vibrato, Delay Vibrato, Sustain Reverberation, Precussion, 3 Couplers, etc., at **£572·55.**

ALL COMPONENTS CAN BE BOUGHT SEPARATELY. SEND 50p FOR LATEST CATALOGUE, WHICH INCLUDES SPECIALIZED COMPONENTS, HI-FI EQUIPMENT AND ELECTRICAL HOUSEHOLD APPLIANCES.


ELVINS ELECTRONIC *MUSICAL INSTRUMENTS*

12 BRETT ROAD, LONDON, E.8
TEL. 01-986 8455

PRINTED CIRCUIT KIT

BUILD 60 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX

CONTENTS: (1) 2 Copper Laminate Boards 4¼in × 2½in. (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleanser/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs.* (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit: (10) Essential Design Data, Circuits, Chassis Plans, etc. for 60 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements.

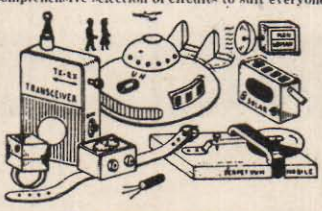

EXPERIMENTER'S PRINTED CIRCUIT KIT

70p

Postage & Pack. 10p (UK)
Commonwealth:
SURFACE MAIL 15p
AIR MAIL 60p
Australia, New Zealand, South Africa, Canada

(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photocell Radio. (8) "TRI-FLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World. 3 Subminiature Radio Receivers based on the "Triflexion" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1·6in × 0·95in × 0·25in. (11) Wristwatch Radio 1·15in × 0·80in × 0·55in. (12) Ring Radio 0·70in × 0·70in × 0·55in. (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P/P Amplifier. (16) Intercom. (17) 1-valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal, Guided Missle. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive-Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wire-less Microphone. (32) Rain Alarm. (33) Ultrasonic Switch/Alarm. (34) Stereo Pre-amplifier. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Telephone "Photophone". (37) Light-Beam Transmitter. (38) Silent TV Sound Adaptor. (39) Ultrasonic Transmitter. (40) Thyristor Drill Speed Controller. (41) Light Dimmer. (42) I.C. Pre-amplifier. (43) I.C. Amplifier. (44) I.C. Intercom. (45) I.C. Radio. (46) Raudive Voices Receiver. (47) Biofeedback Amplifier. (48) Brainwave Detector. (49) Proximity Switch. (50) Laser Projector.
Plus 10 Photoelectric Circuits, Simple Alarms, Long Range Alarms, Projector, etc.

YORK ELECTRICS, Mail Order Dept.

335 BATTERSEA PARK ROAD, LONDON, S.W.11

Send a S.A.E. for full details and a brief description of all kits and Projects.

BRAND NEW SEMICONDUCTORS AND COMPONENTS GUARANTEED

WE SUPPLY NEARLY ALL THE COMPONENTS FOR PROJECTS ADVERTISED IN THIS MAGAZINE

TRANSISTORS

2G301	0·15	2N3403	0·19	3N128	0·63	AF200	0·35	BCY31	0·40	BFX29	0·25
2G302	0·15	2N3404	0·24	3N138	1·65	AF239	0·41	BCY32	0·60	BFX30	0·25
2G303	0·25	2N3405	0·27	3N199	1·36	AF240	0·72	BCY32	0·75	BFX37	0·30
2G306	0·30	2N3414	0·10	3N140	0·92	AF279	0·54	BCY33	0·34	BFX44	0·33
2G309	0·30	2N3415	0·10	3N143	0·75	AF280	0·54	BCY34	0·35	BFX63	2·48
2G346B	0·25	2N3416	0·15	3N152	0·92	AF211	0·55	BCY39	1·05	BFX84	0·24
2G371	0·15	2N3417	0·21	3N153	0·81	AL102	0·75	BCY40	0·81	BFX85	0·29
2G374	0·15	2N3570	1·25	3N154	0·94	AL103	0·70	BCY42	0·15	BFX86	0·24
2N174	1·40	2N3571	1·12	3N159	1·17	ASY26	0·30	BCY43	0·15	BFX87	0·25
2N404	0·43	2N3572	0·97	3N187	1·30	ASY27	0·36	BCY58	0·21	BFX88	0·26
2N456	0·75	2N3702	0·10	3N200	2·49	ASY28	0·28	BCY59	0·22	BFX89	0·45
2N456A	0·75	2N3703	0·10	3N201	1·05	ASY29	0·30	BCY66	0·63	BFY10	0·35
2N457A	0·80	2N3704	0·14			ASY55	0·35	BCY67	0·94	BFY11	0·45
2N491	3·25	2N3705	0·10			ASZ21	0·55	BCY70	0·17	BFY17	0·90
2N584	0·26	2N3706	0·09	40050	0·78	AU103	1·25	BCY71	0·22	BFY18	0·25
2N696	0·15	2N3707	0·13	40251	0·81	BC107	0·14	BCY72	0·13	BFY19	0·25
2N697	0·15	2N3708	0·07	40309	0·33	BC108	0·13	BCY87	3·47	BFY20	0·50
2N698	0·25	2N3709	0·09	40310	0·59	BC109	0·14	BCY88	2·40	BFY29	0·40
2N699	0·28	2N3710	0·12	40313	0·92	BC113	0·13	BCY89	0·80	BFY37	0·20
2N706	0·10	2N3711	0·90	40316	0·50	BC114	0·12	BCZ10	0·35	BFY41	0·43
2N706A	0·12	2N3712	0·95	40318	0·92	BC115	0·15	BCZ11	0·50	BFY43	0·62
2N708	0·13	2N3713	1·08	40322	0·92	BC116	0·15	BD115	0·75	BFY50	0·16
2N709	0·88	2N3714	1·15	40360	0·46	BC116A	0·18	BD116	0·75	BFY51	0·18
2N711	0·80	2N3715	1·23	40361	0·48	BC117	0·21	BD121	0·75	BFY52	0·16
2N718	0·21	2N3716	1·30	40362	0·50	BC118	0·11	BD123	0·82	BFY53	0·15
2N718A	0·30	2N3773	2·35	43063	0·88	BC119	0·27	BD124	0·67	BFY56	0·34
2N720	0·50	2N3774	3·33	40389	0·46	BC121	0·23	BD130	0·57	BFY64	0·41
2N721	0·55	2N3775	4·19	40394	0·56	BC123	0·29	BD131	0·40	BFY75	0·40
2N914	0·22	2N3776	5·95	40395	0·50	BC125	0·15	BD132	0·50	BFY76	0·22
2N916	0·17	2N3778	2·25	40406	0·44	BC126	0·20	BD135	0·43	BFY77	0·24
2N918	0·30	2N3779	3·15	40407	0·33	BC132	0·30	BD136	0·49	BFY78	0·36
2N919	0·20	2N3780	4·50	40408	0·50	BC134	0·11	BD137	0·55	BFY90	0·60
2N929	0·14			40409	0·52	BC135	0·11	BD138	0·68	BFY39	0·35
2N930	0·14	2N3781	3·67	40410	0·53	BC136	0·15	BD139	0·71	BSX19	0·13
2N1090	0·23	2N3782	3·37	40411	2·25	BC137	0·15	BD140	0·83	BSX20	0·14
2N1091	0·24	2N3789	1·76	40414	3·55	BC138	0·20	BDY10	1·25	BSX21	0·20
2N1131	0·20	2N3790	2·20	40438	1·44	BC140	0·34	BDY11	1·50	BSX26	0·34
2N1132	0·20	2N3794	2·06	40467A	0·69	BC141	0·39	BDY17	1·50	BSX27	0·34
2N1302	0·16	2N3791	2·06	40468A	0·44	BC142	0·24	BDY18	1·75	BSX28	0·25
2N1303	0·16	2N3792	2·20	40600	0·69	BC143	0·21	BDY19	1·97	BSX29	0·47
2N1304	0·20	2N3794	0·10	40601	0·67	BC144	0·24	BDY20	0·92	BSX30	0·88
2N1305	0·20	2N3819	0·37	40602	0·46	BC145	0·21	BDY38	0·65	BSX59	0·78
2N1306	0·22	2N3820	0·47	40603	0·58	BC147	0·11	BDY60	0·90	BSX60	0·54
2N1307	0·22	2N3823	0·97	40604	0·56	BC148	0·10	BDY61	0·85	BSX61	0·42
2N1308	0·25	2N3824	0·75	40636	1·10	BC149	0·13	BDY62	0·75	BSX76	0·15
2N1309	0·25	2N3826	0·23	40673	0·50	BC153	0·18	BF115	0·23	BSX77	0·20
2N1483	0·90	2N3854	0·16	AC107	0·35	BC154	0·18	BF117	0·43	ASX78	0·25
2N1507	0·24	2N3854A	0·16	AC113	0·16	BC157	0·14	BF119	0·53	BSW70	0·28
2N1613	0·20	2N3855	0·16	AC115	0·16	BC158	0·13	BF121	0·25	BSY24	0·20
2N1631	0·35	2N3855A	0·16	AC117	0·20	BC159	0·14	BF123	0·27	BSY25	0·15
2N1637	0·30	2N3856	0·16	AC121	0·13	BC160	0·37	BF125	0·25	BSY26	0·20
2N1638	0·27	2N3856A	0·16	AC126	0·25	BC167B	0·11	BF127	0·27	BSY27	0·15
2N1701	1·10	2N3858	0·16	AC127	0·25	BC168B	0·13	BF152	0·20	BSY28	0·15
2N1702	2·15	2N3858A	0·16	AC128	0·25	BC168C	0·11	BF153	0·29	BSY38	0·15
2N1711	0·17	2N3859	0·16	AC141K	0·30	BC169B	0·13	BF154	0·16	BSY39	0·15
2N1893	0·34	2N3859A	0·16	AC142K	0·25	BC169C	0·13	BF158	0·15	BSY51	0·25
2N2102	0·30	2N3860	0·16	AC151V	0·14	BC170	0·11	BF159	0·27	BSY52	0·25
2N2147	0·70	2N3866	0·70	AC152V	0·17	BC171	0·18	BF160	0·23	BSY53	0·25
2N2148	0·60	2N3877	0·25	AC153	0·22	BC172	0·11	BF161	0·35	BSY54	0·30
2N2192	0·40	2N3877A	0·26	AC153K	0·25	BC182	0·10	BF163	0·20	BSY56	0·79
2N2192A	0·40	2N3878	1·22	AC154	0·20	BC182L	0·12	BF166	0·35	BSY65	0·15
2N2193	0·40	2N3879	1·81	AC176	0·18	BC183	0·09	BF167	0·18	BSY78	0·40
2N2193A	0·42	2N3900	0·20	AC187K	0·20	BC183L	0·09	BF173	0·19	BSY79	0·40
2N2194	0·27	2N3900A	0·21	AC188K	0·26	BC184	0·11	BF177	0·25	BSY790	0·45
2N2194A	0·30	2N3901	0·32			BC184L	0·11	BF178	0·25	BSY95A	0·09
2N2195	0·37	2N3903	0·20	ACY17	0·25	BC186	0·25	BF179	0·30	BU104	1·42
2N2195A	0·18	2N3904	0·17	ACY18	0·15	BC187	0·25	BF180	0·35	BU105	2·25
2N2218A	0·30	2N3905	0·21	ACY19	0·20	BC204	0·11	BF181	0·32	C111	0·53
2N2219	0·37	2N3906	0·22	ACY20	0·20	BC205	0·10	BF182	0·30	D40N3	0·55
2N2219A	0·51	2N4036	0·63	ACY21	0·18	BC206	0·11	BF183	0·40	GET111	0·45
2N2220	0·20	2N4037	0·42	ACY22	0·13	BC207	0·10	BF184	0·17	GET113	0·20
2N2221	0·20	2N4058	0·16	ACY28	0·18	BC208	0·09	BF185	0·17	GET114	0·20
2N2221A	0·33	2N4059	0·09	ACY30	0·42	BC209	0·10	BF194	0·14	GET115	0·50
2N2222	0·31	2N4060	0·11	ACY39	0·55	BC211	0·30	BF195	0·15	GET119	0·35
2N2222A	0·41	2N4061	0·11	ACY40	0·17	BC212K	0·10	BF196	0·15	GET120	0·25
2N2368	0·11	2N4062	0·11	ACY41	0·17	BC212L	0·16	BF197	0·15	GET535	0·20
2N2369	0·39	2N4302	0·25	ACY44	0·31	BC214L	0·23	BF198	0·15	GET536	0·20
2N2369A	0·17	2N4303	0·32	AD136V	0·96	BC236	0·16	BF199	0·18	GET538	0·20
2N2646	0·50	2N4913	0·80	AD140	0·50	BC237	0·09	BF200	0·35	GET873	0·12
2N2647	1·20	2N4914	0·87	AD140	0·55	BC238	0·09	BF224J	0·14	GET880	0·30
2N2711	0·12	2N4915	0·95	AD142	0·50	BC239	0·09	BF225J	0·19	GET883	0·20
2N2712	0·12	2N4916	0·20	AD143	0·45	BC251	0·20	BF237	0·22	GET887	0·20
2N2713	0·17	2N4917	0·17	AD149V	0·66	BC253	0·23	BF238	0·22	GET890	0·22
2N2714	0·17	2N4918	0·50	AD149V	1·26	BC257	0·09	BF244	0·15	GET895	0·25
2N2904	0·18	2N4919	0·53	AD150	0·63	BC258	0·09	BF245	0·33	TIP29A	0·49
2N2904A	0·25	2N4920	0·60	AD161	0·49	BC259	0·13	BF246	0·43	TIP30A	0·53
2N2905	0·26	2N4921	0·50	AD162	0·51	BC261	0·20	BF247	0·49	TIP31A	0·62
2N2905A	0·23	2N4922	0·55	AD161 }	PR	BC262	0·18	BF254	0·14	TIP32A	0·74
2N2906	0·18	2N4923	0·60	AD162 }	1·15	BC263	0·28	BF255	0·15	TIP33A	1·01
2N2906A	0·23	2N4926	0·90	ADZ11	1·50	BC300	0·42	BF257	0·47	TIP34A	1·51
2N2907	0·18	2N4927	1·00	ADZ12	1·75	BC302	0·27	BF258	0·53	TIP35A	2·90
2N2907A	0·25	2N4928	1·80	AF106	0·27	BC303	0·54	BF259	0·48	TIP36A	3·70
2N2923	0·12	2N4929	2·23	AF109R	0·40	BC304	0·43	BF261	0·23	TIP41A	0·79
2N2924	0·12	2N4930	2·25	AF114	0·25	BC307	0·10	BF264	1·45	TIP42A	0·90
2N2925	0·12	2N4931	2·70	AF115	0·24	BC307A	0·10	BF270	0·25	TIP2955	0·98
2N2926		2N5172	0·08	AF116	0·25	BC307VI	0·10	BF271	0·21	TIP3055	0·60
Green	0·10	2N5174	0·22	AF117	0·20	BC308	0·09	BF272	0·53		
Yellow	0·10	2N5175	0·26	AF118	0·50	BC308A	0·09	BF273	0·25		
Orange	0·10	2N5176	0·32	AF121	0·22	BC308B	0·09	BF274	0·23		
2N3053	0·31	2N5245	0·43	AF124	0·24	BC309	0·10	BF457	0·53		
2N3054	3·69	2N5190	0·92	AF125	0·20	BC309A	0·10	BF458	0·65		
2N3054	0·46	2N5191	0·96	AF126	0·19	BC309B	0·10	BF459	0·57		
2N3055	0·60	2N5192	1·24	AF127	0·20	BC313	0·30	BF821	2·10		
2N3390	0·20	2N5193	1·01	AF139	0·38	BC327	0·24	BF821A	2·30		
2N3391	0·20	2N5194	1·10	AF170	0·25	BC328	0·22	BF828	0·22		
2N3391A	0·22	2N5195	1·46	AF172	0·25	BC337	0·19	BF861	0·27		
2N3392	0·13	2N5245	0·43	AF178	0·55	BC338	0·19	BF898	0·28		
2N3393	0·12	2N5457	0·35	AF179	0·65	BC348	0·22	BFW10	0·61		
2N3394	0·17	2N5458	0·33	AF180	0·50	BC349	0·19	BFW11	0·61		
2N3402	0·12	2N5459	0·33	AF186	0·40	BCY30	0·35	BFW15	0·35		
								BFX13	0·23		

RETURN OF POST SERVICE

Post and Packing 13p per order. Europe 25p. Commonwealth (Air) 65p (MIN.). Matching charge (audio transistors only) 15p extra per pair. Prices subject to stock availability.

TTL LOGIC I.C.'s

We stock the full range of the low number 8N7400 series—some examples:

SN7400	0·20	SN7401	0·20	SN7402	0·20
SN7403	0·20	SN7404	0·22	SN7420	0·20
SN7447	1·30	SN7472	0·36	SN7493	0·75

We also stock the unusual numbers as follows:

SN74100	2·50	SN74153	1·53	SN74176	1·50
SN74107	0·43	SN74154	2·00	SN74180	1·55
SN74118	1·00	SN74155	1·55	SN74181	7·00
SN74119	1·92	SN74157	1·80	SN74190	1·95
SN74121	0·60	SN74160	2·60	SN74191	1·95
SN74122	1·35	SN74161	2·60	SN74192	1·90
SN74123	1·35	SN74164	2·26	SN74193	1·90
SN74141	0·90	SN74165	4·00	SN74196	1·60
SN74145	1·50	SN74167	6·25	SN74198	4·60
SN74150	3·35	SN74174	2·00	SN74199	4·00
SN74151	1·10	SN74175	1·35		

FM multiplex stereo demodulator MC1304 £3·60
Dual monolithic stereo preamplifier MC1303 £2·70

SILICON RECTIFIERS

PIV	50	100	200	400	600	800	1000	1200
1A	8p	9p	10p	11p	12p	15p	20p	—
3A	15p	17p	20p	22½p	25p	27p	30p	35p
6A	—	—	25p	30p	32½p	35p	—	—
10A	30p	35p	40p	47p	58p	66p	75p	—
15A	36p	45p	48p	55p	65p	75p	87p	—
35A	70p	80p	90p	£1·00	£1·40	£1·70	£2·75	—

1 amp and 3 amp are plastic encapsulation.

NE555 TIMER I.C. 90p. AS DESCRIBED IN THIS ISSUE.

NE560 phase locked loop, £4·48.
SCORPIO IGNITION KIT for improved performance £10 + 50p P. & P.

MONTHLY NEWS FEATURE

1. NEW HEAD OFFICE: 42 CRICKLEWOOD BROADWAY, N.W.2
2. 65 BATH STREET, GLASGOW. Tel. 041-332 4133.
3. NEW OFFICE OPENING BRISTOL. WATCH THIS SPACE.
4. WE NOW OFFER R.C.A. COSMOS I.C's.

DIODES AND RECTIFIERS

IN34A	10p	AA119	7p	BAX16	12½p	FST3/4	22½p
1N914	7p	AA129	15p	BAY18	17½p	OA5	17p
IN916	7p	AAZ13	12p	BAY31	7p	OA10	20p
IN4007	20p	AAZ15	12p	BAY38	25p	OA9	10p
1844	7p	AAZ17	10p	BY100	15p	OA47	8p
IS113	15p	BA100	15p	BY103	22p	OA70	7p
IS120	12p	BA102	25p	BY122	47½p	OA73	10p
IS121	14p	BA110	25p	BY124	15p	OA79	7p
IS130	8p	BA114	15p	BY126	15p	OA81	8p
IS131	10p	BA115	7p	BY127	17p	OA82	10p
IS132	12p	BA141	17p	BY161	57p	OA90	7p
IS920	7p	BA142	17p	BYX10	22p	OA91	7p
IS922	8p	BA144	12p	BYZ10	35p	OA93	7p
IS923	12p	BA145	17p	BYZ11	32p	OA200	7p
IS940	5p	BA154	12p	BYZ12	30p	OA202	10p
		BAX13	5p	BYZ13	25p	TIV307	50p

OPTOELECTRONICS

MINITRON 3015F 7-SEGMENT INDICATOR (16 PIN DIL) £2.
DRIVER SN7447 £1·80
SOCKETS 20p

TIL 209 LIGHT EMITTING DIODE. Made by TEXAS INST. (Red). 42p

B9900 PHOTORESISTOR 38p

ENCAPSULATED FULL-WAVE RECTIFIER. 1·8A 100 piv 25p ea.

WIRE-WOUND RESISTORS

2·5 watt 5% (up to 270 ohms only), 7p.
5 watt 5% (up to 8·2kΩ only), 9p.
10 watt 5% (up to 26kΩ only), 10p.

POTENTIOMETERS

Carbon:
Log. or Lin., less switch, 17½p.
Log. or Lin., with switch, 29p.
Wire-wound Pots (3W), 38p.
Twin Ganged Stereo Pots, Log. or Lin., 47p.

PRESETS (CARBON)

0·1 Watt	6p	VERTICAL
0·2 Watt	6p	OR
0·3 Watt	7½p	HORIZONTAL

SLIDE POTENTIOMETERS

58mm TRACK
SINGLE GANGED. LOG or LIN 1k to 1M. 40p each.
TWIN GANGED. LOG or LIN 1k to 500k. 60p each.

Small value
SUB-MIN. ELECTROLYTICS
wide range of values only 6p each

ALL PRICES EXCLUSIVE OF 10% VAT

Tel. 01-452 0161/2/3
Telex 21492

A. MARSHALL & SON
42 CRICKLEWOOD BROADWAY, LONDON, N.W.2

VISITORS WELCOME
HRS. 9-5.30 MON.-FRI. 9-5 SAT.

Now available from one company are kits for many of the articles published in the Electronics, Radio and TV Journals. Examples of our range are:

SCORPIO IGNITION SYSTEMS (P.E. Nov. 1971), **£9·50.** This kit includes all the parts for the assembly of this popular and reliable system. The hardware and the construction data are included.

DRILL SPEED CONTROLLER (E.E. Aug. 1972). Kit consists of resistors, rectifiers, thyristor and tag board as specified in the article, price **£1·15.** Kit with M.K. box, switch and plate included, **£2·30.**

ELECTRONIC PIANO (P.E. Sept. 1972). We can supply the various sections for this article in kit form:

Power Supply, £6·60, including all semiconductors, resistors, capacitors, transformer, heat sink and hardware less P.C.B.

Preamp and Tremelo, £3·20, complete with switches, hardware and electronic components, less P.C.B.

Main Amp., £4·20, complete with IC-12, electronic components and P.C.B.

13 Pitch Boards, £39·50. Kit contains all the resistors, capacitors and semiconductors as published, but not the P.C.B.'s or the inductor.

LIGHT DIMMER. Kit contains all parts including circuit and construction data, 480 watts, fully suppressed. Price **£2·10.**

MUSIC MAKER ELECTRONIC ORGAN (P.W. Nov. 1972). Complete kit **£4·40** or kit less resistors, P.C.B. and plastic box, **£2·80.** Stylus not supplied.

MIGHTY MIDGET (P.W. Jan. 1973). Kit contains all parts, less the battery, box and knob, **£2·25.**

TRIFFID RADIO (P.E. Feb. 1973). Kit includes all parts listed, less "tuning coil" and "miscellaneous components", **£4·95.** Ferrite rod and wire optional extra at **50p.** P.C.B. optional extra at **65p.**

We shall be offering kits for most articles published in the popular electronics magazines and will be pleased to quote prices.

Please note, prices shown do not allow for V.A.T. Please add 10% to your order.

Send for details of kits available (please enclose S.A.E.). All kits sent POST FREE within the limits of the U.K.

Please note. We reserve the right to withdraw kits without prior notification.

BARCLAYCARD welcome here

Use Access here

Electrokit

12 Lauderdale Road, London W.9.
Telephone 01-286 0011 Telex 28479

D.I.Y. TECHNICAL BOOKS

PAL RECEIVER SERVICING (280pp)	£3·50
MAKING AND REPAIRING TRANSISTOR RADIOS	£1·00
HOW TO REPAIR SMALL APPLIANCES	£1·20
TRANSISTOR RADIO SERVICING MADE EASY	£1·70
CAR RADIO SERVICING MADE EASY	£1·30
HI-FI PROJECTS FOR THE HOBBYIST	£1·00
TAPE RECORDING FOR THE HOBBYIST	£1·30
RADIO HANDBOOK (896 pp)	£6·00
ELECTRONIC EXPERIMENTS AND PROJECTS	£1·25
TRANSISTOR-TV SERVICING GUIDE	£2·25
99 WAYS TO IMPROVE YOUR HI-FI	£1·50
99 WAYS TO IMPROVE YOUR ELECT-PROJ.	£1·50
101 EASY HAM RADIO PROJECTS	£1·50
ELECTRONIC GAMES, TOYS YOU CAN BUILD	£1·40
HOW TO BUILD SPEAKER ENCLOSURES	£1·50
1-2-3-4 SERVICING STEREO AMPS.	£2·50
99 ELECTRONIC PROJECTS	£1·50
HANDBOOK OF BASIC ELECTRONIC EQUIPMENT	£1·75

Add 10% **FOR POSTAGE AND PACKING**

WHEEL (PE), **41A ADELAIDE GROVE, LONDON W12**

Build Your Own 3½ Digit D.P.M.




Miniature, all solid-state – complete kit includes M.O.S.–L.S.I. device, PCB, solid state displays, mechanics, building instructions, etc.

PRICE: DPM Kit: £36·75 includes VAT, P&P
Power Supply for DPM £8·75 includes VAT, P&P
Kits available by return.

Please send C.W.O. TO:

Integrated Photomatrix Limited,
The Grove Trading Estate, Dorchester, Dorset DT1 1SY

RAYMER MICROCHIP RE500

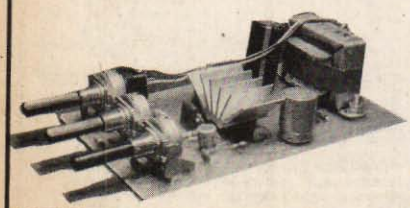

SPECIFICATIONS

OUTPUT 5W RMS (10W peak)
FREQUENCY RESPONSE 10Hz to 50kHz ± 3dB
TOTAL HARMONIC DISTORTION less than 1%

LOAD IMPEDANCE 4 to 16 ohms
INPUT IMPEDANCE 100kΩ nominal
POWER GAIN 40dB typical
SIZE 140mm × 80mm × 45mm
With free instruction sheet
PRICE £6·93 (inc. VAT) + 25p P. & P.

Guaranteed 12 months against failure in normal use. This advanced high-fidelity integrated amplifier is completely self-contained and only requires connecting to mains, speaker and input.
Ideally suited for:
MONO RECORD PLAYERS
MONO CONVERSION TO STEREO
STEREO CONVERSION TO QUADRAPHONIC (× 2 Microchip + Decoder)
TV AMPLIFIER
TAPE AMPLIFIER

PA INSTALLATIONS
AUDIO ALARM, ETC.

TRADE ENQUIRIES WELCOMED

NAME.....

ADDRESS .....

PLEASE SEND .....

I enclose P.O./Cheque/Money Order

RAYMER ELECTRONICS LTD., STANLEY ROAD CAMBRIDGE CB5 8LB

Reg. Bus. 1031205

LARGE STOCKS, ATTRACTIVE DISCOUNTS DEPENDABLE SERVICE

Everything brand new and to makers' specifications.

ELECTROVALUE

Electronic Component Specialists

TRANSISTORS BY SIEMENS AND NEWMARKET

2N3055 *npn* silicon power	60p
AC153K *pnp* germanium low power	25p
AC176K *npn* germanium low power	23p
AD161 *npn* germanium medium power	42p
AD162 *pnp* germanium medium power	40p
AF139 *pnp* germanium UHF	49p

NPN: BC107 13p, BC108 12p, BC109 13p, BC167 11p, BC168 9p, BC169 11p.

PNP: BC177 21p, BC178 19p, BC179 21p, BC257 12p, BC258 11p, BC259 13p.
Standard groupings available.

BD135 *npn* medium power	39p
BD136 *pnp* medium power	38p

DIODES

OA90, OA91, OA95, 6p each; OA200, 9p; OA202, 10p.


Other semiconductors: AC128, 17p; AF117, 35p; BFY51, 19p. Full lists and technical data will be found in Catalogue No. 6. See also amendments list.

SIEMENS' THYRISTORS
0·8A 400V 65p, 600V 50p.
3A 400V 70p, 600V £1·02.

ZENER DIODES full range E24 values: 400mW: 2·7V to 36V, 14p each; 1W: 6·8V to 82V, 21p each: 1·5W: 4·7V to 75V, 48p each. Clip to increase 1·5W rating to 3 watts (type 266F) 4p.

DIN PLUGS AND SOCKETS

by Hirshmann, 4A rating

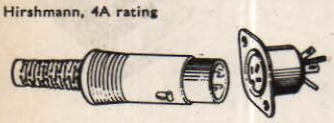

2 way LS —socket 10p, plug 12p
3 way scr.—socket 10p, plug 12p
5 way scr.—socket 11p, plug 15p

TRANSISTOR ACCESSORIES
TO3 cover, 7p; Heat sinks 1°C/W, type 6W1. undrilled, 60p.

SWITCHES




1011 SPST toggle, 20p; 409 DPDT toggle, 29p (these are chrome plated, 2·5A rating); 7201 sub-miniature DPDT 250V a.c./2A, 48p.

ROTARY SWITCHES

Radiospares Miniature Maka-switch (in assembly kit form). Shaft, 48p. Wafers, MBB-2P5W, 1P11W: BBM1P12W, 2P6W, 3P4W, 4P3W, 6P2W, 32p each.

WAVECHANGE SWITCHES

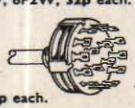

1P12W, 2P6W, 3P4W, 4I3W, 24p each.

ELECTROLYTIC CAPACITORS AXIAL LEAD

Rated voltage: 3V	6·3V	10V	16V	25V	40V	63V	100V
Capacity μF							
0·47	—	—	—	—	—	7p	7p
1·0	—	—	—	—	7p	—	7p
2·2	—	—	—	7p	—	7p	7p
4·7	—	—	7p	—	7p	7p	7p
10	—	—	7p	7p	7p	7p	7p
22	—	—	7p	7p	7p	8p	12p
47	7p	—	7p	7p	8p	12p	16p
100	7p	7p	7p	8p	10p	17p	26p
220	7p	7p	8p	9p	17p	24p	41p
470	7p	8p	9p	12p	23p	40p	—
1,000	9p	12p	17p	20p	40p	—	—
2,200	14p	16p	22p	36p	40p	—	—
4,700	23p	26p	40p	—	—	—	—
10,000	37p	40p	—	—	—	—	—

Prices subject to amendment by the manufacturer.

POLYCARBONATE—5% TOLERANCE
250V up to 0·1μF: 100V, 0·1μF and above.
0·01; 0·012; 0·015; 0·018; 0·022; 0·027; 0·033; 0·047; 0·056; 4p each. 0·068; 0·082; 0·1; 0·12; 0·15; 4p each. 0·18; 0·22; 5p each. 0·27; 0·33; 6p. 0·39 7p. 0·47 8p. 0·56 10p. 0·68 11p. 1μF 13p. *Prices subject to amendment by the manufacturer.*

Minitron Digital Counter
Type 3015F. Seven Filament segment indicators to make 0-9 + decimal point. Compatible with standard logic modules. nett £2. Decoder driver type FLL 121T nett £1·36. DIL socket, nett £2.

RESISTORS – 10%, 5%, 2%

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99 (see note below)	100 up
C	1/20W	5%	82Ω–220KΩ	E12	9	8	7·5
C	1/8W	5%	4·7Ω–470KΩ	E24	1	0·9	0.75
C	1/4W	10%	4·7Ω–10MΩ	E12	1	0·9	0·75
C	1/2W	5%	4·7Ω–10MΩ	E24	1·2	1	0·8
C	1W	10%	4·7Ω–10MΩ	E12	2·5	2	1·6
MO	1/2W	2%	10Ω–1MΩ	E24	4	3	2
WW	1W	10% ± 1/20Ω	0·22Ω–3·9Ω	E12	7	7	6
WW	3W	5%	1Ω–10KΩ	E12	7	7	6
WW	7W	5%	1Ω–10KΩ	E12	9	9	8

Codes: C = carbon film, high stability, low noise.
MO = metal oxide, Electrosil TR5, ultra low noise.
WW = wire wound, Plessey.
Values:
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51 62, 75, 91 and their decades.


Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions on total value of resistor order.)

We regret that where substantial price increases have occurred in some items, they are due to increased costs of imported goods. S.A.E.

KNOBS

All grub screw fitting for ¼in shafts. Black. For other types —see Catalogue No. 6, p. 54.

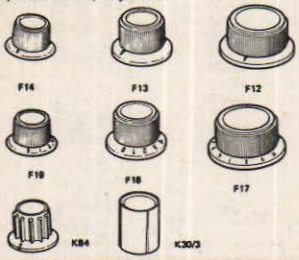F.14 (20mm) pack of 2, 32p; F.13 (26mm) pack of 2, 38p; F.12 (33mm) pack of 2, 40p; F.19 (20mm) pack of 2, 32p; F.18 (26mm) pack of 2, 38p; F.17 (33mm) pack of 2, 40p; KB.4 (20mm) pack of 4, 40p; K30/3 (17mm) aluminium, 24p each.



TRANSFORMERS—MAINS

MT3 30V/2A plus 4 taps	£2·85
MT103 50V/1A plus 4 taps	£2·55
MT104 50V/2A plus 4 taps	£3·50
MT127 60V/2A plus 4 taps	£3·80
13TO5 13V/¼A, CT	£1·25
28TO5 12+12V, 2–0–2V.	£1·65

IT'S ALL IN THE LATEST ELECTROVALUE CATALOGUE

No. 6 (4th printing) contains details of 100's of semiconductors; ICs with circuit diagrams, R's and C's of practically every kind, accessories, components, tools, materials, etc., information and equivalent tables, etc. Well illustrated (96 pages, 5¼in × 8¼in) 25p post free with refund voucher for 25p allowable on orders over £5 or more.

with 25p refund voucher

POTENTIOMETERS

Rotary, carbon track, double wipe
SINGLE P20 lin. 100Ω to 2·2MΩ, 12p; P20 log. 4·7KΩ to 2·2 Meg. 12p; JP20 log. 4·7KΩ, to 2·2MΩ, 12p; **Dual gang** lin. 4·7KΩ to 2·2MΩ, 42p Dual log. 4·7KΩ to 2·2MΩ 42p; Log/antilog, 10K, 22K, 47K, 1MΩ only, 42p; Dual antilog. 10K only, 42p. Any type with 2A D.P. mains switch, 12p extra.
Only decades of 10, 22 and 47 available in ranges quoted.


TYPE P20

DUAL CONCENTRIC DP20 in any combination of P20 values, 60p; with switch, 72p.


TYPE JP20

SLIDER
Lin. or log. 10K to 1 meg. in all popular values, each 26p.
Control knobs blk./white/red yel./gr./blue/dk. grey/lt. grey, 5p each.


TYPE DP20

CARBON SKELETON PRE-SETS
Small high quality, PR lin. 100Ω, 220Ω, 470Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10MΩ. Vertical or horizontal mounting, 5p each.


SLIDER

DISCOUNTS

All items offered for sale in accordance with our stated terms of business, copy of which available on request.
Not allowed on nett price items. 10% on orders for £5 or more. 15% on orders of £15 or more. *Prices subject to alteration without prior notice.* Prices quoted DO NOT include V.A.T. Orders received from U.K. customers must be accompanied by an additional 10% of the nett value for V.A.T. Overseas orders are exempt.

POSTAGE AND PACKING FREE
SURCHARGE 10p on small mail orders under £2. Overseas orders carriage and insurance charged at cost.

ELECTROVALUE

(Dept. PE7), 28 ST. JUDE'S ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Hours: 9—5.30. Sat. 1 p.m. Tel.: Egham 3603 Telex 264475
Eng. Reg. No. 1047769 Registered Office: 28 St. Jude's Rd., Englefield Green, Egham, Surrey TW20 0HB

BELLING LEE INSULATED TERMINALS. Red or Black, 5 amp max. 10p pair, p.p. 4p.

FINNED ALUMINIUM HEATSINK. 9in × 1½in. Ready drilled. **20p**, p.p. 7p.

SUB-MIN. CROC. CLIPS. Red or Black, insulated **4p.** Min. quantity, 6, p.p. 4p.

GARRARD MAG. TAPE DECKS: 1¾i.p.s., 50V, solenoid operated brakes, etc. Mains voltage motors **£7·50** each, p.p. 60p.

MOTEK 3 speed tape deck (1¾in × 3¾in × 7¼in) reel to reel 7in mains operated, **£7·50**, p.p. 60p.

10 REED SWITCHES operated by push buttons and magnets, **50p**, p.p. 25p.

COMPONENT PANEL 6 s'crs (200V 4 amps), 6 condensers, 12 resistances, **30p**, p.p. 8p.

COMPONENT PANEL (9 ICs FJH131) (1-CA300), 1 crystal 7·68kHz + various other components, **£1**, p.p. 8p.

AUDIO CONNECTORS

3 pin Din Plug	18p each
5 pin Din Plug A type, B type	18p ,,
2 pin Din Speaker Plug/Socket	10p ,,
3 pin Din Line Socket	18p ,,
3·5mm Jack Plug Screened	10p ,,
Standard Jack Plug	10p ,,
Screened Standard Jack Plugs	15p ,,
Stereo Jack Plug	18p ,,
Screened Stereo Jack Plug	18p ,,

Phono Plugs: Red or Black **3p** each. P.p. on above items 4p.

MAINS NEONS
Red or Green. Size: ¼in × ¼in × 1¼in. **15p**, p.p. 4p

LEVER ACTION P.C.1000 TYPE SWITCHES
Lock 4-pole changeover, **15p**, p.p. 4p. Ex equip. Lock 2-pole changeover, **10p**, p.p. 4p. Ex equip.

MULLARD & MALLORY SCREW TERMINAL CAPACITORS 4,500μF 64V, 7,100μF 40V, **50p** each. 20,000 30V, 25,000 25V, 35,000 15V, **30p** each, p.p. 10p.

MULLARD FULLWAVE RECTIFIERS
6-48V, 15 amp, **75p**, p.p. 9p.

BELLING LEE 1·5 amp in-line rubber covered interference suppressor, **25p**, p.p. 8p.

RUBBER 3 PIN 5 AMP NON-REVERSIBLE CABLE CONNECTORS, 20p, p.p. 5p.

SOLENOIDS 12 VOLT PULL ACTION
2in × 1in × ¾in, **40p**, p.p. 8p.

SOLENOIDS 12–24V d.c. pull action 1¾in × 1¾in × 1¾in, **40p**, p.p. 5p.

SOLENOIDS 240V a.c. pull action 2¾in × 1¾in × 1¾in, **50p**, p.p. 9p.

SANGAMO WESTERN TIME LAPSED METER
1¾in × 1¼in × 2in, **£1·50** p.p. 7p.

OMRON MK2 MIDGET POWER RELAY. 12V d.c. Double pole changeover. New, **70p**, p.p. 5p.

STC MINIATURE RELAY 280Ω, perspex cover, 6-15V new, **35p**, p.p. 5p.

STC VARLEY, miniature relays 700Ω, perspex cover, 4 pole changeover, **40p**, p.p. 5p.

POTTER BRUMFIELD 12V d.c. 3 pole changeover with base, contacts rated 7A d.c., **£1**, p.p. 10p.

GARDNER'S POTTED TRANSFORMER, 0-250V. Input: 18V 800m/a, 50V 150m/a, 6V 250m/a output. Size: 3in × 2¼in × 2¼in, **£1**, p.p. 20p. Ex equip. tested.

RIPLEY MAINS TRANSFORMER, Pri: 110V-240V, Sec: 12·5V: 0:12·5V 750m/A 7V:0:7 V1A, **£1**, p.p. 25p.

MAINS TRANSFORMER, Pri: 100-250V, Sec: 22:0:22 200m/A. 22:0:22 100m/A 0:24V 20m/A, **80p**, p.p. 25p.

TELESCOPIC AERIALS
Chromed 7in closed, 28in extended, 6 section ball jointed base, **28p**, p.p. 5p new.

MULLARD 4 DM 160 INDICATORS in plastic holder/cover, ex equip., size approx. 1¾in × 1¾in × ¾in, **36p**, p.p. 5p.

PRINTED CIRCUIT BOARD/19 ACY 19's 10 OA200 Diodes: 1 reed relay: 1 AZ 229 zenner ass. capacitor/resistors. Power supply 22V, 250 m/A d.c. Output 240V a.c. **£1**, p.p. 20p. Ex equip.

WIRING CABLE
Size: 1·020. Various colours. 350yd, **60p**, p.p. 23p.

TAPE POSITION INDICATOR
Re-settable 3 digits, **30p**, p.p. 5p.

All orders add 10% V.A.T.

FIELD ELECTRIC LIMITED

3 Shenley Road
Borehamwood, Herts.
Tel.: 01-953 6009

EX COMPUTER PC PANELS
2 × 4in packed with semiconductors and top quality resistors, capacitors, diodes, etc. Guaranteed min. 35 transistors plus data. 10 boards **50p** (9p).

SPECIAL BARGAIN PACK
25 boards **£1** (25p). Panels with 4 power transistors sim OC28 **50p** (9p).

ELECTROLYTICS
10,000μ 75V, 68,000μ 16V, 4½ × 2in dia. 25,000μ 25V, 20,000μ 30V, 5,000μ 90V, 35,000μ 15V, 8,000μ 55V, 4½ × 3in dia. **50p** (15p). 15,000μ 15V, 10,000μ 35V, 4½ × 2in dia. **30p** (10p). 2,000μ 25V wire ends **15p** (5p), 12 for **£1·50** (15p).

20A DIODES 4 for **£1** (7p)
3A DIODES 4 for **50p** (5p)
8 BLACK TOGGLES dpst **50p** (8p).
250 MIXED CAPACITORS **60p** (8p)
250 MIXED RESISTORS **60p** (8p)
150 HI-STAB RESISTORS **60p** (8p)
200 SI PLANAR DIODES UNTESTED **50p** (5p)
SUB-MIN. CO-AX. PLUGS & SKTS. 4 pairs **50p** (5p)
REED RELAYS, MIXED 10 for **50p** (5p)
MICRO SWITCHES 8 for **50p** (8p)
ASSORTED RELAYS 8 for **£1** (12p)
MIN. GLASS NEONS 12 for **50p** (5p)
10 WAY TERMINAL BLOCKS 10 for **55p** (5p)
QH BULBS 12V 55W **50p** (5p)
PAPST EXTRACTOR/BLOWER FANS
100 cfm 4½ × 4½ × 2in. **£3·50** (28p)

Postage and package shown in brackets.
Please add 10% VAT to prices.

KEYTRONICS

(Mail Order only)
44 EARLS COURT ROAD
LONDON W8
01-478 8499

GETTING BORED WITH ELECTRONICS?

Some things are repetitive, once you have built an astable multivibrator, they tend to get boring—tried a 555 timer? It works in mono or astable modes for long or short pulses (**95p**). How about building a radio tuner for your record player, the ZN414 chip makes this simple (**£1·10**). LEDs? We have a fantastic choice—LED lamps—TIL209 or HP4480, 4 for **£1**, 50 for **£10**; large lamps (HP4880), **35p** each, 50 for **£15**, RED and GREEN LEDs **£1** per pair. LED displays—TIL302 (or similar) **£2·50** each. TIL312 (similar to MAN4) **£2** each—limited quantity. TIL360 6 digit package **£18**, DL34 four digit package **£15**. DL62 (⅜") **£6·50**. Phosphor diode displays DG10 or DG12 **£2** each.

CLOCKS CLOCKS CLOCKS CLOCKS
Bywood is now foremost in the LSI clock chip market (who else has four different clock chips *in stock* with two more on order?). MM5311—the original—**£12·50**. MK5017AN with alarm and radio controls **£15·50**. MK5017AA with alarm or MK5017BB with calendar, either of these two is offered with a PCB, socket and suitable displays (4 DG12s) at **£24** or as a full kit with a Perspex case for **£32**.

Don't get bored, if none of the above fascinate you how about liquid crystal displays, DVM chips, etc? This technology is here to stay. Bywood have got it or can get it—give us a try.

VAT. All prices above EXCLUDE VAT, add 10%. P. & P. Please add 10p post and packing.

You can have clock data sheets for a S.A.E. or our 1973 catalogue (2nd issue) for **15p**. (And we havn't even mentioned our calculators yet—but they are in the catalogue.)

You may phone us for help on 0442-62757 and you can use your ACCESS card for phone or personal purchases—Service from Bywood!

BYWOOD

ELECTRONICS
181 EBBERNS ROAD, HEMEL HEMPSTEAD, HERTS. 0442 62757

[redacted]ER

BARGAINS

Fa[redacted] 100W, 18", 8/15 ohm	£21·45
Fan[redacted] Pop 60W, 15", 8/15 ohm	£12·26
Fane Pop 50W, 12", 8/15 ohm	£10·17
Fane Pop 25/2 25W, 8/15 ohm	£5·94
Fane Pop 15 12" 15W, 8/15 ohm	£4·40
Fane 122/10a or 122/12	£9·90
Fane Crescendo 15", 8 or 15 ohm	£27·50
Fane Crescendo 12", 8 or 15 ohm	£24·20
Fane 8" d/cone 808T, 8 or 15 ohm	£2·64
Fane 8" d/cone, roll surr. 807T, 8 or 15 ohm	£3·16
Baker Group 25, 3, 8 or 15 ohm	£6·00
Baker Group 35, 3, 8 or 15 ohm	£7·50
Baker De Luxe 12" d/cone	£9·62
Baker Major	£7·50
EMI 13" × 8", 3, 8 or 15 ohm	£2·25
EMI 13" × 8" type 150 d/cone, 3, 8 or 15 ohm	£2·58
EMI 13" × 8" type t/tw, 3, 8 or 15 ohm	£3·85
EMI 13" × 8" type 350, 8 ohm	£8·25
EMI 6½" 93850, 4 or 8 ohm	£2·80
Elac 9" × 5" 59RMLO9, 15 ohm	£2·53
Elac 9" × 5" 59RMLL4, 8 ohm	£2·53
Elac 6½" d/cone 6RM220, 8 ohm	£2·59
Elac 6½" d/cone, roll surr. 6RM171, 8 ohm	£3·22
Elac 4" tweeter TW4, 8 or 15 ohm	£1·21
Celestion PS8 for Unilex	£2·16
Celestion MFL000 25W horn, 8 or 15 ohm	£10·45
Elac 5" 3 ohm	£1·75
Elac 7" × 4", 3 or 8 ohm	£1·52
Elac 8" × 5", 3, 8 or 15 ohm	£1·93
Wharfedale Bronze 8 RS/DD	£3·11
Wharfedale Super 8 RS/DD	£5·50
Wharfedale Super 10 RS/DD	£9·80
Goodmans 8P, 8 or 15 ohm	£3·80
Goodmans 10P, 8 or 15 ohm	£4·49
Goodmans 12P, 8 or 15 ohm	£11·55
Goodmans 15P, 8 or 15 ohm	£17·05
Goodmans 18P, 8 or 15 ohm	£29·70
Goodmans Twinaxiom 8	£6·79
Goodmans Twinaxiom 10	£7·61
Goodmans Axent 100	£6·60
Eagle DT33 dome tweeter, 8 ohm	£4·95
Eagle HT15 tweeter, 8 ohm	£3·46
Eagle CT5 tweeter, 8 ohm	£1·21
Eagle MT10 tweeter	£3·30
Eagle CT10 tweeter	£1·92
Eagle Xovers CN23, 28, 216	£1·10
Kef T27	£4·67
Kef T15	£5·50
Kef B110	£6·16
Kef B200	£7·42
Kef BL39	£10·72
Kefkit 2	£12·75
Richard Allan 12" d/cone, 3 or 15 ohm	£2·20
Richard Allan 8", 3, 8 or 15 ohm	£2·27
10" × 6", 3, 8 or 15 ohm	£1·92
8" × 5", 3 or 8 ohm	£1·38
7" × 4", 3 or 8 ohm	£1·38
3", 8 ohm or 80 ohm	65p
2½", 64 ohm	65p
Speaker matching transformer, 3/8/15 ohm	£1·10
Adastra Hiten 10", 10W, 8 or 15 ohm	£2·80
Adastra Top 20 12", 25W, 8 or 15 ohm	£6·32

Stephen speaker kits and cabinets—send for illustrated brochure and list of recommended speakers.

Car stereo speakers—ask for leaflet.

PA/Disco amplifiers (carr. and ins. £1):

Baker 100W	£46·00
Linear 30/40	£25·00
Linear 40/60	£30·00
Linear 80/100	£50·00

FREE with speaker orders over £7—"Hi-Fi Loudspeaker Enclosures" book.

All units guaranteed new and perfect.

Prompt despatch.

Carriage and insurance 25p per speaker.

(Tweeters and Crossovers 15p each.)

All prices quoted inclusive of V.A.T.

WILMSLOW AUDIO, Dept. PE

SWAN WORKS, BANK SQUARE, WILMSLOW
CHESHIRE SK9 1HF

Henry's

YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards – call and see for yourself.

INTEGRATED CIRCUITS

Why buy alternatives when you can buy the genuine article from us at competitive prices from stock. BRANDED FROM TEXAS I.T.T FAIRCHILD





Type	1/11	12/24	25/99
	p	p	p
SN7400	0·20	0·18	0·16
SN7401	0·20	0·18	0·16
SN7402	0·20	0·18	0·16
SN7403	0·20	0·18	0·16
SN7404	0·20	0·18	0·16
SN7405	0·20	0·18	0·16
SN7406	0·30	0·27	0·25
SN7407	0·30	0·27	0·25
SN7408	0·20	0·19	0·18
SN7409	0·45	0·42	0·35
SN7410	0·20	0·18	0·16
SN7411	0·23	0·22	0·20
SN7412	0·42	0·40	0·35
SN7413	0·30	0·27	0·25
SN7416	0·30	0·27	0·25
SN7417	0·30	0·27	0·25
SN7420	0·20	0·18	0·16
SN7422	0·48	0·44	0·40
SN7423	0·48	0·44	0·40
SN7425	0·48	0·40	0·35
SN7427	0·42	0·39	0·35
SN7428	0·50	0·45	0·42
SN7430	0·20	0·18	0·16
SN7432	0·42	0·39	0·35
SN7433	0·70	0·61	0·44
SN7437	0·65	0·60	0·50
SN7438	0·65	0·60	0·50
SN7440	0·20	0·18	0·16
SN7441AN	0·75	0·72	0·70
SN7442	0·75	0·72	0·70
SN7443	1·00	0·95	0·90
SN7445	2·00	1·75	1·60
SN7446	2·00	1·75	1·60
SN7447	1·75	1·60	1·45
SN7448	1·75	1·60	1·45
SN7450	0·20	0·18	0·16
SN7451	0·20	0·18	0·16
SN7453	0·20	0·18	0·16
SN7454	0·20	0·18	0·16
SN7460	0·20	0·18	0·16
SN7470	0·30	0·27	0·25
SN7472	0·30	0·27	0·25
SN7473	0·40	0·37	0·35
SN7474	0·40	0·37	0·35
SN7475	0·55	0·52	0·50
SN7476	0·45	0·42	0·39
SN7480	0·80	0·75	0·67
SN7481	1·25	1·15	1·10
SN7482	0·87	0·80	0·70
SN7483	1·00	0·90	0·85
SN7484	0·90	0·85	0·80
SN7486	0·45	0·41	0·38
SN7490	0·75	0·70	0·65
SN7491AN	1·00	0·95	0·90
SN7492	0·75	0·70	0·65
SN7493	0·75	0·70	0·65
SN7494	0·80	0·75	0·70
SN7495	0·80	0·75	0·70
SN7496	1·00	0·97	0·95
SN7497	6·25	5·50	5·00
SN74100	2·50	2·30	2·00
SN74104	1·45	1·35	1·20
SN74105	1·45	1·35	1·20
SN74107	0·50	0·45	0·40
SN74110	0·80	0·70	0·60
SN74118	1·00	0·95	0·90
SN74119	1·90	1·78	1·65
SN74121	0·60	0·55	0·50
SN74122	1·35	1·25	1·10
SN74123	2·70	2·55	2·47
SN74141	1·00	0·95	0·90
SN74145	1·50	1·40	1·30
SN74150	3·35	2·95	2·15
SN74151	1·10	0·95	0·90
SN74153	1·35	1·27	1·20
SN74154	2·00	1·75	1·55
SN74155	1·55	1·47	1·35
SN74156	1·55	1·47	1·35
SN74157	1·80	1·70	1·50
SN74160	2·60	2·40	2·25
SN74161	2·60	2·40	2·25
SN74162	3·40	3·25	2·70
SN74163	3·40	3·25	2·70
SN74164	2·75	2·30	2·10
SN74165	4·00	3·50	3·00
SN74166	4·00	3·50	3·00
SN74167	6·25	5·60	5·10
SN74170	4·10	3·55	3·05
SN74174	2·00	1·75	1·30
SN74175	1·35	1·27	1·15
SN74176	1·60	1·35	1·20
SN74177	1·60	1·35	1·20
SN74180	1·55	1·30	1·20
SN74181	7·00	6·00	5·50
SN74182	2·00	1·80	1·60
SN74184	2·40	2·00	1·80
SN74185A	2·40	2·00	1·80
SN74190	1·95	1·85	1·75
SN74191	1·95	1·85	1·75
SN74192	2·00	1·90	1·80
SN74193	2·00	1·90	1·80
SN74194	2·50	2·25	1·90
SN74195	1·85	1·70	1·60
SN74196	1·50	1·40	1·30
SN74197	1·50	1·40	1·30
SN74198	4·60	3·70	3·35
SN74199	4·60	3·70	3·35

PRICES OF 7400 SERIES ARE CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX
LARGER QUANTITY PRICES PHONE (01) 402 4891
HIGH POWER SN 74 H00 } Now in stock—send
LOW POWER SM 74 L00 } for list No. 36

A SELECTION OF SEMI-CONDUCTORS FROM STOCK

AAY30	10p	BC147	12p	BU105	2·25	OC44	15p
AAY42	15p	BC169C	12p	BY100	15p	OC45	15p
AAZ13	10p	BC182	10p	BY126	15p	OC57	50p
AC107	35p	BC214	15p	BY127	15p	OC71	15p
AC126	25p	BCY32	75p	BYZ13	35p	OC72	25p
AC127	25p	BCY34	35p	C106D	65p	OC77	45p
AC128	25p	BCY39	1·00	GET111	55p	OC81	25p
AC176	25p	BCY42	30p	GET115	55p	OC83	25p
AC187	25p	BCY43	25p	GET880	45p	OC140	55p
AC188	25p	BCY55	2·50	LM309K		OC170	25p
ACY17	30p	BCY70	15p	(T03)	1·87	OC171	30p
ACY20	20p	BCY71	20p	MAT121	25p	OC200	45p
ACY21	20p	BCY72	15p	MJE340	50p	OC201	75p
ACY39	55p	BCY87	2·99	MJE370	70p	OC202	80p
AD140	50p	BCZ11	50p	MJE520	75p	OC203	50p
AD149	50p	BD124	80p	MJE2955		OCP71	1·25
AD161	35p	BD131	75p		1·10	ORP12	50p
AD162	35p	BD132	80p	MJE3055		ORP60	40p
AF117	20p	BF115	25p		75p	P346A	20p
AF118	50p	BF167	25p	MPF105	40p	RAS310AF	
AF124	25p	BF173	25p	NKT214	20p		45p
AF139	30p	BF179	30p	NKT216	40p	RAS508AF	
AF186	40p	BF180	30p	NKT217	40p		55p
AF239	40p	BF194	15p	NKT403	70p	TAA263	75p
ASY27	30p	BF195	15p	NKT404	50p	TIL209	39p
ASY28	25p	BF861	25p	OA5	50p	TIP29A	50p
BA102	30p	BFS98	25p	OA10	35p	TIP30A	60p
BA115	7p	BFX13	25p	OA81	10p	TIP31A	60p
BA145	15p	BFX34	75p	OA91	7p	TIP32A	70p
BAX13	5p	BFX37	30p	OA200	7p	TIP33A	
BAX16	7p	BFX88	20p	OA202	10p		1·00
BC107	10p	BFY50	20p	OC16	75p	TIP34A	
BC108	10p	BFY51	20p	OC20	95p		1·50
BC109	10p	BFY52	20p	OC23	85p	TIP35A	
BC109C	12p	BFY64	50p	OC25	40p		2·50
BC113	15p	BFY90	59p	OC28	65p	TIP36A	
BC117	20p	BLY36	8·00	OC35	50p		3·00
BC143	35p	BSX20	15p	OC36	65p	TIP41A	75p
		BSY27	15p	OC42	40p	TIP42A	85p

SPECIAL OFFERS! SEMI-CONDUCTORS

BFY90 59p
1000 MC/S
25 + 50p
100 + 45p
500 + 40p

2N2926 10p
All Colours
25 + 9p
100 + 8p
500 + 6p
1000 + 5p

AF117 Mullard 25p
25 + 17p
100 + 15p
500 + 12p

2N3819 Texas 35p
25 + 30p
100 + 25p
500 + 20p
1000 + 15p

OC170 Mullard 25p
25 + 20p
100 + 18p
500 + 15p
1000 + 13p

BC107, BC108, BC109 10p each
All Makes
25 + 8p
100 + 7p
500 + 6p
1000 + 5p

BY127 Mullard 15p
25 + 12p
100 + 10p
500 + 9p
1000 + 8p

AD161, AD162 35p each
25 + 32p
100 + 28p
500 + 25p
1000 + 22p

OA202 10p
25 + 8p
100 + 7p
500 + 6p
1000 + 5p

2N3053 20p
25 + 18p
100 + 15p
500 + 12p
1000 + 10p

OC35 Mullard 50p
25 + 45p
100 + 40p
500 + 35p
1000 + 30p

2N3055 55p
25 + 50p
100 + 45p
500 + 38p
1000 + 33p

ZENER DIODES

400 M/W 5%
Miniature
BZY 88 Range

All voltages
3·3 – 33 Volt
10p each.

25+	9p
100+	8p
500+	6·5p
1000+	5p

Any one type.

1½ Watt 5%
Wire Ends
Metal Case
All voltages
6·8 – 100 Volts
20p each

25+	18p
100+	16p
500+	12p
1000+	10p

Any one type.

3 Watt Plastic
Wire Ends 5%
3EZ Range

All voltages
6·8 – 100 Volts
30p each.

LINEAR (O/P AMPS)

702C	TO5	75p
709C	TO99	35p
709C	D.I.L.	35p
723C	TO99	£1·00
723C	D.I.L.	95p
725C	TO99	£4·50
741C	TO99	55p
741C	D.I.L.	55p
747C	TO99	£1·10
747C	D.I.L.	
		£1·10
72741P	D.I.L.	60p
72748P	D.I.L.	60p
SINCLAIR		
	IC12	£1·80
TOSHIBA		
TH9013P		
20 WATT AMP		
£4·47 POST PAID		
TH9014P Pre Amp		
		£1·50

DATA AND CIRCUITS REF. 42 10p

FREE WITH PURCHASES

TRANSISTORS, IC's, TRIACS, BRIDGES, SCR's, LDR's



NEW FREE BOOKLET (No. 36) OVER 1500 TYPES—

Send for yours today!

SILICON RECTIFIERS WIRE ENDED PLASTIC

Type	P.I.V.	1-11
1 amp miniature		
IN4001	50	6
IN4002	100	7
IN4003	200	8
IN4004	400	8
IN4005	600	10
IN4006	800	12
IN4007	1000	15
1·5 amp miniature		
PL4001	50	8
PL4002	100	9
PL4003	200	10
PL4004	400	10
PL4005	600	12
PL4006	800	15
PL4007	1000	16

PLESSEY INTEGRATED CIRCUIT
3 Watt Amplifier SL403 D
Complete with 8-page booklet, circuits and data
£1.50 each



TRIACS

STUD WITH ACCESSORIES

Type	Volts P.I.V.	Price 1-11
3 AMP RANGE		
SC35A	100	75p
SC35B	200	79p
SC35D	400	85p
6 AMP RANGE (TO48)		
SC40A	100	85p
SC40B	200	90p
SC40D	400	£1·00
SC40E	500	£1·20
10 AMP RANGE (TO48)		
SC45A	100	95p
SC45B	200	£1·00
SC45D	400	£1·25
SC45E	500	£1·45
15 AMP RANGE (TO48)		
SC50A	100	£1·25
SC50B	200	£1·35
SC50D	400	£1·65
SC50E	500	£1·85
DIAC D32		25p
TRIACS—		
Additional Types		
40430	(TO66)	85p
40669	(Plastic)	£1·00
40486	(TO5)	80p


3 Amp T048


15 Amp T048

NEW BRIDGE RECTIFIERS

SMALL SIZE AND LOW COST

Type	Volts P.I.V.	Price 1-11
HALF AMP		
BO5/05	50	20p
BO5/10	100	25p
ONE AMP ½ × ½ H TUBULAR		
B1/05	50	25p
B1/10	100	25p
B1/20	200	30p
B1/60	600	35p
ONE AMP (G.I.) TUBULAR		
W005	50	30p
W01	100	35p
W02	200	40p
W06	600	45p
TWO AMPS ½ H × ½ L × ¼		
B2/05	50	35p
B2/100	100	40p
B2/200	200	45p
B2/600	600	50p
B2/1000	1000	60p
FOUR AMPS ½H × ½L × ¼		
B4/100	100	60p
B4/200	200	65p
B4/400	400	70p
B4/600	600	75p
B4/800	800	£1·00
SIX AMPS ½H × ½L × ¼		
B6/100	100	70p
B6/200	200	75p
B6/400	400	90p
B6/600	600	£1·00






SILICON CONTROLLED RECTIFIERS

Type	Volts P.I.V.	Price 1-11
ONE AMP		
CRS 1/05	50	25p
CRS 1/10	100	30p
CRS 1/20	200	30p
CRS 1/40	400	35p
CRS 1/60	600	45p
THREE AMP (TO48)		
CRS 3/05	50	30p
CRS 3/10	100	30p
CRS 3/20	200	35p
CRS 3/40	400	45p
CRS 3/60	600	55p
FIVE AMP (TO66)		
CRS 5/400	400	60p
SEVEN AMP (TO48)		
CRS 7/100	100	60p
CRS 7/200	200	65p
CRS 7/400	400	70p
CRS 7/600	600	95p
SIXTEEN AMP		
SCR 16/100	100	65p
SCR 16/200	200	70p
SCR 16/400	400	80p
SCR 16/600	600	£1·00


1 Amp T05

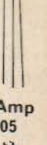
3 Amp T048

VAT Prices DO NOT include Value Added Tax. From 1st April 10% must be added and shown separately to your total order (inclusive post/packing). Help us help you receive your order without delay.

QUANTITY DISCOUNTS

10% 12+ : 15% 25+ ANY ONE TYPE
20% 100+ : 25% 250+

From above sections except Integrated Circuits and Special Offers where discounts are included.
Minimum order value £1 please.
Postage 7p on all orders.

Henry's RADIO LIMITED

EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
354-356 High Fidelity and Tape Equipment 01-402 5854/4736
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Open:- 9 am-6 pm 6 days a week (309 closed Thursday) All stores open all day Saturday

Bensham

Recording Ltd.

It's sound in a new light!

BRL Disco Equipment is something new, exciting and reliable. It comes from a team of audio-engineers whose thorough knowledge of the subject benefits you with quality, wide choice and, above all, VALUE FOR MONEY. Write, 'phone or call now for information. **All items in stock for prompt delivery.**

● STUDIOMINOR

Transportable, self-contained, mains-powered mixer for two decks with pre-fade listen and mic. input with individual bass and treble controls. Output may be taken from front or rear. An attractively-priced, high-performance unit.

£28·00 *plus VAT*

● POWERMASTER 1

An outstandingly rugged, reliable power amplifier built to cope with the rigours of constant running at high outputs. Accepts outputs from most commercially-available mixers and, of course, both Bensham mixers. Up to 10 power-master amps may be operated simultaneously from "Studio-master' or 'Studiominor'. Full overload and output protection 4 o/p Transistors have total output dissipation capability up to 460 watts.

£48·50 *plus VAT*

● POWERMASTER 2

Basically similar to Powermaster 1, but with 200 watts R.M.S. output.

£69·00 *plus VAT*

● SOUNDLITE A

A comprehensive three-channel SOUND-TO-LIGHT con-vertor handling 1,000 watts per channel. Individual channel indicating lamps; override switches and interference suppression circuitry. Sensitive enough for use with all normal disco amps.

£35·00 *plus VAT*

● SOUNDLITE B

Operates directly from soundwaves and does not need connecting to main amplifier. Its sensitivity is such that a cough or finger-snap is sufficient to trigger the SOUNDLITE B into operation.

£38·50 *plus VAT*

● MULTIMIX 100

A beautifully engineered and very versatile 100-watt R.M.S. amplifier with four separately-controlled input channels plus master control, all sliders. Wide range of bass and treble controls. This robust, low distortion unit is ideal for P.A. as well as disco applications in clubs, pubs., etc.

£62·00 *plus VAT*

● MULTIMIX 50

A 50-watt R.M.S. version of the MULTIMIX 100

£48·50 *plus VAT*

BE FIRST to get to know and use this fine, new value for money equipment. Built for years of hard work. Write, 'phone or call—information on request.

Bensham Recording Ltd.

WORKS AND MAIL ORDER:
BENSHAM MANOR ROAD PASSAGE, THORNTON HEATH, SURREY.
DEMO ROOMS AND R.O.
333 WHITEHORSE ROAD, THORNTON HEATH, SURREY.
Telephone: 01-684 6385

COMPARE OUR PRICES

Speaker Bargains	£p
E.M.I. 13in × 8in 3, 8 & 15 ohms plain	2·00
with tweeter	2·25
twin tweeter	3·50
Type 350 -20 watt with tweeter 8 ohms. P.P. 37p.	7·25
8in × 5in 3, 8 & 15 ohms	1·10
7in × 4in 3 & 8 ohms	90
FANE 8in 8 ohm, dual cone	2·10
CELESTION 8in 15 ohm	1·40
BAKER GROUP 25 12in 25W 8 or 15 ohm	6·00
Postage 25p per speaker	
2½in 8 or 64 ohm P.P. 10p	45

Kit-form cabinets, teak	
(17in × 10in × 6in)	2·95
with a 13in × 8in or 8in cut out	
18in × 11in × 9in with 13in × 8in cut out for EMI 350	£3·95
(12in × 12in × 6in) with a 8in × 5in or 8in cut out, (please specify cut out)	2·25
Add 35p per Cabinet for post & packing	

Microphone Bargains	£p
MIC45 "ACOS" metal case, crystal hand	95
CM 20 Crystal Hand	45
DX143 Dynamic, cassette-type stick	1·00
CM70 PLANET stick metal, switch crystal	1·45
DM160 Dynamic uni-dir, ball metal	3·75
UD130 50K/600 ohm uni-dir, ball metal	4·50
TW209 Lesson dual imp ball metal uni-dir	5·75
Condenser Mike uni-dir 600 ohm	7·95
Guitar mike	45
Lapel type, crystal	40
Postage 17p each	

Cartridges—with standard fittings & stylii	£p
GOLDRING G850	2·80
GOLDRING G800	4·40
ACOS GP91/28C or GP91/38C stereo compatible	90
ACOS GP94 stereo ceramic	1·50
ACOS GP95 stereo crystal	1·15
ACOS GP96 stereo ceramic	1·50
9THAC Sonotone stereo ceramic (diamond)	1·70
9THAC/G Sonotone stereo ceramic (diamond) slimline	1·70
ACOS GP67/2C mono crystal	65
ACOS GP101 compatible crystal	65
19-TI Sonotone stereo crystal	80
Postage 5p per cartridge	

Battery Eliminators	
240v input 6 or 9v d.c. output at 150 mA	1·99
240v input 6, 7½ or 9v output at 300 mA	2·99
12v d.c. input (for cars, fits in lighter socket) 6, 7½ or 9v d.c. output at 300 mA	2·50
P. & P. 10p	

Tapes—"MYLAR" base finest quality British made.

5in	600ft 38p	5½in	1800ft 85p
5in	900ft 45p	7in	1200ft 55p
5in	1200ft 60p	7in	1800ft 80p
5½in	900ft 49p		
5½in	1200ft 55p	7in	2400ft 95p

Postage 9p each

Plastic Library Cases for
5in Reels 16p
5½in Reels 19p
7in Reels 21p
P. & P. 5p each


THIS MONTH'S SPECIAL OFFER
PLINTH to suit GARRARD 2025, SP25, etc. Teak finish complete with perspex cover.
Our price £3·20 P. & P. 50p

Add 10% V.A.T. on prices incl. P. & P.


RIVERSDALE ELECTRONICS

Mail Order Dept. E7/73, P.O. Box 470, Manchester M60 4BU
SEND 25p FOR COMPLETE CATALOGUE

ALL OUR MERCHANDISE IS FULLY GUARANTEED

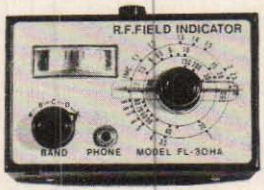

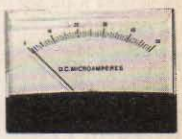R.F. FIELD INDICATOR
Model FL-30HA. Frequency Range: 5 ranges 1Mc/s to 250Mc/s, £3.



4½in × 3½in METER. 30μA, 50μA or 100μA, £2·50.

TAPE RECORDER LEVEL METER
500μA, 50p



MULTI-METER
Model 200H
20,000 ohm/volt, £4·80.





CARDIOID DYNAMIC MICROPHONE
Model UD-130. Frequency response 50–15,000c/s. Impedance Dual 50K and 600 ohms, £4·50.



MULTI-METER Model
C-708IGN Range Doubler 50,000 ohm/volt, 15μA High Sensitivity Meter, £11·25.

All items advertised in previous numbers of this magazine still available. There is 10% V.A.T. charge on all items. Please add 10p for P. & P. on orders under £5. LARGE S.A.E. for List No. 5. Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate • Bolton • Lancs. BL2 1BA

ALL OUR PRICES INCLUDE V.A.T.

BSR LATEST SUPERSLIM STEREO & MONO



Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250V
Size 13½ × 11¼in.
Above motor board 3¼in. below motor board 2¼in.

with STEREO and MONO XTAL **£8·25** Post 25p.

PORTABLE PLAYER CABINET

Modern design. Black rexine covered. Silver front grille.

Motor board cut for BSR deck **£4·50** Post 25p

E.M.I. WOOFER AND TWEETER KIT £5·75

Post 25p.



Available separately
Woofer £4·25 Tweeter £1·90
Comprising a fine example of a Woofer 10¼ × 6¾in. with a massive Ceramic Magnet, 44oz. Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3¼in. square has a special light-weight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.
Impedance Standard ..... 8 ohms
Maximum Power ..... 12 watts
Useful Response ... 35 to 18,000 c/s
Base Resonance ..... 45 c/s
SUITABLE ENCLOSURE 20 x 13 x 9in.
MODERN DESIGN. TEAK WOOD FINISH **£9·90** Post 25p

SPECIAL OFFER!



SMITH'S CLOCKWORK 15 AMP TIME SWITCH
Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Two types available 0 to 60 minutes or 0 to 6 hours. Makers last list price £4·50. Brand new and fully guaranteed. Fully insulated.
OUR PRICE £1·50. P. & P. 15p or £3 pair.
(PLEASE STATE TYPE A OR B WHEN ORDERING)

WEYRAD P50 — TRANSISTOR COILS

RA2W Ferrite Aerial .. 72p	Spare Cores 3p
Osc. P50/1AC 33p	Driver Trans. LFDT4 .. 58p
I.F. P50/2CC 470 kc/s .. 36p	Printed Circuit, PCA1 .. 58p
3rd I.F. P50/3CC 36p	J.B. Tuning Gang 65p
P51/1 or P51/2 ..... 36p	Weyrad Booklet 10p
P50/3V 36p	OPT1 ..... 58p

Mullard Ferrite Rod 8 × ¼in, 20p. 6 × ½in, 20p.

VOLUME CONTROLS

5 K. ohms to 2 Meg. LOG or LIN. L/S 15p. D.P. 25p.
STEREO L/S 55p. D.P. 75p.
Edge 5K.S.P. Transistor 25p.

80 Ohm Coax 4p yd.

BRITISH AERIALITE AERAXIAL-AIR SPACED
40 yd, £1·40; 60 yd, £2.
FRINGE LOW LOSS Ideal 625 and colour **10p yd**

8in. or 10in. ELAC HI-FI SPEAKER



Dual cone plasticised roll surround. Large ceramic magnet. 50–60,000 c/s. Bass resonance 55 c/s. 8 ohm impedance, 8in 10 watts, 10in 12 watts music power. **£3·75** Post 25p

E.M.I. 13½ × 8in. SPEAKER SALE!



With twin tweeters. And crossover. 10 watt. State 3 or 8 or 15 ohm. As illustrated. **£4·50** Post 25p

With flared tweeter cone and ceramic magnet. 10 watt. Bass res. 45–60 c/s. Flux 10,000 gauss. State 3 or 8 or 15 ohm. **£2·75** Post 25p

Bookshelf Cabinet 16 × 10 × 9in. **£5·50** Post 25p

BRITISH MADE STEREO MULTIPLEX DECODER £6·95 Post 15p

Brand New. 7 transistors Plus integrated circuit. Fibre-Glass printed circuit board. Size 2½ × 6½ × ¾. Pre-Aligned. Complete with stereo beacon indicator. 12V d.c. operation. 400mV Output for 100mV Input. Full instructions for any FM Tuner. Some technical experience essential.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2¼in sides 6 × 4in 45p; 8 × 6in 53p; 10 × 7in 65p; 12 × 8in 85p; 14 × 9in 90p; 16 × 6in 90p; 12 × 3in 50p; 16 × 10in £1.
ALUMINIUM BOX 6 × 4 × 4in 80p.
ALUMINIUM PANELS 18 s.w.g. 6 × 4in 9p; 8 × 6in 15p; 14 × 3in 16p; 10 × 7in 19p; 12 × 5in 20p; 12 × 8in 28p; 16 × 6in 28p; 14 × 9in 34p; 12 × 12in 40p; 16 × 10in 50p.
PAXOLIN PANEL 10 × 8in 15p.

ANOTHER R.C.S. BARGAIN!

4 TRANSISTOR MONO AMPLIFIER

Powerful 3 watt output, 15 ohm. AC mains operated with transformer. 3-Controls, volume, treble, bass and On/Off switch with knobs. Ready made on printed circuit board. Fused inputs and outputs. Famous make. size 8in wide × 4in deep × 3in high. **£5·95** Post 25p
Suitable 7" × 4" speaker, £1.

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240V a.c. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less
PLEASE STATE VOLTAGE REQUIRED. **£2·20** Post
Details S.A.E. Size 3½ × 1½ × 1¼in. 15p

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12V or H.T. line 200-300V d.c. operation. Size: 1¾ x 1¼ x ¾in. Response 25 c/s to 25 kc/s. 26 dB gain. For use with valve or transistor equipment. **99p** Post 10p
Full instructions supplied. Details S.A.E.

COMPACT PORTABLE STEREO HI–FI

Two full size loudspeakers 13¾ × 10 × 3¾in. Player unit clips to loudspeakers making it extremely compact, overall size only 13¾ × 10 × 8¾in. 3 watts per channel, plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls. 240V AC mains. Attractive Brown colour, weight 13 lb. **£25** Plus 85p carriage.

BRITISH FM/VHF TUNING HEART

88 to 108 M/CS British made. 2 Transistors ready aligned require 10·7 M/CS I.F. Complete with tuning gang. Connections supplied but some technical experience essential. **Our price £3·95** Post 20p

MAINS TRANSFORMERS

	All post 25p each
Eagle MT12 12-0-12V	90p
250-0-250 80mA 6·3V 3·5A, 6·3V 1A, or 5V 2A	£2·50
350-0-350 80mA, 6·3V 3·5A, 6·3V 1A, or 5V 2A	£3
300-0-300V 120mA, 6·3V 4A C.T.; 6.3V 2A	£3·25
MINIATURE 200V, 20mA, 6·3V 1A, 2½ × 2½ × 2in	75p
MIDGET 220V 45mA, 6·3V 2A, 2½ × 2½ × 2in	90p
HEATER TRANS. 6·3V 3A	60p
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2A, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V	£2·25
1A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V	£2·25
2A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V	£3·25
5A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V	£3·75
3A, 5, 8, 13V £1·00, Ditto 5A	£1·20
3A, 5, 8, 10, 13V, 5-0-5V £1·30, Ditto 5A	£1·50
6–0–6 500 mA	90p
9V 1 amp	95p
12V 300 mA	75p
12V 500 mA	85p
12V 750 mA	95p

AUTO TRANSFORMERS. 115V to 230V or 230V to 115V. 150W £2·25; 500W £3·25; 750W £10; 1000W £15.
CHARGER TRANSFORMERS. Input 200/250V.
for 6 or 12V, 1½A, £1·50; 2A, £1·80; 4A, £2·50.
BATTERY CHARGERS. 1½A £2; 3A £3; 4A £4; 5A £4·50.

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V. 3A. 720W. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. OUR PRICE **£10** Carr. 50p
Famous make. (Value £19)
Can be used as 800W auto transformers 240-110V.

NEW ELECTROLYTIC CONDENSERS

2/350V..	14p	250/25V .. 14p	50+50/350V .. 35p
4/350V..	14p	500/25V .. 20p	60+100/350V .. 58p
8/450V..	14p	1000/25V .. 35p	32+32/250V .. 18p
16/450V	15p	1000/50V 47p	32+32/450V .. 33p
32/450V	20p	8+8/450V 18p	350+50/325V .. 50p
25/25V..	10p	8+16/450V 20p	32+32+32/350V 43p
50/50V..	10p	16+16/450V 25p	100+50+50/350V 48p
100/25V	10p	32+32/350V 25p	


LOW VOLTAGE ELECTROLYTICS.
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.
500mF 12V 15p; 25V 20p; 50V 30p.
1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p.
2000mF 6V 25p; 25V 42p; 50V 57p.
2500mF 50V 62p; 3000mF 25V 47p; 50V 65p.
5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 95p.

CERAMIC, 1pF to 0·01mF, 4p. Silver Mica 2 to 5000pF, 4p.
PAPER 350V-0·1 4p, 0·5 13p; 1mF 15p; 2mF 150V 15p.
500V-0·001 to 0·05 4p; 0·1 5p; 0·25 8p; 0·47 25p.
SILVER MICA. Close tolerance 1%. 2·2-500pF 8p; 560-2,200pF 10p; 2,700-5,600pF 20p; 6,800pF-0·01, mid 30p each.
TWIN GANG. "0-0" 208pF+176pF, 65p; 500pF standard 45p.
365pF+365pF with 25pF+25pF, Slow motion drive 50p;
SHORT WAVE SINGLE. 10pF, 30p, 25pF, 55p, 50pF, 55p.
NEON PANEL INDICATORS 250V AC/DC. Amber 20p.
RESISTORS. ¼W, ⅓W, 1W, 20% 1p; 2W, 5p. 10Ω to 10M.
HIGH STABILITY. ¼W 2% 10 ohms to 6 meg., 10p.
Ditto 5%. Preferred values 10 ohms to 10 meg., 4p.
WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 10p each; 0·5 ohm to 8·2 ohms 10p.
TAPE OSCILLATOR COIL Valve type 35p.

ALL MODELS "BAKER SPEAKERS" IN STOCK
Hi Fi Enclosure Manual containing 20 plans, designs, crossover data and cubic tables. 42p Post Free

BAKER 12in. MAJOR £10

Post 25p

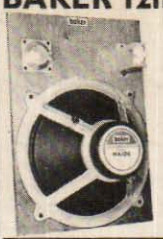

30-14,500 c/s, 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 20W. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£12·50** Post 25p

BAKER "BIG-SOUND" SPEAKERS Post 25p

'Group 25'	'Group 35'	'Group 50'
12in. **£8·80**	12in. **£9·90**	15in. **£22**
25W	35W	50W
3 or 8 or 15 ohm	3 or 8 or 15 ohm	8 or 15 ohm

TEAK VENEERED HI-FI SPEAKER CABINETS.
For 12in or 10in dia. speaker 20 × 13 × 9in, £9·90. Post 25p.
For 13 × 8in or 8in speaker 16 × 10 × 9in, £5·50. Post 25p.
For 8 × 5in speaker 16 × 8 × 6in, £4·40. Post 25p.
For 6in and Tweeter 12 × 8 × 6in. £4·00. Post 25p.
LOUDSPEAKER CABINET WADDING 18in wide, 15p ft.

GOODMANS 6½in. HI-FI WOOFER



8 ohm. 10W. Large ceramic magnet.
Special Cambric cone surround. Frequency response 30-12,000 c/s. Ideal P.A. Columns. Hi-Fi Enclosure Systems, etc.
Suitable Cabinet 12 × 8 × 6 £4 Suitable Tweeter £2 **£4**



ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 18,000 c/s. Size 3½ × 3½ × 2in deep. Rating 10W, 3 ohm or 15 ohm models. **£1·90** Post 10p.
Crossover 95p

SPEAKER COVERING MATERIALS. Samples Large S.A.E.
Horn Tweeters 2-16kc/s, 10W 8 ohm or 15 ohm £1·95.
De Luxe Horn Tweeters 2-18kc/s, 15W, 15 ohm £3. TWO-WAY 3,000 c/s. CROSSOVERS 3 or 8 or 15 ohm 95p.
LOUDSPEAKERS P.M. 3 OHMS. 7x4in., £1·25; 6½in., £1·50; 8 × 5in, £1·60; 10in, £2·00; 8in, £1·75; 10 × 6in, £1·00.
SPECIAL OFFER! 80 ohm, 2¼in, 2¾in; 35 ohm, 2in, 3in, 25 ohm, 2¾in dia., 3in dia., 5in dia. **£1** EACH
15 ohm, 3¼in dia. 6 × 4in, 7 × 4in, 8 × 5in. TYPE
3 ohm, 2¾in, 2¼in, 3¾in, 5in dia. 6 × 4in 8 ohms £1·50.
RICHARD ALLAN TWIN CONE LOUDSPEAKERS 8in. diameter 4W; 10in diameter 5W; 12in diameter, 6W; 3 or 8 or 15 ohm models. £2·20 each. Post 15p.
VALVE OUTPUT TRANS. 25p; MIKE TRANS. 50:1 25p.
5 WATT MULTI-RATIO, 3, 8 and 15 ohms 80p.
Mike trans. mu metal 100:1 £1·25.

MAJOR 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER



4 inputs speech and music, 4 way mixing.
Response 10-30,000 c/s. Matches loudspeakers, 8/15 ohm. A.C. 200/250V. Separate Treble and Bass controls. Guaranteed. Details S.A.E. **£49** Post Free

BARGAIN AM TUNER. Medium Wave. Transistor Superhet, Ferrite aerial. 9 volt. **£4·95**

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9V. **£3·95**
STEREO VERSION OF ABOVE **£5·95**

BARGAIN FM TUNER 88-108 Mc/s Six Transistor. 9V. Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 × 5 × 4in. **£14·85**
BARGAIN FM TUNER as above less cabinet **£9·85**

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control and on/off switch, 9 volt. **£4·50**

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p.
OUTLET BOXES. SURFACE OR FLUSH 25p.
BALANCED TWIN RIBBON FEEDER 300 ohms. 5p yd.
JACK SOCKET Std. open-circuit 14p, closed circuit 23p; Chrome Lead-Socket 45p. Phono Plugs 5p. Phono Socket 9p.
JACK PLUGS Std. Chrome 15p; 3·5mm Chrome 12p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10. DIN SOCKETS Lead 3-pin 18p; 5-pin 15p. DIN PLUGS 3-pin 18p; 5-pin 25p.
VALVE HOLDERS, 5p; CERAMICS 8p; CANS 5p.

ONE RPM GEARED MOTOR **95p** Post 25p.
240V A.C. mains.
Ideal for displays/disco light wheels.
E.M.I. GRAM. MOTORS. 120V or 240V a.c. 2,400 r.p.m. 2 pole 70mA. Size 2½ × 2½ × 2½in. Post 25p. **£1**
Deluxe 4 Pole Motor 1,400 r.p.m. 42W size 3½" × 3". Post 25p. **£1·95**

RADIO COMPONENT SPECIALISTS

337 WHITEHORSE ROAD, CROYDON

Illustrated Colour Brochure, Radio Books and Component Lists 10p. (Minimum posting charge 15p.)

Open 9-6. Wed. 9-1, Sat. 9-5 (Closed for lunch 1.15-2.30)
Buses 50, 68, 159. Rail Selhurst. Tel. 01-684-1665

Practical Electronics Classified Advertisements

RATES: 9p per word (minimum 12 words). Box No. 20p extra. Semi-Display £7 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4H 4AD

EDUCATIONAL

LEC

TELEVISION TRAINING

(MONOCHROME AND COLOUR)

This private College provides theoretical and practical training in Radio and TV Servicing. Courses of 16 months' duration, with daily attendance, are available for beginners and shorter courses for men with previous training in Electronics and Radio. Next course commences September 10th. Training courses in Marine Radiocommunication and Radar are also available. Write for prospectus to: **London Electronics College, Dept. B/7, 20 Penywern Road, Earls Court, London SW5 9SU. Tel. 01-373 8721.**



Department of

ELECTRICAL AND ELECTRONIC ENGINEERING

4 year sandwich courses leading to C.N.A.A. Degrees in

ELECTRONIC ENGINEERING
ELECTRICAL ENGINEERING
ELECTRO MECHANICAL ENGINEERING

Designed cover all aspects of Electrical and Electronic Engineering. Both men and women are welcome on these courses.

H.N.D. in ELECTRICAL AND ELECTRONIC ENGINEERING

Further details may be obtained from the Head of Department of Electrical and Electronic Engineering, North Staffordshire Polytechnic, Beaconside, Stafford or telephone him at Stafford 52331.

Please quote reference 3525PE on both envelope and letter.

A SUCCESSFUL CAREER IN RADIO

Get the success you deserve—take an ICS home study course. Pass C&G, M.P.T. exams FIRST TIME! Free books. Low cost. Personal tuition. Send TODAY for FREE Guide on Radio, TV, Electronics, Electrical Engineering.

Name _____

Address _____

ICS Dept. 730P Stewarts Road, London SW8 4UJ

ENGINEERS. Get a technical certificate. Postal courses in Engineering, Electronics, Radio, TV, Computers, Draughtsmanship, Buildings, etc., FREE book from: BIET (Dept. ZC BPE 28), Aldermaston Court, Reading, RG7 4PF. Accredited by CACC.

North Staffordshire Polytechnic

Stoke on Trent & Stafford

INTERESTED IN ELECTRONICS WITH PHYSICS?

A Higher National Diploma in Applied Physics at the North Staffordshire Polytechnic offers a study of the principles and practical uses of modern solid state devices and gives prospects for careers either in electronics or a wide variety of science based industries.

For further details write to Head of Physics Department, North Staffordshire Polytechnic, College Road, Stoke-on-Trent ST4 2DE.

BOOKS AND PUBLICATIONS

THOSE 1,000 BANBURY UFO'S! Details our prediction. List **10p** and S.A.E. Prediction Chart **50p.** Flight Pattern **42p.** R & E, Highlands, Needham, Suffolk.

DIGITAL COMPUTER Logic and Electronics. A four volume Self-instructional course, **£2·99** post free. Money back assurance. CAMBRIDGE LEARNING, 8a Rose Crescent, Cambridge.

SITUATIONS VACANT

MEN! £50 p.w. can be yours

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £2500+p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you **FREE** to world-wide opportunities. Write or 'phone **TODAY**, without obligation.

London Computer Operators Training Centre
M87, Oxford House
9-15 Oxford Street, W.1.
Telephone 01-734 2874

127 The Piazza, Dept. M87
Piccadilly Plaza, Manchester 1
Telephone 061-236 2935

SERVICE SHEETS

SERVICE SHEETS, Radio, TV, etc. 8,000 models. Catalogue **15p.** S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from **5p** with free Fault-Finding Guide. S.A.E. orders/enquiries. Catalogue **15p.** HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

Electro-Medical Service Department requires

ENGINEERS

for testing and servicing electronic apparatus. Applicants should be aged 20-30, and should be of O.N.C. standard.

Apply in first instance in writing to:

SIEREX LIMITED
Electro-Medical Department
Heron House, Wembley Hill Road
Wembley, Middlesex HA9 8BZ

FOR SALE

SEEN MY CAT? 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

TV LINE OUT-PUT TRANSFORMERS
Tidman Mail Order Ltd., 236 Sandycombe Road, Richmond, Surrey TW9 2EQ
01-948 3702

METER REPAIRS. Ammeters. Voltmeters, Multi-Range meters, etc., also Linear scale Transistorised Ohmmeters for sale. METER REPAIRS, 39 Chesholm Rd., London N16 0DS.

FIBRE OPTICS

Flexible Light Pipe for conveying light to inaccessible positions. Fibroflex Type I. Glass 1·14mm effective dia. PVC sheathed. **44p** per metre. (VAT inc.), P. & P. 10p. Any quantity.

Polariser Sheet up to 1 sq. ft. max. size. **16½p** per sq. in. (VAT inc.), P. & P. up to 6 in. square **10p**; over 6 in. square **30p**

- ★ Cut down glare
- ★ See those nixie tubes
- ★ Cross them for light control
- ★ Make your own strain gauge for plastics and glass

Circuit Board Etching Kits. Full instructions. **£1·37½** (VAT inc.), P. & P. **14p**

Photographic CDS Light Cells—used (with part of original circuit free), **33p** (VAT inc.), Post free.

All items are strictly C.W.O.

From: ARVIN SERVICE COMPANY
12 CAMBRIDGE ROAD
ST. ALBANS


CATALOGUE NO. 18, Electronic and Mechanical Components and manufacturers' surplus. Credit vouchers value 50p. Price **23p,** including post. ARTHUR SALLIS RADIO CONTROL LTD., 28 Gardner Street, Brighton, Sussex.

WANTED

TOP PRICES PAID
for new valves and components
Popular T.V. and Radio types
KENSINGTON SUPPLIES
(B) 367 Kensington Street
Bradford 8, Yorks.

RECEIVERS AND COMPONENTS

DRY REED INSERTS

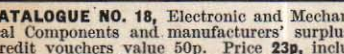

Overall length 1·85" (Body length 1·1"). Diameter 0·14" to switch up to 500 mA at up to to 250v D.C. Gold clad contacts. **69p** per doz.; **£4·12** per 100; **£30·25** per 1,000; **£275** per 10,000. All carriage paid.

G.W.M. RADIO LTD.
40/42 Portland Road, Worthing, Sussex 0903 34897

Trampus electronix



Add 10% VAT (⅛) to all prices. All brand new, no rejects. Money Back Warranty.
5V DIGITAL INDICATOR: 0–9DP socket and filter **£1·45.**
LED TYPE ½" 0–9DP DIL **£2·25** each; 6× **£2·19** each. 4 digit type **£11.**
LIGHT EMITTING DIODES. All with data and panel clip. TIL 209 ¼" dia. **26p.** Red ¼" dia. type **33p.** Green **75p.**
INFRA RED beam LED **£1·10.**
GAS detector **£1·69.** Ultrasonic transducer **£2.**
DALO PCB resist marking pen 69p. Copper board 12" × 6" SRBP **40p.** FeC etch PAK **19p.**
INTEGRATED CIRCUITS: with data if required.
IC LITE SWITCH: Photo amp/trigger 40mA/11–20V relay or TTL **87p.** Dil relay **£1·10.**

IC digital clock

MOS/LSI type. 28 pin, 4 or 6 digit, 12/24hr. Chip with socket **£13**; PCB **£1·69**; KIT **£21·49.** DVM voltmeter **£12.** Data **39p.** 3W AF amp **£1·24.**
741 Dil 8 pin **28p**; 709 **19p.** Dil **29p**; 748 **29p**; mono 710 **33p.** **555 TIMER**/mono/astable osc. clock **93p.**
REGULATORS: 1½A 5 to 20V **£1·49**; 723 **57p.**
RECEIVER ZN414 **£1·19.** Mini Rx Kit **£1·99.**
1310 stereo decoder for tuner **£2·69**, KIT **£3·45.**



74H TTL NEW LOW PRICES

GATES 7400/1/2/3/4/5/10/20/30/40/50, etc., **14p** each. 7413 **27p**; 7441 **73p**; 7447 **£1·09**; 7470, 7472 **28p**; 7473, 7474 **36p**; 7475 **60p**; 7476 **32p**; 7490 **59p**; 7492 **67p**; 7480 **69p**; 7483 **£1·10**; 7486 **37p**; 7493 **73p**; 7494 **83p**; 7495 **83p**; 7496 **89p**; 74121 **45p**; 74141 **99p**; 74190/91/92/93/96 **£2·39.** DIL Plugs/IC case 10mm high 16 pin **35p.**
DIL SOCKETS: low or high profile 8/14/16 pin **13p.**
SEMICONDUCTORS:
2N3055 **40p**; BC107 **8p**; BC108 **8p**; BC109 **8p**; BC147/8/9 **10p**; BC167/8/9 **13p**; BC177/8/9 **15p**; BC182/3/4 **10p**; BC212/3/4 **11p**; BCY70/72 **13p**; BD131/2 **55p**; BFY50/51/52 **13p**; TIS43 UJT **24p**; 2N706 **11p**; 2N2369 **12p**; 2N2926Oy **8p**; 2N2646 **49p**; 2N3053 **17p**; 2N3055 **40p**; 2N3614 **55p**; 2N3702/3/4/5/6/7/8/9/10/11 All **9p** each.
FETS: 2N3819 **27p**; 2N3823 **29p**; SCR 400V; 1A **23p**; 4A **55p.** TRANSFORMER: ½A 6 and 12V **£1.**
CAPACITORS: Disc 22pF to 0·1μF **4p.** 25V electrolytic 10, 50, 100μF **5p**; 1,000μF **15p.** **PRESETS 5p** each. RESISTORS ¼W 5% **1½p** each. **CARBON POTS 12p** each. Dual **40p.** Switch +**12p.** All Din Plugs **13p**; sockets **9p**; Vero RRP.

FLUORESCENT LIGHTS 12VOLT **£2·79**

13" 8 watt fully built with diffuser.
TRIO and **CODAR** communications and Hi-Fi retailer. ELECTRONIC ORGANS from **£67,**
PW ELECTRONIC CAR IGNITION KIT £6·67.
VAT: YOU MUST ADD 10% (⅛) to all prices.
FREE CAT. S.A.E. Data sheets 8p each. P. & P. 8p. C.W.O.

P.O. BOX 29, BRACKNELL, BERKS.

COMPUTER PANELS. 9in × 7½in long lead trans. and comps., E4, 8 trans., **27p** (10p); E45, 16 trans., **44p** (10p); E47, 10 trans., **32p** (10p). Panels with epoxy and TO18 Silicon transistors 4, **66p** (12p).
MC METERS. 2in or 3in, three assorted, **£1·15** (25p).
WIRE ENDED NEONS 10, **50p** (8p); 20, **82p** (8p).
Bank of 5 with 5 C407 driver Trans., **50p** (8p).
Bank of 30 ditto, **£2·20** (15p).
MAINS STEPPING SWITCH 22 WAY with reset. **85p** (15p). **RESETTABLE COUNTER,** 5 figure 18/22V. will work on 12V. **£2·20** (15p).
SILICON DIODES 650V 1½A. 10 on tag board, **35p** (5p). New 800V ¾A. 6 for **25p** (5).
7400 SERIES I.C. ON PANEL(S), 10, **82p** (8p).
COPPER CLAD PAX. PANELS. 5½in × 5½in., quantity 6 for **33p** (10p).
MIXED POLYSTYRENE/S. MICA CAPS. 100, **50p.**
7lb **ASSORTED COMPONENTS, £1·60.**
2lb **ASSORTED COMPUTER PANELS, £1·60.**
S.A.E. 9in × 4in for list of computer panels, etc.

J.W.B. RADIO
75 Hayfield Road, Salford 6, Lancs
Postage in brackets Mail order only

BEDFORD ELECTRONICS

2 Grove Place · Bedford
Bedford 51961

YOUR LOCAL COMPONENTS SUPPLIER

PRECISION
POLYCARBONATE CAPACITORS

Close tolerance. High stability. All 63V d.c.

0·47μF:	±5%	**30p**;	±2%	**40p**;	±1% **50p**
1·0μF:	±5%	**40p**;	±2%	**50p**;	±1% **60p**
2·2μF:	±5%	**50p**;	±2%	**60p**;	±1% **75p**
4·7μF:	±5%	**70p**;	±2%	**90p**;	±1% **£1·15**
6·8μF:	±5%	**95p**;	±2%	**£1·15**;	±1% **£1·50**
10μF:	±5%	**£1·10**;	±2%	**£1·40**;	±1% **£1·80**
15μF:	±5%	**£1·60**;	±2%	**£2·10**;	±1% **£2·70**

TANTALUM BEAD CAPACITORS. Values available 0·1, 0·22, 0·47, 1·0, 2·2, 4·7, 6·8μF at 35V, 10μF 25V, 15μF 20V, 22μF 15V, 33μF 10V, 47μF 6V, 100μF 3V—all at **9p** each; 6 for **50p**; 14 for **£1.** Special pack 6 off each value (78 capacitors) **£5.**
NEW!—TRANSISTORS. BC107, BC108, BC109. All at **9p** each; 6 for **50p**; 14 for **£1.** All brand new and marked. Full spec. devices. May be mixed to qualify for quantity prices. **AFI78** at **35p** each or 3 for **95p.**
POPULAR DIODES. IN914, 7p each; 8 for **50p**; 18 for **£1. IN916, 9p** each; 6 for **50p**; 14 for **£1. 1S44, 5p** each; 11 for **50p**; 24 for **£1.** All brand new and marked.
NEW LOW PRICE—400 mW Zeners. Values available 4·7, 5·6, 6·8, 7·5, 8·2, 9·1, 10, 11, 12, 13·5, 15V. Tol. ±5% at 5mA. All new and marked. Price **9p** each; 6 for **50p**; 14 for **£1.** Special offer 6 off each voltage (66 zeners) **£4·25.**
RESISTORS. Carbon film 5%, ¼W at 40°C, ⅛W at 70°C. Range from 2·2Ω to 2·2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at **1p** each; **8p** for 10 of any one value; **70p** for 100 of any one value. Special pack—10 off each value 2·2Ω to 2·2MΩ (730 resistors) **£5.**
440V A.C. CAPACITORS. 0·1μF, size 1¼in × ¼in, **25p**; 0·25μF, size 1¾in × ¾in, **30p**; 0·47 and 0·5μF, size 1¾in × ¾in, **35p**; 1·0μF, size 2in × ¾in, **45p**; 2·0μF, size 2in × 1in **75p.**
SILICON PLASTIC RECTIFIERS 1·5A—Brand new wire-ended DO27. **100PIV** at **8p** each or 4 for **30p**; **400PIV** at **9p** each or 4 for **34p**; **800PIV** at **14p** each or 4 for **50p.**

5p post and packing on all orders below £5.
Please add 10% VAT to all orders

MARCO TRADING
(Formerly V. ATTWOOD)
Dept. E7, The Maltings, Station Road
Wem, Shropshire

5—N-Channel FETs 3819E—£1

Full specification devices complete with circuit details for building voltmeter, timer, ohmmeter, etc.
Send 10p for full list of field effect transistors and other top quality transistors available at bargain prices.

REDHAWK SALES LTD.
45 Station Road, Gerrards Cross, Bucks.
MAIL ORDER ONLY

BRAND NEW COMPONENTS by return. Electrolytics 16V, 25V, 50V—0·47, 1, 2·2, 4·7, 10 mF, **4p**; 22, 47, **4½p** (50V, **5p**); 100, **5½p** (50V, **7p**); 220, **6p** (50V, **9p**). Subminiature bead-type tantalums 0·1/35V, 0·22/35V, 0·47/35V, 1/35V, 2·2/35V, 4·7/35V, 10/16V, **8p.** Mylar Film 100V—0·001, 0·002, 0·005, 0·01, 0·02, **2p**; 0·04, 0·05, **3p**; 0·068, 0·1, **3½p.** Polystyrene 63V E12 series 10–1,000pF, **2p**; 1,200–10,000pF, **3p.** Miniature highstab resistors, 5%, E12 series—Carbon Film ¼W, 1Ω–10MΩ (10% over 1 MΩ). Metal Film ¼W, 10Ω–2·2MΩ and 1W, 27Ω–10MΩ all **2p** each. Postage 8p. The C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield, S8 0RN.

Have you a bright Idea? We specialise in the Design, Manufacture and testing of Electronic Circuits to your specification. We also manufacture a range of Professional Sound Effects Units, and our supply department can provide a large range of components by return of post. Please send us a detailed list of your requirements for a free quotation.

M.M. ELECTRONICS
25 Silver Street, Ottery St. Mary, Devon

R.T. SERVICES
(MAIL ORDER ONLY)
77 Hayfield Rd., Salford 6, Lancs.

Mullard A.M. Module. I.F. Strip, LP1166, £1·10 inc. P.P.
FM Tuner with R.F. Stage and A.G.C., 3 plug-in transistors, neg. earth, 2½×2×1½ in with circuit, £1·37½ inc. P.P.
Crouzet Geared Motors, 10-30-60 r.p.m. New, £1·54 inc. P.P.
UHF TV Tuners. Transistorised, £1·65 inc. P.P.
3BP1 with Base and Screen, **£2·75** inc. P.P.
VCR138 CRT. New, boxed, **£3·30** inc. P.P.
Brand New Panel VU Meters, 4½×3¼ in calibrated, **£3·30** inc. P.P.
Transformers. 7·5V + 7·5V ¼A, **66p** inc. P.P. 18-0-18V, 200mA + 24V, **77p** inc. P.P. 9-0-9V, 100mA, **69p** inc. P.P. 12-0-12V, 100mA **69p** P.P. 20V, 1A **88p** inc. P.P.
Transformers. 52-0-52V, 1A + 22-0-22V, 200mA, **£2·20** inc. P.P.
P.C. Board. S/S, 5½ × 5½in, 10 for **70p** inc. P.P.
Panel with 5-200 PIV 1A SCRs + 14 OA200 diodes plus components **70p** inc. P.P.
2,500 mfd 100VW capacitor 4¼"×1¾". New, **85p** inc. P.P.
Panel Meter 50uA. Brand new, 4½"×3¼". **£3·30.**

BRAND NEW FULL SPEC. DEVICES
SATISFACTION OR YOUR MONEY BACK
U.K. ORDERS—Add 10% VAT to total

MICROCIRCUITS: 709 24p; 710 36p; 723 51p; 741 27p; 748 37p; PA230 60p; SL402A £1. **FET** Op. Amp. £1·62. **SOLDERCON** IC Pin Sockets 0·5p per pin. **SOCKETS** 14 pin DIL HI or LO 12p each. **RECTIFIERS:** 1A 50V 3½p; 100V 4p; 200V 4½p; 400V 5p; 800V 6p; 1,000V 7p. **ZENERS** (BZY88 Series): 2·7V to 33V 8p each. **DIODES** IN916 4p; OA90 6p; IN4148 4p. **LED PANEL LAMP** with Bush and Data 28p. **DALO PC RESIST PEN** 68p. **TRANSISTORS:** 2N2926 BROWN 5p, RED 6p, ORANGE 7p, YELLOW 8p, GREEN 9p; 2N3053 15p; 2N3054 40p; 2N3055 35p; 2N3702 10p; 2N3704 10p; 2N3819 26p; 2N4058 12p; BC107A 8p; BC108A 8p; BC109B 8p; BC109C 8p; BCY70 15p; BFY50/51/52 15p; OC44/45/70/71 12p. Above prices on April 30. Check our list.

JEF ELECTRONICS (PE7)
York House, 12 York Drive, Grappenhall, Warrington WA4 2EJ. Mail Order Only. C.W.O. P. & P. at cost. 10p min. List free.

SPECIAL INTRODUCTORY OFFER OF BRAND NEW & MARKED COMPONENTS ALL PRICES INCLUDE V.A.T.
TRANSISTORS: BC107B, BC108A/B/C, BC109B/C all at 8p; BFY50/51 14p; 2N3055 38p. **DIODES:** IN4148 4p; IN914 4p. **CARBON FILM RESISTORS:** ¼W 5%. ½p each, 30p/50 any mix (22Ω-2·2M) E12.
UNMARKED BARGAIN PAKS: These transistors have been properly tested and are guaranteed to have the specified hfe spreads. Pak of 5, Plastic BC108A hfe 125–240, 25p; Pak of 5, Plastic BC109B hfe 240–500, 25p; Pak of 5, Plastic BC179A hfe 125–240, 25p; Pak of 4, BFY51 20p; Pak of 4, 2N697 20p. **DIODES:** Pak of 5 OA200 20p; Pak of 12 IN4148 20p.
C.W.O. P. & P. 10p. on orders below £4. Overseas at cost. S.A.E. for lists (free with orders). Mail Order only. **Money back if not satisfied.**
ADFONIC (Dept. PE), 18 YEW LANE ASHLEY, NEW MILTON, HANTS BH25 5BA

COMPONENTS GALORE. Pack of 500 mixed components manufacturers surplus plus once used. Pack includes resistors, capacitors, transistors, diodes, I.C., gang, pots, etc. Tremendous value. Send £1 plus 10p P. & P. C.W.O. to CALEDONIAN COMPONENTS, Fosterton Firs, Strathore Road, Thornton, Fife.

RADIO & TELEVISION AERIAL BOOSTERS £2·95, five television valves **45p. 50p** bargain transistor packs, bargain **£1** resistor and capacitor packs. UHF-VHF televisions **£7·50.** Carr. £1·50. S.A.E. for 3 leaflets. VELCO ELECTRONICS, Bridge St., Ramsbottom, Bury, Lancs.

BUILD A LOW COST NO I.C. SYNTHESISER PROJECT for **£35** with surplus components. Contains ring mod., vco sustain electronic filter, white noise oscillators, psu, etc. For circuits, etc., send **£1** to: SARNIA ELECTRONICS, 6 Lower Clarence Road, Norwich.

TUNBRIDGE WELLS. Components from TELESERVICE, 108 Camden Road, Tunbridge Wells, Kent. Telephone 31803.

MISCELLANEOUS

AT LAST YOU CAN TRANSMIT AND FORGET ABOUT LICENCE EXAMINATIONS

because this Ministry approved transmitter/receiver kit does not use R.F.
Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND **£5·80** (inc. VAT) NOW
S.A.E. for details) MAIL ORDER ONLY
TO: 'BOFFIN PROJECTS'
DEPT. KE2010
4 CUNLIFFE ROAD
STONELEIGH, EWELL, SURREY

HARDWARE—Screws, nuts, washers and other useful items in small quantities. Sheet aluminium to individual requirements, punched/drilled. Send 6p for list. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwickshire.

NEW FROM ELBON

L.E.D.'s (Red Emitting) Ideally suited for panel indicators
Price only: **33p** each or **£2·50** for 10

Light SENSITIVE SWITCHES
Two types available giving wide operating voltages:
LITE-IC2 11V-20V working – **£1** each – **£8·50** for 10
LITE-IC3 20V-30V working – **£1** each – **£8·50** for 10
Applications include: Relay, Triac or Logic Drive, automatic light switching and door control, beam/break detection – burglar alarm, batch counting and code reading.

BARGAIN PACK!
2 LITE-IC2, 2 LITE-IC3 and 5 LED's all for **£5·00**

ALL PRICES INCLUDE VAT, PACKING AND CARRIAGE
Please send C.W.O. to:
LITE-IC; ELBON, SUMMERFIELD,
THE CRESCENT, WEST WITTERING, SUSSEX

FIBRE OPTIC SUPPLIERS (PE)
P.O. BOX 702 · LONDON W10 6SL

FIBROFLEX SIZE 1: Glass fibre flexible light conduit, 1·14mm active dia. bundle sheathed in P.V.C. Supplied complete with epoxy resin and 10 ferrules. Prices: 5 metres, **£2·97**; 10m, **£3·85**; 25m, **£6·60**; 50m, **£11**; 100m, **£17·15.**
FIBROFLEX SIZE 4: 2·28mm active dia. with epoxy resin. Prices: 1m, **£1·54**; 2m, **£2·75**; 5m, **£5·50**; 10m, **£9·90**; 25m, **£18·70.**
CROFON 1610: 1·80mm active dia., 64 filament plastic light conduit. Prices: 1m, **£1·32**; 2m, **£2·64**; 5m, **£5·50**; 10m, **£10·45**; 25m, **£22.**
PLASTIC OPTICAL MONOFILAMENT: Type FP20, 0·5mm dia. unsheathed, 100m, **£3·85**; 200m, **£6·60**; 500m, **£13·75.** Type FP40, 1mm dia., 10m, **£1·98**; 25m, **£3·85**; 50m, **£6·60**; 100m, **£12·10.** Type FP50, 1·5mm dia., 5m, **£1·98**; 10m, **£3·85**; 25m, **£7·70**; 50m, **£13·20.**
MARE'S TAILS: Spray of several thousand glass fibres about 400mm long. Ready to use as part of decorative displays. **£11 each.**
HN32 LINEAR POLARIZER: 0·030in thick, 32% luminous transmittance, 0·005% extinction. Applications leaflet, inc. light intensity control, stress analysis, glare reduction, etc., supplied with orders. 2in × 2in square, **£1·21 per pair.**
Prices include VAT, P. & P. and expansive booklet.

LOOK! NEW REDUCED PRICES

MUSIC

If your interest is in **SYNTHESISERS** and other **ELECTRONIC MUSIC** projects, you need our 1973 catalogue of circuit assemblies and units. Detailed and informative, complete with project layouts. Send 20p P.O. to:
TAYLOR ELECTRONIC MUSIC DEVICES
P.O. Box 42, Chester CH1 2PW

THERMOCOUPLES

Acramet and Acraspeed thermocouples, from IC are:-

Extremely accurate for fluid, gas or metal temperature measurement.

Individually calibrated and carry a certificate plus a one year guarantee.

Available with immersion or contact, non-earthed, multiples, boss or plug.

Details available on request.

International Combustion Limited, Sinfin Lane, Derby DE2 9GJ



A precision tool using a combination of butane and compressed oxygen or micronox. Gives a flame of pencil lead thickness. Adjustable **temperatures up to 5,000°F.** Lights instantly, no priming. Cuts metals, welds, brazes and solders, etc., gold and silver. Ideal for **electrical work,** jewellers, clockmakers, silversmiths. Up to 40 minutes' operation using fuel supplied. Replacement set of 2 micronox and 1 butane cylinders **£1·45** extra inc. post. Complete with instructions.
Our price £12·65 + 35p p. & p. **Send £13·00.**
JOHN DUDLEY & CO. LTD., Dept. PE7
301 Cricklewood Lane, Child's Hill, London, N.W.2
Tel. 01-458 5917. Callers welcome.

Build the Mullard C.C.T.V. Camera
Kits are now available with comprehensive construction manual (also available separately at 76½p)
SEND 5" 7" S.A.E. FOR DETAILS TO:
CROFTON ELECTRONICS
15/17 Cambridge Road, Kingston-on-Thames, Surrey KT1 3NG

ELECTRONICS FANATICS

whether beginner or advanced — we offer a range of over 35 SUPER projects.

Have you ever wanted to build A MACHINE THAT LEARNS? Or perhaps make a TEACHING DEVICE? Maybe you fancy the idea of an ELECTRONIC FANTASY MACHINE? How about a "Thing" capable of REPRODUCING ITSELF? Whatever your electronic turn-of-mind, there's just GOT TO BE LOADS TO INTEREST YOU in the science-fiction-world of BOFFIN.

GET YOUR CATALOGUE — SEND JUST 15p NOW!
MAIL ORDER ONLY
TO: BOFFIN PROJECTS
4 CUNLIFFE ROAD
STONELEIGH, EWELL
SURREY

Designs by GERRY BROWN and JOHN SALMON and presented on TV.

GLASS FIBRE P.C. BOARD—large supplies available. 1/16in single sided one ounce copper, **2p** per 3 sq in (under 1ft); **75p** per sq ft (over 1ft). 1/16in double sided one ounce copper, **1p** per sq in (under 1ft); **£1** per sq ft (over 1ft). Please add 10p per sq ft postage and packing. We can cut to your size at 1p per cut. SOLID STATE LIGHTING, The Firs, Smallworth Lane, Garboldisham, Diss, Norfolk.

CLEARING LABORATORY, scopes, V.T.V.M's, V.O.M's, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, M C relays, components, etc. Lower Beeding 236.

PSYCHEDELIC MINI-STROBE

A very POWERFUL, POCKET-SIZED STROBE-LIGHT that is SELF-CONTAINED and you can take anywhere. Go to parties and really BRAIN-FREEZE them with DAZZLING PSYCHEDELIC EFFECTS and STOP-MOTION FLASHES. Boffin's new MINI-STROBE kit constitutes a fully solid-state electronic device which is COMPLETE with FUTURISTIC case/reflector unit, printed-circuit board, electronics, and source-lamp—the only extra is a battery which you can buy locally. The whole thing can be easily built in a few hours.
A veritable FLICKERING FASCINATOR! Adjustable flash-rate.
GET ONE (or two) NOW and BEGIN STEALING THE THUNDER at DISCOS and PARTIES with your own POCKET-LIGHTNING!

SEND £2·10 (inc. VAT) for *YOUR* MINI-STROBE. MAIL ORDER ONLY

To: Boffin Projects
4 Cunliffe Rd., Stoneleigh, Ewell, Surrey

ENAMELLED COPPER WIRE

S.W.G.	1lb Reel	½lb Reel
10–14	£1·15	65p
15–19	£1·15	65p
20–24	£1·18	68p
25–29	£1·25	75p
30–34	£1·30	80p
35–40	£1·40	85p

Please add 10% to all above prices to cover VAT
The above prices cover P. & P. in U.K. Supplied by

INDUSTRIAL SUPPLIES

102 Parrswood Rd., Withington, Manchester 20
Telephone No. 061-224 3553

CONSTRUCTION AIDS. Screws, nuts, spacers, etc., in small quantities. Aluminium panels punched to spec. or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit boards—masters, negatives and boards, one-off or small numbers Send 6p for list. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwks.

FIBRE GLASS BOARD. 1/16in single sided **2p** per square inch. Double sided **3p** per square inch. Minimum order 50p. F. H. FREEMANTLE, 18 Pennine Road, Millbrook, Southampton.

P.E. SYNTHESISER KNOB KIT

Complete kit as Feb. issue 43 knobs, 7 calibrated discs. **£3·91** post free
DE LUXE KIT as above but calibrated for programming. **£5·89** post free
Inclusive postage and V.A.T.

RE-AN PRODUCTS LTD.
Burnham Road, Dartford, Kent
Tel.: Dartford 20785

ALUMINIUM SHEET to individual sizes or in standard packs, **3p** stamp for details. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwks.

COMPONENTS—assorted packs. Good value **£1** or **£2** packs plus 15p postage. C.W.O. B. WILYMAN, 15 Sarsfield Road, Perivale, Middx.

P.E., NOVEMBER, 1967 to present. What Offers? G. JAMES, 15 Sarsfield Road, Perivale, Middx.

PRINTED CIRCUITS. Photographic and manufacturing service for both the amateur and professional. Single or multiple boards. 10-day delivery. Details: E.M.C. PRODUCTS, 4b Station Road, Woolston, Southampton.

LADDERS

LADDERS, 24½ft **£9·80,** carr. 80p. Please add 10% V.A.T. to total order. Leaflet. HOME SALES LADDER CENTRE (PEE2), Haldane, Halesfield (1) North, Telford, Salop. Tel. 0952-586644.

ELECTRONIC BARGAINS

COMPAKS

Manufacturers' fall-outs which include functional and part-functional units. Ideal for learning and experimenting.

PAK 1	13 mixed 7400 series	66p
PAK 2	10 unijunction TIS43	55p
PAK 3	6 S.C.R.'s	55p
PAK 4	50 silicon and germanium NPN and PNP transistors	55p

Valve Equivalent Book 40p
Transistor Equivalent Book 40p
List over 3,000 equivalents

ACOUSTIC WADDING

Bonded Acrylic Fibre ¼in thick. Per square yard **50p**

VYNIAR SPEAKER CLOTH
Black—Black and Silver—Black and Gold

Sizes:	
18in × 25in	60p
36in × 25in	£1·10
36in × 50in	£2·20

Send S.A.E. for samples

SOLDERING IRONS

	Retail Price	Our Price
Antex CCN240	£1·98	£1·58
Antex CN240	£1·87	£1·49
Antex X25	£1·92	£1·54

FERRANTI RADIO CHIP

ZN414 **£1·23**

AMPLIFIER MODULE

5 watt, 9 volt supply, 4, 8 or 16 Ω speaker, **£3·30**

Fully Guaranteed. Mail order only. P. & P. 13p. V.A.T. included. Cheque or P/O to:

T. F. J. ELECTRONICS
25 EASTBURY COURT
LEMSFORD ROAD
ST. ALBANS, HERTS.

4-STATION INTERCOM



£7·99

Solve your communication problems with this **4-Station Transistor Intercom** system (1 **master** and 3 **Subs**), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from **Master** to **Subs** and **Subs** to **Master.** Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft and other accessories. P. & P. 44p.

MAINS INTERCOM (new model)

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price **£16·40.** P. & P. 60p extra.

INTERCOM/BABY ALARM



£3·99

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft connecting wire. Complete with battery. P. & P. 30p.




£3·46

Why not boost business efficiency with this incredible De-Luxe **Telephone Amplifier.** Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Complete with battery. P. & P. 24p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE/7)
169 KENSINGTON HIGH STREET, LONDON, W.8

DECADE T.T.L COUNTER UNIT

COMPLETE OR IN KIT FORM

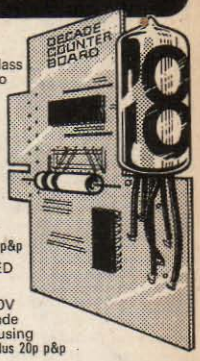

COMPLETE UNIT

Decade TTL Unit on fibreglass PCB using 74 series TTL to count up to 18MHz with Nixie tube display. These units may be coupled to provide a multi-digit readout for Frequency Counters, Timers, DVM's, Batch Counters etc. (Application details not available) Requires 200/250V D.C. & 5V D.C. reg.

KIT PRICE: **£5.06** plus 10p p&p

ASSEMBLED AND TESTED **£5.40** plus 10p p&p

TRANSFORMER, 200/250V to 6V, 1A & 250V for decade power supply, with circuit using 5V Regulator I/C: **£2.20** plus 20p p&p

COMPONENTS

400V, 8A Triac isolated tab type 1L48, 125A surge **85p**
32V Diac Type D30 suitable for triggering 1L48 **23p**
5V Voltage Regulator I/C. T03 case 600 m/A output from 7.5V—15V D.C. input, with instructions **£1.98**
Heat Sink, T03, twisted vane, 8°C/W for 5V Regulator **20p**
BC 107, BC 108 ..... **6p**
(All plus 6p p&p)

Prices include VAT. Please send c.w.o to:

DEXTER & COMPANY
1 ULVER HOUSE 19 KING STREET
CHESTER CH1 2AH
Tel: 0244-25883

ZIGGY'S 2001 ELECTRONICS Co. Ltd. RARE BARGAINS



SPECS. MULTIMETER U4324. Sensitivity 20,000 OPV DC. Usually high current ranges. 3 amps a.c./d.c. Voltages AC3 to 900V d.c. 0·6 to 1200V. Resistance 500 ohms–20-200-2,000kΩ. Transmission level −10 to +12dB. This high quality instrument has diode protection. Complete with test leads, batteries, etc. PRICE £8 plus 25p post, etc.

MULTIMETER 4313. Similar to above but special features include 3 amp current range and instrument is housed in metal case with carrying handle. (Illustrated leaflet sent on request.) ONLY **£9·50** plus 25p P. & P.

SANWA JP-5D. Diode protected. D.C. and A.C. volts 0–500V. D.C. current 0–500 mA. Res. 0–1MΩ. **£5·95.** P. & P. 20p.

EAGLE LT700 TRANS., LT44 TRANS. Our price **32p** each, postage 6p.

ARE YOU HUMBLE ABOUT YOUR RUMBLE? SP25 drive wheels, 65p plus 5p P. & P. MP60 drive wheels, 65p plus 5p P. & P.

SUBMINIATURE TOGGLE SWITCHES—very useful, very small. S/P, **25p,** DP/ST, **33p.** Postage 5p each, over 10, post free.

SUBMINIATURE MAINS TRANSFORMERS. Eagle MT6, 6–0–6, 100 M/A, **80p,** postage 10p.

MINIATURE TYPE MAINS TRANSFORMERS. Eagle Type MT280, 6–0–6 280 M/A, £1·20; MT150, 12–0–12, 150M/A, £1·20, MT100, 24–0–24, 100 M/A, £1·20. R/S types, 13V, 0·5 amp, C. Tapped, £1·06, 16·3V, 0·3 amp, C.T., £1·06. **Post 15p on min. size.**

DIAMOND STYLI FOR SONOTONE 9TAHC, LP/78, **65p** plus 5p P. & P. LP/LP, **95p** plus 5p P. & P.

FOR SPEEDY DELIVERY OF THESE MINT CONDITION COMPONENTS PLEASE SEND C.W.O. to ZIGGY'S 2001 ELECTRONICS CO. LTD., DEPT. P.E.3, 34 MABLEY STREET, LONDON, E.9.

N.B.—Please add 10% for VAT—Sorry.

BUILD A CHORDING PROFESSIONAL SYNTHESISER



The Synthesiser shown above is the **Dewtron** "Apollo" A.1. which we sell ready-built to professionals. Believe it or not, it uses the SAME precision modules as we sell to you, the Constructor, to build any kind you like. The revolutionary Modumatrix system of routing makes old-fashioned patching a thing of the past. VCO-2 voltage-controlled oscillator module has accurate built-in log-law for chording and other professional effects. 3 and 4 octave keyboards and contacts.

VCO-2 STABLE, PRECISION V/C OSCILLATOR gives SINE, TRIANGULAR AND SQUAREWAVE outputs, 1 volt/octave voltage control. **£22** each or **£25** each 2 or more matched. **SHE-1 SAMPLE, HOLD AND ENVELOPE MODULE** gives variable attack, sustain, touch sensitive playing when used with VCO-2 signals. **£15.** OFT-1 chording module **£7·50.** Modules (except VCO-1) guaranteed two years.

using **Dewtron** (Regd. Trademark)

PROFESSIONAL MODULES
CASH SAVINGS
by buying modules and parts in bulk!
All modules are available separately:
Ring Modulator RM2, **£8.** Voltage-controlled Oscillator VC01, **£10·50,** giving sawtooth and square-wave outputs. Envelope shapers, ES1, self-triggered or ES2 keyboard-triggered, either type **£13.** White noise type WN1, **£7.** Voltage-controlled amplifier VCA1, **£10.** Voltage-controlled selective amplifier (filter for waa-waa, etc.) SA1, **£12.** Voltage-controlled Phase PH1, **£17.** Automatic Announcement Fader module for fading of music by microphone announcement, AF1, **£9.** etc., etc. ALL MODULES ARE BUILT, TESTED AND SEALED FOR LONG LIFE. Simply connect coloured wire connections as per easy instructions, build cabinet and wire in controls and patchboard connections! Joystick controls **£4·50.** REVERB Module and spring unit **£15.** V.A.T. 10% extra. V.A.T. paid orders over **£75.**

With over 7 years' unblemished reputation in these pages, ***Dewtron*** *continues to lead in new technical developments in electronic sound effects! Ask any of our customers. See our products in the music stores, too. Suppliers of special equipment to leading group. Our modules are used in professional equipment by other manufacturers and in our own built synthesisers, e.g. "Gipsy" G.I.* ***Approved by the Association of Musical Instrument Industries.*** *Send 15p for full catalogue of our famous musical effects.*

D.E.W. LTD.

254 Ringwood Road, FERNDOWN, Dorset BH22 9AR

FERRANTI

ZN414 Radio i.c.

only £1.32 WITH DATA

WE ARE SPECIALISTS IN FERRANTI SEMICONDUCTORS

BFS59	15p	ZTX310	9p	ZTX504	43p	ZS170	10p
BFS60	20p	ZTX311	10p	ZTX510	17p	ZS171	13p
BFS61	20p	ZTX312	10p	ZTX530	21p	ZS172	16p
BFS96	15p	ZTX313	11p	ZTX531	22p	ZS174	17p
BFS97	23p	ZTX314	13p	ZTX550	17p	ZS176	23p
BFS98	20p	ZTX320	31p	ZTX551	17p	ZS178	38p
ZTX107	9p	ZTX330	15p	2N3055	72p	ZS270	11p
ZTX108	8p	ZTX331	16p			ZS271	16p
ZTX109	11p	ZTX382	13p	* DIODES *		ZS272	18p
ZTX212	14p	ZTX383	15p	ZS120	8p	ZS274	19p
ZTX213	14p	ZTX384	18p	ZS121	10p	ZS276	26p
ZTX214	15p	ZTX450	17p	ZS122	13p	ZS278	37p
ZTX300	12p	ZTX451	17p	ZS123	16p		
ZTX301	13p	ZTX500	12p	ZS124	18p	* ZENERS *	
ZTX302	17p	ZTX501	13p	ZS140	25p	KS030A to	
ZTX303	14p	ZTX502	17p	ZS141	43p	KS180A—	
ZTX304	21p	ZTX503	14p	ZS142	33p	all types	19p

ALL DEVICES TOP GRADE, BRAND NEW, AND FULLY GUARANTEED
WE CAN SUPPLY ANY FERRANTI DEVICE. Send S.A.E. for quotation
PRICES SLASHED! RCA CA3090Q **£3·25**; CA3075 **99p.** Limited quantity only.
P. E. Triffid. ZT1711 **24p**; 2N1132 **25p.**
POSTAGE AND PACKING 10p—Free over £2. Send S.A.E. for our full price list and data sheet.
ALL PRICES INCLUDE V.A.T.

DAVIAN ELECTRONICS

PO BOX 38, OLDHAM, LANCS. OL2 6XJ

STEREO IC DECODER

HIGH PERFORMANCE PHASE LOCKED LOOP (as in 'W.W.' July '72)
MOTOROLA MC1310P

EX STOCK DELIVERY

Specn. Separation: 40dB 50Hz—15kHz. Distortion: 0·3%. I/P level: 560mV rms. O/P level: 485mV rms per channel. Input impedance: 50k. Power requirements: 8–12V @ 16mA. Will drive up to 75mA stereo 'on' lamp or LED. Simple to build.

KIT COMPRISES FIBREGLASS PCB
(Printed and tinned), Resistors, I.C., Capacitors, Preset Potm. and Instructions. Only **£3·50** post free + V.A.T.

LIGHT EMITTING DIODE (Red)
Suitable as stereo 'on' indicator. For above with panel mounting clip and instructions. Only **35p** + p.p. + V.A.T.

MC1310P only £2·77 + p.p. **6p** + V.A.T.

14 PIN DIL SOCKETS. 16p each + V.A.T.

NOTE.—As the supplier of the original decoder kit, of which we have sold literally thousands, our customers can benefit from our wide experience.

Fi-Comp Electronics

BURTON ROAD, EGGINTON, DERBY DE6 6GY



BAKER 12" MAJOR £9·90

30-14,500 cps. Double cone woofer and tweeter combination. Baker ceramic magnet assembly, flux density 145,000 gauss. BASS RESONANCE 40 cps 20 watt RMS.

MAJOR MODULE KIT £12·50

30-17,000 cps. response. Tweeter, crossover and baffle as illustrated.

BAKER LOUDSPEAKERS

Regent 12 in. 15W	£8·80	Superb 12 in. 20W	£16·50
Major 12 in. 20W	£9·90	Group 25 12 in. 25W	£8·80
Deluxe 12 in. 15W	£11·00	Group 35 12 in. 35W	£9.90

ALL PRICES INCLUDE V.A.T.

BAKER LOUDSPEAKER CO., BENSHAM MANOR PASSAGE
THORNTON HEATH, SURREY Tel. 01-684 1665
LOUDSPEAKERS CATALOGUE AND ENCLOSURE PLAN 5p

FREE!

Over 150 ways to engineer a better future



HIGHER PAY | A BETTER JOB | SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, *you* could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you . . . but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained – a view echoed by two colleagues who recently commenced the course".—Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters – and there are many more on file at Aldermaston Court – speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help *you*. **Write to B.I.E.T. Dept. BPE06, Aldermaston Court, Reading RG7 4PF.**

Practical Radio & Electronics Certificate course includes a learn while you build ***3 transistor radio kit.*** Everything you need to know about ***Radio & Electronics*** maintenance and repairs for a ***spare time income*** and a ***career*** for a better future.

CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

MECHANICAL
- A.M.S.E. (Mech.) ☐
- Boiler Inspect. & Operation ☐
- C & G Eng. Crafts ☐
- C & G Fabricat. ☐
- Diesel Eng. ☐
- Eng. Inspection ☐
- Eng. Metallurgy ☐
- Inst. Eng. & Tech. ☐
- Inst. Motor Ind. ☐
- Mainten. Eng. ☐
- Mechanical Eng. ☐
- Sheet Metal Work ☐
- Welding ☐

ELECTRICAL & ELECTRONIC
- A.M.S.E. (Elec.) ☐
- C & G Elec. Eng. ☐
- C & G Elec. Inst. ☐
- C & G Elec. Tech. ☐
- Computer Elect. ☐
- Elec. Maths ☐
- Elec. Science ☐
- Electronic Eng. ☐
- Electrical Eng. ☐
- Install. & Wiring ☐
- Meters & Measuring Instruments ☐

MANAGEMENT & PRODUCTION
- Auto. Control ☐
- Computer Prog. ☐
- Electronic Data Processing ☐
- Estimating ☐
- Foremanship ☐
- Inst. Cost & Man Accountants ☐
- Inst. Marketing ☐
- Management ☐
- Metrication ☐
- Motor Trade Man. ☐
- Network Plan. ☐
- Numerical Cont. ☐
- Operational Research ☐
- Personnel Man. ☐
- Planning Eng. ☐
- Production Eng. ☐

Man. Prod.—cont.
- Quality Control ☐
- Salesmanship ☐
- Storekeeping ☐
- Work Study ☐
- Works Management ☐

DRAUGHTSMANSHIP
- A.M.I.E.D. ☐
- Design of Elec. Machines ☐
- Die & Press Tool Design ☐
- Electrical Draughtsmanship ☐
- Gen. Draughtsmanship ☐
- Jig & Tool Des. ☐
- Tech. Drawing ☐

RADIO & TELE-COMMUNICATIONS
- Colour TV ☐
- C & G Radio/TV/Electronics ☐
- C & G Telecomm. Tech. ☐
- Prac. Rad. Elec. (with kit) ☐
- Radio Amateurs Exam. ☐
- Radio Servicing & Repairs ☐
- Radio & TV Eng. ☐
- Trans. Course ☐
- TV Main. & Serv. ☐

AUTO & AERO
- Aero Eng. ☐
- A.M.I.M.I. ☐
- A.E.C. Cert. ☐
- Auto Engineer. ☐
- Auto Repair ☐
- C & G Auto. Eng. ☐
- Garage Management ☐
- MAA/IMI Dipl. ☐
- Motor Vehicle Mechanics ☐

CONSTRUCTIONAL
- A.M.S.E. (Civil) ☐
- Architecture ☐

Constructional-cont.
- Building ☐
- Building Drawing ☐
- Build. Foreman ☐
- Carpentry & Join. ☐
- Civil & Municipal Engineering ☐
- Constructional Engineering ☐
- Construction ☐
- Surveyors ☐
- Institute Clerk of Works ☐
- Council Eng. ☐
- Geology ☐
- Health Eng. ☐
- Hydraulics ☐
- Inst. of Builders ☐
- Inst. Works & Highway Sup. ☐
- Painting & Dec. ☐
- Public Hygiene ☐
- Road Engineer. ☐
- Structural Eng. ☐
- Surveying ☐

GENERAL
- Agricultural Eng. ☐
- Council of Eng. Inst. ☐
- Farm Science ☐
- General Educat. ☐
- Gen. Plastics ☐
- Pract. Maths ☐
- Pract. Slide Rule ☐
- Pure & Applied Maths ☐
- Refrigeration ☐
- Rubber Tech. ☐
- Sales Engineers ☐
- Tech. Report Writing ☐
- Timber Trade ☐
- University Ent. ☐

Coaching for many major exams. including C & G and assistance in O/C/H.N.C.

G.C.E.
58 'O' & 'A' LEVELS SUBJECTS
Over 10,000 group passes

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPE06 QN
Aldermaston Court, Reading RG7 4PF **BPE06**

NAME.....
Block Capitals Please
ADDRESS.....
.....
.....
OTHER SUBJECTS..... AGE.....

Accredited by C.A.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/sia) Ltd.: South Africa—Central News Agency Ltd.: Rhodesia and Zambia—Kingstons Ltd.: East Africa—Stationery and Office Supplies Ltd. Subscription Rate (including postage): For one year to any part of the world £2·65 (£2.13.0).
Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

Henry's

YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards – call and see for yourself.

BUILD THE TEXAN

★ **FREE TEAK CASE** with complete kits!

FEATURES: New slim design with 6 ICs, IC sockets, 10 silicon transistors, 4 rectifiers, 2 zeners. Special Gardners low field slim line transformer. Fibre glass PC panel. Complete chassis work.

HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES —DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.


FACILITIES: On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, Input selector: Mag. P.U., Radio Tuner, Aux. Can be altered for Mic, Tape, Tape head etc. (Parts list Ref. 20 on request). Constructional Details Ref. No. 21. 30p.

SPECIAL KIT PRICE **£28·50** P. & P. 45p

COMPLETE WITH FREE TEAK CABINET

20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER

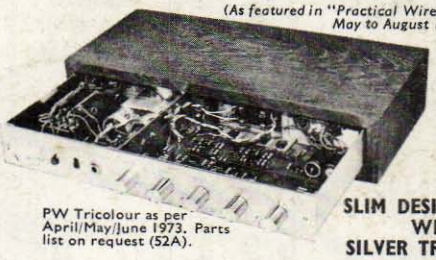(As featured in "Practical Wireless" May to August 1972)



PW Tricolour as per April/May/June 1973. Parts list on request (52A).

SLIM DESIGN WITH SILVER TRIM

Overall chassis size 14½ in. x 6 in. x 2 in. high

Designer approved kits distributed by Henry's!

LOW COST HI-FI SPEAKERS




E.M.I. Size 13½in x 8½in and Ceramic Magnet

TYPE 150 6 watt, 3, 8 or 15 ohms **£2·20.** Post 22p.
TYPE 150TC Twin cone version **£2·75.** Post 22p.
TYPE 450 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. **£3·50.** Post 25p.
TYPE 350 20 watt with tweeter and crossover, 8 and 15 ohms. **£7·50.** Post 28p.



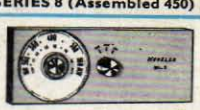POLISHED CABINETS 150, 150TC, 450 **£4·60.** Post 30p.
ASSEMBLED IN POLISHED CABINETS (8 OHM)
SERIES 6 (Assembled 150TC) per pair **£16·50.** Post 70p.
SERIES 8 (Assembled 450) per pair **£18·95.** Post 70p.



ML3 MW/LW TUNER TO BUILD

Uses Mullard Module. Slow motion tuning. Built-in battery. Ferrite aerial. Overall size 7in x 2¾in x 3¼in. TOTAL COST TO BUILD **£4·85.** Post 15p. All parts sold separately—Leaflet No. 6.

"BANDSPREAD" PORTABLE TO BUILD



Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. 600mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance. TOTAL COST TO BUILD **£7·98,** p.p. 32p (Batt. 22p).

CATALOGUE




Fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information. 10,000 Stock lines at Special Low Prices and Fully Guaranteed.

PRICE 55p Post paid **(40p FOR CALLERS)**

PLUS! FIVE 10p VOUCHERS

Send to this address—Henry's Radio Ltd. (Dept. PE), 3 Albemarle Way, London, E.C.1—for catalogue by post only. All other mail and callers to "303", see above.

TEST EQUIPMENT Just a selection

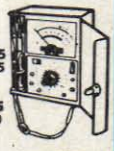


SE250B Pocket Pencil Signal Injector, **£1·90**
SE500 Pocket Pencil Signal Tracer, **£1·50**
THL33D Robust 2 K/Volt, **£4·55**; with case **£4·95**
TE15 Grid Dip Meter 440 KHz—280 MHz, **£13·45**
500 30 K/Volt Multimeter, **£9·25**; with leather case, **£10·50**
200H 20 K/Volt Multimeter, **£4·20**; with case **£4·95**
AF105 50K/V Multimeter, **£8·50**; with case, **£9·50**
U4341 AC/DC Multimeter with transistor tester with steel case, **£10·50**
TE20D RF Generator 120KHz—500MHz, **£16·50.** Carr. 35p
TE22D Audio Generator 20Hz—200KHz, **£17·50.** Carr. 35p
CI-5 3in Pulse Scope 10Hz—10MHz, **£39·00.** Carr. 50p
TE65 Valve Voltmeter 28 ranges, **£17·50.** Carr. 40p
ALL NOMBREX MODELS IN STOCK

BUILD THIS VHF FM TUNER



5 TRANSISTORS 300kc/s BANDWIDTH PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7. **TOTAL £6·97,** p.p. 20p.
Mk I Decoder Kit **£5·97.** Built IC Decoder **£6·50.** Tuning meter unit **£1·75.**
Mains unit (optional) Model PS900 **£2·47.** Post 20p.
Mains unit for Tuner and/or Decoder PS6/12 **£3·25.** Post 20p.

PA—DISCO—LIGHTING

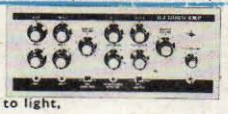

UK's Largest Range—Write phone or call in. Details and demonstrations on request.
DJ30L 3 Channel sound to light unit, 3kW. **£29·50**
DJ40L 3 Channel Mic (Built-in) to light, 3kW. **£38·75**
DJ70S 70 watt Disco amp/mixer, **£49·75**
DISCOAMP 100 watt Disco amp/mixer, **£65·85**
DJ105S 30 watt Disco amp/mixer, **£32·25**
Anti-Feedback Quality Mic., **£11·50**
DJ500 50 watt PA amplifier, **£43·95**
DJ700 70 watt **£52.75**
DJ1000 100 watt **£63·00**
Group 300 150 watt rms Group Valve amplifier, **£86·00**
● **Portable discos—details on request**
● **Credit terms for callers**

FIBRE OPTICS · LIGHTING · MICS · EFFECTS · PROJECTORS · SPOTS · DIMMERS · STANDS · MIXERS · SPEAKERS
Everything for PA — Disco — Lighting.
FREE Stock List Ref. No. 18.

SINCLAIR PROJECT 60 MODULES —SAVE POUNDS



Z30 **£3·57** Z50 **£4·37**
STEREO 60 **£7·97** PZ5 **£3·97**
PZ6 **£6·37** PZ8 **£4·77.**
Transformer for PZ8 **£2·95.**
Active Filter Unit **£4·45.**
Stereo FM Tuner **£16·95.**
IC12 **£1·80** Q16's **£15** pair.
Post, etc. 20p per item.

PACKAGE DEALS Post 25p
2 x Z30, Stereo 60, PZ5 **£15·95**
2 x Z30, Stereo 60, PZ6 **£18·00**
2 x Z50, Stereo 60, PZ8 **£20·25**
Transformer for PZ8 **£2·95**
PROJECT 605 KIT **£19·95**

ELECTRONIC KITS

Henry's introduce new huge range of audio and electronic kits now in stock, everything supplied, tremendous value. Detailed list Ref. No. 14 on request.

IC RECEIVER

ZN414 Radio integrated circuit as featured in Practical Wireless, January, 1973. Article reprint Ref. No. 19. **10p.**

BATTERY TAPE DECK

Garrard 9V tape deck with heads, etc. As previously advertised. Limited quantity. **£9·50.** Post 30p.

LEARN A LANGUAGE

Recorded Cassettes with step by step phrase books. French, German, Spanish, Italian. **£1·36** per course. **£5·00** per set of four.

DISCO SPOTBANK

As illustrated on the front cover of Practical Wireless, April, 1973. **£12·75.** P. & P. 35p.

HI-FI EQUIPMENT

Warehouse prices with BIG DISCOUNTS plus demonstrations (for callers) and GUARANTEES.

FREE 24-page detailed brochure (Ref. No. 17).

★ **You can see the savings** ★

HIGH QUALITY CASSETTES

The best U.K. low noise tapes but at a special price. "Living Sound" cassettes meet the highest international standard (IEC94A). Fantastic price savings.

	C60	C90	C120
3 for	**£1·00**	**£1·33**	**£1·62**
6 for	**£1·80**	**£2·57**	**£3·15**
10 for	**£2·80**	**£4·20**	**£5·00**

Full guarantee. Post paid. Made by EMI especially for Henry's.

ULTRASONIC TRANSDUCERS

Operate at 40kc/s up to 100 yds. Ideal remote switching and signalling. Complete with data and new I.C. circuits.
PRICE PER PAIR **£5·90.** Post 10p.

MARRIOT TAPE HEADS

4 TRACK MONO or 2 TRACK STEREO

"17" High Impedance	**£2·00**
"18" Med. Impedance	**£2·00**
"36" Med.-Low Imp.	**£3·50**
Erase Heads for above	**75p**
"63" 2 track mono — High Impedance	**£1·75**
"43" Erase Head for above	**75p**

7 SEG & NIXIE TUBES

(Post 15p per 1 to 6)

XN3, XN13, GN6 0–9 side view with data, **85p.**
GNP-7, GNP-8 0–9 side view with decimal points and data, **95p.**
3015F 7 seg. **£2** each, **£7** per 4 with data.
12 and 24 hour clock circuits. Ref. No. 31 **15p.**

MINIATURE AMPLIFIER

5 transistor. 300mW o/p. Fitted volume and sensitivity control 9 volt operated. **£1·75** each, p.p. 15p.

QUALITY SLIDER CONTROLS

60mm stroke singles and ganged. Complete with knobs. 5kΩ, 10kΩ, 25kΩ, 100kΩ, 250kΩ, 500kΩ. 1 meg. Log and Lin. **40p** each, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, Log and Lin. ganged. **60p** each.

VAT All prices are exclusive of 10% VAT which must be added to all orders inc. carr./packing. (Note: Catalogue is not subject to VAT).

See earlier page of this magazine for transistors, I.C.'s and Semiconductor prices. Latest List Ref. No. 36 on request

E & O E

Henry's RADIO LIMITED

EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
354-356 High Fidelity and Tape Equipment 01-402 5854/4736
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Open:- 9 am-6 pm 6 days a week (309 closed Thursday) All stores open all day Saturday