RADIO-ELECTRONIC ENGINEERING EDITION

RADIO & TELEVISION NEWS

FEBRUARY
1954

INCLUDING
TV & RADIO ENGINEERING

IN THIS ISSUE

RIDGE TRANSISTOR TESTER

CAST WAVE GUIDES

ERROR VOLTAGE DETECTOR

TRANSISTOR CONTROL OF MAGNETIC AMPLIFIERS

INTERNATIONAL TELECOMMUNICATIONS

A CITIZENS BAND GARAGE DOOR CONTROL


OLOR RECEIVER ALIGNMENT

AMATEUR'S 4-TUBE SUPERHET

PICTURES ON TAPE


RESISTOR TRIAL BY TEST

(See Page 68)

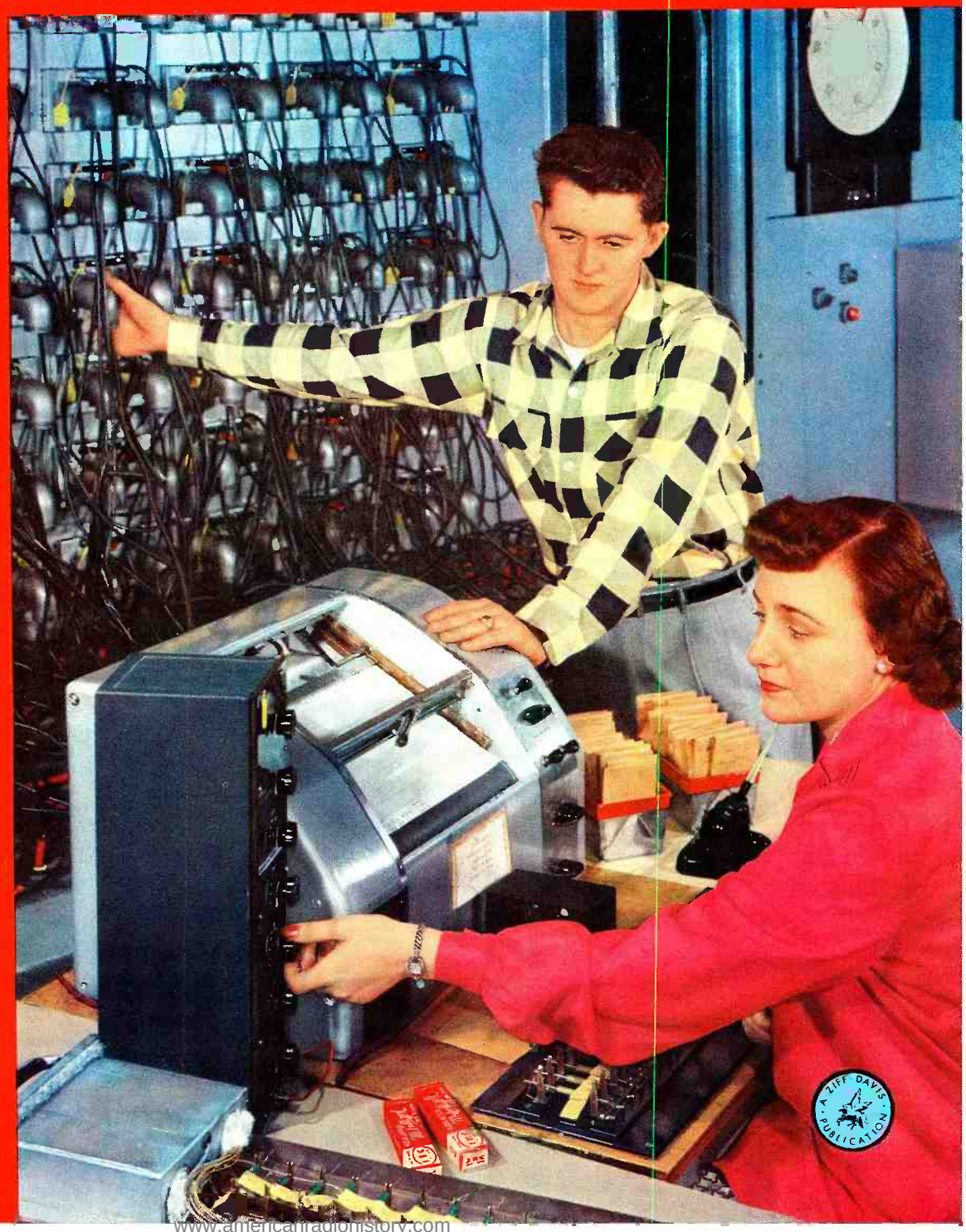

www.americanradiohistory.com

CALL BACKS COST MONEY...

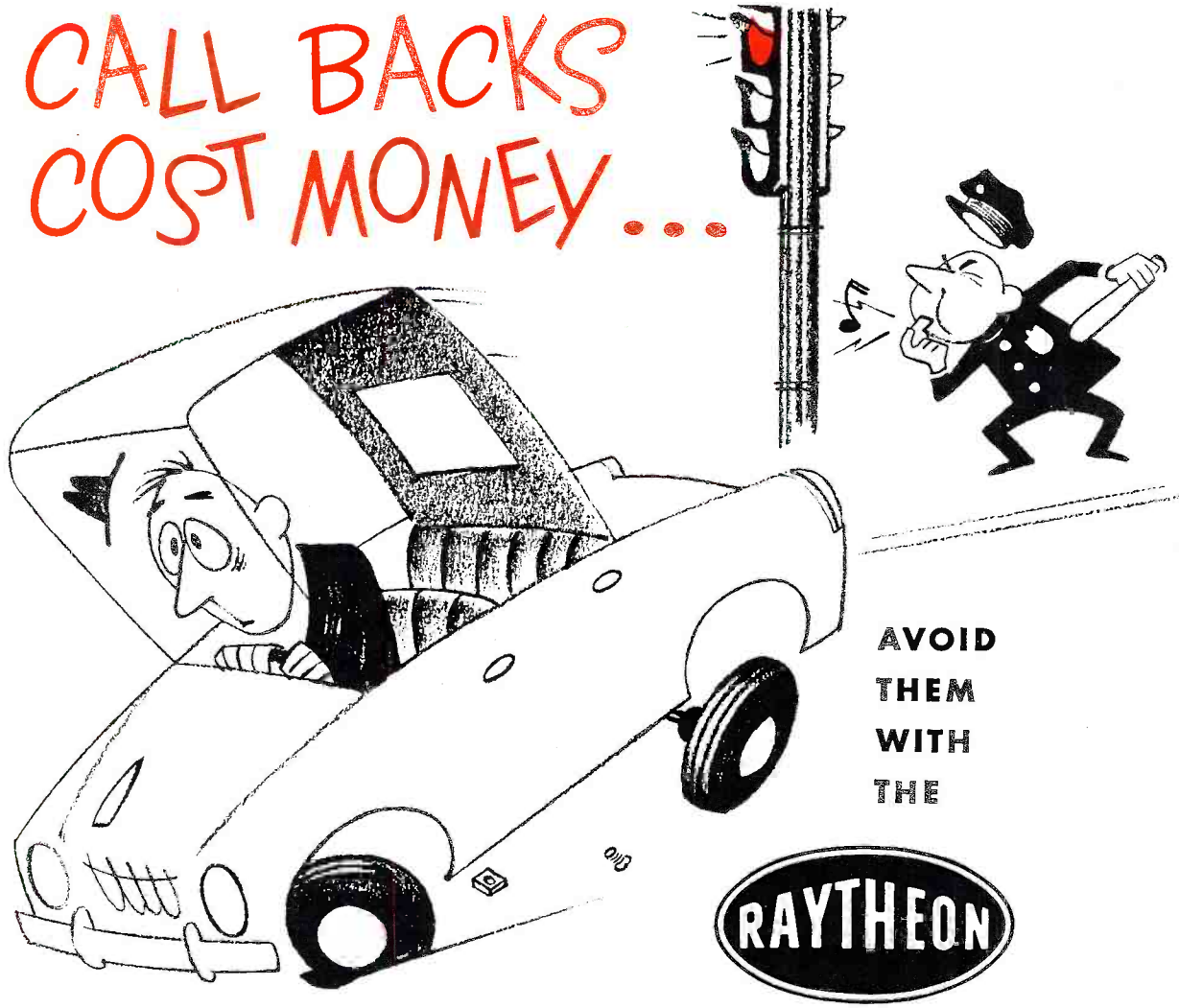

AVOID THEM WITH THE

RAYTHEON

SERVICE SAVER PLAN

available through your RAYTHEON TUBE DISTRIBUTOR

The Raytheon Service Saver Plan, which permits customers to identify about 85% of all the troubles that may occur on the screen of a defective TV receiver — *and accurately transmit this information to the Service Dealer via telephone* — is helping to minimize costly call-backs two ways.

First, when a Service Dealer goes on a call knowing in advance what ails a TV receiver (thanks to Raytheon's Service Saver Plan), he goes completely equipped to do the job — no more running back to the shop for tubes or parts.

Second, customers frequently call about TV receiver trouble when a minor control adjustment is all that is needed to correct the fault. The Raytheon Service Saver Plan helps Service Dealers avoid these needless, unprofitable calls.

Ask your Raytheon Tube Distributor to tell you how to put the Raytheon Service Saver Plan to work for you.



RAYTHEON RADIO AND TELEVISION TUBES cut call-backs, too! Their outstanding quality reduces early tube failures to a minimum. Use them. You'll find them Right . . . for Sound and Sight . . . and *you!*

RAYTHEON®

Excellence in Electronics

RAYTHEON MANUFACTURING COMPANY


Receiving Tube Division

Newton, Mass., Chicago, Ill., Atlanta, Ga., Los Angeles, Cal.

RAYTHEON MAKES ALL THESE:

RECEIVING AND PICTURE TUBES • RELIABLE SUBMINIATURE AND MINIATURE TUBES • SEMICONDUCTOR DIODES AND TRANSISTORS • NUCLEONIC TUBES • MICROWAVE TUBES

www.americanradiohistory.com

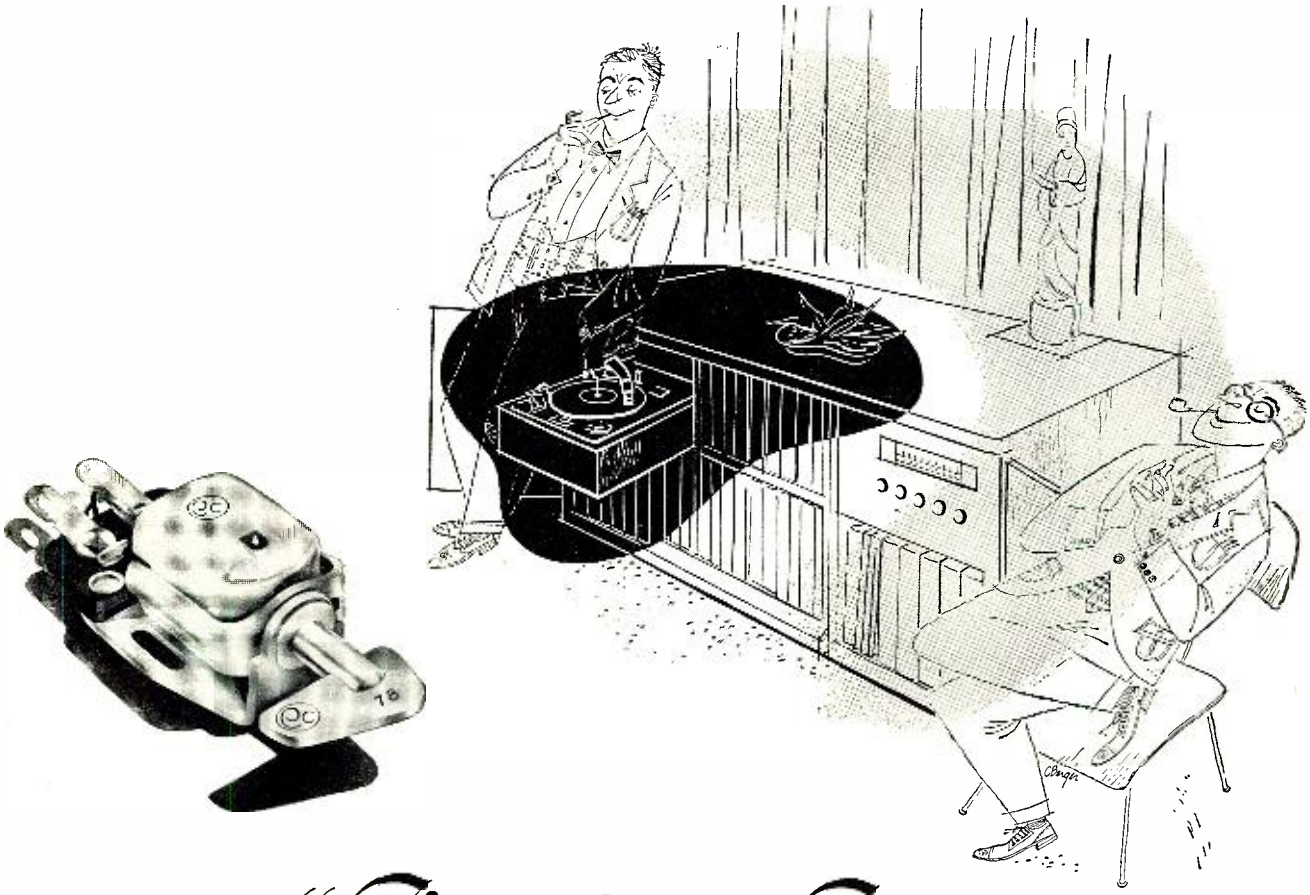

"I'm glad I waited..."

Here's how I solved a problem that bothered me . . . and may be bothering you.

Many of my favorite recordings happen to be 78's. They mean as much to me as any of my newer LP's or 45's. Changing pickups was often a real nuisance—and yet I wasn't willing to give up the superior quality of my two Pickering cartridges.

Last fall my dealer offered a suggestion. "Wait a little longer," he said. "You'll be glad you did."

He was right. I now have Pickering's new turn-over cartridge. A simple flip of the handy lever and I'm ready to play any favorite that fits my mood—whether it's standard or microgroove. *More than that,* I'd swear my recordings sound better than ever.

I'm glad I waited . . . but you won't have to.

Ask your dealer to show you this convenient new turn-over cartridge. Have him demonstrate it. See if you, too, don't hear the difference!

PICKERING ***and company incorporated • Oceanside, L. I., New York***

PICKERING PROFESSIONAL AUDIO COMPONENTS

"For those who can hear the difference"

...Demonstrated and sold by Leading Radio Parts Distributors everywhere.
For the one nearest you and for detailed literature, write Dept. C-3

RADIO & TELEVISION NEWS is published monthly by Ziff-Davis Publishing Company at 64 E. Lake St., Chicago 1, Ill. Entered as second-class matter July 21, 1948, at the Post Office, Chicago, Ill., under the act of March 3, 1879. Authorized by Post Office Department, Ottawa, Canada, as second-class matter.
SUBSCRIPTION RATES: Radio & Television News—one year, U. S. and Possessions and Canada $4.00; Pan-American countries and all other foreign countries $5.00. Radio-Electronic Engineering Edition—one year, U. S. and Possessions, Pan-American countries, and Canada $6.00; all other foreign countries, $7.00.
Postmaster—Please return undelivered copies under form 3589 to 64 E. Lake St., Chicago 1, Ill.

www.americanradiohistory.com

Editor and Asst. Publisher
OLIVER READ, D.Sc., W4TI

Managing Editor
WM. A. STOCKLIN, B.S.

Technical Editor
H. S. RENNE, M.S.

Service Editor
CHARLES TEPFER

Assistant Editors
P. B. HOEFER
M. C. MAGNA

Television Consultant
WALTER H. BUCHSBAUM

Short-Wave Editor
KENNETH R. BOORD

Art Editor
FRANK SAYLES

Draftsmen
A. A. GANS, W2TSP
J. A. GOLANEK

Advertising Manager
L. L. OSTEN

Midwest Adv. Manager
JOHN A. RONAN, JR.

Western Adv. Manager
JOHN E. PAYNE



COVER PHOTO: This big load-life oven, built to test resistors under load at raised temperatures, is part of the equipment used by IRC in its test program. (See page 68) (Ektachrome by Henry Gregg)

ZIFF-DAVIS PUBLISHING COMPANY

Chairman of the Board and Publisher
WILLIAM B. ZIFF

President
B. G. DAVIS

Vice-Presidents
H. J. MORGANROTH
M. H. FROELICH

Secretary-Treasurer
G. E. CARNEY

Circulation Manager
M. MICHAELSON

BRANCH OFFICES
CHICAGO (1)
64 E. Lake St., AN 3-5200
LOS ANGELES (14)
Statler Center, 900 Wilshire Blvd., Mich. 7856

First in radio-television-audio-electronics

Average Paid Circulation over 230,000

RADIO & TELEVISION NEWS

Reg. U. S. Pat. Off.

Radio News Trademark Reg. U. S. Pat. Office • Television News Trademark Reg. U. S. Pat. Office.

CONTENTS — FEBRUARY, 1954

A Citizens Band Garage Door Control	*Hartland B. Smith, W8VVD*	35
The DU-201 "Duette"		39
A Subminiature Code Practice Oscillator	*Louis E. Garner, Jr.*	40
High Performance Headphone Radio	*Irving Gottlieb*	42
Amateur's 4-Tube Miniature Superhet	*Paul Popenoe, Jr., W6IWM*	43
QRZ Mobile	*Leon A. Wortman, W2LJU*	46
U.H.F. Measurements	*Dan Lerner & Winston Starks*	48
Pages from a Tape Editor's Notebook (Part 4)	*Donald C. Hoefler*	50
Color Receiver Alignment	*Walter H. Buchsbaum*	52
Pictures on Tape		55
Certified Record Revue	*Bert Whyte*	56
Know Your 1954 Admiral TV Receivers	*Admiral Corp. Service Dept.*	57
The Music Probe for Faster Servicing	*Stan Johnson, WØLBV*	61
Positive Grid Circuits in TV Receivers	*Milton S. Kiver*	62
Waveform Tracing Aid	*Louis E. Garner, Jr.*	64
The Scott 99-A Amplifier	*Victor H. Pomper*	66
Resistor Trial by Test	*Guy B. Entrekin*	68
A New Line of Hi-Fi Speakers	*Harry F. Olson & John Preston*	69
Mac's Radio Service Shop	*John T. Frye*	74
New TV Stations on the Air		94
The Tri-Pole Antenna	*Dr. Yuen T. Lo*	104
World's Most Powerful Radio Transmitter		112
TV on Mt. Fuji	*Koichi Kasahara*	120
New TV Grants Since Freeze Lift		128
Radio-TV Service Industry News		160
Wireless Ops of Old	*C. Howard Bowers*	186
Service Hints on Admiral TV Sets		188

DEPARTMENTS

For the Record	*The Editor*	8	What's New in Radio	92
Spot Radio News		16	New TV Products	134
Within the Industry		24	Manufacturers' Literature	177
Short-Wave	*K. R. Boord*	76	New Audio Equipment	180

Technical Books 192

COPYRIGHT 1954
(All Rights Reserved)
ZIFF-DAVIS PUBLISHING COMPANY
Editorial and Executive Offices
366 Madison Ave., New York 17, N. Y.

VOLUME 51 • NUMBER 2

Member
Audit Bureau of
Circulations

SUBSCRIPTION SERVICE: All communications concerning subscriptions should be addressed to Circulation Dept., 64 E. Lake St., Chicago 1, Ill. Subscribers should allow at least four weeks for change of address.

CONTRIBUTIONS: Contributors are advised to retain a copy of their manuscripts and illustrations. Contributions should be mailed to the New York Editorial Office and must be accompanied by return postage. Contributions will be handled with reasonable care, but this magazine assumes no responsibility for their safety. Any copy accepted is subject to whatever adaptations and revisions are necessary to meet the requirements of this publication. Payment covers all author's, contributor's, and contestant's rights, title, and interest in and to the material accepted and will be made at our current rates upon acceptance. All photos and drawings will be considered as part of the material purchased.

www.americanradiohistory.com

Now IN YOUR OWN HOME Learn TELEVISION RADIO-ELECTRONICS the Amazingly Effective D. T. I. WAY



NO PREVIOUS EXPERIENCE NEEDED

NOW . . . get EVERYTHING YOU NEED for real Laboratory-type training AT HOME

Above: Work over 300 fascinating experiments with this equipment





Build and keep this BIG DTI engineered TV set—easily converted to U.H.F.

1. Build over 300 fascinating experiments from 16 BIG SHIPMENTS of Electronic-Radio parts which you KEEP.

2. Build valuable commercial-type test equipment—as shown to the left—which you KEEP. This includes a quality 5 INCH oscilloscope and jewel bearing Multi-Meter—both highly useful for Television work.

3. Build and keep a big 21 INCH TV Set. (D.T.I. offers another home training in Television-Radio-Electronics, but without the TV set.)

4. Use a 16 mm. movie projector and new series of highly instructive movies—a wonderful aid to help you grasp important fundamentals faster . . . easier . . . better.

5. Enjoy well-illustrated, easy-to-read lessons with handy FOLD-OUT diagrams.

6. Get an honest-to-goodness EMPLOYMENT SERVICE to help you get a good job after graduating—or assistance in starting your OWN SALES AND SERVICE BUSINESS. Mail coupon today for the complete details.

—with the aid of BOTH HOME EQUIPMENT and HOME MOVIES

What will mailing the coupon below *do for YOU?* Just this! You'll find out about one of today's most remarkable . . . practical ways to prepare to get into America's amazing billion dollar opportunity field of TELEVISION-RADIO-ELECTRONICS. You'll see how to get into fascinating work that pays well . . . that offers one of America's most promising futures . . . that enables you to start your own business almost "on a shoe string," if you prefer this to a job opportunity.

And above all, you'll get some GOOD NEWS especially welcomed by men anxious to earn REAL MONEY in this thrilling field. For you'll see that NOW you can get the kind of practical, laboratory-type training so desirable for making real progress in Television-Radio-Electronics *AND WITHOUT* LEAVING HOME.

You'll see that DeVry Technical Institute sends everything needed to set up your own HOME LABORATORY. You get and keep the same type of basic electronic equipment used in our modern Chicago Training Laboratories. You get home training that includes the knowledge and experience gained from training thousands of students first hand in Chicago. And to top it all, you use DTI's amazingly effective and exclusive home training aid—INSTRUCTIVE MOVIES. But why not get the complete story? Mail coupon today for information-packed literature.

MODERN LABORATORIES

If you prefer, get all your preparation in our new Chicago Training Laboratories—one of the finest of its kind. Ample instructors, modern equipment. Write for details!

MILITARY SERVICE!

If you're subject to military service, the information we have for you should prove very helpful. Mail coupon today.

Get this information-packed publication



FREE!

Mail Coupon Today



"ONE OF AMERICA'S FOREMOST TELEVISION TRAINING CENTERS"
— Established 1931 —

DEVRY TECHNICAL INSTITUTE
AFFILIATED WITH
DEFOREST'S TRAINING, INC.
CHICAGO 14, ILLINOIS

DEVRY TECHNICAL INSTITUTE RN-2-K
2533 N. Ashland Avenue, Chicago 14, Ill.

I would like your valuable information-packed publication showing how I can get started toward a good job or my own business in Television-Radio-Electronics.

Name_____ Age_____

Street_____ Apt._____

City_____ Zone_____ State_____

www.americanradiohistory.com


FOR ALL OF TODAY'S REPLACEMENT CONTROL NEEDS



IRC Volume Control Plant, Asheville, North Carolina.


Name your requirement; it's in full production *now* at IRC's new volume control manufacturing plant. From no other single source can you get such wide replacement coverage. And no other replacement control gives you the IRC combination of easy installation and trouble-free performance.

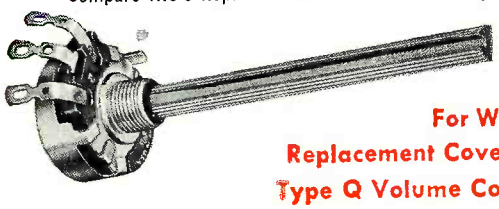Compare IRC's Replacement Control Line with any other:




For Widest Replacement Coverage Type Q Volume Control

82 values—7 tapers—give greatest TV, AM, FM coverage with least stock. Flatted, knurled and slotted Knobmaster Fixed Shaft fits most knobs without alteration. 13 Interchangeable Fixed Shafts give fast conversion to "specials" with fixed shaft security. Small ¼" long bushing and compact 15/16" design ideal for small sets—yet handle large set needs as well. Cushioned-turn rotation. Quiet element. Handsome appearance.

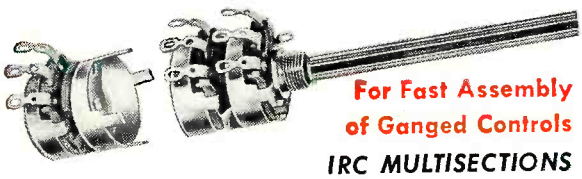

For Fast Assembly of Ganged Controls IRC MULTISECTIONS

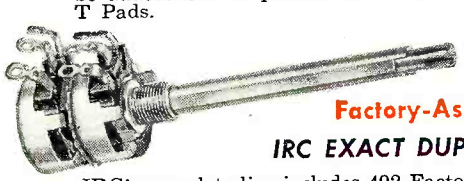In just a few minutes you can assemble standard duals, triples, even quadruples—with IRC Multisections and Q Controls. Simply remove control cover and attach Multisection. Over 15,000,000 combinations. 20 resistance values. Switches can be added. Use to provide low-cost L Pads and T Pads.




Factory-Assembled IRC EXACT DUPLICATES

IRC's complete line includes 492 Factory-Assembled Exact Duplicate Concentric Duals. Mechanical fit and electrical operation double-money-back guaranteed—specifications are based on set manufacturers' procurement prints. Resistance values are matched; tapers are closely followed; shaft lengths are never less than manufacturers' nominal—never more than 3/32" longer. Cover more than 5,000 TV sets. Carbon and wire wound.

For Concentric Duals in Less Than A Minute IRC CONCENTRIKITS



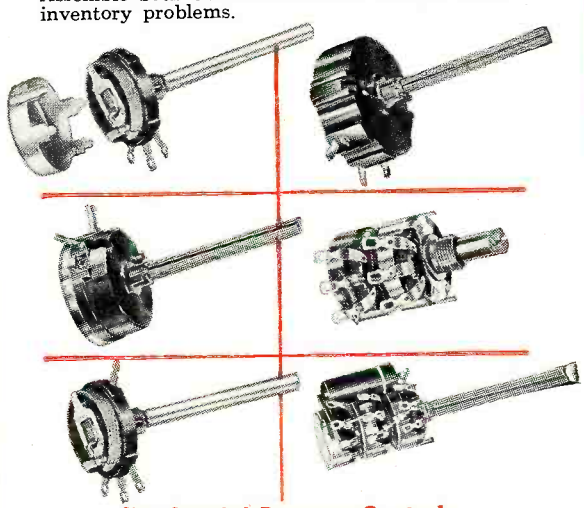Here's coverage of more than 5,000 TV models. Revolutionary 4-piece Universal Concentrikits assemble with shafts and elements in less than a minute to give you the exact duplicate replacement control you want. Mechanical fit and electrical operation double-money-back guaranteed. Assemble both carbons and wire wounds. Fewer inventory problems.



For Special Purpose Controls IRC's Complete Line

2-Watt Wire Wounds—2 styles, full rounded shaft and Knobmaster shaft. *High Voltage Controls*—2-watt carbon-element control with Knobmaster shaft. *4-Watt Wire Wounds*—2 styles, short, knurled and slotted shaft or Knobmaster shaft. *TV Attenuators*—Carbon-element control for adjustment of signal input. *TV Centering Controls*—2-Watt Wire Wound Control with centering tap. *Loudness Controls*—Continuously variable, bring higher fidelity to ordinary audio.

No other brand of replacement controls offers you wider variety — greater efficiency. Send for New IRC Control Catalog DC1D.

...service on all your control ...Distributor.

IRC

INTERNATIONAL RESISTANCE COMPANY

Wherever the Circuit Says —


www.americanradiohistory.com



Arthur Godfrey, famous CBS-TV star


GET BETTER THAN NEW-SET PERFORMANCE

WITH CBS-HYTRON MIRROR-BACK SCREEN

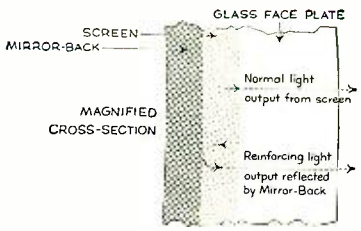


Mirror-Back (aluminized) screen mirrors *all* the light output to the viewer. Offers: Brighter pictures. Greater contrast. Better resolution. Reduced strain on other components. Full effective anode potential. Prevention of cross-burns. And longer life. For greater customer satisfaction . . . more profit, replace with original CBS-Hytron Mirror-Back tubes. Many types now available.

WITH CBS-HYTRON BLUE-WHITE SCREEN

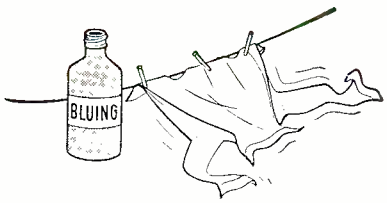


Ever notice how a shirt laundered with bluing appears whiter? With the CBS-Hytron Blue-White screen, whites are whiter; blacks, blacker. Expanded gray scale gives noticeably sharper pictures in fringe areas. No wonder CBS-Hytron's original Blue-White screen has become the universally preferred standard. Your customers, too, will prefer Blue-White screens.

WITH CBS-HYTRON SMALL-SPOT GUN

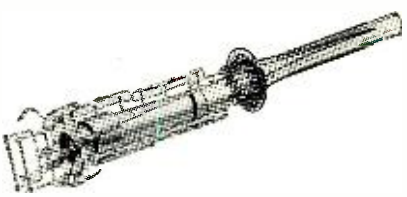

Smaller the spot produced by electron beam, sharper the picture. New lens focusing system of CBS-Hytron Small-Spot Gun reduces spot size 30 per cent. Prove it. Replace with a new CBS-Hytron Small-Spot tube. *See*, yourself, the superior resolution. Profit more. Combine all three: CBS-Hytron Mirror-Back . . . Blue-White Screen . . . Small-Spot Gun. Get and give that better-than-new-set thrill!

LOOK TO CBS-HYTRON FOR COLOR, TOO!

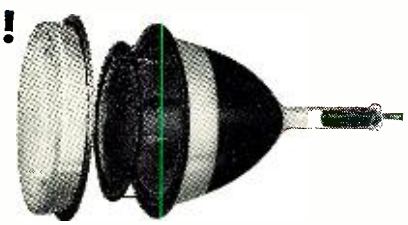

New CBS-Colortron stresses simplicity. Offers many advantages: Simpler construction. Fool-proof assembly. Lower cost. Lighter weight. Adaptability to mass production in large sizes. Improved contrast. Simplified focusing . . . circuitry . . . adjustment. Resistance to overload. Greater stability. All stemming from unique spherical mask and face plate. You'll appreciate these advantages when *you* start servicing color TV.

FREE CATALOG . . . CBS-HYTRON BUSINESS BUILDERS



Describes all CBS-Hytron Business Builders to date: *Certified* Quality Service tags, streamers, decals, illuminated and flange signs, clocks, postal cards, and ad mats. The famous CBS-Hytron service tools. Technical literature. Price lists. Special offers. Get your Business Builders Catalog, PA-37, today . . . from your distributor, or direct.

NEW . . . *FREE* CBS-COLORTRON DATA

For a look into the future, get complete advance data on the new, revolutionary CBS-Colortron: Construction . . . operation . . . application . . . installation and adjustment . . . electrical and mechanical data. FREE . . . from your CBS-Hytron distributor . . . or direct.



CBS HYTRON

Manufacturers of Receiving Tubes Since 1921

CBS-HYTRON Main Office: Danvers, Mass.

A Division of Columbia Broadcasting System, Inc.

A member of the CBS family: CBS Radio • CBS Television Columbia Records, Inc. • CBS Laboratories • CBS-Columbia • and CBS-Hytron

RECEIVING • TRANSMITTING • SPECIAL-PURPOSE • TV PICTURE TUBES • GERMANIUM DIODES AND TRANSISTORS


www.americanradiohistory.com


Electro-Voice EV
CARTRIDGES
Guarantee
FINER REPRODUCTION
LONGER RECORD LIFE
MORE NEEDLE PLAYS



MODEL 43
Ceramic Cartridge. Plays 78, 45, 33⅓ rpm with single 2.3-mil all-purpose needle-tip. Output .7 to 1.0 volt.
43. Osmium. List $6.50
43-S. Sapphire. List $7.50

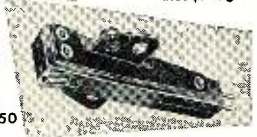MODEL 44
Ceramic Cartridge. Plays 45 and 33⅓ rpm. with 1-mil needle. Impervious to heat and humidity. Output .7 volt.
44. Osmium. List $6.50
44-S. Sapphire. List $7.50




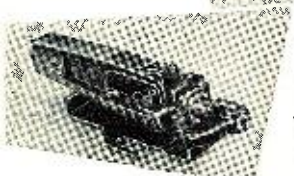

MODEL 46-T
Ceramic Turnover. Plays 78, 45, 33⅓ rpm with separate 3-mil Osmium and 1-mil Sapphire tip needles. Output .7 volt. With turnover mechanism.
46-T. List $10.00
46. Without turnover mechanism. List $9.00

MODEL 16-TT
Crystal Twin Tilt. Uses one piece twin tip needle for 78, 45, 33⅓ rpm. Merely turn selector handle for 1-mil Sapphire or 3-mil Osmium tip. Output 1 volt.
16-TT. List $10.00
16. Same without tilt mechanism. List $9.00



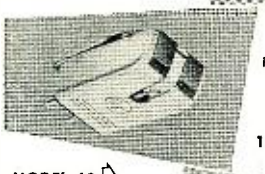

MODEL 12
Crystal Cartridge. Plays 78 rpm with 3-mil needle. Light weight. High compliance. Tracks perfectly. Output 2 volts. With snap-in holder.
12. Osmium. List $7.50
12-S. Sapphire. List $8.50

MODEL 60
Crystal Duo Volt. Permits selection of high or medium output (2 or 4 volts on 33⅓-45, and 3 or 6 volts on 78). No soldering. Uses any standard 3-mil, 1-mil or all purpose needle. ½" mounting hole centers.
60. Less needle. List $4.95



6 BASIC TYPES make over 92% of all replacements

With these preferred types, you can quickly make most replacements. By demonstrating the improvement in performance, you can make many more sales. Furthermore, the new E-V high output, high compliance, permanent Ceramic Cartridges are not affected by moisture or heat—and are directly interchangeable with silent-needle type crystal cartridges that do not use a thumb screw. E-V cartridges are widely used in original equipment and for replacement. *Send now for FREE Phono-Cartridge Replacement Chart No. 170-A.*

Crystal cartridges licensed under Brush patents.

Electro-Voice
BUCHANAN • MICHIGAN

For the RECORD

BY THE EDITOR

RETROSPECT

ONE of the greatest thrills that I have had during the past 15 years as your editor was the expected announcement by the FCC on December 17 of last year giving approval of a compatible color television system. Our readers may recall my editorial four years ago which was written several months prior to any decision or approval for any color television system. The title of my editorial was, "Why The Rush For Color Television?" and in that editorial I made the following statement: "Several of the systems under development do show promise. Unfortunately, the better systems fall short of being compatible. It may be that a combination of systems can be devised, utilizing the best features of each, which will result in something really worth considering. Only time will tell."

And time did tell! The events that followed are now a matter of record and in spite of the fact that the FCC saw fit to give the nod to the *CBS* incompatible revolving color disc system on September 1, 1950 our faith in our industry's ingenuity and know-how remained unshaken. In my editorial of December, 1950 I stated: "Dealers and servicemen are already feeling the impact, not only of the FCC's color decision, but the attendant publicity which implies that color service will soon be available on full schedule. Such publicity creates doubt in the minds of the public as to the advisability of purchasing a present black-and-white television set." Remember those promises in the dailies?

In this same editorial I said: "Must servicemen be emissaries to John Q. Public in an attempt to convince him that the FCC just couldn't wait for some practical method for color television that, according to most engineers, can be fully developed within a reasonably short time? Is it unreasonable to assume that within a short length of time there will be developed an acceptable compatible television system, employing new developments and making use of those already under test?" And I concluded with the following: "These United States are blessed with the finest electronic technicians in all the world. Is it not probable that this 'brain power' will develop a real honest-to-goodness compatible television system for the public? Developments in recent months have definitely shown real progress in the dot-simultaneous system, the tricolor tube and others, to the point where it is quite probable that the entire goal in achieving a flicker-free compatible color television system may be almost at arm's reach. This feeling is shared by the vast majority in the television industry who know what can be perfected to give the public what it really wants, and not what the FCC and *CBS* want it to have. It now appears that the *CBS* system (except for superior rendition) is so impractical that it may die out when the public learns all the facts . . ."

The following months saw the acquisition of *Hytron* and *Air King* by *CBS*. That was in 1951. *Hytron* has since made a great contribution to color tube development (RADIO & TELEVISION NEWS, December, 1953) and has made other contributions towards a compatible system. *Hazeltine,* in 1951, also produced a satisfactory color picture using only a 4 mc. bandwidth for the picture information. It is interesting to here note that *RCA* has now recorded color video information on magnetic tape approaching this same bandwidth (see page 55). *Bell Laboratories, General Electric, Philco,* and others were undertaking extensive research during this period.


The NTSC was organized to study the entire matter of compatible television circuitry and to place recommendations before the FCC for their consideration. Fortunately the Korean situation held back further color development for some time.

In my editorial of June, 1951 I said: "At least one highly qualified observer has expressed the opinion that when engineers can agree on such a system and can back their decision up with experimental evidence, they will receive a favorable hearing from the FCC, irrespective of the Supreme Court decision in the present controversy. It appears, then, that in spite of the defense emergency, an all-electronic, compatible, high-quality color television system will be available for the general public within a reasonable period of time. We have stated many times that the public may be the deciding factor in the final choice of a color television system—and we still believe that to be so, regardless of legal entanglements and public gimmicks."

The smoke of battle has cleared. No individual or laboratory can claim all the glory and credit for producing compatible color TV. It has been a combined industry effort! We'll wind this column up as we did in June, 1951: "One thing is certain—if the television set owner has not had the opportunity of witnessing good color television he has missed the thrill of a lifetime in video enjoyment." O.R.

www.americanradiohistory.com

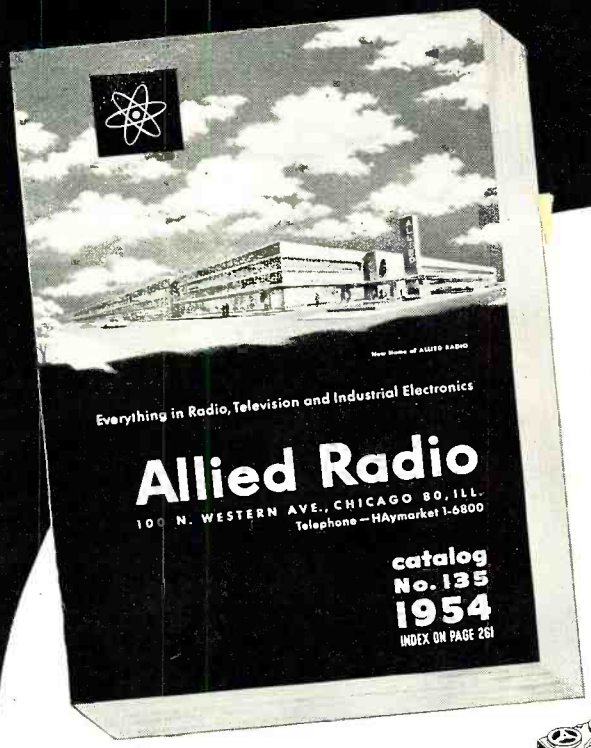
the only COMPLETE catalog for Everything in TV, Radio and Industrial Electronics



FREE value-packed


1954 ALLIED

268-PAGE CATALOG

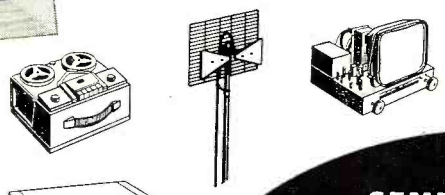

The World's Largest Stocks

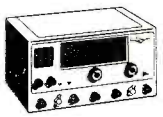- TV and Radio Parts
- Test Instruments
- High-Fidelity Equipment
- Custom TV Chassis
- AM, FM Tuners and Radios
- Recorders and Supplies
- P.A. Systems, Accessories
- Amateur Station Gear
- Builders' Kits, Supplies
- Equipment for Industry









SEND FOR IT TODAY

Get ALLIED'S latest catalog—268 pages packed with the world's largest selection of quality equipment at lowest, money-saving prices. See all the latest releases in custom TV chassis, TV antennas and accessories; AM and FM tuners and radios; *everything* in High-Fidelity custom components; latest P. A. Systems and accessories; recorders and supplies; Amateur receivers, transmitters and station gear; specialized industrial electronic equipment; test instruments; builders' kits; huge listings of parts, tubes, tools, books—your choice of the world's *most complete stocks* of quality equipment. ALLIED gives you *every* buying advantage: speedy shipment, expert personal help, lowest prices, assured satisfaction. Get the big 1954 ALLIED Catalog. Keep it handy—and save time and money. Send for your FREE copy today.

SAVE ON EVERYTHING IN ELECTRONICS

Fastest Service in Electronic Supply

NEW HOME OF ALLIED RADIO
ultra-modern facilities
TO SERVE YOU BEST



SEND FOR THE LEADING ELECTRONIC BUYING GUIDE FREE!



ALLIED RADIO
World's Largest Electronic Supply House

EASY PAY TERMS

Use ALLIED'S liberal Easy Payment Plan—only 10% down, 12 months to pay—no carrying charge if you pay in 60 days. Available on Hi-Fi and P.A. units, recorders, TV chassis, test instruments, Amateur gear.

TV and HI-FI SPECIALISTS

To keep up with developments in High-Fidelity and TV, look to ALLIED. Count on us for *all* the latest releases and largest stocks of equipment in these important fields. If it's anything in High-Fidelity or Television—we have it *in stock!*

ALLIED RADIO CORP., Dept. 1-B-4
100 N. Western Ave., Chicago 80, Illinois

☐ Send FREE 268-Page 1954 ALLIED Catalog

Name_____

Address_____

City_____ Zone____ State_____

www.americanradiohistory.com

ADJUSTABLE


for added gain on the cha

NEW 82 CHANNEL FALCON "VARI-CON"

- Provides all channel reception, VHF and UHF!
- Variable patterns eliminate ghosts and co-channel interference!
- Single lead-in operation!
- Provides a very sharp lobe on UHF!
- Provides excellent reception on VHF while peaked for UHF!
- With two-bay model, you can point and peak one antenna in one direction and point and peak the other bay in another direction — obtaining excellent results from both with but a single lead-in!
- No isolation transformer or network to give trouble, attenuate the signal, or add to installation cost!
- Low, low price!


VARIABLE PATTERNS OVERCOME "GHOST" AND CO-CHANNEL PROBLEMS

With other antennas you're "stuck" with a fixed pattern that nothing short of a hack-saw can change. NOT SO WITH THE "VARI-CON"! By changing the angle of the dipole elements — and it takes only seconds — it is possible to shift the positions of minor lobes and nulls to fit any particular reception problem. There are very few cases of ghost or co-channel interference that can't be quickly solved by use of the "VARI-CON".

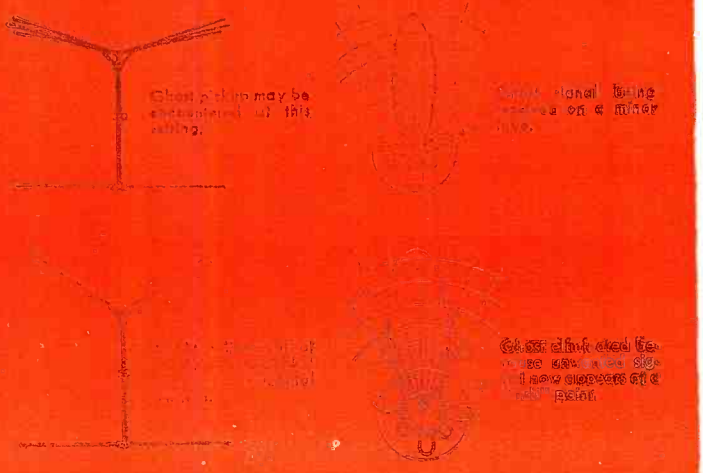


TOTAL ASSEMBLY AND PEAKING TIME — 10 SECONDS!

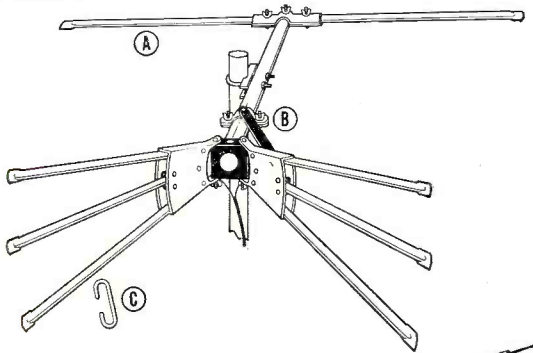You only need swing reflector elements (A) into position and tighten wing nuts. Slide adjusting sleeve (B) to calibrated channel range on which added gain is desired and tighten wing nuts. It's just like opening an umbrella. Remove retaining clamps (C) from dipole elements; the elements automatically fan out and are locked securely in position by snap-action spring assemblies.




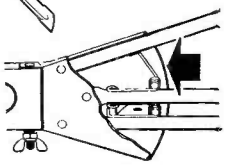Once opened the elements are locked in rigid, vibration-proof position by the 90° angle of the arms. Spring action is NOT employed to hold elements in position.



www.americanradiohistory.com


nnels of your choice...

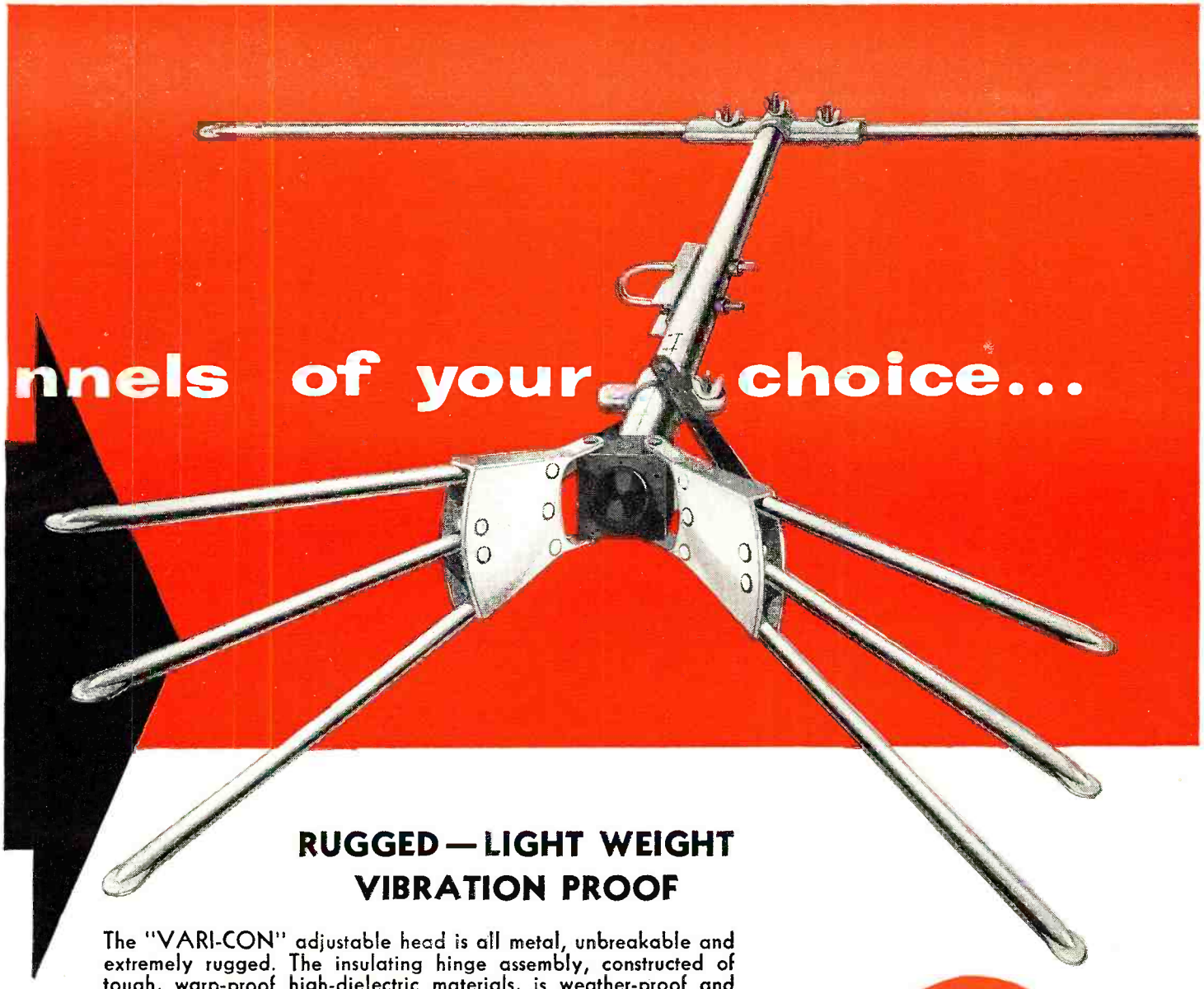

RUGGED — LIGHT WEIGHT VIBRATION PROOF


The "VARI-CON" adjustable head is all metal, unbreakable and extremely rugged. The insulating hinge assembly, constructed of tough, warp-proof high-dielectric materials, is weather-proof and can't short out. Full 48 inch elements are used, yet weight has been kept to a minimum without sacrificing rigidity.

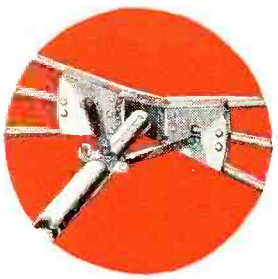The FALCON "VARI-CON" gives you all the desirable features of a conical PLUS adjustable, calibrated channel range peaking — for added gain where you need it . . . variable patterns, to cope with those difficult ghost and co-channel problems, plus all-channel VHF & UHF coverage! Give your customers the best — the FALCON "VARI-CON"!



Heart of the "VARI-CON"

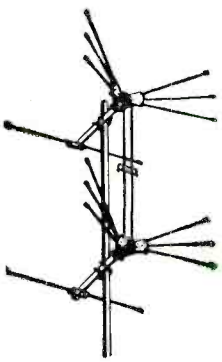FALCON ELECTRONICS COMPANY, 2003 Cedar St., Quincy, Ill.



Stack VARI-CONs for even higher gain! One bay can be pointed and peaked in one direction, and the other bay pointed and peaked in a different direction. Three bay models also available.



www.americanradiohistory.com

$5,600
IN PRIZES

... easy to win

503
PRIZES!

$2000 - 1st prize

$500 - 2nd prize, **$100 - 3rd prize**
100 - $10 prizes, **400 - $5 prizes**

HOW TO WIN

To win one of these 503 prizes all you have to do is complete in 25 words or less "I like Pyramid capacitors because_____" You fill in this statement on a Pyramid contest entry blank which can be obtained from any electronic parts jobber selling Pyramid capacitors. You have this entry blank countersigned by your jobber or one of his salesmen and forward it to us attached to a Pyramid Dry Electrolytic Capacitor box top —the top being the part which carries the description of the item. There is no limit to the number of entries which you may make in this contest but each entry must be accompanied by a box top. Full rules for the contest appear on the entry blank.

It's so easy. Here is the kind of statement that might win:

"I like Pyramid capacitors because they always check out perfectly and don't deteriorate and so I know I won't have to call back at my expense."

"I like Pyramid capacitors because the line is so complete that I can always get what I need and don't have to worry about an off-brand capacitor."

PYRAM D



PYRAMID FEATURES:


1. Only one quality—the best at no premium. All Pyramid capacitors are made of materials commanded by rigid military specifications.
2. All Pyramid capacitors are non-hygroscopic.
3. Highest quality insulator material used in all production results in low leakage factor.
4. Exclusive non-contamination technique guarantees close tolerances and no deterioration. Peak performances for life.
5. Pyramid capacitors operate unchanged at ambient temperature of 85° centigrade.
6. Designed by service technicians across the country for their requirements.
7. Individually packaged for protection.
8. Permanently legible, high visibility ratings on each item.
9. 100% absolute electronic inspection before shipment.

Pyramid is in its 10th year as a leading manufacturer of high-quality capacitors.

PYRAMID ELECTRIC COMPANY
1445 HUDSON BOULEVARD
NORTH BERGEN, N. J.

Burton browne advertising

www.americanradiohistory.com

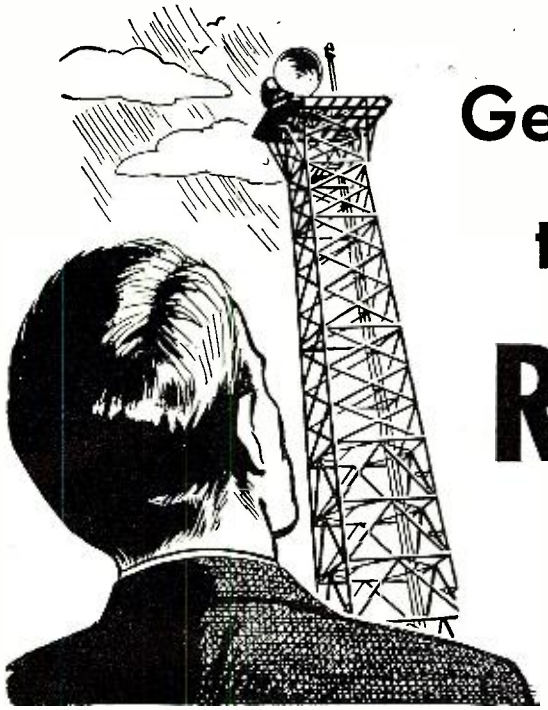

Get yourself on the beam to the BIG MONEY in RADIO AND TV

THAT'S the way to become an expert Radio or Television service man. Study the bedrock theories and principles. These are vitally important. Nothing can take their place—not even the most elaborate kits.

Listen to what radioman R. G. Hamlin of Bay City, Michigan, says, "There's no royal road to learning. I am convinced more than ever after examining the lessons of friends who were lured by the alleged short-cut methods of competitors . . . 'understandability' and 'rememberability' are of utmost importance and I.C.S. lessons qualify on both counts."

I.C.S. offers you two new courses in radio and television servicing—one for beginners, the other for experienced amateurs.

The beginner's course, Radio and Television Servicing with Training Equipment, is extremely thorough. You get extra texts featuring experiments and job assignments. You get equipment second to none. Matched parts for an excellent 5-tube superheterodyne receiver. Your own professional-quality multitester. A complete single generator kit. High-grade servicemen's tools. "Rider's Perpetual Trouble-Shooter's Manual." The principles of Television including the most-up-to-date developments (VHF and Color TV, for example).

The second course quickly reviews the essentials then goes step by step into advanced phases of Radio and Television, including modern methods of installation and repair. Course contains valuable supplementary material. For example, you get a special book giving characteristics of all tubes used in Radio and Television receivers.

Learn by doing! That's the world-famous I.C.S. method. Thoroughly practical. Completely modern. Success proved. The coupon below brings you full details—on Radio and Television Servicing or any of the more than 400 I.C.S. Courses. Mark and mail it *today!*

I. C. S., Scranton 9, Penna.

INTERNATIONAL CORRESPONDENCE SCHOOLS

BOX 2251-D, SCRANTON 9, PENNA.

Without cost or obligation, send me "HOW to SUCCEED" and the booklet about the course BEFORE which I have marked X:

ART
- ☐ Commercial Art
- ☐ Magazine Illustrating
- ☐ Fashion Illustrating
- ☐ Cartooning
- ☐ Sketching and Painting
- ☐ Show Card and Sign Lettering

AUTOMOTIVE
- ☐ Automobile, Mechanic
- ☐ Auto Elec. Technician
- ☐ Auto Body Rebuilding and Refinishing
- ☐ Diesel—Gas Engines

AVIATION
- ☐ Aeronautical Engineering Jr.
- ☐ Aircraft Engine Mechanic
- ☐ Airplane Drafting

BUILDING
- ☐ Architecture
- ☐ Arch. Drafting
- ☐ Building Contractor
- ☐ Estimating
- ☐ Carpenter and Mill Work
- ☐ Carpenter Foreman
- ☐ Reading Blueprints
- ☐ House Planning
- ☐ Plumbing
- ☐ Heating
- ☐ Painting Contractor
- ☐ Air Conditioning
- ☐ Electrician

BUSINESS
- ☐ Business Administration
- ☐ Certified Public Accountant
- ☐ Bookkeeping and Accounting
- ☐ Office Management
- ☐ Stenography and Typing
- ☐ Secretarial
- ☐ Federal Tax
- ☐ Business Correspondence
- ☐ Letter-writing Improvement
- ☐ Personnel and Labor Relations
- ☐ Advertising
- ☐ Retail Business Management
- ☐ Managing Small Business
- ☐ Ocean Navigation
- ☐ Sales Management
- ☐ Short Story Writing
- ☐ Creative Salesmanship
- ☐ Traffic Management

CHEMISTRY
- ☐ Chemical Engineering
- ☐ Chemistry
- ☐ Analytical Chemistry
- ☐ Petroleum—Nat'l Gas
- ☐ Pulp and Paper Making
- ☐ Plastics

CIVIL, STRUCTURAL ENGINEERING
- ☐ Civil Engineering
- ☐ Structural Engineering
- ☐ Surveying and Mapping
- ☐ Structural Drafting
- ☐ Highway Engineering
- ☐ Reading Blueprints
- ☐ Construction Engineering
- ☐ Sanitary Engineering

DRAFTING
- ☐ Aircraft Drafting
- ☐ Architectural Drafting
- ☐ Electrical Drafting
- ☐ Mechanical Drafting
- ☐ Structural Drafting
- ☐ Sheet Metal Drafting
- ☐ Ship Drafting
- ☐ Mine Surveying and Drafting

ELECTRICAL
- ☐ Electrical Engineering
- ☐ Electrician
- ☐ Electrical Maintenance
- ☐ Electrical Drafting
- ☐ Electric Power and Light
- ☐ Lineman

HIGH SCHOOL
- ☐ High School Subjects
- ☐ Mathematics
- ☐ Commercial
- ☐ Good English

MECHANICAL AND SHOP
- ☐ Mechanical Engineering
- ☐ Industrial Engineering
- ☐ Industrial Supervision
- ☐ Foremanship
- ☐ Mechanical Drafting
- ☐ Machine Design-Drafting
- ☐ Machine Shop Practice
- ☐ Tool Design
- ☐ Industrial Instrumentation
- ☐ Machine Shop Inspection
- ☐ Reading Blueprints
- ☐ Toolmaking
- ☐ Gas—Electric Welding
- ☐ Heat Treatment—Metallurgy
- ☐ Sheet Metal Work
- ☐ Sheet Metal Pattern Drafting
- ☐ Refrigeration

POWER
- ☐ Combustion Engineering
- ☐ Diesel—Electric
- ☐ Electric Light and Power
- ☐ Stationary Steam Engineering
- ☐ Stationary Fireman

RADIO, TELEVISION COMMUNICATIONS
- ☐ Practical Radio—TV Eng'r'ing
- ☐ Radio Operating
- ☐ Radio and TV Servicing
- ☐ Television—Technician
- ☐ Electronics
- ☐ Telephone Work

RAILROAD
- ☐ Locomotive Engineer
- ☐ Diesel Locomotive
- ☐ Air Brakes ☐ Car Inspector
- ☐ Railroad Administration

TEXTILE
- ☐ Textile Engineering
- ☐ Cotton, Rayon, Woolen Mfg.
- ☐ Carding and Spinning
- ☐ Warping and Weaving
- ☐ Loom Fixing ☐ Throwing
- ☐ Finishing and Dyeing
- ☐ Textile Designing

Name_____ Age_____ Home Address_____


City_____ Zone_____ State_____ Working Hours_____ A.M. to P.M._____

Occupation_____

Canadian residents send coupon to International Correspondence Schools Canadian, Ltd., Montreal, Canada. . . . Special tuition rates to members of the U. S. Armed Forces.

www.americanradiohistory.com

MEASURABLE

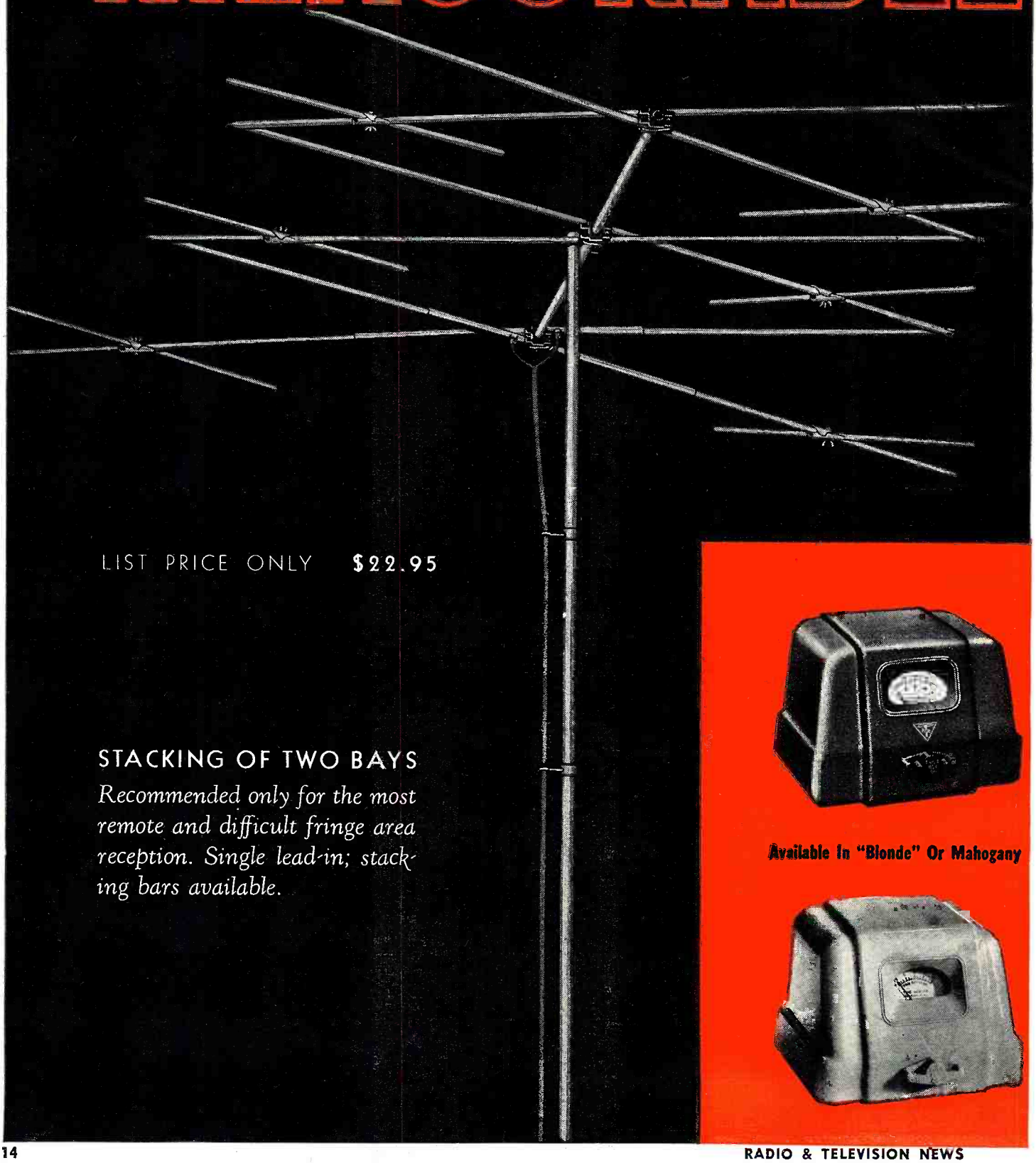

LIST PRICE ONLY **$22.95**


STACKING OF TWO BAYS

Recommended only for the most remote and difficult fringe area reception. Single lead-in; stacking bars available.

Available In "Blonde" Or Mahogany

www.americanradiohistory.com

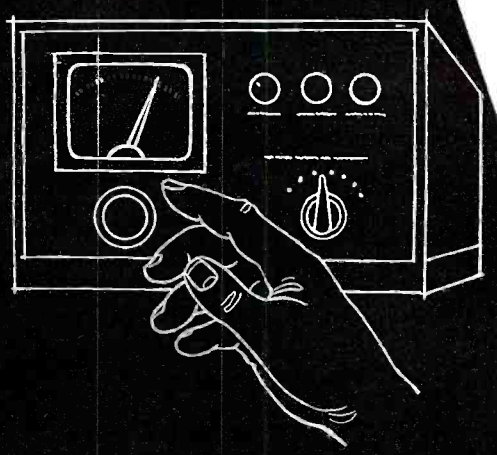higher gain than any other All-Channel VHF Antenna!




New TRIO "TWIN-SIX"

(channels 2-83)

ONE BAY DOES IT ALL

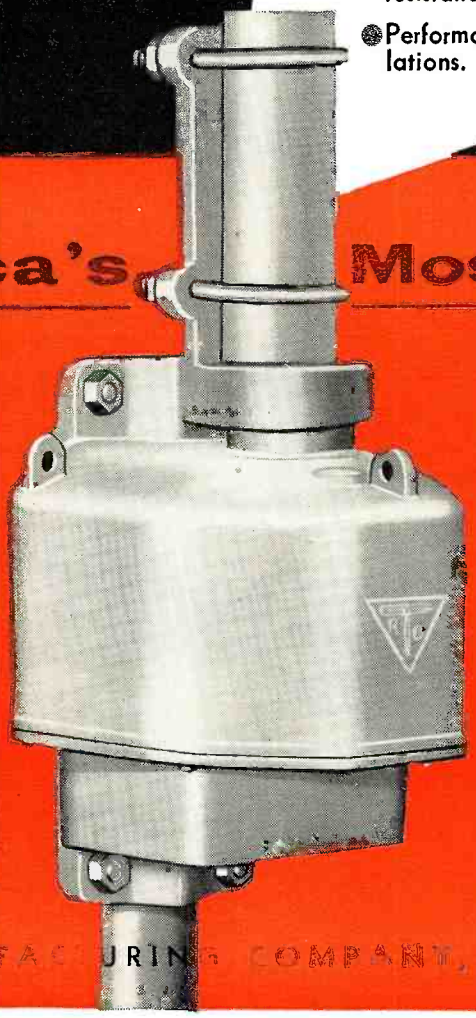- No stacking necessary for most fringe areas.
- Exclusive Zig-Zag principle provides that additional gain.
- Single lead-in operation.
- Excellent UHF reception in primary and near fringe areas.
- Rugged "bridge-type" construction, low wind resistance, attractive appearance.
- Performance proved in thousands of actual installations.



America's Most Dependable TV ROTATOR

- Only rotator that provides a 2 year guarantee.
- Only rotator with 2 motors.
- Only rotator that passes the 200 lb. weight test.



TRIO

TRIO MANUFACTURING COMPANY, GRIGGSVILLE, ILLINOIS

www.americanradiohistory.com

Trav-Electric

DC to AC

CURRENT CONVERTERS
for Land . . . Sea . . . Air

JUST PLUG INTO CIGAR LIGHTER ON DASH
Change 6 or 12 Volt D. C.
to 110 Volt A. C. - 60 cycle



Operates Test Equipment,
All Electric Shavers

SIZE: 2"x2"x3½"

Trav-Electric MIDGET $11.95 List

Model 6-11160, 60 Cycle, 10-15 Watts



OPERATES
- Test Equipment
- Turntables
- Lights
- Short, Long Wave Radios
- Portable Phonographs
- Electric Shavers, etc.

SIZE: 2½"x2½"x4½

Trav-Electric SENIOR $15.95 List

Model 6-1160, 60 Cycle, 35-40 Watts



OPERATES
- Curling Irons
- Radios
- Turntables
- Small Dictating Machines
- Test Equipment,
- Electric Shaver
- Portable Phonographs

SIZE: 4"x5"x6"

Trav-Electric MASTER $24.95 List

Model 6-51160, 60 Cycle, 40-50 Watts



OPERATES
- Wire Recorders
- Amplifiers
- Soldering Iron
- Radios
- Dictating Machines
- Turntables
- Small Electric Drill
- Electric Shaver

SIZE: 4"x5"x6"

Trav-Electric SUPER $37.95 List

Model 6-71160, 60 Cycle, 60-75 Watts

FULLY GUARANTEED
See your Jobber or Dealer

Terado COMPANY

ST. PAUL 14, MINNESOTA

In Canada Write: Atlas Radio Corp., Ltd.
560 King St. West, Toronto 28, Ont.

Export Sales Division: Scheel International, Inc.
4237 N. Lincoln Ave., Chicago 18, Ill. U.S.A.
Cable Address—*Harsheel*

Spot Radio News

*** Presenting latest information on the Radio Industry.**

By RADIO & TELEVISION NEWS' WASHINGTON EDITOR

POLISHING OF THE final script for color TV's princely entrance onto the dazzling stage set for '54, breathlessly awaited not only by the nation but by the world after thousands of turbulent days of delay, practically choked the calendar of the Commission in the closing days of '53.

There were few days that members of the staff and allied groups did not have to meet to discuss some phase of the hue decision as it would appear on the official record. Some sessions lasted for hours and revolved about problems of cost, complexity of receiver design, station changes and additions, compatibility, conversions, term definitions, color fidelity, servicing and installation, and the long-term nature of the standards, plus color-system patents and their criss-cross relationship to members of industry who did and did not participate in the NTSC studies.

In the meantime, set makers were feverishly pushing their pilot lines of color chassis for exhibition at dealer meetings during the annual shows in Chicago, Los Angeles, and New York. Some chassis producers told the Commission that they would have as many as 100 tricolor sets ready for demonstration during these important yearly conclaves.

Officialdom was also notified that one of the four types of color tubes would be used in these models (*RCA, Lawrence, CBS-Hytron,* and *Rauland*) and that corresponding changes in the picture-tube circuitry would obtain in these receivers. Of course, all will follow the basic receiver standards prescribed by the National Television System Committee. Most of the receivers, it was said, would use about 36 tubes, exclusive of the picture tube, and carry tentative list prices of between $795 and $1000.

Industry associations also reported to the Commission that they were considering the publication of a pamphlet aimed at the technician level which would detail some of the key aspects of color TV, and offer answers to basic problems that might be encountered. It was also announced that several manufacturers were planning field lectures on color TV for dealers and technicians, with the association's booklet being used as a classroom primer. Originally, plans called for a series of cooperatively-sponsored talks, but this idea was shelved because of a lack of manpower and also symposium-routing problems.

Two commissioners, George E. Sterling and Headman Rosel H. Hyde, experienced an interesting afternoon of viewing with color a few weeks ago, during the special broadcast of "Carmen" from New York. The government agents sat in the labs of the FCC at Laurel, Maryland, about twenty miles from Washington, and watched the program on test sets supplied by *RCA* and *G-E*. They said that they were extremely impressed with the performance of the broadcast and the receivers' operation.

A SENSITIVE ELECTRONIC device, that is expected to shed some light on the tremendous potential—upwards of 100,000 volts—that exists between our earth and the upper stratosphere, a problem pertinent to long-range communications now, and one that might eventually affect future interplanetary flight, has been developed for the Air Force's Air Research and Development Command.

Weighing but six and one-half pounds, the unit is powered by special batteries and packed with subminiature parts. It is housed in an aluminum case with special insulation which it is expected will minimize the problem of solar radiation and low temperatures found at high altitudes. It was explained that at stratospheric altitudes, although outside air temperatures may be as low as 80 degrees below zero, the sun's rays could generate enough heat inside the instrument to melt some of the parts.

According to one of the research and development engineers on the project, the instrument is so sensitive that it will measure minute flows of electric current—as low as one-million ions per second. (An ion is an atom or group of atoms with an electric charge.)

Carried aloft by huge plastic, free-flying balloons, the instrument instantaneously radios back to a ground-recording station the electrical conductivity, air temperature, and air pressure. By interpreting the temperature and pressure readings, scientists will be able to determine accurately the altitude of the instrument, thus obtaining a record of the variation of the electrical conductivity with the altitude. Upon reaching maximum height, the balloon is mechanically broken and

www.americanradiohistory.com

BLACK BEAUTY® TV TUBULARS

first and still finest... accept no substitutes



Imitation, they say, is the sincerest form of flattery. If so, you who have installed some of the 250,000,000 Black Beauty Telecaps in the past 7 years can be mighty proud. Few Sprague developments have been so closely copied as this capacitor in which you have placed your confidence.

Black Beauty imitations are available in almost every color imaginable . . . including black! But no other molded tubular can equal the unprecedented record set by Sprague TV Tubulars since 1947 when they were first introduced.

Don't be vague — insist on Sprague Black Beauty Telecaps for your TV and radio service needs! There is only one Sprague Black Beauty, *and it has no equal.* Accept no imitations.

Write today for the complete Sprague television and radio service catalog C-609 to Sprague Products Company,* 51 Marshall Street, North Adams, Mass.

There is a Sprague Distributor in every sales area in the United States. Write for the name of your nearest source of supply today.

SPRAGUE

dry-assembly phenolic molded paper capacitors offer:


- extra high insulation resistance
- minimum capacitance change with temperature variations
- absence of drift with repeated heating and cooling

Don't Be Vague...Insist on SPRAGUE

WORLD'S LARGEST CAPACITOR MANUFACTURER

*Sprague Products Company is the Distributors' Division of the Sprague Electric Company

www.americanradiohistory.com

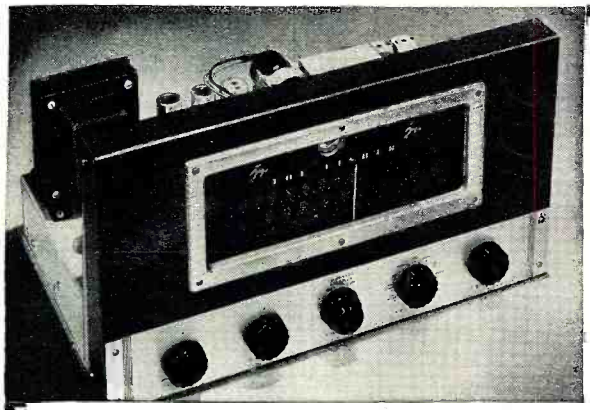

New! And Terrific!


FISHER

SERIES "70"

■ When the FISHER 50-R Tuner and 50-A Amplifier first appeared, two things promptly happened. We were besieged with orders; as well as with requests (from those with limited space) for a tuner with audio control facilities and preamplifier. Many also wanted a low-cost, high output, quality amplifier. It took us time, but here they are. *And they're tops!*


FISHER FM-AM Tuner MODEL 70-RT

■ Features *extreme sensitivity:* (1.5 mv for 20 db of quieting), works where others fail. Armstrong system, *adjustable* AFC plus switch, *adjustable* AM selectivity, separate FM and AM front ends. Complete shielding and shock-mounting on main *and* subchassis. Distortion less than 0.04% for 1 volt output. Hum level: better than 90 db below 2 volts output on radio, better than 62 db below output with 10 mv input on phono. Two inputs. Two cathode-follower outputs. Self powered. Six controls: BASS-AC, TREBLE, VOLUME, LOUDNESS, CHANNEL and EQUALIZATION, TUNING. $184.50

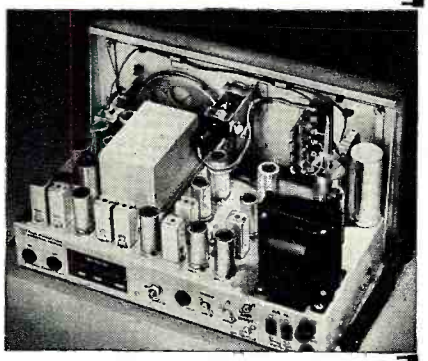

FISHER 25-Watt Amplifier 50-WATT PEAK

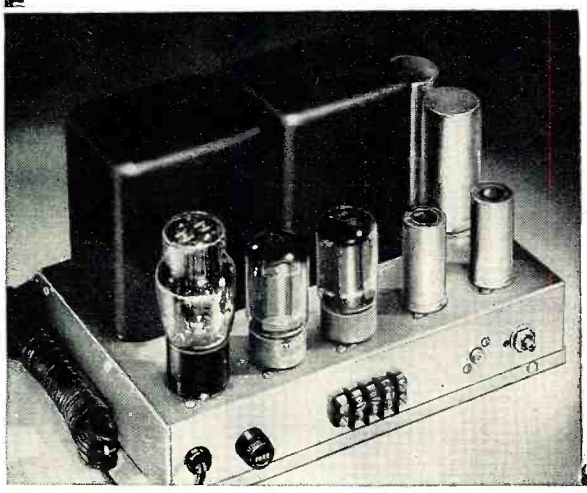■ The FISHER Model 70-A Amplifier offers more *clean* watts per dollar at its price than any amplifier made—25 *clean* watts for only $99.50! The 70-A costs no more than "basic" 10-watt units, but has 150% *greater power!*



■ High output (less than ½% distortion at 25 watts; 0.05% at 10 watts). IM distortion less than 0.5% at 20 watts; 0.2% at 10 watts. Uniform response ±0.1 db, 20-20,000 cycles; 1 db, 10-50,000 cycles. Power output constant within 1 db at 25 watts, 15-35,000 cycles. Hum and noise virtually non-measurable (better than 95 db below full output!) Four separate feedback loops, unique cathode and screen feedback circuit. Outstanding transient response. 8 and 16 ohm outputs. SIZE: 6¾" x 10¼" x 6⅛" high. $99.50

PRICES SLIGHTLY HIGHER WEST OF ROCKIES

Write for full details

FISHER RADIO CORP.
39 EAST 47th STREET • N. Y.

the equipment descends to ground. Additional data is taken on the descent.

The new device, called an *aerial electrometer,* will be carried as high as 100,000 feet. Until now, it has only been possible to collect data on atmospheric electricity from measuring instruments carried by planes reaching a height of 35,000 feet. This ingenious item will make it possible to understand eventually why there is a current of 1800 amperes constantly flowing toward earth; for over fifty years scientists have been trying to discover the source of this tremendous amount of current.

CONELRAD, developed to alert the nation in case of an air attack, can now be activated by over 200 clusters of broadcasters and 500 single stations according to the engineering manager of the National Association of Radio and Television Broadcasters. Should our country ever be attacked, he said, there is no question that the role of the broadcast stations will be equal to that of the defense arm of the military.

Describing the dissemination of the alert signal, he noted that all notifications for alerts and all-clears will be issued by air defense control centers, under the authority of the air division commander or an authorized representative, to all basic key stations. All relay key stations will, in turn, be notified by the basic key stations or other relay key stations. The remaining stations will then be notified by basic key stations or relay key stations. These notifications will be accomplished either by telephone messages or by radio broadcasts. Continuing, the NARTB engineering head said that during the experimental period (midnight to local sunrise) many of the regular key stations may be off the air. All standard, FM, and TV stations have been supplied with the list of *skywave* key stations, at least one of which must be monitored during any period of operation when the regularly-used key station is not on the air.

To receive the alert and all clear, it is mandatory that every standard, FM and TV station has a suitable radio receiver, which should be located at transmitter control. Such a set must be installed regardless of wire-line terminations, such as at the basic key or relay key stations. This ruling was adopted, it was said, to back up any failure that might occur on the wire-line circuits.

In a review of coverage during Conelrad operation, it was pointed out that the system is intended to provide intelligible coverage rather than the usual high type of broadcast quality. This is particularly true, it was emphasized, in areas where the signal intensities are low and where there is rather a wide divergence among the signals of different stations in a sequential cluster. The automatic volume control in the average set can take care of this up to a point, but will not entirely compensate when one signal is considerably weaker and inter-

(*Continued on page* 125)

www.americanradiohistory.com


INCLUDING
TV & RADIO ENGINEERING

RADIO-ELECTRONIC *Engineering* SECTION

Reg. U.S. Pat. Off.

RADIO & TELEVISION NEWS

FEBRUARY, 1954

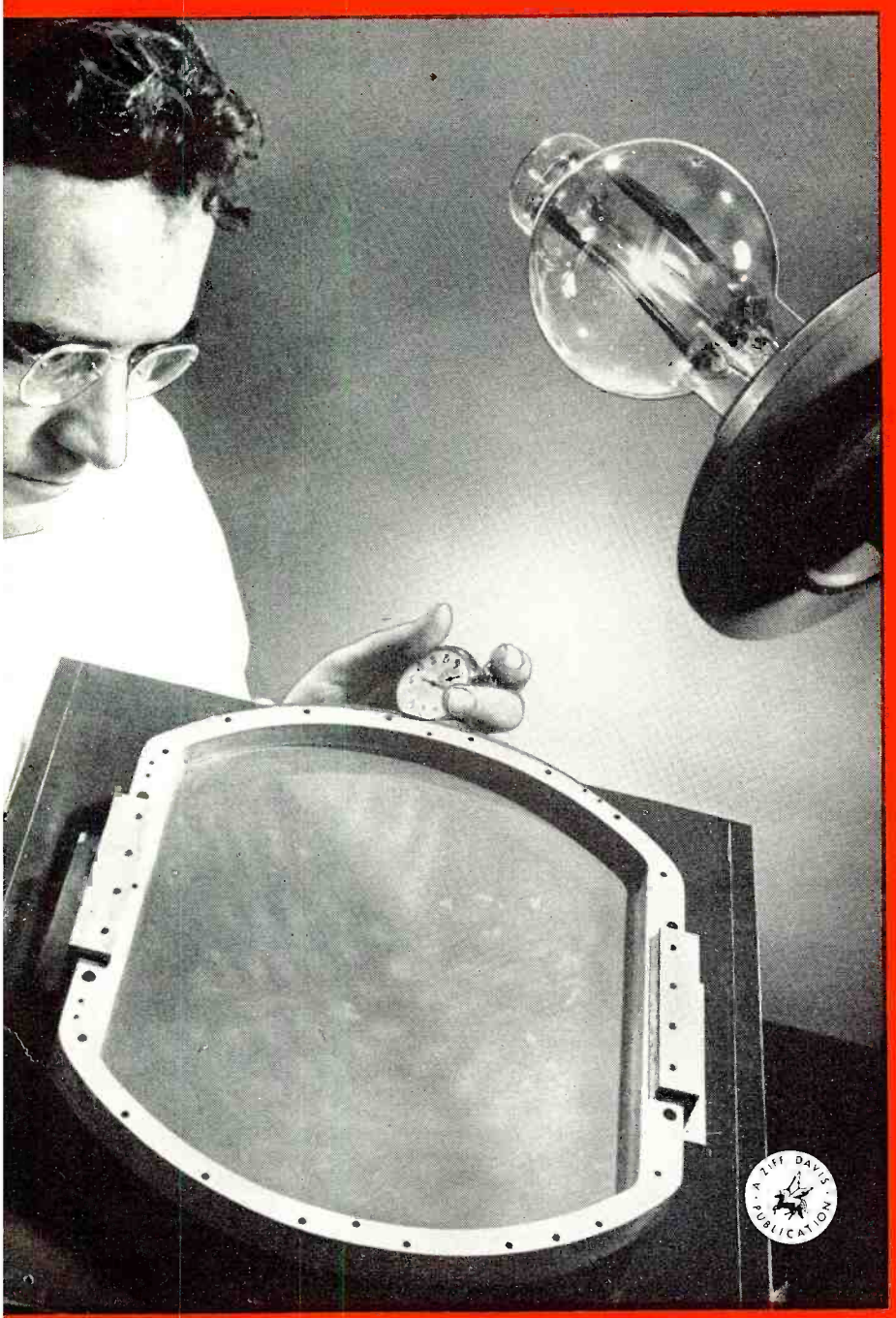

A BRIDGE TRANSISTOR TESTER
-5-

ESTABLISHING A POWER LINE CARRIER CHANNEL
-8-

CAST WAVE GUIDES
-10-

ERROR VOLTAGE DETECTOR
-12-

TRANSISTOR CONTROL OF MAGNETIC AMPLIFIERS
-13-

INTERNATIONAL TELECOMMUNICATIONS VIA V.H.F. RELAYS
-16-

DIODE-CAPACITOR MEMORY FOR COMPUTERS
-20-

HELICAL ANTENNA DESIGN
-40-

DEPARTMENTS

NEW TUBES ..... -22-
NEW PRODUCTS ..... -24-
NEW LITERATURE ..... -26-
NEWS BRIEFS ..... -28-
PERSONALS ..... -30-
TV-AM-FM PRODUCTION ..... -34-
TECHNICAL BOOKS ..... -37-
CALENDAR ..... -38-

Copyright, 1954, by Ziff-Davis Publishing Company

RADIO-ELECTRONIC ENGINEERING is published each month as a special section in a limited number of copies of RADIO & TELEVISION NEWS, by the Ziff-Davis Publishing Company, 366 Madison Avenue, New York 17, N. Y.

Edited by H. S. RENNE
and the Radio & Television News Staff


Color TV picture tube screen being formed by a photographic process at *Sylvania* Research Laboratories. An aperture plate containing more than 200,000 precisely spaced small holes is used in this process.

TELEVISION • ELECTRONICS • COMMUNICATIONS • AUDIO • MICROWAVES • RADAR • RESEARCH


www.americanradiohistory.com

FOR Higher Fidelity*

THE Linear Standard SERIES

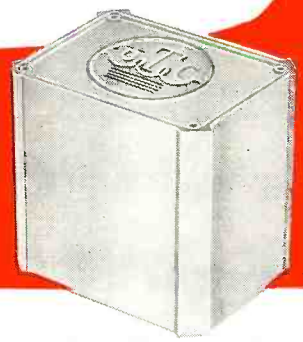

The ever increasing use of wide range equipment for broadcast service has reached the point where the major limiting factor is the frequency range of the transformers employed. UTC Linear Standard components represent the closest approach to the ideal transformer from the standpoint of uniform frequency response, low wave form distortion, high efficiency, thorough shielding, and dependability. Typical LS units are described below.

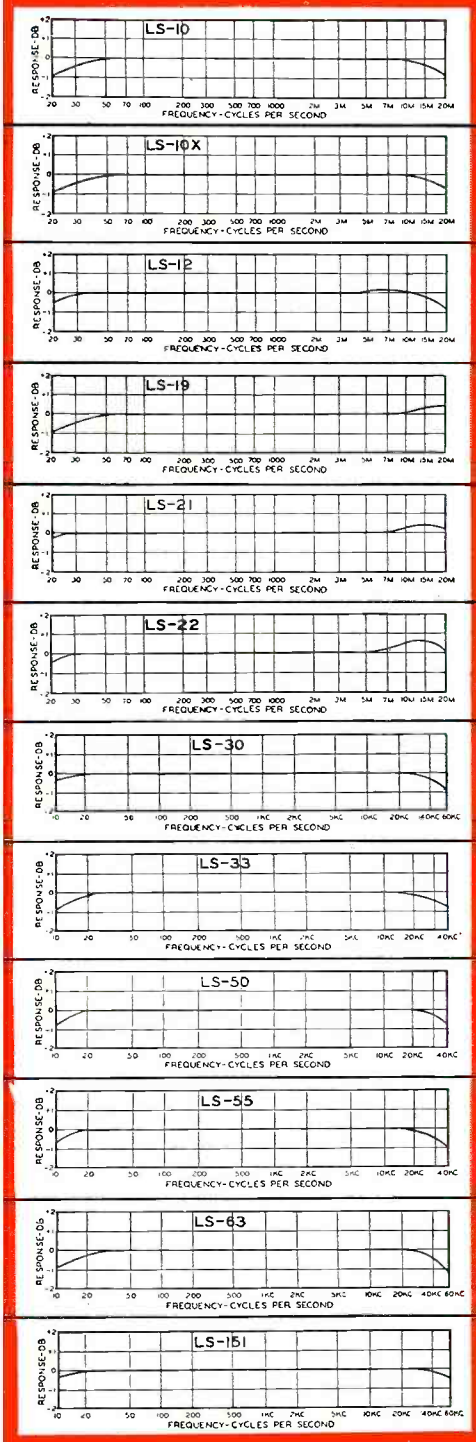

INPUT TRANSFORMERS

Case Size	LS-1	LS-2
Length	3⅛"	4 7/16"
Width	2⅝"	3½"
Height	3¼"	4 3/16"

Type No.	Application	Primary Impedance	Secondary Impedance	± 1 db from	Max.† Level	Relative* hum	Unbal. DC in prim'y	Case No.	List Price
LS-10	Low impedance mike, pickup, or multiple line to grid	50, 125/150, 200, 250, 333, 500/600 ohms	60,000 ohms in two sections	20-20,000	+10 DB	−74 DB	.5 MA	LS-1	$25.00
LS-10X	As above	As above	50,000 ohms	20-20,000	+10 DB	−92 DB-Q	.5 MA	LS-1	35.00
LS-12	Low impedance mike, pickup, or multiple line to push pull grids	50, 125/150, 200, 250, 333, 500/600 ohms	120,000 ohms overall, in two sections	20-20,000	+10 DB	−74 DB	.5 MA	LS-1	28.00
LS-12X	As above	As above	80,000 ohms overall, split	20-20,000	+10 DB	−92 DB-Q	.5 MA	LS-1	35.00
LS-15X	Three isolated lines or pads to one or two grids	30, 50, 200, 250 ohms each primary	60,000 ohms overall, in two sections	20-20,000	+10 DB	−92 DB-Q	.5 MA	LS-1	37.00

INTERSTAGE AND MATCHING TRANSFORMERS

Type No.	Application	Primary Impedance	Secondary Impedance	Response	Max.† Level	Relative* hum	Unbal. DC in prim'y	Case No.	List Price
LS-19	Single plate to push pull grids like 2A3, 6L6, 300A. Split secondary	15,000 ohms	95,000 ohms; 1.25:1 each side	± 1 db 20-20,000	+12 DB	−50 DB	0 MA	LS-1	$26.00
LS-21	Single plate to push pull grids. Split pri. and sec.	15,000 ohms	135,000 ohms; 3:1 overall	± 1 db 20-20,000	+10 DB	−74 DB	0 MA	LS-1	26.00
LS-25	Push pull plates to push pull grids. Medium level. Split primary and sec.	30,000 ohms plate to plate	50,000 ohms; turn ratio 1.3:1 overall	± 1 db 20-20,000	+15 DB	−74 DB	1 MA	LS-1	32.00
LS-30	Mixing, low impedance mike, pickup, or multiple line to multiple line	50, 125/150, 200, 250, 333, 500/600 ohms	50, 125/150, 200, 250, 333, 500/600 ohms	± 1 db 20-20,000	+15 DB	−74 DB	.5 MA	LS-1	26.00
LS-33	High level line matching	1.2, 2.5, 5, 7.5 10, 15, 20, 30, 50 125, 200, 250, 333, 500/600	50, 125, 200, 250, 333, 500/600 ohms	± .2 db 20-20,000	15 watts			LS-2	30.00

OUTPUT TRANSFORMERS

Type No.	Application	Primary Impedance	Secondary Impedance	Response	Max.† Level	Relative* hum	Unbal. DC in prim'y	Case No.	List Price
LS-50	Single plate to multiple line	15,000 ohms	50, 125/150, 200, 250, 333, 500/600	± 1 db 20-20,000	+15 DB	−74 DB	0 MA	LS-1	$26.00
LS-52	Push pull 245, 250, 6V6 or 245 A prime	8,000 ohms	500, 333, 250, 200, 125, 50, 30, 20, 15, 10, 7.5, 5, 2.5, 1.2	± .2 db 25-20,000	15 watts			LS-2	35.00
LS-55	Push pull 2A3's, 6A5G's, 300A's, 275A's, 6A3's, 6L6's, 6AS7G	5,000 ohms plate to plate and 3,000 ohms plate to plate	500, 333, 250, 200, 125, 50, 30, 20, 15, 10, 7.5, 5, 2.5, 1.2	± .2 db 25-20,000	20 watts			LS-2	35.00
LS-63	Push pull 6F6, class B 46's, 6AS7G, 807-TR, 1614-TR	10,000 ohms plate to plate and 6,000 ohms plate to plate	30, 20, 15, 10, 7.5, 5, 2.5, 1.2	± .2 db 25-20,000	15 watts			LS-2	25.00
LS-151	Bridging from 50 to 500 ohm line to line	16,000 ohms, bridging	50, 125/150, 200, 250, 333, 500/600	± 1 db 15-30,000	+18 DB	−74 DB	1 MA	LS-1	27.00

The values of unbalanced DC shown will effect approximately 1.5 DB loss at 30 cycles.
* Comparison of hum balanced unit with shielding to normal uncased type. Q Multiple alloy magnetic shield.
† 6 MW as ODB reference.

*UTC LINEAR STANDARD transformers are the ONLY audio units with a GUARANTEED uniform response... ± 1 DP from 20 to 20,000 cycles.

United Transformer Co.
150 VARICK STREET • NEW YORK 13, N. Y.
EXPORT DIVISION: 13 EAST 40th STREET, NEW YORK 16, N. Y. CABLES: "ARLAB"

www.americanradiohistory.com

Put your UHF signal where the population is

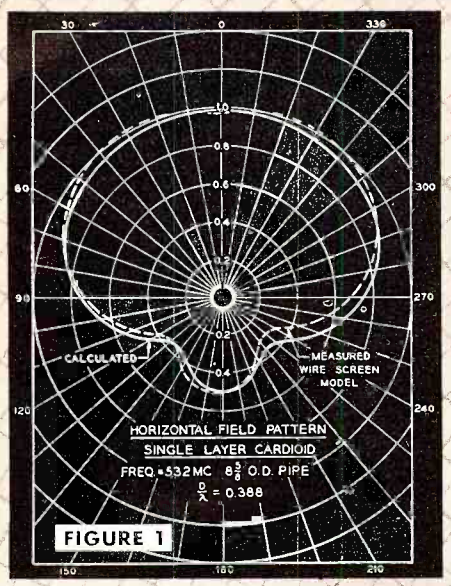


FIGURE 1

Use an RCA "contour-engineered" UHF Pylon Antenna

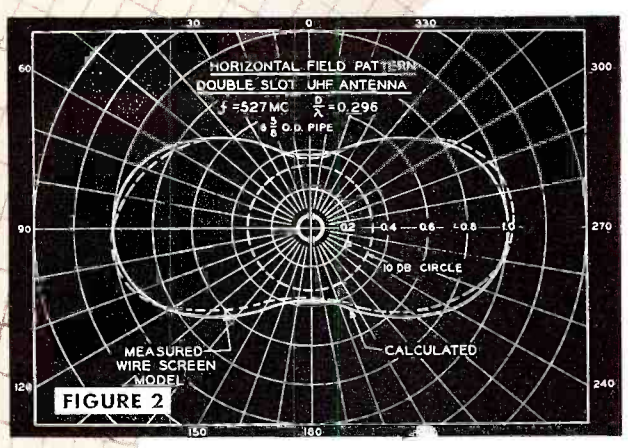


FIGURE 2

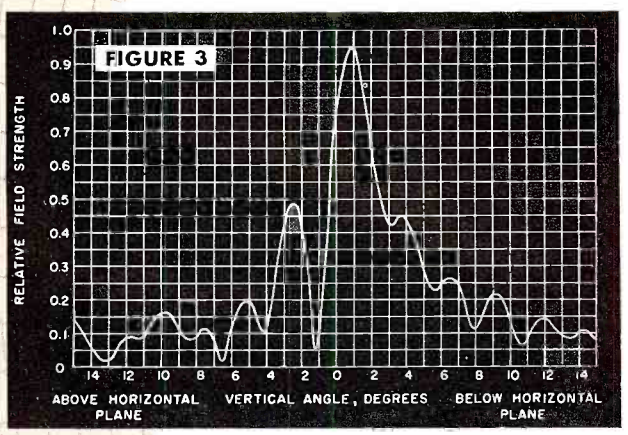


FIGURE 3

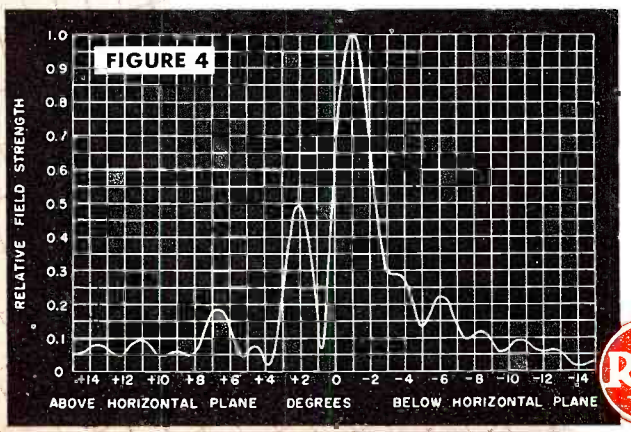
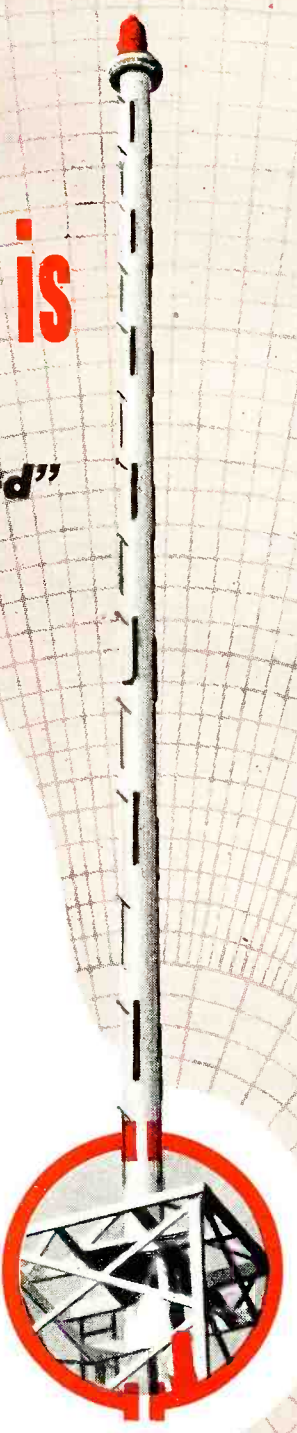


FIGURE 4

- **For "single-direction" coverage,** RCA has UHF Pylons that produce a horizontal field pattern shaped like a Cardioid (see Fig. 1).
- **For "elongated" coverage,** RCA has UHF Pylons that produce a horizontal field pattern shaped like a peanut (see Fig. 2).
- **For "circular" coverage,** RCA has a wide selection of UHF Pylons that produce equal signals in ALL directions.
- **For better overall coverage,** RCA UHF Pylons have built-in "Beam Tilt" that minimizes power loss in vertical radiation.
- **For better "close-in" coverage,** RCA UHF Pylons are equipped with a new, advanced type null fill-in system (used in conjunction with beam tilting). See Figs. 3 and 4.
- **The gain that's published is the gain you get.** RCA UHF Pylons include no tuning compromises that would result in loss of gain. RCA UHF Pylons can be furnished with gains in the order of 3, 6, 9, 12, 21, 24, and 27!
- **RCA has all UHF antenna accessories:** towers, mitered elbows, line transformers, spring hangers, dummy loads, wattmeters, frequency and modulator monitors, filterplexers, and transmission line (measured performance—VSWR—is better than 1.05 to 1.0). You can get everything from ONE responsible source—RCA!


RCA Adjustable Beam High-Gain UHF Pylon —installed

An antenna system can make or break a TV station. Make sure yours is right. Your RCA Broadcast Sales Representative can help you plan.

RADIO CORPORATION of AMERICA
ENGINEERING PRODUCTS DEPARTMENT CAMDEN, N.J.

www.americanradiohistory.com



Capacitors shown 2½ times actual size


CM-15 EL-MENCO CAPACITORS

are only 9/32"x1/2"x3/16"... but they give


DOUBLE VALUE PER DOLLAR

ALL fixed mica El-Menco capacitors are *factory-tested at double their working voltage.* Couldn't that mean that they'll last twice as long as other capacitors which cost no less? They also meet all significant requirements of JAN-C-5. So, you can depend on them to perform perfectly on all military and civilian electronic applications. Our tiny CM-15 silvered mica capacitors come in capacities from 2 to 420 mmf. at 500vDCw — 2 to 500 mmf. at 300vDCw. Our other types run all the way up to 10,000 mmf. It will pay you to compare El-Menco capacitors with all others — performance-wise, price-wise. *The Electro Motive Manufacturing Co., Inc., Willimantic, Conn.*

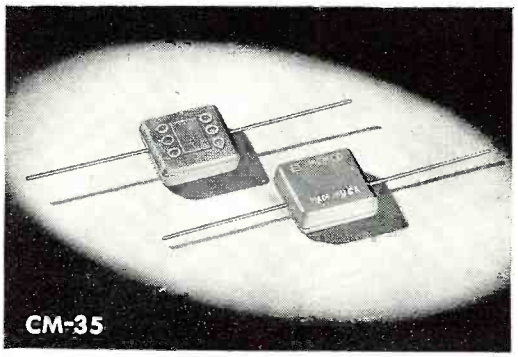Electro Motive is now supplying special silvered mica films for the electronic and communication industries in any quantity — just send us your specifications.



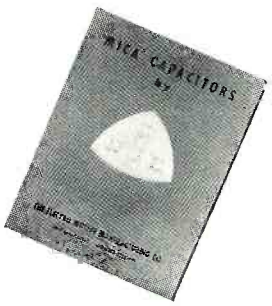WRITE FOR FREE SAMPLES AND CATALOG ON YOUR FIRM'S LETTERHEAD



Jobbers and distributors are requested to write for information to Arco Electronics, Inc., 103 Lafayette St., New York, N. Y. — large stocks on hand — spot shipments for immediate delivery. Sole Agent for Jobbers and Distributors in U. S. and Canada.

El-Menco CAPACITORS

MOLDED MICA **MICA TRIMMER**

Foreign and Electronic Manufacturers Get Information Direct from our Export Dept. at Willimantic, Conn.

THE ELECTRO MOTIVE MFG. CO., INC. **WILLIMANTIC, CONNECTICUT**


www.americanradiohistory.com

A BRIDGE TRANSISTOR TESTER

By **DAVID DORMAN**

Research Laboratories
Sylvania Electric Products Inc.

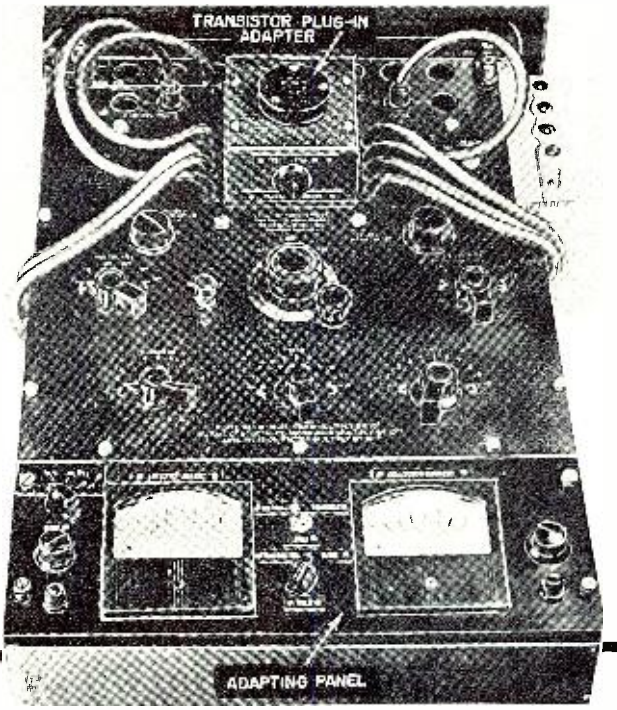Commercial vacuum tube bridge may be adapted to measure point-contact transistor parameters.



The *General Radio* vacuum tube bridge Type 561-D adapted for transistor measurements.

MANY TESTING procedures previously described in the literature utilize the short-circuit mode of operation to provide transistor characteristics in terms of conductances. These short-circuit conditions are well suited for the measurement of junction transistors; however, the same conditions result in very unstable point-contact transistor operation. An important advantage of the measurement technique described herein is that the open-circuit mode of operation which is most favorable for point-contact transistor measurement is utilized.

The *General Radio* Type 561-D vacuum tube bridge is well known as a measuring device for vacuum tubes. A study of this bridge has revealed that it is readily adaptable for accurate and simple measurement of point-contact transistor parameters R_{11}, R_{22}, R_{12}, R_{21}, and α. If the transistor is considered as an active four-terminal network, as shown in Fig. 1, these small a.c. signal parameters may be defined as follows:

R_{11}= input resistance with the output open-circuited (i_c=0)

R_{22}= output resistance with the input open-circuited (i_e=0)

R_{12}= feedback resistance with the input open-circuited (i_e=0)

R_{21}= forward resistance with the output open-circuited (i_c=0)

α = current gain with the output short-circuited (v_c=0)

Over a small region of the static characteristics, the linear relations between the incremental emitter and collector voltages and currents can be described by the linear equations:

$$v_e = R_{11}i_e + R_{12}i_c \quad . \quad . \quad . \quad . \quad . \quad (1)$$

$$v_c = R_{21}i_e + R_{22}i_c \quad . \quad . \quad . \quad . \quad . \quad (2)$$

and the slopes of the appropriate set of characteristic curves are expressed by:

$$R_{11} = \left.\frac{\delta v_e}{\delta i_e}\right|_{i_c = 0} \quad . \quad . \quad . \quad . \quad . \quad (3)$$

$$R_{22} = \left.\frac{\delta v_c}{\delta i_c}\right|_{i_e = 0} \quad . \quad . \quad . \quad . \quad . \quad (4)$$

$$R_{12} = \left.\frac{\delta v_e}{\delta i_c}\right|_{i_e = 0} \quad . \quad . \quad . \quad . \quad . \quad (5)$$


$$R_{21} = \left.\frac{\delta v_c}{\delta i_e}\right|_{i_c = 0} \quad . \quad . \quad . \quad . \quad . \quad (6)$$

The expression for α is:

$$\alpha = \left.\frac{\delta i_c}{\delta i_e}\right|_{v_c = 0} \quad . \quad . \quad . \quad . \quad . \quad (7)$$

Resistance parameters or coefficients, Eqts. (3)-(6), and α, Eqt. (7), may be closely correlated with the dynamic coefficients of vacuum tubes, R_p, G_m, and μ. The *General Radio* bridge measures these tube coefficients by means of null-balance arrangements of the various alternating increments [1,2]. It is possible to adapt these bridge null-balance arrangements to permit accurate and direct measurements of the point-contact transistor coefficients.

Fig. 1. Equivalent circuit of transistor shown as an active four-terminal network.

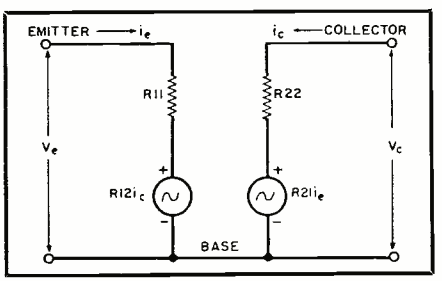

It is not intended at this time to describe the theory of operation of the bridge, which already has been very adequately done[2], but rather to present the circuitry in order to illustrate fully the direct measurement correlations between tubes and transistors which may be advantageously exploited.

Bridge modifications and all but one switch (the transistor switch which enables one to use the bridge for transistor measurements) are housed in a panel mount measuring approximately 15½" x 5½" x 5". Two power supplies wired into the bridge setup supply the emitter and collector bias requirements. The transistor is inserted into the bridge by means of a plug-in type octal adapter, and the transistor switch—which applies or removes the desired bridge terminals to the emitter, collector, and base—is mounted on the plug-in octal adapter.

The close analogy which exists between the dynamic coefficients of the vacuum tube and the transistor may be more easily observed by a study of the definitions of both groups of coefficients. Transistor coefficients are defined in Eqts. (3)-(7), and those for vacuum tubes in Eqts. (8)-(10).

$$R_p = \left.\frac{\delta v_p}{\delta i_p}\right|_{v_g = 0} \quad . \quad . \quad . \quad . \quad . \quad (8)$$

$$G_m = \left.\frac{\delta i_p}{\delta v_g}\right|_{v_p = 0} \quad . \quad . \quad . \quad . \quad . \quad (9)$$

$$\mu = \left.\frac{\delta v_p}{\delta v_g}\right|_{i_p = 0} \quad . \quad . \quad . \quad . \quad . \quad (10)$$

Upon examining Eqt. (8), the expression for R_p, it becomes apparent

www.americanradiohistory.com

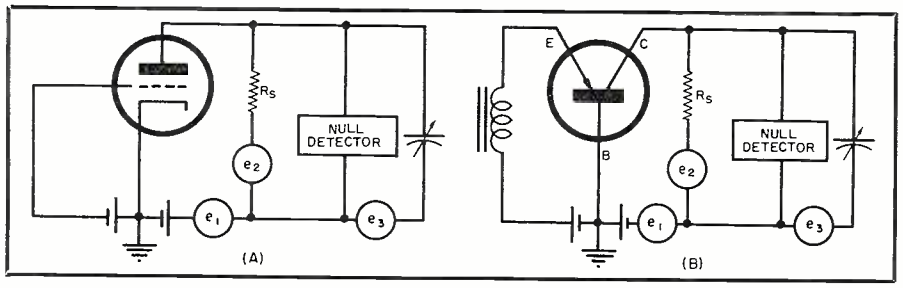


Fig. 2. (A) Simplified bridge circuit for measuring R_p. (B) Modified R_p bridge circuit designed to measure R_{22} of point-contact transistors.

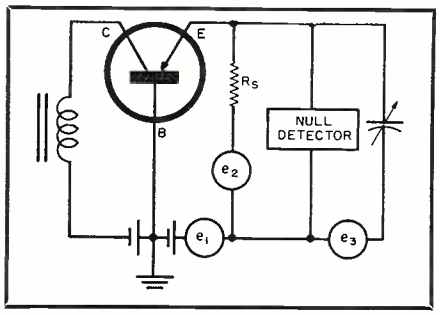


Fig. 3. Modified R_p bridge circuit designed to measure R_{11}.

that the increments of alternating voltage and current involved correspond to those for R_{22} of the transistor, i.e., v_c and i_t correspond to v_p and i_p, respectively, while the condition $i_e = 0$ may be considered the dual[3] of $v_g = 0$. It is very simple to satisfy the condition $i_e = 0$ with the insertion of a 600-henry audio choke in the emitter circuit; this essentially opens the circuit to the bridge test signal of 1000 cps. The simplified bridge circuit for measuring R_p and the associated circuit for measuring R_{22} are shown in Figs. 2A and 2B.

In the circuit for measuring R_p, as illustrated in Fig. 2A, it is desired to measure the alternating plate current flowing as a result of a small voltage change introduced into the plate circuit under the condition that there be no alternating voltage on the grid. The small voltage change introduced into the plate circuit is represented by the test voltage e_1. Test voltage e_2 is adjusted so that the resultant current flowing through R_s balances the plate current. When the two currents are equal, there is no voltage across the null detector. Since the sharpness of the null may be obscured by reactive current which arises from the interelectrode capacitances of the tube being tested, lead capacitances, etc., a reactive current generator, e_3, (capacitance balancing winding in series with a variable capacitance) is introduced—as shown—and may be adjusted to pass an equal and opposite reactive current.

Increments of R_{11} likewise are analogous to those of R_p. Since R_{11} is defined as the transistor input resistance, the bridge R_p measuring circuit must therefore be placed in the emitter circuit, as shown in Fig. 3. This is done simply by reversing the transistor emitter and collector leads. It is necessary to maintain the proper d.c. biasing when reversing the transistor, and this is insured in the switching procedure.

The test setup for measuring R_{11} provides an a.c. open collector circuit, and the bridge R_p circuit measures the alternating emitter current flowing as a result of a small voltage change introduced into the emitter circuit by e_1. The collector circuit is effectively open-circuited to a.c. by the audio choke. Test voltage e_2 is adjusted so that the resultant current flowing through R_s balances the emitter current. When the two currents are equal, a null will be exhibited by the detector and the bridge decade resistor balance will yield the value of R_{11}.

When measuring the transconductance of a tube with the bridge, it is necessary to determine the alternating plate current flowing as a result of a small signal voltage introduced into the grid circuit under the condition that there be no alternating voltage on the plate. A nearly parallel situation exists in the measurement of α. α has been defined to be a measure of the alternating collector current flowing as a result of small changes in emitter current under the condition that there be no alternating voltage on the collector. Figure 4A shows the bridge circuit for measuring G_m, and Fig. 4B shows the modified G_m circuit designed to measure α. The G_m position measures:

$$\left.\frac{\delta i_c}{\delta v_e}\right|_{v_c = 0} \quad \ldots\ldots\ldots \quad (11)$$

To measure α, a 100,000-ohm resistance—designated as R_E in Fig. 4B—is inserted in the emitter circuit. Since typical values of R_{11} are of the order of 500 ohms, the effective resistance of the emitter circuit is R_E. The partial derivative of v_e may then be replaced by $\delta i_e R_E$, and the quantity measured by the bridge becomes:

$$\left.\frac{1}{R_E}\,\frac{\delta i_c}{\delta i_e}\right|_{v_c = 0} = \frac{1}{R_E}\alpha. \quad \ldots \quad (12)$$

The bridge reading is in micromhos:

$$\therefore \text{Alpha } (\alpha) = 0.1\text{X bridge reading} \quad (13)$$

Figures 4A & B show that necessary conditions are satisfied by placing the null detector directly between the collector and base, so that at null balance $v_c = 0$. It is very important in measuring α to throw the sign of coefficient switch to negative. Since signals transmitted through the vacuum tube undergo a phase reversal, while on the other hand signals are transmitted through the transistor without phase changes, reversing the sign of coefficient switch is necessary to supply accurate in-phase test voltages to the transistor under test.

The next tube coefficient to be considered is μ. The μ position of the bridge measures:


$$\left.\frac{\delta v_p}{\delta v_g}\right|_{i_p = 0} \quad \ldots\ldots\ldots \quad (14)$$

Here again, with some very simple adaptations, the exact requirements for measuring R_{21} are met. Figures 5A and 5B show the bridge circuit for measuring μ and the modified μ circuit designed to measure R_{21}.

To measure R_{21}, R_E (the 100,000-ohm resistor) is once more inserted into the emitter circuit, thus making the effective resistance of the emitter circuit equal to R_E. The partial derivative of v_e may then be replaced by $\delta i_e R_E$, and the quantity measured by the bridge becomes:

$$\left.\frac{1}{R_E}\,\frac{\delta v_c}{\delta i_e}\right|_{i_c = 0} = \frac{1}{R_E}R_{21} \quad \ldots \quad (15)$$

Fig. 4. (A) Simplified bridge circuit for measuring G_m. (B) Modified G_m bridge circuit designed to measure α of point-contact transistors.

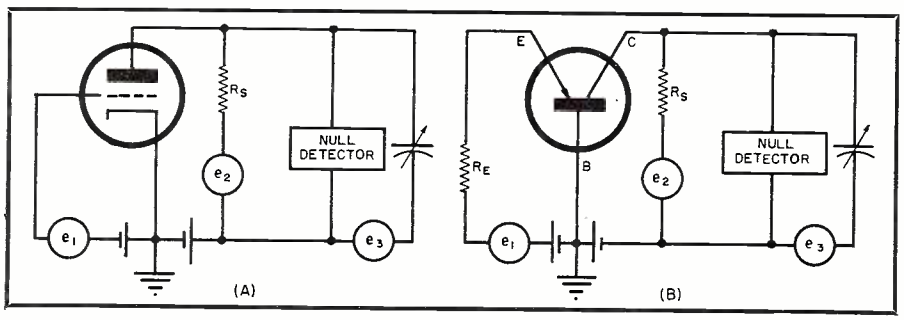

www.americanradiohistory.com

$\therefore R_{21} = \mu$ reading $\times 10^5$ ohms. . (16)

To measure R_{21}, it is necessary to throw the sign of coefficient switch to negative —as before—to supply accurate in-phase test voltages to the transistor under test. On examining Fig. 5B, it will be clear that the necessary conditions for measuring R_{21} are satisfied. At the point of null balance indicated by the null detector, $i_e=0$.

Alternating increments of R_{12} likewise correspond to those of μ with the exception that the transistor input circuit is to be measured. This problem is again overcome simply by reversing the transistor emitter and collector leads so that the bridge measuring circuit is placed in the emitter circuit. The test setup for R_{12} now provides an a.c. open circuit in the emitter when a null balance is obtained. Figure 6 shows the modified μ measuring circuit designed to measure R_{12}. The quantity measured by the bridge is:

$$\left.\frac{\delta v_c}{\delta v_e}\right|_{i_e = 0} \quad . \quad . \quad . \quad . \quad . \quad . \quad (17)$$

Since $\delta v_e = \delta i_e R_{22}$, this quantity becomes:

$$\left.\frac{\delta v_c}{\delta i_e R_{22}}\right|_{i_e = 0} = \frac{1}{R_{22}}(R_{12}) \quad . \quad . \quad . \quad (18)$$

$$\therefore R_{12} = \mu \text{ reading} \times R_{22} \text{ ohms} \quad . \quad (19)$$

The value of R_{22} previously measured by the bridge (Fig. 2B) is used with this measurement of μ to calculate R_{12}.

An external resistance of a value much larger than R_{22} was not used for this test, as the value of R_{22}—being of the order of 20,000 ohms—would require the use of an external resistance of the order of 2,000,000 ohms. Essentially constant-current bias is supplied to both the emitter and the collector of the transistor under test. A simple and convenient means of providing this bias has been through the use of two high-voltage power supplies with a large series resistance introduced in both the emitter and collector leads. Placing a 2,000,000-ohm resistance into the collector circuit would then require a power supply capable of providing more than 1000 volts, which is impractical.

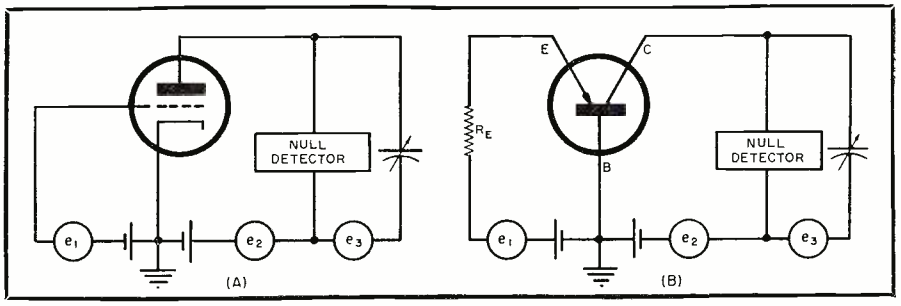


Fig. 5. (A) Simplified bridge circuit for measuring μ. (B) Modified μ bridge circuit designed to measure R_{21} of point-contact transistors.

In the test procedure outlined in Table 1, a bridge oscillator output of approximately 1000 cps at 25 volts results in a test signal level of 3.4 volts. This signal level appears in the test circuitry when the "multiply by" switch is set to 1. With the aid of an oscilloscope null detector, it is possible to observe whether or not the test signal overloads the transistor under test. Setting the "multiply by" switch to the position marked 10 results in a decrease of the test signal level by a factor of 10 to 0.34 v. The next larger "multiply by" switch positions result in proportionately lower test signal levels. Therefore, with the aid of the scope detector, an appropriate test signal can be chosen. Table 1 lists the "multiply by" switch positions found suitable for performing the various required tests on those transistors measured to date.

One of the difficulties sometimes encountered in the measurement of point-contact transistors by the bridge balance method is that balance may be obscured by transistor noise. The transistors that have been measured so far exhibited low enough noise levels so that bridge balances to three significant figures were possible. If other transistors exhibit higher noise levels, it should be fairly simple to minimize the effects of noise by increasing the input test signal (at the same time making sure that the increased signal level does not produce distortion). The possibility of signal analysis is one of the most important advantages of utilizing an oscilloscope for purposes of null detection.

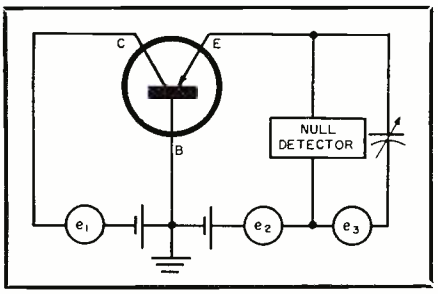


Fig. 6. Modified μ bridge circuit designed to measure R_{12}.

Another difficulty which may arise in measuring point-contact transistors is that oscillations may occur with short-circuit terminations of the transistor. This method of termination, although somewhat undesirable for point-contact transistor parameter measurements, is known to be used in other testing techniques which measure the conductance rather than resistance parameters[1]. Thus, a second important advantage of the modified bridge method can be pointed out, i.e., open-circuit a.c. terminations for all tests except that for α—which utilizes a 100,000-ohm resistor in the emitter circuit—make it very unlikely that a transistor will break into oscillations.

(Continued on page -34-)

Table 1. Procedure for measuring various transistor parameters by means of the modified vacuum tube bridge.

BRIDGE ADJUSTMENTS						ADAPTING PANEL ADJUSTMENTS				
Parameter to be Measured	Coefficient Selector Switch & Sign	"Multiply by" Switch	"Divide by" Switch	Decade Resistor Balance	Capacitor Multiplier Switch	Transistor Switch	Switch #1	Switch #2	Switch #3	Bridge Measurements
R_{11}	R_p (+)	1	10^2	adjust for balance	out	test	reverse	transistor	R_{11}	R_p
R_{22}	R_p (+)	1	10	"	"	"	normal	"	R_{22}	R_p
R_{12}	μ (−)	10	10	"	"	"	reverse	"	R_{12}	$\mu \times R_{22}$
R_{21}	μ (−)	1	10	"	"	"	normal	"	R_{21}	$\mu \times 10^5$
α	G_m (−)	10	1	"	"	"	normal	"	α	$G_m/10$

www.americanradiohistory.com

ESTABLISHING A POWER

By
NICHOLAS ALCHUK

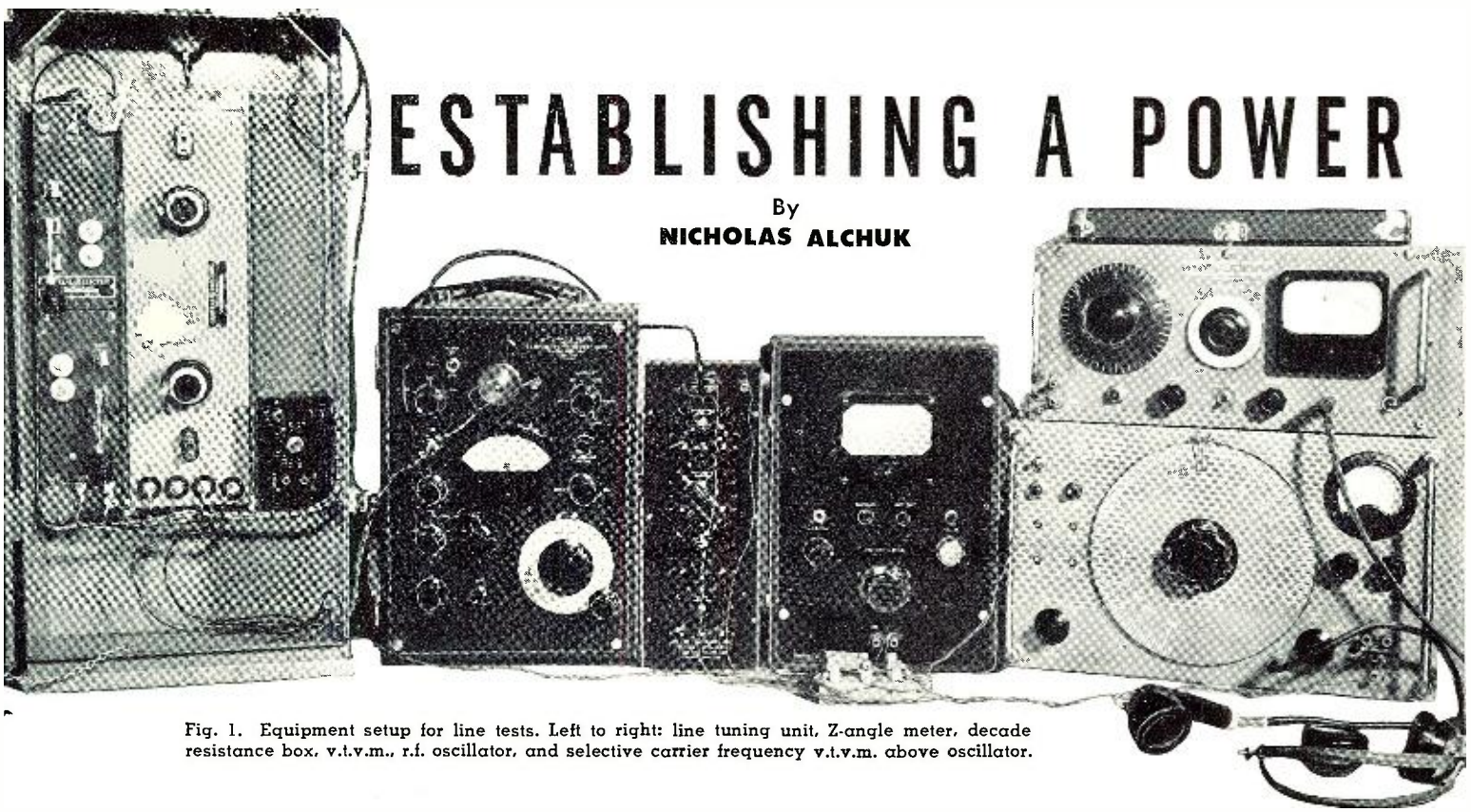



Fig. 1. Equipment setup for line tests. Left to right: line tuning unit, Z-angle meter, decade resistance box, v.t.v.m., r.f. oscillator, and selective carrier frequency v.t.v.m. above oscillator.

GENERATION and distribution of power require the use of much auxiliary equipment. In the past decade, the power industry has relied heavily upon power line carrier facilities. Their value for telemetering, load control, and other functions has been established.

Problems confronting a power line carrier engineer differ greatly from those met by the communication engineer. The power line carrier channel must be fitted into the existing transmission line network. In many instances, special devices must be used and measures taken to insure consistent operation of the equipment. Determination of the behavior of r.f. signals on transmission lines is more difficult than predicting their performance in free space.

The method of coupling an r.f. carrier to the transmission line depends greatly on line configuration. Attenuation, impedance, carrier frequency, and single- or double-circuit tower construction all have an effect on the transmission. Phase-to-ground and phase-to-phase coupling (shown schematically in Fig. 2) are the two methods most widely used.

Fig. 2. Methods of coupling r.f. carrier to transmission line: (A) phase-to-ground, and (B) phase-to-phase.

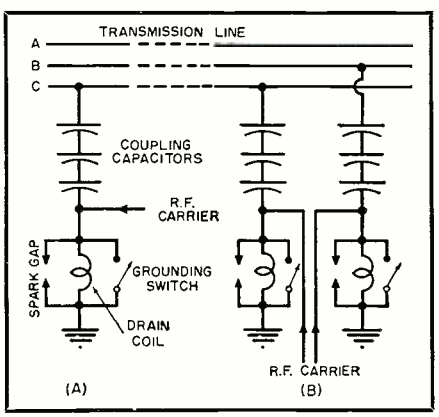

Coupling Capacitors

The vital link in injecting the carrier onto the transmission line is the coupling capacitor. It is usually made up of individual series-connected oil-impregnated paper capacitors, installed in a porcelain housing, and may be used on lines up to 230 kv. A typical 115-kv. assembly is shown in Fig. 4.

When determining the over-all attenuation of a carrier channel, it is essential to know the impedance of the capacitor. Not only is the information important from a transmission consideration, but it is a check on the capacitor itself. Once the capacitor has been mounted and connected to a line, it is not economically feasible to take the line out of service and perform measurements.

Measurements are made with and without protective equipment connected to the capacitor. In addition, the high side of the capacitor is grounded in order to place the low side at a high r.f. potential, thus simulating its actual operating condition. Generally, an unknown impedance can be measured by means of a *Q* meter or an r.f. bridge. The *Q*-meter method is more versatile, since certain liberties can be taken in the measurements owing to the low frequencies used (50 to 200 kilocycles).


Wave Traps

To confine the carrier to a transmission line and reduce losses into the steel network or tap lines, wave traps are employed at both ends of a carrier channel. The traps are parallel-tuned devices, of either single or double frequency, wound with heavy bar or stranded wire. Since they are connected in series with a phase wire, they must carry the line currents which range from 100 to 400 amperes. The traps are rated at 800 amperes for 230 kv., and 400 amperes for 115 kv. Figure 6 shows a 230-kv. installation.

Successful operation of a carrier channel depends upon the received signal level. Equipment losses may be readily calculated; however, an untrapped transmission line contains so many variables that a usable figure of attenuation is difficult to compute. Wave traps, inserted at known high attenuation points, insure that the attenuation is kept to a minimum.

The impedance of wave traps is important. The higher the impedance, the more of the carrier signal is confined to the transmission line. Single frequency traps have impedances of ap-

Fig. 3. Typical circuit for measuring the impedance of a wave trap.

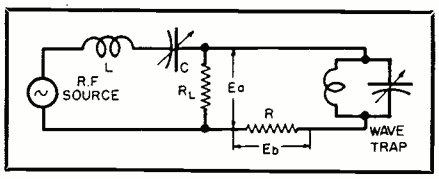

www.americanradiohistory.com

LINE CARRIER CHANNEL

Factors to be considered include coupling methods, power line characteristics, and impedances of traps and coupling capacitors.

proximately 10,000 ohms at the operating frequency. This value drops to about 3000 and 5000 ohms, respectively, for the low and high frequencies of double-frequency traps. Several methods are available for measuring impedance; and when the frequency, inductance, and Q are known, the method shown in Fig. 3 is normally used. The equation for determining the impedance Z in Fig. 3:

$$Z = \frac{E_a}{E_b} R$$

is accurate for normal operating conditions. The voltages E_a and E_b are measured by a v.t.v.m. This arrangement gives the total impedance but does not evaluate the resistive and reactive components.

Line Tuning Unit

For maximum transfer of power, the r.f. source must look into an essentially resistive component. Using the capacitor alone as a coupling source, the load is capacitive. The function of the line tuning unit is to resonate the capacitor at the frequency of operation. This unit consists of series inductance variable within the 50 to 200 kc. range. In addition, a coupling transformer is utilized to match the tuning unit to a coaxial cable. Single- and double-frequency units are manufactured, as well as phase-to-phase and phase-to-ground couplers. The tuning unit as a whole has a broadband characteristic, with an insertion loss of approximately 2 db. Figure 5 shows a double-frequency line tuning unit which may be operated either single or double frequency phase-to-phase, or single frequency phase-to-ground. The tuning unit is normally mounted at the base of the coupling capacitor, and a coaxial cable connects it to the carrier equipment.

In the early years of power line carrier installation, it was common practice to mount the terminal equipment near the coupling capacitor and line tuning unit. Connection to the line tuning unit was made by a high impedance insulated cable. This condition resulted in the lead and the terminal equipment operating at the line impedance. If the lead were not aerially supported, shunt conductance losses to ground became excessive in lead lengths of 100 feet or more. Development of coaxial cable made it possible to locate equipment 1000 feet or so away from the coupling units because of the reduced losses in such cable.

Line Tests

Although not often necessary, line tests are desirable to determine the impedance of the transmission line. In addition, the attenuation and optimum operating frequency can be determined. It is possible to calculate the performance of a transmission line; however, the many factors involved—such as transposition schemes, spacing of conductors, size of conductors, and type of insulators—make for a tedious and sometimes laborious task. The calculated values on many occasions are too high and contribute additional errors in the over-all transmission scheme. Line test results are useful for obtaining figures of the following items: (1) frequency coordination, (2) impedance and attenuation, (3) carrier frequency noise.

Frequency Coordination

Power line carrier frequencies have been allocated in the 50 to 200 kc. frequency band. Since many utilities operate in a loop system, with all generating plants feeding power into a hypothetical loop, care must be exercised in the choice of frequency for

(*Continued on page* –36–)



Fig. 4. A 115-kilovolt 0.002-microfarad coupling capacitor unit for power line applications.

Fig. 5. Typical line tuning unit used to resonate a coupling capacitor such as the one in Fig. 4.


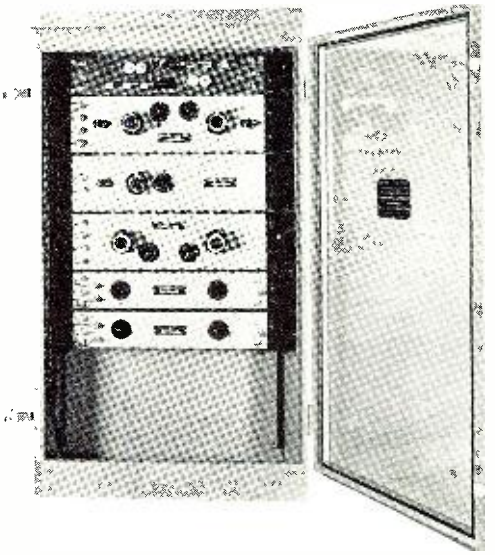


Fig. 6. A 230-kilovolt phase-to-phase coupling arrangement using principles outlined in Fig. 2B.

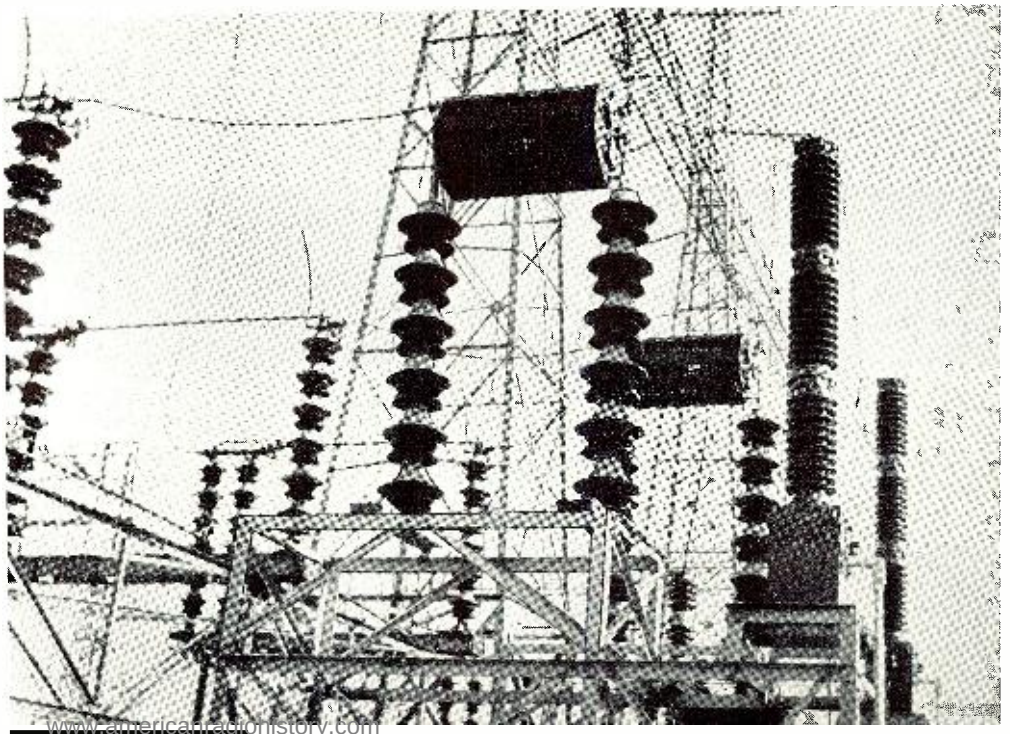

www.americanradiohistory.com

CAST

By

SAMUEL FREEDMAN

Sightmaster of California Company



Fig. 1. Forming the metal pattern for a 3000-9000 mc. cast wave guide adapter, complete with flanges.

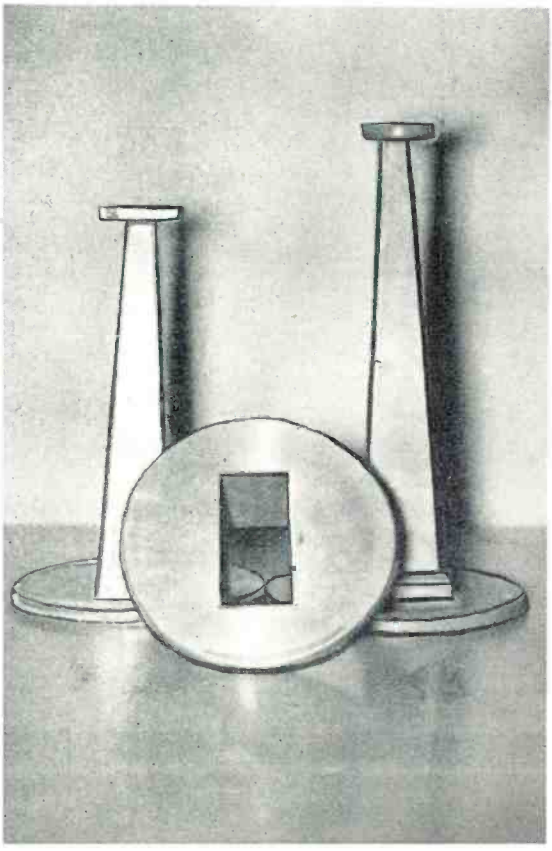


Fig. 2. Finished wave guide adapters made by the Sightmastermold process: a 3000-9000 mc. transition (left), and a 3000-30,000 mc. transition (right).

BONDING fine sands with synthetic resins makes it possible to precision-mold wave guides complete with flanges to any dimension or configuration in a single casting operation. This is accomplished by the "Sightmaster-mold" process which has been developed by *Sightmaster of California Company*, of Santee, California. Use of this process, which incorporates a shell molding technique, improves the performance and very substantially reduces the cost of microwave wave guides, particularly with new designs and components made of aluminum.

Shell-molded wave guides may be of a quality and composition difficult to achieve by other known wave guide fabricating methods such as extruding, brazing, investment casting or electroforming. In the case of aluminum, it is difficult to extrude the stronger alloys to JAN dimensional tolerances and to braze them without heat deformation. Also, it is impossible to electroform aluminum and some other metals as plated depositions on "lost materials" which are subsequently removed. The Sightmastermold process facilitates the use of aluminum with its general advantages of light weight, low cost, plentiful domestic supply and attractive appearance, and is suitable for use with all known metals having melting points from as low as 500° F or less up to over 2000°F.

A problem that has always existed in producing wave guides has been the lack of satisfactory flanging or joining techniques. Flanges have usually been secured from sources other than those which furnish the extruded wave guide tubing, thereby necessitating the soldering, brazing or welding of such flanges and the use of corrosive fluxes at every flange or junction. Every time flanges are brazed to wave guide tubing (normally extruded pipe), particularly in the case of aluminum, the heat causes deformation of the metal which results in misalignment and rejection of material or parts. In order for any flange to fit into brazing position on a wave guide, there must be some dimensional clearances—which result in misalignment and reduction in efficiency.

No wave guide performance can be better than its flanges and flange clearance/alignment permit. In some cases, wave guides must be held to a dimensional tolerance of two-thousandths of an inch and should have a smooth surface of less than 25 microinches. Misalignment, nonuniformity of dimension and discontinuity cause a mismatch which is manifested in the form of an increased voltage standing wave ratio. A mismatch causing a VSWR of 1.22 was reported to be sufficient to make a leading military radar inoperative because the magnetron tube would break down and arcing could be detected.

VSWR must be kept as low as possible in pulsed systems where peak powers are of a magnitude so much in excess of average power that adequate component safety factors are difficult and costly to provide. In aircraft or airborne pulsed radar equipment, high safety factors would result in excessive weight and space needs. In high powered megawatt ground radar installations, high safety factors would involve components larger than are normally available as standard. The best way of obtaining minimum

www.americanradiohistory.com

WAVE GUIDES

Wave guides and adapters can be cast complete with flanges by the Sightmastermold process.

VSWR's is to eliminate completely any soldering, brazing or welding in wave guide fabrication and flanging.

A common sight in wave guide plants is the "Lady with the File," or her male counterpart, whose sole task is to file down wave guide and flange extremities so that parts will pass electrical test inspection. Sometimes, the deformation or discontinuity is too great to be overcome by this elementary method, and the part has to be scrapped. At other times, in desperation or because of lack of proper components, two defective or high VSWR parts have been known to be joined together in reverse in an attempt to balance out the defects. In extreme cases, rather than start all over again, there have been situations where "dent tuning" has been resorted to in order to secure satisfactory operation.

In fabricating tapered wave guide adapters, it is very difficult to overcome electrical discontinuities and mismatch. For a transition from one size to another, 14 distinct brazed surfaces must be joined, counting the four-sided rectangular flange as one operation. Such wave guide adapters have many uses in the microwave art.

When *Sightmaster of California Company* expanded its microwave calorimeter program after the Korean outbreak, the need for more and better adapters increased. As a result of the poor availability of adapters as well as the high number of physical/electrical discontinuities present in conventional adapters of heavy brass, a program of research and development was started. The approach was from the standpoints of better availability, lower cost, lighter weight and improved performance. It became desirable to abandon old methods and concepts of making wave guides. After considerable research and investigation, a decision was made to cast wave guides, not using ordinary casting techniques, but by means of a modified and improved version of a shell molding process originally invented in Germany during World War II and delayed in adoption pending the availability of more suitable resins. Since wave guides are normally hollow, thin-walled and sharp-cornered instead of solid or thick-walled, the word "Sightmastermold" is used to differentiate from "shell mold."

A metal pattern is used as the starting point in this process. Illustrated in Fig. 3 is a simple pattern for a straight wave guide section. Figure 1 shows a pattern maker forming the first half of the metal pattern complete with flanges for a wave guide adapter; it is held to close dimensions with proper allowance for metal shrinkage and time cycle dimensional changes during the production process to take care of metals such as aluminum that can shrink 3/16" per foot in every plane. Another type of pattern is a core box (Fig. 4) which makes the core and decides the wall thickness as well as the internal surface smoothness of a wave guide.

When heated and immersed in a special sand-resin mix, the heat from the metal pattern penetrates the mix, thereby causing the resin to become plastic and bond the sand to form an accurate impression or mold of the pattern configuration. The pattern is formed in two halves, with alignment provisions, to make up a complete shell mold ready to go into position for pouring. When the metal has solidified after pouring, the shells are destroyed in order to remove the finished pieces. Being made of plentiful and inexpensive sands and resins, an unlimited number of shells can be formed rapidly from a single metal pattern and they are therefore expendable. The concept is to save the metal casting and destroy the shell mold. The casting is worth dollars while the shell mold is worth only pennies in relative terms of value and cost.

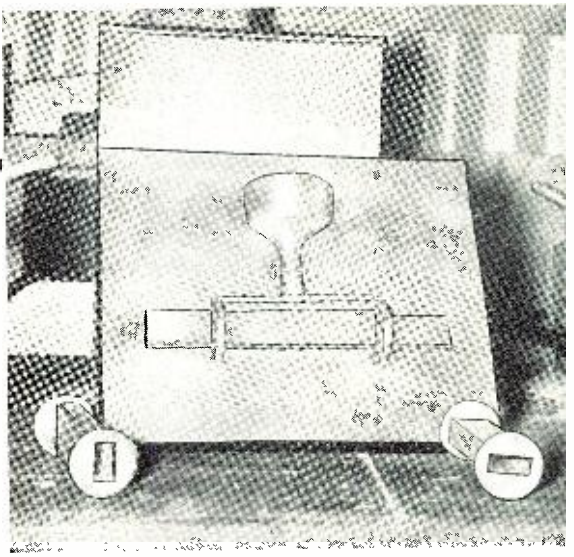



Fig. 3. Metal pattern used to fabricate the *X*-band (9375-mc.) wave guides shown on the table.

Figure 2 shows finished wave guide adapters made by the Sightmastermold process, complete including flanges. They are surface-smoothened and drilled as required. VSWR's in tapered wave guide adapters made by this process are very low. In a typical example, a tapered adapter was used to join a small wave guide to a larger wave guide containing a water load, and the VSWR for the whole combination was only 1.03.

One metal pattern can be used to make thousands of shells. Each pair of shells comprises a mold. Each mold makes a complete wave guide part, including flanges or appendages. The pattern can be stowed away and brought out whenever needed. Although the mold is made in two parts, thereby creating a visible seam when the component is first removed from the mold, this seam is external only. No internal seam or discontinuity is present since metal flows around an internal core properly spaced to yield required wall thickness. The external seam can be completely eradicated by surface buffing of the part, as can the pouring path or gating

(*Continued on page* –31–)


Fig. 4. Sand-resin core form being removed from core box.

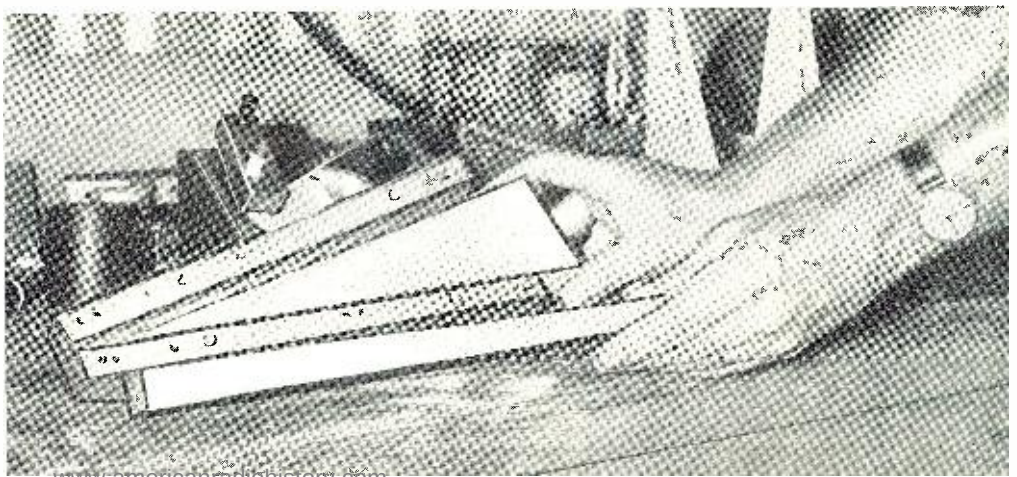

www.americanradiohistory.com

ERROR VOLTAGE DETECTOR

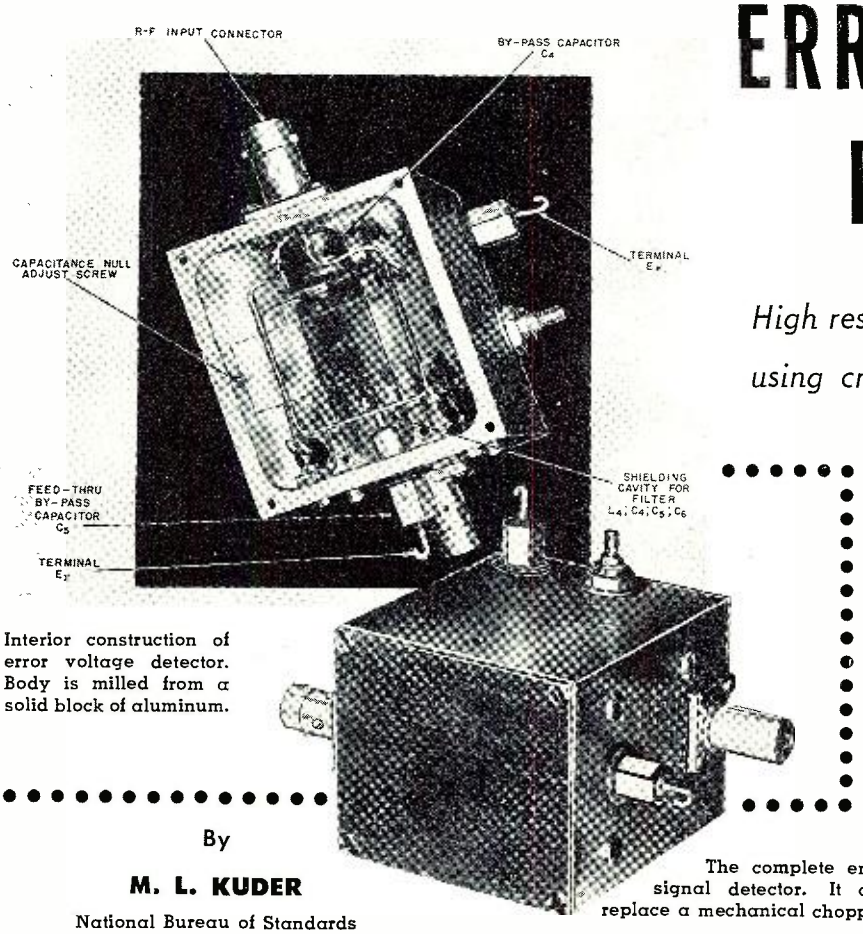High resolution and stability are attained using crystal diodes in a bridge circuit.



Interior construction of error voltage detector. Body is milled from a solid block of aluminum.

The complete error signal detector. It can replace a mechanical chopper.

By

M. L. KUDER


National Bureau of Standards

SOME OF the most important and rapid technological advances of the past decade have been in the automatic control of machines and processes, and substantial extension of this trend toward automatization in industrial and military technology seems highly probable. Many significant applications of automatic control are based on servo feedback systems. These systems may be thought of as arrangements in which any deviation of a controlled device or process gives rise to an error signal—usually an electrical voltage. The servo system then initiates a corrective action which continues until the error signal is brought very nearly to zero, i.e., until the desired condition is reached.

A crucial element of any servo system is the method or device used for sensing the error signal, which usually means detecting the difference between two voltages. Ideally, a signal detector should be able to measure the error signal immediately when the controlled process deviates from the desired condition by even the smallest amount, and to initiate remedial action in the shortest possible time. The need for greater response speeds in some servo applications brought about a search for a detector which would make a more rapid sampling of the output than a mechanical vibrator or chopper with its limited frequency. Inertia characteristics of a mechanical device place a definite limitation on the over-all response speed. The chopper principle, however, must be retained in order that the error detector may respond to d.c. signals as well as a.c. signals up to video frequencies—a fundamental requirement of many servo applications.

In order to achieve a more rapid sampling rate, it was found necessary to eliminate the mechanical parts altogether and to use electronic circuit elements. Some sensitivity is sacrificed, but the speed of response of the system is tremendously increased, and resolution to 1 millivolt with a bandwidth of 1 mc. can be achieved. The best stability in an electronic circuit is usually obtained when only passive components are used in the critical parts of the system. At present, a germanium diode appears to be the best passive chopper element. When it is designed into a device that is self-compensating for temperature coefficients of the crystals, zero-drift stability to 1 millivolt is readily attainable.

Circuit of the error voltage detector.

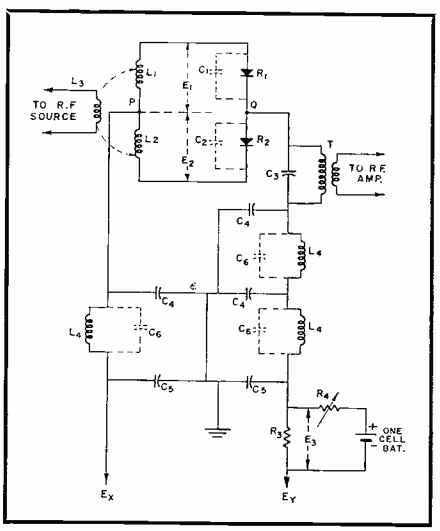

Essentially, the NBS error voltage detector is a bridge modulator with an r.f. carrier as its source and the modulating signal as a dynamic controller of resistive balance. High sensitivity for signals near zero in amplitude is the primary aim, and nonlinear reduction in sensitivity for signals departing from zero is both convenient and desirable. Two of the arms of the bridge are germanium diodes whose forward resistances are compared, and the other two arms are inductors which serve as r.f. voltage sources for excitation of the diodes. The usual difficulty with contact potentials in germanium diodes is minimized by having the crystals operate at a carrier voltage high compared to the contact potential.


During one half of the carrier cycle, neither diode conducts, and the output is zero. During the other half-cycle, the output is still zero when the two diodes have the same forward resistance. But an error voltage applies a differential bias, unbalances these resistances, and causes a portion of the r.f. carrier to appear at the output. Thus, the error voltage causes partial half-wave rectification of the r.f. source, and the output voltage itself contains a component at the r.f. frequency which is amplified and serves as the indication of the error-signal voltage.

Mechanical details are important in the design and construction of the detector. Excellent shielding between in-

(*Continued on page* –34–)

www.americanradiohistory.com

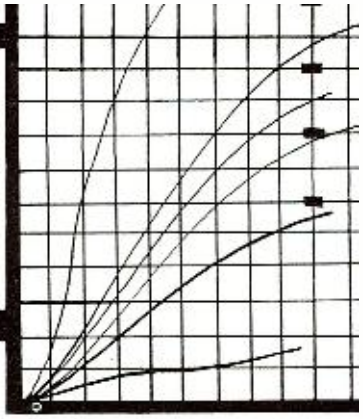TRANSISTOR CONTROL OF MAGNETIC AMPLIFIERS*



By

G. F. PITTMAN, JR.

Westinghouse Electric Corporation

Possible applications of transistors as control elements in self-saturating magnetic amplifiers.

IT IS the purpose of this article to present some results of an investigation of possible applications for transistors in magnetic amplifier circuitry. Although the transistors which are available commercially at present leave much to be desired—especially in terms of temperature sensitivity—transistor technology is advancing at a rapid pace, and it is felt that an awareness of possible applications in the magnetic amplifier field may prove valuable in permitting utilization of improved transistor characteristics as they become available. The applications discussed involve the use of transistors as control elements of self-saturating magnetic amplifiers.


General Concepts

Although the operation of self-saturating magnetic amplifiers has been treated numerous times in the literature[1], several general concepts which are directly related to the subject of this article bear mentioning.

Control of self-saturating magnetic amplifier output is exercised directly by controlling the flux level to which a core is reset during the half-cycle preceding its firing[2,3,4]. In order to accomplish resetting of the core, power (both current and voltage) must be supplied to a control winding on the core. In particular types of circuits, however, it is more convenient to consider either the control current or the control voltage as the independent control variable; both concepts will be used in discussing the operation of the circuits to be considered—the choice being one of convenience of explanation.

The response time characterizing the response of a self-saturating magnetic amplifier output to a step change in the control variable depends upon the manner in which resetting is accomplished. If the resetting of a core of a two-core, self-saturating magnetic amplifier is dependent only upon the value of the control variable during that half-cycle in which the core is reset, then the output on a given half-cycle will depend only upon the value of the control variable during the preceding half-cycle. The minimum possible response time, one cycle of the a.c. source frequency, is obtained under these conditions. Assuming that there is no interaction between the two cores of a self-saturating magnetic amplifier through the output circuit, the conditions are fulfilled if resetting is carried out independent of the voltage induced in the control winding of the core proceeding toward firing. Circuits in which this is the case, and which yield one-cycle response, have been described in the literature[3]. In practice, it is found that the assumption of no interaction between the resetting and firing cores through the output circuit is valid for full-wave bridge and center-tap d.c. self-saturating output circuits, but that some interaction takes place in the doubler output circuit. This results in the minimum or residual response time of the doubler circuit being somewhat longer than the one-cycle minimum response time of the other circuits.

Fig. 1. **(A) Idealized nonlinear characteristics of a junction transistor. (B) Common base transistor connection.**

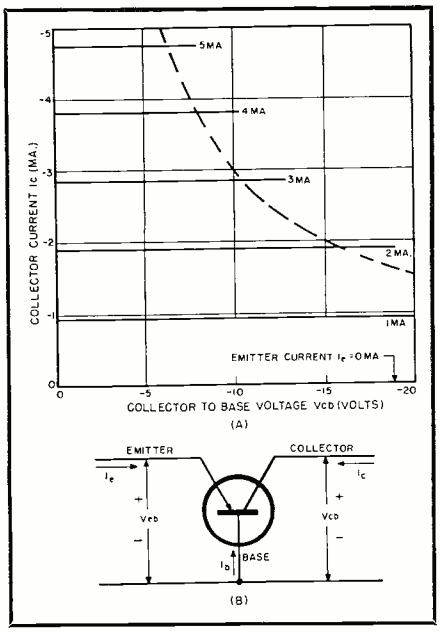

On the other hand, in the case of conventional self-saturating circuits with low control circuit impedance, a major portion of the resetting is produced by the voltage induced in the control winding of the core proceeding toward firing. Thus, a change in the control voltage produces—in the half cycle following its occurrence—only a relatively small percentage of the ultimate change in reset flux level, and response times far in excess of one cycle of the a.c. source frequency result.

The transistors referred to in this article are of the *p-n-p* junction type; however, the results apply equally well to the *n-p-n* junction type with due regard for polarities, and basically to point-contact transistors as well.

In general, the transistor is considered as a circuit element exhibiting nonlinear characteristics of the type shown idealized in Fig. 1A. Referring to the common base connection of Fig. 1B, the plot gives collector current I_c as a function of collector-to-base voltage V_{cb}, with emitter current I_e as a parameter. These characteristics indicate that if a load is placed in the collector circuit the transistor will function essentially as a controllable constant-current source controlled by the current supplied to the emitter, provided the collector-to-base voltage is maintained between zero and some negative value dictated by the power dissipation capabilities of the transistor (as shown by the dashed line in Fig. 1A). Approximately a one-to-one correspondence is seen to exist between output (collector) and input (emitter) currents; however, the impedance level

*This article is based on a paper presented at the 1953 National Electronics Conference, held in Chicago, Ill., Sept. 28-30.

www.americanradiohistory.com

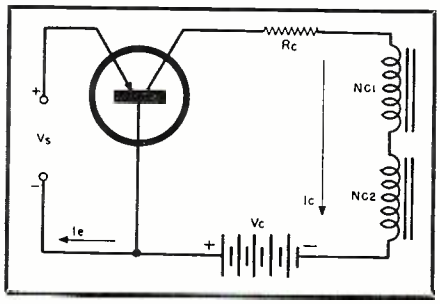


Fig. 2. Transistor preamplifier for magnetic amplifier control windings.

of the emitter circuit is considerably lower than that of the collector circuit, resulting in a net power amplification.

Although the common base transistor connection shown in Fig. 1B is used as the basis for the applications discussed in this report, other connections are possible, and at times are advantageous. For instance, the common emitter connection—in which the signal current is supplied to the base terminal—provides output circuit characteristics quite similar to the common base connection, and is applicable to any of the uses to be described. Input current and power requirements of the common emitter connection are considerably lower than those of the common base connection; however, changes in characteristics with temperature are much more severe.

Methods of Control

An application which is immediately suggested by the power amplification capabilities of the transistor is the use of the transistor as a preamplifier feeding the control windings of a magnetic amplifier as its load, shown in Fig. 2; (only the control windings, N_{c1} and N_{c2}, of the magnetic amplifier are shown since the output circuit may incorporate any of the conventional self-saturating connections). Because of the interdependence of magnetic amplifier input power and response time, the power gain obtained through the transistor preamplifier may be used to achieve any of several desirable effects, depending upon the design of the magnetic amplifier and its control windings:

1. Input power to the magnetic amplifier for a given signal power may be increased, resulting in a shorter magnetic amplifier response time.
2. Signal power required to obtain a given magnetic amplifier output may be reduced by the amount of the transistor power gain without a corresponding increase in magnetic amplifier response time.
3. A combination of the above two effects may be achieved, i.e., both response time and signal power requirements may be reduced to some degree.

In any case, an increase in over-all figure of merit (power gain/response time) is effected by the insertion of the transistor preamplifier.

The constant-current source or high differential resistance characteristic of the transistor collector circuit has an important effect upon the magnetic amplifier being controlled. Assuming that the transistor operates at all times within the region of its characteristics, as shown in Fig. 1A (the collector-to-base voltage being maintained at less than zero at all times), the control circuit current will have a constant value as determined by the emitter current supplied to the transistor. The flow of induced harmonic currents in the control circuit under this condition is prevented by the high differential resistance of the transistor collector circuit. In the absence of induced current flow, no coupling exists between the two cores of the magnetic amplifier through the control circuit, and the resetting of one core is in no way affected by the induced voltage in the control winding of the other core in its firing half-cycle. Thus, the response time of the magnetic amplifier is the minimum or residual value corresponding to the self-saturating output circuit in use (one cycle of the a.c. source frequency for full-wave bridge and center-tap d.c.-output circuits and somewhat longer for the doubler circuit).


Blocking of induced current flow by the transistor implies that voltages induced in the magnetic amplifier control windings will appear in full across the transistor collector and base terminals superimposed upon the d.c. voltages existing in the circuit. The condition is therefore imposed that induced control-winding voltages, acting in conjunction with the d.c. voltages present, must be of a sufficiently low magnitude that transistor voltage and power dissipation ratings are not exceeded and that the collector-to-base voltage does not go positive. This condition must be given careful consideration in the design of control windings to be fed by the transistor preamplifier.

Use of the transistor preamplifier with the self-saturating magnetic amplifier circuit thus results in a transistor-magnetic amplifier with a response time equal to the residual or minimum response time of the magnetic amplifier but with lower signal power requirements than those of the magnetic amplifier under residual response time conditions. The over-all figure of merit is therefore significantly higher than that of the magnetic amplifier alone.

The transistor control scheme just discussed is a straightforward cascading of two power amplification units with due allowance being made for the active nature of the magnetic amplifier input circuit. A number of less conventional methods of control may be developed if the transistor is considered, not as an amplifier, but rather as a circuit element which may be integrated into the magnetic amplifier circuitry. Two examples will be given of such a utilization of transistors as variable circuit elements for the control of magnetic amplifier output.

Figure 3A shows, in half-wave form, a circuit which permits control of magnetic amplifier output by a variable impedance control element[5]. The control circuit contains an a.c. voltage source, V_c, of such magnitude and polarity that—with the control element exhibiting its minimum impedance—the core is reset just the amount necessary to prevent firing on the subsequent half-cycle. The rectifier in series with the control circuit serves to prevent the flow of current in this circuit during the firing half-cycle. During the resetting half-cycle of the a.c. source voltage, the voltage drop across this element due to the flow of control-circuit current subtracts from the effectiveness of the control-circuit a.c. voltage source in resetting the core. Thus, by varying the impedance of the control element, the amount of resetting and—hence—the output on the subsequent half-cycle may be controlled. The transistor is admirably suited to this application since the impedance seen between its collector and base terminals is variable between essentially zero and infinity, permitting full control of magnetic amplifier output from cutoff (with zero impedance) to full saturation output (with infinite impedance).

Fig. 3. (A) Circuit which permits control of magnetic amplifier output by a variable impedance control element. (B) Full-wave version of (A).

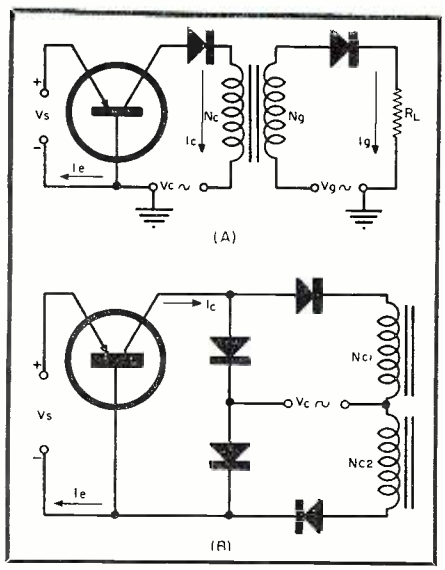

www.americanradiohistory.com

A full-wave circuit using a transistor in this manner is shown in Fig. 3B; as in Fig. 2, only the control windings of the magnetic amplifier are shown. In this circuit, the a.c. voltage source in series with the transistor appears across the control windings of the two cores on alternate half-cycles, the control circuit of the other core being blocked by the rectifier in series with it. The rectifier arrangement is such that the current flow through the transistor is always in the same direction. Control of resetting is exercised, just as in the half-wave circuit above, by the impedance seen between the transistor collector and base terminals varying in accordance with the signal current supplied to the transistor emitter circuit.

As in the case of the transistor preamplifier, the resetting in this circuit proceeds independently of the action of the firing core; the response time is again the minimum or residual value for the output circuit used. The transistor provides a power amplification in this circuit also, since the power controlled by the transistor is greater than that required by the emitter circuit to control it. Consideration of the operation of this circuit and of the transistor preamplifier circuit shows that overall power gains and response times of the two circuits will be very nearly the same for a given magnetic amplifier and transistor.

A different method of utilization of the transistor as a variable impedance element to control magnetic amplifier output is shown in Fig. 4A, again in half-wave form. The core is biased to cutoff by the bias current which is supplied from a stiff current source in order to prevent the flow of induced currents in the bias winding. Polarities are such that—during the firing half cycle of the a.c. source voltage—the voltage induced in the control winding is blocked by the control-circuit rectifier. On the other hand, during the resetting half-cycle, the induced voltage appears across the transistor collector and base terminals. Depending upon the signal current supplied to the emitter, the transistor permits more or less induced current to flow in the control winding during the resetting half-cycle. This current acts as an additional controlling magnetomotive force on the core in a direction opposing the resetting action of the bias magnetomotive force.


In the extreme case of zero emitter current, the transistor exhibits a very high impedance between its base and collector terminals. Thus, the flow of induced current is essentially prevented, and the core resets fully under the action of the bias current. Minimum output results with zero signal.

At the other extreme, if an emitter current is supplied which corresponds to a transistor collector current equal to or slightly greater than the bias current reduced to the control winding turns base, the transistor appears as a very low impedance across the control winding, and induced current flows freely. Under this condition, the core acts as a current transformer during the resetting half-cycle, and a current flows in the control winding approximately equal to and opposite the bias current on a common turns base. The net controlling magnetomotive force is approximately zero, and the core does not reset at all; full output is obtained.

For intermediate values of emitter current, proportional induced currents are permitted to flow; control of resetting—and thus of output—is achieved.

A full-wave control circuit using this method of control is shown in Fig. 4B. Here again, the cores are controlled on alternate half-cycles while the control circuit of the other core is blocked by the rectifier in series with its control winding. As with the methods previously discussed, the over-all response time is the minimum value corresponding to the output circuit used. The power controlled by the transistor and the signal power requirements are approximately the same as in the previous method for a given magnetic amplifier, so that the performance of this method of control is comparable to the first two in all respects.

Fig. 4. (A) Another method for controlling a magnetic amplifier output by a variable impedance control element. (B) Full-wave version of (A).

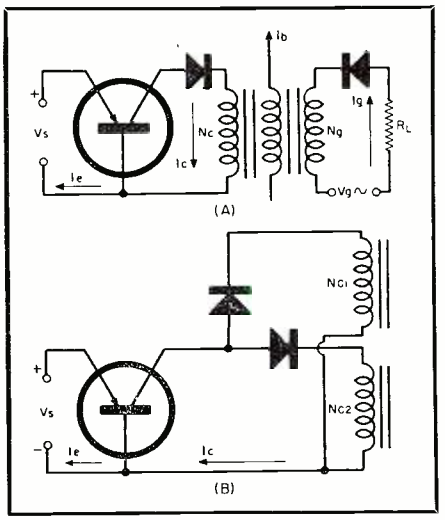

Experimentation

Figure 5 shows experimental transfer characteristics obtained for the three methods of transistor control applied to a full-wave bridge self-saturating magnetic amplifier with the specifications given in Table I. The transistor used is a CK-722 *p-n-p* junction type with common base connection.

Cores:	1" I.D. x 1½" O.D. x ½" tape wound of 2-mil "HIPERNIK V" material
Windings:	
	gate winding turns—1240
	control winding turns—480
	bias winding turns—20
Rectifiers:	
	self-saturating—two 1½"-sq. selenium cells per leg
	load—one 1½"-sq. selenium cell per leg
	control circuit—1N63 germanium diodes
Load Resistance:	25 ohms
A.C. Supply:	30 volts (r.m.s.), 60 cps


Table 1. Specifications used in obtaining the characteristics of Fig. 5.

Curve 1 shows magnetic amplifier output current plotted against transistor emitter input current for the transistor d.c. preamplifier shown in Fig. 2. In this case, the collector d.c. source voltage was 16.5 volts and the total control circuit resistance 4100 ohms. A d.c. bias current of 70 ma. was applied to yield magnetic amplifier cutoff at zero emitter current.

Curve 2 shows similar data for the transistor control scheme of Fig. 3B. For this curve, the emitter input cur-

(Continued on page –30–)

Fig. 5. Experimental transfer characteristics. (1) Magnetic amplifier output vs. emitter input current for Fig. 2. (2) Similar curve for Fig. 3B. (3) Transfer characteristic for Fig. 4B using a 70-ma. bias current. (4) Transfer characteristic of magnetic amplifier with high control circuit impedance.

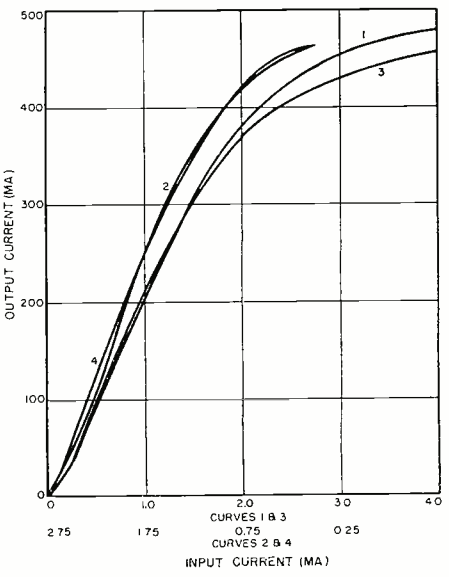

www.americanradiohistory.com

INTERNATIONAL TELECOMMUNICATIONS VIA V.H.F. RELAYS

By

VICTOR J. NEXON and **WILLIAM S. HALSTEAD**

Microwave Services, Inc. Unitel, Inc.

Part 1. A review of recent findings with respect to propagation of radio waves beyond the horizon at frequencies above 30 mc.

SERIOUS congestion on the limited number of international radio channels at frequencies below 30 mc., the need for speedier and more reliable radiotelephone service between continental areas, and the unstable propagation characteristics of the present high-frequency radio circuits have led to consideration of means by which expansion and improvements in international radio facilities may be attained.


In addition to these important factors, continuing progress in the development of international television and radio broadcasting, superspeed facsimile, and multiplex telephony has presented a basic technical requirement for transmission bandwidths far greater than those available in the existing radio channels at frequencies below 30 mc. Because these advanced communication techniques can become powerful new tools in unifying, strengthening and informing the free world, engineers dealing with international telecommunications are seeking enough radio spectrum space to accommodate these wide-band services.

In the opinion of the authors of this article, the utilization of carrier frequencies above 30 mc. and employment of relay techniques in which concentrated energy is directed along narrow paths in the earth's atmosphere present an effective means with which to meet the expanding requirements of international radiocommunications. With these higher frequencies—ranging upwards from 30 mc. through the v.h.f., u.h.f. and s.h.f. bands—and employment of radio beam propagation methods, a high order of efficiency of radio spectrum utilization is obtained which enables the same frequency allocations to be used in many geographic areas without risk of interference. Moreover, the greater channel widths that are practicable in the v.h.f., u.h.f. and s.h.f. bands permit full utilization of wide-band modulation and multiplex methods of relatively great efficiency and traffic-handling ability.

As an example, a single wide-band v.h.f. channel of modest proportions, having a modulation base-band of 500 kc. and employing a relatively small number of multiplex telephone channels, can carry the equivalent of all of the radiotelephone, telegraph and facsimile traffic now transmitted across the Atlantic by the many short-wave radio stations and cables utilized in overseas services.

Such a system, utilizing a transmission path within the earth's atmosphere, would be relatively free of the interference and distortion now commonly experienced on long-distance radio circuits that utilize ionosphere reflection paths. By employing modulation bandwidths of several megacycles or increasing the number of radio carriers at relay stations, it is possible to provide hundreds of duplex telephone channels and circuits for tone-teletype, facsimile, and international broadcast services—including television on important occasions of international interest.

Fig. 1. Profile of path between v.h.f. relay stations separated by a mountain, illustrating "obstacle-gain" principle.

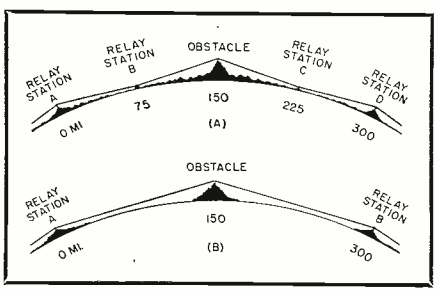

Basic relay methods which permit wide-band transmission through a large number of stations in a chain extending over continental distances have already demonstrated their practicability and high degree of performance in the *AT&T* microwave relay system between the Atlantic and Pacific coasts. It is logical, in view of the successful operation of the American transcontinental system, to give consideration to the use of similar radio relay principles in the s.h.f., u.h.f., or v.h.f. bands in traversing long distances in areas outside of the United States, where—in many instances—telecommunication facilities are inadequate to meet basic needs of countries with respect to domestic as well as international services.

In this larger world area, where improved telecommunications can do much to expand trade and assist in unifying the free world, a radio relay system can span territory between the principal cities of countries in which wire lines cannot meet present requirements or effectively be maintained or protected. The radio relay systems can, if desired, be integrated with v.h.f. communication facilities—at elevated points strategically located in different regional areas of a country through which the relay chain extends—to serve many important domestic needs while simultaneously serving to carry international traffic between the nation's borders.

In this manner, by combining in a single coordinated system the radio transmission facilities for a number of services, such as domestic and international telephone, telegraph, radio and television broadcasting, mobile and airway communications, and radar, the system becomes economically feasible for countries in which the cost would otherwise remove from consideration the use of radio relay methods.

www.americanradiohistory.com

Location of Relay Link	Airline Distance (miles)	Elevation of Stations Above Sea Level (ft.)	Frequency (mc.)	Antenna (1) Input (2) Gain	Character of Path	Service Facilities
Grasse, France	127	1902	97	(1) 100 w. (2) 10 db	over water	multichannel telephone (24 carrier channels)
to Calenzana, Corsica		1049	107	(1) 100 w. (2) 10 db		
Mt. Cavo, Italy	242	3200	40-50	(1) 500 w. (2) 20 db	over water	multichannel telephone (48 carrier channels)
to Mt. Serpeddi, Sardinia		3200	40-50	(1) 1 kw. (2) 20 db		

Table 1. Characteristics of two v.h.f. relay links using transmission paths beyond the radio horizon.

While the potential of wide-band radio relay at frequencies above 30 mc. and especially above 1000 mc. has been realized in many domestic services in the United States and abroad, the limitations of transmission range of many of these systems within quasi-optical distances have presented many technical and economic problems that have restricted the general application of wide-band relay methods in the international field. The high cost of a wide-band microwave relay system in which average interstation distances of the order of 30 miles are involved, as in typical radio relay systems in the United States, may make it impracticable to consider the utilization of these short-range relay techniques in many areas of the world where communication facilities are inadequate to meet basic needs and where wide-band relay services could be of great value. For this reason, consideration has been given to the use of high power transmitting systems at frequencies in the v.h.f. and u.h.f. bands to span distances of the order of 150 miles or more between relay stations in areas where this would be desirable.

To date, there has been accumulated a considerable amount of measured data that indicates the practicability of v.h.f.-u.h.f. relay systems in which separations between stations of 150-300 miles may be attained by utilization of high transmitter power, high antenna gains, and sensitive receivers. Work conducted by manufacturers, laboratories and users, including reports of the Central Radio Propagation Laboratory[1] and Federal Communications Commission[2], leaves little doubt that useful signals in the v.h.f. and u.h.f. bands can be transmitted over these distances.

As a review of some of the work and the results experienced over "beyond horizon" distances, information will be given on several reports and their conclusions. In addition, data on commercial operating systems will be presented.

Reference is made to a report by Irvin H. Gerks[3], published in the Proceedings of the I.R.E. for November, 1951. Utilizing a 30-kw. transmitter at a carrier frequency of 412 mc., with antenna gains of 28 db at the transmitter and 20 db at the receiver, results were obtained that led to the following partial conclusion at the time: "For communication grade of service, it appears entirely feasible to operate a 100-mile link with low, directional antennas and about 10 kw. of transmitter power with a probability of satisfactory field strength more than 90% of the time. In fact, quite effective use of the scattered wave can be made to a distance of 200 miles."

A further reference is made to a paper by Kenneth Bullington[4] in the Proceedings of the I.R.E. for January, 1953. Various tests were made at 460 mc., 535 mc. and 3710 mc., utilizing high transmitting power and large antennas. The data presented in this paper indicated that median signals received at 300 miles were approximately 65 db to 90 db below free space, depending on the test area and the frequency. A comparison of this data with long-term data accumulated by the FCC—as presented in the Bullington paper—shows similar variations of median received signals with distance, and indicates a received median signal level of approximately 78 db below free space for frequencies from 40 to 300 mc. at 300 miles.

A conclusion is quoted from this report: "Although the signal levels are much higher than was commonly expected, high transmitter power and large antennas are needed to obtain

Table 2. Reports on long-range transmission of television signals over distances up to 330 miles.

Location of Television Transmitting and Receiving Points	Airline Distance (miles)	Elevation of Antennas Above (1) Average Terrain (2) Sea Level (ft.)	Frequency of Video Carrier (mc.)	Power (ERP, kw.)	Character of Path	Remarks
KEYL-TV, San Antonio, Texas	254	(1) 450 (2) 1187	77.25 (Ch. 5)	35.2	over land; flat terrain	Programs from KEYL-TV received directly by XELD-TV and retransmitted on schedule*.
to XELD-TV, Matamoros, Mexico		(1) 335 (2) 400				
KGUL-TV, Galveston, Texas	300	(1) 550 (2) 608	199.25 (Ch. 11)	235	over water	Consistent reception of KGUL-TV in Brownsville for 11 days in March, 1953. No multipath distortion noted*.
to Brownsville, Texas		(1) (2) (approx. 50-100)				
WBZ-TV, Boston, Mass.	140	(1) 530 (2) 669	67.25 (Ch. 4)	100	over land; hilly to mountainous	Excellent TV reception at summit of Mt. Washington. No observable multipath effect or fading. Measured field in excess of 1 mv/m.
to Mt. Washington, N. H. (*Unitel* field studies)		(1) 3817 (2) 6346				
WNAC-TV, Boston, Mass.	135	(1) 480 (2) 600	175.25 (Ch. 7)	200	over land; hilly to mountainous	Excellent TV reception. No multipath effect noted. Measured field in excess of 1 mv/m.
to Mt. Washington, N. H. (*Unitel* field studies)		(1) 3817 (2) 6346				
XEW-TV, Cortez Pass, Mexico City	330	(1) 5800 (2) 12800	187.25 (Ch. 9)	25	over land; mountainous to flat	Television image received at 130 miles. No multipath effect observed. Estimated field strength of 10-20 μv/m.
to Aircraft employed in field measurements of *Unitel, Inc.*		(1) 5900 (2) 6000				

**Data from Albert Metcalf, Director of XELD-TV, Matamoros, Mexico*

www.americanradiohistory.com

reliable voice channels over distances of 200 miles or more. The high-gain antennas needed at both the transmitter and receiver indicate that the most likely application of long-path transmission will be for point-to-point service over difficult terrain."

By utilization of the Bullington data in which a loss of 78 db below the free-space value for a path length of 300 miles at a frequency of 250 mc. is indicated, and assuming a free-space propagation loss of approximately 135 db, it is calculated that the total propagation loss between two isotropic antennas at this distance is 213 db. To offset this loss, a 50-kw. transmitter providing a power level of + 47 dbw, and two paraboloid antennas having diameters of approximately 50 feet giving a combined gain of 58 db, may be utilized to provide a total power level of + 105 dbw. This will provide a resulting input level at the receivers of — 108 dbw, excluding line losses, which is considered to be within the useful range of a typical v.h.f. receiver for satisfactory operation with bandwidths of several megacycles.

If the transmitting station is located at maximum practicable elevation to increase the distance to the region beyond the horizon where the largest propagation losses occur, it is probable that these power requirements may be reduced—as is borne out in practice at many v.h.f. stations where high elevations are commonly employed.

Antennas having the necessary high-gain characteristics in v.h.f. and u.h.f. bands can be constructed, as evidenced by the fact that one company—*RCA*—is now developing a paraboloid antenna of large dimensions which will provide the very substantial amount of effective radiated power required in superoptical transmission paths in the v.h.f. or u.h.f. bands. This antenna is 40 feet in diameter and is designed for use with frequencies from 230 to 500 mc. Its gain is from 26 to 32 db over this range.

Presently available tubes and other components for use in commercial television transmitting equipment have power output ratings up to 50 kw. in the v.h.f. television band and to at least 12 kw. in the u.h.f. television band. Thus, the tools now exist which—when used in combination with high gain antennas—provide megawatts of effective radiated power within the v.h.f. and u.h.f. regions of the radio spectrum below 1000 mc. As an illustration, a wide-band u.h.f. transmitter having a modulation bandwidth of several megacycles, and capable of providing 10 kw. at the input of a paraboloid antenna which has a power gain of 30 db at a carrier frequency of 500 mc., will develop an effective radiated power of 10 megawatts.

In the upper portion of the v.h.f. television band, where transmitters of higher output ratings are practicable at this time, it is possible to provide on a wide-band basis an antenna input power of 50 kw., which—with a paraboloid antenna having a power gain of 30 db—will give an effective radiated power of 50 megawatts.

With this order of effective radiated power, when viewed in the light of available data on u.h.f. and v.h.f. propagation beyond the horizon, reliable operation of relay systems having interstation distances of 200-300 miles on overland or over-water routes appears to be feasible.

When it is realized that a distance of approximately 290 miles represents the greatest over-water hop on projected international relay routes along the island chains that extend between the continents of the world, the ability to accomplish reliable wide-band v.h.f. or

(*Continued on page* –37–)

"OBSTACLE-GAIN" TRANSMISSION


RECENT experiments with long-range v.h.f. transmission in mountainous regions have demonstrated the possibility of utilizing knife-edge obstacles as a means for increasing the received signal energy of television, FM, and military communications. These experiments have verified the "obstacle-gain" theory which predicts the possibility of tremendous power gains for v.h.f. propagation over mountain obstacles. Analyses of the experimental data and interviews with scientists and engineers in the field were conducted jointly by the U. S. Army Signal Corps, the National Bureau of Standards, and *Radio Corporation of America*. Indications are that the disadvantages previously attributed to the transmission of very high frequencies (30 to 100 mc.) among high mountain ridges can actually become powerful aids for reducing both transmission loss and tropospheric fading. The results of these obstacle-gain experiments may have a deciding influence on the future choice of sites for transmitting and booster station installations.

The obstacle-gain theory states that the transmission of very high frequencies over a knife-edge type obstacle should be considered as a four-ray combination of reflection, diffraction, and atmospheric refraction. Thus, if a transmitter and receiver are separated by a mountain, the radio waves would be received by means of the following mechanisms: (1) diffraction at the top of the obstacle; (2) reflection from the ground between the transmitter and the obstacle and then diffraction over the obstacle; (3) diffraction over the obstacle and reflection from the ground between the obstacle and the receiver; and (4) a combination of the two ground reflections with diffraction over the obstacle.

A requirement for the use of the obstacle-gain method for increasing signal strength is that the height of the obstruction must be greater than the elevation of the common horizon. For example, transmission losses will be considerably reduced at 100 mc. if a knife-edge type of obstacle for a 150-mile circuit is at the mid-point of the path and about 1300 feet above the surrounding terrain. Theoretically, these conditions should result in a 30-db decrease in transmission loss over that which would be calculated if the obstacle were not there. The amount of reduction in transmission loss can be varied by different combinations of antenna heights, obstacle heights, and frequency.

One of the obstacle-gain experimental paths examined in detail was a 38-mc., 160-mile communication circuit between Yakutat and Gustavous, Alaska, operated by the Civil Aeronautics Administration. The radio wave transmissions, which originated from and terminated at low-level installations (approximately 200 feet above sea level), passed over a 9000-foot ridge of Mt. Fairweather. On the basis of the existing smooth-earth diffraction theory for an unobstructed path, the calculated transmission loss for the circuit was 207 db. However, on the basis of the four-ray theory and the assumption that Mt. Fairweather acted as a single 8775-foot knife edge, the expected transmission loss was only 127 db. Experimental results showed that the actual transmission loss was approximately 134 db, within 7 db of the value predicted by the knife-edge calculations. The net obstacle gain was 73 db.

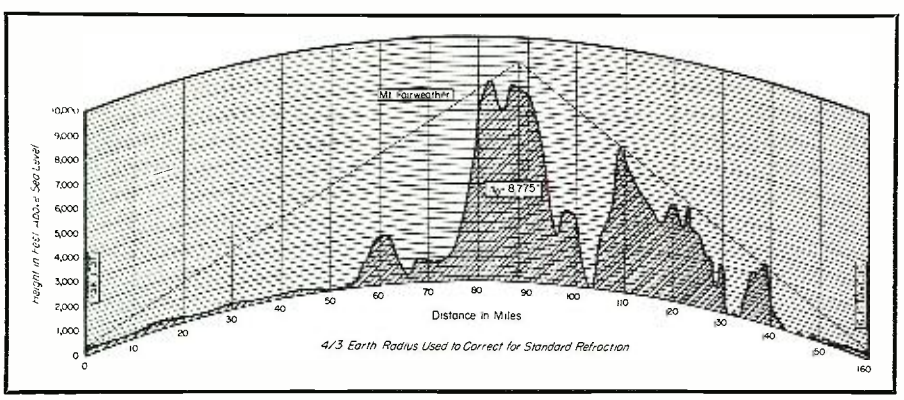Profile of v.h.f. path from Yakutat to Gustavous, Alaska (160 miles).



www.americanradiohistory.com


What means most to an Engineer?



PROFESSIONAL RECOGNITION



GOOD SALARY

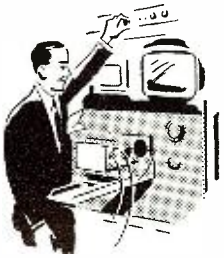

UNEXCELLED FACILITIES



SUBURBAN LIVING

A Career at RCA offers all Four!

RCA offers opportunities now—real career opportunities—for qualified ELECTRONIC, COMPUTER, ELECTRICAL, MECHANICAL and COMMUNICATIONS ENGINEERS . . . PHYSICISTS . . . METALLURGISTS . . . PHYSICAL CHEMISTS . . . CERAMISTS . . . GLASS TECHNOLOGISTS.

Positions are open in research, development, design and application. Long range work in many fields is being carried on both for commercial developments and military projects for war and peace.

At RCA you'll work in an exciting professional atmosphere, with technical and laboratory facilities unsurpassed anywhere in the radio-electronic industry. You are in close and constant association with leading scientists and engineers. Individual accomplishment is not only recognized, it is sought out. Delightful suburban living is easily available for your family. And there's ample opportunity for income and position advancement.

Plus, Company-paid hospitalization for you and your family . . . accident and life insurance . . . progressive retirement plan . . . fine recreational program . . . modern tuition-refund plan at recognized universities for advanced study.

Join the team at RCA, world leader in electronic development, first in radio, first in recorded music, first in television. Rest easy in the knowledge that your future is secure, the rewards many and varied.

Personal interviews arranged in your city.
Please send a complete resume of your education and experience to:

MR. JOHN R. WELD
Employment Manager, Dept. 304B
Radio Corporation of America
30 Rockefeller Plaza, New York 20, N.Y.

***Positions Open In*: RESEARCH—DEVELOPMENT—DESIGN—APPLICATION**
in any of the following fields:

RADAR—Circuitry—Antenna Design—Servo Systems—Information Display Systems—Gear Trains—Stable Elements—Intricate Mechanisms

COMPUTERS—Digital and Analog—Systems Planning—Storage Technique—Circuitry—Servo Mechanisms—Assembly Design—High Speed Intricate Mechanisms

COMMUNICATIONS — Microwave — Aviation — Mobile—Specialized Military Systems

MISSILE GUIDANCE—Systems Planning and Design—Radar and Fire Control—Servo Mechanisms—Vibration and Shock Problems

NAVIGATIONAL AIDS—Loran—Shoran—Altimeters—Airborne Radar

TELEVISION DEVELOPMENT—Receivers—Transmitters and Studio Equipment

COMPONENT PARTS—Transformer—Coil—Relay—Capacitor—Switch—Motor—Resistor

ELECTRONIC TUBE DEVELOPMENT—Receiving—Transmitting—Cathode-Ray—Phototubes and Magnetrons

ELECTRONIC EQUIPMENT FIELD ENGINEERS — Specialists for domestic and overseas assignment on military electronic communications and detection gear.

RADIO CORPORATION of AMERICA

www.americanradiohistory.com


DIODE-CAPACITOR MEMORY FOR COMPUTERS

By

ARTHUR W. HOLT

National Bureau of Standards

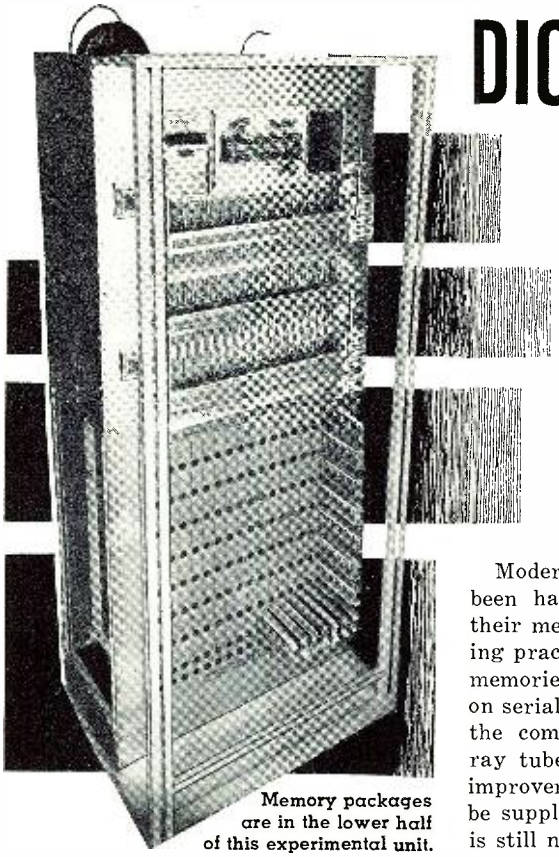
This simple, reliable memory provides very short access times for high speed computers.



Memory packages are in the lower half of this experimental unit.

CONTINUED research on rapid-access memories for high speed electronic computers has resulted in the development of an information storage device utilizing diodes and capacitors as the basic storage units. A recently completed prototype memory based on this idea appears to be faster than any other system; it more than matches the speed of the arithmetic unit used presently in SEAC (National Bureau of Standards Eastern Automatic Computer) and should at the same time, because of its simplicity, be more reliable than other memories now in use. The most difficult part of the basic problem of high speed access was overcome by the development of a selector matrix switch using diodes and transformers.

Fig. 1. Portion of the word selector matrix used in the high speed memory system.

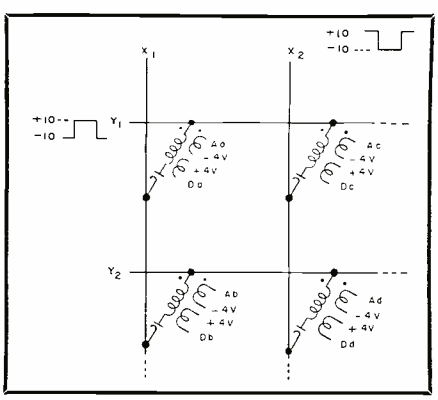

Modern electronic computers have been handicapped by the inability of their memories to attain speeds matching practical arithmetic units. Acoustic memories are slow because they depend on serial presentation of information to the computer. The Williams cathode-ray tube storage system is a distinct improvement because information can be supplied in parallel, but access time is still not small enough to balance the capabilities of possible arithmetic units. The diode-capacitor memory, however, which can be designed to present in excess of 100,000 randomly located 50-digit words per second to the computer, attains a speed corresponding to that of the arithmetic unit—with a resulting decrease in machine computation time for mathematical problems. In contrast, SEAC's acoustic memory has a random access of 6000 words per second while the Williams memory has an access rate of up to 60,000 words per second.

The system developed by NBS uses ordinary linear capacitors as discrete storage elements in a matrix arrangement. These capacitors provide memory by storing one of two voltage states; the charge which gradually leaks away through the associated circuitry is periodically restored. The memory circuit employs two diodes and a capacitor for each digit stored. If properly constructed, this type of memory promises very high reliability, because the minimum signal is of the order of one or two volts and need only be recognized as positive or negative in order to read the information. In the mercury memory and Williams memory schemes, the value of the low-level signal output is critical.


The basic circuit for the storage element is shown in Fig. 2. Point E is used for both reading and writing, while the two diodes are used as a "squeezer" to connect the capacitor to the read-write circuits. During holding, both diodes are biased in their back direction. For example, the anode of one diode might be held at -4 volts while the cathode of the other is held at $+4$ volts. Then, if the capacitor has a charge of, say, 2 volts, both diodes will be biased in their back direction, and only small currents will flow into or out of the capacitor.

When the ends of the diodes are both forced to ground potential ("squeezed"), one diode or the other will conduct, and a voltage will appear across the resistor. If the capacitor has been charged with 2 volts of such polarity as to make its lower terminal more negative than its upper terminal, there will appear at the output E a pulse of -2 volts, which dies out with the time constant RC. This negative pulse is recognized by the reading circuits at the output as the binary digit "zero." If the polarity on the capacitor had been in the opposite direction, the squeeze would have produced a positive pulse which would be recognized as the binary digit "one." Thus, the content of the storage element has been read; but in the process it has been at least partially discharged, and the information has been lost from the storage element. The information must be rewritten to continue the storage beyond the reading operation.

In order to write (or rewrite) information, it is only necessary to force the point E to the desired state and hold it there until the squeeze is over.

(*Continued on page* –32–)

Fig. 2. Basic circuit of storage element.

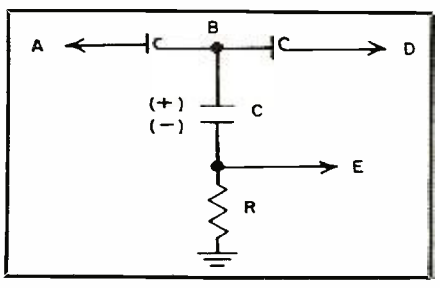


www.americanradiohistory.com


PRECISION *in* PINT-SIZE!

Bliley

BANTAM BX

CRYSTAL UNIT

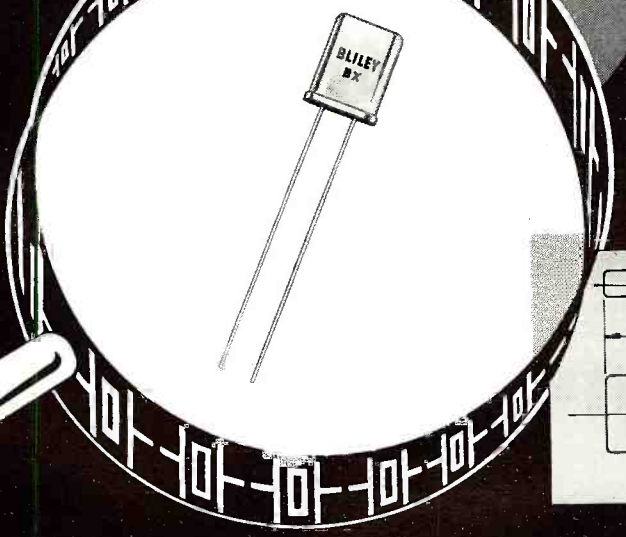

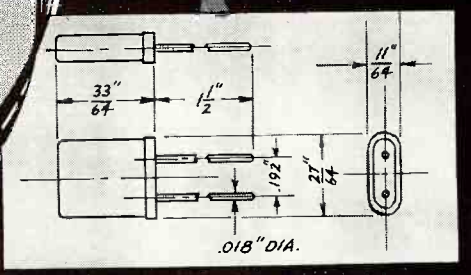

ACTUAL SIZE

BLILEY BANTAM BX
FREQ: 15mc-100mc

The new **BANTAM BX** has wire leads for mounting in a miniature selector switch or can be soldered to a printed circuit terminal board.

The new **BANTAM BX** does not sacrifice precision or dependability. It meets same performance and tolerance requirements as larger crystal units such as MIL types CR-23 or CR-32.

The new **BANTAM BX** is fully described in Bulletin 46. Now available for prototypes or in production quantities.

Bliley CRYSTALS


BLILEY ELECTRIC COMPANY
UNION STATION BLDG., ERIE, PA.

www.americanradiohistory.com

NEW TUBES

TV TETRODE

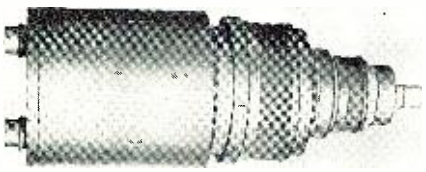Gain in excess of 10 and a power output of 25 kw. are features of the GL-6251, a v.h.f. TV tetrode being produced at the Schenectady, N. Y., plant of *General Electric Company's* Tube Department.



It is said to be the most powerful transmitting tube able to operate in all v.h.f. channels. Maximum ratings apply up to 220 mc., and only 5 kw. is needed to drive a pair of these tubes.

When used as a class B grounded-grid broadband TV amplifier, the GL-6251 has a useful synchronizing peak-power output of 30 kw. at 220 mc. In narrow-band class C service, the output is 25 kw. of continuous power when the tube is used as an amplifier or oscillator. Because of its ratings, the GL-6251 is also well adapted to dielectric heating equipment.

MINIATURE TWIN TETRODE

Having an over-all length of only 3 1/16" and a 7/8" diameter, Type 6360 is the newest addition to the *Amperex* line of twin tetrode tubes. It is particularly suitable for low-drain mobile transmitters and multiplier chains, where its ability to increase the power level quickly and to deliver a balanced output makes it ideal for driving higher power and higher frequency push-pull stages.

The *Amperex* 6360 is designed for use as a class C amplifier and oscillator, frequency multiplier and modulator for frequencies up to 200 mc. at maximum ratings, and is capable of delivering 16 watts at 200 mc. under ICAS conditions. For further information, write to *Amperex Electronic Corporation*, 230 Duffy Ave.. Hicksville, L. I., N. Y.


HIGH VACUUM RECTIFIER

Design rating charts and curves which define the performance of *CBS-Hytron's* 5AW4 high vacuum rectifier under a wide variety of operating conditions have been incorporated in a new data sheet on this tube. The data sheet, known as Bulletin #E-205A, is available from the Commercial Engineering Department of *CBS-Hytron*, Danvers, Mass.

A CTS-Rated tube, the 5AW4 was designed to replace the 5U4G; it has electrical characteristics similar to those of the older tube but includes many of the features of transmitting tubes that make for greater reliability and much longer life.

HEAVY-DUTY TRIODE

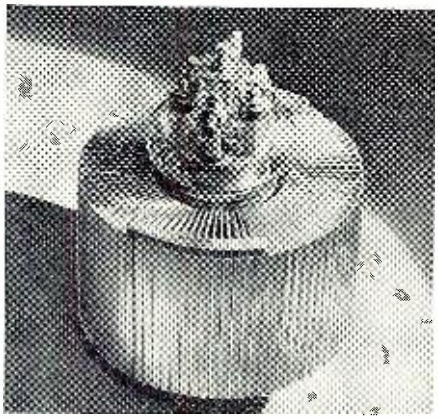Machlett Laboratories, Inc., Springdale, Conn., has announced the ML-5531—a forced-air-cooled heavy-duty triode for industrial and broadcast use. Operating at frequencies up to 30 mc., the



ML-5531 meets the need for a single-tube oscillator in 15-kw. output electronic heater service and a single-tube final-stage amplifier in 10-kw. AM broadcast service.

Incorporating a heavy-wall anode, stress-free and self-supporting thoriated tungsten filament, sturdy electrode mountings and kovar seals, the ML-5531 is designed to provide long low-cost operation under rigorous conditions. Maximum ratings include 30-kw. plate input and 10-kw. plate dissipation. The filament operates at 6.3 volts, 92 amperes.

COLOR TV TUBE PRODUCTION

Color TV picture tubes will be available to set manufacturers "in limited quantities" from the *General Electric Company* during the first quarter of 1954. Pilot production of the 15", round, all-glass type, which gives an approximately 12" picture, was scheduled to begin in January.

Using three electron guns and a planar shadow mask for color selection, these tubes are being made at the *G-E* tube plant at Electronics Park, Syracuse, N. Y., and will cost a set manufacturer "about ten times" the price of comparable black-and-white tubes.

RCA TUBES

A half-wave vacuum rectifier, a 21" rectangular glass kinescope, and two "pencil-type" u.h.f. triodes with external plate radiators have been announced by the Tube Department of *Radio Corporation of America*, Harrison, N. J.

Vacuum Rectifier


Intended for service as a damper diode in TV receivers, the glass-octal type 6AU4-GT (shown at left) is particularly suited for receivers which utilize picture tubes having 90° deflection. It is rated to withstand a maximum peak inverse plate voltage of 4500 volts, and can supply a maximum peak plate current of 1050 ma.

Kinescope

The 21ZP4-A is a rectangular glass picture tube utilizing magnetic focus and magnetic deflection. It has a screen size of 19 1/8" x 14 3/16" with slightly curved sides and rounded corners, spherical Filterglass faceplate, and a diagonal deflection angle of 70°. Other features include an external conductive bulb coating and an ion-trap gun.

"Pencil-Type" Triodes

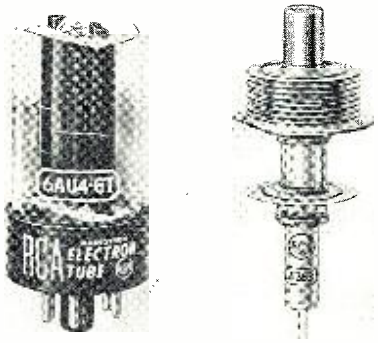
Designated as the 6263 and 6264, these two u.h.f. tubes are designed for use in low-power mobile transmitters and in aircraft transmitters at altitudes up to 60,000 feet without pressurized chambers. They have a maximum plate dissipation rating of 13 watts (ICAS), and can be operated with full ratings at



frequencies up to 500 mc. and with reduced ratings at frequencies as high as 1700 mc.

The 6263 (shown at right) has a μ of 27 and is intended for service as an r.f. power amplifier and c.w. oscillator, while the 6264—with a μ of 40—is primarily a frequency multiplier but may also be used as an r.f. power amplifier and c.w. oscillator.

www.americanradiohistory.com

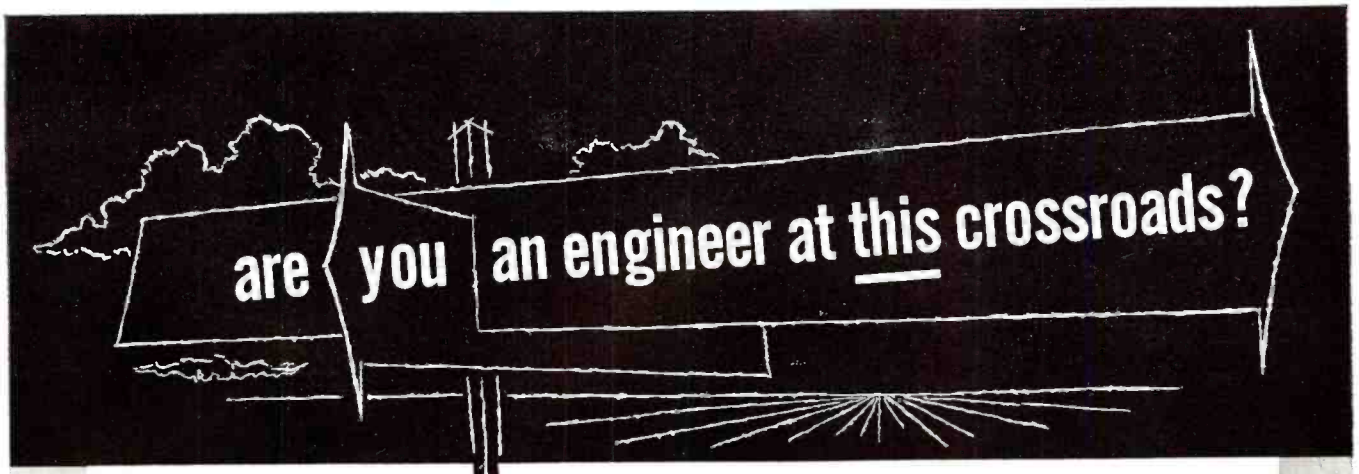

Never in the history of the electronics industry has it been more important for engineers to choose the right path for their careers to follow.

Everyone has done a lot of military work . . . but now the industry must find new markets in the industrial field!

As a leader in the production of industrial electronic equipment, Westinghouse has the necessary sales, distribution and field engineers organized to enter these new markets. We need research, design and development men to turn out the products. Now is the time to get into our organization, so that you'll be in on the ground floor as the industrial field expands!

Investigate the real future! Salaries at Westinghouse are open, commensurate with experience and ability. In addition to the usual employee benefits, we offer a stimulating patent-award plan and excellent opportunities for advanced study and degrees. Write for information today!

NUCLEAR REACTOR CONTROL ENGINEERS

Duties: Design, development, and application of electronic circuitry including vacuum tubes and magnetic amplifiers as applied to the control of nuclear reactors.

Requirements: Three or more years experience and a B.S. degree in Electrical Engineering or in Physics.

SENIOR RADAR ENGINEERS

Duties: Applied research, development, and design of advanced radar, fire control and missile guidance equipment. Openings exist in the fields of local oscillators and associated circuitry, indicators, feed-back problems (closed-loop electronic circuits), pulsed circuits, video, simulators, i.f. strips, and in analysis of complex radar.

Requirements: Three or more years experience and a B. S. degree in Electrical Engineering or in Physics.

SENIOR COMMUNICATIONS ENGINEERS

Duties: Applied research, development, and design of advanced communications equipment and systems. Openings exist in the fields of automatic transmitters and communications circuitry.

Requirements: Three or more years experience and a B. S. degree in Electrical Engineering or in Physics.

TRANSFORMER DESIGN ENGINEER

Duties: The applied research, development and design of audio transformers, modulation transformers and reactors, electric-wave filters, iron-core radio frequency transformers, radio frequency chokes, etc.

Requirements: Three or more years experience and a B. S. degree in Electrical Engineering or in Physics.

OR if you have experience in the fields of antennas, rf plumbing, magnetic amplifiers, technical writing, or in high frequency heating design and application, please apply.

To apply send resume of education and experience to
R. M. Swisher, Jr.
Employment Supervisor, Dept. F—1
Westinghouse Electric Corporation
109 West Lombard Street
Baltimore 1, Maryland


Westinghouse
ELECTRONICS DIVISION
BALTIMORE, MARYLAND

www.americanradiohistory.com

NEW PRODUCTS

CATHODE-RAY INDICATOR

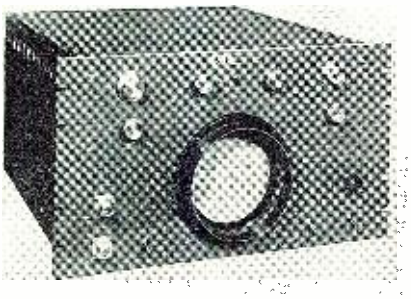Total writing speeds in excess of 500 cm./μsec. can be obtained with the *SKL* Model 600 cathode-ray indicator when it is used in conjunction with



an *SKL* Model 610 high speed sweep generator. It was designed to utilize the high writing speed capabilities of the type 5XP cathode-ray tube in advanced or special applications.

Single transients having very high writing speeds, such as are found in high tension studies of insulation breakdown, lightning, and extremely short pulses, may be easily displayed. The Model 600 can also be used with high speed cameras to record the waveform and characteristics of transient voltages. For further information, write *Spencer-Kennedy Laboratories, Inc.*, 186 Massachusetts Ave., Cambridge 39, Mass.

POWER OSCILLATOR

At the flick of a switch, the Model 1040 power oscillator will provide a frequency of either 400 or 1000 cps. Three watts of undistorted power (less



than 1%) are supplied at various output impedance levels by this instrument, which has been introduced by the *Industrial Test Equipment Co.*, 55 East 11th St., New York 3, N. Y.

Frequencies are factory-set to 0.25% and are maintained with high stability even with line voltage variations; a control on the front panel allows for a continuously variable output from 0 to 120 volts. While the Model 1040 is especially useful as a power source for all types of bridges and test setups, an isolated output transformer permits its use in modulation applications.

TV "IMAGE BOX"

Should regular film camera equipment fail, TV stations can televise films and slides on an emergency basis by



means of a low-cost device announced by *General Electric Company*, Electronics Park, Syracuse, N. Y. Called an "image box," this new device consists of an enclosed, specially ground glass plate developed for *G-E* by the *Bausch and Lomb Optical Company*. Images from films or slides projected upon one side of the glass plate can be picked up from the reverse side by a regular studio camera and relayed to the station's transmitter.

Q-CIRCUIT INDUCTORS

Boonton Radio Corporation, Boonton, N. J., has announced a new line of inductors, Type 590-A, designed for use in the *Q* circuits of this company's *Q* meters Type 170-A and Type 190-A. Available in six types, these inductors are useful for measuring the r.f. characteristics of condensers, resistors, and insulating materials over a frequency range of 20 to 230 mc. They may also be used as reference coils.

Each inductor consists of a high *Q* coil mounted in a shield, and is provided with spade lugs for connection to the coil terminals of the *Q* meters. The shield is connected to the lugs which connect to the low coil terminal




in order to minimize any changes in characteristics caused by stray coupling to elements or to ground.

MICROWAVE SPECTRUM ANALYZER

Vectron, Inc., has announced a new microwave spectrum analyzer with interchangeable r.f. heads—the Model SA25. A "low-noise" 20-kc. bandwidth i.f. strip (50 kc. available) incorporates the latest circuit techniques for higher usable gain and lower noise, and 12 interchangeable microwave r.f. heads are available to provide coverage in specific areas of the microwave band.

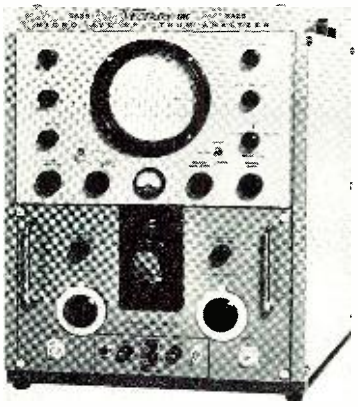The Model SA25 has a double-range sweep, covering 2 to 20 cps (or 6 to 60 cps) in two overlapping ranges, for improved operation with long or short



pulses at low or high repetition rates. Full information and specifications are contained in Bulletin SA25, which may be secured on request from *Vectron, Inc.*, 406 Main St., Waltham 54, Mass.

BROADBAND AMPLIFIER

High gain over the 2000 to 4000 mc. frequency range is provided by the


www.americanradiohistory.com

Westlabs Model 24 broadband r.f. amplifier which utilizes a traveling-wave tube. The small-signal gain averages 35 db, and the saturation output power 30 mw. Maximum noise figure is 20 db.

Recently announced by *Westlabs Incorporated*, P. O. Box 1111, Palo Alto, Calif., the Model 24 is completely self-contained, including regulated power supplies and traveling-wave tube focusing structure. It is housed in a case of JAN aircraft equipment dimensions, and is directly usable as either a laboratory tool or a system component.

MICROWAVE CALORIMETER

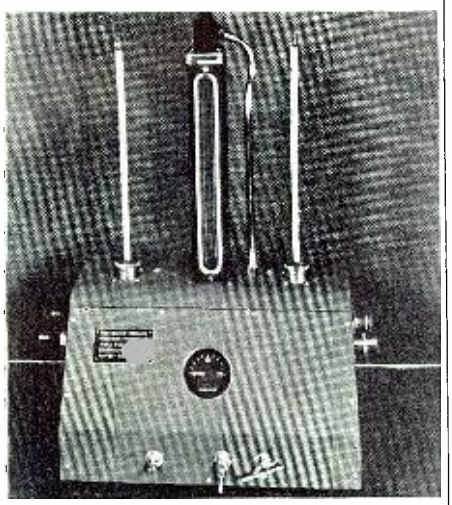Sightmaster of California Company, Santee, Calif., has announced an improved microwave calorimeter and dummy load for the measurement and absorption of microwave power of any



magnitude between 500 and 90,000 mc. In addition to outperforming other known calorimeters in accuracy and power/frequency coverage, the new water tap design permits a selling price approximately a quarter that of previous basic units.

Responding to energy levels from a fractional watt to over 50,000 watts average power, this instrument is capable of measuring or absorbing the power of any radar, u.h.f. TV transmitter, microwave relay or communication device, microwave tube, or energy source. As now designed, it weighs only 20 pounds.


CLOSED CIRCUIT TV CAMERA

Measuring 4¼" wide by 6⅛" high, with an over-all length of 9⅛", the Model 50-A is a new and smaller TV closed circuit camera for use in industry, commerce and education. Just announced by the *Dage Electronics Corporation*, this camera weighs only 7½ pounds.

A total of but seven tubes are required for the Model 50-A, and the con-

(*Continued on page* –39–)

A New, Efficient Crystal Diode Holder

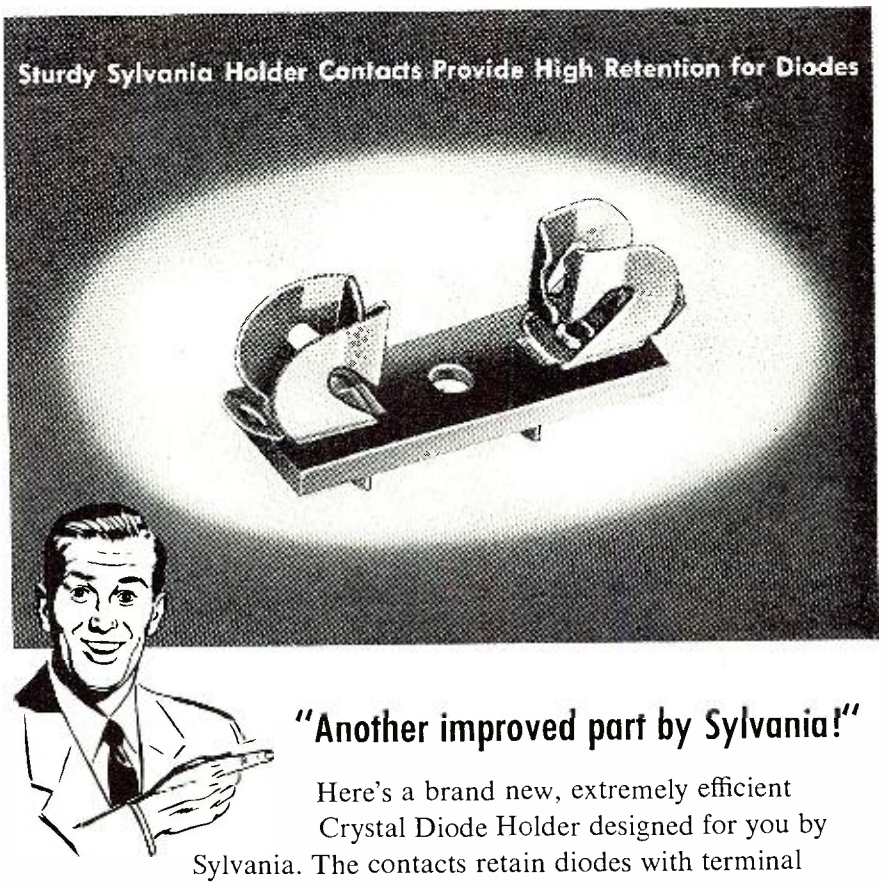

"Another improved part by Sylvania!"

Here's a brand new, extremely efficient Crystal Diode Holder designed for you by Sylvania. The contacts retain diodes with terminal leads ranging from .078 to .125 diameter, with ease of insertion and withdrawal. The centerline of retention is specially located from the surface of the mounting plate to allow installation of large diameter Crystal Diodes. The mounting plate is made of laminated phenolic and the contacts can be furnished in either phosphor bronze or brass with silver plating. Eyelets are made of nickel plated brass. For detailed specification sheets, write to Sylvania today!

SYLVANIA

Sylvania Electric Products Inc., Dept. 4A-3702, 1740 Broadway, New York 19, N. Y.

In Canada: Sylvania Electric (Canada) Ltd., University Tower Bldg., St. Catherine St., Montreal, P. Q.

LIGHTING · RADIO · ELECTRONICS · TELEVISION

www.americanradiohistory.com

NEW LITERATURE

WAVE GUIDE ENGINEERING DATA

Wave guide engineering data and curves are available in a new 20-page booklet which has been published by *Airtron, Inc.* Entitled "Microwave Nomograms and Charts," this booklet represents practical techniques and approaches developed over the years by *Airtron's* engineering staff in designing and using wave guide components such as mixers, duplexers, flexible and rigid wave guides, directional couplers, and allied accessories. It is intended to simplify the day-to-day handling of microwave problems.

Copies may be obtained free of charge by writing directly to *Airtron, Inc.*, Dept. H, Linden, N. J.

MAGNETIC IMPULSE COUNTER

Operating principles and characteristics of the *Kellogg* magnetic impulse counter and typical basic circuits are given in a four-page bulletin issued by the *Kellogg Switchboard and Supply Company*, 79 West Monroe St., Chicago 3, Ill.

The *Kellogg* magnetic impulse counter is a selector switch used to solve many switching or control problems where the intelligence to be registered, stored, and released is supplied in the form of electrical pulses. It has a wide application in the fields of industrial control, computer design, telephone, v.h.f. radio, microwave selective signaling and telemetering.

TUBE CHART

Amperex Electronic Corporation has prepared a chart that shows the rating in power output vs. frequency for *Amperex* power tubes in typical operation. It includes the FCC frequency allocations and associated applications correlated with tube performance.

Coded in color, this comprehensive chart is planned for quick use and easy readability; at a glance, it is possible to find the tube or tubes that will meet the general requirements for practically any r.f. or audio operation. A copy may be obtained free by writing to *Amperex Electronic Corporation*, Hicksville, L. I., N. Y.

ELECTRONIC COMPONENTS

The 1954 edition of the *Alden* Handbook, "Ideas—Techniques—Designs," is packed with new standard components for unitizing electronic equipment. It provides new data and planning sheets on plug-in packages and basic chassis, and describes the latest components for indicating and monitoring the operation of electronic equipment. New models of connectors and interconnecting systems that allow dynamic color-coding for easy circuit tracing have been added.

This booklet is available to manufacturers and designers writing on their respective letterheads to Department HB, *Alden Products Co.*, Brockton, Mass.

CUSTOM-BUILT TV EQUIPMENT

Since no two television stations have the same operating requirements, the equipment needs differ for each installation. Catalog B.30 pictures typical examples of *RCA* custom-built equipment for television, as used by various stations, demonstrating many unique features that may serve as a guide in solving a number of switching and control problems.

A list of basic equipment considerations is also included in this catalog, which is available on request from the Engineering Products Department, *RCA Victor Division*, Camden 2, N. J. Specify Form B.30.

AUDIO AMPLIFIER

Bulletin DB 85-950 describes the new *Westinghouse* Type FG 5 or 10 kw. variable frequency audio amplifier which will amplify 30 to 10,000 cycle signals as much as a million times. Applications are suggested; operation is discussed; design and construction features and complete electrical characteristics are given. For a copy of Bulletin DB 85-950, write to *Westinghouse Electric Corporation*, Box 2099, Pittsburgh 30, Pa.

HYPERBOLIC PROTRACTOR

How to use a hyperbolic protractor is the subject of a 44-page book published by the *International Telephone and Telegraph Corporation*, 67 Broad St., New York 4, N. Y. It is entitled "A Hyperbolic Protractor for Microwave Impedance Measurements and Other Purposes," by G. A. Deschamps, of the *Federal Telecommunication Laboratories*, and includes an actual protractor in its price of $2.50 a copy.

This protractor is used in connection with a projective chart to solve various problems on transmission lines, wave guide junctions, and polarization. The latter part of the book consists of a paper originally given by Mr. Deschamps at the IRE Professional Group Symposium on Microwave Circuitry in 1952 which presents some of the basic properties of this projective chart. The protractor can also be used for the same purpose with the more familiar reflection charts of the Smith or Carter types or with the rectangular impedance plot.

GAGE PRESSURE POTENTIOMETER

Brochure No. 3553, announced by *Bourns Laboratories*, describes the Model 304 miniature gage pressure potentiometer—a sensitive pressure pickup actuated by a miniature Bourdon tube. Photographs illustrate the method of accurately transmitting the movement of the tube to the sliding contact of the wire-wound potentiometer; and diagrams, curves, and charts provide additional technical information.

Write to Dept. NL, *Bourns Laboratories*, 6135 Magnolia Ave., Riverside, Calif., for a copy of this four-page brochure.

ELECTRONIC TEST EQUIPMENT

"Electronic Test Equipment" is the title of a 12-page bulletin just released by *Cal-Tronics Corporation*. In addition to a description of the company, its services and facilities, this bulletin contains eight pages of illustrations and descriptions of various types of test equipment built by *Cal-Tronics*. Equipment covered includes a synchonizer test unit, an electronic control amplifier test unit, a computer systems test unit, and a signal data converter test unit.

Copies of "Electronic Test Equipment" may be had by writing to *Cal-Tronics Corporation*, 11305 Hindry Ave., Los Angeles 45, Calif.

COMMUNITY ANTENNA SYSTEM

Advantages of the *Jerrold* W + K five-channel community antenna system are outlined in a four-page folder issued by the *Jerrold Electronics Corporation*, 26th and Dickinson Sts., Philadelphia 46, Pa. This community system is the first to deliver successfully more than three channels of clear consistent television in an economically practical fashion; the new Model K equipment, which has been added to the original *Jerrold* W system to distribute the two extra channels, is described in detail in the folder.

AUDIO GUIDE

Of special interest to technicians, engineers, designers and servicemen working with audio equipment is the 1954 edition of *Terminal's* "Audio Guide,"

www.americanradiohistory.com

available from *Terminal Radio Corporation*, 85 Cortlandt St., New York 7, N.Y.

The most complete catalog of its kind, this buying guide contains 130 pages of ready reference to high fidelity audio, communications, and public address sound equipment . . . radio and TV tuners, record changers, recorders and recording equipment, amplifiers, speakers, parts, accessories and cabinets.

ANALOG COMPUTERS

George A. Philbrick Researches, Inc., 230 Congress St., Boston 10, Mass., has reprinted a paper entitled "An Introduction to Analog Computers" in the form of a 24-page illustrated booklet; this paper was presented at the Eighth National Instrumentation Conference in Chicago, Ill., last September by Jerry Roedel, Head of the Computer and Electronics Section of the *Pullman-Standard Car Manufacturing Company*.

The history, classification, and precision of computing devices are discussed, with particular emphasis on analog computers, and consideration is given to the basic elements in the operational amplifier type of analog computer. Photographs of typical installations of this type of computer are included in the booklet.

MAGNETIC TAPE SPLICING

General considerations in magnetic tape splicing are discussed in a three-page bulletin now available on request from *Minnesota Mining and Manufacturing Company*, 900 Fauquier St., St. Paul 6, Minn. Included are solutions to such problems as splice weakness, loss of recorded signal due to poor head contact, and adhesive transfer causing sticky layers.

"Sound Talk" Bulletin No. 26, entitled "Splicing Techniques for Magnetic Tape," also contains detailed instructions for properly splicing magnetic tape for audio recording, as well as information on splicing critical recordings used in computer work and instrumentation.

TWO-WAY RADIO

"How to Modernize Your Materials Handling Operations" is the title of a six-page illustrated booklet published by the *General Electric Company* on the use of two-way radio. The booklet relates the ways in which two-way radio can cut costs, improve efficiency, and increase production, and it describes *G-E* equipment now available for a wide variety of applications.

Copies are free on request from the Advertising Inquiry Section, *General Electric Company*, Electronics Park, Syracuse, N. Y.

Looking for **ANSWERS** *on*

ANTENNAS?

GABRIEL, *first source of supply* for most of the nation's manufacturers, offers you these excellent antenna design and manufacturing facilities.



DESIGN

Gabriel design has paced the growth of antenna development. Outstanding are its Parabolic Microwave Antennas for 940, 2000, and 7000 MC bands, and new Gabriel Cosecant UHF Broadcast models featuring null fill-in.


TEST

Gabriel's three major test pattern ranges — an 1130' range, a 2000' range, and 3200' range — are fully equipped with transmitting towers, an array of revolving mounts, and complete pattern recording instruments.



This 16-bay VHF antenna, shown at right, modified for production from prototype design of Federal Telecommunication Laboratories, is typical of Gabriel engineering and manufacturing that can help you.

PRODUCTION

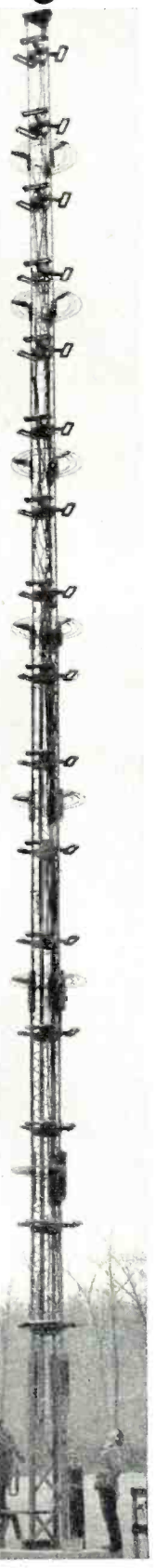


WRITE . . . for your specific requirements, or for bulletins on Gabriel Microwave, UHF and Communication Antennas.

GABRIEL ELECTRONICS DIV.

Formerly Workshop Associates Division

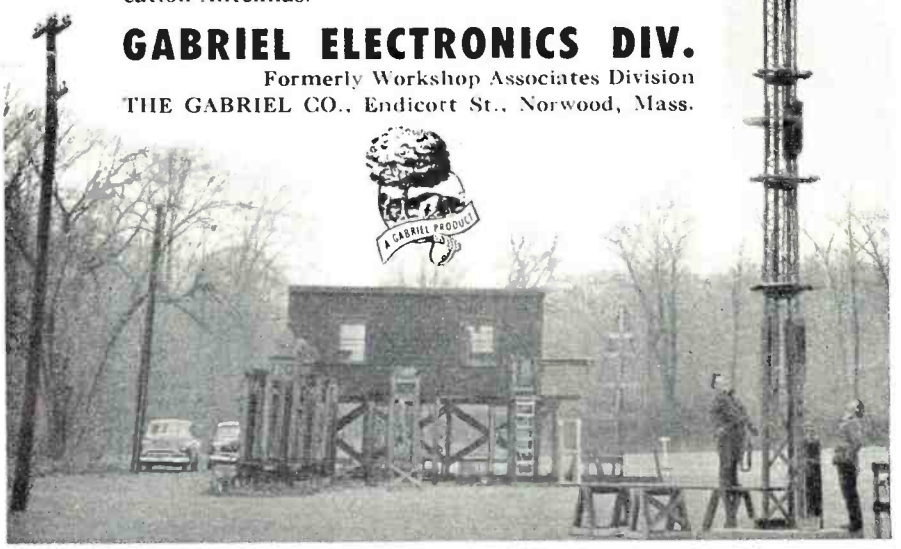THE GABRIEL CO., Endicott St., Norwood, Mass.




www.americanradiohistory.com

NEWS BRIEFS

GERMANIUM PHOTOCELL

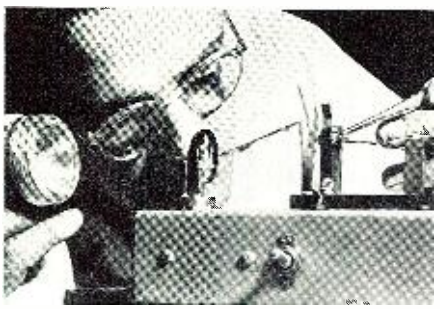Slightly thicker than a pencil lead, and only ⅜" long, the tiny germanium photocell announced by the *General Electric Company*, Schenectady, N. Y., is more sensitive to light than vacuum photo units a hundred times larger. Still in the developmental stage, this cell is so versatile that it can regulate domestic or industrial heating devices



or detect industrial targets for guided missiles. It is shown being tested by Dr. W. C. Dunlap, Jr., the *G-E* Research Laboratory scientist who developed it.

Called a "*p-n* junction photocell," the unit is simple in design: it consists of a metal cartridge housing a glass lens and a germanium wafer in contact with a metallic button of indium, and a whisker links the wafer to an outside lead. Comparatively large power output makes this photocell suitable for operating relays directly to control many production processes, whereas power developed by selenium and vacuum cells has to be amplified before such cells can operate most relays used in industrial controls.

NEWS FROM NARTB

Robert D. Swezey, WDSU-TV, New Orleans, La., has been elected chairman of the NARTB Television Circulation Study Committee. This committee, along with management and research executives of the four TV networks, is conducting a study with regard to a method of measuring the circulation of TV broadcasting in the United States.

The AM Committee of NARTB has expanded its membership to include representatives of radio networks. NBC will be represented by William H. Fineshriber, Jr., and MBS by Earl M. Johnson. Chairman of the AM Committee is G. Richard Shafto, Station WIS, Columbia, S. C.

For the first time, NARTB will be represented on the Accrediting Committee of the American Council on Education for Journalism. Hugh B. Terry, president and general manager of Stations KLZ and KLZ-TV, Denver, Colo., has been appointed by NARTB to serve on the ACEJ Committee.

POWER-TYPE TRANSISTOR

Held in the left hand of Dr. Finn J. Larsen, research director of the *Minneapolis-Honeywell Regulator Company*, Minneapolis, Minn., is a thimble-size transistor which is 100 times more powerful than present commercially available models. It has the same output as the large vacuum tube shown—20 watts, or enough to operate motors, valves, relays and other equipment previously impossible to operate with transistors.


The key to *Minneapolis-Honeywell's* development of this power-type unit was the discovery of an effective means of removing heat from the germanium-alloy junction, the lack of which has hitherto been responsible for the inability of transistors to handle sizable amounts of current. Although the new transistor is not yet in commercial pro-



duction, it has already been incorporated in a prototype aircraft electronic fuel gauge, and may greatly expand the range of transistor uses.

ADAPTABLE ELECTRONIC CHASSIS

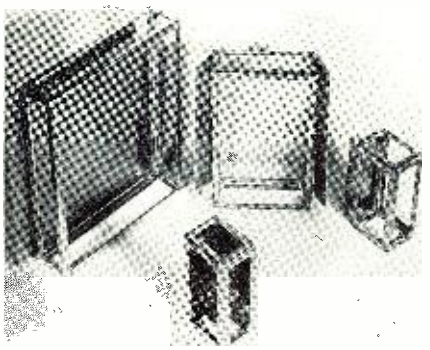In response to the need for a components chassis that would lend itself to varied and changing electronic designs, the National Bureau of Standards has developed a widely adaptable chassis that is both economical and convenient. Its design includes a rectangular frame made of ⅜" x 1/16" steel



angle and sets of flat plates that are fitted to the frame with screws.

Several sizes of the NBS chassis are shown in the photograph. The 3" x 4" x 4" chassis in the foreground illustrates the freedom of accessibility to components in even the smallest model. Other circuits may easily be added by mounting the components on a plate of the proper size and screwing the plate to the frame. For special requirements, plates of a nonconducting material may be used.

ENGINEERS AT IIT

Two additions have been made to the staff of the Armour Research Foundation of Illinois Institute of Technology: Hillard M. Wachowski and Henry F. Schunk have both been appointed as full electrical engineers.

Mr. Wachowski, formerly assistant professor of electrical engineering at Northwestern University, is a specialist in microwaves, field theory, antennas, and electronics. He will work in the communications and radio-frequency applications section of the Foundation's Electrical Engineering Department.

Mr. Schunk, who held the rank of technical engineer at *International Business Machines Corporation*, Poughkeepsie, N. Y., is a specialist in input and output devices for digital computers, and will serve on the Computing Center staff.

SRI EXPANSION

Stanford Research Institute, Palo Alto, Calif., has acquired the facilities of the *Microwave Engineering Co.*, Los Angeles, located at the top of Mount Lee in the Hollywood district. The latter company will henceforth be part of the Engineering Division's Radio Systems Laboratory, and the location will be known as the Mount Lee Laboratory of Stanford Research Institute. Robert Krausz, former vice president and chief

www.americanradiohistory.com

engineer for *Microwave Engineering*, has been appointed to head the new SRI operation.


APPOINTMENTS AT *G-E*

Key appointments in the broadcast equipment unit of the newly formed Commercial Equipment Department in the Electronics Division of *General Electric Company*, Syracuse, N. Y., include those of C. Graydon Lloyd as manager of engineering, Frank P. Barnes as manager of marketing, and Glenn R. Lord as manager of manufacturing.

Mr. Lloyd joined the *Canadian General Electric Company* in 1935, and in 1952 was transferred to the *G-E* Electronics Division where he has been manager of engineering for broadcast equipment. Mr. Barnes, who joined *G-E* at Schenectady in 1937, became sales manager for broadcast equipment in 1950. Mr. Lord has been with *G-E* at Syracuse since 1951, serving in several supervisory manufacturing positions before becoming manager of manufacturing facilities for commercial products.

BATTERY RESEARCH

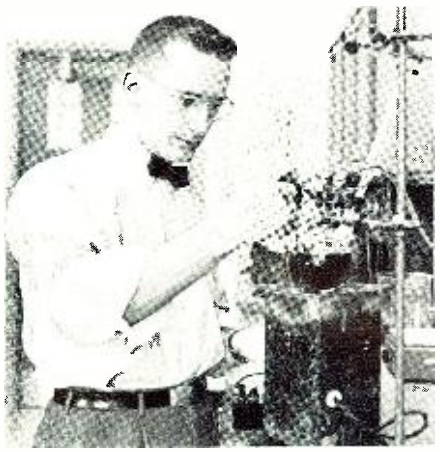Dr. Joseph Varimbi has joined the expanding chemical research group of the *Edison Laboratory* of *Thomas A.*




Edison Inc., West Orange, N. J. His major project will be research in the battery field, in which *Edison* has held leadership from the time the laboratory's founder invented batteries as a source of electrical energy.

Dr. Varimbi received his Ph.D in chemistry from the University of Pennsylvania last June on the basis of his thesis on solutions of alkali metals in methylamine.

DU MONT ENGINEERS

Increased programing and other expanding network activities have resulted in the creation of four additional technical administrative posi-

(*Continued on page* –34–)

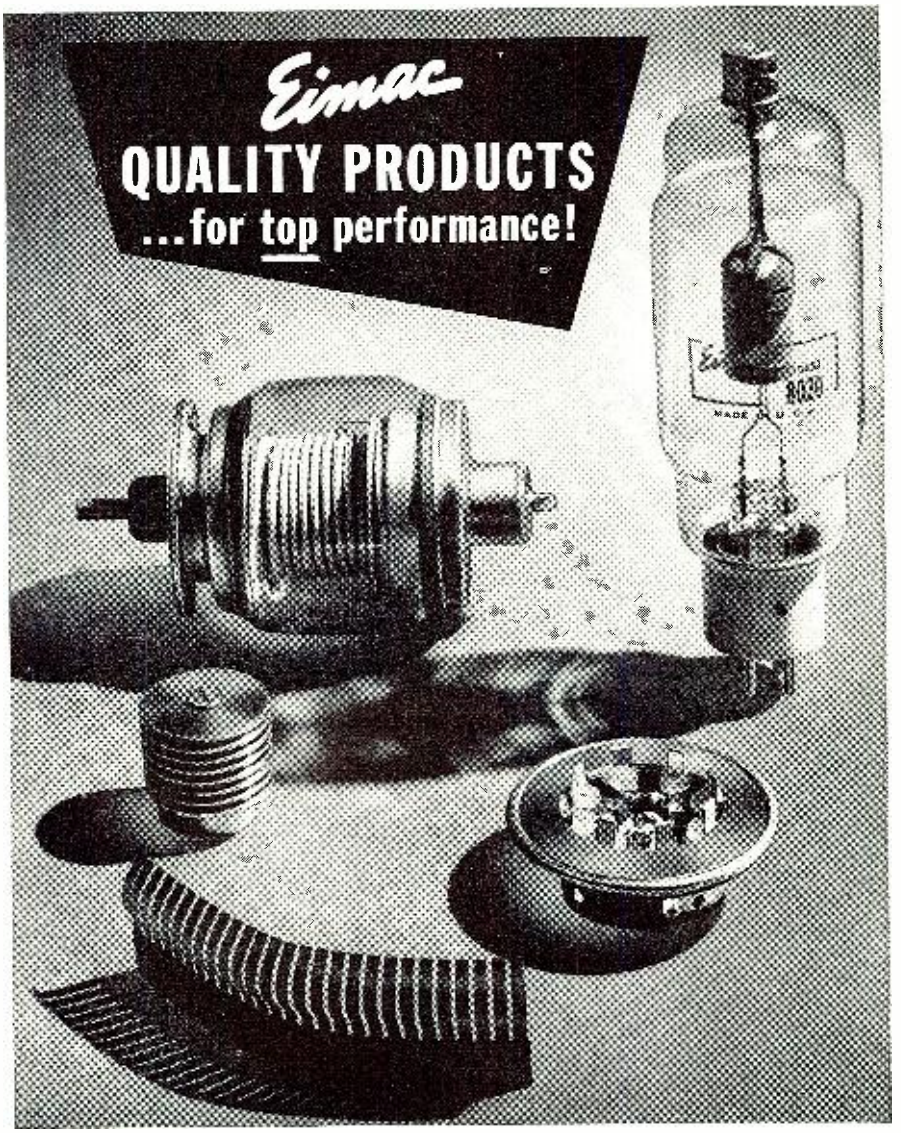

Preformed Contact Finger Stock is an ideal electrical weather stripping around doors of equipment cabinets as well as being excellent for use with VHF and UHF circuitry. Silver plated, it comes in three widths—$\frac{17}{32}$, $\frac{31}{32}$ and $1\frac{7}{16}$ inches.

Variable vacuum capacitors come in three models, are lightweight, compact, eliminate the effects of dust and atmospheric conditions and have low inductance. Also available are eight types of fixed vacuum capacitors.

Air-system sockets, designed for Eimac tube types 4-400A, 4-1000A, 4X150A, and 4X150D, simplify cooling and assure adequate air-flow to various seals. The 4-400A socket can also be used with the 4-125A and 4-250A radial-beam power tetrodes if desired.

HR heat dissipating connectors provide efficient heat transfer from the tube element and glass seal to the air while making electrical connections to plate and grid terminals. Precision machined from dural rod, HR connectors come in ten sizes to fit most of Eimac's internal anode tubes.

High Vacuum Rectifiers come in eight models, are instant heating, have radiation-cooled pyrovac* plates and can be operated in a variety of rectifying and voltage multiplying circuits. Also available are four types of mercury-vapor rectifiers.

* An Eimac trade name.

• For further information write our Application Engineering department

Eimac

EITEL-McCULLOUCH, INC.
SAN BRUNO • CALIFORNIA
Export Agents: Frazar & Hansen, 301 Clay St., San Francisco, California

www.americanradiohistory.com

Personals



JAMES T. CAMPBELL has been appointed district sales engineer manager for Washington, D. C., by the *Standard Electronics Corporation*, Newark, N. J. In addition to his duties with the FCC and consultants in Washington, he will serve this company's customers in Delaware, Maryland, Virginia and West Virginia. Mr. Campbell comes to his new assignment after 14 years with *Trans World Airlines* in radio communications engineering and sales.



DR. P. S. CHRISTALDI is the new manager of the Instrument Division of *Allen B. Du Mont Laboratories, Inc.*, Clifton, N. J. Associated with *Du Mont* since 1938, Dr. Christaldi was made chief engineer of the company in 1941, engineering manager of the Instrument Division in 1947 and assistant manager of this division in 1952. He holds a Ph.D. degree in physics from Rensselaer Polytechnic Institute, and is a Fellow of the Institute of Radio Engineers.



DR. ALFRED N. GOLDSMITH will be presented the Founders Award by the Institute of Radio Engineers in March "for outstanding contributions to the radio engineering profession through wise and courageous leadership in the planning and administration of technical developments which have greatly increased the impact of electronics on the public welfare." Co-founder of the IRE in 1912, Dr. Goldsmith has served as its editor since that time.



JAMES E. KEISTER, with *General Electric Company* since 1935, has just been appointed manager of engineering of the germanium products unit, Commercial Equipment Department of *G-E's* Electronics Division, Syracuse, N. Y. Mr. Keister served in a number of electronics engineering posts at both Schenectady and Syracuse, principally involving radar and TV transmitting equipment; he has been manager of semiconductor engineering since 1952.



FRANK KREMPEL, formerly assistant chief engineer of *Stewart-Warner Electric*, division of *Stewart-Warner Corporation*, Chicago, Ill., is now engineering head of government development and production contracts in the electronics field. He will direct operations of the Engineering Department in design or development work for Armed Forces contracts and in the modification of current military items to meet changing requirements.



DR. JAMES L. THOMAS has been appointed chief of the newly organized Resistance and Reactance Section of the Electricity Division of the National Bureau of Standards, Washington, D. C. With NBS since 1927, Dr. Thomas has made many contributions to the field of electrical measurements; he developed the special type of precision standard used by most standardizing laboratories for maintaining the unit of electrical resistance.

Transistor Control

(*Continued from page* –15–)

rent is plotted positive to the left and the curve shifted to cause the cutoff point to coincide with that of Curve 1, facilitating comparison of the curves. The control circuit a.c. source voltage used was 12.7 volts (r.m.s.), 60 cps.

Curve 3 is the transfer characteristic for the transistor control scheme of Fig. 4B using a 70-ma. d.c. bias current supplied through 3000 ohms.

Curve 4 shows the transfer characteristics of the magnetic amplifier alone under conditions of very high control circuit impedance, plotted to the same abscissa scale as Curve 2.

Comparison of Curves 1, 2, and 3 shows the similarity of performance between the three schemes. Measurements of emitter input power yield an over-all incremental power gain of approximately 22,000 in all cases. Since the response time is one cycle, the over-all figure of merit is about 22,000. Curve 4 indicates the similarity of these characteristics to the high control circuit impedance transfer characteristic of the magnetic amplifier alone.

Performancewise, there is little difference between the three transistor control schemes presented. In terms of apparatus, the d.c. preamplifier in general requires whatever transformers and rectifiers are necessary to provide the proper collector d.c. voltage supply. The second scheme generally requires a transformer to provide the proper control circuit a.c. voltage and the four control circuit rectifiers; since in this scheme maximum output is obtained with zero signal, some sort of signal biasing means may be necessary. The last method requires only the two control circuit rectifiers; to be sure, a bias current is also needed, but this is usually necessary in any case and no special impedance level is dictated. On the basis of equipment, the latter scheme seems to possess some advantage. In the final analysis, however, each method has features which may make it more applicable to the situation at hand.

Conclusion

Three examples of methods of utilizing the unique characteristics of transistors in the control of magnetic amplifiers have been presented which are intended to illustrate several possible types of applications and their salient features and to point out factors to be considered in these applications. No attempt has been made to provide an exhaustive treatment of possible uses of transistors in magnetic amplifier circuitry, nor should it be implied that the examples given represent optimum methods.

www.americanradiohistory.com

In many cases, because of temperature sensitivity and limitations and because of lack of consistency in characteristics of available transistors, the examples given—as well as numerous other possible applications—may be impractical at present. However, with the advent of improved transistors and more thorough investigation of their operation in magnetic amplifier applications, it is expected that the transistor will become an extremely useful magnetic amplifier circuit component.

REFERENCES:

1. *Finzi, L. A., and Pittman, G. F., Jr., "Comparison of Methods of Analysis of Magnetic Amplifiers," Proc. of the National Electronics Conference, Vol. 8, 1952, pp. 144-157.*
2. *Dornhoefer, W. J., "Self-Saturation in Magnetic Amplifiers," A.I.E.E. Transactions, Vol. 68, 1949, pp. 835-50.*
3. *Ramey, R. A., "On the Mechanics of Magnetic Amplifier Operation," A.I.E.E. Transactions, Vol. 70, 1951, pp. 1214-22.*
4. *Lehman, H., "Pre-determination of Control Characteristics of Half-Wave Self-Saturated Magnetic Amplifiers," A.I.E.E. Transactions, Vol. 70, 1951, pp. 2097-2103.*
5. *Ramey, R. A., "On the Control of Magnetic Amplifiers," A.I.E.E. Transactions, Vol. 70, 1951, pp. 2124-28.*

Cast Wave Guides

(Continued from page -11-)


used to get the molten metal into the mold.

The production cycle for Sightmastermolds is governed by three primary factors: (1) temperature used to heat the pattern, (2) pattern temperature, and (3) "dwell time," or the time that the hot pattern is immersed in the sand-resin mix before it is removed. The pattern temperature varies with the time that the pattern remains in and out of a heating oven. If oven temperature is 600° F, loading and unloading time is 30 seconds and oven curing time is two minutes, a constant pattern temperature of about 375° F may result. Thickness of the shell is determined by the "dwell time," which varies in practice between 5 and 30 seconds, depending on the mix used, the desired thickness of the shell, degree of pattern heat, etc. Shell molds are cured in an oven one-half to three minutes before being stored for immediate or eventual use. They may be stockpiled until ready for use.

Optimum formulas and techniques to improve wave guides constructed by this process are being developed with the cooperation of tooling, resin and silica firms. The selection of special clay-free washed sands, the use of correct mesh sand coarse enough to permit each grain to be bonded by plastic resin while fine enough to yield a smooth metal surface, shrinkage tables for conditions of operating practice, metal gating and breathing during solidification to eliminate casting voids, parting agents, core removal procedures, etc., are but some of the improvements which have been made.

better all around...

Precision COIL BOBBINS

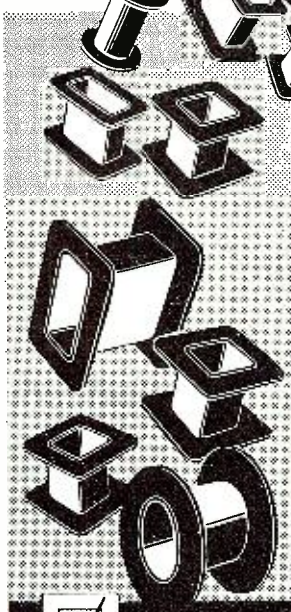

because PRECISION Coil Bobbins are quality controlled you can be sure they'll improve your coils all-around. Every PRECISION Coil Bobbin is precision-engineered to give you:

- Greater Insulation
- Better Heat Dissipation
- Higher Moisture Resistance
- 15 to 20% Greater Strength
- Lighter Weight
- More Winding Space

All at lower unit cost!

PRECISION Coil Bobbins can be designed to your exact specifications . . . any size or shape in dielectric Kraft or fish paper, cellulose acetate, combination or phenol impregnated materials. Flanges are supplied plain or fitted with leads, slots, holes flat, recessed or embossed to fit any mounting.

Send specifications for free sample and ask for new Arbor list of over 2000 sizes.

PRECISION PAPER TUBE CO.

PRECISION

2063 W. Charleston St. Chicago 47, Ill.

Plant No. 2, 79 Chapel St., Hartford, Conn.

Also Mfrs. of PRECISION Paper Tubes

Use it..

For Quick and Complete AUDIO Buying Information



FREE! NEW 1954 Terminal AUDIO CATALOG

Audio Engineers — Technicians — Purchasing Agents will instantly appreciate this ready-reference to everything in Audio . . . the most complete Buying Guide of its kind. Contains over 130 pages packed with sound values of the World's finest High Fidelity Audio, Public Address, and Sound Equipment for communications, industry, and the home . . . Amplifiers, Speakers, FM-AM-TV Tuners, Recorders and Recording Equipment, Record Players and Changers, Packaged Systems. Whether you are a music lover or professional user, the new Audio Guide will save you time and money on all your needs. **Write, or come in for your FREE copy today.**

Radio • Audio • Video • Electronic Equipment

Phone: WOrth 4-3311

Terminal RADIO CORP.

85 Cortlandt St. • New York 7, N. Y.

JOBBERS — EXPERIMENTERS — LABORATORIES

Write or phone WA 5-9642 for your RELAY requirements. Ask for Mr. Greenberg or Mr. Herzog. We have a large variety of standard types of relays and solenoids in over 1100 types.



D.C. SENSITIVE PLATE RELAYS

Allied FID; 8 ma; 1A; 3000 ohm; No. R916 . . 1.50
RBM 23024; 6 ma; 4PST [illegible] o (4A [illegible]); 6500 ohm; No. R802 . . 2.95
Clare Type J (K102); 6 ma; SPDT; 3500 ohm; No. R30 . . 3.50
Cooke Type C; 4 ma; 1A; 6500 ohm; No. R59[illegible] . . 3.50
Clare B 11613 (K101), 2 ma; SPDT; 6500 ohm; No. R588 . . 4.25
RBM 452-1041; 4 ma; 12000 ohm; DPDT; Telephone type; No. R685 . . 4.95
Leach P3; 3 ma; SPDT; 1280 ohm; No. R941 . . 1.25
Sigma 4F8000S; 1 ma; SPDT; 8000 ohm; No. R287 . . 5.95
Sigma 41FS7; 2 ma; SPDT; 10000 ohm; No. R914 . . 2.95
Sigma 41F8000S; 2.5 ma; SPDT; 8.000 ohm; No. R1002 . . 2.95
Sigma 4AH; 4 ma pull in; [illegible] ma hold; SPDT; 2000 ohm; Air Tight Seal; RTMA [illegible] prong Plug Base; No. R444 . . 4.25
Sigma 5RJ2000G; 2.3 ma; SPDT; 2000 ohm; Hermetically Sealed; No. R100[illegible] . . 7.50
Sigma 5RJ5000G; 1.4 ma pull-in; 0.4 ma hold; SPDT; 5000 ohm; Hermetically Sealed; No. R281 . . 6.95
Clare Type G; 4 ma; DPDT; 20,000 ohm; No. R302 . . 3.50
Kurman or Ward Leonard BK35; 0.4 ma; SPDT; 11,000 ohm; No. R277 . . 5.95
Allied B06D40; 30 ma; DPDT; 2380 ohm; No. R305 . . 4.95
Clare 5036; 15 ma; 2A, 1C; 2450 ohm; Hermetically Sealed; No. R440 . . 6.95
Advance K1604; 12½ ma; DPDT; 6500 ohm; No. R532 . . 2.95

ALL MERCHANDISE IS GUARANTEED AND MAY BE RETURNED FOR FULL CREDIT

Our normal inventory includes over 80,000 different items in the electronic, radar and radio fields.

824 CANAL ST. (Near B'way) N. Y. — WA 5-9642

Universal general corp.

www.americanradiohistory.com

Professional Directory

GEORGE P. ADAIR
Engineering Co.
Consulting Engineers
Radio, Television, Communications, Electronics
1610 Eye St., N.W. *EXecutive 3-1230*
Washington 6, D. C.

GABRIEL ELECTRONICS DIVISION
Formerly Workshop Assoc. Div.
THE GABRIEL COMPANY
Specialists in High-Frequency Antennas
Endicott St. Norwood, Mass.
NOrwood 7-3800

Paul W. Klipsch
Professional Engineer
Acoustic development and consulting

Klipsch and Associates
building the authentic
KLIPSCHORN
world's finest sound reproducer

Hope, Arkansas Tel. Hope PRospect 7-3395

FRANK H. McINTOSH
Consulting Radio Engineer
1216 Wyatt Bldg., Washington 5, D. C.
MEtropolitan 8-4477

MEASUREMENTS CORPORATION
Research & Manufacturing Engineers
Harry W. Houck John M. Van Beuren M. A. Honnell
Specialists in the Design and Development of Electronic Test Instruments
BOONTON, N. J.

RATES FOR
PROFESSIONAL CARDS
IN THIS DIRECTORY
Single insertions—$20
6 times—$17.50 per insertion
12 times—$15.00 per insertion

Diode-Capacitor Memory

(*Continued from page* -20-)

While the ends of the diodes are at zero voltage, assume that E is forced to $+2$ volts and held there until the diodes are returned to their normal voltages of -4 and $+4$ volts. Then the capacitor is left with a charge of 2 volts and upon the next squeeze will produce a positive pulse at E, i.e., a "one" will be written. The opposite is equally possible: forcing E negative until the end of the squeeze will write a "zero." Once the diodes have been returned to their normal voltages, the charge on the capacitor will be undisturbed by later changes at E, provided that the magnitude of the voltage at E never exceeds 2 volts. Thus, E can have other pulses on it—either positive or negative—and the charge stored on the capacitor will remain unaffected because both diodes still have backward bias. This is important for organizing many basic storage elements into an efficient memory assembly and is the reason for charging the capacitor to only ± 2 volts while biasing the diodes twice as much.

In this description, the diodes have been assumed to be ideal, having practically infinite forward conductance and practically zero backward conductance. The effect of finite forward conductance will reduce somewhat the output pulse amplitude, and it will determine how long a writing pulse must last to charge the capacitor adequately. The effect of finite backward resistance, however, is critical. Relatively long times will elapse during the holding operation, and even minute currents through the diodes would disturb the capacitor charge. The unit would gradually leak toward a condition of no charge on the capacitor or even a condition in which the sign of the charge on the capacitor is reversed. Thus, the permissible duration of the holding operation is determined by the rate at which the capacitor leaks charge through the back currents of the diodes. Arbitrarily long periods of storage of information are achieved by regeneration; before the capacitor charge can change to a point where there is danger of losing the information, the memory control circuits read the content of each cell and rewrite it.


An amplifier is accordingly needed at point E to sense the polarity of E during the early part of the squeeze period, together with a gate structure which will force E to the desired polarity during the latter part of the squeeze period. For reading or regeneration, E is forced to the same polarity that was read; for writing new information, the polarity to which E is forced is independent of what was read, but is determined by the new information being written. Such a gating amplifier is easy to construct. The amplification required is small since the input is a pulse whose amplitude is of the order of one or two volts. Gating can be accomplished with standard techniques, and the circuit can be constructed using two or three vacuum tubes and about a dozen diodes.

In order to achieve acceptable efficiency, it is essential that the gating amplifier serve many basic storage elements. The buses to the diodes are made common to all the digits of a particular computer word, and a particular gating amplifier serves the same digit on each of many words. Thus, for 256 words of 50 binary digits each, there would be 256 pairs of leads to the diodes and 50 gating amplifiers. For reference to a particular word, the proper pair of buses is squeezed to zero voltage, while all the other pairs are held at their normal value of -4 and $+4$ volts. In this way, each gating amplifier receives a pulse from its particular digit of the selected word, so that the word is available in parallel at the gating amplifiers. These amplifiers can then write into this word or rewrite it without affecting the other words in the memory, since all diodes in other words remain with backward bias. After the squeezing buses on this word are returned to normal, any other word may be referred to in the same way. This is the basis of a fully parallel random-access memory. Regeneration is handled by having the memory control intersperse regeneration cycles—in which the words are read one after the other and rewritten into their former state—between the computer access cycles.

The system described achieves reasonable efficiency for the gating amplifiers but requires a selection circuit capable of squeezing the appropriate pair of buses for a particular word. This could be accomplished by the customary diode matrix, but the usual form of such a matrix requires large standby currents. In this memory, the squeezing buses call for relatively high currents; the resultant diode selection matrix is feasible but not practical because it draws a large amount of standby power. To avoid this, a selection matrix consisting of transformers and diodes is used which has no standby power requirement, although it does require more input drivers than would be necessary with a multidimensional diode matrix. For the "transformer and gate" matrix, developed at the NBS Electronic Computers Laboratory, $2n$ inputs are required to select from n^2 words. The matrix is made up of two sets of crossing buses, X and Y (Fig. 1); at each crossing a diode and transformer primary are connected in

www.americanradiohistory.com

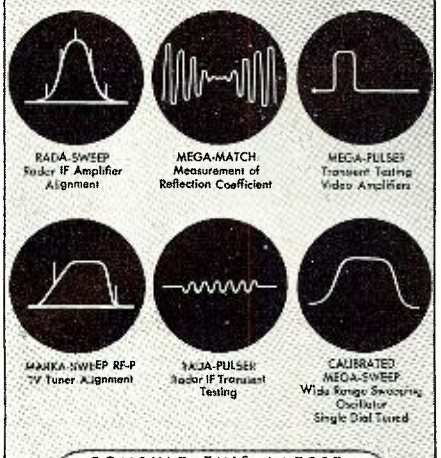NEED INSTRUMENTS TO SOLVE ELECTRONIC P OBLEMS?...



CONSULT THIS LATEST 64-PAGE CATALOG



Write FREE

KAY ELECTRIC CO.

4 MAPLE AVE. PINE BROOK, N. J.

series, with the cathode of the diode tied to the X bus. Normally, all of the X buses are held at $+10$ volts and all the Y buses at -10 volts. This puts backward bias on the diodes associated with each transformer, so that normally no current flows through any transformer. If one X bus is dropped to -10 volts, still no current flows; but if one Y bus is simultaneously raised to $+10$ volts, then just one transformer at the crossing of these two buses will receive a signal, the transformer secondaries connected to the diode-capacitor will squeeze the buses together, and the desired word will be selected.

Complete repetition of the extremely simple basic circuit allows a new type of preventive maintenance. If the majority of failures have a single simple cause (low back resistance of a memory diode), a technique can be devised which will rapidly and thoroughly check for marginal diodes by means of a machine program. This routine loads the memory with a known pattern and then slows down the regeneration rate of the memory while checking for errors. Any cell which fails too soon will have its position typed out, and the cell can be replaced in a matter of seconds. The entire program could be run every hour, if necessary, without seriously detracting from computation time. Other types of marginal checks—such as voltage variation—are possible, but the regeneration check seems to be most direct.

The elements of the diode-capacitor system were tested individually. Then a laboratory model was built containing 16 words of four digits each. Several storage tests were successfully carried out with this model in its final form. On five occasions the unit was left running for three-day periods, and on another occasion for one week. It was found to have the correct information at the end of each period.

Results with the laboratory model have been sufficiently promising to justify the construction of a system more nearly approaching a full memory. The prototype unit is designed for a capacity of 256 words of 45 digits each, but a system capable of storing only 128 words of 8 digits has been built as a start. Because the words have only 8 of the customary 45 digits, it is not now possible to operate SEAC exclusively from this trial memory unit. However, since SEAC can operate from both the acoustic and diode-capacitor memories in integrated fashion, it is feasible to do extensive testing of the new memory by using test routines stored in the acoustic memory. With 40 words connected, a test run was carried out for 12 hours without a single memory malfunction.

PLANS into PLASTICS

PRECISION MACHINING OF ALL THE PLASTICS

including

POLYSTYRENE • COPOLYMER 1422
BUTYRATE • NYLON • TEFLON • KEL-F

PLASTIC FABRICATING

Printloid is equipped for the complete production of a wide variety of consumer and industrial items in any quantity. We work with any plastic material in sheets, rods and tubes. Die-cutting, deep drawing, stamping, forming, finishing, and assembling in our own plant.

PLASTIC PRINTING

LETTERPRESS • SILK SCREEN • HOT STAMPING


for Containers, Displays, Dials, Laminated Charts, Machined Parts, Etc.

Ask for brochure illustrating various plastic products fabricated to specification by Printloid.

Printloid INC. PLASTIC FABRICATION
95 Mercer Street
N. Y. 12, N. Y.

Auricon Hollywood

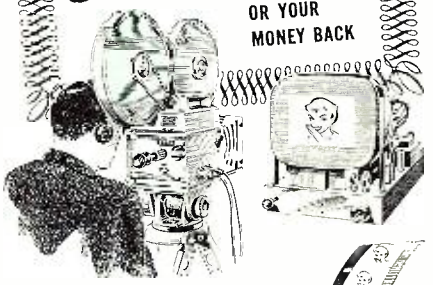KINESCOPE RECORDING with Guaranteed Results! OR YOUR MONEY BACK



NOW, A DUAL-PURPOSE "SUPER 1200" CAMERA with TeleVision-Transcription "TV-T" Shutter...



...designed for Kinescope Recording...and also shoots regular Live Action 16 mm Sound-On-Film Talking Pictures with no Camera modification! The "Super 1200" Camera with "TV-T" Shutter (Pat. Appl'd. for 1949) can Kinescope Record a 30 minute continuous show using 1200 foot film magazines. Write today for information and prices.

USE AURICON "TV-T" KINESCOPES FOR:

★ DELAYED RE-BROADCASTING
★ SPONSOR PRESENTATIONS
★ COMPETITION CHECKS
★ PILOT KINESCOPES
★ SHOW-CASE FILMS
★ "HOT KINES"
★ AIR CHECKS

Auricon 16 mm Sound-On-Film Cameras are sold with a 30-day money-back guarantee. You must be satisfied!

Auricon 50 ft. Kinescope "TV-T" Demonstration Films are available on loan to TV Stations and Film Producers. Please request on your letterhead.

Auricon Hollywood

BERNDT-BACH, INC.

7349 Beverly Blvd., Los Angeles 36, Calif.

MANUFACTURERS OF SOUND-ON-FILM RECORDING EQUIPMENT SINCE 1931

www.americanradiohistory.com

Error Voltage Detector

(*Continued from page* –12–)

put and output circuits is essential, since a small leak from the r.f. source will greatly reduce the sensitivity. Adequate shielding is provided by milling the main body of the transducer from a block of aluminum. A solid partition between the milled-out cavities reduces r.f. leakage to a minimum, and thick walls furnish a heat sink for the two germanium diodes. Filters used in the circuit are well protected from stray fields of the bridge circuit, making it possible to achieve an unusually good null balance and thus insuring high sensitivity.

The transducer is not limited to a 30-mc. carrier frequency. The general principle is readily adaptable to the use of a u.h.f. carrier and will extend the bandwidth of the instrument if desired. If less bandwidth is required, a lower frequency signal may be utilized with consequent economy of construction.

Use of an r.f. carrier in combination with the transducer containing only passive elements makes multichannel operation unusually attractive with its complete freedom from switching transients. One possible practical scheme involves a rotating r.f. link coupling between a number of transducers and a single amplifier. All moving contacts are avoided, and it is merely necessary to sample synchronously the amplifier output coincident with the positioning of the link coupling. Moreover, this method of multichannel sampling permits the transducer units to be placed near the sources of the signals to be amplified. It is quite practical then to provide coaxial cable connections from the numerous units to a common point where the r.f. commutation into the amplifier is accomplished.

Bridge Transistor Tester

(*Continued from page* –7–)

It will be apparent, therefore, that the measurement of transistor parameters becomes a very simple and straightforward operation when the Type 561-D bridge is utilized. The range of the bridge, as quoted by the *General Radio Company*, enables the measurement of R_{11} and R_{22} values of from 50 ohms to 20 megohms. The α measurement range is 0.002 to 5000. R_{21} values of 100 ohms to greater than 10 megohms can be detected; and for R_{12}, values of from 10 ohms to 10 megohms may be measured. One restriction for the accurate measurement of both α and R_{21} is that the value of R_{11} must not exceed 1000 ohms. Since a fixed resistance (R_E) of 100,000 ohms has been used to describe the input resistance in both the α and R_{21} tests, an effective value of R_{11} of more than 1000 ohms would introduce an error of greater than 1%. As most point-contact transistors exhibit R_{11} values of 200 to 500 ohms, there is little need for concern.

Accuracy of the bridge as quoted by the *General Radio Co.* is ± 2% for the R_p test position for values of from 10^2 to 10^6 ohms. At lower and higher values, the error increases slightly. The expression $\mu = G_m R_p$ will check to ± 2% when the quantities are all measured by the bridge and when R_p is between 1000 ohms and 1 megohm.

REFERENCES:

1. *Operating Instructions for Type* 561-D *Bridge, General Radio Company, Form* 397-D.
2. *Tuttle, W. N., "Dynamic Measurement of Electron-Tube Coefficients," Proc. I.R.E., Vol.* 21, *June,* 1933, *p.* 844.
3. *Wallace, Jr., R. L., and Raisbeck, G., "Duality as a Guide in Transistor Circuit Design," B.S.T.J., Vol. XXX, April,* 1951, *p.* 381.
4. *Bousquet, A. S., "Transistor Measurements with the Vacuum Tube Bridge," G. R. Experimenter, March,* 1953.

News Briefs

(*Continued from page* –29–)

tions in the Engineering Department of *Du Mont Television Network*, 515 Madison Avenue, New York 22, N. Y. They will be filled from the ranks by men with long experience in the network's technical operations: Michael Stefanik, John Auld, Robert Crossman and Kenneth M. Reichenbach. The four additional positions will enable *Du Mont* to have seven-day-a-week coverage at the top engineering administrative level.

IRE AWARDS

The Vladimir K. Zworykin Television Prize Award for 1954 has been awarded to Mr. Alda V. Bedford, *RCA Laboratories Division*, Princeton, N. J., by the Institute of Radio Engineers "for his contributions to the principle of mixed highs and its application to color television." This award is presented annually to engineers who have made the most important contributions to electronic television.


One of the highest awards in the radio engineering field, the Institute's Morris Liebmann Memorial Prize, was bestowed on Dr. Robert R. Warnecke, Technical Director of *Companie Generale de Telegraphie Sans Fil*, Paris, France, "for his many valuable contributions and scientific advancements in the field of electron tubes, and in particular, the magnetron class of traveling-wave tubes."

Dr. Harold A. Zahl, Director of Research, Signal Corps Engineering Labs., Fort Monmouth, N. J., was named the recipient of the Harry Diamond Memorial Award for 1954 "for his technical contributions, his long service, and his leadership in the U. S. Army Signal Corps research program." This award is given annually to persons in government service for outstanding contributions in the field of electronic research.

In addition, 76 radio engineers and scientists have been named Fellows of

TV-AM-FM SET PRODUCTION

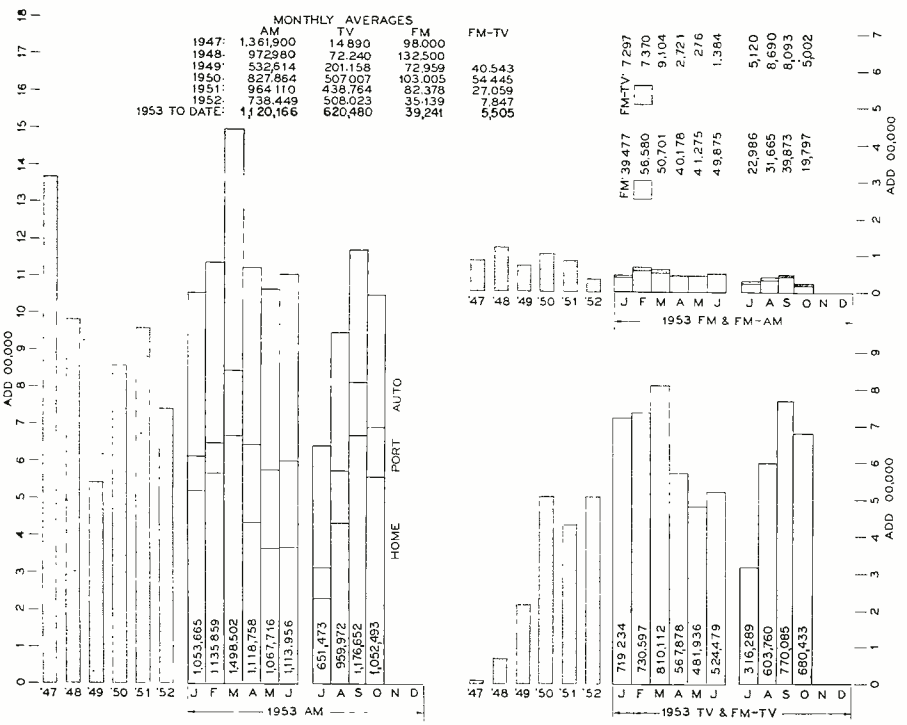Information based on latest reports from RETMA.




www.americanradiohistory.com

the IRE, the grade of Fellow being the highest membership grade offered by the Institute and bestowed only by invitation on those who have made outstanding contributions to radio engineering or allied fields.

Presentation of all of the above awards will be made at the annual banquet of the Institute of Radio Engineers on March 24, held at the Waldorf-Astoria Hotel, New York, N. Y., during the IRE National Convention.

CONVEYER BELT SORTER

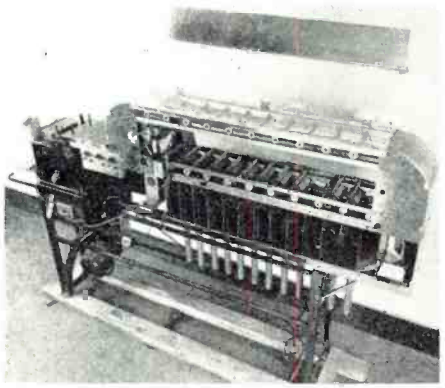An improved machine for sorting physical objects into a large number of categories has recently been developed by the National Bureau of Standards. Although the NBS conveyer belt sorter was built to sort punched cards at the rate of 420 cards per minute, its principle is also applicable to sorting such objects as mail, electrical and mechanical components, checks, invoices, and even farm produce.




The NBS machine consists of five major components: (1) a sensing unit that reads the data-bearing cards and decides where they should go; (2) an addressing device that loads the conveyer with the cards and their corresponding address numbers; (3) a conveyer belt that carries both the card and its address number; (4) a series of recognition devices, actuated by the information-bearing mechanism of the conveyer belt, which operate trip mechanisms to release the cards from the conveyer; and (5) a series of receptacles, or gates to other devices, into which the material borne by the conveyer is sorted.

TI PLANT EXPANSION

Texas Instruments Incorporated, producer of precision electronic, electromechanical and geophysical equipment, has added 90,000 sq. ft. to its main plant at 6000 Lemmon Avenue, Dallas, Texas. Total plant area is now 200,000 sq. ft., as compared to the 37,000 sq. ft. plant of 1946. An all-day "Open House" was held in November to mark the completion of the expansion program.

PREMIER SLIDES INTO FIRST

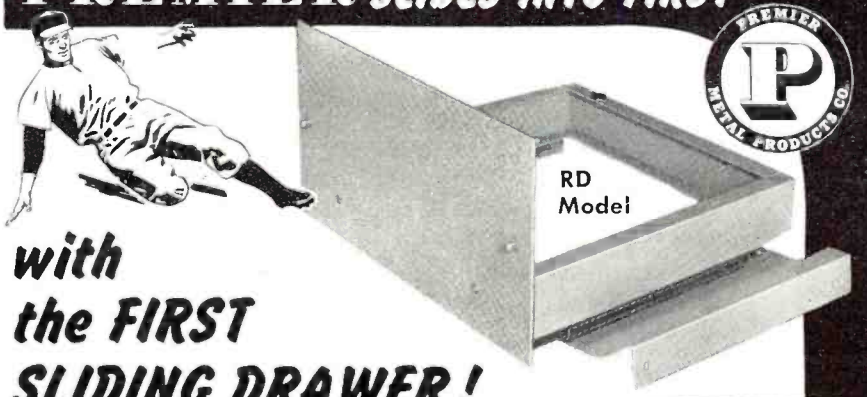

with the FIRST SLIDING DRAWER!

PREMIER pioneers again — with a new SLIDING drawer made to fit standard 19" enclosed relay rack cabinets. You just *slide* your equipment out whenever necessary! Ideal for record changers, telephone work, and other industrial applications.



STAR FEATURES

★ Unit Mounted on Ball Bearing Suspension Slides
★ Drawer Extends 11" and Sustains 40 lbs.
★ Supplied Knocked Down for Easy Assembly
★ Available in 2 Sizes

SEND FOR FREE CATALOG

PREMIER METAL PRODUCTS COMPANY
PRECISION BUILT METAL HOUSINGS
3160 WEBSTER AVENUE • BRONX 67, NEW YORK

INSURE Proven Quality with JONES PLUGS & SOCKETS



P-306-CCT — Plug, S-306-AB — Socket
Cable Clamp in cap. with Angle Brackets.

Series 300 Small Plugs & Sockets for 1001 Uses

Made in 2 to 33 contacts for 45 volts, 5 amps, for cap or panel mounting. Higher ratings where circuits permit. All plugs and sockets polarized. Knife switch socket contacts phosphor bronze, cadmium plated. Engage both sides of flat plug — double contact area. Bar type plug contacts hard brass cadmium plated. Body molded bakelite.

Get full details in Catalog 18. Complete Jones line of Electrical Connecting Devices, Plugs, Sockets, Terminal Strips. Write today.

Howard B. Jones Division
Cinch Manufacturing Corporation
CHICAGO 24, ILLINOIS
Subsidiary of United-Carr Fastener Corp.

HICKOK
Model 650C



for Color TV

An absolute necessity for accurate color receiver adjustments.
• FOCUS • CONVERGENCE
• CENTERING OF INDIVIDUAL BEAMS
• LINEARITY
• ASPECT RATIO
• PURITY YOKE
• DYNAMIC CONVERGENCE
Write for technical details . . .

THE HICKOK ELECTRICAL INSTRUMENT CO.
10534 DUPONT AVE. CLEVELAND 8, O.

www.americanradiohistory.com

Power Line Carrier

(*Continued from page –9–*)

each location. In general, the following procedures are adhered to.

Voice channels are located in the frequency band of 70 to 150 kc., and are spaced ± 10 kc. apart. However, FM transmitters can operate at the same frequency at one location provided that they are coupled to the transmission line through separate couplers. Second harmonics can be serious if common coupling is employed. This condition is somewhat nullified because power amplifiers are now designed so that the second harmonic is 40 db down. The losses through the coupling capacitor and line tuning unit will increase this figure to approximately 50 db.

Telemetering is normally applied to frequencies above 150 kc., with protective relaying of the transmission lines below 70 kc. The general principles involving frequency allocation are flexible, however, and will depend largely on the type of equipment and conditions prevailing at the terminal location.

Impedance and Attenuation

Figure 1 illustrates the equipment line-up for impedance and attenuation tests. Modifications may be made, depending upon circumstances. Tests are performed on energized or de-energized lines. Measurements are conducted by voltage-current or substitution methods. An attempt was made to use an impedance-angle meter, but owing to extraneous voltage pickup, it was set aside.

Typical impedance values for a 100-mile single-circuit transmission line are as follows: phase-to-ground at 100 kc., 330 ohms; phase-to-phase, 370 ohms. The attenuation per mile for the same line was: phase-to-ground, 0.14 db; phase-to-phase, 0.10 db. From these values, it can be seen that the phase-to-phase coupling is preferable for long circuits. However, economy will dictate whether the extra gain is desirable.

Carrier Frequency Noise

The transmitting equipment is selected with adequate power output to insure a good signal-to-noise ratio at the receiving end. Noise in a carrier channel originates in the power line itself. Atmospheric noise is of no importance, and occurs only through lightning strokes on or near a transmission line. Normal noise in a transmission line occurs through current leakage over dirty insulators and loose joints, and the level increases during wet or snow weather conditions. Normally, on fair, dry days, noise levels are barely audible on carrier channels.

Noise may be classified into two categories: random and impulse. Random noise covers a continuous frequency band, with all frequencies at equal amplitudes. This type of noise is distinguished by its characteristic steady hissing sound in the output of a receiver. The r.m.s. value of this type of noise is proportional to the square root of the bandwidth of the receiver, i.e., the value of noise power is proportional to the bandwidth. This is true also for the average and peak amplitudes.

Impulse noise is of greater importance in carrier systems, and its effect is determined by the manner in which it is produced. If the pulses are irregular, and well separated, the frequency band is continuous and the noise will depend slightly on frequency. On the other hand, if the pulses are uniform and regularly spaced, the noise band contains well-defined frequency components that may shock the input stage of a receiver into damped oscillation. Power line noise is a combination of these two types of pulses, and their amplitude values set the criterion of a transmission channel.

No definite standards for quiet or noisy lines have been established. However, tests have revealed certain information that is useful. Noise levels at a receiver input will depend on the operating voltage of the circuit (115 or 230 kv.), and on the type of coupling employed. Noise in the carrier band (50 to 200 kc.) on 115-kv. lines is approximately 70 db below 1 mw. on energized and de-energized lines; the figure is somewhat higher on 230-kv. lines. The phase-to-phase noise voltages are less than the phase-to-ground voltages. On de-energized lines, the noise level decreases linearly with frequency; on energized lines, it increases linearly.

CONSTANT-AMPLITUDE OSCILLATOR


A CONSTANT-AMPLITUDE oscillator, developed by N. C. Hekimian of the National Bureau of Standards, provides an r.f. voltage that remains reasonably stable regardless of changes in tube parameters, supply voltage, heater voltage, or load impedance. This device consists essentially of a conventional oscillator with a diode connected across its output terminals. Output stability is provided by a biased control clamper tube sharing the same plate-dropping resistor with the oscillator.

The circuit is designed to maintain the apparent grid-plate gain of the oscillator reasonably steady. Input and output capacitances are held practically constant, and clipping of the output waveform is reduced to very low levels. The moderate amount of clipping that does occur is due only to the diode detector across the oscillator output.

Originally designed as a fixed-frequency local oscillator in a gain-stable receiver, the device utilizes both sides of a 12AT7 twin-triode as the oscillator and clamper tube, respectively, and a 6AL5 diode detector. The grid tank circuit is composed of a fifth overtone crystal (30 mc.), a frequency-shifting trimmer, and a crystal-peaking coil. A coil in the plate circuit of the oscillator section of the 12AT7 is designed to resonate at the crystal frequency.

The clamper tube is initially biased in the region of plate cutoff. After rectification by the diode, the oscillator output is applied as a positive voltage to the grid of the control tube—the other half of the 12AT7. When the oscillator output voltage reaches a sufficiently high level, the clamper begins to draw plate current and causes a reduction of plate voltage. Because the oscillator is connected to the same plate-dropping resistor, it too suffers a reduction of plate supply. Thus, the tendency of the clamper, as the oscillator output voltage increases, is to maintain the final output voltage at a relatively fixed level.

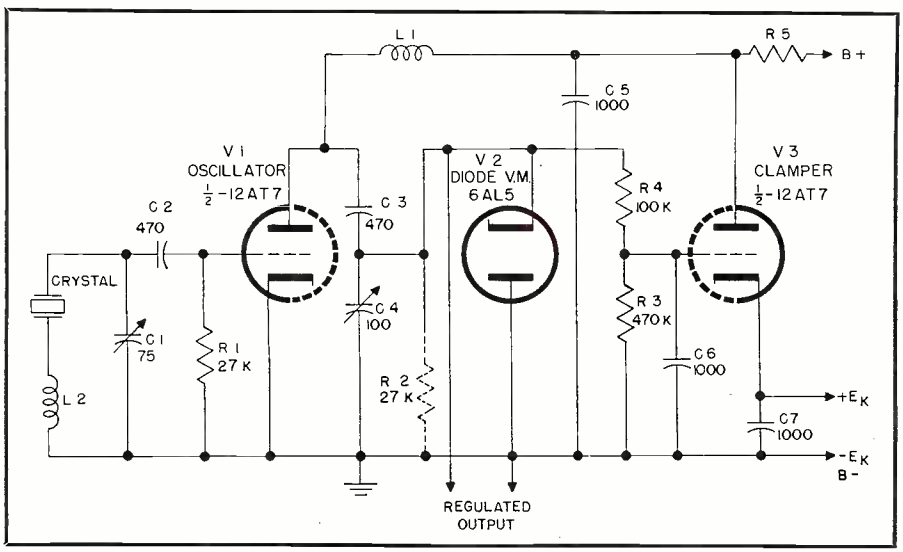Circuit diagram and parts values for the constant-amplitude oscillator.



www.americanradiohistory.com

TECHNICAL BOOKS

"COMPLEX VARIABLE THEORY & TRANSFORM CALCULUS" by N. W. McLachlan, D. Sc. (Engineering). Second Edition. Published by Cambridge University Press, American Branch, 32 East 57th St., New York 22, N. Y. 388 pages. $10.00.

Originally published in 1939 under the title "Complex Variable and Operational Calculus with Technical Applications," this book is intended primarily for the mathematical technologist. It provides a modern treatment of the so-called operational method and illustrates its application to problems in various branches of technology.

The volume is divided into four parts: theory of complex variable; theory of transform calculus; technical applications and examples to be worked out by the reader; appendices and list of references. In this second edition, the chapters on complex variable theory have been rewritten, amplified, and made rigorous enough for all but the pure mathematician. The rest of the book has been revised completely and brought up to date, the number and variety of the examples to be worked out by the reader has been increased, and the reference list has been extended.

"TELEVISION RECEIVER DESIGN—Monograph 2—Flywheel Synchronization of Saw-Tooth Generators" by P. A. Neeteson. Published by *N. V. Philips' Glocilampenfabrieken*, Eindhoven, Holland. Distributed in the United States by *Elsevier Press Inc.*, 155 East 82nd St., New York 28, N. Y. 156 pages. $4.50.

Part VIIIB in the Philips Technical Library series of books on electronic valves, this monograph gives an analysis of the flywheel action of resonant circuits, a study of automatic phase control, and a discussion of practical circuits. It is the second in the series which deals with the subject of television receiver design.

In addition to providing a comprehensive treatment of the principles governing the action of flywheel synchronizing circuits, Part VIIIB includes an elementary discussion which serves as an introduction to the subject for those not fully acquainted with the generation of saw-tooth voltages and currents. A number of practical applications are given, as well as a survey on a number of electronic valves which have been specially developed for use in these saw-tooth generator circuits.

Telecommunications

(Continued from page -18-)

u.h.f. transmission in paths within the earth's atmosphere over this distance becomes a matter of considerable significance from the viewpoint of future international telecommunication in all of its forms.

In addition to the use of high power in the u.h.f. and v.h.f. bands as a means of increasing the range of relay stations in sparsely settled geographic areas outside of the United States where this is necessary or desirable, advantage may also be taken of the principle of "obstacle gain" in mountainous country in order to extend transmission range further.

In this propagation technique, use is made of the knife-edge ridge of a mountain located between transmitting and receiving stations and extending well above the horizon of both the stations (as illustrated in Fig. 1A) to increase the interstation distance greatly or reduce power requirements. By this method, measured "obstacle gains" of 73 db greater than the field strength to be expected over a smooth spherical earth have been reported recently by Dickson, Egli, Herbstreit and Wickizer[5] in the Proceedings of the I.R.E., August, 1953. This transmission principle, which promises to be of considerable aid in applying radio relay methods in the international field, also is important because of the relatively small amount of fading that has been found to exist in v.h.f. communication circuits where the "obstacle-gain" effect has been utilized. In one instance, reported in the paper to which reference has been made, for a period of 30 days recordings of v.h.f. signals received over an obstructed path between two stations 160 miles apart showed that the instantaneous transmission loss varied from its mean value by less than ± 2 db.

By employing the "obstacle-gain" principle and placing relay stations at strategically located mountain sites, transmission range between relay stations may further be increased (as indicated in Fig. 1B). By this combination of techniques, which appears to be of particular significance on international relay routes where it may be desirable or necessary to integrate radar and omnidirectional v.h.f. communication services at selected elevated points to obtain maximum range, the transmission range with a given amount of effective radiated power can be substantially extended as compared with a relay system in which stations are at relatively low elevation (Fig. 1A).


Design Electronic Controls for RELIABILITY IN SERVICE with Alden Components for PLUG-IN UNIT CONSTRUCTION



Be sure your Engineers are working with the Alden Handbook of plug-in unit design. Presents complete line of basic components of tremendous flexibility for adapting your equipment to plug-in construction.


REQUEST FREE 250-PAGE "ALDEN HANDBOOK"

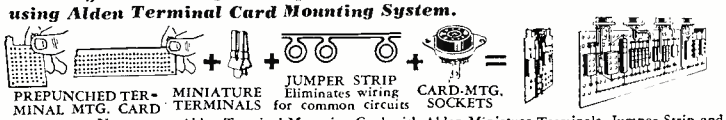1. *Unitize your circuitry in compact vertical planes using Alden Terminal Card Mounting System.*



You can use Alden Terminal Mounting Card with Alden Miniature Terminals, Jumper Strip and Sockets staked to accommodate any circuitry — making complete units ready for housing. Components snap into unique Alden Terminals, are held ready for soldering.

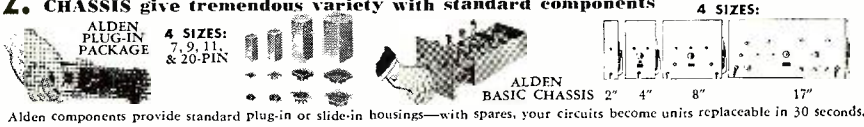
2. To mount this vertical circuitry, ALDEN PLUG-IN PACKAGES AND CHASSIS give tremendous variety with standard components




Alden components provide standard plug-in or slide-in housings—with spares, your circuits become units replaceable in 30 seconds.

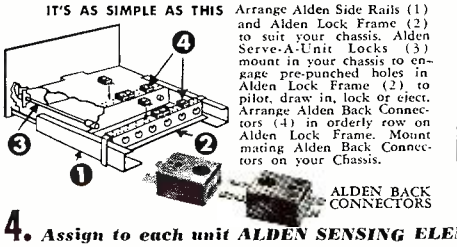3. Give chassis easily traceable interconnects and 30-second replacement with ALDEN SERVE-A-UNIT KIT

IT'S AS SIMPLE AS THIS Arrange Alden Side Rails (1) and Alden Lock Frame (2) to suit your chassis. Alden Serve-A-Unit Locks (3) mount in your chassis to engage pre-punched holes in Alden Lock Frame (2) to pilot, draw in, lock or eject. Arrange Alden Back Connectors (4) in orderly row on Alden Lock Frame. Mount mating Alden Back Connectors on your Chassis.



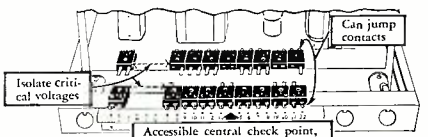GIVING YOU 1) Chassis that plugs in, locks and ejects with half turn of the wrist. 2) leads so beautifully organized, accessible and identified that non-technical personnel can service.



4. *Assign to each unit ALDEN SENSING ELEMENTS — to spot trouble instantly:*



2145 N. Main St., Brockton 64, Mass.

ALDEN PRODUCTS CO.

From Alden's Line of Ready-made Components for Unitized Plug-in Unit Construction.

www.americanradiohistory.com

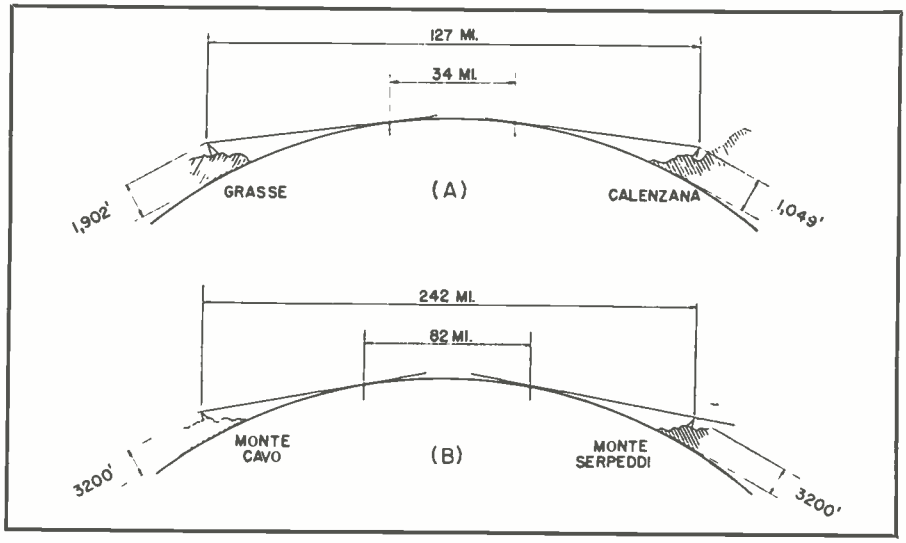


Fig. 2. Profile of v.h.f. relays using transmission paths beyond radio horizon.

Operational Data

In order to provide evidence of the practicability of wide-band v.h.f. transmitting systems now in operation over superoptical paths, data has been assembled as shown in Tables 1 and 2. Referring to Table 1 and Fig. 2A, the wide-band v.h.f. system between Grasse, France, and Calenzana, Corsica, utilizing an over-water transmission path of 127 miles between stations (as shown in Fig. 2A) provides 24 carrier telephone channels in each direction, utilizing two r.f. carrier frequencies. Employing 100-watt transmitters at each end of the circuit, with effective antenna gain of 10 db at operating frequencies of 97 and 107 mc. at the two stations—which are located at elevations of 1902 feet and 1049 feet above sea level, it is reported that measured signal-to-noise ratio in the telephone channels is about 60 db under normal operating conditions[6]. It is stated that fading limits are such that they can be accommodated by the equipment and do not present an operational problem.

Another v.h.f. wide-band system now operating between Mt. Cavo, Italy, and Mt. Serpeddi, Sardinia (shown in Fig. 2B), employs an over-water path of 242 miles between stations which are located at elevations of approximately 3200 feet at each end of the circuit. It is stated that the system accommodates 48 carrier telephone channels in each direction, and provides a signal-to-noise ratio in excess of 50 db. It is understood that transmitting equipment has a power output rating of approximately 500 watts, with antenna gain of about 20 db. Operation is reported to be satisfactory.

In addition to the data based on experience with operation of these two wide-band v.h.f. systems over superoptical distances, reports on long-range transmission of television signals over distances of 250 miles have been received from Texas (as summarized in Table 2). The reports of consistent reception of KGUL-TV, Galveston, at Brownsville, Texas, for a period of 11 days during the initial operating period of the station are significant, as the transmission path in this instance is predominantly over water. An effective radiated power of 235 kw. was employed at the transmitting station, at a video frequency of 199.25 mc. Standard television broadcast receivers were employed throughout the Brownsville area in receiving the programs from Galveston. Quality of the television image and sound was reported to be comparable to that of a local station at Matamoros, Mexico.

In field studies of long-range v.h.f. transmission conducted by *Unitel, Inc.*, additional data has been assembled (as shown in Table 2) to indicate further that signal intensities adequate for reception of television images with commercial television broadcast receivers have been observed at points located at distances up to 330 miles from the transmitter. No multipath effect was noted at these superoptical distances, and in each case a directional antenna —positioned toward the horizon in the direction of the transmitter—was employed at the receiving point. These two factors indicate that the propagation path was predominantly within the earth's atmosphere, and that the signals arrived at the receiver by normal atmospheric refraction and—to a varying degree, dependent on the terrain—by diffraction caused by obstacles in the transmission path. On v.h.f. transmission paths over water or over land up to distances of 300 miles, it would appear that problems due to multipath effects should be minor compared with those experienced at lower frequencies in transmission systems in which dependence is placed on reflection of wave energy from the ionosphere.



REFERENCES:

1. *Chambers, G. R., Herbstreit, J. W., and Norton, K. A., "Preliminary Report on Propagation Measurements from 92-1046 mc at Cheyenne Mountain, Colorado," National Bureau of Standards Report No. 1826, July 23, 1952.*
2. *Fine, H., and Higgins, F. V., "Long Distance Tropospheric Propagation in the Ultra High Frequency Band 288-700," Federal Communications Commission T.R.R. Report No. 2.4.10, October 13, 1950.*
3. *Gerks, Irvin H., "Propagation at 412 megacycles from a High-Power Transmitter." Proc. I.R.E., Vol. 39, No. 11, November, 1951, pp. 1374-1382.*
4. *Bullington, Kenneth, "Radio Transmission Beyond the Horizon in the 40 to 4,000 mc Band," Proc. I.R.E., Vol. 41, No. 8, January, 1953, pp. 132-135.*
5. *Dickson, F. H., Egli, J. J., Herbstreit, J. W., Wickizer, G. W., "Large Reductions of VHF Transmission Loss and Fading by the Presence of a Mountain Obstacle in Beyond-Line-of-Sight Paths," Proc. I.R.E., Vol. 41, No. 8, August, 1953, pp. 967-969.*
6. *Rivère, P., "La Liaison Radiotéléphonique Multiplex Continent-Corse," Annales de Radioelectricite, Vol. III, No. 13, July, 1948.*

(To be continued)

CALENDAR of Coming Events

JANUARY 27—IRE - IAS - ION - RTCA Conference on Electronics in Aviation, Hotel Astor, New York, N. Y.

FEBRUARY 4-6—Sixth Southwestern Conference and Electronics Show, Tulsa, Okla.

FEBRUARY 4-6—"1954 Audio Fair—Los Angeles," Alexandria Hotel, Los Angeles, Calif.

MARCH 22-25—Radio Engineering Show and IRE National Convention, Kingsbridge Armory and Waldorf-Astoria Hotel, New York, N. Y.

APRIL 24—Annual Spring Technical Conference of the Cincinnati Section, IRE, Engineering Societies Bldg., Cincinnati, Ohio.

MAY 3-7—Society of Motion Picture and Television Engineers, 75th Annual Convention, Hotel Statler, Washington, D. C.

www.americanradiohistory.com


New Products

(*Continued from page* -25-)

servative design and small number of components provide for a minimum of maintenance. Only two controls are required, plus the "on-off" switch. For full details, specifications, and application information, write *Dage Electronics Corporation*, 69 North 2nd St., Beech Grove, Ind.

REMOTE CONTROL SYSTEM

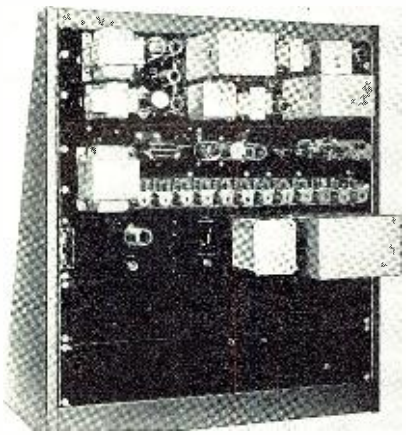Equipment for the remote control of transmitters and receivers used for air-ground communications has been introduced by the *Hammarlund Manufacturing Co., Inc.*, 460 West 34th St.,



New York 1, N. Y. Using tones in the a.f. spectrum and eliminating the need for d.c. circuitry, the remote control system is intended for installation both at airports and along the air routes.

The system requires only a single telephone line having conventional voice characteristics to carry all the standard operations needed for rapid switching between transmitter and receiver, and for switching between equipment groups to cover the various frequency channels. A high frequency radio signal or a microwave link are equally suitable as transmission media.

CORRECTION NOTICE

There were two omissions in the circuit diagram, Fig. 2, of the article entitled "Constant-Output Broadcast Amplifier" which appeared in the November, 1953, issue. There should be a connection from the junction of C_{15} and R_{16} to the bottom end of R_{19}, and from the junction of C_{19} and R_{18} to the bottom end of R_{20}.

PHOTO CREDITS

PAGE	CREDIT
-5-	Sylvania Elec. Prod. Inc.
-9- (top & ctr.)	General Electric Co.
-10-, -11-	Sightmaster of Calif. Co.
-12-, -20-	Nat. Bureau of Standards

Multiple telephone circuits are no longer necessary.

POWER METER

A new type of power meter is available from *Polarad Electronics Corporation* which measures r.m.s. power over the d.c. through X-band frequency range without the need for frequency-limited bolometer mounts. Incorporating a power sensitive element that does not utilize a hot wire barretter or other delicate components, this instrument can withstand 150% overload without burnout or other ill effects.

The *Polarad* power meter is completely self-contained as it employs a single power probe for all frequencies. One terminal of the probe is connected permanently to the meter, while the other terminal is fastened directly to the equipment under test, thus avoiding the errors involved in the use of r.f. connecting cables. For complete information, write to *Polarad Electronics Corporation*, 100 Metropolitan Avenue, Brooklyn 11, N. Y.


TAPPED DELAY LINES

Excellent transient response is featured in the wideband tapped delay lines introduced by *Advance Electronics Co., Inc.*, P. O. Box 394, Passaic, N. J. In addition, light weight, small size, and hermetically sealed construction make these delay lines particularly suitable for use in electronic circuits. They are available in six different types, with various time delays.

A unit of tapped delay line consists of ten sections of *m*-derived networks, and a capacitor with one-half the normal shunted capacity is connected at each end of a network. Each section is designed to give linear phase shift beyond 70% of the cutoff frequency, and to give a frequency response curve approaching Gaussian in shape. Thus, both the rise time and overshoot of the tapped delay lines are much smaller than any other lines having equal time delay.

"MONITRAN"

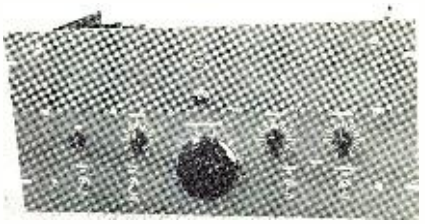The "Monitran," a low-powered r.f. TV transmitter designed to meet broadcasting station monitoring needs, is



now available from the Broadcast Equipment Section of the Engineering Products Department, *RCA Victor Division*, Camden, N. J. Consisting of a 12-channel crystal-controlled oscillator, frequency multiplier, and amplifier turret, the "Monitran" develops both a picture and a sound carrier on any one of the v.h.f. channels.

Several units can be employed simultaneously on different channels to provide a selection of signals at TV monitor receivers by tying their outputs together with an inexpensive resistor matching network.

ZOPHAR

WAXES

COMPOUNDS

Zophar waxes, resins and compounds to impregnate, dip, seal, embed, or pot, electronic and electrical equipment or components of all types; radio, television, etc.

Cold flows from 100°F. to 285°F.

Special waxes non-cracking at —76°F.

Compounds meeting Government specifications, plain or fungus resistant.

Let us help you with your engineering problems.

ZOPHAR MILLS, INC.
112-130 26th Street,
Brooklyn 32, N. Y.

www.americanradiohistory.com


HELICAL ANTENNA DESIGN

By

JOSEPH SODARO

Nomograph for determining the optimum dimensions of a six-turn helical antenna at various frequencies.

Fig. 1. The nomograph. Symbols are identified in Fig. 2.

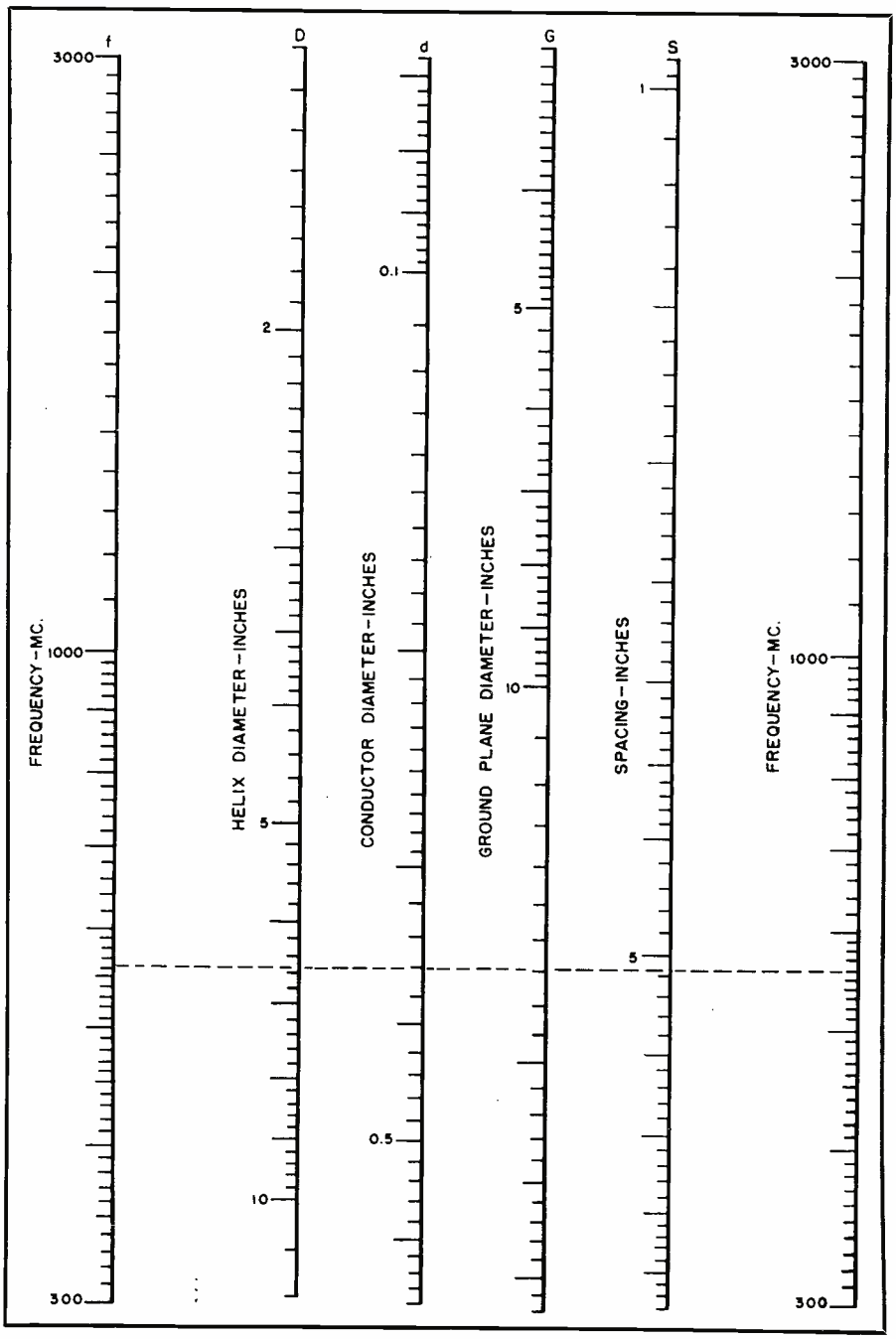

A HELICAL ANTENNA can be used with vertically, horizontally, or circularly polarized radiation. In some cases, it covers a frequency range as high as 2 to 1, with nearly maximum gain throughout the entire range[1]. More than 10-db gain has been measured with this type of antenna[2]. It is well suited for the u.h.f. TV band as well as for v.h.f. and s.h.f. regions.

Basic construction of a helical antenna is shown in Fig. 2. Dimensions to be determined include the helix diameter D, spacing between turns S, conductor diameter d, distance to the first turn g, over-all length l, and ground plane diameter G.

Investigation has shown that an optimum helix consists of six turns with a winding pitch of 14 degrees[1]. Furthermore, a helix circumference of the order of one wavelength is required. Dimensions for this type of helical antenna can be obtained from the nomograph shown in Fig. 1. To use this nomograph, the center operating frequency is located on both f scales and a straightedge or ruler placed through these two points. Dimensions D, d, G, and S are read at the intersection of the straightedge with the corresponding scales. The value of g is $S/2$, while the value of l is $6S + g$.


For example, assume that a u.h.f. antenna is to be designed with the center frequency at 560 mc. The 560-mc. point should be located on both f scales and a straightedge placed through these points. Dimensions are then read at the respective intersections as follows: $D = 6.55''$, $d = 0.362''$, $G = 16.8''$, and $S = 5.13''$. The value of g is $S/2$, or $2.57''$, while the over-all helix length is $6 \times 5.13'' + 2.57''$, or $33.4''$.

The frequency range can be extended by multiplying or dividing the f scales by 10; the opposite operation is performed on the answer scales.

REFERENCES:

1. *Kraus, J. D., "A Helix Theorem," Proc. IRE, May,* 1951, *p.* 563.
2. *Kraus, J. D., "Helical Beam Antennas for Wide-Band Applications," Proc. IRE, Oct.,* 1948, *pp.* 1236-1242.

Fig. 2. Identification of symbols.

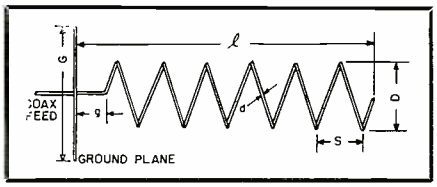

www.americanradiohistory.com


The Best Paying Jobs in


TELEVISION
RADIO-ELECTRONICS


go to the Well Trained Men -- the CTI GRADUATES!


TV cameraman


Radio – TV serviceman

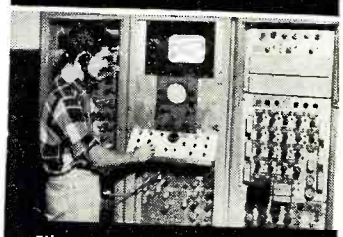
Film camera control technician

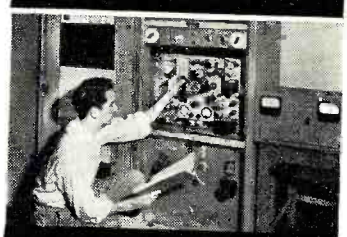
Radio transmitter engineer

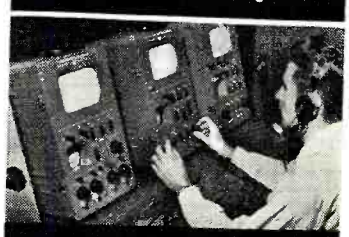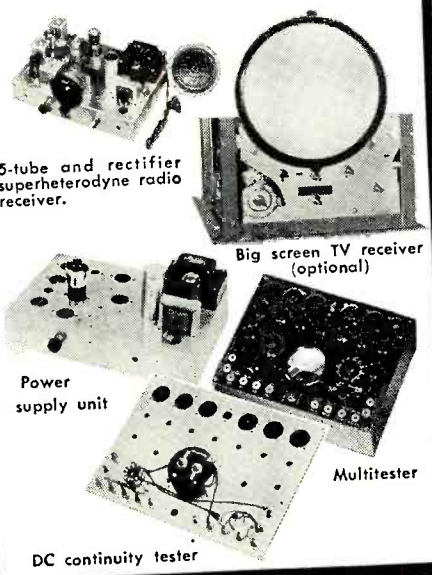

TV studio technician

Now CTI offers you *MASTER TRAINING* in Electronics, Radio and Television – a combination extension-resident program ACCREDITED by a nationally recognized accrediting agency.

You Learn By Doing — Earn As You Progress!

CTI's MASTER TRAINING gives you everything you need for a good-paying job in America's fastest-growing industry! You get over 200 valuable pieces of electronic equipment which you use to perform 100 practical, educational experiments. THIS EQUIPMENT IS YOURS TO KEEP! It isn't make-believe, mock equipment . . . it's genuine commercial apparatus which you can use to set up a PROFIT-MAKING HOME WORKSHOP. *Earn spare-time money while you learn!* Many CTI students, after a few weeks, earn up to $25 or more a week repairing and servicing neighbors' radio and TV receivers! Your earnings can pay for your entire training!

This equipment - and more - - is yours to keep!



Test your aptitude

We will send you, FREE, a self-evaluation aptitude guide which will tell you whether you are cut out for this exciting, big-paying profession. Mail coupon at once!

Thousands of highly paid career jobs must be filled in the ever-expanding Electronics Industry. And CTI graduates—men who have sound, thorough training in TV-Radio-Electronics—are the men who fill these important positions!

CTI Training Can Lead to These Jobs!

TV cameraman, broadcast engineer (AM-FM-TV), manufacturing technician, radio-TV serviceman, transmitter engineer, TV studio technician, recording technician, maintenance technician and many, many more!

Let CTI Training Prove Its Worth

With MASTER TRAINING in Electronics-Radio-Television, CTI gives you a PROGRESSIVE TRAINING PLAN. Every CTI lesson you complete . . . every fascinating home-laboratory experiment you perform . . . brings you closer to the Electronics job you want. You PROGRESS from one section to another, and every section you complete qualifies you for a better job, higher earnings. You have something to show—more knowledge of Electronics, more practical skill, greater job qualifications—for every hour you invest in CTI MASTER TRAINING!

- **Approved for Veterans and Non-Veterans**
- **An Approved Technical Institute Offering Accredited Electronic Curricula**

Get in on the Ground Floor!

Don't deny yourself the good pay, the security, the prestige connected with this fascinating industry. The sooner you act, the sooner you can enjoy all benefits of CTI training.

Important!

Ask for information on CTI's accredited resident program leading to Associate of Science (A.S.) Degree. Radio and Electronics training through home study only also available.

CTI — RADIO TELEVISION ELECTRONICS AIRLINES — CENTRAL TECHNICAL INSTITUTE

FREE – Official monograph on opportunities in Electronics; FREE: "The Electronics Technician" brochure which includes aptitude guide.

USE THIS COUPON To Insure Your Future!

Central Technical Institute
formerly Central Radio & TV Schools
Att. Electronics Division
1644 Wyandotte St.
Kansas City, Mo.

Rush FREE official monograph, aptitude guide and brochure. I understand this places me under no obligation.

Name_____ Age____


Address_____

City_____ State_____

I (am, am not) a Korean Veteran.

www.americanradiohistory.com

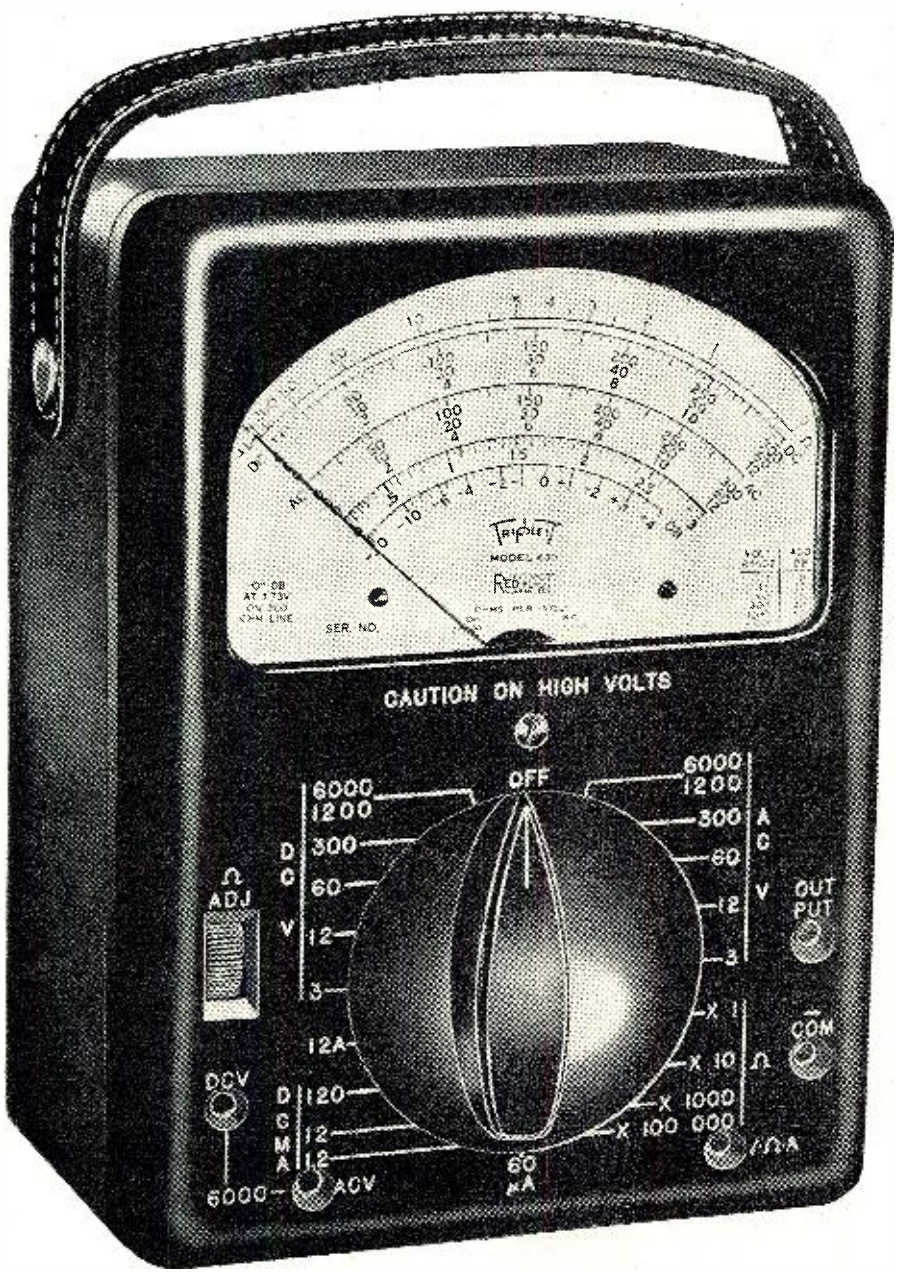TRIPLETT 630 Volt-Ohm-Mil-Ammeter "speaks" for itself in any company



TRIPLETT 630 Volt - Ohm - Mil - Ammeter has many significant advantages and features that make it stand distinctly apart from similar instruments in its price class. Actually in components, in engineering, in minutely accurate performance, Triplett 630 closely approaches laboratory standards.

Since the scales of any VOM comprise the means by which it makes its multiple services most valuable, the legibility and easy-read-ability are of prime importance. Triplett engineers have created in Triplett 630 the longest scales available in this size tester. (The upper arc by actual measurement is four and three-eighth inches.)

This long-scale factor accounts for the ease with which precise readings are easily made. Further legibility is gained by use of black and red scale markings. D.C. and D.B. are black and white. A.C. and Ohm markings are red on white. Ohms from one hundred million to one-tenth ohm mark the range of this amazing scale. On low ohms, center scale reading is 4.5 ohms.

The Single Switch

Futher indication of the practical skill and engineering "know-how" behind Triplett 630 is the Single Switch. Its simplicity of operation assures no burn-outs thru momentary memory lapses. There is instant switching to desired circuit thru a single 2½" knob flush with the face panel. The molded switch itself embodies the most advanced engineering practices. Fully enclosed, the silvered contacts are kept permanently clean. Its rugged construction means stronger performance and longer life.

These two factors are but samples of the many ways in which on-the-job needs have been anticipated and provided for in a beautiful streamlined tester. It provides A.D-D.C. Volts, D.C. Micro-amperes, Milliamperes, Amperes, Ohms, Megohms, Decibel and Out Put readings in a no-short design embodying interior construction with all direct connections; no harness cabling. Its fool-proof unit switch construction houses precision resistors in insulated recesses in direct connection with switch contacts.

Study the following Ranges and descriptions and compare them point by point with *any* similar instrument for conclusive proof that Triplett 630 "speaks" for itself in *any* company.

Ranges

D.C. Volts: 0-3-12-60-300-1200—at 20,000 Ohms/Volt (For Greater Accuracy on TV and other High Resistance Circuits.)
A.C. Volts: 0-3-12-60-300-1200-6000—at 5,000 Ohms/Volt (For Greater Accuracy in Audio and other High Impedance A.C. Circuits.)
Decibels: —30, +4, +16, +30, +44, +56, +70. (For Direct Reading of Output Levels.)
D.C. Microamperes: 0-60—at 250 Millivolts.
D.C. Milliamperes: 0-1.2-12-120—at 250 Millivolts.
D.C. Amperes: 0-12—at 250 Millivolts.
***Ohms:** 0-1,000-10,000—(4,4-44 at center scale).
***Megohms:** 0-1-100—(4,400-440,000 center scale).
Output: Condenser in series with A.C. Volt ranges.

**Resistance ranges are compensated for greatest accuracy over wide battery voltage variations. Series Ohmmeter circuits for all ranges to eliminate possibility of battery drain when leaving switch in Ohms position.*

Get a Triplett 630 into your own hands at your distributor.
U.S.A. Dealer Net $3950


TRIPLETT ELECTRICAL INSTRUMENT COMPANY
BLUFFTON, OHIO

TRIPLETT

www.americanradiohistory.com

Six months from today Which Will You Hold?

this-

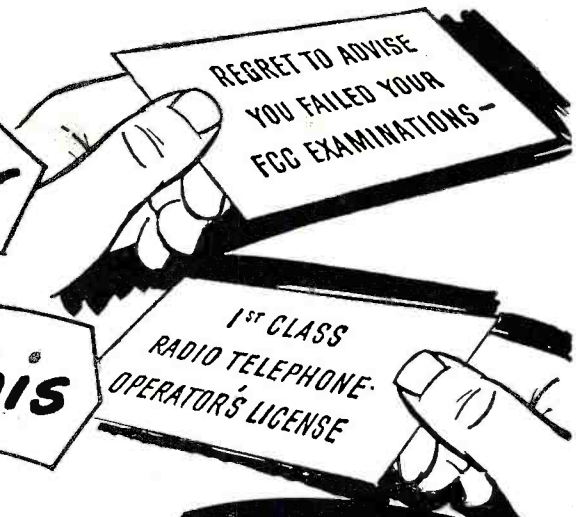

or this

Add Technical Training To Your Practical Experience-

GET YOUR FCC LICENSE IN A HURRY!

Then use our Amazingly Effective JOB-FINDING SERVICE

Money-Making FCC Commercial Radio Operator LICENSE Information

TV ENGINEERING INCLUDED IN OUR TRAINING & COACHING

Get This Valuable Booklet FREE!

TELLS HOW-

Here Is Your GUARANTEE

If you fail to pass your Commercial License exam after completing our course, we guarantee to continue your training without additional cost of any kind until you successfully obtain your Commercial license, provided you first sit for this examination within 90 days after completing your course.

WE GUARANTEE

TO TRAIN AND COACH YOU AT HOME IN SPARE TIME UNTIL YOU GET

YOUR FCC LICENSE

If you have had any practical experience—Amateur, Army, Navy, radio repair, or experimenting.

TELLS HOW-

Employers make JOB OFFERS Like These to Our Graduates Every Month

Letter from nationally known manufacturer of high quality AM and FM transmitters. "We are very much in need at the present time of radio-electronics technicians and would appreciate any helpful suggestions that you may be able to offer." Salary up to $412 per month to start.

Letter from nationally known airplane manufacturer. "We need men with electronic training or experience in radar maintenance to perform operational check-out of radar and other electronics systems . . . starting salary . . . amounting to $329.33 per month."

These are just a few samples of the job offers that come to our office periodically. Some licensed radioman filled each of these jobs . . . it might have been you!

HERE'S PROOF FCC LICENSES ARE OFTEN SECURED IN A FEW HOURS OF STUDY With OUR Coaching AT HOME in Spare Time.

Name and Address	License	Lessons
Lee Worthy 2210½ Wilshire St., Bakersfield, California	2nd Phone	16
Clifford E. Vogt Box 1016, Dania, Florida	1st Phone	20
Francis X. Foerch 38 Beucler Pl., Bergenfield, New Jersey	1st Phone	38
S/Sgt. Ben H. Davis 317 North Roosevelt, Lebanon, Illinois	1st Phone	38
Albert Schoell 110 West 11th St., Escondido, California	2nd Phone	23

Carl E. Smith, E.E., Consulting Engineer, President

CLEVELAND INSTITUTE OF RADIO ELECTRONICS

Desk RN-61, 4900 Euclid Bldg., Cleveland 3, Ohio

TELLS HOW-

Our Amazingly Effective JOB-FINDING SERVICE Helps CIRE Students Get Better Jobs

Here are a few recent examples of Job-Finding results:

GETS CIVIL SERVICE JOB

"Thanks to your course I obtained my 2nd phone license, and am now employed by Civil Service at Great Lakes Naval Training Station as an Engineering Specialist."

Kenneth R. Leiser, Fair Oaks, Mtd. Del., McHenry, Ill.

GETS STATE POLICE JOB

"I have obtained my 1st class ticket (thanks to your school) and since receiving same I have held good jobs at all times. I am now Chief Radio Operator with the Kentucky State Police."

Edwin P. Healy, 264 E. 3rd St., London, Ky.

GETS BROADCAST JOB

"I wish to thank your Job-Finding Service for the help in securing for me the position of transmitter operator here at WCAE, in Pittsburgh."

Walter Koschik, 1442 Ridge Ave., N. Braddock, Pa.

OURS IS THE ONLY HOME STUDY COURSE WHICH SUPPLIES FCC-TYPE EXAMINATIONS WITH ALL LESSONS AND FINAL TESTS.

GETS AIRLINES JOB

"Due to your Job-Finding Service, I have been getting many offers from all over the country, and I have taken a job with Capital Airlines in Chicago, as a Radio Mechanic."

Harry Clare, 4537 S. Drexel Blvd., Chicago, Ill.

Your FCC Ticket is recognized in all radio fields as proof of your technical ability



Get All 3 Free

MAIL COUPON NOW

CLEVELAND INSTITUTE OF RADIO ELECTRONICS
Desk RN-61—4900 Euclid Bldg., Cleveland 3, Ohio
(Address to Desk No. to avoid delay)

I want to know how I can get my FCC ticket in a minimum of time. Send me your FREE booklet, "How to Pass FCC License Examinations" (does not cover exams for Amateur License), as well as a sample FCC-type exam and the valuable booklet, "Money-Making FCC License Information." Be sure to tell me about your Television Engineering Course.

B

NAME .....

ADDRESS .....


CITY ..... ZONE ..... STATE .....

Paste on two-cent postcard or send airmail

www.americanradiohistory.com

THI BOOK HELPS YOU

Make Increased Profits

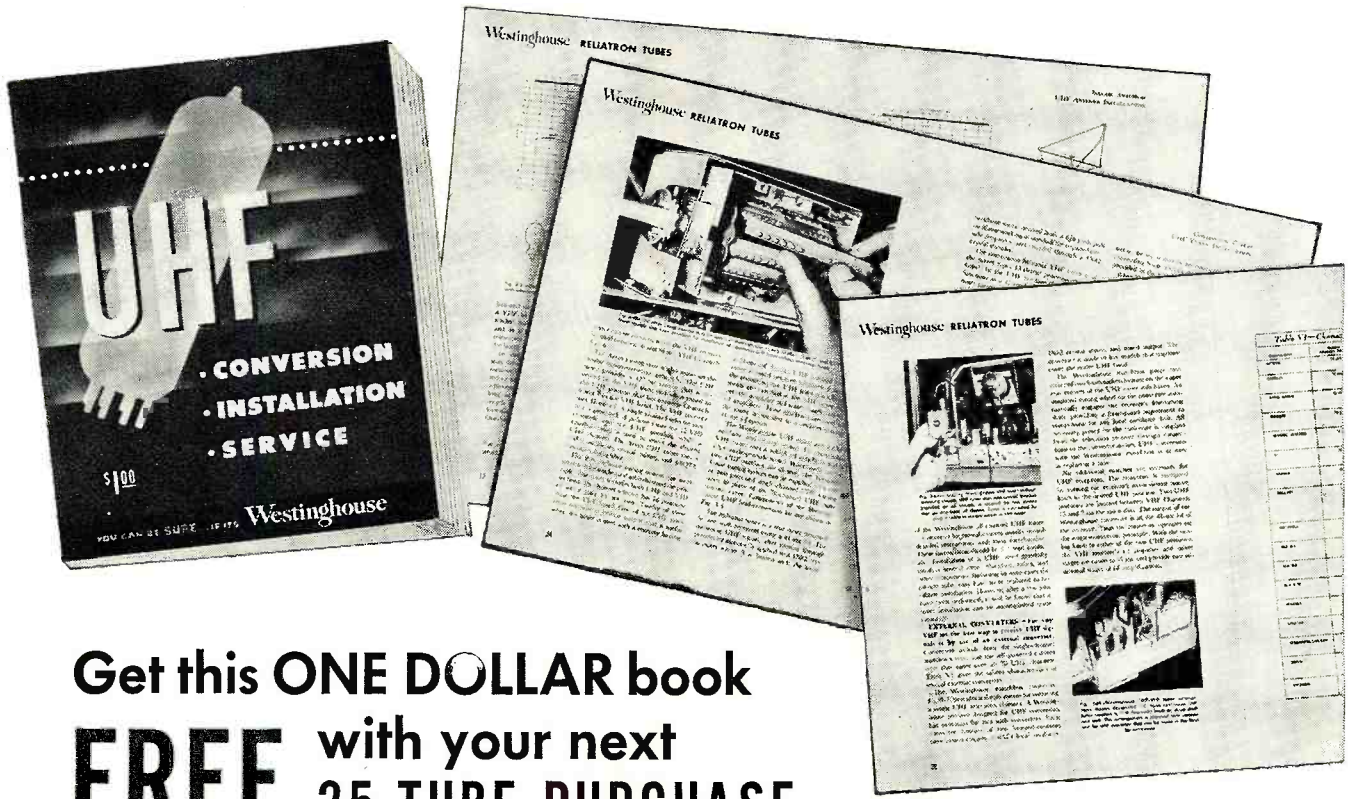

Get this ONE DOLLAR book FREE with your next 25-TUBE PURCHASE

This newest, most helpful book on UHF conversions is yours free when you buy 25 RELIATRON receiving tubes or one picture tube from your Westinghouse Distributor.

This vital handbook covers conversion data, tuners and converters, antenna installations, channel frequency charts, station coverage, and many other necessary, conveniently arranged facts you will need.

There's a gold mine in UHF conversions. And this book will help you make the most out of the biggest profit opportunity since television came alive.

Get this dollar value for no extra charge with your next order of 25 tubes! See your nearest Westinghouse RELIATRON Tube Distributor for your copy of this new "how to do it" book that will build your profits.

Act Now for **UHF PROFITS**

See Westinghouse Tube Listings in 1954 Photofact Folders.

ET-95046A

YOU CAN BE SURE...IF IT'S Westinghouse

RELIATRON™ TUBES

WESTINGHOUSE ELECTRIC CORPORATION, ELECTRONIC TUBE DIVISION, ELMIRA, N. Y.

www.americanradiohistory.com

ADVANCE! Raise your earning power—learn RADIO-TELEVISION-ELECTRONICS by SHOP-METHOD HOME TRAINING

GOOD JOBS AWAIT THE TRAINED RADIO-TV TECHNICIAN

There is a place for *you* in the great Radio-Television-Electronics industry when you are trained as National Schools will train you at home!

Trained technicians are in growing demand at good pay—in manufacturing, broadcasting, television, communications, radar, research laboratories, home Radio-TV service, and other branches of the field. National Schools Master Shop-Method Home Training, with newly added lessons and equipment, trains you in your spare time, right in your own home, for these fascinating opportunities. OUR METHOD IS PROVED BY THE SUCCESS OF NATIONAL SCHOOLS TRAINED MEN, ALL OVER THE WORLD, SINCE 1905.

EARN WHILE YOU LEARN

Many National students pay for all or part of their training with spare time earnings. We'll show you how you can do the same! Early in your training, you receive "Spare-time Work" Lessons which will enable you to earn extra money servicing neighbors' and friends' Radio and Television receivers, appliances, etc.

MASTER ALL PHASES!




Get Master Shop-Method Home Training from an Established Practical Resident School with its own Training Shops, Laboratories, Studios — almost 50 Years of Successful Experience in Training Ambitious Men.

We Bring National Schools To You!



Superheterodyne Receiver

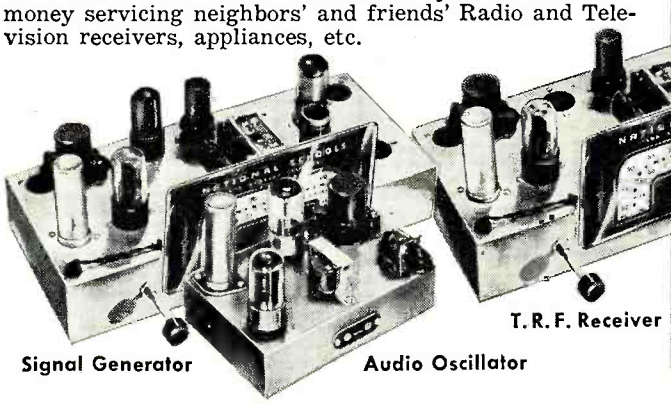

Signal Generator

Audio Oscillator

T. R. F. Receiver

LEARN BY DOING

You receive and keep all the modern equipment shown above, including tubes and valuable, professional quality Multitester. *No extra charges.*

FREE! RADIO-TV BOOK AND SAMPLE LESSON!

Send *today* for National Schools' new, illustrated Book of Opportunity in Radio-Television-Electronics, and an actual Sample Lesson. No cost—no obligation. Use the coupon now—we'll answer by return airmail.

This course also offered in Spanish and Portuguese



National Schools Training is All-Embracing

National Schools prepares you for your choice of many job opportunities. Thousands of home, portable, and auto radios are being sold daily—more than ever before. Television is sweeping the country, too. Co-axial cables are now bringing Television to more cities, towns, and farms every day! National Schools' *complete* training program qualifies you in all fields. Read this partial list of opportunities for trained technicians:

Business of Your Own • Broadcasting
Radio Manufacturing, Sales, Service • Telecasting
Television Manufacturing, Sales, Service
Laboratories: Installation, Maintenance of Electronic Equipment
Electrolysis, Call Systems
Garages: Auto Radio Sales, Service
Sound Systems and Telephone Companies, Engineering Firms
Theatre Sound Systems, Police Radio
And scores of other good jobs in many related fields.


APPROVED FOR VETERANS AND NON-VETERANS
Check coupon below

Both Resident and Home Study Courses Offered!

NATIONAL SCHOOLS

LOS ANGELES 37, CALIFORNIA • ESTABLISHED 1905
IN CANADA: 811 W. HASTINGS STREET, VANCOUVER, B.C.

TELEVISION TRAINING

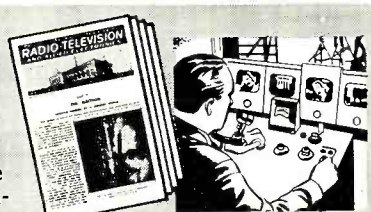

You get a complete series of up-to-the-minute lessons covering all phases of repairing, servicing and construction. The same lesson texts used by resident students in our modern and complete Television broadcast studios, laboratories and classrooms!

GET FACTS FASTEST! MAIL TO OFFICE NEAREST YOU!

(mail in envelope or paste on postal card)

NATIONAL SCHOOLS, Dept. RH-24

4000 S. Figueroa Street, Los Angeles 37, Calif. or **323 West Polk Street, Chicago 7, Ill.**

Send FREE Radio-TV Electronics book and FREE sample lesson. No obligation, no salesman will call.

NAME_____ BIRTHDAY_____ 19____

ADDRESS_____

CITY_____ ZONE____ STATE_____

☐ Check here if interested in Resident School Training at Los Angeles.
VETERANS: Give Date of Discharge_____

www.americanradiohistory.com

Did you hear?



Centralab
has
Something New
in high-voltage
ceramic
capacitors



See the
announcement by
Centralab
on page 118
in this issue

Within the INDUSTRY

LYNN EATON has been appointed vice-president in charge of sales for *National Company, Inc.*, electronic engineering and manufacturing firm of Malden and Melrose, Mass.



Mr. Eaton has, for the past four years, served as general sales manager of another well-known eastern manufacturer of electronic products. Prior to that he was sales manager of *Bendix Home Appliances, Inc.*

In his new post he will supervise all sales activities, both foreign and domestic; advertising and promotion, and market surveys. He will also serve as chairman of the new projects committee of the company.

* * *

RETMA has created an international department and authorized the employment of special counsel for the newly-established Electronics Industry Committee in its continuing program of expansion.

The new international department will be governed by an executive committee representing both radio-TV and electronics interests and will comprise various product sections. An export manager will be employed and stationed at RETMA headquarters in Washington.

The service committee of the association has approved plans to hold a three-week "teacher training seminar" for television service instructors this summer. The seminar will be based on teaching techniques and subject material covered in RETMA's "A" pilot course.

* * *

A. W. KEEN has been named commercial engineering manager for the television picture tube division of *Sylvania Electric Products Inc.* He will make his headquarters at the picture tube division's plant in Seneca Falls, N. Y. . . . The Tube Division of *Westinghouse* has named **JOHN A. CURTIS** to the post of general sales manager . . . **GRANT GRAHAM,** previously in the jobber sales division of *Triad Transformer Corporation,* has been named to fill the newly-created post of product applications engineer . . . *Jerrold Electronics Corporation* has promoted **CAYWOOD C. COOLEY** to the post of vice-president and general manager of the company's service division while **ROBERT J. TARLTON,** who formerly headed the service corporation, has been named manager of the company's new community operations division . . . **C. H. SHARP** has been promoted to the post of general manager of *H. H. Buggie, Inc.* of Toledo. The company also upped **C. R. THORPE** to the post of chief engineer. He was formerly sales manager of the firm . . . **BARNEY EDWARDS** is the new national sales manager for *Recoton Corp.* of New York . . . *CBS-Columbia* has appointed **FRANK R. DAY** production engineer. He has more than thirty years' experience in the radio-television field . . . **W. K. TRUKENBROD** is the new merchandise and sales manager of *Warwick Manufacturing Corporation's* home receiver department. He was formerly with *Raytheon's* distributor division . . . **LINCOLN THOMPSON** has been named a vice-president of *Raymond Engineering Laboratory* of Middletown, Conn. . . . **MYLES SPECTOR** has rejoined *Insuline Corporation of America* after a tour of duty in the Air Force. He is in charge of the company's new product development program . . . *Bellevue Tube Mill, Incorporated,* an affiliate of *Snyder Manufacturing Company,* has appointed **DICK MORRIS** to the post of sales manager . . . **C. G. BARKER,** former vice-president in charge of sales for *Magnecord, Inc.,* has been named distribution manager of the *National Company, Inc.*

* * *

DR. THOMAS T. GOLDSMITH, JR. has been named vice-president-research of the *Allen B. Du Mont Laboratories, Inc.*



One of the country's outstanding electronics and television scientists, Dr. Goldsmith is a member of the company's board of directors and is also president and a director of *Du Mont Television & Electronics, Ltd.* of Canada.

Dr. Goldsmith joined the company in 1936 as director of research. He is active on various committees of RETMA, IRE, SMPTE, NARTB, AIEE, and NTSC.

* * *

SUPEREX ELECTRONICS CORPORATION of Yonkers, N. Y. is now operating **RAYBURNE CORPORATION** of that city and will market the combined lines of electronic components and equipment under the parent company's name. The new subsidiary makes "Ferri-Loopsticks," "Vari-Loopsticks," TV interference filters, etc. This line will be continued and expanded in the new setup . . . **J. L. CAPPELS & ASSOCIATES** has been formed as a manufacturers representatives firm with headquarters at 800 North Clark Street, Chicago 10. Mr. Cappels, principal in the new firm, was formerly associated with *Hallicrafters, Meissner,* and *Stewart-Warner* . . . **SUPERIOR TUBE**

www.americanradiohistory.com


HERE ARE 31 REASONS WHY THE hallicrafters SX-88


's the hottest ham news in years.



SX-88

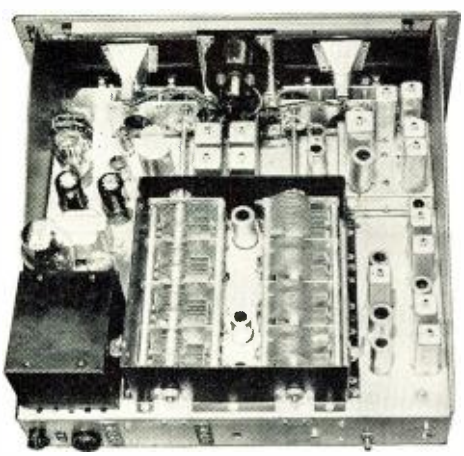SELECTIVITY—
For the first time, selectivity from 10 kc to 250 cycles in six steps. Compare with ANY other receiver!



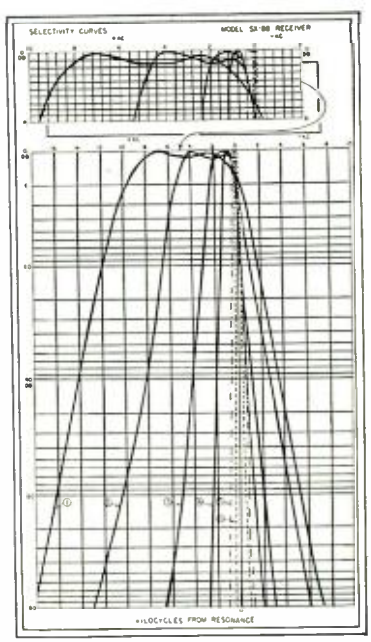

1. Heavy gauge steel welded chassis for mechanical stability.
2. Full precision gear drive for main and band spread tuning.
3. Six position Band Width Control (selectivity) from 250 cycles to 10 kc.
4. 10 watt inverse feed back and push-pull audio output.
5. Exhalted B.F.O. for tops in single side band reception.
6. Buffer amplifier in B.F.O. circuit.
7. Antenna trimmer.
8. Amplified and delayed A.V.C.
9. Built-in 100 kc calibration crystal.
10. Second conversion oscillators crystal controlled.
11. Inertia tuning (fly wheels both dials).
12. Full frequency coverage from 535 kc. to 33 mc.
13. Calibrated electrical band spread 160, 80, 40, 20, 15, 11, and 10 meters.
14. Logging scales on each tuning shaft.
15. Dial locks on each tuning shaft.
16. Tuning dial indicators resetable from front panel for maximum calibration accuracy.
17. Auxiliary A.C. socket on rear of chassis.
18. Illuminated band-in-use indicator.
19. Illuminated S meter.
20. Dual S meter calibration S units and microvolts.
21. Auxiliary power socket plus .6 amps at 6.3 volts and 10 ma at 150 volts for accessories.
22. Standard 8¾" by 19" panel for rack mounting if desired.
23. 50 kc i.f. output jack via cathode follower for teletype converter, etc.
24. Five position response control (tone control).
25. Two r.f. stages (Bands II to VI).
26. 17 tubes plus voltage regulator, ballast tube and rectifier.
27. Automatic noise limiter circuit.
28. Phono Jack.
29. Audio output transformer for 3.2, 8, 500/600 ohm loads.
30. Fuse for overload protection.
31. Auxiliary sensitivity control permits monitoring of local transmissions in standby position.

hallicrafters

World's Leading Exclusive Manufacturer of Communications and High Fidelity Equipment, Radio and Television

4401 West Fifth Avenue, Chicago 24, Illinois • Hallicrafters Ltd., 51 Camden Street, Toronto, Canada

www.americanradiohistory.com

WHY TIE UP TIME AND MONEY WITH DOZENS OF CARTRIDGES?



JUST TWO TITONE CERAMIC CARTRIDGES

will replace OVER 90% of present-day phono installations!



For the CUSTOMER, TITONE will

1. Not only *replace* his present crystal, but *improve* the performance of the system with thrilling new TITONE SOUND.

For the JOBBER and DEALER, TITONE will

1. Reduce inventory 2. Increase sales

And TITONE makes REPLACEMENT easy through its

1. Small Size 2. Universal Bracket 3. Accessory Hardware

TITONE Ceramic Cartridges are unaffected by temperature and humidity. They do not deteriorate on the shelf or in equipment, as crystals do.

The ceramic principle is an original discovery and development of the Sonotone laboratories. The demand for TITONE is growing daily. More and more quality-conscious manufacturers are specifying TITONE for original equipment. The same high quality is available to you in every TITONE CERAMIC PICKUP CARTRIDGE.

Other SONOTONE Products:

Sonotone Hearing Aids • Subminiature vacuum tubes • Cathode ray electron guns for television tubes • Nickel cadmium storage batteries for the armed services.

ELECTRONIC APPLICATIONS DIVISION

O OTO E CO PORATIO

Elmsford, New York

COMPANY of Norristown, Pa. has purchased a controlling interest in **FINE TUBES LIMITED,** Surbiton, Surrey, England . . . **SERVOMECHANISMS, INC.** has formed a new component division which will be located at 625 Main Street, Westbury, N. Y. The new division will produce miniature servo and instrument motors, etc . . . **RADIO-TECHNICAL SALES COMPANY** has been formed to represent radio-electronic-television manufacturers in the central midwest area. Lew H. Morse, organizer of the firm, advises that the firm will provide technical sales representation in Nebraska, Iowa, Kansas, Missouri, Oklahoma, and Arkansas.

* * *

JOHN R. THOMPSON has been appointed manager of commercial electronic sales for *Hycon Mfg. Company.*



He was formerly manager of electronic sales for the Cincinnati district of *Graybar Electric Company.* As a former electronic engineer for the Navy Department, Mr. Thompson was one of the designers of the underwater submarine and mine detection devices in the field of sonar. He also set up installations and trained personnel in its use.


He is a member of the IRE and was formerly chief engineer for *Stone and Smith Company,* Los Angeles.

* * *

CANNON ELECTRIC COMPANY of Los Angeles has established a third plant in the Lincoln Heights area of Los Angeles at 210 W. Avenue 26 near Barranca Street. The new plant covers approximately 6000 square feet and has a 4000 square foot parking area . . . **ELECTRO PRODUCTS LABORATORIES** of Chicago has expanded its production area at its plant 4501 N. Ravenswood Avenue. Approximately 30 per-cent more floor space has been added to the company's present manufacturing facilities . . . **SUPERIOR INSULATED WIRE COMPANY** has just completed a modern manufacturing plant at Haverstraw, N. Y. The new plant adds over 15,000 square feet to the company's existing facilities for producing electric wires and television transmission lines . . . **PENTRON CORPORATION** of Chicago has leased additional manufacturing facilities at 2355 S. Indiana Avenue and 2441 S. Michigan Avenue in Chicago for assembly operations . . . The newly-occupied 77,000 square foot plant of the electronics division of **THERMADOR ELECTRICAL MANUFACTURING COMPANY,** Los Angeles, is now in full operation . . . The electronics division of **DIAMOND POWER SPECIALTY CORPORATION** has moved into its new electronics laboratory adjacent to its manufacturing plant at Lancaster, Ohio. The new building has approximately 30,000 square feet of floor space and houses the most advanced facilities . . . **ELCO CORPORATION** has added a new plant to its facilities located at

(*Continued on page* 185)

www.americanradiohistory.com

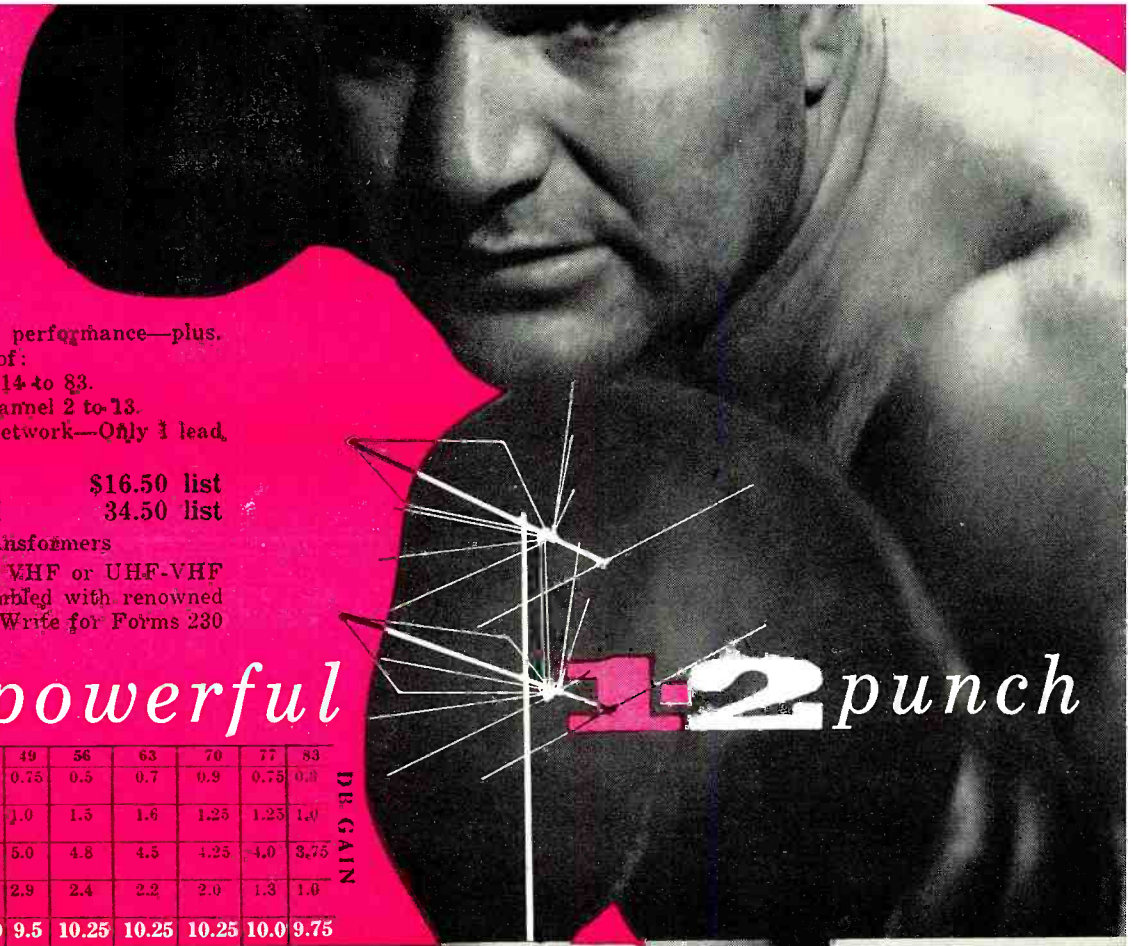

JFD JeTOMIC

Produces brilliant deep fringe UHF performance—plus.
Produces heretofore unachieved gain of:
Stacked* UHF Rhombic on Channels 14 to 83.
Stacked JeT conical on every VHF Channel 2 to 13.
Featuring exclusive no-loss isolation network—Only 1 lead to set.

Model JeT 454 Single $16.50 list
Model JeT 454 S* Stacked 34.50 list

* complete with stacking transformers

Guaranteed to out-perform any other VHF or UHF-VHF antenna. Both units factory pre-assembled with renowned Jet-action all-aluminum construction. Write for Forms 230 and 241.

the most powerful 1-2 punch

Channels	14	21	28	35	42	49	56	63	70	77	83
Competitor A Conical with Bowtie (2 stack)	4.0	3.25	2.0	1.0	1.0	0.75	0.5	0.7	0.9	0.75	0.8
Competitor B Bedspring with UHF	0.75	0.75	0.9	1.0	0.8	1.0	1.5	1.6	1.25	1.25	1.0
Competitor C Conical with V (2 stack)	3.0	3.3	4.0	4.6	4.9	5.0	4.8	4.5	4.25	4.0	3.75
Competitor D Filter type with attached "V"	2.0	2.0	2.5	2.75	2.9	2.9	2.4	2.2	2.0	1.3	1.0
JFD JeT 454 S	**7.0**	**7.25**	**7.4**	**8.5**	**9.0**	**9.5**	**10.25**	**10.25**	**10.25**	**10.0**	**9.75**

DB GAIN

JFD SUPER-JeT

Delivers Spectacular Deep fringe VHF performance—plus.
Packs Unprecedented gain of:
Single 10-Element VHF Yagi on each channel from 2 to 13.
Stacked UHF Bowtie-Reflector off side lobes on Channels 14 to 83.

Model JeT 213 Single $20.75 list
Model JeT 213 S* Stacked 42.50 list

* complete with stacking transformers

JFD Electronics

Burton browne advertising

JFD Manufacturing Company
Brooklyn 4, N. Y.

in antenna history!


CHANNELS	2	3	4	5	6	7	8	9	10	11	12	13
Competitor A Mattress (4 Stack)	4.0	5.0	7.0	6.25	5.0	5.25	6.0	5.25	7.25	9.25	6.5	7.0
Competitor B Radar Screen Type A	0.0	3.0	4.0	3.25	3.0	4.5	7.0	7.0	8.0	10.0	10.0	9.0
Competitor C Radar Screen Type B	0.75	3.25	4.5	3.5	3.5	6.0	7.0	6.5	7.75	8.0	7.5	6.0
Competitor D CHS 2-13 YAGI	4.50	5.00	5.75	3.00	2.50	3.50	1.00	0.0	.875	.875	.50	.75
JFD JeT 213 S	6.0	7.5	8.75	7.75	6.75	10.0	9.0	7.0	9.0	10.0	11.0	9.75

DB GAIN

	1" Square Crossarm	Completely Preassembled	LIST PRICE
Competitor A	NO	YES	$55.00
Competitor B	NO	NO	$34.95
Competitor C	NO	NO	$47.50
Competitor D (2 STACK)	NO	NO	$65.90
JFD JeT 213 S	YES	YES	$42.50

World's largest manufacturers of TV antennas and accessories.

www.americanradiohistory.com

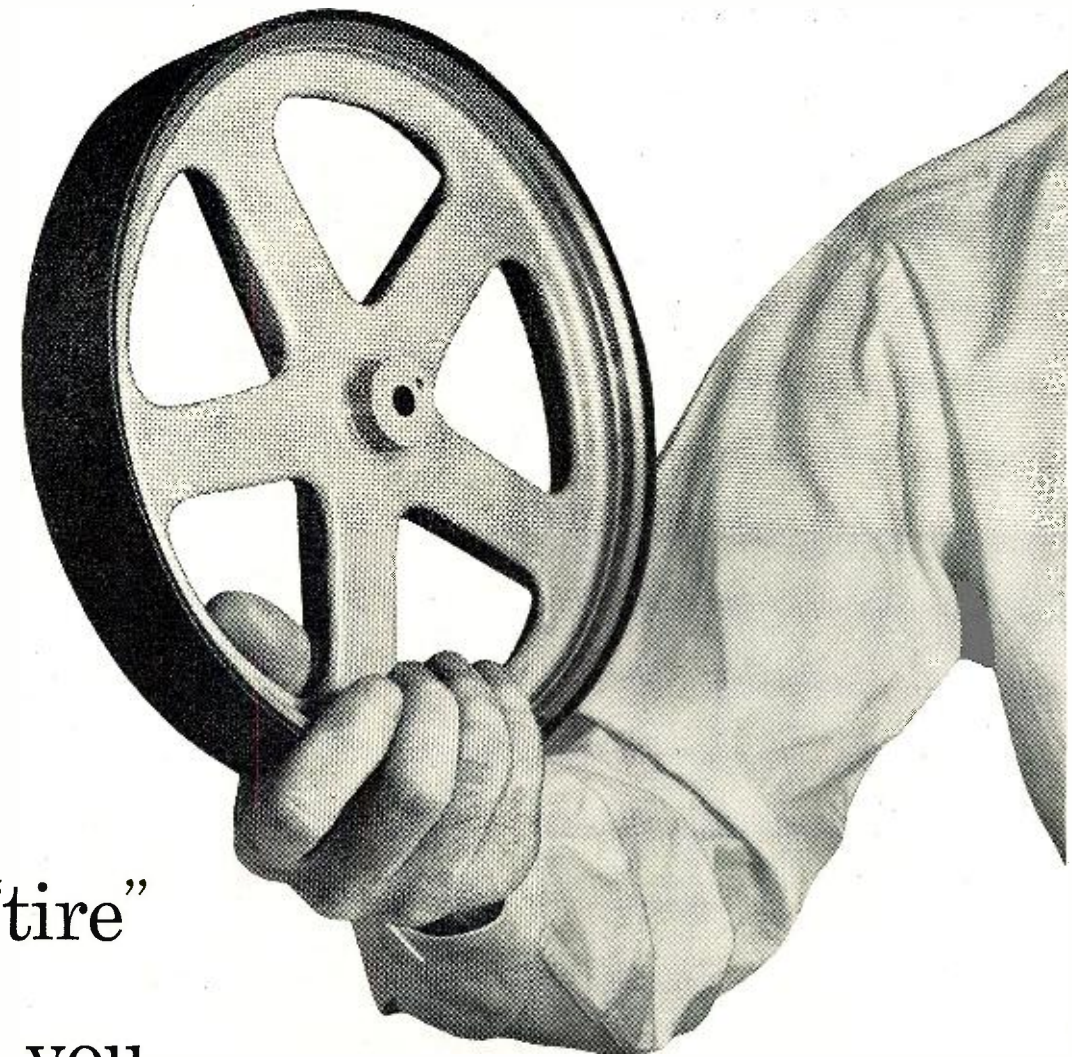

This rubber "tire" talks to you

Bell Laboratories engineers have developed a new and highly economical way to record sound magnetically.

Instead of tape or wire they use a mixture of rubber and iron oxides which is formed into a band and mounted on a wheel. This simple and very rugged "talking rubber" can play back messages clearly millions of times.

Talking rubber is already at work for the Bell System announcing weather and answering customers who call vacant or disconnected numbers. It promises to have many other uses. In a new machine, it answers your telephone in your own voice when you are away—and takes a message for you in the voice of your caller.

Many businesses, too, other than telephone, are expected to find a variety of ways to use talking rubber—especially whenever a message must be given quickly to many people.

Talking rubber proves again the downright practicality of Bell Laboratories' research to improve telephone service.



One of a bank of recorder-reproducers operated by the New York Telephone Company for the New York Stock Exchange. They give instant stock quotations to brokers who dial a code number. Recording and pickup heads are shown above wheel.

BELL TELEPHONE LABORATORIES

Improving telephone service for America provides careers for creative men in scientific and technical fields.

www.americanradiohistory.com

No matter where you live
or what you are doing now...

I WILL TRAIN YOU FOR A BIG PAY JOB IN TELEVISION



L. C. Lane, B.S., M.A.
President: Radio-Television Training Association.
Executive Director: Pierce School of Radio-Television.

CIVILIANS! VETERANS!


Thousands of new jobs in TV are opening up in every state as new stations go on the air. You too can take your place in America's booming TELEVISION and Electronics industry. enjoy the success and happiness you always wanted out of life! Now... prepare for a life-time career as a trained TV TECHNICIAN, often within months... using the same successful "learn-by-doing" home study methods that have helped hundreds of men with NO PREVIOUS TRAINING!

NO EXPERIENCE NECESSARY

LEARN TELEVISION AT HOME IN YOUR SPARE TIME!



Giant Screen TV Receiver

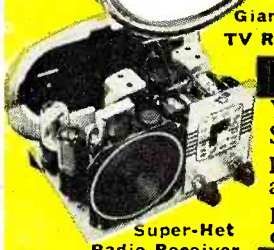

Super-Het Radio Receiver



C-W Telephone Receiver



Combination Voltmeter-Ammeter-Ohmmeter



Public Address System

RF Signal Generator



GET MORE! LEARN MORE! EARN MORE!

I give you ALL the equipment and training you need to prepare for the BETTER PAY jobs in TV. While training, many of my students make $25.00 a week repairing Radio-TV sets in their spare time... start their own profitable service business.

MORE EQUIPMENT!

You build and keep this professional GIANT SCREEN TV RECEIVER complete with big picture tube (designed and engineered to take any size up to 21-inch). Also all units illustrated, plus additional equipment! Everything supplied complete with all tubes.

FREE FCC COACHING COURSE!

Prepares you at home for your FCC License. The best jobs in TV and radio require an FCC License. My FCC Coaching Course is given to you at NO EXTRA COST after TV Theory and Practice is completed.

NEW! PRACTICAL TV CAMERAMAN & STUDIO COURSE!

For Men With Previous Radio & TV Training

I train you at home for an exciting big pay job as the man behind the TV camera. Work with TV stars in TV studios or "on location" at remote pick-ups! A special one-week course of practical work on TV studio equipment at Pierce School of Radio & TV, our associate resident school in New York City, is offered upon your graduation.

FM-TV TECHNICIAN TRAINING!

My FM-TV Technician Course will save you months of training, if you have previous Armed Forces or civilian radio experience. Complete with kits, BIG SCREEN TV RECEIVER, and FREE FCC Coaching Course.

OPTIONAL: TWO WEEKS TRAINING IN NEW YORK CITY AT NO EXTRA COST

You get two weeks, 50 hours, of intensive Laboratory work on modern electronic equipment at our associated school in New York City—Pierce School of Radio and Television. And I give you all this AT NO EXTRA COST whatsoever, after you finish your home study training in the Radio-FM-TV Technician course and FM-TV Technician Course.

RADIO-TELEVISION TRAINING ASSOCIATION

52 EAST 19th STREET, NEW YORK 3, N. Y.
Licensed by the State of New York Approved by the VA

VETERANS.



MY SCHOOLS FULLY APPROVED TO TRAIN VETERANS UNDER *NEW* G.I. BILL! If discharged after June 27, 1950—CHECK COUPON BELOW! Also approved for RESIDENT TRAINING in New York City... qualifies you for full subsistence allowance up to $160 per month. Write for details.

MAIL COUPON TODAY!

MY 4 FREE AIDS SHOW YOU HOW AND WHERE TO GET A BETTER PAY JOB IN TELEVISION!

See for yourself how my simple, practical methods make success easy.



NO SALESMAN WILL CALL!

Dept. T-2B

Mr. Leonard C. Lane, President
RADIO-TELEVISION TRAINING ASSOCIATION
52 East 19th Street, New York 3, N. Y.

Dear Mr. Lane: Mail me your NEW FREE BOOK, FREE SAMPLE LESSON, and FREE aids that will show me how I can make BIG MONEY IN TELEVISION. I understand I am under no obligation and no salesman will call.

(PLEASE PRINT PLAINLY)

NAME_____ AGE_____

ADDRESS_____

CITY_____ ZONE____ STATE_____

I AM INTERESTED IN:


- ☐ Radio-FM-TV Technician Course
- ☐ FM-TV Technician Course
- ☐ TV Cameraman & Studio Course


VETERANS! Check here for Training under NEW G.I. Bill . . . . . ☐

www.americanradiohistory.com

THIS ANTENNA OUT-PERFORMS:

this . . . | this . . . | this . . . | or this

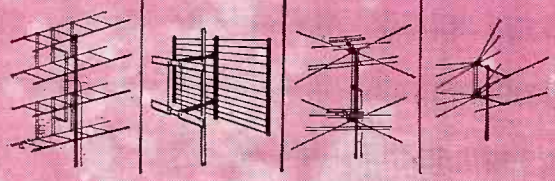

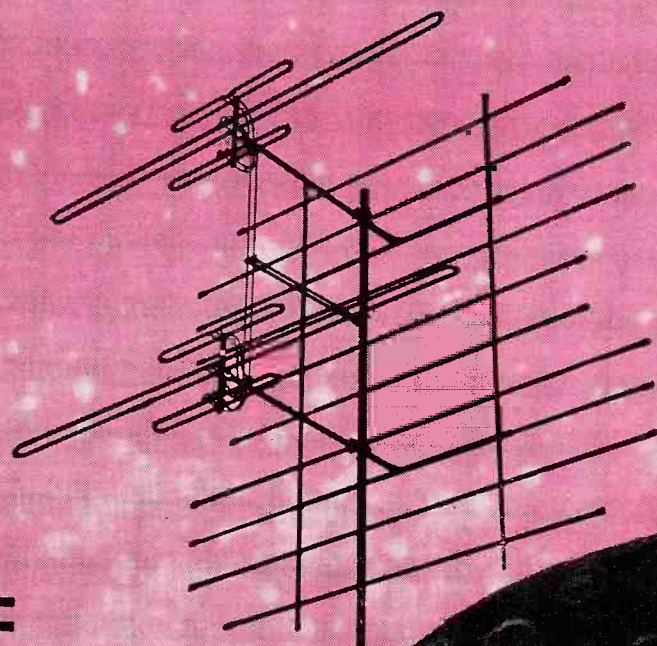

the AMAZING VHF CHAMPION*


a NEW KIND of Antenna that out-performs every all-channel VHF antenna ever made — — and many Yagis, too!


America's servicemen have spoken! In only 3 months, they've made the CHAMPION the nation's top-selling VHF antenna! It's the highest gain all-channel VHF antenna ever developed, and its performance has now been proven by over 50,000 outstanding installations.

Only the CHAMPION has the unique new "Tri-Pole", a *triple-powered dipole system* in which the Low Band dipole also functions as *three* dipoles tied together, in phase, on the High Band.

Folded dipoles throughout give close to 300 ohms impedance across entire band. Lightweight, all-aluminum construction. Available in one, two, or four-bays.


CHANNEL MASTER CONQUERS SPACE!

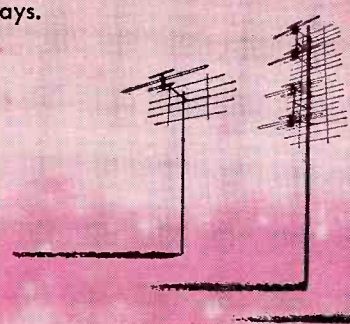

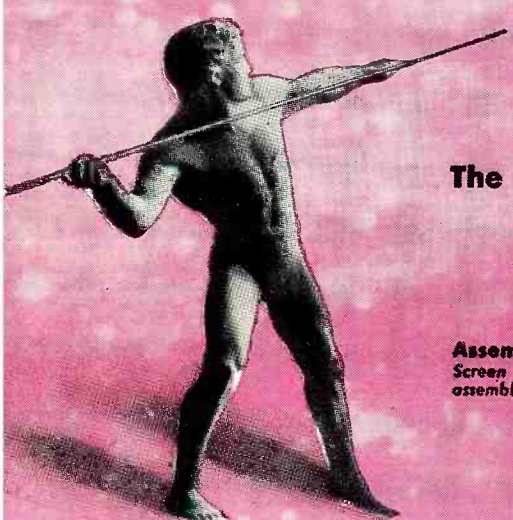


The stacked CHAMPION provides:

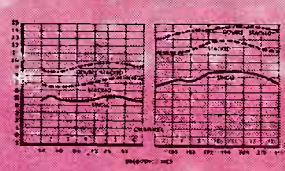- **11-13 DB** *High Band gain*
- **6½-7½ DB** *Low Band gain*



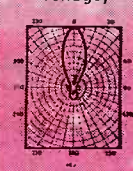horizontal polar pattern (relative voltage)



Assembles faster *than a five-element Yagi. Screen "Pops-Up" instantly. "Tri-Pole" assembly just snaps into place.*

model no.		list price
325	single bay	$20.83
325-2	two bay	42.36
325-4	four bay	88.89
Separate Stacking Harnesses		
325-3	2 bay harnesses	$2.08
325-5	4 bay harnesses	4.15

CHANNEL MASTER CORP.
ELLENVILLE, N. Y.

*Pat. Pend.

www.americanradiohistory.com

3 great, new UHF antennas


by CHANNEL MASTER

STACKED TWIN CORNER REFLECTOR model no. 406-2

The most powerful UHF fringe area installation you can make today!

- Broad Band coverage — yet out-performs most stacked Yagis.
- Covers every UHF channel, *not* just segments of the band.
- New impedance-matching, two-stage stacking system.

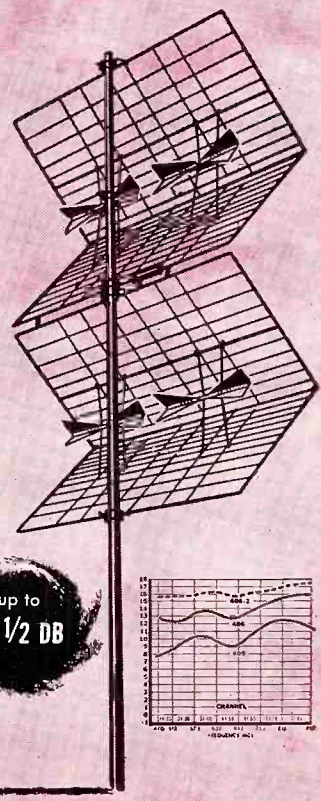Another original Channel Master development!




up to 17½ DB

Model No.	Description	List Price
406	Twin Corner Reflector	$18.06
406-2	2-Bay Twin Corner Reflector. Stacking harness furnished free.	36.10
406-3	Stacking harness only, furnished separately.	2.08

powerful new antennas span vast distances

only $9.03 list

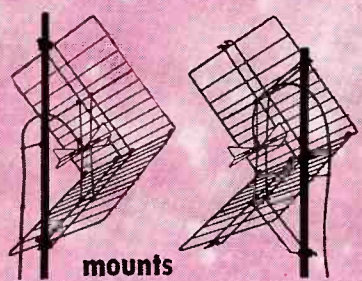the first UHF CORNER REFLECTOR with optional "2-way" mounting!



mounts this way . . . or this way

model no. 409

Only CHANNEL MASTER'S CORNER REFLECTOR can be adapted to any kind of UHF installation — with or without VHF — at no extra cost. Every antenna contains all necessary hardware and braces for BOTH popular types of mounting. Sharp directivity and unusually high gain across entire UHF band.

Installs instantly! Original Channel Master assembly feature: Screen swings open like a book — dipole assembly snaps into place.

"SWEET 16" The World's First 16-Element UHF Yagi!

- Custom-designed for your particular area.
- Super-power! Sensational fringe area reception.
- Delta-Weld design. Elements WELDED to crossarm. Delta-matched dipole gives uniform impedance.
- Wide band coverage, up to 21 channels.
- Average gain: 13 DB single 16 DB stacked

model no. 420

$8.20 list



Send for complete technical literature.

CHANNEL MASTER CORP.
ELLENVILLE, N. Y.


LEADER IN PRE-ASSEMBLED ANTENNAS

Copyright 1953, Channel Master Corp.

www.americanradiohistory.com

the newest *addition*

TR-4

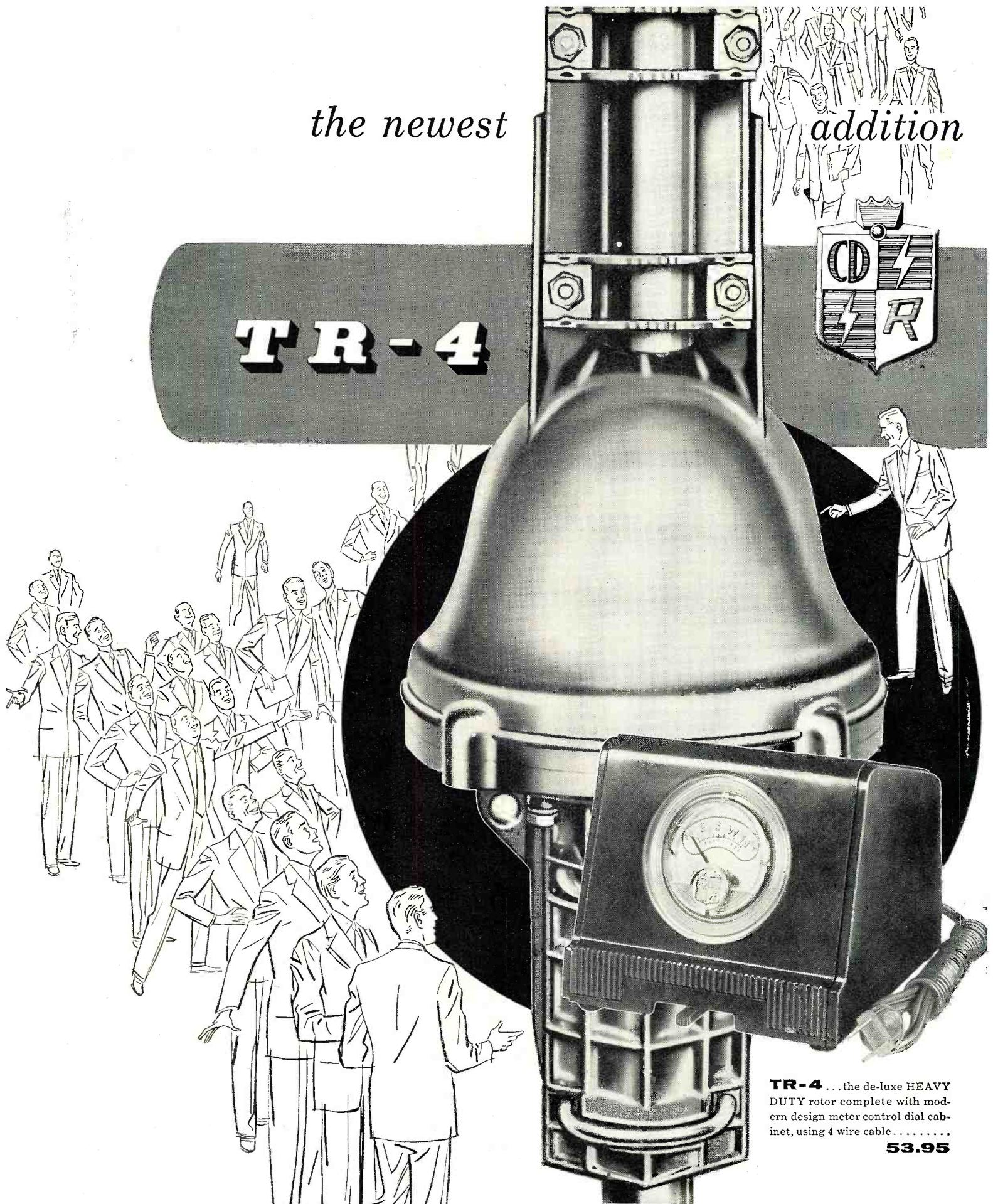

TR-4 . . . the de-luxe HEAVY DUTY rotor complete with modern design meter control dial cabinet, using 4 wire cable **53.95**

CORNELL-DUBILIER

SOUTH PLAINFIELD, NEW JERSEY

www.americanradiohistory.com


to the family of C·D·R Rotors

C·D·R ROTOR


the ultimate in heavy duty Rotors

incorporating all the fine features
that have made the TR-2 outstanding
plus these fine features:

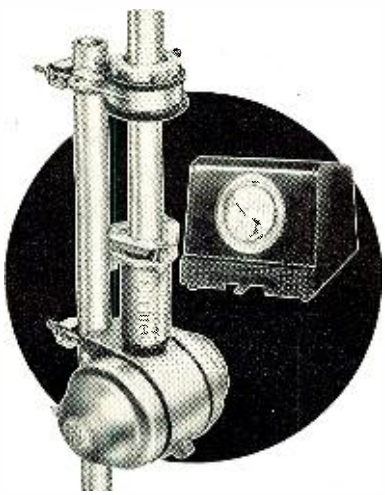
★ **Handsome Meter Dial Cabinet** ★ **Uses 4 Wire Cable**



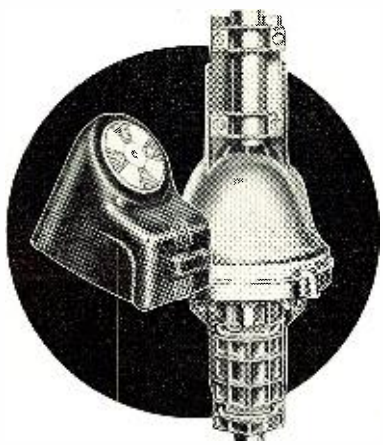
TR-12 . . . a special combination value consisting of complete rotor, including thrust bearing . . . handsome modern design cabinet with meter control dial, 4 wire cable
47.95



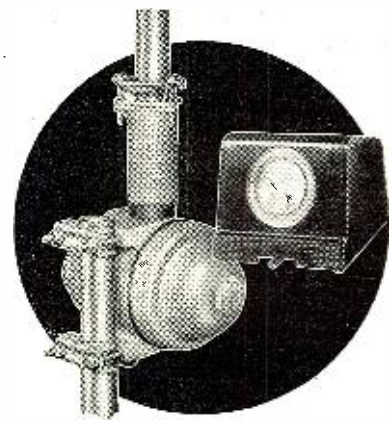TR-2 . . . . the Heavy-Duty rotor, complete with "Compass Control" cabinet having illuminated "perfect pattern" dial . . .
49.95



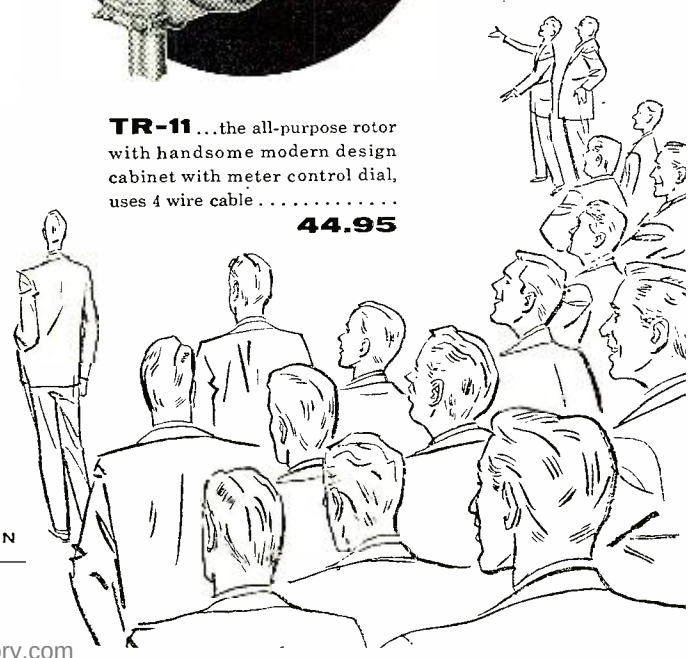TR-11 . . . the all-purpose rotor with handsome modern design cabinet with meter control dial, uses 4 wire cable . . . . . .
44.95



THE **RADIART** CORPORATION
CLEVELAND 13, OHIO

www.americanradiohistory.com


NOW . . . 2 SENSATIONAL EICO SCOPE VALUES!

NEW AMAZING FEATURE PACKED

7" PUSH-PULL OSCILLOSCOPE

Only EICO Has All These Features

- VERTICAL FREQ. RESPONSE: flat ± 2 db 10 cps – 1 mc
- VERTICAL SENS.: .01 volts rms/inch
- HOR. FREQ. RESP.: flat ± 0 db 10 cps – 200 kc, –4 db at 500 kc
- HOR. SENS.: .3 volts rms/inch
- SWEEP RANGE: 15 cps-100 kc
- 3-STEP FREQ.-COMPENSATED ATTENUATOR eliminates freq. distortion, overloading.
- CATHODE FOLLOWER inputs to both amplifiers
- PUSH-PULL outputs in both amplifiers
- RETURN TRACE BLANKING
- INT. VOLTAGE CALIBRATOR
- V & H TRACE EXPANSION & CENTERING: 1.5X full screen without distortion.
- DIRECT CONNECTION to vert. CRT plates.
- PHASING CONTROL of internal 60 cps sine wave sweep.
- AT FRONT PANEL: intensity mod. input; 60 cps, sawtooth outputs.

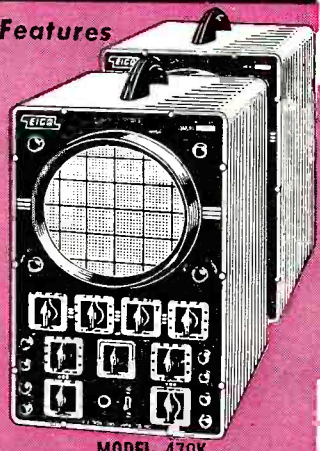

MODEL 470K
KIT $79.95. WIRED $129.50.

EICO EXCLUSIVE! 5" PUSH-PULL SCOPE, 425K, Amazing feature-packed economy-priced Wired, $79.95. KIT, $44.95.

- PUSH-PULL V & H amplifiers. Sens: 0.5-1 rms v/in. Useful to 2.5 mc.
- SWEEP: 15 cps-76 kc. Z-axis intensity modulation. Dual trace positioning controls.



SCOPE VOLTAGE CALIBRATOR KIT 495K KIT $12.95. WIRED $17.95.

- Sq. wave output at power-line freq. with full-scale readings of .1, 1, 10 or 100 V. peak-to-peak.
- Accuracy ± 5% of full-scale on each range.

6V & 12V BATTERY ELIMINATOR KIT 1050K KIT $29.95. WIRED $38.95.

- DC output: 0-8 V or 0-16 V.
- Continuous current rating: 10 A at 6 V, 6 A at 12 V.
- Intermittent current rating: 20 A at 6 V, 12 A at 12 V.
- Separate Voltmeter & Ammeter.



NOW! ONLY EICO KITS & WIRED INSTRUMENTS Gives You LIFETIME SERVICE & CALIBRATION GUARANTEE*

*at less than our cost of handling (See EICO Guarantee Card enclosed with each Kit & Instrument).


221K VTVM KIT $25.95. WIRED $49.95.

- AC & DC volts: 0-5, 10, 100, 500, 1000 V (30 KV with HVP-1 probe).
- 5 ohm ranges from .2 ohm to 1000 megs.
- DC input Z 26 megs.
- 4½" meter movement in can't-burn-out circuit.
- 1% mult. resistors.



360K SWEEP GEN. KIT $34.95. WIRED $49.95.

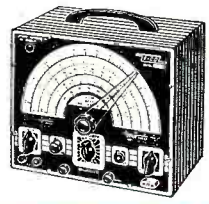- Continuous coverage of all TV & FM freqs. from 500 kc to 228 mc.
- Sweep width variable 0-30 mc.
- Crystal marker oscillator, variable amplitude.



HIGH VOLTAGE PROBE $6.95


- Extends range of VTVMs & voltmeters to 30 KV.





PIX TUBE ADAPTER for Tube Testers $4.50. Checks TV picture tubes while in set.

214K VTVM KIT $34.95. WIRED $54.95.

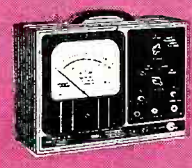

- Large 7½" meter, can't-burn-out circuit.
- AC/DC volts: 0-5, 10, 100, 500, 1000 (30 KV with HV Probe).
- 5 ohms ranges from .2 ohm to 1000 megs.
- DC input Z 26 megs.
- 1% mult. resistors.

625K TUBE TESTER KIT $34.95. WIRED $49.95.



- Illum. gear-driven "Speed Rollchart."
- New lever-action switches for individual testing of every element.
- Tests all conventional & TV tubes.

COUNTER CABINET for above: add $10.00 to Kit or Wired Prices.


950A-K R-C BRIDGE & R-C-L COMP. KIT $19.95. WIRED $29.95.



- Measures & tests all resistors; .5 ohm to 500 megohms.
- Every type condenser, 10 mmf to 5000 mfd.
- 0-500 DC voltage source for capacitor leakage testing.

1171K RES. DECADE BOX KIT $19.95. WIRED $24.95.

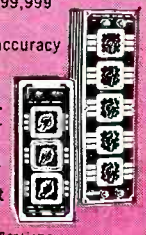- Resistance values from 0 to 99,999 ohms with 0.5% precision.
- All resistors have 0.5% accuracy




DECADE CONDENSER BOX KIT 1180K KIT $14.95. WIRED $19.95.

- All capacitors precision silver mica, accuracy ± 1%.
- Range from 100 mmf – 0.111 mfd in steps of 100 mmf.
- Smooth-action positive detent ceramic switches.

Prices 5% higher on West Coast. Specifications and prices subject to change without notice.

New! EICO SCOOPS!

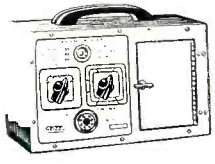


CATHODE RAY TUBE CHECKER 630K, WIRED $24.95 KIT, $17.95.

- Checks all types of TV picture and C.R. tubes in the set or carton. Bridge measurement of peak beam current (proportional to screen brightness).
- Detects shorted & open elements.

BAR GENERATOR 352K, WIRED $19.95 KIT, $14.95

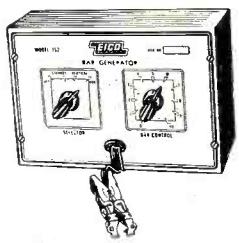- Enabels rapid adjustment of TV picture V & H linearity without hard-to-find station-transmitted test pattern.
- Produces 16 V or 12 H bars. Operates on TV channels 3, 4, or 5.





RTMA RESISTANCE SUBSTITUTION BOX 1100K WIRED $9.95 KIT, $5.50.

- Enables rapid substitution of resistances from 15 ohms to 10 megs in decade multiples of 15, 22, 33, 47, 68, 100 ohms.
- Uses 36 standard 1 watt, ± 10% RTMA resistors.

315K DELUXE SIG. GEN. KIT $39.95. WIRED $59.95.



- Covers range of 75 kc to 150 mc.
- 7 calibrated scales: accuracy better than 1%.
- Bandspread vernier tuning.
- 4-step RF shielded output multiplier: constant output Z.

565K MULTIMETER KIT $24.95 WIRED $29.95.

555K MULTIMETER KIT $29.95 WIRED $34.95. (1% precision resistors)



- 20,000 Ω/V; 31 ranges.
- DC/AC/Output volts: 0-2.5, 10, 50, 250, 1000, 5000.
- DC Current: 0-100 ua; 10, 100, 500 ma; 10 A.
- Ohms: 0-2K, 200K, 20 meg.

377K SINE & SQUARE WAVE AUDIO GEN. KIT $31.95. WIRED $49.95.



- Complete sine wave coverage, 20-200,000 cps in 4 direct-reading ranges.
- Complete square wave coverage, 60-50,000 cps.
- Cathode follower output circuit.

145K SIG. TRACER KIT $19.95. WIRED $28.95.



- Audibly signal traces all IF, RF, Video & Audio circuits from ANT to SPKR or CRT in all TV, FM, AM, etc. without switching.
- Germanium crystal diode probe responsive to over 200 mc.
- Integral test speaker.

536K MULTIMETER KIT $12.90. WIRED $14.90.
526K MULTIMETER KIT $13.90. WIRED $16.90.



- 1000 Ω/V; 31 ranges
- DC/AC volts: Zero to 1, 5, 10, 50, 100, 500, 5000.
- DC/AC Current: 0-1, 10 ma; 0.1, 1 A.
- Ohms: 0-500, 100 K, 1 meg.

320K SIG. GEN. KIT $19.95. WIRED $29.95.
322K SIG. GEN. KIT $23.95. WIRED $34.95.



- Fundamentals 150 kc to 34 mc, harmonics to 102 mc.
- 5-step band switching.
- Colpitts audio oscillator generates 400 cps pure sine wave voltage.
- Permits pure RF, modulated RF, or pure AF.

Write NOW for FREE latest Catalog R-2

Ask your jobber for FREE EICO business building decals.

EICO

Seperate Assembly & Operating Manuals supplied with each EICO KIT!

You build EICO Kits in one evening, but . . . they last a lifetime!

SAVE OVER 50%! *See the famous EICO line TODAY, at your local jobber.*


© 1953

www.americanradiohistory.com

A CITIZENS BAND GARAGE DOOR CONTROL

By
HARTLAND B. SMITH, W8VVD

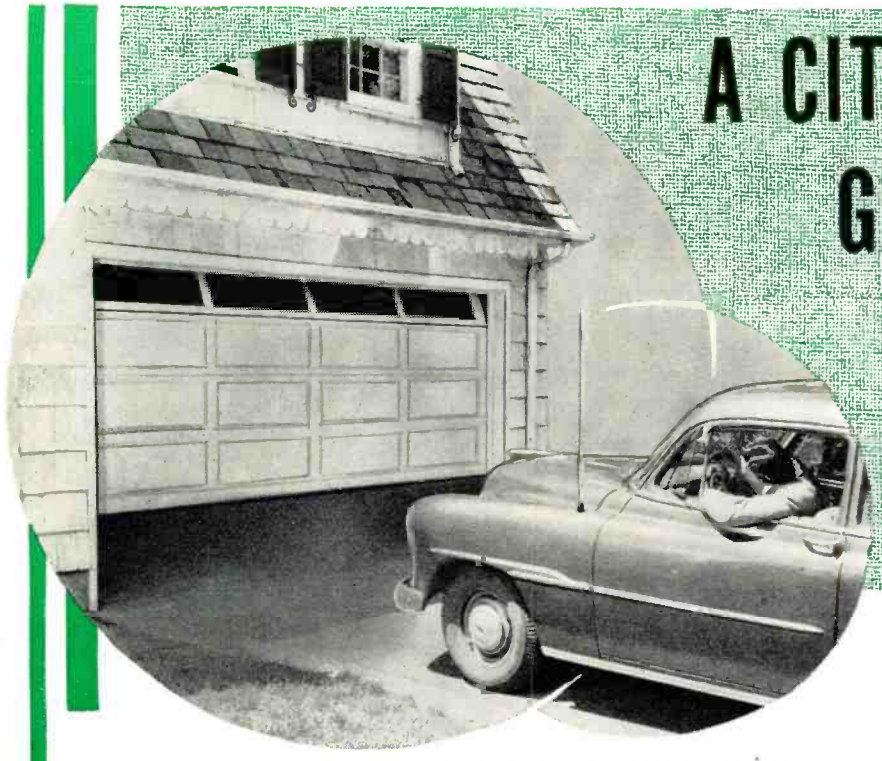A TVI-proof unit which operates on the 27 mc. Citizens Band. A station license is required.



An overhead garage door, this one made by Overhead Door Company, Inc., of the type suitable for use with the radio-control unit described.

FEW situations are more disconcerting to a motorist than to arrive home in a pouring rain and find the garage door locked. Although happenings of this nature can be avoided by the simple expedient of leaving the door open while away from home, this practice is not recommended in areas peopled by curious toddlers or borrowing neighbors—at least not if you expect to find the lawn mower and garden spade in their accustomed places when you return from a drive in the country.

Radio control is a practical method for reducing to a minimum the inconvenience of garage door opening and closing. By merely flipping a switch you can open or close the door at will without leaving your car. The Citizens Band radio gear to be described, when used in conjunction with a commercially-built electric door opener, will prove so handy that you'll be the envy of all your non-mechanized acquaintances.

The heart of any radio-control system is the receiver. It must be sensitive enough to respond to its companion transmitter and yet selective enough to reject signals produced by other radio equipment. One way to solve this problem is to use a special modulating circuit which produces a coded signal from the transmitter. A decoding circuit in the receiver will respond only to this signal, rejecting transmissions from all other radio devices.

The complications involved in the construction and adjustment of coding circuits are numerous, however, and so it was decided, for simplicity's sake, to employ a rather insensitive receiver—one which would respond only to a strong signal emanating from a nearby transmitter. The receiving circuit finally evolved, although somewhat unique, has proven both simple and practical. It consists of a voltage tripling crystal detector followed by a d.c. amplifier which, in turn, is followed by a thyratron tube with a sensitive relay in its plate lead.

When a signal from the transmitter in the car is picked up on the receiving antenna, it is rectified by the crystal detector and appears as a negative voltage on the grid of V_1, the d.c. amplifier. This negative voltage reduces the plate current of V_1, thus lowering the voltage drop across R_3. A reduction in the voltage across R_3 cuts the bias of V_2 and, since this tube is a thyratron, its plate current abruptly increases. This large increase in current closes RL_1 and actuates the door opening mechanism.

The crystal detector is in the form of a voltage tripler. Thus, its output is appreciably greater than that provided by the customary half-wave crystal circuit. Use of high back resistance 1N54 germanium diodes, in place of 1N34's, further increases the voltage available at the grid of V_1, a 6AH6 chosen for its very high transconductance.

The receiver is constructed in a 6" x 5" x 4" utility cabinet containing a built-in chassis. Although there is plenty of room for mounting the various components, a portion of the front lip of the box must be filed or cut out in order to clear the top of the power transformer as the receiver is placed in the cabinet. The rear lip should be similarly treated, to make way for the antenna terminals and the relay plug on the rear of the chassis. In addition, a 1¼" strip should be cut from the bottom edge of the rear panel to provide easy access to these same terminals.


The receiver's power supply contains a selenium rectifier, and so the reader may wonder why a plate transformer is employed in place of an ordinary a.c.-d.c. circuit. Since the unit is to be installed in a garage, a location with floors that are often damp, the shock hazard of an a.c.-d.c. circuit was felt to be too great. A filament transformer is required for the tubes, anyway. Consequently, the use of a transformer which includes a plate power winding adds little to the cost of the finished receiver.

Once plate current starts to flow in a thyratron, the grid loses control. Current through the tube will stop and the grid can only regain control if plate voltage on the tube is reduced to zero. Since an alternating voltage goes to zero many times per second, a.c. is applied to the plate of V_2, a 2D21. The a.c. is obtained from one half of the transformer high voltage secondary. The d.c. voltage for V_1, the d.c. amplifier, is taken from the other half of this winding.

A half-wave power transformer of the type found in TV boosters should *not* be used. If the plate currents for both tubes are drawn through the same winding, the voltage drop in the transformer, which results from the firing of the 2D21, will cause the plate voltage of the 6AH6 d.c. amplifier to vary. As a result, the receiver will be quite unstable and RL_1 will operate erratically if R_3 is set for maximum sensitivity.

Certain components must be carefully selected if top receiver perform-

www.americanradiohistory.com

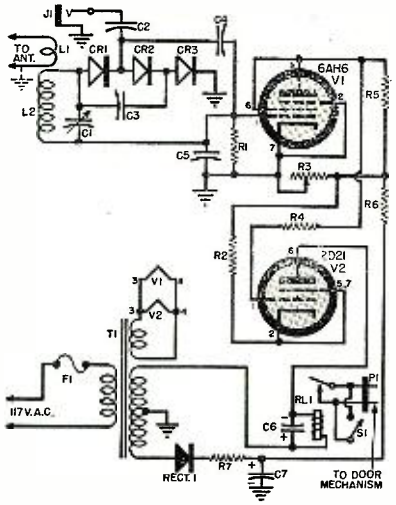

R_1—*5 megohm, ½ w. res.*
R_2—*1000 ohm, 1 w. res.*
R_3—*2000 ohm, 4 w. wirewound pot (Mallory A2MP)*
R_4—*1 megohm, ½ w. res.*
R_5—*2.7 megohm, 2 w. res.*
R_6—*25,000 ohm, 10 w. wirewound res.*
R_7—*100 ohm, ½ w. res.*
C_1—*3-30 μμfd. mica trimmer cond.*
C_2—*.01 μfd. disc ceramic cond.*
C_3, C_4, C_5—*.001 μfd. disc ceramic cond.*
C_6, C_7—*20 μfd., 150 v. elec. cond.*
J_1—*Open circuit phone jack*
P_1—*Male chassis connector for TV set a.c. line cord*
RL_1—*5000 ohm plate relay*
S_1—*S.p.s.t. toggle switch*
CR_1, CR_2, CR_3—*1N54 germanium diode*
$Rect._1$—*100 ma. selenium rectifier*
F_1—*½ amp fuse (Type 3AG)*
T_1—*Power trans. 125-0-125 v. @ 25 ma.; 6.3 v. @ 1 amp (Stancor PS-8416)*
L_1—*7 t. #20 en., 1" dia., 3/8" long (B & W "Miniductor" 3015)*
L_2—*8 t. #20 en., 1" dia., ½" long (B & W "Miniductor" 3015)*
V_1—*6AH6 tube* V_2—*2D21 tube*

Fig. 1. Schematic and parts list covering the receiver installed in the garage.

ance is to be expected. R_3, R_5, and R_6 should be purchased new and operated well below their maximum ratings. If you rely on the junk box for these particular items, or skimp on their size, the receiver may be so affected by temperature changes that the optimum setting of the sensitivity control will vary constantly.

Despite the low plate current required by the receiver, a 100 ma. selenium rectifier is employed. The large plate area of a 100 ma. rectifier does a good job of heat radiating, a factor which should be kept in mind when constructing a device that must operate reliably, 24 hours a day.

C_6 smooths out the ripples in the plate current of the 2D21 to keep the relay from chattering. It is an electrolytic condenser, and proper polarity, as shown in Fig. 1, should be observed.

No a.c. power switch is required because the receiver operates continuously. A switch on the front panel is provided, however, to bypass the relay and is normally left in the "off" position. It can be used to actuate the door opener for tests, if the receiver becomes inoperative, or when it happens to be inconvenient to provide a signal from the car transmitter. As a safety measure, a ½ amp fuse is wired in series with the primary of the power transformer.

The leads of the 1N54 germanium diodes should be kept long in order to reduce the possibility of damage to the crystals during the soldering process. By gripping the leads tightly with a pair of long nosed pliers, you can make sure that excessive heat from the iron is dissipated before it has a chance to do any harm. Three slightly anemic 1N54's in my junk box offer mute testimony to the dangers of short leads and careless use of a soldering iron.

The transmitter is built into a 5" x 3" x 4" utility box, a smaller version of the type used for the receiver. It contains a 2E30, instant heating beam pentode, with a regenerative crystal oscillator circuit operating in the 27 mc. Citizens Band. Power for the unit is furnished by a commercially-built *Mallory* VP-551 "Vibrapack."

If the transmitter is to be relatively free from TVI producing harmonics, a little care must be exercised during its construction. All paint should be removed from those points where the front and rear covers fasten to the case, thus insuring good electrical contact between adjacent metal parts. A low-pass filter consisting of L_1, C_1, and C_2 in the antenna lead reduces the strength of harmonics attempting to escape along this path, while C_8 and C_9 are needed to filter r.f. from the power leads. These few precautions will keep your televiewing neighbors happy and, at the same time, will insure compliance with the FCC's rule which requires spurious radiations from class C Citizens transmitters to be at least 40 db less than the carrier.

Only a couple of other pointers need be kept in mind while wiring the transmitter. The leads of C_8 and C_9 must be very short. The ground connections to C_3 and C_4 should go to the plates which are directly beneath the adjusting screws. This makes it possible to tune the transmitter without having to use an insulated screwdriver, because the adjustment screws are then almost at ground potential.

A radio-controlled garage door is rather novel and you will probably be kept busy showing yours to friends and neighbors. For this reason you'll want to do a neat construction job. After completing the transmitter and receiver, you can give them a really professional look by lettering the panels with decals. Best results will be obtained if you let the decals dry for at least 24 hours after application. Then, spray them with a light coat of clear lacquer. This procedure,

Fig. 2. Rear view of the receiver unit with the major components identified. Over-all dimensions are 6" x 5" x 4".


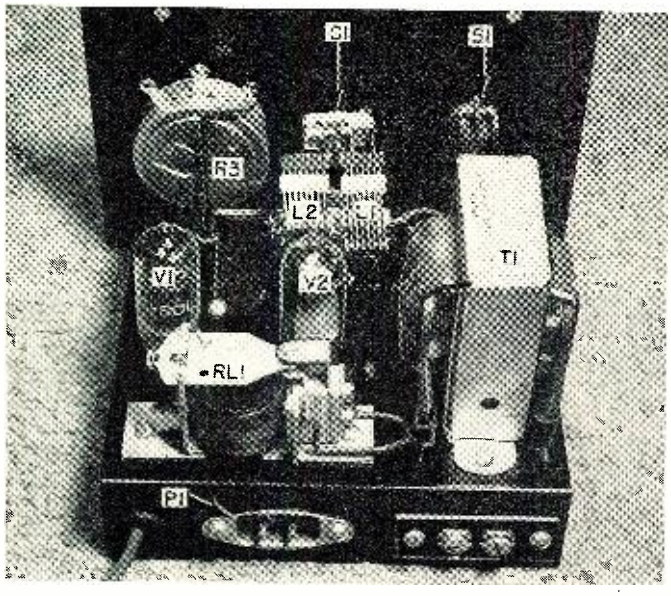


Fig. 3. Bottom view of receiver. Long leads on 1N54 crystal diodes prevent excessive heating while soldering.

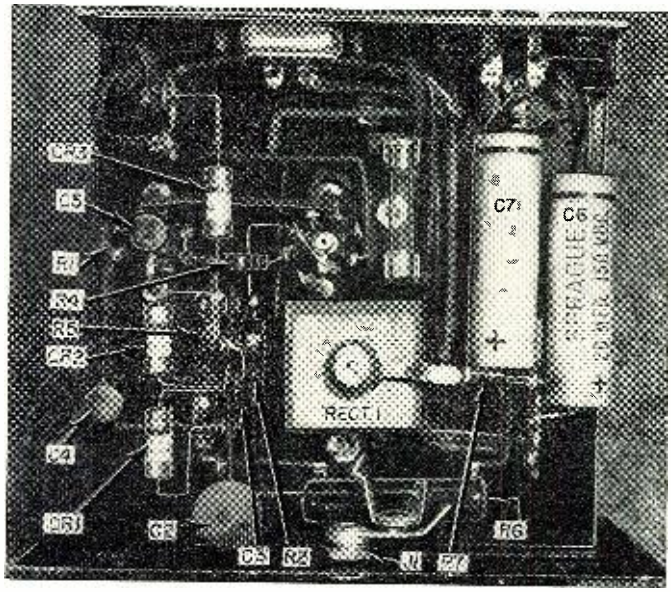

www.americanradiohistory.com



Fig. 4. Front panel view of receiver. Note slot for the screwdriver adjustment cut in shaft of the control, R_3.



Fig. 5. Over-all view of the transmitter. It is built in a 5" x 3" x 4" box and occupies little space in the car.

a trick that I learned from W8GBT, dissolves the transparent backing on which the letters are printed and makes them appear to become part of the panel, not just something that has been stuck on as an afterthought. At the same time, the decals are provided with a protective coating which keeps the letters from rubbing off.


Tuning the transmitter is simple, but the process must be carried out under the direction of someone holding a commercial operator's license issued by the FCC. Preliminary tests may be made with the unit out of its case and with no antenna connected. A milliammeter with a range of approximately 0-100 should be temporarily connected in series with the "B plus" lead. Apply "A" and "B" power and adjust C_4 until the plate current dips sharply, indicating oscillation. Tune a communications receiver to 27.255 mc. to make sure that the transmitter is oscillating at the crystal frequency. If it isn't, try another setting of C_4. A regenerative circuit is employed and if C_4 is incorrectly adjusted, the oscillator may take off on its own without regard for the frequency stamped on the crystal. Once the transmitter is working on the proper frequency, C_3 may be tuned for maximum brightness of PL_1, the output indicator. Since it is wired ahead of the low pass filter, PL_1 will glow even though no antenna is connected to the transmitter.

When it is found to be operating satisfactorily, the transmitter may be installed in the car. A handy place to mount it is on the inside of the firewall, as far up under the dash as possible, the "Vibrapack" being placed close to it. A control panel, with switch and pilot bulb, may then be mounted at a convenient spot under the dash and connected as shown in Fig. 7. Only a momentary signal is required to start the door opening mechanism. Thus, after the opener begins to function, the transmitter can be turned off. For this reason, the switch on the control panel may be of the simple push-button variety. I used a toggle switch merely because no suitable push-button could be found in my junk box.


Three different transmitting antenna systems are shown in Fig. 11. Greatest range will be obtained from an eight foot whip of the type used for ham mobile operation. Such an antenna will radiate sufficient energy to actuate the door opening mechanism at distances up to at least 150 feet. If the wife objects to such an arrangement, and she probably will, the next best system is to utilize a receiving-type auto antenna extended as high as possible. The longer it is, the better, but even 4 feet of antenna will produce an adequate signal 100 feet from the garage. Two antennas on a car, one for a broadcast receiver and the other for a radio-control transmitter may appear a bit ridiculous to some folks. Although it is possible to feed power from the transmitter into the antenna used by the car receiver, this procedure is not recommended because it is apt to reduce receiver sensitivity and introduce ignition and other unwanted noises.

A practical substitute for an external transmitting antenna is an 8½ foot insulated wire strung around the engine compartment. One end of this wire can be plugged into J_1 and the remainder fished through a small hole in the firewall. The wire should be kept an inch or so away from the body by supporting it on insulators. The small plastic ones used for TV lead-ins will work very well for the purpose. If possible, a portion of the wire should be placed between the radiator and its protective grille. The engine compartment is far from a perfect shield,

Fig. 6. (A) Method for wiring receiver to typical door opener requiring an external latching relay. (B) Hookup when an "Ebbert" door opener is used.

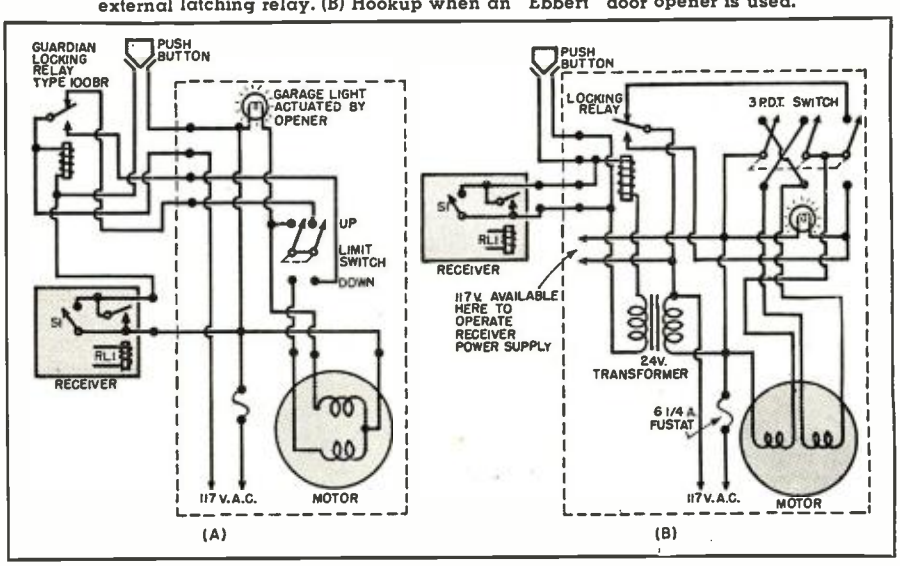

www.americanradiohistory.com

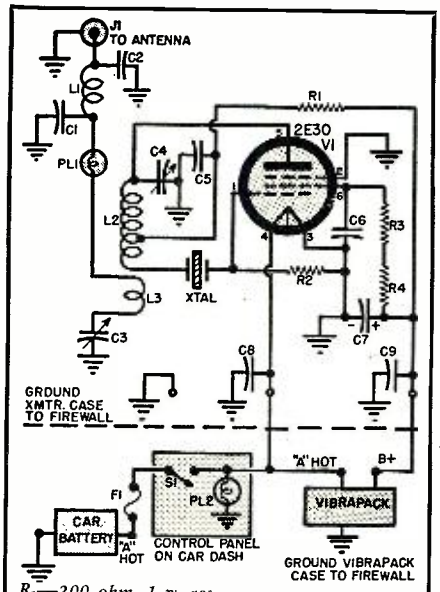

R_1—200 ohm, 1 w. res.
R_2—68,000 ohm, 1 w. res.
R_3—33,000 ohm, 1 w. res.
R_4—150 ohm, 1 w. res.
C_1, C_2—120 μμfd. tubular ceramic cond.
C_3-C_4—7.5-80 μμfd. dual mica padder (El-Menco Type 50)
C_5—.0047 μfd. disc ceramic cond.
C_6—.001 μfd. disc ceramic cond.
C_7—2 μfd., 450 v. elec. cond.
C_8, C_9—.01 μfd. disc ceramic cond.
J_1—Shielded phono pin jack
PL_1—Pilot light, 6 v. @ 250 ma. (#46)
PL_2—Pilot light, 6 v. @ 150 ma. (#40)
S_1—S.p.s.t. toggle switch
F_1—32 volt automotive fuse (Buss SFE9)
Xtal.—27.255 mc. Citizens Band crystal
Vibrapack—Mallory VP-551 vibrator power supply
L_1—5 t. #18 en., 3/8" dia., 1/2" long (B & W "Miniductor" 3006)
L_2—6 t. #18 en., 1" dia., 3/8" long, tapped 2 1/2 t. from grid end (B & W "Miniductor" 3014)
L_3—4 t. #18 en., 1" dia., 3/8" long (B & W "Miniductor" 3014)
V_1—2E30 tube

Fig. 7. Complete schematic and parts list for the transmitter unit installed in the car. The unit operates on the 27.255 mc. Citizens Band. See text on the FCC rules.

and as the wire is approximately a quarter-wave long, it will do a fairly good job of radiating. A simple arrangement of this kind will produce a usable signal 50 or more feet from the receiving antenna.

Some readers may feel that an operating range of 50 to 150 feet is not great enough. Experience, however, has shown that the door should not be controllable at distances beyond which it can be seen. After all, you wouldn't want to inadvertently close the door on a child or pet that might be sitting under it. While most electrically operated doors will stop automatically before applying enough pressure to kill a person, being pinned under such a device is certainly not an experience one would anticipate with pleasure. For safety's sake, operating range must be restricted.

After the transmitter is installed in the car, only slight retuning of the oscillator and antenna condensers will be required. C_3 and C_4 should both be adjusted for maximum antenna current as indicated by the brilliance of PL_1. It may be necessary to tune C_4 a little off the maximum setting in order to make sure that the crystal starts to oscillate immediately after plate and filament power are applied. The carrier frequency should now be rechecked, to make sure that it is within .04% of 27.255 mc.

With 200 volts from the "Vibrapack," plate current should be in the neighborhood of 25 ma., thus resulting in a power input of 5 watts, the maximum allowed to class C Citizens stations. When calculating input power, the plate current may be found by measuring the total "B" drain of the transmitter. Subtract from this amount the value of the screen current shown by a milliammeter temporarily connected in parallel with R_4. The result, for all practical purposes, will be the total plate current of the 2E30 tube.

The receiver can be installed close to, or even inside, the case of the opening mechanism. A 17-foot antenna, connected to the receiver *via* 75-ohm receiving twin-lead, should be mounted as near the front of the garage as possible. Although most of the antenna should be vertical, many garages are not 17 feet high. Consequently, it may be necessary to run a portion of the antenna horizontally, as shown in Fig. 12.

To tune the receiver, drive the car close to the garage and turn on the transmitter. Plug a pair of headphones into J_1 on the front panel of the receiver and, with an insulated screwdriver, adjust trimmer C_1 until the hum on the transmitter's carrier sounds loudest in the headphones. The capacity of transmitter condenser C_7 is purposely kept low in order that a certain amount of hum will remain on the carrier to aid in the tune-up process. Only enough capacity is used at this point to hold the transmitted bandwidth under 10 kc. C_7 must not be omitted, however, because without it the signal is very broad as a result of the hash kicked up in the "Vibrapack."

Power may now be applied to the receiver. Allow it to warm up for at least 15 minutes. With the transmitter off, advance the receiver sensitivity control, R_3, until the relay closes. Then, back off on R_3 just enough to let the relay open. When the car transmitter is turned on, the relay should now close. While the transmitter is still running, have someone back the car away until the relay opens. Readjust C_1 until the relay again closes. Back the car farther away, and again retune the trimmer. If you continue this process until the car is at least 50 feet away, the receiver will be peaked for maximum sensitivity.

In Fig. 1 a dotted line is drawn from one side of the antenna coil to the chassis ground. If you are inter-

(*Continued on page* 130)

Fig. 8. Rear view of transmitter with components identified.



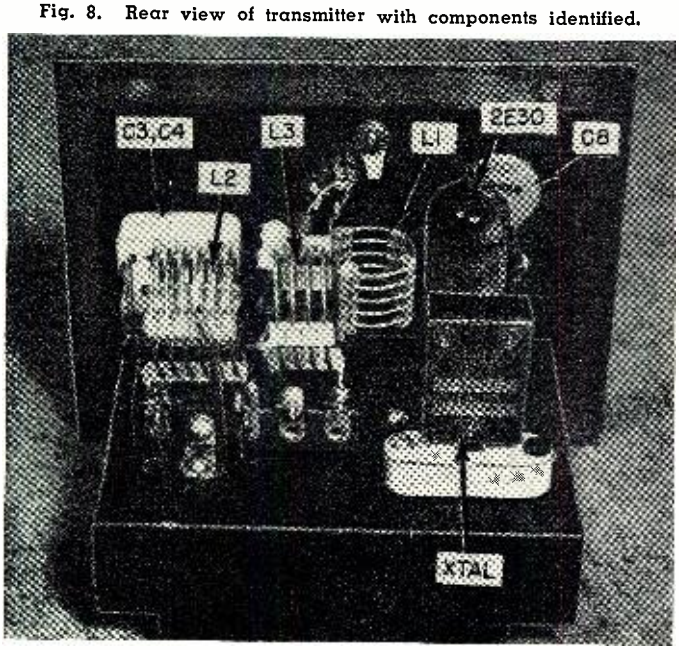


Fig. 9. Bottom view shows simplicity of underchassis wiring.

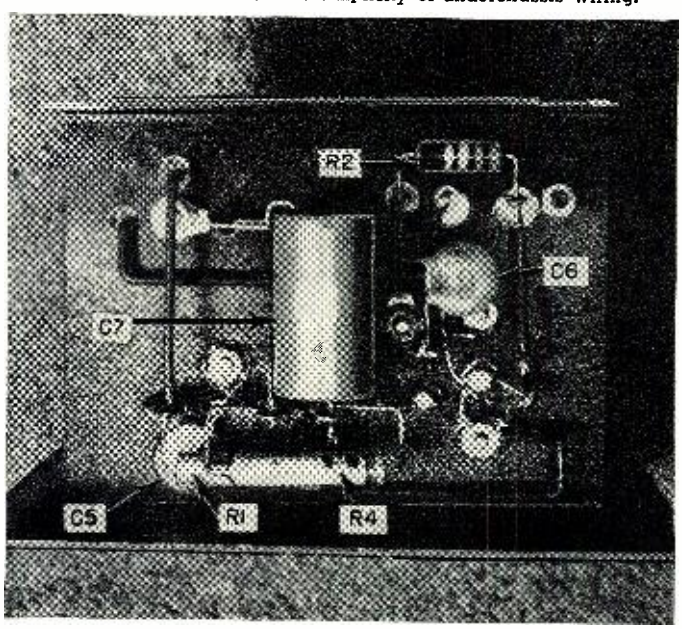


www.americanradiohistory.com


THE DU-201 Duette

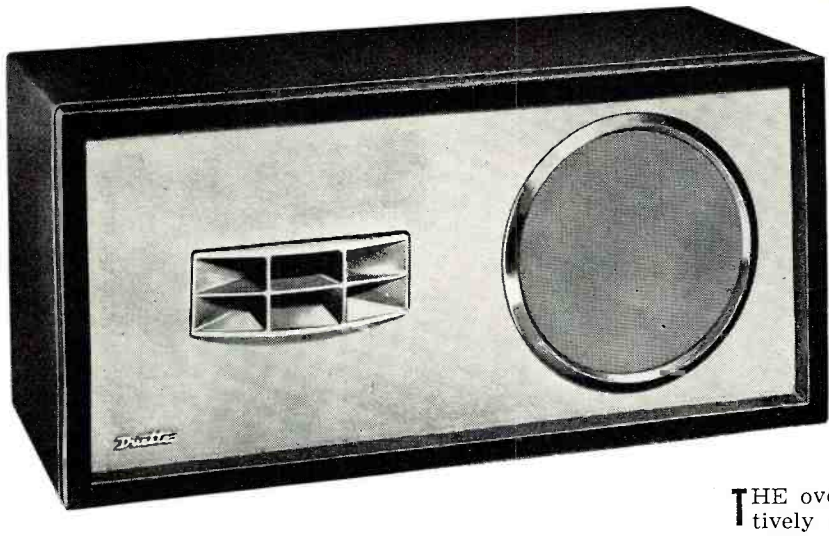


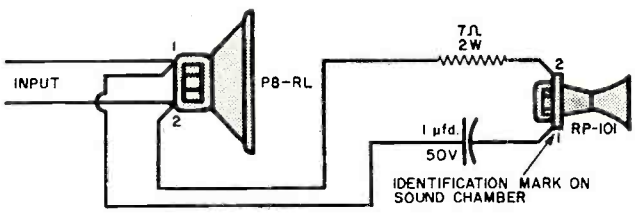
Designed by Jensen Mfg. Co., this unit is compact and easy to build. Its sound reproduction is excellent. Their P8-RL 8 inch speaker and RP-101 horn are used.




THE over-all construction of this cabinet is relatively simple. All dimensions are clearly indicated. One point that bears specific mention is that its theoretical operation is somewhat similar to that of the *R-J* cabinet in that the waves emanating from the rear of the speaker emerge through a port spaced between the speaker mounting board and the front panel of the cabinet. In this particular design the speaker mounting board is placed ½ inch from the front panel and the left side, looking at the top view of the diagram, is open, providing a port for the sound waves. —30—

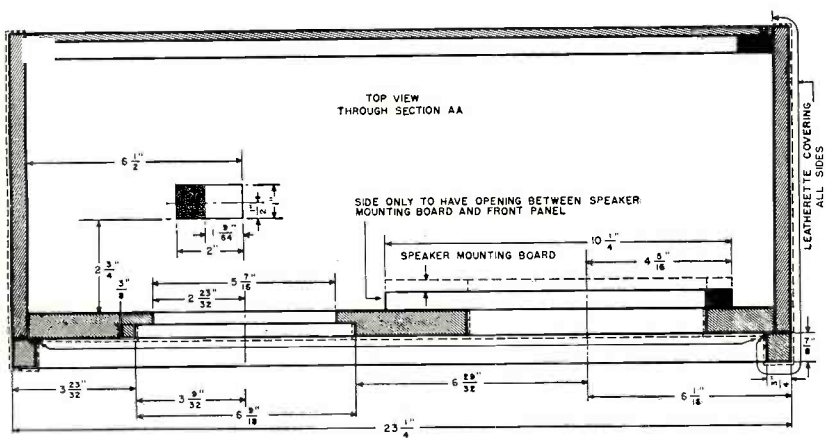

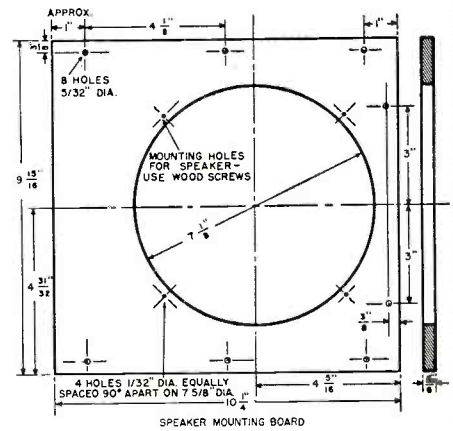

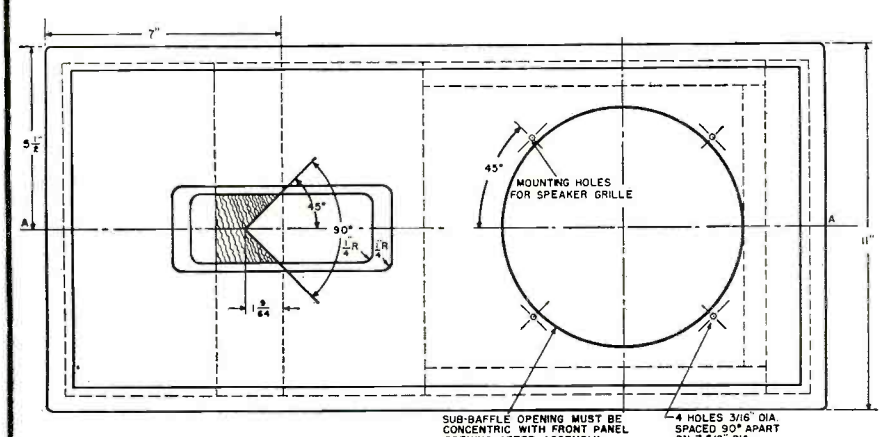

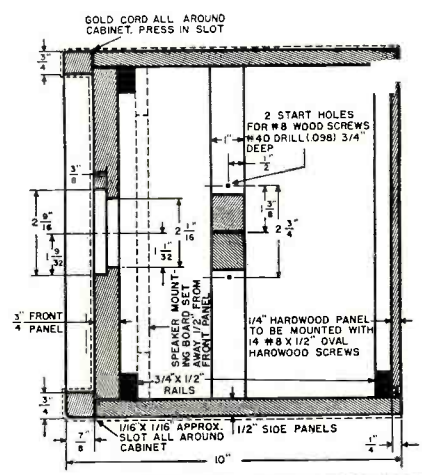

www.americanradiohistory.com

A SUBMINIATURE CODE PRACTICE OSCILLATOR

By
LOUIS E. GARNER, JR.

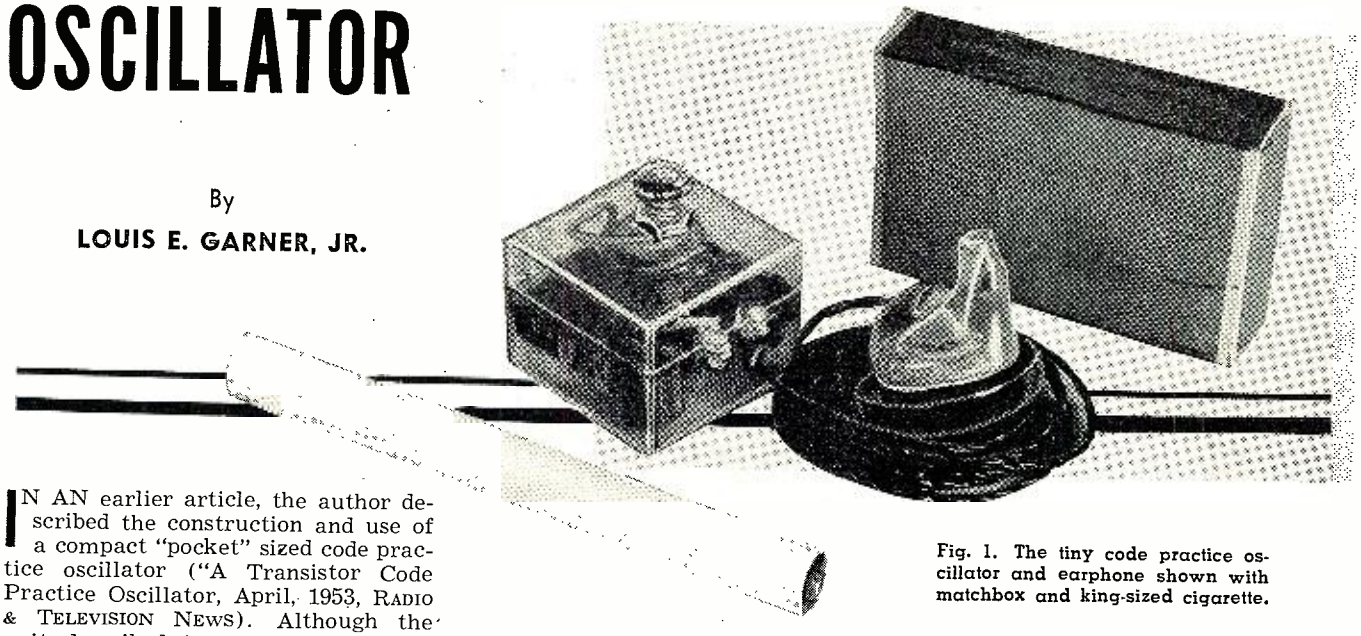


Fig. 1. The tiny code practice oscillator and earphone shown with matchbox and king-sized cigarette.

Although housed in a plastic box measuring just 7/8" x 1 1/8" x 1 1/8", this "watch pocket" unit really works

IN AN earlier article, the author described the construction and use of a compact "pocket" sized code practice oscillator ("A Transistor Code Practice Oscillator, April, 1953, RADIO & TELEVISION NEWS). Although the unit described in the earlier article was quite compact, no real attempt was made to "miniaturize" it . . . except for a hearing aid type battery and the transistor, all components used were standard-sized, and the unit was intended to be used with a regulation hand-key and standard earphones.

Nonetheless, the author received a good deal of good-natured kidding from friends about the size of the oscillator. Such remarks as "why not build a vest-pocket sized oscillator?" and "sure the oscillator is small, but the key and headphone take up too much space" were not uncommon.

Being human, a decision was quickly reached to build a code practice oscillator that was *really small* . . . one in which every part would be so compact that the entire practice set-up, oscillator, power source, key and headphone, could be easily fitted not only in a vest-pocket, *but even in a watch pocket* . . . and yet one which could be used for serious code practice, rather than a tiny "museum piece" destined to collect dust in a forgotten corner. It was also decided to design a unit that could be easily duplicated by any competent technician, using parts available through most of the larger wholesale electronic parts distributors.

The result is shown in Fig. 1 alongside a standard matchbox and a king-sized cigarette. The entire code practice set-up is shown here, including ing the "key," the oscillator, the power source, and the headphone. The key, oscillator, and power supply are all within the small plastic box, with the hearing aid type earphone (and its cord) shown alongside.

As can be seen by reference to the schematic diagram of Fig. 2, the *Raytheon* junction transistor (*"p-n-p"* type) is connected in a modified "tickler" feedback grounded-emitter audio oscillator circuit, with feedback provided by transformer T_1.

In operation, no current flows until the "key" is depressed . . . this eliminates the need for a separate "on-off" switch.

When the key is closed, d.c. can flow over two paths. Part of the current flows over the R_1-base-emitter path, establishing the base "bias" current for the transistor. Another part of the current flows over the path consisting of the primary of T_1 and the collector-emitter circuit of the transistor.

The current drain on the power source depends primarily on the size of R_1, not only because this resistor is in series with the base-emitter current path, but also because the amount of base current flow, in turn, determines the d.c. collector current flow. By keeping R_1 large (10 megohms in the author's model) the current drain is kept small and long battery life is insured. The actual battery life, in normal use, should approach the "shelf" life of the cell.

Variations in the primary current of T_1 are coupled, through magnetic lines of force, to the secondary winding, where they appear as an a.c. voltage. This signal, in turn, is applied through the d.c. blocking condenser C_1 to the base-emitter circuit of the transistor. The step-down turns ratio between the primary and secondary winding of T_1 permits matching the low input impedance of the transistor amplifier stage.

The signal is amplified by the transistor and re-applied to the primary of T_1. In this fashion, the basic condition of signal amplification with positive feedback is set up, and oscillation occurs.

The output audio signal is obtained through coupling condenser C_2 and applied to the *Brush* crystal earphone.

Construction Hints

All the electrical and mechanical components for this unit, except the earphone and its cord, are assembled in a small plastic box measuring 7/8" x 1 1/8" x 1 1/8". A somewhat larger case may be employed, if desired, and will make the wiring easier.

Although a metal case may be used in place of the plastic box, plastic is preferred as it simplifies insulation problems.

The general parts arrangement used by the author is apparent from the exterior and interior views of the oscillator, Figs. 1 and 4, respectively. Layout is not critical, however, and the builder may use any layout that will permit fitting the various parts compactly into the particular case used.

Mounting Parts: Only the two major components, the *"Sub - SubOuncer"* transformer and the *Mallory* RM-1000 mercury cell are actually "mounted." The other parts, *i.e.*, the transistor, the two condensers, and the resistor are allowed to more or less "hang free." Actually, the wiring is sufficiently compact so that the pressure between parts when the case is closed is adequate to hold them immobile.

The transformer is mounted by

www.americanradiohistory.com

cementing it to the case, using either *Duco* cement or general purpose *radio service cement.*

A small "L" bracket is used to hold the mercury cell in place, pressing it against the side of the case. This bracket also serves to make electrical contact to the outer shell (positive terminal) of the cell.

Wiring: Special care must be exercised when wiring the oscillator unit, both to prevent damage to the transistor and to the plastic case. Because so little space is available for components, it was not found practicable to use a socket for the transistor, and soldered connections had to be made directly to the transistor leads.

If the builder uses a somewhat larger case, so that a little "extra" space is available, it is suggested that a socket be used for the transistor, and that the transistor not be installed until all wiring is completed. A standard 5-pin subminiature tube socket is suitable for the CK722 transistor (only three pins are used.)

For best results, a small "pencil" type iron should be used. Keep the iron well-tinned and clean. Tin each wire or component lead prior to making the final connection, and use *quickly* soldered lap joints.

The transformer secondary leads (black) should be arranged so they can be easily interchanged should such a step prove necessary during final testing of the completed unit.

Once the oscillator wiring has been completed, *and the unit tested,* exposed connections may be effectively insulated by applying two or three coats of fingernail polish. Do not coat the negative terminal of the mercury cell, or the contact of the "key," however!

Assembling the "key": The construction of the miniature "key" is clearly visible in the photographs and in the side view sketch given in Fig. 3. Required parts are a small machine screw (preferably one having a smooth head), a small compression spring, and a nut to fit the machine screw used.

A small hole is drilled in the plastic case directly above the location of the mercury cell, and the key assembled so that contact is made with the negative terminal of the cell when the key is depressed.

Contact to the key is made by lap-soldering a wire to the side of the machine nut. This connection should be made *before* assembling the key to avoid melting the plastic case.

For best results the threads of the machine screw above the section where the nut fits on should be filed smooth. Otherwise, there is a certain tendency to catch on either the spring or the sides of the hole (in the case).

The side of the nut facing the battery should be filed smooth to insure good positive contact each time the key is depressed, as well as to reduce the thickness of the nut.

Testing And Adjustment

Once all wiring is completed, *carefully* check each connection to make sure there are no errors in wiring and that all joints are secure. Holding the earphone close to the ear, depress and release the "key" a few times.

If oscillation does not take place, try reversing the secondary (black) leads of the transformer (T_1). It is important that these leads be connected correctly to insure proper phasing of the feedback signal if oscillation is to take place.

Should it still be impossible to obtain operation, it may indicate that good electrical contact to the battery is not made when the "key" is depressed, or that the battery, transistor, transformer, or some other part is defective. Check each part in turn. Since it may prove somewhat difficult to properly check the transistor, all tests may be concentrated on other parts, *including the earphone and cord.*


In some instances it may be necessary to change the value of R_1. Should this be the case, temporarily connect a potentiometer or resistance substitution box in place of R_1, adjusting the value until oscillation takes place. Then install a fixed resistor having the appropriate value.

Because of the small size and construction of the "key" used this unit should not be used exclusively in learning the radiotelegraph code. A standard hand-key (which, if desired, may be connected in place of the miniature key) should be used for regular practice sessions in order to develop a good "fist." Use the miniature key only for supplementary practice.

When using the miniature key, try to simulate, as far as is practicable, the normal hand movements used with a standard hand-key. One technique is illustrated in Fig. 5.

The oscillator is held *lightly* between the thumb and middle finger, with the forefinger pressing on the "key." Code is sent using a normal wrist motion, *not the motion of the forefinger alone.* In order to do this, the thumb and middle finger (holding the oscillator) are allowed to flex slightly as the key is depressed.

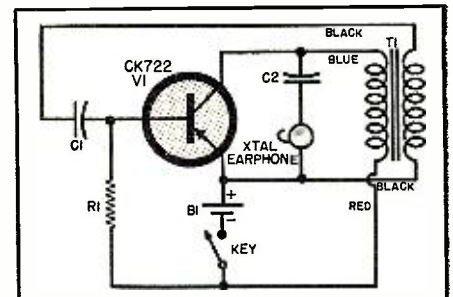A little practice will enable almost anyone to acquire this technique.—30—



R_1—*10 megohm, ½ w. res. (see text)*
C_1—*.002 μfd. disc ceramic cond.*
C_2—*.001 μfd. disc ceramic cond.*
B_1—*Mallory RM-1000 mercury cell*
T_1—*"Sub-SubOuncer" transformer (UTC #SS03)*
V_1—*"p-n-p" junction transistor (Raytheon CK722)*

Fig. 2. Complete schematic of the subminiature oscillator which uses a transistor.

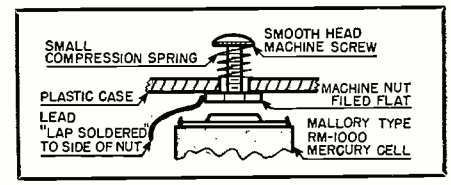


Fig. 3. Mechanical details for building the key to be used with the oscillator.

Fig. 4. Interior view of unit showing parts layout.


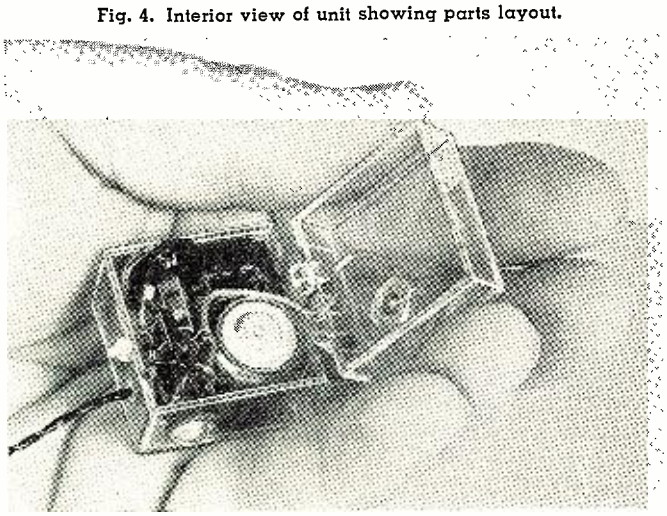



Fig. 5. Correct position for operating oscillator.

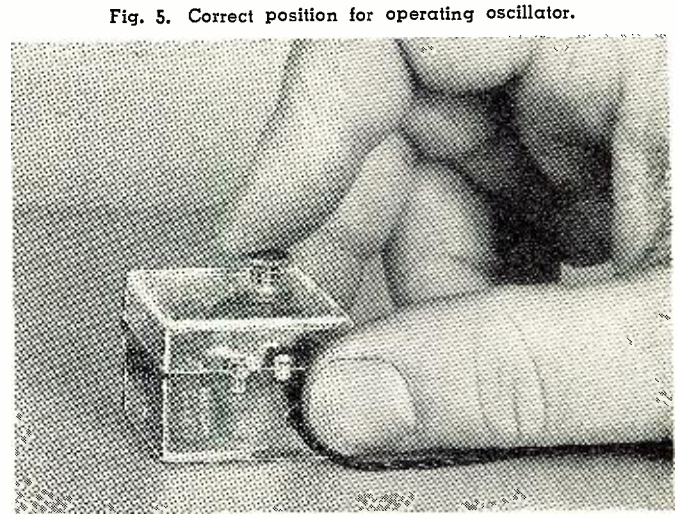

www.americanradiohistory.com

HIGH PERFORMANCE HEADPHONE RADIO

By IRVING GOTTLIEB

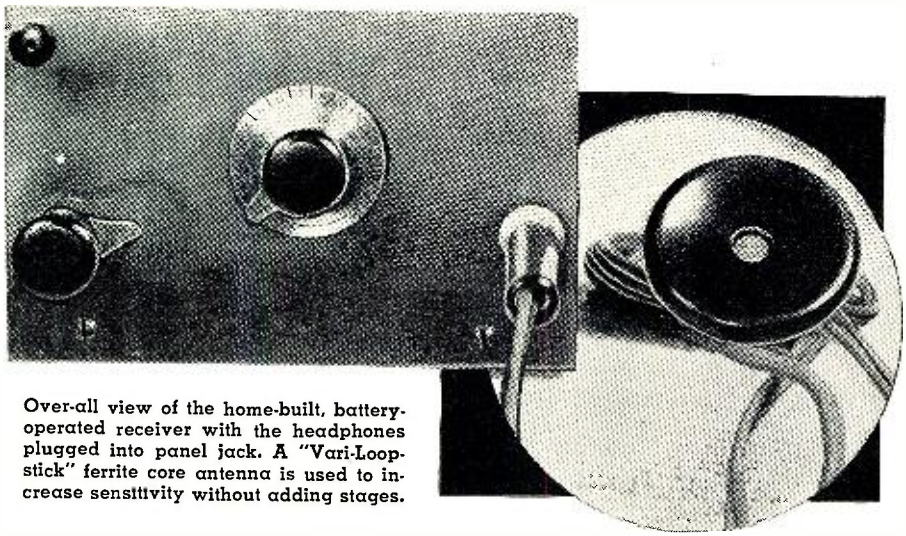

Over-all view of the home-built, battery-operated receiver with the headphones plugged into panel jack. A "Vari-Loopstick" ferrite core antenna is used to increase sensitivity without adding stages.

Construction details on a simple, compact receiver that uses a ferrite core antenna coil to increase sensitivity.


SIMPLE radio receivers which provide reception at headphone level retain a modicum of popularity, for there are occasions when solitary listening is desirable. Such sets are enjoyable as bedside radios in the home or in the hospital. They are welcome as a means of enabling the junior members of the family to tune in their individual program favorites and, in general, whenever others would be disturbed by a blaring speaker. Then too, these sets are often nice to take along on hiking and field trips.

Compromises in the performance of small radio receivers have been accepted as inherent in the simplicity of the circuit arrangement. The common drawbacks have been broad tuning, lack of sensitivity, and weak reception. Additionally, the need for a long and cumbersome antenna has frequently proved an inconvenience. It is not necessary to resort to relatively complex multi-tube circuits in order to achieve a high order of performance. The utilization of a recently developed circuit component in a simple single tube hook-up results in an inexpensive receiver with excellent sensitivity and selectivity. A four-foot vertical rod antenna will bring in about the same number of stations that can be heard with the ordinary four-tube table radio.

This has been made possible by the new high *"Q"* ferrite core antenna coils intended as a substitute for the much bulkier loop antenna commonly used in a.c.-d.c. radios. The higher the *"Q"* of a resonant circuit, the higher the e.m.f. developed across its terminals, other things being equal. The higher *"Q"* likewise implies sharper tuning response. Thus, an appreciable increase in the *"Q"* of the resonant circuit can be expected to pep up performance in much the same manner as the addition of a tuned r.f. amplifier. This is indeed the case and the experimenter who harbors any fixations regarding alleged limitations of simple receivers is due for a pleasant surprise:

The schematic diagram, Fig. 1, is a conventional circuit. From casual inspection one would not deduce anything unusual about it. A small amount of positive feedback is used in


(*Continued on page* 172)

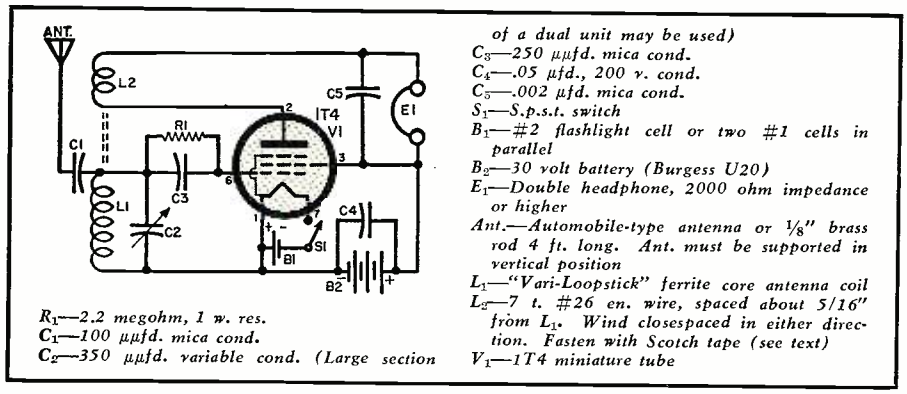


R_1—*2.2 megohm, 1 w. res.*
C_1—*100 μμfd. mica cond.*
C_2—*350 μμfd. variable cond. (Large section of a dual unit may be used)*
C_3—*250 μμfd. mica cond.*
C_4—*.05 μfd., 200 v. cond.*
C_5—*.002 μfd. mica cond.*
S_1—*S.p.s.t. switch*
B_1—*#2 flashlight cell or two #1 cells in parallel*
B_2—*30 volt battery (Burgess U20)*
E_1—*Double headphone, 2000 ohm impedance or higher*
Ant.—Automobile-type antenna or 1/8" brass rod 4 ft. long. Ant. must be supported in vertical position
L_1—*"Vari-Loopstick" ferrite core antenna coil*
L_2—*7 t. #26 en. wire, spaced about 5/16" from L_1. Wind closespaced in either direction. Fasten with Scotch tape (see text)*
V_1—*1T4 miniature tube*

Fig. 1. Complete circuit diagram of headphone set. A miniature 1T4 tube is used.

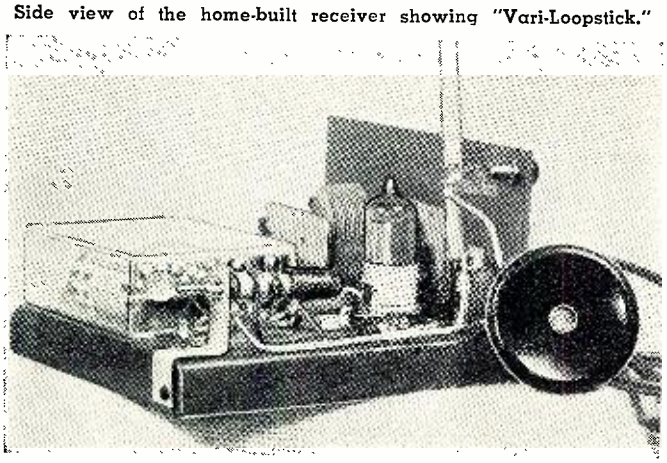Side view of the home-built receiver showing "Vari-Loopstick."



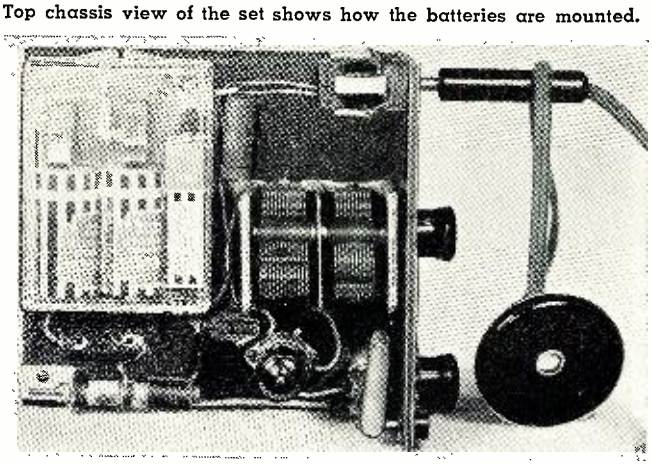Top chassis view of the set shows how the batteries are mounted.



www.americanradiohistory.com

AMATEUR'S 4-TUBE MINIATURE SUPERHET

By
PAUL POPENOE, JR.
W6IWM

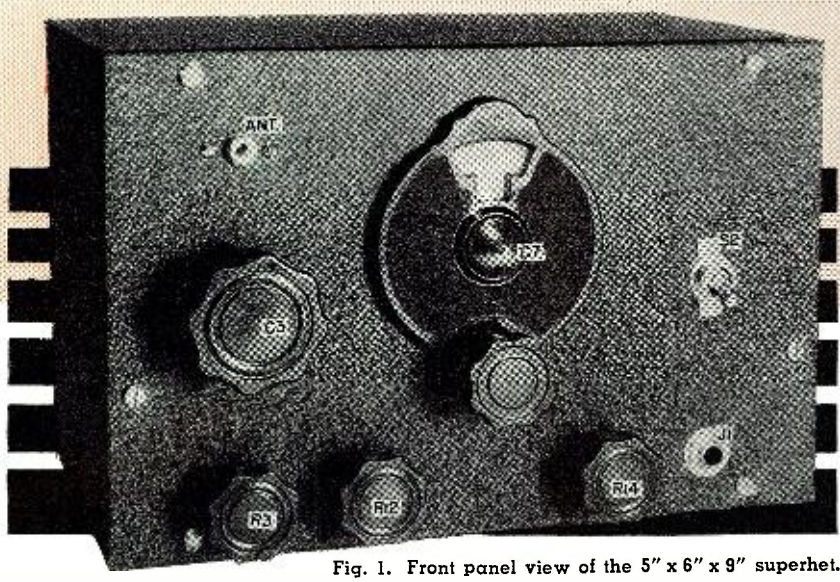


Fig. 1. Front panel view of the 5" x 6" x 9" superhet.

A compact unit which tunes the 40 and 80 meter bands without bandswitching and has its own self-contained power supply.

WHILE articles on the construction of amateur transmitters appear quite frequently in the radio magazines, there is a general dearth of constructional articles on amateur receivers. This is especially true of small portable receivers such as might be desired for use with a midget transmitter. The regenerative receiver is probably still widely used for portable work. However, those amateurs who have spent long hours operating on today's crowded bands realize the importance of a stable receiver with high selectivity, such as is obtainable only in a superhet.

The receiver described in this article was designed specifically with the amateur radio operator in mind and contains no features which are not of use to the ham. Forty and eighty meters are the only bands covered, and no bandswitching or plug-in coils are required. The set uses four dual-purpose tubes in a double conversion superhet circuit with regenerative mixer and detector stages; it is small, being contained in a 5 x 6 x 9-inch steel utility box; and it has a self contained selenium rectifier power supply.

Another factor that should please the ham is the low cost of this receiver. Using first quality components throughout, the cost is approximately $40. At that price many hams could afford this as a second receiver in the shack or as a good little portable to take traveling. On the other hand, some may even find this set desirable for their main receiver since it has performance equivalent to receivers having from eight to ten tubes and costing many times as much.

Is it difficult to build? This is the first question that will come to the mind of many amateurs who have never built a receiver, or at least never a superhet. While this set is not one that should be recommended to a Novice for his first receiver (although it makes a dandy Novice job), any person who has sucessfully constructed several pieces of electronic equipment and who has a fair knowledge of high frequencies should have no difficulty in constructing this set. It is certainly much less complicated in design and circuitry than many of the amateur transmitters published in the radio magazines. Also, it should be pointed out that a lot of specialized test equipment is not required for aligning this set. The only instruments used in the original alignment were a grid-dip meter and a communications receiver. One could probably get by with less.

Circuit Description


As shown in the diagram, Fig. 2, the input stage uses a type 6X8 miniature triode-pentode tube as oscillator and mixer. The mixer, using the pentode section of the tube, is regenerative with feedback obtained from a cathode tap on L_1. Regeneration is controlled by screen voltage variation from potentiometer R_3. Tuned circuit L_1-C_3 covers the entire range from 3.5 megacycles to 7.3 megacycles in order to obviate the need for bandswitching in the mixer circuit. A mica compression trimmer condenser is used to couple the antenna directly to the tuned circuit and may be adjusted for different lengths of antenna. The antenna lead is brought out to the front panel in a shielded plug which may be used to connect a fixed tuned converter for coverage of other bands.

The high frequency oscillator, using the triode section of the 6X8, covers a frequency range of 5000 to 5800 kilocycles. The portion of the tuning range from 5000 to 5500 kc. beats with incoming signals in the band 3500 to 4000 kc. to give a mixer output frequency of 1500 kc., the first i.f. frequency. Likewise, the oscillator range from 5500 to 5800 kc. gives an i.f. of 1500 kc. when mixed with signals in the 7000 to 7300 kc. band. The oscillator tuning condenser, C_7, is the main tuning control and is connected to the vernier dial on the panel. The eighty-meter band covers about two thirds of the dial and forty meters, one third. An iron slug-tuned coil, L_3, is used in the oscillator circuit in order that the inductance may be adjusted to allow the tuning condenser to cover the proper range.

Control grid injection of the oscillator signal into the mixer is used. The condenser shown in the diagram as C_4 consists of a length of hookup wire, one end of which is connected to the oscillator grid and the other insulated end is wrapped two times around the wire going to the mixer grid. This arrangement was found to give adequate oscillator injection with no trace of pulling as the mixer tuning condenser was varied. The builder may wish to experiment with this to get greatest conversion efficiency; however, the two turns of wire should prove satisfactory in nearly all cases.

A frequency of 1500 kc. was chosen for the first intermediate frequency for two principal reasons. First of all, 1500 kc. i.f. transformers were readily available at the local radio dealers and secondly this frequency allowed coverage of both the 40- and 80-meter bands without changing oscillator coils. Another advantage is that the

www.americanradiohistory.com

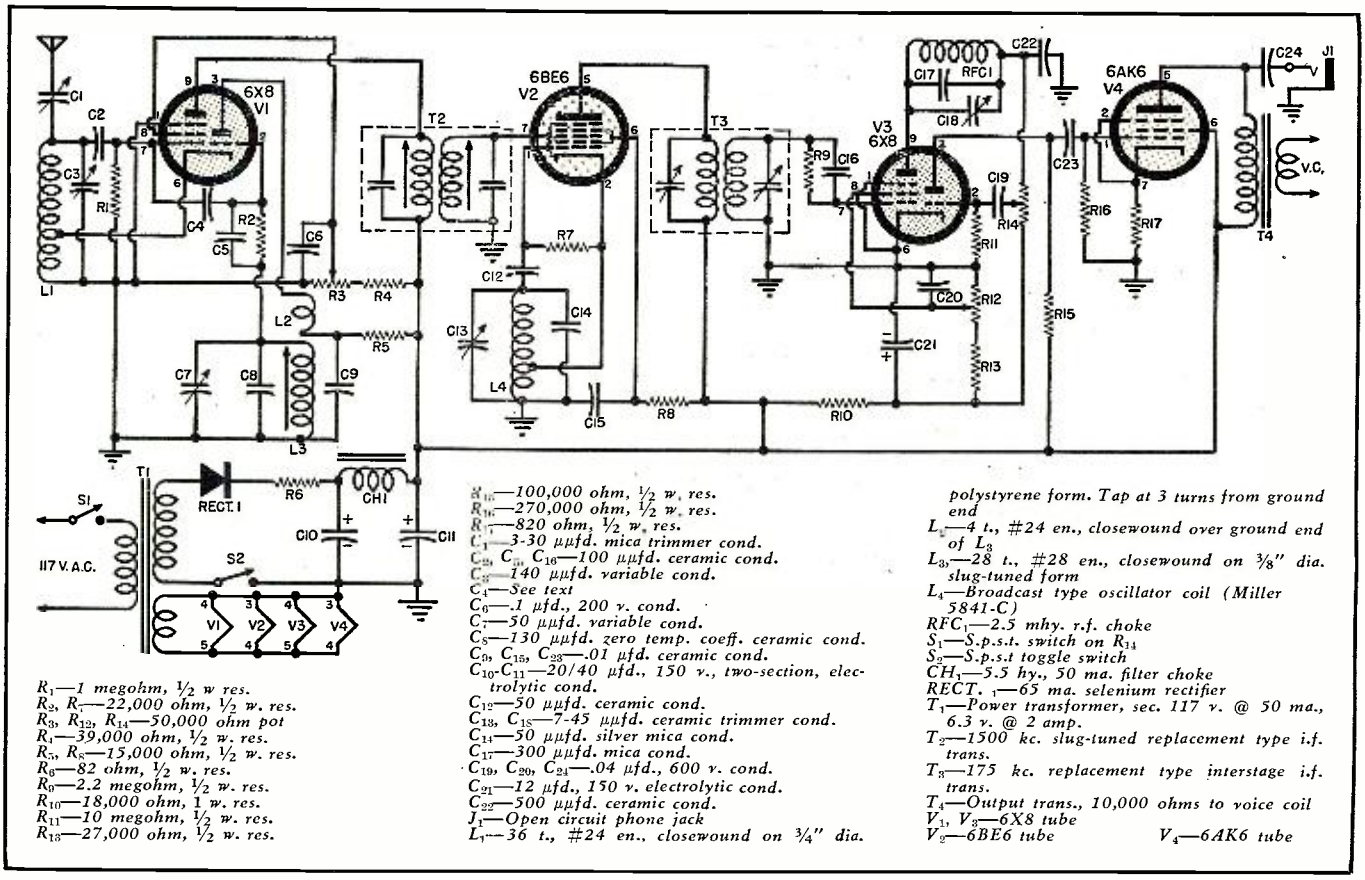

R_1—*1 megohm, ½ w res.*
R_2, R_7—*22,000 ohm, ½ w. res.*
R_3, R_{12}, R_{14}—*50,000 ohm pot*
R_4—*39,000 ohm, ½ w. res.*
R_5, R_8—*15,000 ohm, ½ w. res.*
R_6—*82 ohm, ½ w. res.*
R_9—*2.2 megohm, ½ w. res.*
R_{10}—*18,000 ohm, 1 w. res.*
R_{11}—*10 megohm, ½ w. res.*
R_{13}—*27,000 ohm, ½ w. res.*
R_{15}—*100,000 ohm, ½ w. res.*
R_{16}—*270,000 ohm, ½ w. res.*
R_{17}—*820 ohm, ½ w. res.*
C_1—*3-30 μμfd. mica trimmer cond.*
C_2, C_{15}, C_{16}—*100 μμfd. ceramic cond.*
C_3—*140 μμfd. variable cond.*
C_4—*See text*
C_6—*.1 μfd., 200 v. cond.*
C_7—*50 μμfd. variable cond.*
C_8—*130 μμfd. zero temp. coeff. ceramic cond.*
C_9, C_{15}, C_{23}—*.01 μfd. ceramic cond.*
C_{10}-C_{11}—*20/40 μfd., 150 v., two-section, electrolytic cond.*
C_{12}—*50 μμfd. ceramic cond.*
C_{13}, C_{18}—*7-45 μμfd. ceramic trimmer cond.*
C_{14}—*50 μμfd. silver mica cond.*
C_{17}—*300 μμfd. mica cond.*
C_{19}, C_{20}, C_{24}—*.04 μfd., 600 v. cond.*
C_{21}—*12 μfd., 150 v. electrolytic cond.*
C_{22}—*500 μμfd. ceramic cond.*
J_1—*Open circuit phone jack*
L_1—*36 t., #24 en., closewound on ¾" dia. polystyrene form. Tap at 3 turns from ground end*
L_2—*4 t., #24 en., closewound over ground end of L_3*
L_3—*28 t., #28 en., closewound on ⅜" dia. slug-tuned form*
L_4—*Broadcast type oscillator coil (Miller 5841-C)*
RFC_1—*2.5 mhy. r.f. choke*
S_1—*S.p.s.t. switch on R_{14}*
S_2—*S.p.s.t toggle switch*
CH_1—*5.5 hy., 50 ma. filter choke*
$RECT._1$—*65 ma. selenium rectifier*
T_1—*Power transformer, sec. 117 v. @ 50 ma., 6.3 v. @ 2 amp.*
T_2—*1500 kc. slug-tuned replacement type i.f. trans.*
T_3—*175 kc. replacement type interstage i.f. trans.*
T_4—*Output trans., 10,000 ohms to voice coil*
V_1, V_3—*6X8 tube*
V_2—*6BE6 tube* V_4—*6AK6 tube*

Fig. 2. Complete schematic diagram of the 4-tube ham superhet. It uses standard parts and can be built for about forty dollars.

image frequency is 3000 kc. away from the frequency being tuned. With the high selectivity of the regenerative mixer this means that little or no difficulty should ever be encountered with image interference.

A miniature slug-tuned replacement type i.f. transformer is used at T_2. This couples into a 6BE6 second converter tube which is used in a standard pentagrid circuit. In order to shift the first intermediate frequency to a second intermediate frequency of 175 kc., the oscillator section operates on a frequency of 1675 kc. An ordinary midget broadcast type oscillator coil with tap suitable for use with 6BE6 was used here. While the oscillator could operate on 1325 kc. and still give the required i.f., the higher frequency is preferable since no harmonics of 1675 kc. fall within the bands used. It is essential that the decoupling filter, R_8-C_{15}, be used since without it considerable trouble will be encountered with "birdies."

The second intermediate frequency of 175 kc. was again chosen with the ready availability of components in mind. In this case a miniature i.f. transformer was not available so a regular sized interstage unit was used. The 175 kc. frequency has another advantage in the higher numerical selectivity realized at the lower frequencies.

Regeneration is used in the second detector circuit both to improve overall selectivity of the set and to provide a source of the local oscillations required for beat frequency reception of c.w. signals. The pentode section of a 6X8 tube is employed as a grid leak detector. Feedback is obtained by means of a tuned-plate, tuned-grid oscillator circuit using RFC_1, C_{17}, and C_{18} as tuning elements in the plate of the detector. This tuned circuit requires no special elements as RFC_1 is merely a 2.5 millihenry r.f. choke resonated to the i.f. frequency of 175 kc. by means of the two condensers. Although this arrangement has the disadvantage of causing a slight detuning of the i.f. stage, it has the very important advantage of not requiring any alteration of the i.f. transformer, T_3. Control of regeneration is accomplished by means of screen voltage variation using the 50,000 ohm potentiometer, R_{12}.

After the signal has been demodulated in the pentode section of the 6X8, it is amplified in the triode section. Grid leak bias is used, so it is necessary to have the volume control, R_{14}, in the plate lead of the detector.

The signal is further amplified in the output stage of the set, which uses a 6AK6 tube. For space saving purposes no cathode bypass condenser has been used in this stage. If greater audio gain is required, the constructor may add a 25 microfarad, 25 volt, electrolytic condenser from the cathode of the 6AK6 to ground. The output transformer, T_4, is an ordinary replacement type unit. Since the original thought was to use headphones exclusively, the voice coil winding of the transformer is not shown connected in the diagram. It may be brought out to a jack, however, in case it is desired to use a dynamic speaker.

For reasons of convenience and portability a selenium rectifier power supply has been built into the set. Although this arrangement is quite satisfactory, it is virtually impossible to get rid of all a.c. hum. It is therefore suggested that, where feasible, the power supply be constructed as a separate unit external to the receiver. One precaution that must be taken to insure a low hum level is to make sure that one side of the heater circuit is grounded as shown on the diagram.

The main power switch, S_1, is included on the volume control, R_{14}. Switch S_2 is a standby switch to turn off the high voltage supply during periods of transmission.

Construction

Mechanical construction of the set should be self explanatory from an examination of the photographs. However, certain features will be pointed out. The set is built on a 1½ x 4½ x 8 inch aluminum chassis and contained in a 5 x 6 x 9 inch steel utility box. In order that the chassis may be moved freely in and out of its cabinet, it is necessary to remove the bottom flange of the utility box and make the side flanges slightly narrower. The panel is connected directly to the chassis and is held in place by the three potentiometers and phone jack located underneath the chassis. Mounted on the panel above the chassis are the mixer tuning con-

www.americanradiohistory.com

denser, the oscillator tuning condenser, and the standby switch. The antenna input jack is mounted directly above the mixer tuning condenser. The oscillator tuning condenser, C_7, is the main tuning control and is connected to the vernier dial.

The top view photograph of the set shows the general arrangement of tubes and transformers. All parts have been located to provide for short leads in the r.f. wiring. The audio output transformer is located at the opposite side of the chassis from the power transformer in order to prevent inductive coupling between the two.

The general arrangement of the wiring is shown in the bottom view of the set. It is desirable to employ miniature components as much as possible. Although the chassis size is small, the set is not overcrowded and no difficulty should be encountered in its construction.

Since each constructor will have his own techniques, wiring methods will not be discussed here except to mention the necessity for following good practices, such as making all r.f. leads as short as possible. Because of the design features no difficulty should be encountered with extraneous feedback, which often causes serious difficulty to the home constructor.

Alignment

The first alignment procedure to be suggested here requires the use of a standard modulated signal generator. The first circuit to adjust is the second i.f. transformer. With modulation on, the signal generator should be tuned to 175 kc. and its output coupled to the grid of the 6BE6. With the regeneration control, R_{12}, at a low setting, the transformer, T_3, should be adjusted for maximum output from the set. Next, modulation should be removed from the signal generator and the regeneration control should be advanced to about the half way point. Condenser C_{18} should be adjusted so the detector will oscillate at a point near zero beat with the 175 kc. signal. If no oscillation is obtained, various settings of the regeneration control may be tried. If there is still no oscillation, or if it is not possible to tune close to zero beat, it will be necessary to add or remove capacity from C_{17} until C_{18} will tune RFC_1 to 175 kc. This circuit is a sure-fire oscillator, and no trouble should be encountered with inadequate feedback.

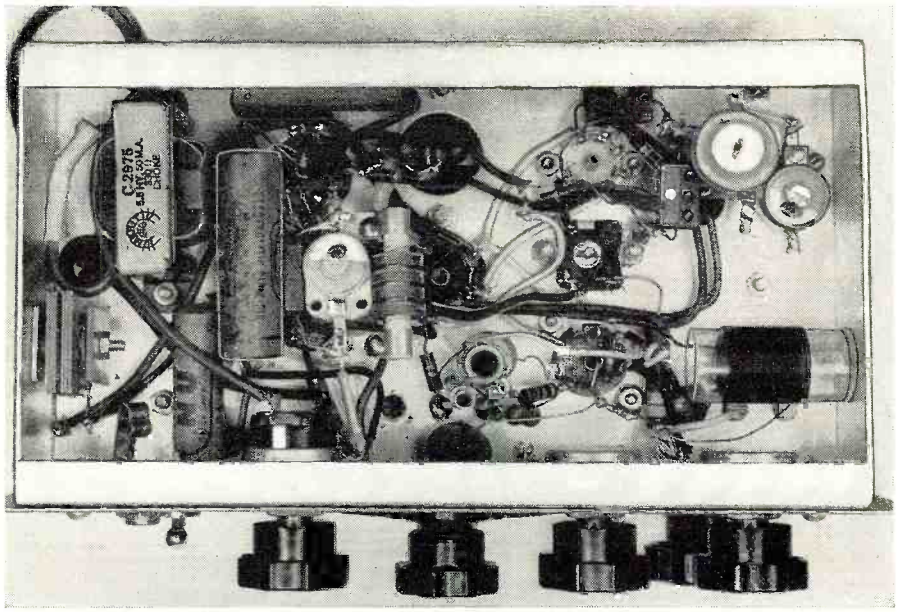


Fig. 3. Under chassis view. Miniature components are used throughout.

The next step in the alignment is the adjustment of the first i.f. transformer, T_2, and the setting of the frequency of the second oscillator. The signal generator is tuned to 1500 kc. and is connected to the antenna side of the mixer coil. Adjust C_{13} to give a second oscillator frequency of 1675 kc. This may be done by tuning the condenser while listening for the signal. The signal will be heard at two different points. It is essential that the higher frequency point, corresponding to 1675 kc., be selected. Next, the slugs in T_2 should be adjusted to pass maximum signal at 1500 kc.


The final step of alignment consists of adjustment of the mixer and first oscillator. The slug in the first oscillator coil is adjusted to give a range of approximately 5000 to 5800 kc. in the first oscillator tuning control, C_7. With the mixer regeneration control retarded and C_7 set to maximum capacity, tune the signal generator to 3500 kc. and connect it to the antenna terminal. Then adjust the slug in L_3 until a signal is heard; the oscillator should be operating on 5000 kc. With the signal generator set to 4300 kc. the signal should be heard when C_7 is nearly at minimum capacity, corresponding to an oscillator frequency of 5800 kc. If it is not possible to cover the full range, it may be necessary to decrease slightly the size of C_8 and make a corresponding increase in the inductance of L_3. With the signal generator output reduced and loosely coupled to the input of the set, the mixer tuning may be checked. Advance the mixer regeneration control until a slight pop is heard and then retard it to just below this point. It should be possible to peak up signals in the range 3000 to

(*Continued on page* 114)

Fig. 4. Rear view of receiver with component parts identified.



Fig. 5. Top view of chassis illustrates the uncrowded layout.

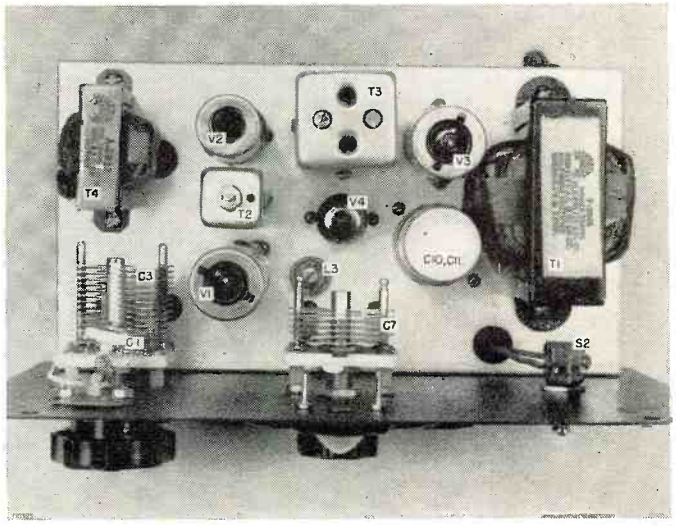

www.americanradiohistory.com

QRZ MOBILE

By
LEON A. WORTMAN, W2LJU



Fig. 1. Author holds compact radiotelephone rig. Controls are identified in text.

Bandswitching for 10, 20, and 75 meters, push-to-talk operation, and circuit metering are features of this rig.

"AND DON'T tell me you're only using an 8-foot whip! . . . not with the signal you're putting in here, old man." That's the kind of report that warms a ham's heart, when he's running low power into his home-brewed mobile rig. The mobile-ing aspect of ham-ming has really caught on and the same guy who has concentrated on running a full kilowatt into a rhombic is getting a brand new kick out of an old hobby by discovering that he can "work out" to lots of DX with only 20 or 25 watts and a length of steel rod.

The bug hit me, hard, after giving loads of S9 reports and tape recorded QSL's to mobiles in all states and DX countries. It looked like another way to have fun with the gear and, although the XYL insists I went mobile only because I wouldn't tear myself away from the rig long enough to drive her to market, it has really given us both hours of good fun. I offer the following detailed recipe for my "home-brew" to any ham who is thinking of going mobile, in the hope that some of the ideas employed in this rig may help clarify and simplify some ideas of his own. This rig is a complete and compact radiotelephone transmitter with all the features of a big rig, containing bandswitching for 10, 20, and 75 meters in all stages, push-to-talk operation, circuit metering, and convenient controls.

In planning any installation, one must first attempt to predict many of the problems which may arise, thereby constructing the equipment in such a fashion as to preclude all anticipated difficulties. For example, I was very much concerned about the ability of my automobile generator to maintain the serviceability of the battery after an extended period of mobile operation. Coasting transmitter tube filaments can really "whiff up the juice" during standby . . . 20 to 30 watts of wasted power which, as any one who has left the car radio on overnight will tell you, can stimulate a call for a tow! Not being a traveling salesman and using the car mostly on weekends I couldn't depend on the generator for recharges. Living in an apartment house in the city, I had no power facilities for a battery charger. I didn't want the expense of a "police-type" low cut-in generator. The anticipated difficulty then was dead battery troubles. The solution to this problem seemed to be instant-heating filament type tubes for the rig, tubes which illuminate and draw filament current *only during transmit periods*. So, with the exception of the oscillator tube, all tubes are completely shut off during standby. The oscillator tube is a heater type tube for two reasons: minimization of drift due to sudden heating conditions, and simplicity of harmonic oscillator design.

The r.f. lineup is a 6AQ5 harmonic oscillator capacity coupled to a 5516 final amplifier. The audio modulator is a carbon button mike transformer to push-pull 2E30's. The modulator operates in class "B" for maximum efficiency and minimum plate current drain consistent with good audio quality. It supplies more than sufficient audio power to fully modulate the final r.f. amplifier without making it necessary to shout one's head off. The 30-volt bias for the modulator is obtained from a small hearing aid type "B" battery. The battery is mounted on the underside of the chassis with a clamp such as is used for mounting electrolytic condensers. Because of the exceedingly small and intermittent current drain while transmitting, the battery's life is almost as long as its shelf life.

Like nine out of ten hams who "roll their own," I always expect to have to yank out an installation regularly in anticipation of troubleshooting. Whether or not we eventually have to do any troubleshooting isn't important at the moment. What is important is planned accessibility to the rig and its "innards." Therefore, the mechanical layout of this rig and the technique of its installation was decided upon as shown in the accompanying illustrations. The entire rig is built into a grey hammertone finish 5" x 6" x 9" aluminum box with removable top and bottom cover plates. An aluminum chassis was bent, using a vise for the purpose, to fit the inside 6" x 9" dimensions of the box. The chassis is made to be approximately 1" short in its longest dimension, with the short end at the front of the box to make adequate room for mounting the front panel controls. Half-inch flanges on the sides of the chassis enable it to be rigidly mounted. The parts and tube layouts are not critical so an actual template plan is not included here. Simply make certain to use the shield between the oscillator and the final tank coils. This minimizes the mutual coupling between the two circuits, eliminating this possibility as a cause for the final stage to behave as a tuned-


www.americanradiohistory.com

plate, tuned-grid oscillator. The shield for the oscillator tube is included in the mechanical design for the same reason. The modulator tubes should also be shielded to minimize their ability to pick up r.f. energy due to their proximity to the final amplifier. No other shielding was found necessary in the rig. Adequate r.f. bypassing is given by the condensers shown in the diagram. The small antenna changeover and filament power relay should be mounted on the side of the box midway between the coax antenna connectors and the final tank coils to minimize losses and maintain high efficiency.

The bandswitch is assembled from a *Centralab* (or its equivalent) parts kit consisting of an index assembly (Type X). Fig. 3 shows how the wafers are assembled with the switch piercing the vertical shield plate which separates the oscillator coils from the final r.f. coils. The oscillator coils use a solder lug type terminal strip for their common terminus and as a convenient tie point for the .01-μfd. disc-type r.f. bypass condenser C_{14}. The Bakelite wafer section closest to the front panel serves as the band selecting terminus for the oscillator coils L_2, L_3, and L_4. The final tank coils L_8, L_9, and L_7 use two Bakelite wafers for bandswitching. The output coils L_8, L_9, and L_{10} use the stator of C_{12} as their common terminus and the ceramic switch wafer for band selecting. For convenience, neatness, and because of their low cost, all coils are *B & W* "Miniductors." For those who wish to wind their own, data is given in the parts list. RFC_1 is a parasitic choke. RFC_2 is an r.f. choke for shunt feeding the type 5516 tube.

A rather unique feature, which is usually overlooked, was incorporated quite simply. Its inclusion greatly enhances its operability. When making adjustments on the rig, while working a local who is giving you air checks, it's a terrible nuisance to run back and forth from the trunk to the dashboard throwing switches for "transmit-receive" and listening for the comments before running back to the trunk for another adjustment. I obviated that inconvenience by running an extra line in the power cable which interconnects the dashboard mounted remote-control box and the rig itself. That extra line is connected to the "hot" side of the receiver's voice coil. With all "transmit-receive" controls of the remote-

(*Continued on page* 176)

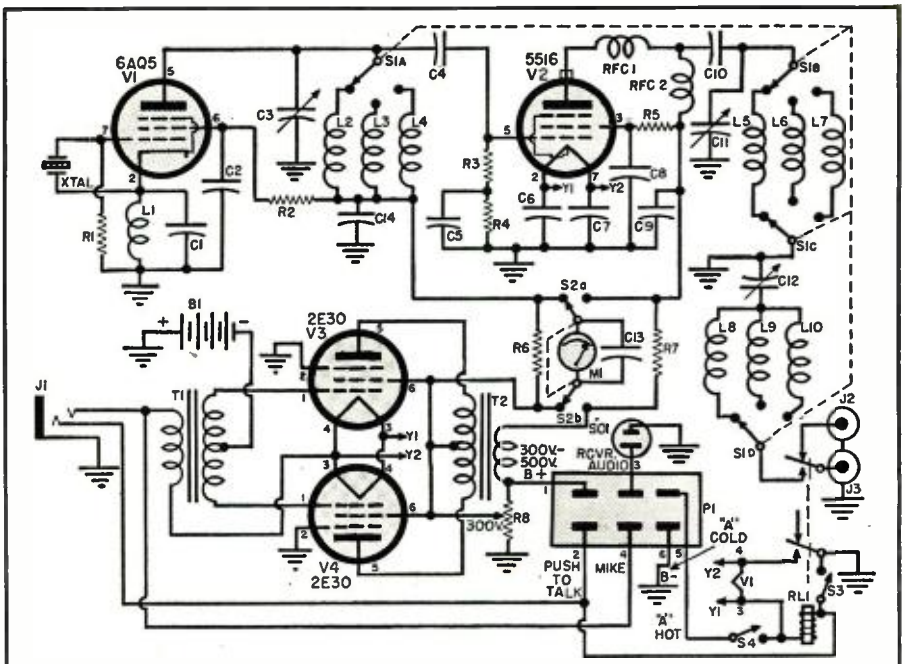

R_1—*100,000 ohm, ½ w. res.*
R_2—*100,000 ohm, 1 w. res.*
R_3—*18,000 ohm, 1 w. res.*
R_4, R_6, R_7—*50 ohm, ½ w. res.*
R_5—*8000 ohm, 2 w. res.*
R_8—*30,000 ohm, 50 w. variable res.*
C_1, C_4—*100 µµfd. mica cond.*
C_2, C_{14}—*.01 µfd. disc ceramic cond.*
C_3, C_{11}—*100 µµfd. var. cond.*
C_5, C_6, C_7, C_8, C_{13}—*.005 µfd. mica cond.*
C_9, C_{10}—*.002 µfd. mica cond.*
C_{12}—*140 µµfd. var. cond.*
S_1—*Ganged bandswitch (assembled from Centralab kit—see text)*
S_2—*D.p.d.t. toggle switch*
S_3, S_4—*S.p.s.t. toggle switch*
J_1—*Microphone handset jack*
J_2—*Coax connector to receiver ant. post*
J_3—*Coax connector to whip antenna*
P_1—*6-pin male connector (cable to remote control box and power supply)*
SO_1—*2-pin female connector (for headset or speaker in car trunk)*
Xtal.—*Crystal for operating frequency (see text)*
T_1—*Single-button microphone-to-push-pull grid trans.*
T_2—*Mod. trans. 10,000 ohms c.t. to 3000 ohms, 10 w. (Thordarson T-21M52 or equiv.)*
RL_1—*D.p.d.t. miniature, 6 v. d.c. coil relay (Advance Type K1504 RF)*
M_1—*100 ma. d.c. meter, 1" dia.*
L_1—*16 t. #22 en., ½" dia., ½" long (or B & W Miniductor #3004—same coil used for all bands)*
L_2—*8 t. #18 en., ⅜" dia., 1" long (or B & W Miniductor #3006—for 10 m. osc. tank)*
L_3—*16 t. #18 en., ½" dia., 1" long (or B & W Miniductor #3003—for 20 m. osc. tank)*
L_4, L_7—*64 t. #22 en., ⅜" dia., 2" long (or B & W Miniductor #3008—for 75 m. osc. tank)*
L_5—*8 t. #18 en., ⅜" dia., 1" long (or B & W Miniductor #3006—for 10 m. final tank)*
L_6—*20 t. #22 en., ⅜" dia., 1¼" long (or B & W Miniductor #3007—for 20 m. final tank)*
L_8—*3 t. insulated wire wound on outside of L_5 (10 m. ant. link)*
L_9—*4 t. ½" "Miniductor" inserted in L_6 (20 m. ant. link)*
L_{10}—*10 t. ½" "Miniductor" inserted in L_7 (75 m. ant. link)*
RFC_1—*1 µhy., 125 ma. parasitic choke*
RFC_2—*2.5 mhy., 125 ma. r.f. choke*
B_1—*Hearing-aid battery (see text)*
V_1—*6AQ5 tube*
V_2—*5516 tube*
V_3, V_4—*2E30 tube*

Fig. 2. Complete schematic. Coil data is provided for those who "roll their own."

Fig. 3. Top view of rig housed in 5" x 6" x 9" aluminum box.



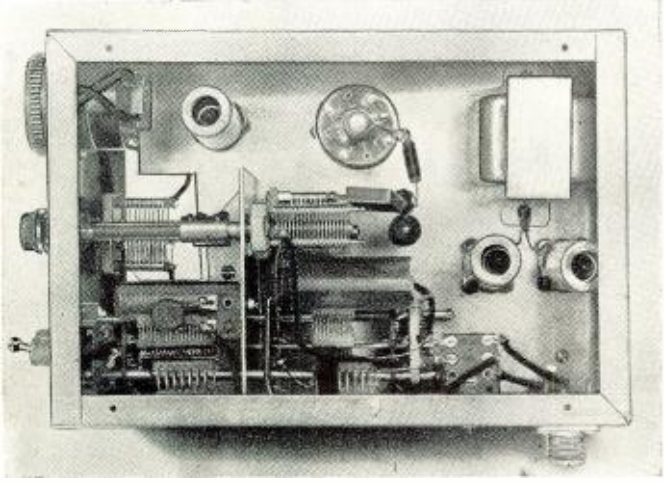


Fig. 4. Roomy layout makes construction and servicing easy.

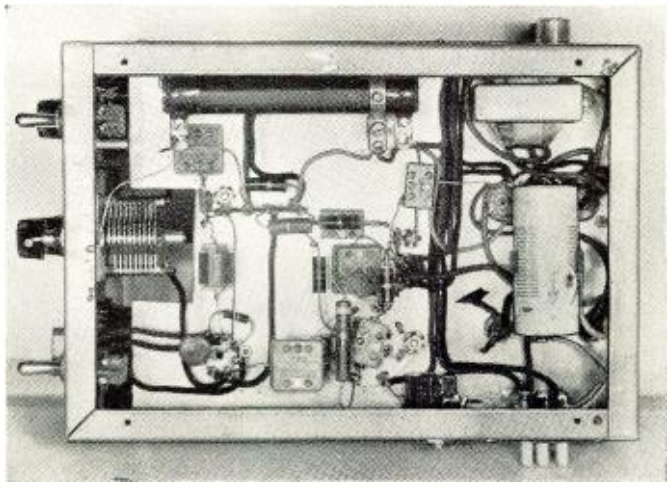

www.americanradiohistory.com

Fig. 1. The new Philco u.h.f. sweep generator for TV service.

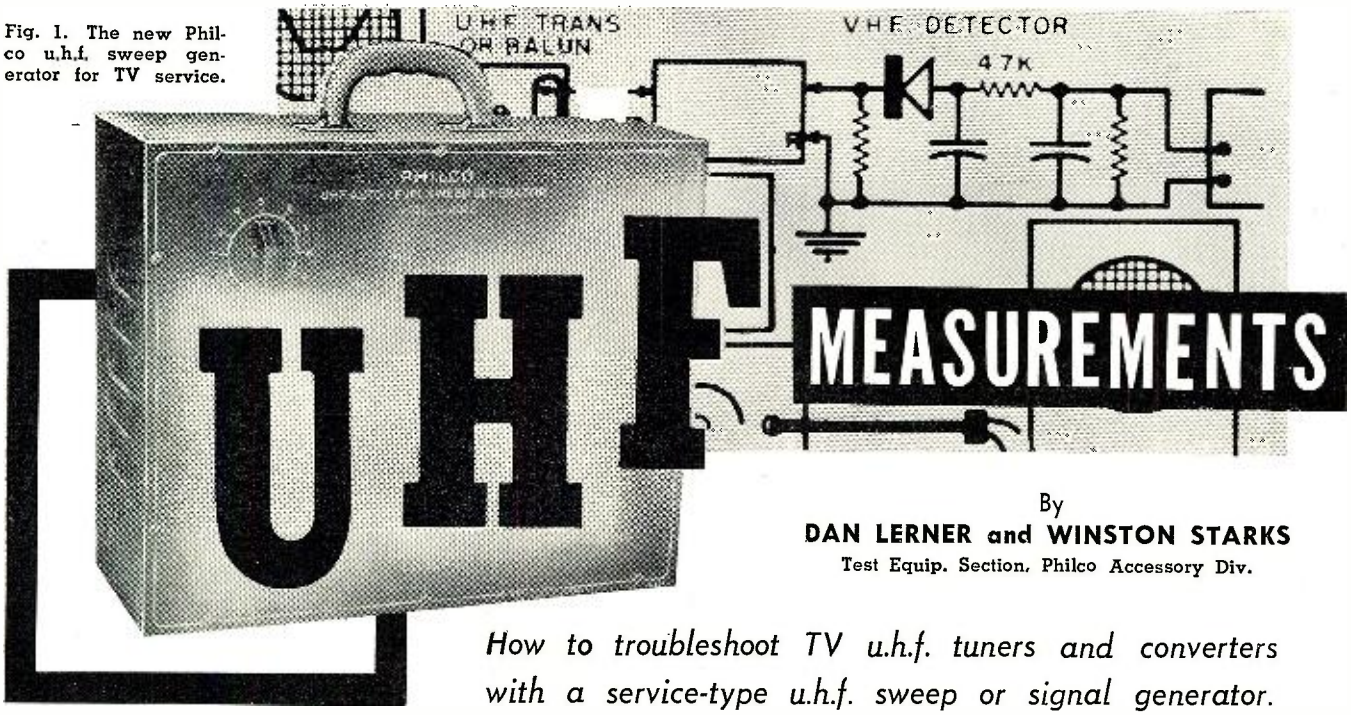

U.H.F. MEASUREMENTS

By
DAN LERNER and WINSTON STARKS
Test Equip. Section, Philco Accessory Div.

How to troubleshoot TV u.h.f. tuners and converters with a service-type u.h.f. sweep or signal generator.

THE service technician's need for u.h.f. test equipment has increased rapidly with the speedy expansion of u.h.f. broadcasting. Presently u.h.f. tuners are being used in steadily increasing numbers, with many types requiring repairs or some alignment.

Since the ordinary v.t.v.m., multimeter, oscilloscope, tube tester, etc. can be used for u.h.f. set servicing as well as for v.h.f., the only special piece of equipment needed is a u.h.f. signal or sweep generator.

Until recently, there were no relatively inexpensive u.h.f. signal or sweep generators designed specifically for TV servicing (see "U.H.F. TV Test Equipment," May, 1953, RADIO & TELEVISION NEWS.) However, such equipment is now available (an example is shown in Fig. 1), and the service technician needs to know how to use it for servicing u.h.f. tuners and receivers, as well as for other possible uses.

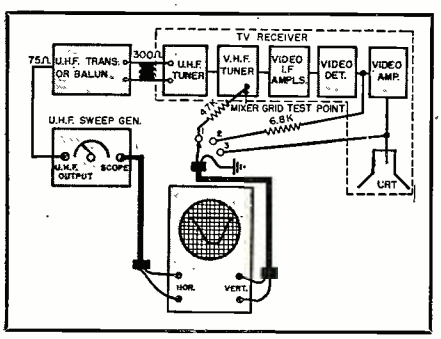


Fig. 2. A u.h.f. test equipment setup for troubleshooting the various sections of a u.h.f.-v.h.f. TV receiver.

Troubleshooting a U.H.F. Set

A quick check of the r.f. and i.f. operation of a u.h.f.-v.h.f. TV receiver may be obtained by simply feeding the u.h.f. sweep into the u.h.f. antenna terminals of the set, and observing the response at the check points indicated in Fig. 2. It will be noted that all the response curves taken at these various test points are inverted. This is because the rectified signals at the mixer grid, the video detector, and the picture tube grid are normally of negative polarity. Since this is the case, it is also common practice to make crystal detectors and probes produce an inverted wave in order to be consistent.

The setup shown in Fig. 2 permits checking the r.f. and i.f. over-all response curve and sensitivity at the picture-tube cathode or grid. If the result is below normal, then the scope is moved to the video detector. To avoid loading down the circuit, it is desirable to connect the scope to the video detector through a resistance of about 6800 ohms. If the response is not normal at the video detector output, the scope input is moved to the mixer grid test point on the v.h.f. tuner. Here again, it is important to connect through a resistor—in this case about 47,000 ohms. If we do not get a satisfactory response at this point, the trouble must be in the v.h.f. or the u.h.f. tuner. If a v.h.f. signal from a v.h.f. generator is available, it can be fed in at the v.h.f. terminals, bypassing the u.h.f. tuner. If this gives satisfactory results, the next step is to check the u.h.f. tuner.

Figs. 3 and 4 show test hookups which can be used to check u.h.f. tuners or converters without the use of a television receiver. Although the setup in Fig. 4 could be used to align a u.h.f. tuner or converter, do not attempt alignment unless you have the manufacturer's specific alignment instructions. The basic principles of alignment of tuners at u.h.f. is very much the same as at lower frequencies; however, many u.h.f. tuners incorporate special gimmicks and adjustments whose purpose should be understood before attempting adjustment. There is usually some provision for high and low frequency oscillator tracking. There will sometimes be a gimmick, consisting of two twisted wires, which may be used to adjust the oscillator feedback. There may also be small movable "tabs" or plates which affect oscillator tank balance and feedback. Such adjustments are sometimes used to eliminate "holes" or dips in the tuner curve due to absorption effects and falling off of converter oscillator output. The u.h.f. tuner will usually have some form of tuner r.f. preselection between

Fig. 3. Checking a u.h.f. tuner with a v.h.f. tuner and u.h.f. sweep generator.


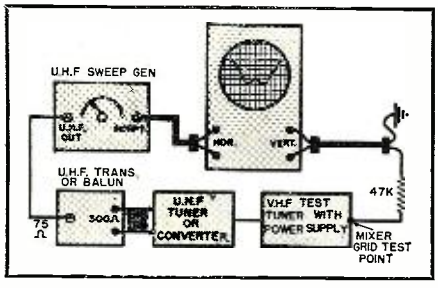


Fig. 4. Checking a u.h.f. TV tuner with a v.h.f. detector and scope.

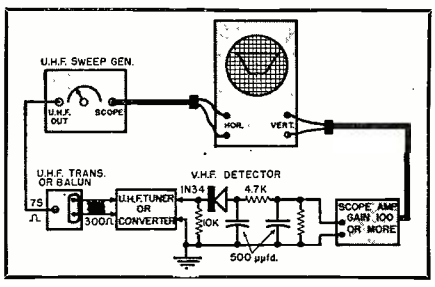

www.americanradiohistory.com

the mixer and the antenna. This circuit should have adjustments such as a high-frequency trimmer and perhaps slotted rotor plates, in the case of condenser tuning, which can be "winged" to provide low and midband r.f. tracking.

The setup of Fig. 3 shows how a u.h.f. sweep generator can be used to check the response and relative gain of a u.h.f. tuner or converter. In this case, the output of the u.h.f. tuner goes to a v.h.f. tuner which serves as a test standard. The rectified signal at the mixer grid of the v.h.f. tuner is viewed with an oscilloscope. The response curve is the result of the combined response of the u.h.f. and v.h.f. tuner. Of course, this does not give the true response of the u.h.f. tuner, but does serve as a means of comparison to determine if the u.h.f. tuner is faulty. With the u.h.f. tuner in this setup, crystals and tubes may be changed while observing their effect on the response and relative gain. A tuner known to be of good quality may be placed in the setup, and the generator and oscilloscope settings can be marked and standardized as a means of future comparison and evaluation.

To check the true characteristics of the tuner, it is necessary that the tuner output be detected without going through other circuits. Fig. 4 shows how this can be accomplished by using a detector followed by a scope amplifier of good low-frequency response. The scope amplifier is usually needed in this setup to amplify the detector output to operate the oscilloscope. The value of the detector output resistor should be approximately 100,000 ohms.

Many u.h.f. signal and sweep generators have a 50- or 75-ohm output rather than 300-ohm output. In order to go from the 75-ohm output of the generator to the 300-ohm input of the tuner, a u.h.f. matching transformer must be used as shown in the hookup of Figs. 3 and 4. Such matching transformers are available from some test equipment manufacturers, and one is shown in Fig. 8; its schematic diagram is shown in Fig. 5.

U.H.F. Frequency Calibration

It is possible to mix signals, as shown in Fig. 6, in a way that will permit accurate spot calibration of generator frequencies. A v.h.f. marker generator (using harmonics) or a u.h.f. marker generator may be used to inject a marker or calibration signal into the line as illustrated. It is accepted practice to calibrate sweep generators with the sweep width set at minimum. When the sweep and marker generators are tuned to approximately the same frequency, a beat will be observed on the scope.

A u.h.f. television station can be used to get an accurate frequency calibration point without a calibration standard by tuning the u.h.f. generator for the beat indication on the scope as shown in Fig. 6. This frequency will be the picture carrier frequency of the television station.

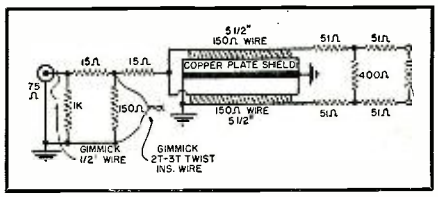


Fig. 5. Schematic diagram of a 75-ohm to 300-ohm matching transformer designed for use at ultra-high frequencies.

In all the u.h.f. setups and measurements which have been discussed, it is necessary that special care be taken to make good connections and to insure that all lines are properly terminated. In cases where a match must be made between a 75-ohm line and a 300-ohm line, a transformer should be used. If 300-ohm lines in a setup are too "hot" (very high standing-wave ratio), they may be cooled off by inserting a 3 or 6 db pad in both ends of the 300-ohm line. The insertion of a 6 db attenuation will cut the available signal in half.

U.H.F. Delay Lines

A u.h.f. sweep generator may be used with a delay line to make numerous tests at u.h.f. The setup shown in Fig. 7 can be used for measuring standing-wave ratios produced by transmission lines or by the terminating device at the end of a line.

The curve on the scope shown in Fig. 7 would be a straight line for a perfect termination of the delay line. If the termination Z is not 75 ohms (for the 75-ohm delay line used) and is not a pure resistance, then there will be ripples on the curve as shown. As might be expected, the SWR is equal to:

$$SWR = \frac{\textit{distance from base line to largest ripple peak}}{\textit{distance from the base line to adj. minimum}} = \frac{Y}{X}$$

It should be remembered that the scope sweep is actually a representation of varying frequency, so that as the generator goes through its sweep, there are points of minimum and maximum SWR. (The termination varies with frequency.) Checking the SWR by this method gives a good approximation only if minimum and maximum points are taken as close together as possible. Obviously, there is some error because the minimum and maximum do not occur at the same frequency. The error can be minimized by using a longer delay line to produce more reflected waves which will be closer together on the scope trace. The limit to making the line longer is the loss which occurs in the line which makes the termination appear better.

The setup in Fig. 7 is also ideally suited for delay line measurement of the velocity of propagation of a transmission line. To measure the velocity of propagation of a line, cut it to a known length (preferably 25 to 100 feet), and substitute it as the delay line. Then, the far end of the line

(*Continued on page* 191)

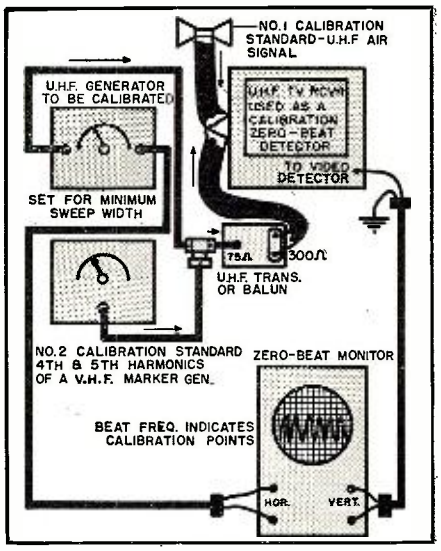


Fig. 6. Shown here is the setup for calibrating a u.h.f. sweep or signal generator using two different standards.

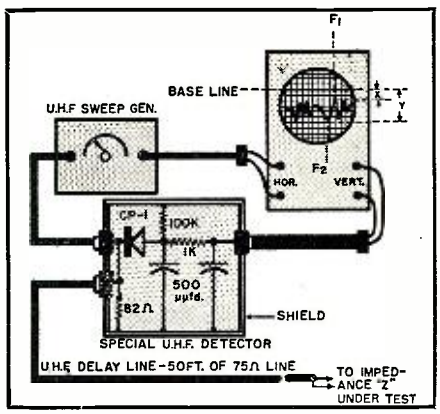


Fig. 7. Test setup for standing-wave ratio measurements with a delay line.

Fig. 8. External appearance of the u.h.f. matching transformer shown in Fig. 5.



www.americanradiohistory.com

PAGES FROM A TAPE EDITOR'S NOTEBOOK

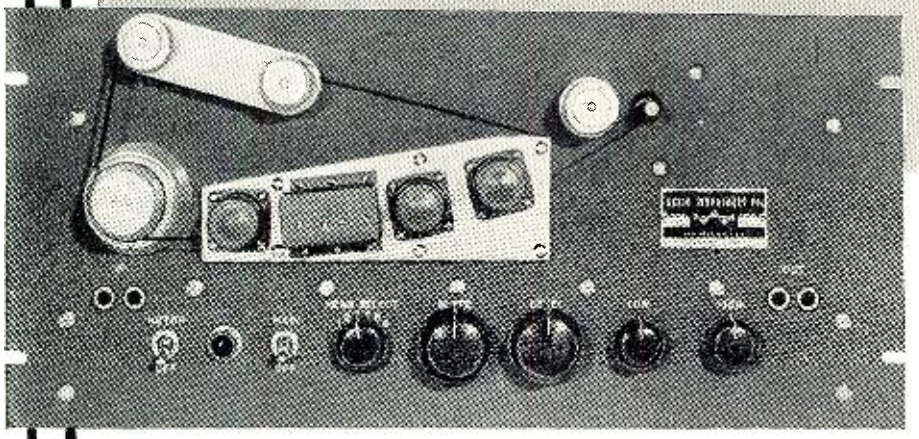


Fig. 1. Audio Instrument's unit permits the use of controlled echo, with audio perspective and reverberation time variable.

Part 4. Concluding article covers a number of "tricks" for which tape is useful and how such effects can be obtained.

By

DONALD C. HOEFLER

THE recording engineer, being equal parts scientist and artist, has never failed to take a new piece of equipment and endow it with even greater virtues than those imagined by its inventor. Never was this truer than in the few years since the advent of magnetic tape. The techniques described here have all been developed since the introduction of tape, although some of them are equally applicable to other media as well.

It has become increasingly common for small U. S. recording companies to buy master tapes from European record companies and radio stations, and to transfer them to commercial LP discs for release in this country. These transactions have enabled tremendous savings in talent costs, but they very often have created equally tremendous headaches for the dubbing engineer, who must translate these foreign tapes into a commercially acceptable LP record for American audiences.

A common problem is the matter of tape width. Our tape is ¼-inch wide, while some European tape is 7 millimeters, just a fraction larger. Some American-made tape machines are equipped with guides which are large enough to permit the 7-mm tape to pass without binding, but for machines which do not, the only cure is to remove the guides and turn them down on a lathe until they fit.

The next big problem is that of overall sound quality. European practice differs widely from American technique in the matter of studio acoustics, microphone placement, equalization, and recording characteristics. Here the engineer and recording director must experiment with equalizing devices until an aural check satisfies them that they have the desired sound.

Finally there is the question of musical pitch. The standard pitch employed almost everywhere in this country is known as the *Stuttgart* pitch, and refers to a middle A pitched at 440 cps. But there have been many other systems of octave nomenclature employed throughout musical history, in which A has varied all the way from 415 to 454.7 cps, and practice among European orchestras still varies widely. This situation is further complicated by the fact that tape speeds will vary somewhat, due to instability of the power frequency supplying the recording equipment.

Thus there has arisen the need for some means of altering the pitch of tape recordings, *i.e.*, of varying the speed of the tape during playback. This can be accomplished by disconnecting the synchronous capstan motor from its usual 60-cycle supply and feeding it instead from a variable-frequency power supply which will operate anywhere between perhaps 55 and 65 cycles. The power pack for the amplifier, of course, remains on the regular power source. The local supply can be a motor-generator set, but a much more satisfactory arrangement consists of a very stable audio oscillator followed by a power amplifier of sufficient output to drive the capstan motor. With this system on a professional machine, it is possible to vary the pitch nearly a half-tone in either direction before the motor falls out of synchronization and begins to hunt. This arrangement is equally applicable to disc reproduction, with the same precaution that the variable supply must feed the turntable motor only.

Another stunt employing tape has made life a little easier for sound-effects men in radio, television, and motion pictures. Most of the brief effects such as gun shots, footsteps, and door slams are produced in the studio as required during a performance. But there are many other background sounds of longer duration such as the noise of a cheering crowd, or of city traffic, or perhaps of the rolling surf which are usually reproduced from recordings. Since these are usually ten-inch records, with a playing time of around three minutes, a scene will often run longer than the record. In such cases, it has been the practice in the past to use two identical records, and to fade from the end of one to the beginning of the other as required. But since most sound-effects setups contain only three turntables, and two of them may be in use for a single background effect, the operator is then severely handicapped.

But none of this is necessary when the sound is recorded on a *continuous tape loop*. Such a loop is made by first dubbing a few seconds of the desired sound from disc to tape. Then the beginning of the tape is spliced to the end of it to form a loop whose length will just permit it to be threaded around the supply reel, past the heads and capstan, around the takeup reel, and then *directly back to the supply reel.* This is illustrated in Fig. 3. A little experimenting will be necessary to determine which tape length works best with a given machine, and it may be necessary to disable the supply and takeup motors to prevent their racing. It is of course possible to record several effects simultaneously on the same tape with this system, thus producing results which would require a very elaborate turntable setup in the studio.

An effective method of noise reduction has been developed by Paul H.

www.americanradiohistory.com

Hickin of the *RCA Victor* studios. It consists simply of reversing the tape and playing it with the plastic base against the head. This results in a reduction in level which discriminates against the higher frequencies, as shown in Fig. 2. A considerable high-frequency roll-off and eventual cut-off is achieved, with the exact shape of the response curve dependent upon the operating speed of the tape. It is important that the tape when played in this fashion have no patch-type splices, as these would raise the oxide further from the head as they passed it, resulting in skip effect. The usual procedure is to make a conventional dub onto tape from the noisy source, and then to make a second dub from the first, playing the first one back with the base in and oxide out. The first tape is then discarded or held for protection, and the second copy edited for ticks and pops.

Numerous other interesting and useful effects may be obtained without any equalizers other than the pre-emphasis and de-emphasis circuits in the tape machines themselves. If a machine has plug-in or switch-in equalizers available for the various speeds at which it operates, it is possible, and sometimes desirable, to use some playback equalization other than the theoretically correct one.

Re-recording at some multiple or fraction of the original recording speed will also alter the response characteristic. If a tape is reproduced at twice the speed at which it was recorded, for example, and a dub made at twice the speed it will be played back, the pre-emphasis and de-emphasis curves are each displaced an octave from their normal positions, and they will no longer be exactly complementary. The differences will depend upon the equipment used and the speeds at which it is operated. A little experimentation along these lines will afford several response curves which are useful for special applications.

The progress of tape recording characteristics has followed a very similar pattern to that of disc and film recording, with each studio having its own concept of the ideal. While standardization would be highly desirable, the recording engineer meanwhile can take advantage of the lack of it. For if he has at his disposal several tape machines of different manufacture, he almost certainly has an equal number of different reproducing characteristics. There again he can give his clients a choice of several variations in sound quality without the additional expense of external equalizers.

There are several methods for the addition of controlled reverberation to recorded material in general commercial use. One of these consists of an electroacoustic drive mechanism, such as that found in a loudspeaker or disc record cutter, which is attached to one end of a set of taut springs made of various gauges of piano wire. The other end of the springs is connected to a reproducer mechanism, such as a contact microphone or phonograph pickup. The vibrations set up in the springs result in a sound which approximates that of an echo.

The method which is most commonly used, when space permits, is the echo chamber. This is essentially a highly reverberant room containing a loudspeaker and a microphone. The amplifier which drives the loudspeaker is bridged across the program source. In live recording this may be a single microphone channel or the output of the entire mixer. In re-recording, the source will be the playback equipment. In either case, the sound from the loudspeaker is reflected many times in the echo chamber and picked up by the microphone, from which it is fed back to the console to be mixed with the original sound in whatever proportion is desired.

The various ways in which an echo chamber can be used to alter the sound of a recording have been thoroughly explored in recent years, and hardly a popular recording is made today which does not make some use of this effect. For many years the reverberation chamber has been standard equipment in motion-picture and broadcasting studios.

But even for this well-known device additional uses have been discovered with the advent of tape. A problem which has often troubled recording companies, when issuing a record of a broadcast or other performance where an audience was present, is how to eliminate the applause at the end of the music. If a slow fade is made, some of the applause will sneak through and prove somewhat annoying to the home listener. With a fast fade, the reverberation on the last note will sound clipped and unnatural. But the combination of tape and an

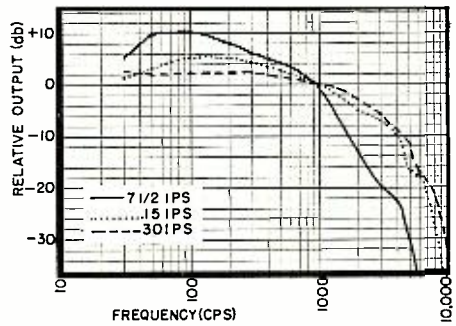


Fig. 2. The effect of frequency response of tape reproduction at various speeds, due to playing back the tape with the base against the reproduce head. See text.

echo chamber has obviated this trouble. The tape is edited so that all of applause is removed and replaced by blank tape. This of course results in a sharply cut off final chord, but the lost reverberation is restored by the echo chamber. A sample of the playback output is bridged to the chamber in the usual manner and returned to a mixer channel. Just as the silent tape approaches the playback head, the return from the echo chamber is faded in to supply the missing reverberation. Often extensive rehearsal is necessary to achieve a natural effect, but when the sound of the echo chamber is equalized to approximate the sound of the original auditorium, and when the cross-fading between the source and the echo are smoothly achieved, the result will be a finely decaying reverberation which will match the music preceding it.

The arrival of LP and EP has caused the use of this trick to become an everyday occurrence. On an EP, for example, there is available a maximum playing time of about eight minutes, while that of a 12-inch standard disc is around five minutes. This means that it is possible to record

(*Continued on page* 98)

Fig. 3. Continuous tape loop permits reproduction of background sound effects for much longer periods than heretofore available on ten-inch recorded discs.



www.americanradiohistory.com

COLOR RECEIVER ALIGNMENT

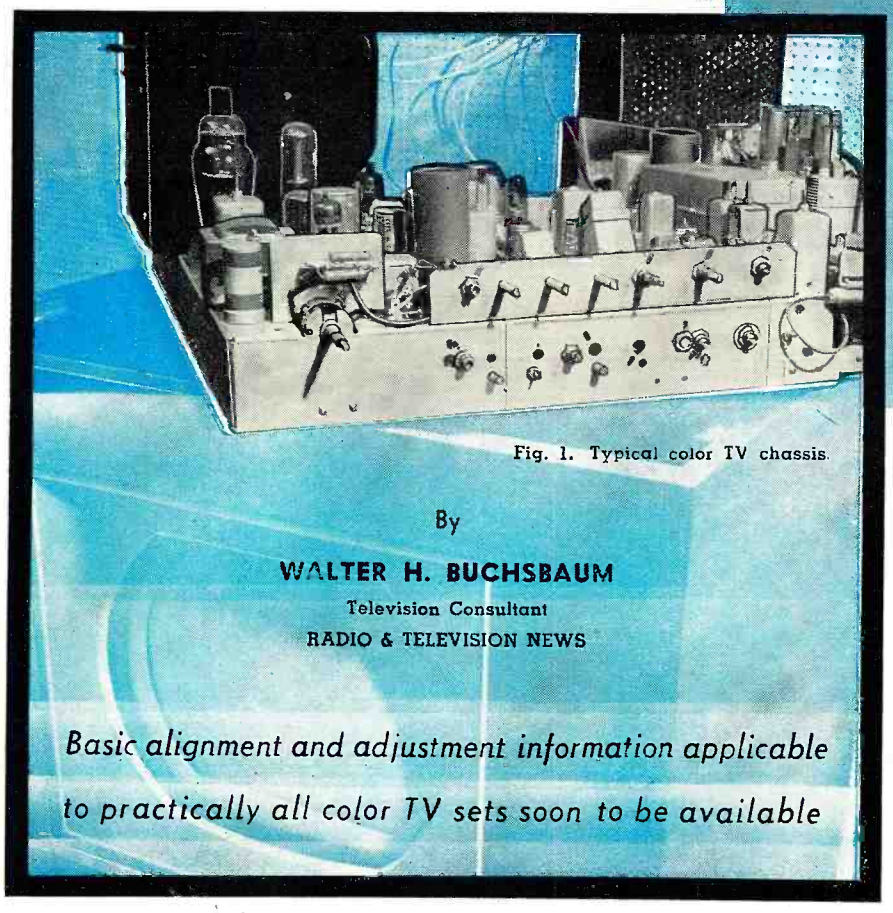


Fig. 1. Typical color TV chassis.

By

WALTER H. BUCHSBAUM

Television Consultant

RADIO & TELEVISION NEWS

Basic alignment and adjustment information applicable to practically all color TV sets soon to be available

NOW that many TV manufacturers have announced plans for color set production in 1954, the service aspects of color TV are gaining new importance. Actually, there are two distinctly different functions which the service technician performs. One function is the installation and adjustment of the set; the second function is troubleshooting and repairing defects.

Installing and aligning color receivers (see Fig. 1) is much more complex than in monochrome work and each manufacturer will provide detailed instructions with his receiver. Certain adjustments and alignment data, however, apply for almost all sets and will be required with every new color installation. Such data is presented here as it applies to those receiver sections which differ from the monochrome TV circuits. Conventional adjustments such as height, width, horizontal or vertical synchronization, etc., are not covered here.

Fig. 2 shows the essential portions in a color receiver, indicating their sequence and interdependence. The "B+" power supply, heater, and d.c. distribution are omitted here. The typical color receiver requires considerable adjustment and precise alignment in five different sections as listed below:

1. I.F. section. The i.f. response is critical and accurate trap setting is essential to avoid color interference.

2. Color synchronization section. Here the color reference burst must be used to control the phase and frequency of the local color subcarrier oscillator. This section usually uses a.f.c. and is similar to the horizontal oscillator in a monochrome set.

3. Decoding section. In this part of the set the color signals are removed from the subcarrier and transformed from the "I" and "Q" signals into voltages corresponding to the three colors.

4. Chromaticity amplifiers. The color signals are amplified, certain bandpass responses are required, and color intensity adjustments are needed.

5. Picture tube components. For a tri-color tube this is the most complex adjustment of all, requiring both electrical and mechanical settings which affect each other and must be optimized for good color reproduction. The purity coil, field neutralizing coil, deflection yoke, and positioning magnets must be carefully set for correct picture tube operation.

While it is not possible to give a detailed and complete procedure for these five alignment problems as they apply to each individual color receiver, this article does give the technician the data needed to set up a color receiver in the customer's home and get it working right.

I.F. Alignment

Although it may not be obvious, the i.f. section of a color TV set is somewhat different from its monochrome counterpart. The reasons for this are the requirements that the color subcarrier must be amplified along with the video and sound carrier and that there must be a constant phase delay throughout the passband to 500 kc. above the color subcarrier to eliminate the possibility of phase error in the color information. Fig. 3 shows the i.f. response required for a color TV set. Note that the subcarrier is 3.58 mc. lower in i.f. frequency than the video carrier. Also note that the flat portion of the response curve extends at least 0.5 mc. below the color subcarrier. A very sharp dip is needed for the sound carrier to prevent it from interfering with the video signal.

For alignment purposes it is not necessary to know exactly what the i.f. circuit looks like and there are a number of different circuit combinations which will produce a response curve like the one in Fig. 3. The important thing for the alignment procedure is to know the location of the various traps and the prescribed frequencies at which certain coils should resonate. This data is usually contained in manufacturers' service data and sometimes is even given with the tube layout diagram.

Alignment of the color i.f. with the sweep generator and oscilloscope method is the same as for monochrome, with emphasis on accurate markers tuned to the color subcarrier, its sidebands, and the various traps. In monochrome receivers it is usual for some change in i.f. response to occur with varying levels of a.g.c. This is not permissible in color sets since this would mean that a change in signal strength would also result in a change of the actual colors on the screen. Check the i.f. response at maximum and minimum a.g.c. to make sure the shape of the curve remains the same.

Color Sync Adjustment

The color synchronizing section has the function of providing the reference phase of the color subcarrier for the demodulator or synchronous detector circuits. For this purpose the short reference burst transmitted after each horizontal synchronizing pulse must be compared with the frequency of the local color subcarrier oscillator and this oscillator must be locked in-phase to the reference burst. Several different circuits are used by various manufacturers to accomplish this. One

www.americanradiohistory.com

method utilizes the reference burst itself through a crystal ringing circuit to provide a constant amplitude sine-wave signal. Another frequently used circuit employs a phase detector type automatic frequency control to lock the local color oscillator with the reference burst. Since the burst only appears after each horizontal synchronizing pulse, the entire a.f.c. system must be gated so as to operate only during the short burst period. The gating signal is at the horizontal sweep frequency and is usually the horizontal flyback pulse.

Alignment of the color synchronizing section depends, in part, on the gating and cannot be started before the horizontal sweep is locked in correctly. Since the color subcarrier frequency is 3.58 mc., a test signal of this frequency will help greatly in the alignment process. When a color telecast is used as a test signal be sure that the i.f. and second detector, as well as the horizontal and vertical synchronizing sections, are adjusted before the color synchronizing section is tackled.

Fig. 4 is a simplified diagram of a typical gated a.f.c. system. Actual circuits may vary with different manufacturers, but the principal components remain the same. First, align the oscillator output transformer for maximum output signal. Connect a crystal diode probe across the input of the following stage, usually a quadrature phase amplifier, and tune for maximum signal. Similarly, tune the 3.58 mc. takeoff coil which removes the burst from the video section for maximum output. The most critical adjustment is the tuning of the phase detector transformer itself. If this circuit locks on the wrong phase, the colors at the picture tube will be wrong. If the phase detector is misaligned so that the local color oscillator is not locked at all, the colors will vary as the oscillator phase and frequency drifts. In other words, wrong colors which remain consistently wrong can be caused by a slight misadjustment of the phase detector, while shifting colors indicate loss of color synchronization.

The local color oscillator frequency must be quite close to the correct frequency and this depends on the tuning of this oscillator. To check for correct tuning, short out the reference burst going to the phase detector and tune the oscillator carefully until correct colors appear on the screen. It will be difficult to maintain correct colors by manual oscillator tuning for any length of time, but if the manual setting of the oscillator frequency is close enough to produce correct colors for an instant, the a.f.c. system usually can take over full control. After correct phasing is obtained and the local oscillator synchronized firmly, the output transformer and subsequent 3.58 mc. tuned networks should be re-aligned for maximum signal transfer.

Two sine-wave subcarrier signals are required, 90 degrees out-of-phase with each other, to demodulate the "I" and "Q" signals. To obtain the necessary 90-degree phase shift, a quadrature

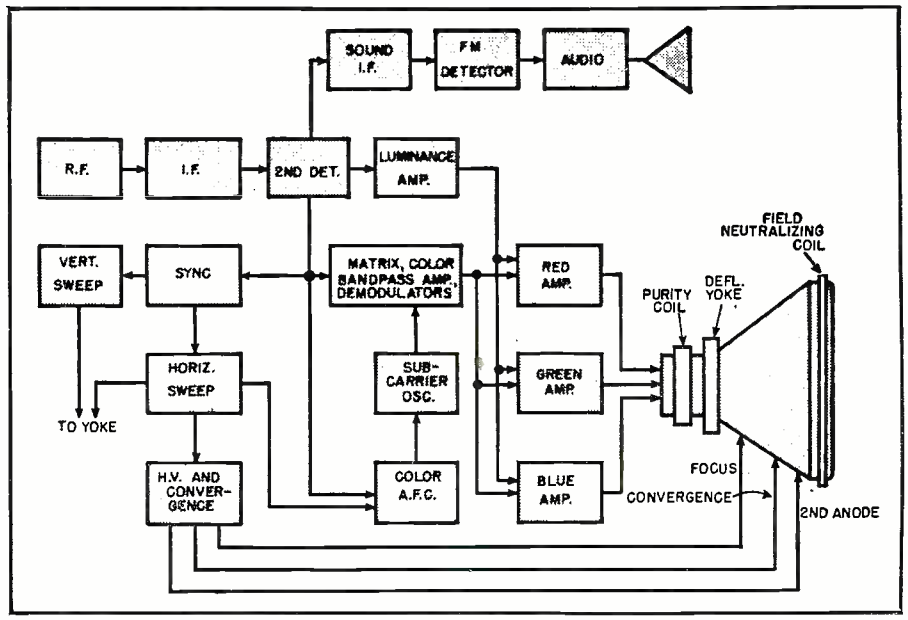


Fig. 2. Partial block diagram of the typical color TV set using tri-color tube.

amplifier is often used. In the system shown in Fig. 4, the 90-degree phase-shift amplifier is also used as a buffer between the oscillator and the phase detector. By adjusting the network marked "phase control," the phase of the feedback signal is shifted to coincide with that of the incoming burst. Needless to say, all 3.58 mc. transformers are tuned for maximum power transfer at the color synchronizing frequency.

Alignment of the crystal ringing system for color synchronizing signals is considerably simpler, since all networks are tuned for maximum and the limiter output transformer is tuned for maximum limiting action. There is no oscillator drift, no trouble of "pull in" limitation, and the only criterion is that the output be a uniform amplitude sine wave free of distortion and harmonics.

Other synchronizing circuits using different a.f.c. systems can usually be aligned in the same manner as the basic circuit of Fig. 4. In some receivers the functions of a crystal ringing circuit and the a.f.c. system of Fig. 4 are combined, but the adjustment problems are essentially the same.

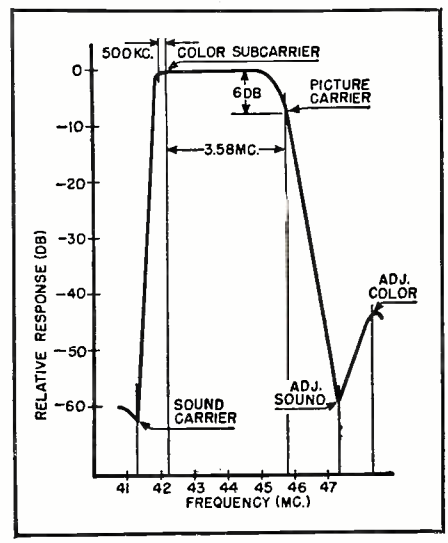


Fig. 3. Color TV set i.f. response.

After the second detector the color signal is separated from the luminance information (monochrome component of the color TV signal) by passing through a bandpass amplifier, often called the chromaticity channel. The frequency response of this stage is such

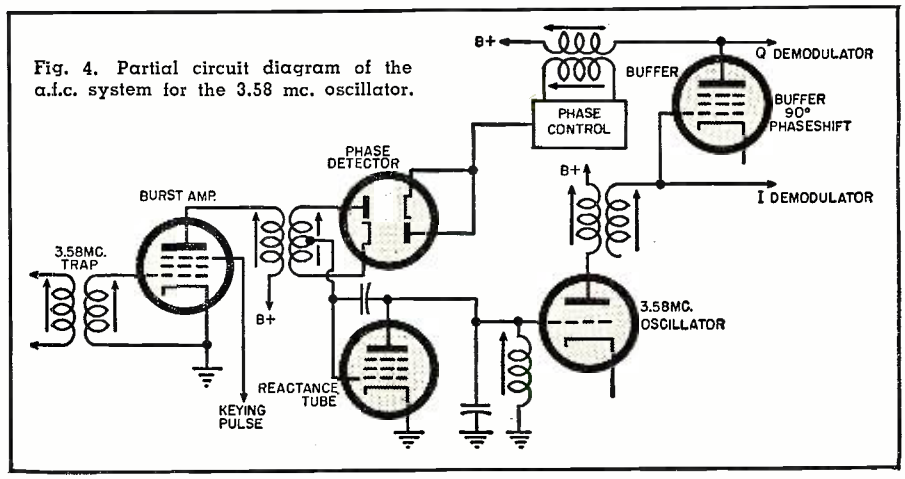


Fig. 4. Partial circuit diagram of the a.f.c. system for the 3.58 mc. oscillator.

www.americanradiohistory.com


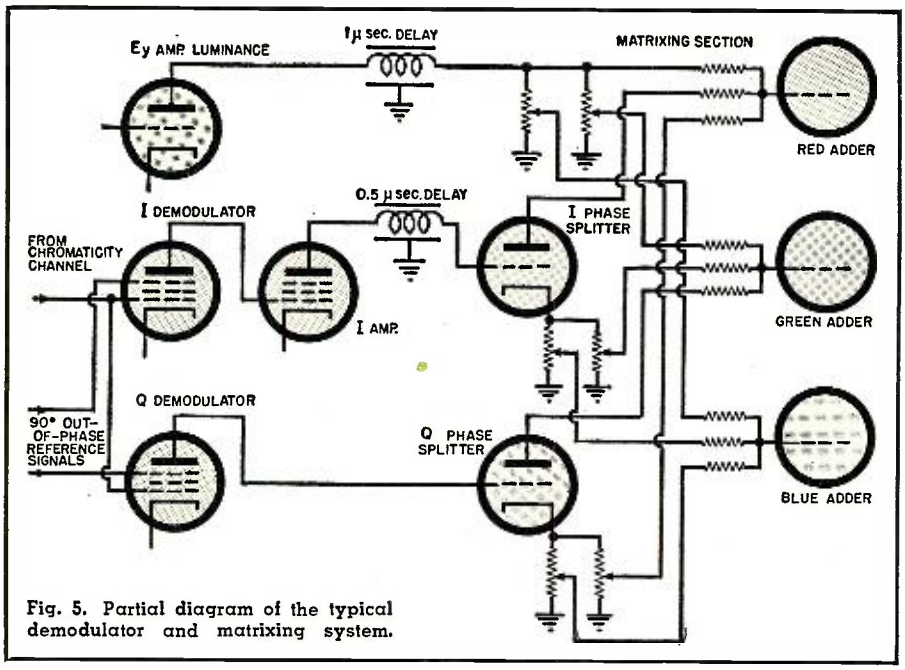


Fig. 5. Partial diagram of the typical demodulator and matrixing system.

that only signals from 2.28 to 3.98 mc. are passed. This frequency spectrum is occupied by the color subcarrier and its two sidebands. After passing through the chromaticity channel, the signal is applied to two demodulators, the "I" and "Q" detectors. As is shown in Fig. 5, these two detectors are controlled by the two color subcarrier reference signals obtained from the color synchronizing section. The two 3.58 mc. sine waves are 90 degrees out-of-phase with each other and 33 and 57 degrees respectively out-of-phase with the reference burst. In order that the "I," "Q," and luminance signals arrive at the combining networks at the same time, a 1 microsecond delay is introduced in the luminance channel and a 0.5 microsecond delay in the "I" channel. A triode is used as phase splitter for each of the two color signals and up to six potentiometers are needed to adjust the amounts of signals to be added. The reason for all these controls is the varying amplification in the three channels requiring adjustments to combine the luminance "E_y," "I," and "Q" signals in the proper amounts to obtain the correct red, green, and blue signals.

In an actual receiver the matrixing section will be adjusted carefully at the factory using special test signals to check for the correct color signal mixing. For the service technician it may be sufficient to touch up some of these controls provided there is reason to believe that wrong colors are not caused by other effects. The adjustment of these matrixing controls requires the presence of a station signal, preferably a test pattern. Only after the picture tube and the other chroma and brightness controls have been carefully adjusted, should the matrixing section be aligned. When one of the three primary colors appears to be off in hue, then the matrixing adjustments can be at fault. Be sure to use each control independently, varying it only slightly and returning to the previous setting if it appears to have no effect on the particular color that is off. In general, matrixing controls should be considered third in line rather than secondary controls.

Fig. 6. Partial schematic diagram of the basic color amplification circuits.

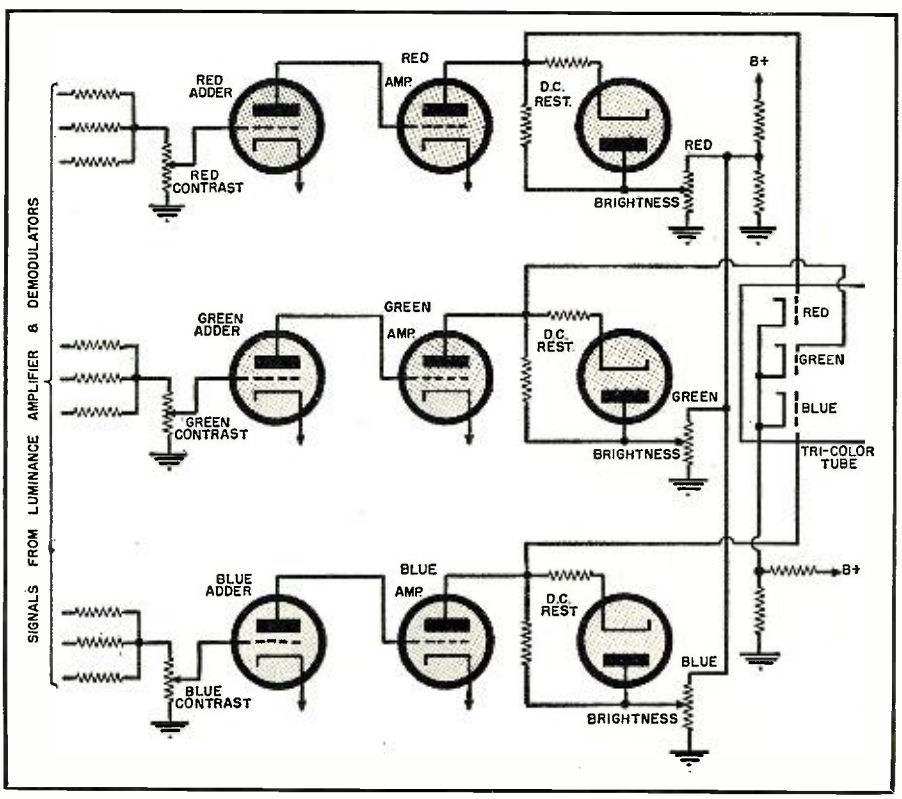

Color Amplifiers

In some receivers the "I" and "Q" signals are not combined with the luminance signal to form the red, green, and blue signals, but instead, are changed over to form three color difference signals with the luminance components added in the picture tube itself. Wherever the luminance signal joins the color information, more gain is needed from the matrixing section to drive the color picture tube. A basic three-channel video system using the final color signals is shown in Fig. 6.

The three color adders each receive some portion of the luminance, "I," and "Q" signals and the total voltages are added at the grid of the tube. A gain control, often the type shown in Fig. 6, controls the gain of each color channel. These controls correspond to the contrast control in the monochrome receiver in that they control the amplitude of the video signal for each color channel. After a stage of amplification, the three color signals are applied to the three control grids of the tri-color picture tube. In the case of a single gun picture tube, some type of sequential keying system is used to apply the three signals to the picture tube grid in the proper sequence.


Similar to some monochrome sets, each video amplifier has a diode d.c. restorer at the output. The d.c. level of each restorer circuit is set by a potentiometer which has the effect of controlling the brightness or background illumination of the screen. In some color receivers a master brightness control is available on the front panel which sets the d.c. level for the separate color brightness controls, designed as secondary adjustments.

A total of six controls is available in a typical color amplifier section. To adjust these controls, a station color signal is helpful, although the brightness controls can be set with a monochrome signal. It is necessary to balance out the three brightness controls to obtain white, and when a color test pattern is

(*Continued on page* 151)

www.americanradiohistory.com

PICTURES ON TAPE

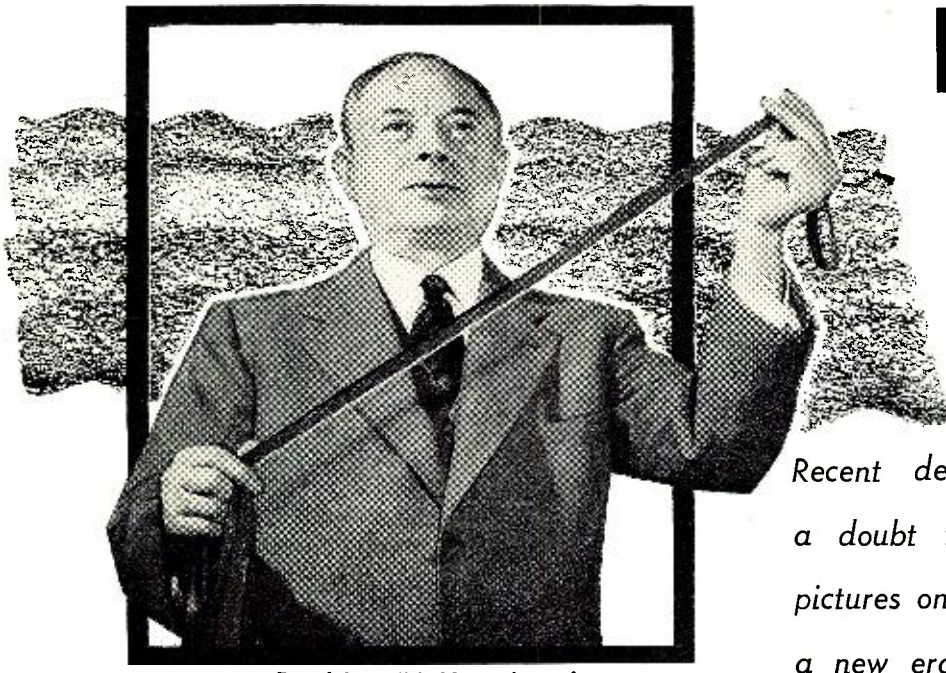

Brig. Gen. David Sarnoff holds a piece of the tape used in the color TV demonstration.

Recent demonstration proved beyond a doubt the feasibility of recording pictures on tape. We saw the dawn of a new era in electronic photography.

RADIO CORPORATION OF AMERICA recently unveiled a new magnetic tape system for television before representatives of the press at Princeton, N. J. The demonstration consisted of several phases. We viewed black-and-white tape recordings on color receivers as well as both live and recorded color programs.

The high point of the demonstration was a live colorcast emanating from the *NBC* studios in New York and microwaved to Princeton. The program was viewed on two color receivers and, at the same time, was being magnetically recorded on tape. Midway in the program one of the color receivers was switched over to receive the taped material. At this point we were actually viewing the same program on two color receivers—one a live telecast and the other a recording of the same program. At a distance of 20 to 30 feet from the receivers, both of the pictures seemed equally good.

In its present state, the quality of video reproduction is better than the poorest kinescope and not quite as good as the best kinescope recording. The bandwidth attained so far is slightly better than 3 mc. with an ultimate goal of nearly 4 mc.

Unlike kinescope recordings, the magnetic tape system stores the electrical signals directly as they come from the station. This system is, to some degree, similar to that used in home tape recording. The tape speed is, however, 30 *feet*-per-second as compared with home recorders which operate at a speed of 3¾ *inches*-per-second or 1/96th the speed of the video tape. Although the demonstration employed a 17-inch diameter reel for showing a four-minute program, plans are being made to record a 15-minute program on a 19-inch reel.

Two sizes of standard plastic-based magnetic tape are employed—a 2-channel, ¼" tape is used for recording the black-and-white telecasts with the video and sync pulses on one channel and the audio on the other; and a 5-channel, ½" tape for color. The video channels comprise the red, blue, and green signals which are recorded separately as is the sync pulse and the audio which make up the 4th and 5th channels.

It is obvious that the cost of magnetic tape recording is considerably lower than that of kinescopes since the kinescope film must be processed before use. It is estimated that the cost of color magnetic tape recordings will run from 5 to 10 per-cent of an equivalent kinescope film. It cannot be denied that this lower cost is important but there is still another feature which will be of equal importance to TV broadcasters and that is the advantage of immediate playback. There is no developing process involved as there is with kinescope films, a worthwhile saving.


The immediate importance of this new system is in the TV broadcasting field but, as pointed out by Brig. Gen. David Sarnoff, it may eventually be used for national defense, motion picture work, industry, schools, and, ultimately, home entertainment. The day may not be too far off when your home movie films will be tape recordings and your projector your television set screen.

RCA estimates that the new system will be ready for commercial use in about two years. While much of the associated equipment needs additional development work, the system, as demonstrated to the press, is technically sound and, with modifications, can be put into production in the not-too-distant future. -30-

Laboratory equipment on which the first public demonstration of tape recording of both black-and-white and color television was made by RCA at Princeton, N.J. Checking the equipment are W. D. Houghton (left) and Dr. Harry F. Olson, director of the company's Acoustical Research Laboratory (right).



www.americanradiohistory.com

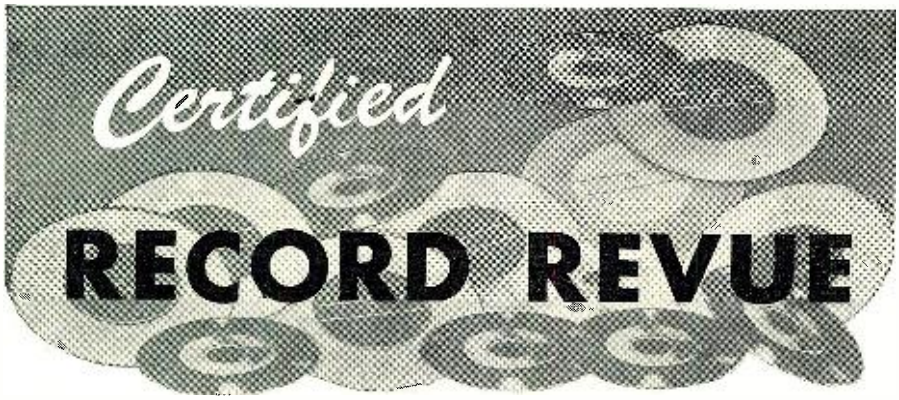

By **BERT WHYTE**

SOME months back, I commented on how the manufacturers of some pretty prosaic portable phonographs were labeling their products as "high fidelity." Since then, nearly every manufacturer in the radio field has come out with his particular version of the "Little Jim Dandy High Futility Phonograph." Not content with usurping the true meaning of the term high fidelity, they have ventured further afield with new advertising asininity. Now all the sterling equipment they make is not only "high fidelity," it is "three dimensional" and "stereophonic" as well!

These manufacturers don't bother with such niceties as stating that their unit produces "three dimensional *type,*" or "stereophonic-*like*" sound. They brazenly give advertising blurbs exploiting the full meaning of stereo-sound. That the portables, table-model, and other phonographs they manufacture *do not* and *cannot* reproduce stereophonic sound, goes without saying. There is not the slightest advantage in the sound of these units to condone this assault on the credulity of the lay public. The *only* thing these two and three speaker phonographs can give you is *sound dispersion* and diffusion. This principle of reproduction is as old as the hills and has been used by high-fidelity enthusiasts for many years. (At least by those who could afford the second or third speaker!) There is positively *no directivity* or *perception of depth* in the sound, as in the case of true stereophonic reproduction. O.K. So some jerks are selling the public a bill of goods; why am I so fired up? *Because of the irreparable damage this loose advertising can do to the cause of legitimate stereo-sound!* Remember, most of the outfits responsible for this lack of discretion are big, corporately and financially. Most honest-to-goodness high-fidelity manufacturers are nickel and dime deals compared with these whoopla merchants. This is most unfortunate, because the little fellow has no spare cash to get a message across to the public that they are being bilked. What can be done about this lamentable situation? Not very much, I'm afraid. This is one time we're really up the creek. You see, the main trouble lies in the very scarcity of "true" stereophonic sound itself.

Since the public has practically no opportunity to hear the real McCoy, they are deluded into thinking these diffuse sounds they hear represent stereophonic reproduction. I don't know how far all this can go; I wish there was some way in which the public could be made aware of the quality difference in true binaural and stereophonic *versus* these "diffuse" sounds issuing from the "high fidelity" and "stereophonic" phonographs. The fact that these "stereophonic" phonographs outnumber the real thing isn't going to make our task any easier.

The only possible solution is for the RETMA to adopt standards by which a unit could truthfully be labeled a high fidelity or stereophonic instrument. The RETMA is a powerful enough organization to police any manufacturer and make certain that the standards they set up are not abused. I have heard a rumor that such a standard is under consideration for adoption at the spring convention of the RETMA. I fervently hope so. I'd hate to see one of the most promising and exciting developments in audio die out by the killing off of public interest by a few greedy and unthinking manufacturers.

Equipment used this month: *Weathers* pickup and arm, *Rek-O-Kut* T12H, *Pickering* preamp-equalizer, *McIntosh* 30-watt amplifier, *Jensen* "Triplex" system in a *Read* "Fold-a-flex."

PROKOFIEV
CLASSICAL SYMPHONY
MOUSSORGSKY
NIGHT ON BARE MOUNTAIN
BORODIN
ON THE STEPPES OF CENTRAL ASIA
GLINKA
RUSSLAN AND LUDMILLA OVERTURE
Orchestre de la Societe des Concerts du Conservatoire de Paris conducted by Ernest Ansermet. London LL864, ffrr curve. Price $5.95.

Here is a tasty potpourri from *London.* To be sure, the works here recorded are nothing new or startling. Nevertheless, these present recordings have some values over the same works in other versions now in the LP catalogue. For one thing, on sound quality alone this disc is quite a few jumps ahead of previous issues. *London* has been turning out some really fine work in the past few months. In the "Classical Symphony" and in Moussorgsky's eerie tale, we have some of the finest *ffrr* sound yet recorded. Beautifully clean, silky strings with none of the harsh steeliness many people accuse *London* records of having. Percussion is crisp and bright without being what you might call "showy." Orchestral balance is excellent in all these works. A very live sounding recording, with just the right amount of reverberation in the hall to enhance this presence. The performance of the "Classical" is beautifully detailed and meticulously wrought. However, you don't have to listen beyond the first few bars to realize that something is very different about this reading. You become aware of very odd tempi, indeed the slowest pace on record. Let me assure you that this choice of tempi was not just a whim of Mr. Ansermet. He predicated this reading on the basis of his friendship with Prokofiev himself and what Prokofiev told him as regards tempi and dynamics, etc. According to Ansermet, the slow pace is just the way Prokofiev intended his "Classical Symphony" should be played. In view of the fact that nearly everyone else who has conducted this work fairly zooms through it, this performance takes a little time to become familiar enough to be comfortable. In a cursory analysis, you find that you rather like this new treatment. It lends the score a stateliness which is in keeping with Prokofiev's original intent. Certainly this dissimilarity with the other available recordings at least makes for renewed interest in this too-often duplicated work. This, plus the superb sound go a long way towards reckoning this version as the best available.

The Moussorgsky, "Night on Bare Mountain" is a real humdinger. This is one of the most superb examples of good acoustical balance extant. The recording is so very much better than that which *London* ordinarily produces (and *London* must be considered among the top rank recording companies) that I am inclined to suspect that something "new" has been added. A better hall? A clever new pickup? A "hotter" and better mike? Or possibly an advance in the type of cutterhead used in transfer from tape to disc? (Any comments, Mr. Farkas?) In any case, this is wonderful sound and we hope to hear more of the same. Performance wise the Moussorgsky receives the usual lavish attention to detail that is characteristic of Mr. Ansermet. His reading is perceptive, and in a score which is obviously programmatic, he manages to evoke the proper emotion. A very good reading, but no one as far as I am concerned, has ever equalled the old Stokowski version on 78 rpm. In spite of the restricted range, dynamic and frequency wise, when he had that

(*Continued on page* 168)

The opinions expressed in this column are those of the reviewer and do not necessarily reflect the views or opinions of the editors or the publisher of this magazine.

www.americanradiohistory.com

KNOW YOUR 954 ADMIRAL TV RECEIVERS

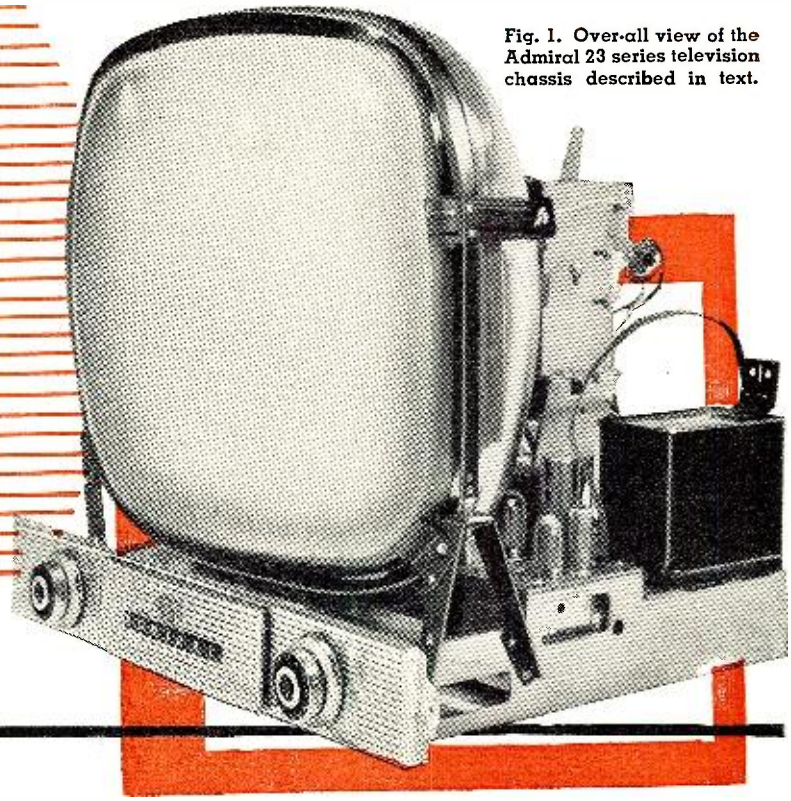


Fig. 1. Over-all view of the Admiral 23 series television chassis described in text.

By
SERVICE DEPT., ADMIRAL CORPORATION

Circuit operation, schematic diagram, alignment data, and other servicing information for 1954 Admiral sets.

AFTER eight years of commercial television transmission and reception, receiver circuitry has reached the stage where more and more time can be devoted to circuit refinement and less and less time to basic circuit changes. This is true for all manufacturers and it is especially true of *Admiral's* 1954 line. The new chassis, for example, contains, among other new features, an improved deflection yoke that provides the 90-degree deflection angle required by the 27-inch picture tube. There is also an improved focusing circuit, a more efficient low-voltage power supply, a sturdier damper tube (6V3), a new vertical output tube (6AV5GT), and a redesigned horizontal output circuit that provides better operation with more flexible control. Each improvement, by itself, is significant; taken together, they represent a considerable advance in the television art from the early days of not-so-long-ago 1946.

Circuit Description

R. F. Section. Circuit-wise, the 1954 *Admiral* 23-series receiver (shown in Fig. 1) follows closely the arrangement established by its predecessor, the *Admiral* 22-series chassis. A low-noise dual-triode 6BZ7 is used in the tuner r.f. amplifier. The circuit (see Fig. 2) is the familiar cascode amplifier which provides higher gain, with reduced noise level, than previous types, and results in a clearer picture in weak-signal areas. Characteristic of the cascode circuit is the direct coupling between the plate of the first triode and the cathode of the second section. Thus, a common current flows through both tubes and a.g.c. bias applied to the first triode grid will be effective for both tubes. Further, since the cathode of the second triode is about 120 volts positive with respect to chassis ground, a voltage divider consisting of resistors R_{111} and R_{112} places the second triode grid at a sufficiently positive potential for proper operating bias with respect to the cathode. R_{110} is a filter resistor.

The oscillator is of the Colpitts type. The tuned circuit consists of L_{102C} and condensers C_{109} and C_{111}, with L_{102C} inductively coupled to mixer grid coil L_{102B} for oscillator injection to the mixer. Condenser C_{109} has a negative temperature coefficient and decreases in capacity with an increase in temperature. Since this action is opposite to that of conventional condensers, it tends to prevent oscillator drift with temperature changes. The fine tuning control is a variable dielectric condenser C_{111}. Further, each channel may be adjusted separately by means of a slug (in L_{102C}) which is accessible from the front of the set.

The oscillator voltage and the incoming signal are combined in the mixer to produce the i.f. signal. Two resistors are used in the mixer grid circuit in order that their junction can be brought out as an alignment test point ("W"). An oscilloscope can then be connected to this point without affecting the operation of the circuit.

Video i.f. System. The output of the r.f. mixer is coupled to the 1st i.f. amplifier V_{301} through two tuned circuits which have a common coupling impedance. L_{103}, C_{112}, and the coupling network combine in a circuit which is tuned to 25.3 mc. by L_{103}. L_{309} and the input capacity of V_{301} combine with the the coupling network to form a circuit which is tuned to 25.3 mc. by L_{309}.

The common coupling impedance includes three tuned circuits. C_{121} and L_{108} form an absorption trap tuned to 19.75 mc. to eliminate the video carrier of the adjacent higher channel. C_{123} couples the output of the r.f. mixer to the 19.75 mc. trap. C_{122} and L_{107} are series resonant at 27.25 mc. to eliminate interference from the sound carrier of the adjacent lower channel. L_{110} is added across these two traps and the entire coupling network becomes parallel resonant at 23.5 mc., which is midway between 19.75 mc. and 27.25 mc.; C_{124} is a d.c. blocking condenser.

The video and sound signals are amplified together in the i.f. system. T_{301} and T_{302} are bifilar-wound transformers that are stagger-tuned to obtain a broad over-all i.f. amplifier response. T_{303} is an impedance coupling between the 3rd i.f. amplifier and the video detector V_{304A}.

The i.f. amplifier response is approximately 3.9 mc. at the 6 db points (50 per-cent down from peak amplitude). L_{310} and C_{324} form an absorption trap for the sound carrier (21.25 mc.) at the input to the 2nd i.f. amplifier, V_{302}. This reduces the sound carrier amplitude to maintain a 10 to 1 ratio between the picture and sound carriers. This is required to prevent sync buzz in strong signal areas. Also, this 21.25 mc. trap, combined with the re-

www.americanradiohistory.com

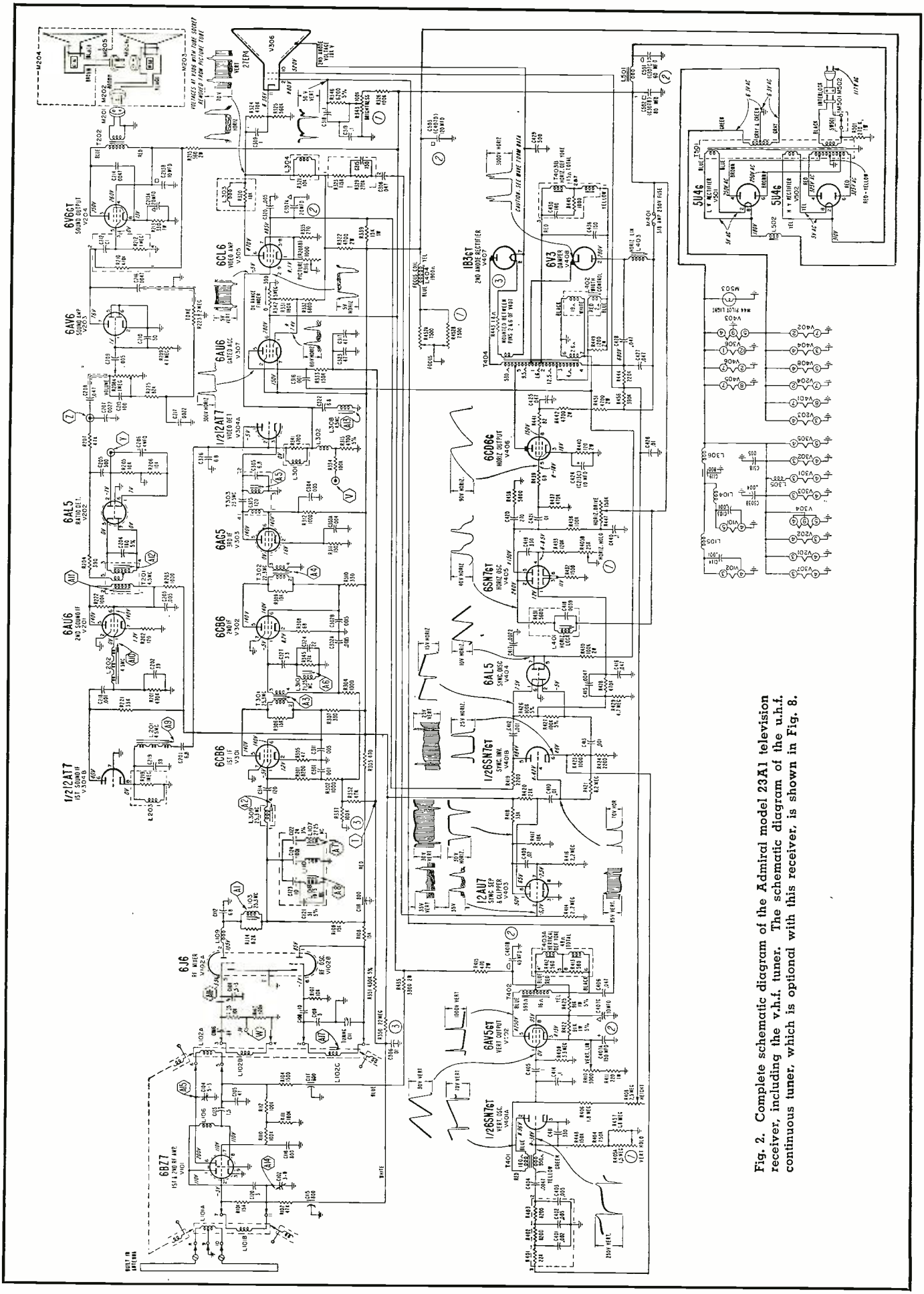


Fig. 2. Complete schematic diagram of the Admiral model 23A1 television receiver, including the v.h.f. tuner. The schematic diagram of the u.h.f. continuous tuner, which is optional with this receiver, is shown in Fig. 8.

www.americanradiohistory.com

sponse characteristics of the coupling network between the output of the r.f. mixer and the 1st i.f. amplifier, results in a "step" or "plateau" on the i.f. amplifier response curve in the region of the 21.25 mc. sound i.f. carrier. This permits adjustment of the fine tuning control over a rather wide range without greatly affecting the sound level. This is of particular importance in fringe areas, where the receiver is often tuned for blackest picture, with the result that the video carrier i.f. frequency of 25.75 mc. falls near the top of the i.f. response curve. Without the "step" or "plateau" for the sound i.f. carrier, the sound level would be so low under these conditions that it would not be possible to achieve satisfactory sound level coincident with maximum picture contrast in weak signal areas.


Video Detector and Amplifier. The video detector is conventional, using a diode to demodulate the i.f. signal. Series and shunt peaking coils serve to maintain the response of the circuit to all of the video frequencies.

Direct coupling is utilized between the detector and the 6CL6 video amplifier that follows it. This results in transfer of the d.c. component together with limiting of noise peaks. Picture (contrast) control R_{316} is a degeneration control in the cathode return circuit. It provides video amplifier gain control by placing a variable opposing signal voltage in series with the input signal voltage applied between grid and cathode of video amplifier V_{305}.

The screen voltage for the video amplifier (and the plate supply for sync inverter V_{401B}) is supplied through dropping resistor R_{339}. Electrolytic condenser C_{307A} does the major portion of the filtering here, although C_{320} is added for more effective bypassing of the higher video frequencies. In the plate circuit, over-all response is again given careful consideration by the use

Table 1. Alignment procedure for the video and sound i.f. systems of the Admiral 23 series chassis.

VIDEO I. F. ALIGNMENT

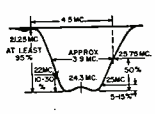STEP	SIGNAL GENERATOR FREQUENCY	SIGNAL GENERATOR CONNECT TO	OUTPUT INDICATOR	CONNECT TO	ADJUST	REMARKS
1	25.3 mc. unmodulated	Tube shield of 6J6 (V_{102}). (Insulate shield from chassis.) Low side to chassis near 6J6 tube base	V.T.V.M.	Test point "V" and chassis	"A_1," "A_2," and "A_3" for maximum	Connect minus side of a 3-volt bias battery to the a.g.c. bus at test point "T." Use lowest scale on V.T.V.M. Set channel switch to channel 12 or other unassigned high channel. When peaking, reduce generator output to give 1-volt maximum reading. See Fig. 4 for test points.
2	22.3 mc. unmodulated	Same as above	V.T.V.M.	Same as above	"A_4" for maximum	
3	23.5 mc. unmodulated	Same as above	V.T.V.M.	Same as above	"A_5" for maximum	
4	21.25 mc. unmodulated	Same as above	V.T.V.M.	Same as above	"A_6" for minimum	
5	27.25 mc. unmodulated	Same as above	V.T.V.M.	Same as above	"A_7" for minimum	Connect minus side of 1½-volt bias battery to a.g.c. bus. Set channel switch between channels.
6	19.75 mc. unmodulated	Same as above	V.T.V.M.	Same as above	"A_8" for minimum	
7	25.3 mc. unmodulated	Same as above	V.T.V.M.	Same as above	"A_1" and "A_2" for maximum	Use 3-volt bias battery. Set channel switch as for step 1.
8	23 mc. center frequency. 7 mc. sweep	Same as above	Oscilloscope	Test point "V" through decoupling network (10,000-ohm series resistor, 330-$\mu\mu$fd. shunt condenser to ground)	All i.f. slugs for curve below 	

SOUND I. F. AND 4.5 MC. TRAP ALIGNMENT

9	4.5 mc. unmodulated	Test point "V" through .01-μfd. condenser	V.T.V.M.	Test point "Y"	"A_9," "A_{10}," and "A_{11}" for maximum	Use lowest d.c. V.T.V.M. scale
	or					
10	Tune in local TV station.		V.T.V.M.	Test point "Z"	"A_{12}" for zero reading. (Between positive and negative maximums.)	Use zero-center scale on V.T.V.M. If "A_{12}" was far off, repeat step 9
11			V.T.V.M.	Test point "Y"	"A_{13}" for minimum	Use lowest d.c. V.T.V.M. scale. Connect a 10-$\mu\mu$fd. condenser from pin 6 of V_{305} (6CL6) to pin 8 of V_{304} (12AT7)

www.americanradiohistory.com

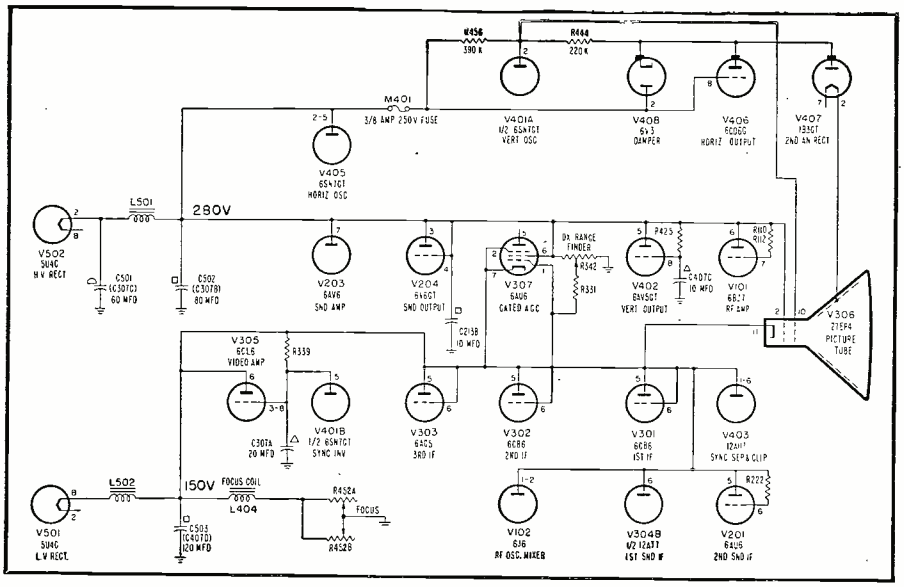



Fig. 3. Simplified diagram of the "B+" distribution in the Admiral 23A1 TV chassis, stamped "Run 2" or higher. Note the two "low-voltage" power supplies.

of two peaking coils (L_{303} and L_{304}) and a low-value load resistor (R_{322}).

As a final step in this chain, the video signal is coupled to the cathode of the picture tube by C_{309}, R_{324}, and R_{325}. Picture brightness is varied by R_{343}.

Sound System. Returning to the video second detector, it will be seen that a portion of the total signal is coupled through C_{201} and L_{201} to the cathode of V_{304B}, the first sound i.f. stage. The sound signal frequency is 4.5 mc. and C_{201} is purposely chosen small in value so that it offers a higher impedance to the video signals which are lower in frequency. The cathode connection of L_{201} is employed to eliminate oscillation that often occurs in a tuned-grid, tuned-plate amplifier circuit. L_{203} provides a d.c. path for the cathode current of V_{304B}. C_{219} and L_{203} form a high impedance for the 4.5 mc. sound i.f. voltage applied to the cathode.

Fig. 4. (A) Top view of chassis showing alignment points and test points used with particular adjustments. (B) Bottom view with test points located.

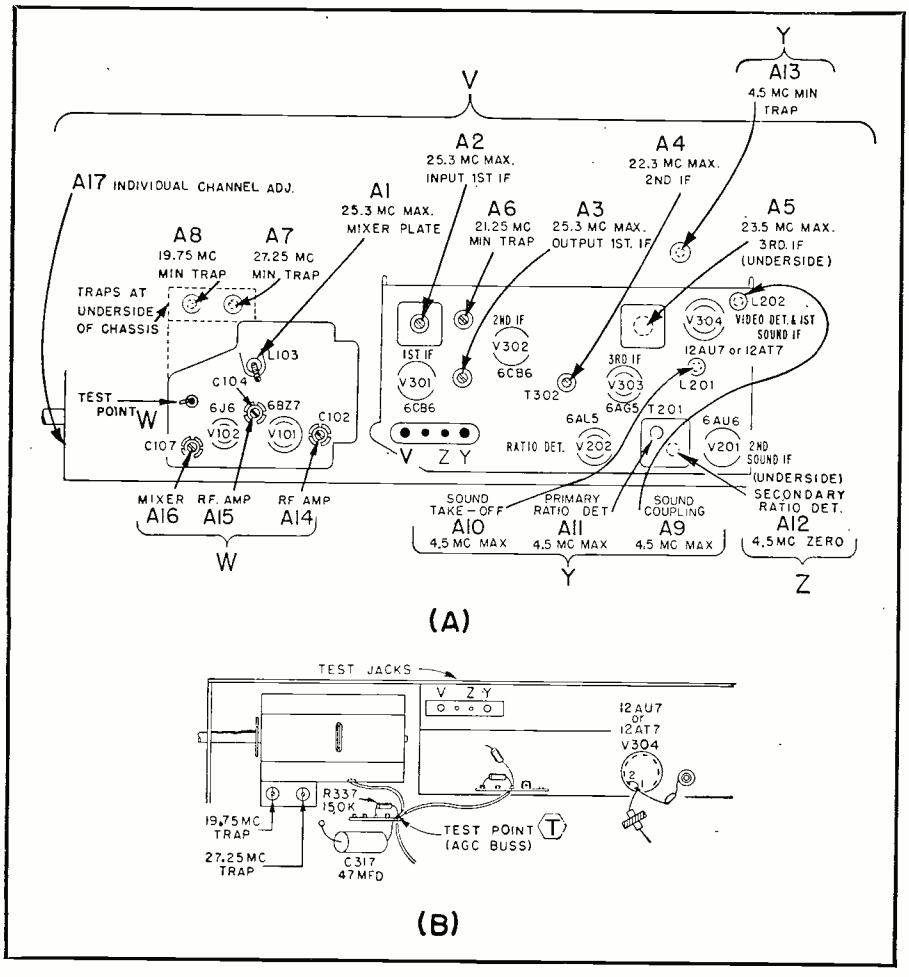

The coupling network between the 1st and 2nd sound i.f. amplifiers consist of C_{218}, C_{202}, L_{202}, stray wiring capacity, and the input capacity of V_{201}. C_{218} is a coupling condenser. The remainder of the network forms a resonant pi-filter. Due to the impedance ratio between the pi-filter input capacity (C_{202}) and the output capacity (stray wiring and tube input capacity), the coupling filter provides a four-to-one voltage gain. This gain, however, could not be realized without the use of a high-"Q" coil. L_{202} is slug-tuned for an alignment adjustment. R_{201} is used merely as a grid return.

The remainder of the sound system follows conventional practice. A ratio detector converts the FM to audio and then a 6AV6 voltage amplifier and a subsequent 6V6 power amplifier raise the audio signal to the level needed to drive two 10-inch PM speakers. The voice coils of these speakers are matched and phased to each other and T_{202} matches them to the output amplifier.

A.G.C. System. Automatic control of the receiver gain is exercised by a gated a.g.c. circuit. As is usual in such arrangements, the grid of the a.g.c. tube (V_{307}) is supplied with the composite video signal voltage (by direct coupling through R_{332}) from the output of the video amplifier V_{305}. Pulsed voltages, developed during the horizontal retrace time, are coupled to the plate of V_{307} through C_{316}. Thus, the a.g.c. tube conducts only during the horizontal sync pulse interval and the level of the control voltage developed is established by the level of the received sync pulses.

The amount of a.g.c. voltage developed is also controlled by the "DX Range Finder" (R_{342}), a potentiometer located in the control grid circuit of the a.g.c. tube. The center tap of the control is connected to the grid of V_{307} through R_{331}. This provides a variable means of setting the bias on the control grid of V_{307}. The "DX Range Finder" also provides for higher gain in fringe areas resulting in more contrast, increased sync stability, and reduction of "flashing."


Caution must be exercised in setting the "DX Range Finder." The control is calibrated from 0 to 300, but the numbers themselves have only a relative meaning. At the "0" setting, maximum a.g.c. is developed. As the control is advanced toward "300," less and less a.g.c. is developed until, at maximum setting of the control, minimum a.g.c. is produced and the gain is greatest. Since the control determines the amount of a.g.c. voltage reaching the controlled tubes, and consequently the gain of the receiver, a too-high setting of this control can result in

(*Continued on page* 140)

www.americanradiohistory.com

THE *Music Probe* FOR FASTER SERVICING

By
STAN JOHNSON, WØLBV

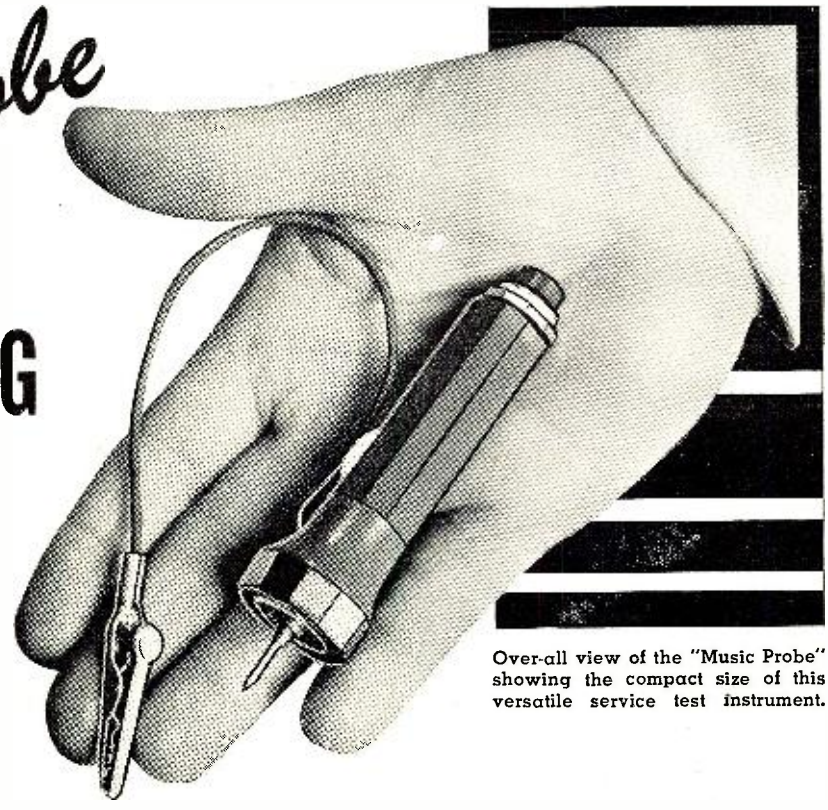

Over-all view of the "Music Probe" showing the compact size of this versatile service test instrument.

This tiny "crystal receiver" unit provides a broadcast station program which can be used for signal tracing.

NINE times out of ten trouble in the audio end of a TV set lies in the ratio detector or associated circuits. But unless you have an "Ouija" board ear—you may be *very* wrong on the tenth set—and spend a lot of time looking for trouble in the r.f. section of the receiver when actually the grief is simpler: plain old audio distortion.

Obviously what is needed is some sort of simple audio generator—small enough to tuck into the service kit along with tools, tubes, and small parts. To provide such a device, the "Music Probe" was designed. It is very little larger than the r.f. probe for the *"Voltohmyst."* But it actually generates music (or voice) with sufficient output to swing the speaker on the business end of any TV set with only one stage of amplification.

The "Music Probe" has some other highly useful qualities, too. Enough so that it has become a permanent part of the writer's test gear.

For example, it is highly useful for running a quick check on the video amplifier. And it is very helpful in servicing AM (including a.c.-d.c.) sets, too, thus providing a 10 second way to isolate trouble to "before" or "after" the volume control on a superhet.

The circuit diagram reveals the "secret" of the music. Actually the unit is a hot little crystal set, using a germanium crystal diode. It is built around the familiar *"Loopstick"*—which gives the crystal set a new lease on life. The *"Loopstick"* tunes the unit to the strongest AM broadcasting station in the area. The signal from this station is made available on the prod end of the probe for applying as an audio signal generator wherever desired in the set under test.

You will notice on the diagram that the unit uses an antenna coil. This was done so that the *"Loopstick"* could be set once and left alone—applying the antenna directly to the end of the coil would result in detuning with different lengths of antennas.


In using the probe, one of the test leads is borrowed from the v.t.v.m. and plugged into the jack on the end of the probe. *The other end is connected to the TV antenna lead-in,* which is disconnected from the TV set. The average TV antenna installation provides a lot of signal on the AM bands as well—which accounts for the good output from the probe. (If the TV set uses rabbit ears, clip the test lead to the finger stop on a dial phone, hot air register, etc. to provide an "antenna.")

Now—for using the "Music Probe."

First, suppose there is distortion in the sound of a TV set and replacing the ratio detector tube and other tubes has not helped.

Pull out the ratio detector—to silence TV sound signal. Then clip the lead on the probe to the chassis near


(*Continued on page* 172)

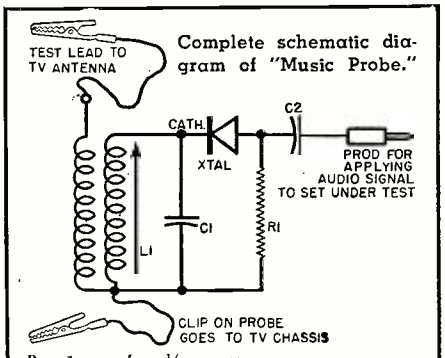

Complete schematic diagram of "Music Probe."

R_1—*1 megohm, ½ w. res.*
C_1—*100 μμfd., or larger, ceramic cond. (Value chosen to provide strongest AM signal in area when slug in coil is adjusted)*
C_2—*.01 μfd. ceramic cond.*
Xtal.—1N34A or similar crystal diode
L_1—*"Ferri-Loopstick" with 30 t. #30 en. wire closewound at bottom end to provide antenna coil*

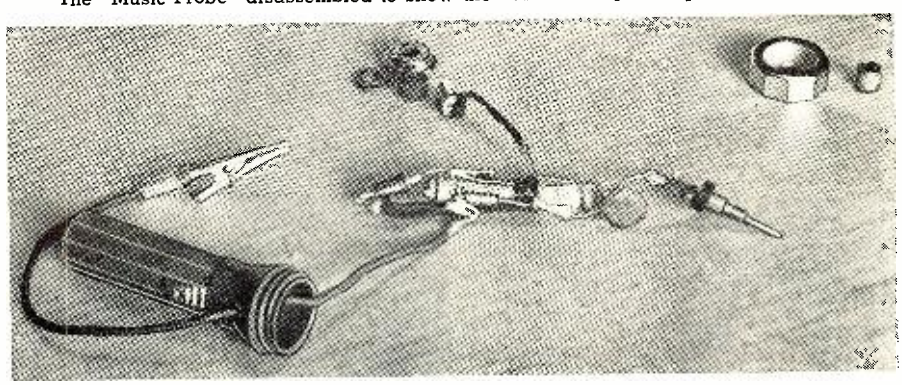The "Music Probe" disassembled to show the various component parts of the unit.



www.americanradiohistory.com

POSITIVE GRID CIRCUITS IN TV RECEIVERS

By
MILTON S. KIVER
Pres., Television Communications Institute

A positive grid does not always indicate a defective circuit; here are some that are normally positive.

THE television technician is frequently confronted with indications in television receivers which appear, at first glance, to run counter to the normal behavior of electronic circuits. One specific situation along these lines which is encountered with increasing frequency is a positive grid circuit, that is, tubes in which the grid is positive with respect to the chassis.

Now, one of the first lessons the beginner learns is that the grid potential should be negative. A positive grid, he is told, can lead to such dire consequences as circuit loading, distortion, and rectification and should be avoided like the plague. So you can imagine his shock when, in the course of taking voltage measurements in a receiver, he comes across a positive grid voltage. Here obviously is something wrong—or so he believes—and thereby wastes good servicing time on a circuit that is often operating perfectly.

Positive grid circuits can be divided into two categories—those which are positive with respect to chassis and cathode, and those which are positive with respect to the chassis only. In the latter group it will be found that the control grid is actually negative with respect to cathode, that is, the cathode has a higher positive voltage than the grid.

In view of the technician's previous instruction and the fact that all things bad are associated with positive grid circuits, why would any one want to utilize them at all? The answer is to be found in (*a*) certain effects which are obtained when the grid is made positive and (*b*) from the voltage distribution within a television receiver.

Let us consider proposition (*a*) first. We know that normally the grid is negative with respect to the cathode and under these circumstances electrons do not flow in the grid circuit. It is also generally accepted that under the same conditions the impedance between grid and cathode is very large. Actually, as we all know, the input impedance depends upon frequency, decreasing as the latter rises. However, for the purpose of this discussion, we will consider the grid-to-cathode impedance high if the grid is negative with respect to the cathode.

Now let us see what happens when the grid becomes positive with respect to the cathode. The grid wires attract electrons from the cathode and current flows in the grid circuit. To be exact, electrons flow from the grid, through whatever resistance exists in the grid circuit, back to the cathode again. As far as the cathode is concerned, the grid has become an element similar to the plate.

Fig. 1. (A) Simplified positive grid circuit showing the rectification (C) resulting from an input sine wave (B).


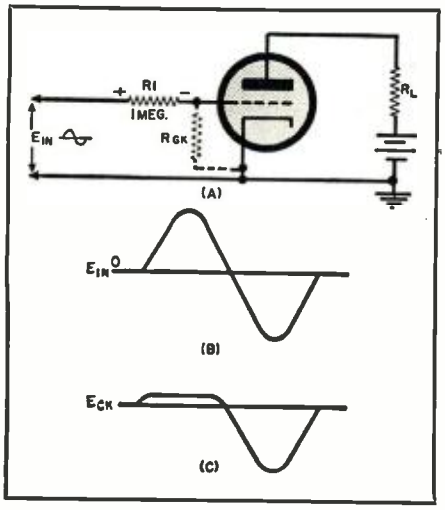


Fig. 2. Sync separator stage used by Philco operates with a positive grid similar to that of the tube in Fig. 1.

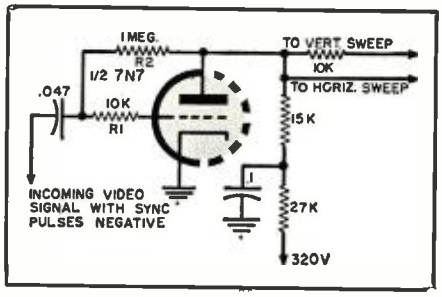

With the flow of current from cathode to grid, the resistance between these two elements has decreased. Thus, if 1 volt is applied between grid and cathode, and a current of .25 milliampere flows, then the external circuit sees a resistance of 4000 ohms. This is because:

$$E = IR$$
$$1 = .00025\,R$$
$$R = \frac{1}{.00025} = 4000 \text{ ohms}$$

Applying a larger positive voltage between grid and cathode will cause a larger current to flow and it will be found that the resistance decreases still further. Eventually it may drop below 1000 ohms.

With this behavior in mind, let us insert a resistance in series with the grid as shown in Fig. 1A. If a value of 1 megohm is used, this resistance will be considerably greater than the grid-to-cathode impedance when grid current flows. Now apply a signal, in the form of a sine wave, to the grid. See Fig. 1B. On the positive half cycle, the grid will be driven positive and grid current will flow. The current, flowing through R_1, will develop a voltage having a polarity opposite to that of the applied positive voltage. This voltage, subtracted from the applied voltage, represents what the tube receives. Thus, as R_1 is made larger, its voltage drop will approach that of the applied voltage. This will leave very little voltage between grid and cathode (Fig. 1C), with the result that very little will appear in the plate circuit. In other words, by this arrangement we have effectively suppressed the positive half cycle of the applied sine wave.

Throughout the negative half cycle, the grid is negative with respect to the cathode, no grid current flows and the full value of the applied negative voltage appears between grid and cathode. This is amplified and appears in the plate circuit.

We have here a form of limiter circuit and variations of this have appeared in television receiver sync separator circuits. Thus, *Philco* uses the circuit in Fig. 2 in its sync separator stages. A 10,000-ohm resistor is placed in series with the grid and then a 1-megohm resistor is connected between the end of the 10,000-ohm grid

www.americanradiohistory.com

resistor and the positive plate. This places a positive voltage on the grid and causes grid current to flow through R_1 and R_2. The combined resistance of R_1 and R_2 greatly exceeds the grid-to-cathode impedance so that the grid voltage is essentially zero with respect to ground.

Now, the video signal with the sync pulses negative is applied to this stage. The negative sync pulses drive the grid negative, forcing the tube current down and raising the plate voltage. Positive sync pulses are developed in the plate circuit by this action. The rest of the video signal, being more positive than the applied sync pulses, is unable to affect the grid-to-cathode voltage. This is because driving the grid more positive increases the grid current which increases the voltage drop across R_1. This increase, in turn, counterbalances the greater positive voltage. Result: the positive video signal portions of the applied signal are effectively suppressed, which is the desired action.

A situation which is somewhat similar to the foregoing is employed in a number of receivers to minimize the effects of noise. Such a circuit is shown in Fig. 5 and utilizes a 6BE6 sync clipper. The cathode of the tube is grounded, which places grid 3 at zero potential, initially. The video signal fed to this grid is obtained from the plate circuit of the first video amplifier and at this point the sync pulses extend upward, in the positive direction. The positive sync pulse tips drive grid 3 positive, current flows in this circuit and condenser C_1 charges up to the peak value of the sync pulses. Between pulses, C_1 discharges somewhat through R_1 but the amount of voltage lost is small and is replenished when the next pulse arrives. At this same instant, amplified pulses also appear in the plate circuit of the 6BE6. These are transferred to the succeeding sweep systems.

The average potential of grid 3 is negative. Consider, however, grid 1. It is tied into the video detector circuit and receives the full video signal with the sync pulses negative. At the same time, enough positive voltage is applied to grid 1 to offset the average negative voltage of the video signal. The resulting d.c. voltage at grid 1 thus hovers about zero, being slightly positive or slightly negative depending upon the average value of the incoming video signal and the setting of the "Fringe Lock" control. The positive portions of the applied video signal at grid 1 do not materially increase the voltage at this element because making grid 1 more positive draws more grid current and this, in turn, increases the voltage drop across R_2 and R_3.

The conditions are thus set so that with normal signals grid 1 permits electrons to flow through the tube.

Consider, now, what happens when a strong noise pulse arrives. At grid 1 it will extend in the negative direction and drive the tube into cut-off, shutting off the flow of electrons. This prevents the noise pulse, which is also at grid 3, from drawing grid current and consequently appearing in the output of the 6BE6 where it could disrupt sweep circuit operation.

The second class of positive grid circuits contains grids which are positive with respect to ground (or chassis) but actually less positive (*i.e.*, negative) with respect to the cathode. The technician runs into trouble with these circuits because voltage measurements are frequently made with respect to chassis and when a positive grid is uncovered in one of these voltage checks, the unwary service technician feels that here is the seat of his trouble.

Positive grid circuits of this second type appear in a variety of stages. Take, for example, the keyed a.g.c. tube shown in Fig. 3. Note that the control grid of the 6AU6 is tied directly into the plate circuit of the 12AT7 video amplifier and therefore it has a positive voltage on it. To offset this, the cathode is returned to the 125-volt terminal of the power supply. Since the grid is positive by 115 volts, the difference between these elments is 10 volts, which is more than enough to keep the tube biased to cut-off.

The reason for this particular arrangement stems from the fact that the video signal applied to the grid of the keyed a.g.c. tube must have all the sync pulses aligned to the same level. To insure this, there is a d.c. path (here) from the video detector to the 12AT7 video amplifier and from the video amplifier to the 6AU6 a.g.c. tube. Inserting capacitive coupling between any of these points would remove the d.c. component of the signal and the level of the sync pulses would no longer be the same for all pulses.

In this same keyed a.g.c. system, the d.c. potential of the plate (with respect to ground or any of the other tube elements) is negative. This is because the plate is triggered by a positive pulse of voltage obtained from the horizontal output transformer. This pulse is several hundred volts in amplitude and it appears during the horizontal retrace interval at the end of every line. At this same instant, strong, positive horizontal sync pulses appear at the control grid of the 6AU6, overcome the 10 volts bias here, and drive the tube into conduction. The flow of current in the plate circuit develops a

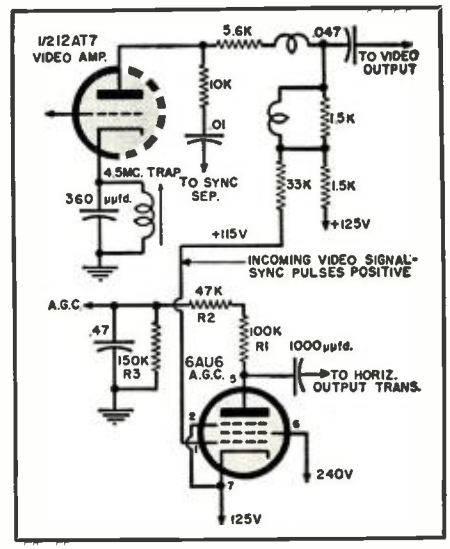


Fig. 3. A keyed a.g.c. stage in which the control grid is positive with respect to ground. The grid is, however, negative with respect to the cathode.

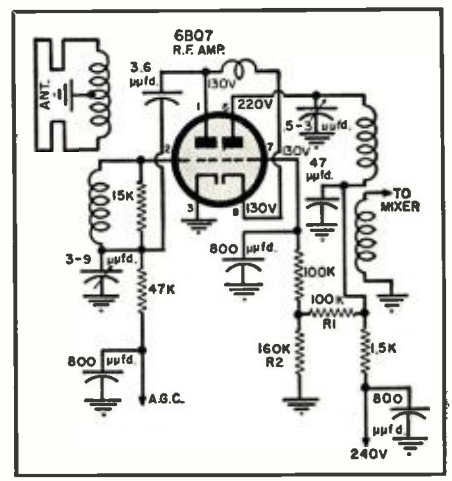



Fig. 4. Cascode amplifier circuit with the second tube section grid positive.

negative voltage across R_1, R_2, and R_3, and this negative voltage is fed, in part, to the r.f. and video i.f. stages as an a.g.c. voltage.

The introduction of the cascode r.f. amplifier also brought with it a positive grid circuit. This is shown in Fig. 4 where it can be seen that the plate of the first r.f. amplifier is tied directly to the cathode of the second r.f. ampli-

(*Continued on page* 116)

Fig. 5. Sync clipper stage which operates with a positive grid. See text.

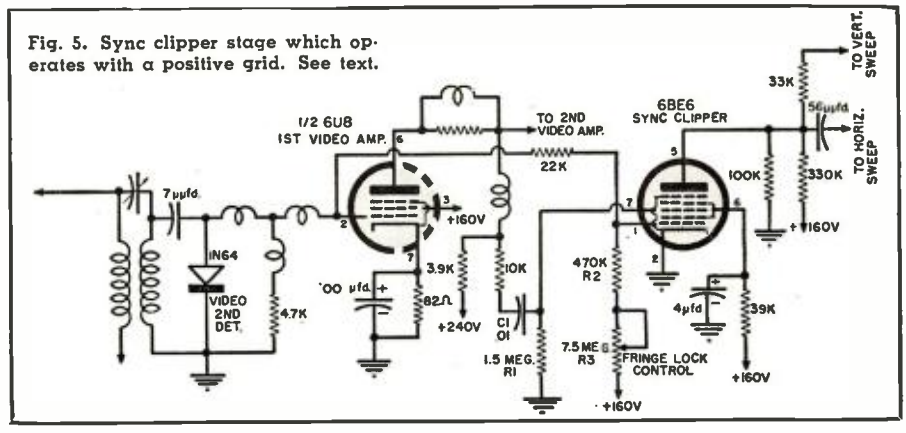

www.americanradiohistory.com

WAVEFORM TRACING AID

By **LOUIS E. GARNER, JR.**

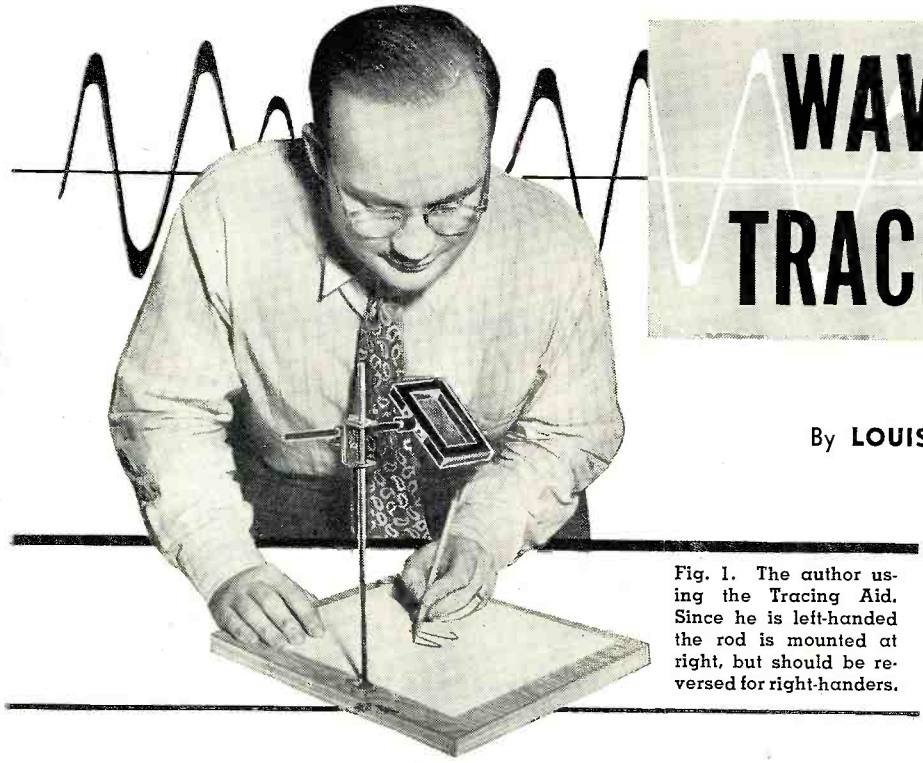


Fig. 1. The author using the Tracing Aid. Since he is left-handed the rod is mounted at right, but should be reversed for right-handers.

A handy device for experimenters and service technicians which permits scope traces to be recorded permanently.

DESIGN and development engineers often have occasion to record oscilloscope waveforms in new circuits. But recording waveforms for future reference may be of value to almost any worker in the technical side of radio, electronics, radar, or television.

The home experimenter, working with unfamiliar circuits, may wish to keep a record of the different waveforms obtained as circuit parameters are changed. The student finds an immediate need for some method of preserving the waveforms of circuits he studies. Even the technician, working on a new TV receiver, may wish to record "normal" waveforms in critical circuits for which service data is not yet available.

Several methods of recording scope patterns have been tried, and all have certain limitations. Free-hand sketching, for example, requires skill, and also makes it difficult to maintain accurate proportions in complex waves, as well as including the finer details. Direct tracing cannot generally be used, for even thin tracing paper diffuses the light too much and prevents a sharp image. Photography requires waiting until the film can be developed and printed, and thus is not suitable for immediate comparison when changes are made in the circuit.

An easily built and quite simple device, shown in use by the author in Fig. 1, permits oscilloscope waveforms to be recorded easily and quickly. The patterns obtained may be used immediately, as for comparing the input and output waveforms of a circuit, or for checking for variations in waveform with circuit changes. The patterns are full size and accurate as to detail.


Theory of Operation

Basically, the device consists of a special mirror (Fig. 6) which has about 50% reflectivity and 50% transparency. Thus, when the mirror is adjusted at a 45° angle (as shown in the sketch), the scope image is reflected over path *A-B-C* to the eye at the same time that the note pad can be seen over path *D-B-C*. The scope image, therefore, appears superimposed upon the note pad, and a direct tracing may be easily made, even by a comparatively unskilled operator.

The note pad may be graph paper, if desired, and thus the traced image will appear as on the scope screen.

Although a special mirror is indicated, this is obtained by a simple modification of a dimestore pocket mirror.

Fig. 2. How to prepare a dimestore mirror so that it can be used in setup. See text.

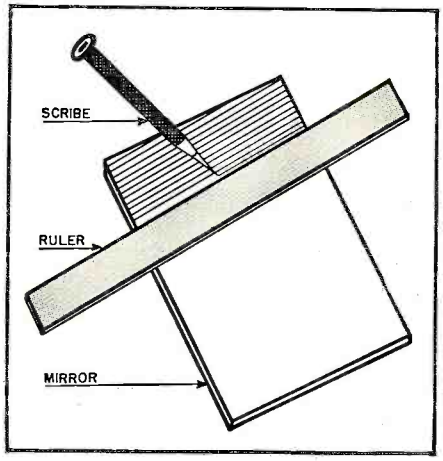

Preparing the Mirror

An ordinary dimestore pocket mirror may be changed to give about 50% reflectivity by removing approximately half the silver backing. This must be done by removing the silver in thin lines, so that the remaining silver is evenly distributed over the mirror.

To do this, lay the mirror face down on a table and use a ruler and a sharp instrument (scribe, sharp nail, icepick, knife, or similar tool) to scratch a series of parallel lines on the back as shown in Fig. 2. The lines should be fairly close (about 3/64") and enough pressure should be exerted on the scratching tool to remove the silver but not to scratch the glass.

Scratch four sets of lines in the silver backing . . . one set parallel to each side and two sets at a 45° angle, forming the pattern shown in Fig. 3. This pattern "breaks-up" the mirror and avoids the effect of lines. A soft cloth should be used to remove the dust formed as the silver backing is scratched off.

After completing this job, test the mirror by holding it at a 45° angle to make sure you can both see through it, and see a reflected image of objects in front of the mirror.

Mounting the Mirror

Use your own ingenuity in mounting the mirror. The scheme used by the author is shown in Fig. 4.

A block of ½" thick wood was cut out about ⅝" larger than the mirror used (all around). A rectangular hole was cut in the center of the block about 3/16" smaller than the mirror, and then a recess carved into one side in which the mirror could be fitted.

Mount a ¼" dowel (wood, plastic, or metal) in one side of the wooden block. The length may be anything from 5 to 8 inches.

Finally, the mirror is placed in the recess and held in place with tape. The author used black *Scotch* elec-

www.americanradiohistory.com

trical tape, completely covering the block and giving the final product the appearance of having been molded from plastic.

If preferred, a small metal plate may be cut out and used to hold the mirror in place. For that matter, the whole mounting may be made of metal, if desired, and if metal working facilities are available to the builder.

The next step is to prepare the clamp which holds the mirror at the proper height and at the correct angle. A simple clamp may be made from a small piece of sheet metal, a ¼" shaft coupler and a few small screws as shown in Fig. 5. The brass shaft coupler may be soldered to the sheet metal if steel is used, or screwed in place if aluminum sheet is employed.

Should the constructor have solid metal stock and metal-working facilities available, the clamp shown in Fig. 5 may be made in one solid piece, and the shaft coupler eliminated.

The dowel mounted on the mirror frame fits into the hole in the shaft coupler and set screw *"A"* used to lock it in place. Set screw *"A"* thus serves to adjust the angle of the mirror and to lock it.

A base plate is made by mounting a 3/16" rod on a piece of ½" plywood or board as shown in Fig. 7, and the clamp fitted over the rod. Set screw *"B"* serves to lock the clamp in position along the rod and thus serves as a height adjustment.

The 10" x 13" base plate serves as a "desk" for the note pad on which the patterns are traced. This size is adequate for a standard 8½" by 11" pad. If a smaller or larger pad is used, the size of the base may be changed accordingly. Too small a base will result in instability of mounting, however.

The author is left-handed, and therefore mounted the rod on the right side of the base, for ease in making sketches. If the user is right-handed, mount the rod on the left side of the base.

Finally, the mirror, clamp, base, and rod are assembled into the complete unit shown in Fig. 7. Once this is done, the device is ready for use.

Adjustment and Use

To use the Tracing Aid, first adjust the mirror to a 45° angle and lock it in place with set screw *"A"*. Place the device in front of the scope and adjust the height of the mirror until its center lines up with the center of the scope screen, locking it in place along the vertical rod with set screw *"B"*.

The eye is placed directly above the mirror, as shown in Fig. 6, and the device moved back and forth until distance *A-B* equals distance *B-D*. This is necessary so that the superimposed scope image will appear to fall on the surface of the pad and not above or below it. A check on this may be made by moving the eye forward and back. With the distance properly adjusted, the image stays in place on the

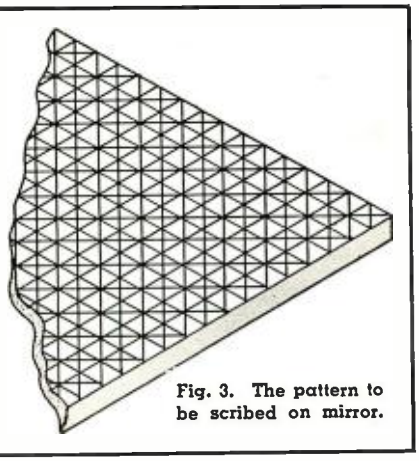


Fig. 3. The pattern to be scribed on mirror.

pad. If the distances are wrong, the image will appear to move over the surface of the pad.

Normal room lighting should be used so that the pad is well-illuminated. If sufficient light is not available, a desk lamp may used to light the pad directly.

The image on the screen of the CRO will appear superimposed on the pad, full size, and not distorted. It will be perfectly clear and sharp, and may be easily traced with a pencil or pen. A little practice is necessary at first, but the proper technique is soon acquired.

Since a reflected image is seen, it is inverted with respect to the pattern on the scope. If, for any reason, a "right side up" tracing is required, simply reverse the connections to the vertical deflection plates of the scope. These connections will generally be found on a plate on the back or side of the scope. Some scopes are provided with an "image reversing" switch in the front panel.

Application


Two typical patterns traced with this device are shown in Fig. 8. In 8A a saw-tooth is shown, and in 8B a sine-wave is illustrated. Note how sharp the peaks of the saw-tooth are and how clean the sine-wave is.

Probably the chief use to which the Tracing Aid will be put is for simply recording waveforms in circuits for future reference. It is ideally suited for this, since the tracings are full size and may be made on graph paper. If copies are desired, as in making reports, simply replace the pad with additional sheets with carbon paper between each sheet. Use a harder pencil, or a ball point pen, and apply somewhat greater pressure when making the tracing.

Another valuable application is in comparing the input and output wave-

(*Continued on page* 119)

Fig. 8. Patterns traced with the Tracing Aid. (A) a saw-tooth and (B) a sine wave.

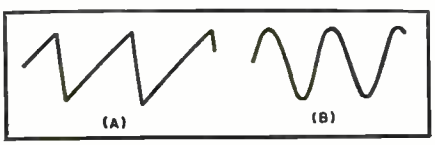

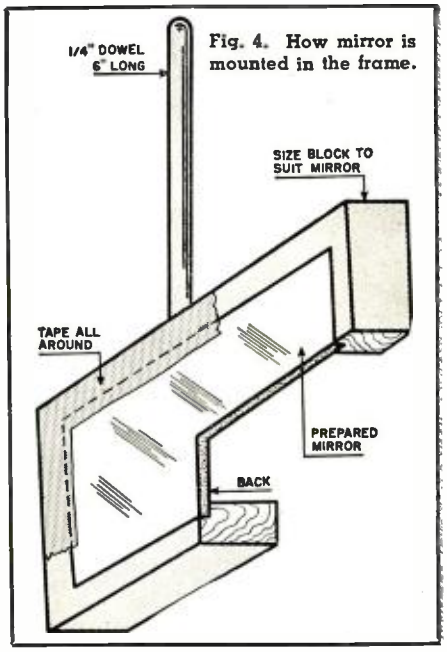


Fig. 4. How mirror is mounted in the frame.

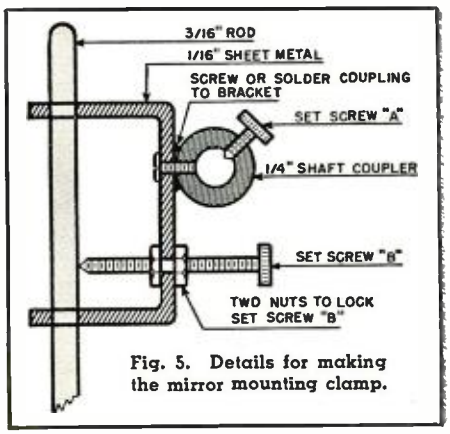


Fig. 5. Details for making the mirror mounting clamp.


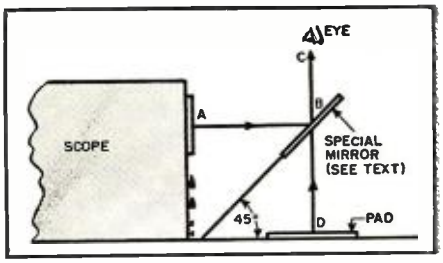


Fig. 6. Setup for tracing waveforms using the easily-built reflecting mirror device.

Fig. 7. Mounting rod on the plywood base. The mirror, clamp, base, and rod can then be assembled into complete tracing unit.

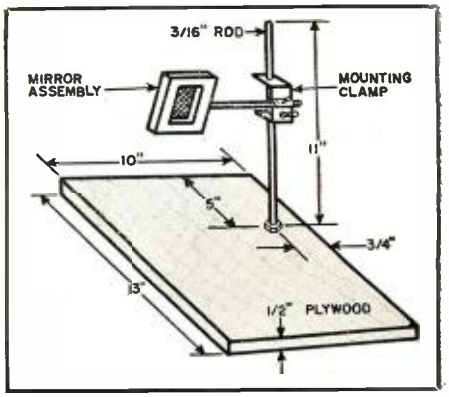

www.americanradiohistory.com

THE SCOTT 99-A AMPLIFIER

By
VICTOR H. POMPER
Hermon Hosmer Scott, Inc.

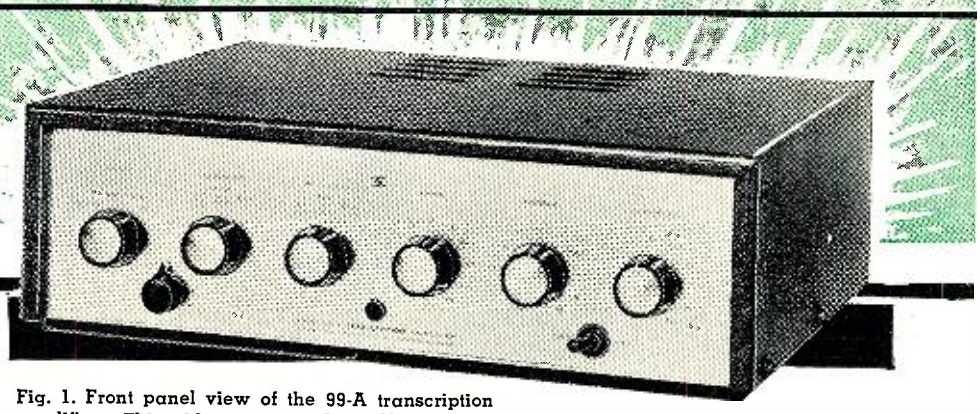


Fig. 1. Front panel view of the 99-A transcription amplifier. This 10-watt unit is self-contained.

Technical details on a 10-watt amplifier which includes a power supply, equalizer, and preamp on a single chassis.

THE new *Scott* 99-A transcription amplifier appears, at first glance, to be a "front end" or equalizer-preamp, yet actually it is a complete 10-watt amplifier, power supply, and equalizer-preamp—all packaged in a single cabinet measuring 13¼" x 3¾" x 9¾". See Fig. 1.

Since heat dissipation as well as the size were important, engineering studies made at the time this amplifier was being designed showed that a 10-watt power output would be most feasible. Higher power outputs would add considerably and undesirably to the size and would also dissipate too much heat to be radiated comfortably from a sheet metal cover. The 10-watt output proved satisfactory for reasons to be discussed shortly.

Beam power tetrode output stages were chosen for several reasons. The greater efficiency of the beam power tetrode meant less power lost in heat and more developed in sound output. This efficiency also allowed use of fewer driving stages which further decreased over-all heat and bulk. Considering all factors, use of beam power tetrodes meant a reduction in generated heat by almost two-to-one. The final system does not overheat, in fact, the metal cover becomes only moderately warm to the touch. The heat generated is conducted through, and radiated from, the plane surfaces of the all-aluminum chassis. Scientifically designed slots in the case, located directly above the output tubes, aid heat dissipation by the convection of heated air rising through these slots.

The reliable 6V6 output tubes were chosen because they produced the 10-watt output with less heat and less distortion than any other tubes tested. With carefully engineered inverse feedback, it is possible to achieve extremely low levels of distortion. At 10 watts, harmonic distortion is less than .8 per-cent. At full rated output the first order difference tone intermodulation distortion is less than .3 per-cent. This latter type of distortion is closely allied to that harsh, discordant growling most noticeable and offensive to the human ear. This distortion component measurement then represents the best criterion for determining over-all quality of a power output system.

Also engineered into the output system were the self-balancing phase inverter circuits which have been standard on *H. H. Scott* amplifiers for six years. These circuits automatically balance the output tubes, reducing distortion and making unnecessary any readjustments after replacement of output tubes in use.

Another factor of output systems receiving careful attention was the often overlooked requirement of clean, symmetrical clipping. On sudden peaks of music and sound, any amplifier will clip to some extent. Some amplifiers may indicate extremely low distortion levels up to their rated undistorted output, and yet above these ratings the clipping may not be clean and symmetrical. Ragged clipping causes extraneous damped transient effects, which sound very harsh and discordant, to be introduced. This was avoided in the 99 by careful engineering to insure that any clipping would be both clean and symmetrical. As long as this requirement is met, the human ear is unable to detect substantial amounts of clipping, and the over-all result is an output system which, though rated at 10 watts, gives performance audibly equal to much higher formal power ratings.

That a 10-watt power amplifier with associated power supply is incorporated into so compact an enclosure while still including sensitive low-level preamplifying and equalizing circuits, seemed to make the hum problem important. Since d.c. heater operation was not feasible because of space considerations, an all-aluminum chassis was used to minimize circulating and ground currents which, in

Table 1. Suggested equalizer settings for a variety of record labels.

33⅓ AND 45 RPM RECORDS

MAKE	TURNOVER	ROLL-OFF	MAKE	TURNOVER	ROLL-OFF
Atlantic	NARTB	LP	London	LP	AES
Bartok	AES	LP	Lyrichord (new)	AES	LP
Blue Note Jazz	AES	AES	Mercury	AES	AES
Caedmon	AES	AES	M-G-M	NARTB	AES
Canyon	AES	AES	Oceanic	LP	LP
Capitol	AES	AES	Philharmonia	AES	AES
Capital-Cetra	AES	AES	Polymusic	NARTB	LP
Cetra-Soria	LP	LP	RCA Victor	RCA	RCA
Columbia	COL	COL	Remington	NARTB	LP
Cook Laboratories[1]	NARTB	AES	Tempo	NARTB	AES
Decca	LP	LP	Urania (most)	NARTB	NARTB
EMS	AES	AES	Urania (some)	LP	LP
Elektra	AES	LP	Vanguard—Bach Guild	LP	LP
Esoteric	NARTB	AES	Vox	LP	LP
Haydn Society	LP	LP	Westminster	NARTB	LP

[1] For inside band of binaural records roll-off should be set at "Flat"

78 RPM

European recordings and old American recordings	EUR	EUR
Columbia	EUR	COL
London	LON	LON
Victor	RCA	RCA or FLAT

www.americanradiohistory.com

a steel chassis, would contribute to hum pickup. Positive bias on the heaters, together with an adjustable center-tapped, hum-bucking potentiometer, reduced hum still further, as did careful engineering of parts placement (Fig. 2) and shielding of all low level circuits. This attention to detail brought over-all hum to the unusually low level of better than 80 db below full output, a level comparable to that generally achieved only by d.c. on the heaters. See Fig. 4 for the schematic of the amplifier.

The over-all frequency response is flat from 20 cps to 30,000 cps. Above 30,000 cps the response is rolled off in order to prevent possible ultrasonic oscillation. Such oscillation is often caused by unavoidable stray coupling between external input and output connections when amplifiers have unnecessarily extended frequency response. While such oscillation is, in itself, inaudible to the ear, it overloads the amplifier, causing noise and distortion in the audible range.

Another feature, usually found only in higher priced amplifiers, is the sharp-cut-off rumble filter which prevents sub-audible overload below 20 cps. Unless the low-frequency response is limited sharply below the lowest audible notes, sub-audible signals may be generated by eccentricity of the record center hole and by turntable rumble. These sub-audible signals often are sufficiently large to cause amplifiers to operate in almost continuous states of overload. Acoustical feedback from the loudspeaker to the pickup cartridge is also decreased considerably by eliminating sub-audible, but high power, low-frequency signals.

For record equalization, separate three-position bass turnover and treble roll-off controls are provided. These separate controls are patterned after those first announced in the *H. H. Scott* 212-A amplifier which was catalogued in 1950 but only few made because of Korea and parts shortages. While two controls must be adjusted for equalization, this type of control is inherently a simpler and less costly means of equalization than the somewhat simpler-to-operate single control giving the complete equalization curve.

In order to give maximum equalization flexibility, a study was made of

(*Continued on page 122*)

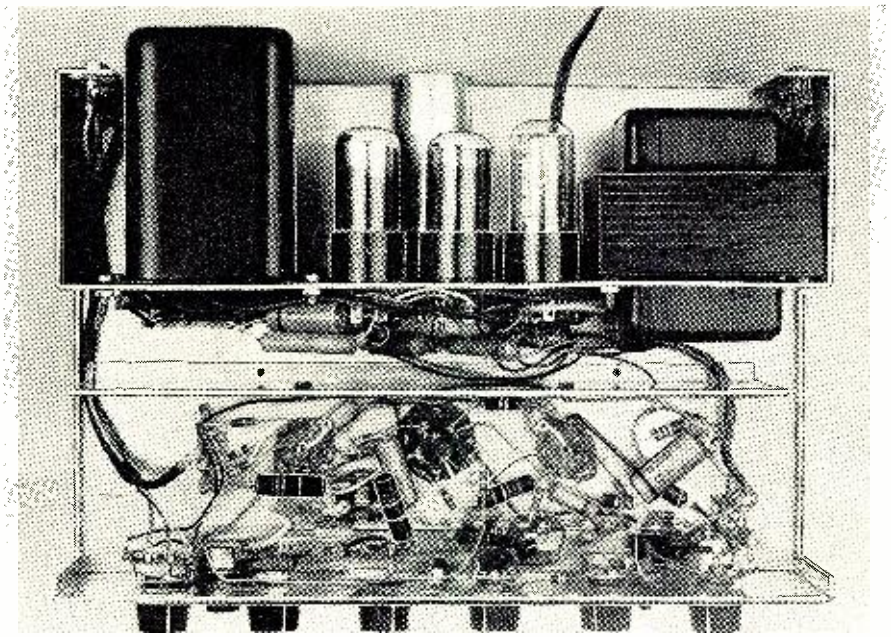


Fig. 2. Top view of the 99-A, showing major assemblies and parts placement.


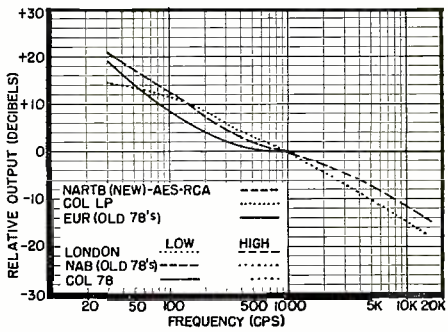


Fig. 3. Equalization curves for the 99-A. Data on other records is given in Table 1.

Fig. 4. Complete schematic diagram of the 99-A. The power supply and equalizer-preamp are housed on the same aluminum chassis.

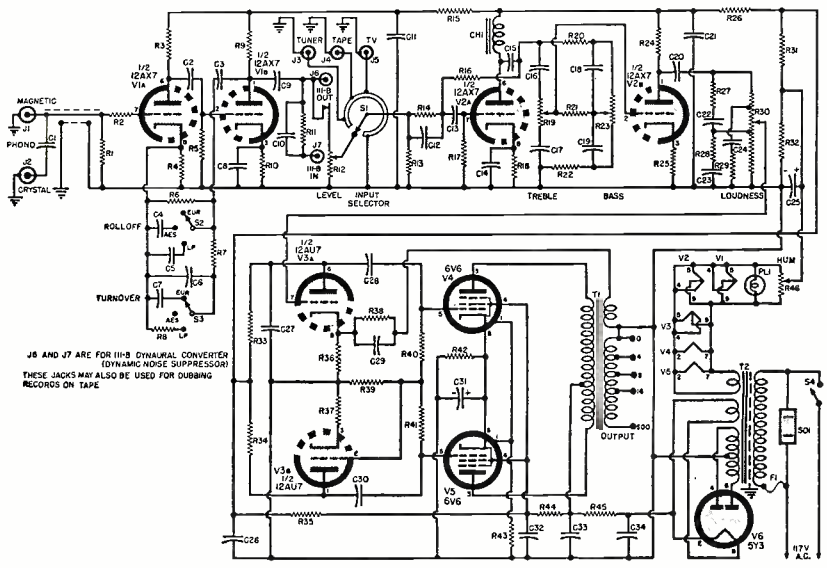


R_1, R_{15}, R_{28}, R_{39}—*47,000 ohm, ½ w. res.*
R_2, R_{26}, R_{38}—*15,000 ohm, ½ w. res.*
R_3, R_7, R_9, R_{41}—*270,000 ohm, ½ w. res.*
R_4, R_{10}, R_{43}—*2700 ohm, ½ w. res.*
R_5, R_{11}, R_{13}—*1 megohm, ½ w. res.*
R_6, R_{22}—*22,000 ohm, ½ w. res.*
R_8—*1.8 megohm, ½ w. res.*
R_{12}—*500,000 ohm pot*
R_{14}, R_{31}—*470,000 ohm, ½ w. res.*
R_{16}—*2.7 megohm, ½ w. res.*
R_{17}—*2.2 megohm, ½ w. res.*
R_{18}—*1000 ohm, ½ w. res.*
R_{19}, R_{23}—*1 megohm pot*
R_{20}, R_{40}—*220,000 ohm, ½ w. res.*
R_{21}, R_{24}, R_{33}, R_{34}—*100,000 ohm, ½ w. res.*
R_{25}, R_{36}, R_{37}—*1500 ohm, ½ w. res.*
R_{27}—*330,000 ohm, ½ w. res.*
R_{29}—*68.000 ohm, ½ w. res.*
R_{30}—*500,000 ohm pot (special Scott control)*
R_{32}—*33,000 ohm, ½ w. res.*
R_{35}—*4700 ohm, ½ w. res.*
R_{42}—*250 ohm, 10 w. wirewound res.*
R_{44}—*2000 ohm, 2 w. res.*
R_{45}—*400 ohm, 2 w. res.*
R_{46}—*500 ohm wirewound pot*
C_1, C_{16}—*100 μμfd. mica cond.*
C_2, C_3, C_{13}—*.022 μfd., 600 v. cond.*
C_4—*180 μμfd. mica cond.*
C_5, C_{27}—*470 μμfd. mica cond.*
C_6—*.0015 μfd., 600 v. cond.*
C_7—*680 μμfd. mica cond.*
C_8-C_{14}-C_{11}-C_{21}—*Single-can elec. cond. C_8, C_{14}—25/25 μfd. @ 25 v., C_{11}, C_{21}—10/10 μfd. @ 450 v.*
C_9, C_{28}, C_{30}—*.047 μfd., 600 v. cond.*
C_{10}, C_{29}—*220 μμfd. mica cond.*
C_{12}—*33 μμfd. mica cond.*
C_{15}, C_{19}, C_{20}, C_{24}—*.01 μfd., 600 v. cond.*
C_{17}—*.0022 μfd., 600 v. cond.*
C_{18}—*.001 μfd., 600 v. cond.*
C_{22}—*47 μμfd. mica cond.*
C_{23}—*.0047 μfd., 600 v. cond.*
C_{25}, C_{31}—*25 μfd., 25 v. elec. cond.*
C_{26}-C_{32}-C_{33}-C_{34}—*20/20/20/20 μfd., 475 v. elec. cond.*
S_1—*Special switch (Scott)*
S_2, S_3—*S.p. 3-pos. switch*
S_4—*S.p.s.t. switch*
CH_1—*250 hy. choke*
PL_1—*6.3 volt pilot light*
J_1, J_2, J_3, J_4, J_5, J_6, J_7—*Phono jack*
T_1—*Output trans. (special Scott unit)*
T_2—*Power trans. (special Scott unit)*

www.americanradiohistory.com

RESISTOR TRIAL BY TEST

By **GUY B. ENTREKIN**
Chief Product Eng., International Resistance Company

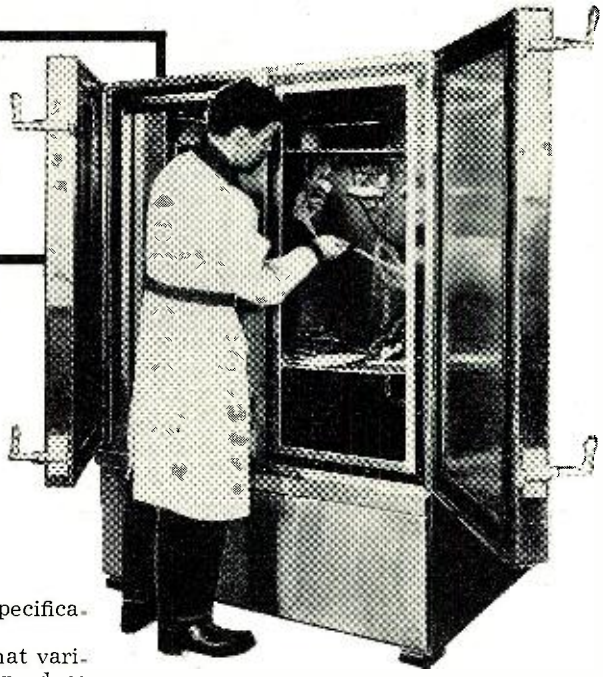Extensive laboratory tests insure reliable service from the components used in electronic equipment.



Moisture cycling box which can duplicate any humidity conditions called for by MIL specifications for testing resistors.

WE HAVE become so used to taking the reliability of electronic components for granted that we often forget "how they got that way." Since the performance of even the most elaborate equipment depends on many small and relatively inexpensive parts, the reliability of a 10-cent resistor is just as important as the most complicated tube.

One example of the lengths to which manufacturers go to insure the reliability of even small components is typified by the resistor testing program at *International Resistance Company,* Philadelphia. Its laboratory checks approximately a half-million resistors a year—putting them through a wide variety of tests to insure uniformity, quality, and performance.

For example, MIL specifications for all types of resistors require tests under load. These tests are made under conditions of various applied voltages and ambient temperatures. *IRC* utilizes several massive load-life ovens, like that pictured on this month's cover and on this page, to perform these load-life tests. Each of these precision-engineered ovens can test approximately 1200 resistors at a time and is uniquely designed to meet the variety of conditions necessary to fulfill military and customer specifications for load-life testing.

The ovens are designed so that various voltages can be applied to produce whatever wattages are specified in the test of a particular resistor. The resistors are supported in such a way that the heat dissipated by one resistor does not affect another unit being tested. "Still air," rather than circulating air, is maintained within the ovens as an added safeguard to guarantee conformity.

Another interesting aspect of MIL specifications for load-life testing is the requirement that ovens be equipped to feed loads intermittently to the resistors. During test, loads are normally applied for 1½ hours, then cut off for ½ hour, then applied for 1½ hours, alternating on and off for the full test period.

This intermittent application of the load produces a temperature cycling effect—important because continuing heating and cooling of any resistor introduces stresses similar to those obtained when equipment is turned on and off.

The actual voltages applied to resistors during test depend on their resistance range and ambient temperature of the test. These load-life ovens have a test voltage range of 0 to 750 volts—more than adequate for standard testing since the majority of all resistors test at 500 volts or less. For tests requiring the application of higher voltages, a specially designed oven in the test section is used.

Since the load-life ovens operate 24 hours a day, 7 days a week, automatic recording equipment and built-in safety devices of many types are used to give tight control over testing. In every test run, intermittent readings are taken to trace the pattern of resistance change with time. MIL specifications usually require at least four readings per thousand hours of test. More frequent readings are taken if tests require them.


Testing a single group of resistors may take six weeks or longer depending on the number and type of tests they must undergo. Where a shelf-life test is indicated, resistors are stored under the same or more severe conditions than they would encounter in a distributor's stock or in a local service shop, and are periodically tested for as long as three years. This test insures that resistors will not deteriorate in stock while awaiting use.

Resistor testing is an involved, lengthy, often laborious undertaking but it has made an invaluable contribution to the development of new and better electrical equipment and the amazing reliability of such gear under all conditions.

This is just one example of the infinite pains manufacturers take to insure uniform, inexpensive, and reliable components.

It is because of such painstaking procedures that U. S.-built electronic equipment has earned a reputation for excellent performance that is second to none in the world. —30—

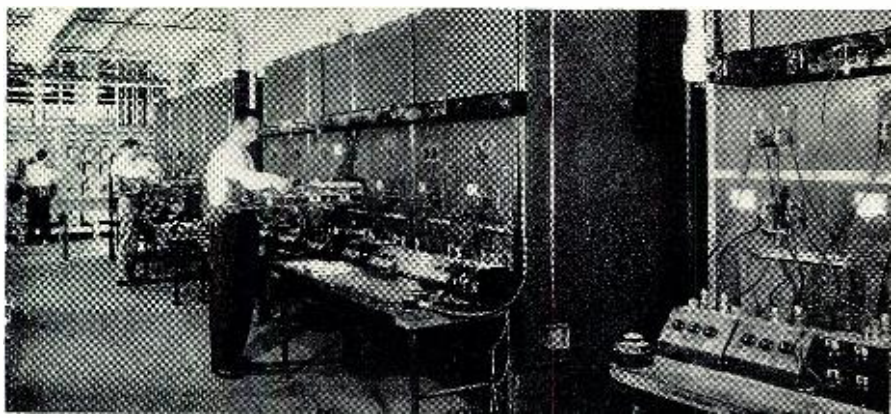These massive load-life ovens in IRC's resistor test section operate 24 hours a day, testing hundreds of resistors of every kind. Resistors hang in trays which are individually controlled at varying loads depending on the test being made.



www.americanradiohistory.com

A NEW LINE OF HI-FI SPEAKERS

By
HARRY F. OLSON and **JOHN PRESTON**
RCA Laboratories, Princeton, N. J.

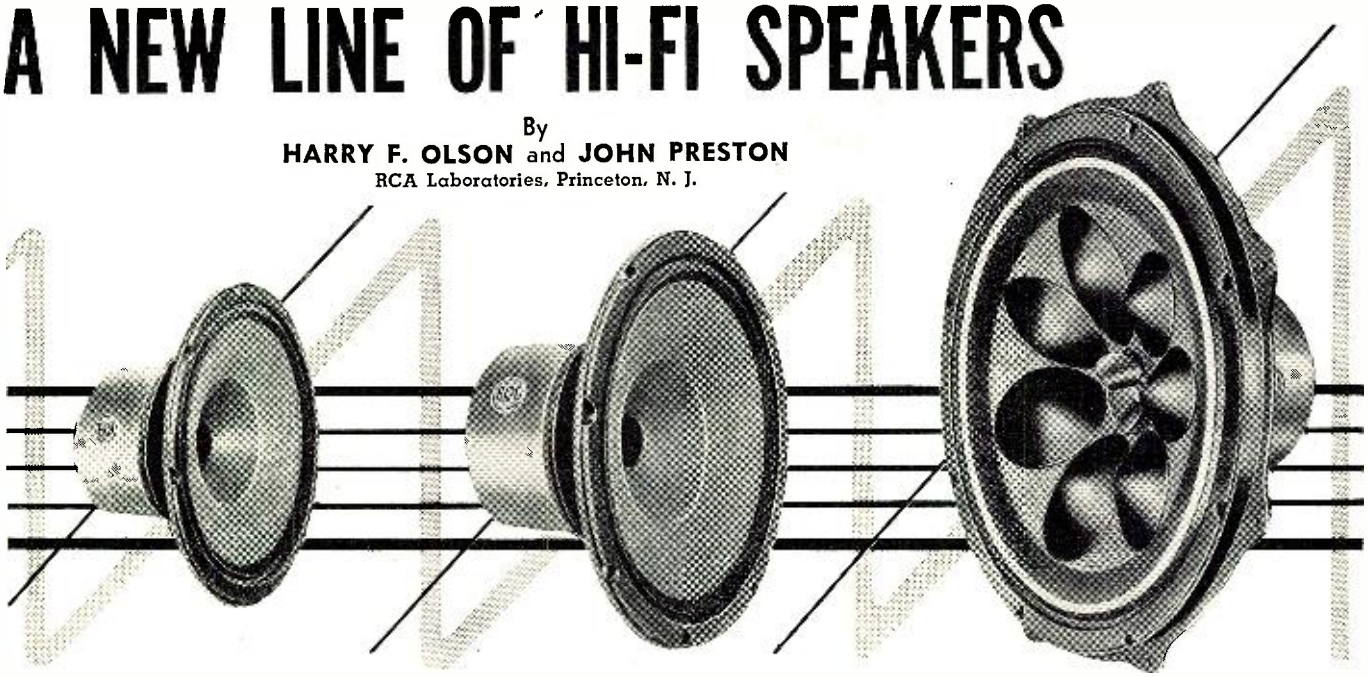


Fig. 1. (left) The RCA Type SL-8, 8-inch speaker. Fig. 2 (center) The Type SL-12, 12-inch unit. Fig. 3 (right) The 15-inch "Duo Cone" loudspeaker, the Type LC-1A.

Direct-radiator loudspeakers—RCA's final results of five years of research and development work

BEGINNING with the advent of radio, the direct-radiator, dynamic loudspeaker has been exclusively used with the electronically amplified disc phonograph, magnetic tape reproducer, and television in turn. Its use in home-type sound reproducing systems is due to the simplicity of construction, small space requirements, and the fundamental relationship between the acoustical resistance load and the total accoustical impedance of the vibrating system. In a properly designed loudspeaker, this fundamental relationship leads to a uniform response frequency characteristic. Extensive research and development during the past five years have resulted in many outstanding improvements in the performance of direct-radiator loudspeakers, including smoother response frequency characteristics, broader directivity patterns, improved transient response, and lower nonlinear distortion.

It is the purpose of this article to describe the results of these developments which have culminated in a new line of high-fidelity, direct-radiator loudspeakers.

High-Fidelity Loudspeakers

The *RCA* Types SL-8 and SL-12, shown in Figs. 1 and 2, are extended-frequency range, 8- and 12-inch, single cone speakers developed and designed for high-fidelity applications. Particular efforts were made to obtain a uniform response frequency characteristic. A loudspeaker without this characteristic will introduce frequency discrimination, will not exhibit good transient response, and will tend to accentuate noise. The smooth response characteristic exhibited by these loudspeakers was obtained by employing a particular shape of the curvilinear cone, a specially developed pulp for the material of the cone, and a damping ring in the outer suspension of the cone, which provides a matched terminating acoustical impedance for the cone.

The transient response is related to the response frequency characteristic. This relationship shows that a loudspeaker with a uniform response frequency characteristic will exhibit good transient response. In wide frequency range loudspeakers, it is important that the directivity pattern be broad and uniform in order to reduce frequency discrimination for observation points removed from the axis.

The shape and material of the cone play important roles in determining the directivity pattern of the loudspeaker and were selected experimentally.

Nonlinearity in a speaker occurs when the force *vs* displacement characteristic deviates from a straight line. In a lightweight cone this deviation occurs at a relatively small input, therefore, it is important that the cone be strong enough to handle the vibratory forces without producing distortion. These precautions were observed in this design.

The physical specifications for the *RCA* Type SL-8 are as follows: over-all diameter, 8½ inches; depth, 4¼ inches; magnet weight, 6.8 ounces; and electrical impedance, 8 ohms. The physical specifications for the *RCA* Type SL-12 are: over-all diameter, 12¼ inches; depth, 6⅛ inches; magnet weight, 14.5 ounces; and impedance, 8 ohms.

The Type LC-1A, shown in Fig. 3, is a "Duo Cone" loudspeaker. Every known acoustical principle, both theoretical and experimental, that would result in an improved loudspeaker, has been employed in the research, development, and design of this unit. The Type LC-1A[1] was first announced and demonstrated[2] at Tanglewood, Massachusetts, in July 1947. Since that time, it has been sold to broadcast and television stations, recording studios, and other users of high-quality sound installations.

One of the outstanding features of the original LC-1A speaker was its broad directivity pattern. This has been broadened even further in the new design and the response frequency characteristic made more uniform. These characteristics have been obtained by the use of the following new features: a series of conical domes placed upon the surface of the large cone; a damping ring in the outer suspension of the large cone, which provides a matched terminating acoustical impedance for the large cone; and a multiple vane deflector in front of the high-frequency cone. The series of cones breaks up the symmetry of the unit and thereby eliminates interference which normally characterizes a symmetrical shape. The high-frequency efficiency is improved because the solid angle into which the high-frequency cone operates is reduced, thereby increasing the acoustical load imposed upon the small cone. At the same time, the conical diffusers increase the distribution angle due to a reduction of the propagation velocity in the low-frequency cone and due to

www.americanradiohistory.com

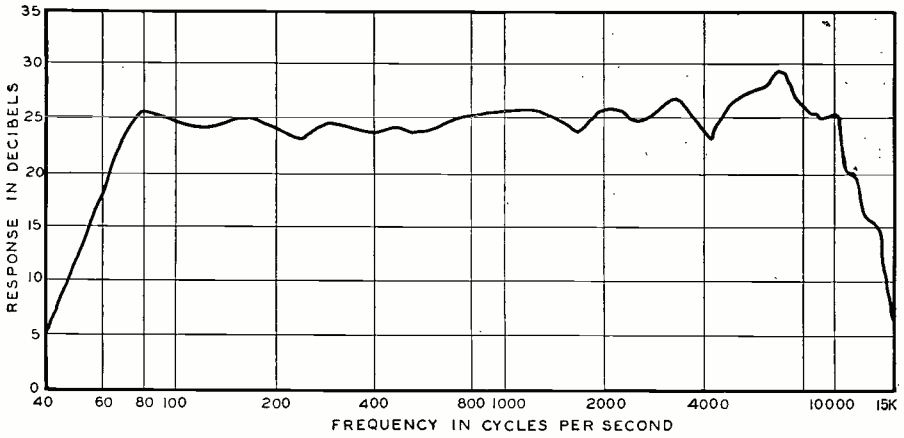


Fig. 4. Response frequency characteristic of the RCA Type SL-8 loudspeaker.

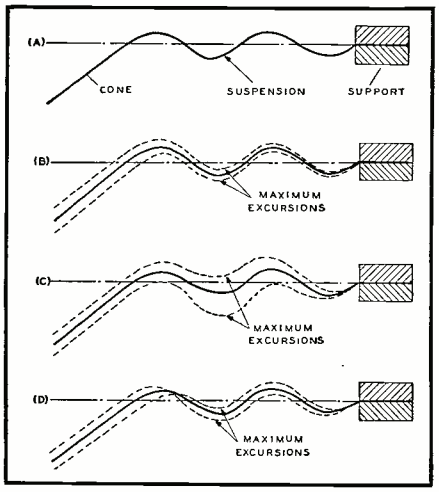


Fig. 5. (A) Outer suspension for a direct-radiator speaker, (B) normal vibration of the suspension, (C) resonant vibration of the suspension in-phase with the cone, (D) resonant vibration of the suspension out-of-phase with the cone of the speaker.

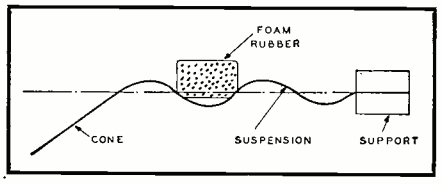


Fig. 6. Suspension with a rubber damper.

diffraction of the sound emitted by the high-frequency cone. The purpose of the two-vane deflector is to increase the radiation angle in the frequency range above 10,000 cycles to conform to the directivity pattern of the remainder of the frequency range. The damping ring in the outer suspension of the low-frequency cone eliminates mid-frequency resonance of the suspension. It also provides a terminating acoustical impedance for the large cone, thereby eliminating standing waves in the cone. The final result is a very smooth response frequency characteristic, a broad directivity pattern, and low nonlinear distortion.

The physical specifications of the Type LC-1A are as follows: over-all diameter, 17 inches; depth, 7 7/16 inches; magnet weight, 2½ pounds; and impedance, 16 ohms.

Performance Characteristics


Response Frequency Characteristics: The response frequency characteristic depicts the sound pressure output of the loudspeaker at some specified observation point, usually on the axis, as a function of the frequency. Of all the performance characteristics of a speaker, the response frequency characteristic is the most useful and important because it conveys the most information. The response frequency characteristic of the *RCA* Type SL-8 is shown in Fig. 4. It will be seen that response covers a very wide frequency range for a loudspeaker of this size.

This uniform characteristic was obtained by employing a particular shape of the curvilinear cone, a special pulp for the material of the cone, and a damping ring in the outside suspension of the cone. The material and shape of the cone were determined from tests made to obtain a smooth response frequency characteristic and a broad directivity pattern. The internal damping in the pulp of the cone plays an important role in the shape of the response frequency characteristic. The shape of the cone influences the high-frequency response and the directivity of the cone. After the shape and material of the cone had been determined it was found that additional damping was required in the suspension system to smooth out the response.

The outside suspension of the cone consists of a corrugated disc which provides a flexible connecting means between the cone and the fixed support, as shown in Fig. 5A. The normal mode of vibration of the cone and suspension is shown in Fig. 5B. The maximum excursions of each part of the suspension and cone are shown by the dotted lines. It will be seen that the amplitude falls off gradually in the suspension from the edge of the cone to the fixed outside edge. Unfortunately, a suspension does not behave in this manner throughout the frequency range, but breaks into resonance in the mid-frequency range. The amplitude of the suspension is thus greater than that of the cone, as shown in Figs. 5C and 5D. The vibration of the suspension is in phase with the cone, as shown in Fig. 5C, and out-of-phase, as shown in Fig. 5D.

In the past, the procedure has been to coat the suspension with some highly viscous material, such as viscoloid, thereby providing damping which reduces the amplitude at resonance. In this way, the response is smooth and free from the peak and the dip. The objection to the use of viscous materials is that these materials tend to dry out, with the result that the damping efficiency is lost. The vibration can be controlled and the effects of any resonance reduced to a negligible amount by means of a special rubber damping ring, as shown in Fig. 6. The curve of Fig. 7, taken without the damping ring, can be compared with that of Fig. 4 taken with the damping ring. It will be seen that the response frequency characteristic without the damping ring exhibits a peak and a dip at 850 and 1050 cycles respectively. Furthermore, the high-frequency response is not as smooth as that with the damping ring. This shows that the damping ring provides a better acoustical impedance termination for the cone. High-frequency vibrations started at the voice coil flow out in the cone, then from the cone into the suspension and damping ring, and are absorbed in this system. As a consequence, standing waves in the cone, which would lead to a ragged response frequency characteristic, are reduced to a negligible quantity.

Fig. 7. Response frequency characteristic of a Type SL-8 without suspension damper.

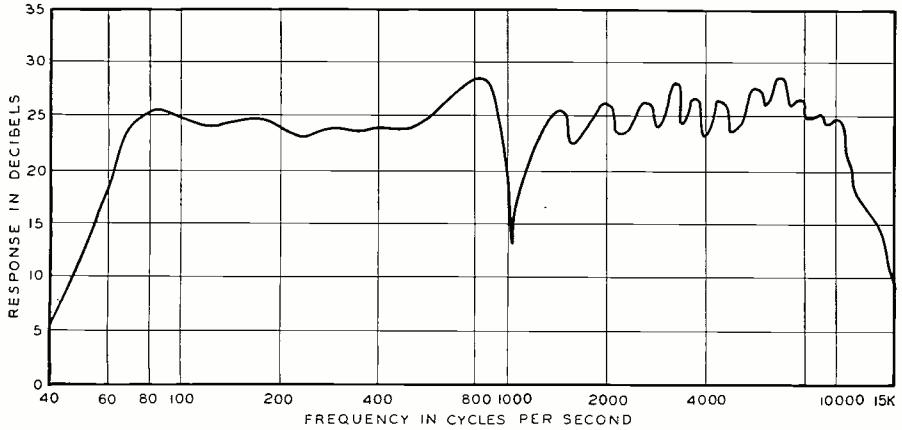

www.americanradiohistory.com

Fig. 8. Response frequency characteristic of the Type SL-12 speaker.

The response frequency characteristic of the Type SL-12, taken in the *RCA* Type SC-8 cabinet, is shown in Fig. 8. This loudspeaker covers the frequency range from 50 to 15,000 cycles with very uniform output. The same features were used in the Type SL-12 as in Type SL-8 to obtain uniform response.

The response frequency characteristic of the Type LC-1A is shown in Fig. 9. The new features which have resulted in the improved performance are as follows: a series of conical domes or cones placed on the surface of the large cone, a damping ring in the outer suspension of the large cone which provides a matched terminating acoustical impedance for the large cone, and a multiple vane deflector in front of the high-frequency cone.

The action of the damping ring in the outer suspension of the cone is the same as that of the Type SL-8 and need not be discussed further.

It was considered desirable to increase the response of the LC-1A loudspeaker in the frequency range from 2500 to 8000 cycles. The output in this range is supplied by the high-frequency unit. The output of any direct radiator loudspeaker can be increased by reducing the solid angle into which the loudspeaker radiates. In this case, it would necessitate a reduction of the angle of the low-frequency cone. By cementing small cones to the large cone, as shown in Fig. 3, the radiation angle into which the high-frequency cone operates is reduced without affecting the effective angle of the large cone. As a matter of fact, the radiation angle of the large cone is increased as will be shown in a later section.

The two-vane deflector operates in the region above 10,000 cps to smooth the response and broaden the directivity. Since the purpose of the deflector is related to the directivity, the action will be explained in the next section.

Directional Characteristics[3]: The directional characteristic depicts the sound pressure output of the loudspeaker as a function of the angle with respect to some reference axis of the system. In general, the reference axis is the symmetrical axis of the loudspeaker.

The directivity pattern of a direct radiator loudspeaker is a function of the ratio of the effective radiation dimensions of the cone to the wavelength, the velocity of sound in the material of the cone, and the geometrical configuration of the cone. Thus there are three ways to establish the directional characteristic of a direct radiator loudspeaker. This will now be illustrated.

Fig. 10 illustrates the role of the shape[4] and material of the cone in determining the directivity pattern. The cone angle in Fig. 10A is 90 degrees. The velocity of wave propagation, V_C, in the cone is 1.4 times the velocity of wave propagation, V_A, in air. Under these conditions, the cone emits practically a plane wavefront in the high-frequency region, which is manifested as a very narrow directivity pattern. The directivity pattern can

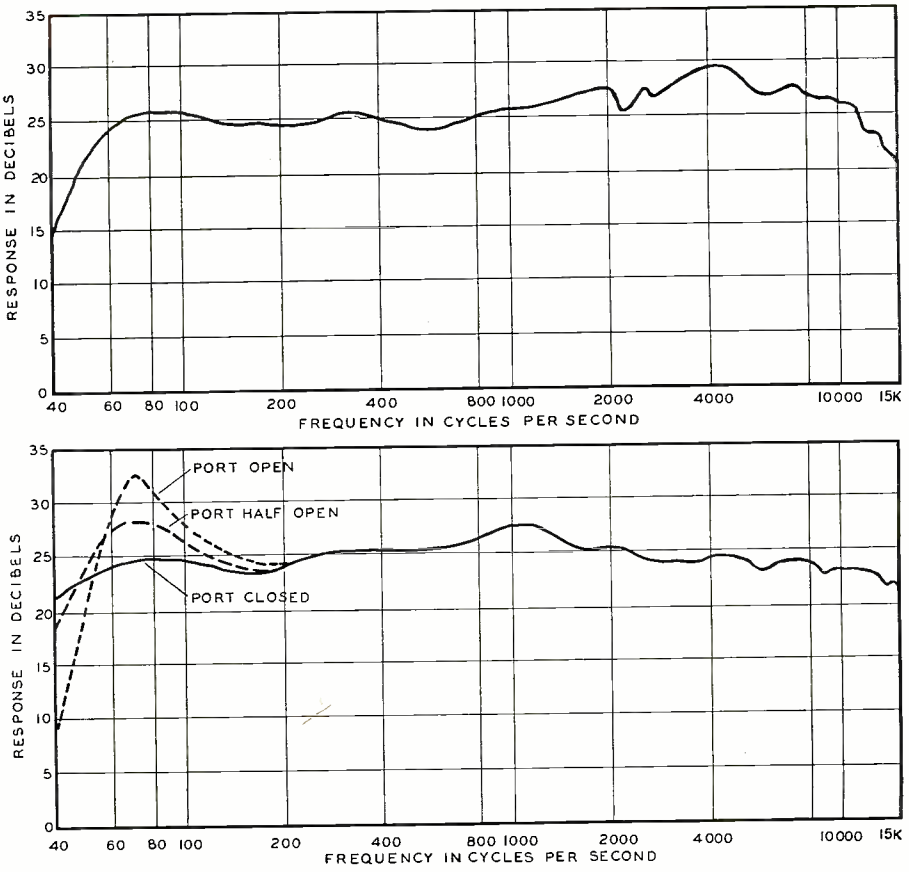


Fig. 9. Response frequency characteristic of the Type LC-1A loudspeaker.

Fig. 10. Wavefronts emitted by various cones. (A) cone with an angle of 90 degrees, (B) cone with angle of 135 degrees, (C) cone with angle of 135 degrees and a very slow propagation velocity of the speaker cone.


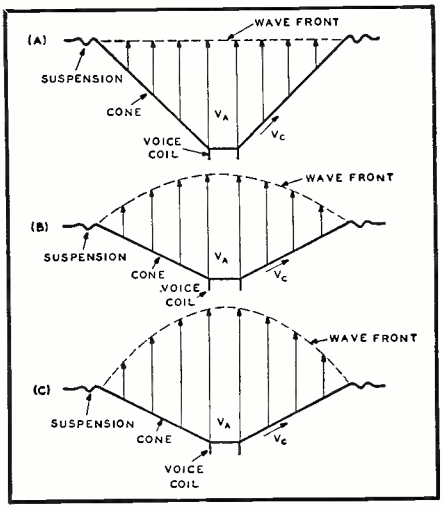


Fig. 11. Directional characteristics of the RCA Type SL-8 speaker.

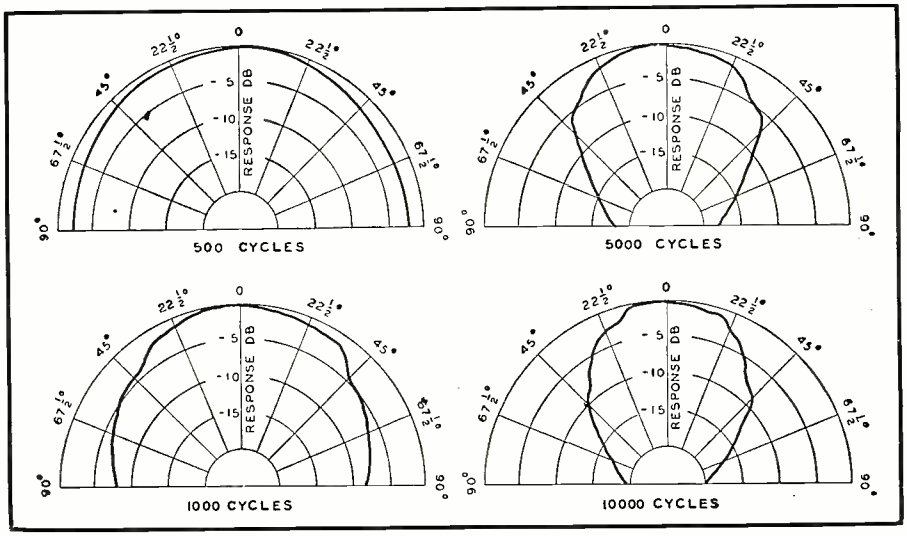

www.americanradiohistory.com

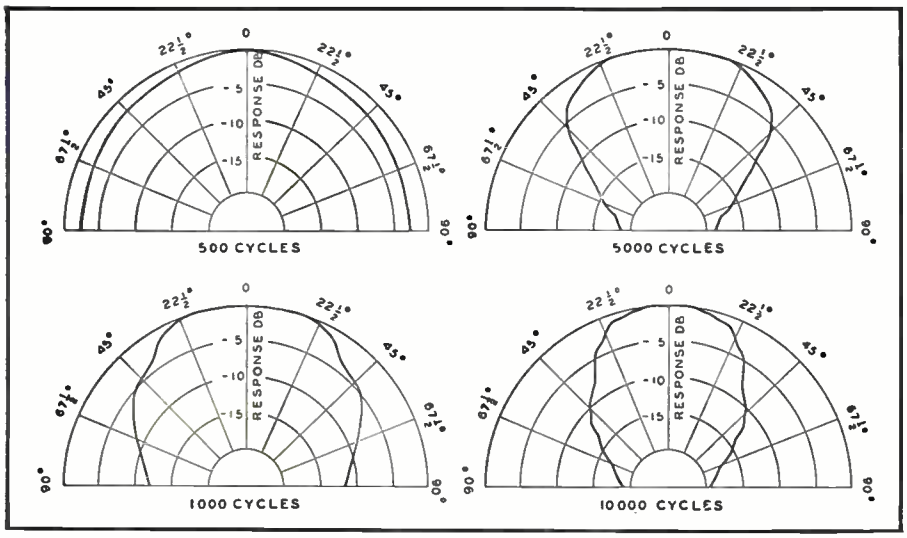


Fig. 12. Directional characteristics of the RCA Type SL-12 loudspeaker.

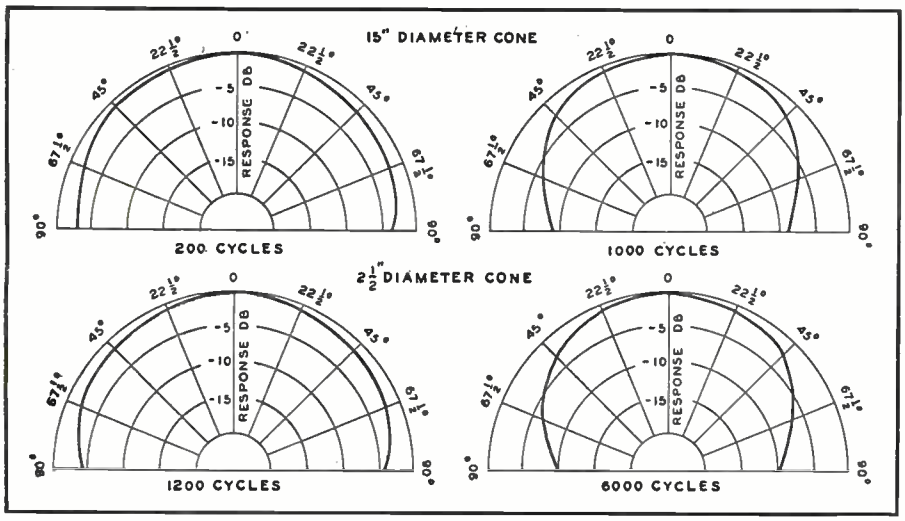


Fig. 13. Directional characteristics of a 15" and 2½" speaker. See text.


be broadened by using a cone with a wider angle. The cone angle in Fig. 10B is 135 degrees. The velocity of wave propagation in the cone is the same as in Fig. 10A. The emitted wavefront is convex, and as the radius of curvature of the wavefront decreases, the directivity pattern becomes broader. Therefore, the directivity pattern of the cone of Fig. 10B will be broader than that of the cone of Fig. 10A. The radius of curvature of the wavefront can be decreased further by reducing the velocity of wave propagation in the cone. In Fig. 10C, the velocity wave propagation, V_C, in the cone is equal to the velocity of sound propagation, V_A, in air. The radius of curvature is reduced and, as a result, the directivity pattern is broadened.

The shape and material of the cone in the Types SL-8 and SL-12 loudspeakers, have been determined from these principles. They give as broad and uniform directivity patterns as possible and still retain uniform response, low distortion, and adequate power handling capacity. The directional characteristics of the Types SL-8 and SL-12 are shown in Figs. 11 and 12. The directivity patterns are exceptionally broad and uniform, with respect to frequency, for single cone loudspeakers.

In a two-unit loudspeaker employing a large cone for the reproduction of the low-frequency range and a small cone for the reproduction of the high-frequency range, a uniform directivity pattern can be obtained over the entire audio frequency range. This is because the ratio of wavelength to linear dimensions can be employed in addition to the expedients used in the cone of the loudspeakers, Types SL-8 and SL-12. This is illustrated in Fig. 13 in which the directivity patterns of 15-inch and 2½-inch loudspeakers are compared for a six to one ratio of frequency, that is, for a constant ratio of diameter to wavelength. Fig. 13 shows that the directivity pattern of a 15-inch loudspeaker at 200 and 1000 cycles corresponds to that of a 2½ inch loudspeaker at 1200 and 6000 cycles. These relationships were used in designing the two units of the LC-1A.

In addition, in the Type LC-1A loudspeaker, the small cones which are attached to the wide-angle cone reduce the velocity of wave propagation in the large cone. This broadens the directivity pattern of the low-frequency cone. In the high-frequency range, the sound emitted by the high-frequency cone is diffracted by the cones attached to the large cone which broadens the directivity pattern of the

Fig. 14. Directional characteristics of the RCA Type LC-1A loudspeaker. See text for a full discussion of these characteristics.

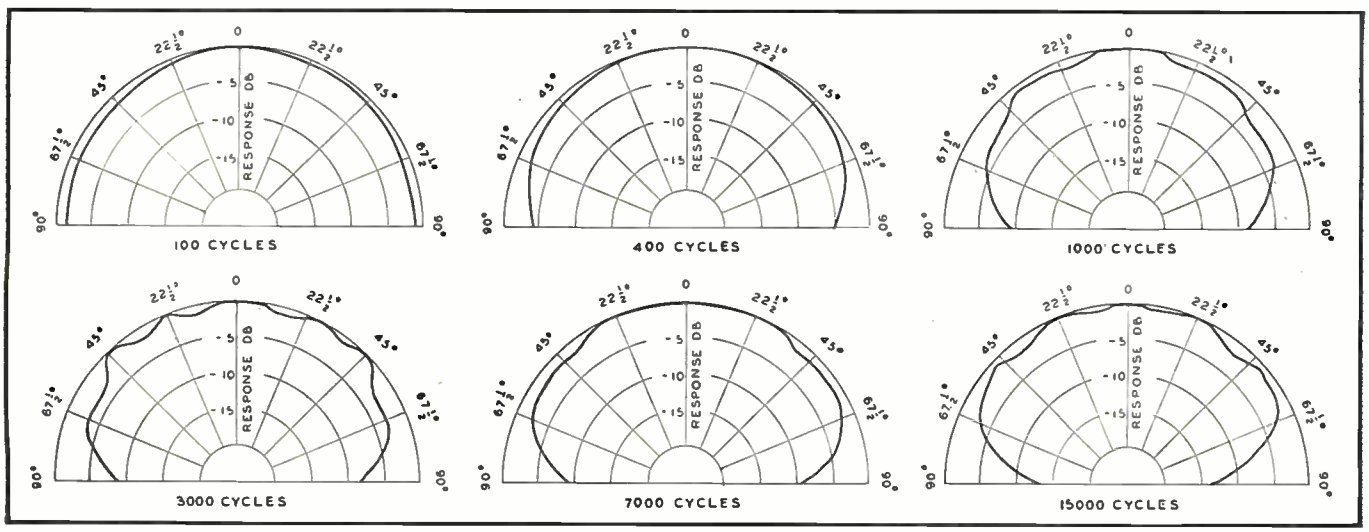

www.americanradiohistory.com

high-frequency cone. Then, in the region around 10,000 cycles, small deflectors are used to broaden the directivity pattern of the small cone to conform with the directivity pattern of the remainder of the frequency range.

The directional characteristics of the Type LC-1A are shown in Fig. 14. It will be seen that uniform directivity is obtained over a total angle of 140 degrees for the entire audio frequency range. These patterns are obtained by the use of the principles relating to directivity outlined in this section.

Nonlinear Distortion Characteristics: This characteristic depicts the total r.m.s. nonlinear distortion in per-cent of the fundamental as a function of the frequency for a specified input. The ones shown were obtained by means of an automatic nonlinear distortion analyzer[5].

The nonlinear distortion frequency characteristics of the Type SL-8 for inputs of one-half and one watt are shown in Fig. 15. This speaker will deliver a sound level of 93 decibels in the average living room for an input of one watt. Fig. 15 shows that the distortion is exceedingly low except for the low-frequency range. However, if a correction is made for the power distribution with respect to frequency for the average orchestra, the distortion for one watt input will be as shown in Fig. 16. Now the distortion is under one-third per-cent over the entire audio frequency range.

These same characteristics for the Type SL-12, for inputs of one-half and one watt, are shown in Fig. 17. The essential difference between the distortion characteristics of the Types SL-8 and and SL-12, is that the distortion in the 12-inch loudspeaker is less than that of the 8-inch loudspeaker in the low-frequency range.

The nonlinear distortion frequency characteristics of the Type LC-1A, for inputs of 1, 2, and 5 watts, are shown in Fig. 18. The nonlinear distortion due to the suspension can be reduced to a negligible quantity by placing the fundamental resonant frequency of the loudspeaker at the lower limit of reproduction. Above the fundamental resonant frequency, the velocity of the cone is not appreciably affected by the suspension. This is because the mechanical reactance due to the compliance of the suspension is small compared to the mechanical impedance of the remainder of the system. In this speaker, the fundamental resonant frequency of the low-frequency unit was placed at 30 cycles.

Another source of nonlinear distortion is the cone. Since the frequency range from 100 to 800 cycles contains the maximum power in both speech and music, it is important that the distortion be reduced to a minimum in this range. This was done by employing a very rigid cone of high strength. In order to obtain sufficient rigidity and strength to insure low distortion, the thickness of the cone was made two and one-half times that of a conventional cone. This increased the rigidity by a factor of 15 times and the strength by more than two and one-half times.

Inhomogeneity of the flux density through which the voice coil moves is another source of distortion. This can be eliminated by making the summation of the product of each turn, and the flux density associated with that turn, independent of the amplitude. This requirement was satisfied by making the voice coil large and slightly longer than the air gap. A heavy voice coil must be used to obtain reasonable efficiency with the heavy cone. A voice coil of 25 grams was used in this loudspeaker. This is about 25 times the mass of tne voice coil used in conventional console type radio loudspeakers. (*Continued on page* 173)

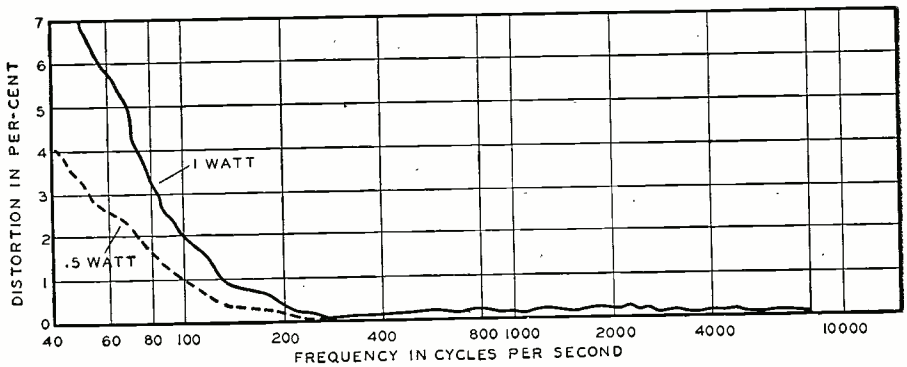


Fig. 15. Distortion frequency curve of the Type SL-8 for ½ and 1 watt inputs.

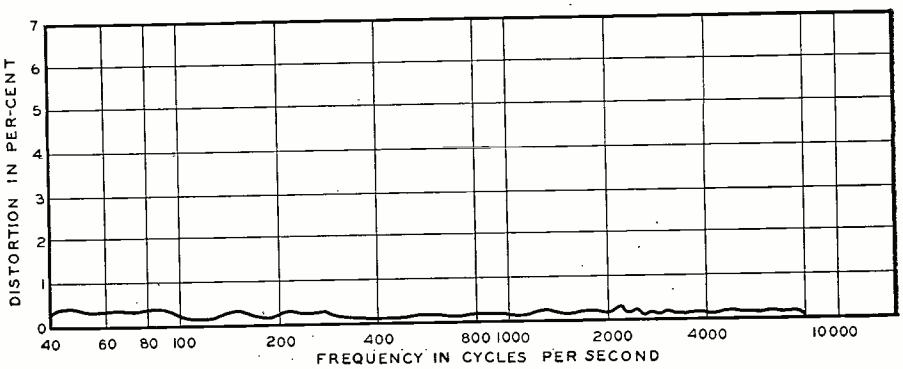


Fig. 16. Distortion frequency characteristic of the RCA Type SL-8 for an input of one watt having the frequency distribution of orchestral music.

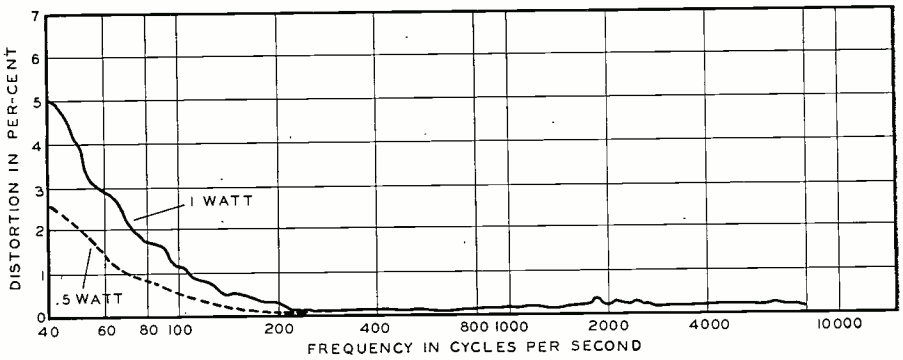


Fig. 17. Distortion frequency curve of the Type SL-12 for ½ and 1 watt inputs.

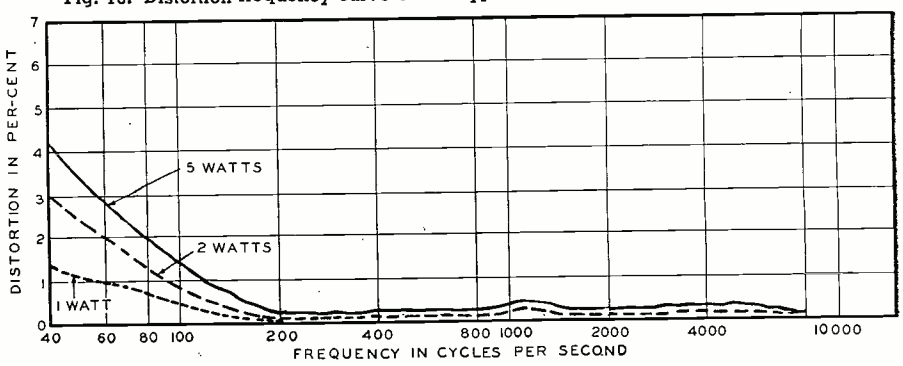


Fig. 18. Distortion frequency curve of the Type LC-1A for 1, 2, and 5 watt inputs.

www.americanradiohistory.com

MAC'S RADIO SERVICE SHOP

By JOHN T. FRYE



REMOTE CONTROL AND COLORED SNOW

A SUDDEN warm-up during the night had left the entire city wrapped in a thick blanket of fog. As Barney entered the service shop that February morning, he thought to himself that this would probably be a "hot" television reception day in the ultra-fringe area. The moisture-saturated air on the ground with drier air above it usually produced a condition in the troposphere favorable for bending TV signals back to earth.

When he opened the door of the service department, he saw his hunch had been right. A chassis on the trial-run bench was displaying a steady, crystal-clear picture. As Barney watched, another channel was switched on and then another and another until five different pictures were revealed. When the program carried by each channel came into view, the fine tuning was adjusted and the volume was cut down to zero and then brought back up. Yet the only other person in the room was Mac, and he was sitting on a stool clear across the room from the set.

"Hey!" Barney exclaimed, "what's going on here? How are you doing that?"

"Now calm down, Buster, or you'll flip your lid," Mac admonished. "It's being done with this new *Regency* remote TV tuner," he explained as he tapped a small mahogany cabinet resting in his lap. Watching closely, Barney saw the picture and sound were being manipulated by two large dual-dials on the face of this cabinet; and he also noticed the unit was connected to the set by a cable about the size of a pencil.

"How does it work?" Barney asked.

"Inside the cabinet is a complete cascode tuner with its own power supply. These concentric dials on the right select the channel and adjust the fine tuning in the usual manner. The output of the tuner feeds through that small coaxial line to the input of the set's i.f. system. Another connection is made to the receiver's audio system so that this outside dial on the left can adjust the volume. Finally, the remote control unit generates a d.c. voltage, either positive- or negative-going, the amplitude of which is controlled by the inside dial on the left; and this voltage is fed to the set for varying the contrast of the picture. A 'local-distance' switch on the back of the unit permits placing proper bias on the tuner for extremes of signal strength."

"Now let me get this straight," Barney interrupted. "If I understand you correctly, that same little concentric cable is carrying an i.f. signal from the remote control unit to the set, an audio signal from the set to the unit, and a d.c. voltage from the unit back to the set. Why that little old chunk of coax must be busier than a party line the night the banker's wife left town with the traveling salesman! How do all those signals keep from getting into each other's hair?"

"A good question," Mac said with a chuckle. "It is all done with an arrangement of chokes, blocking condensers, and filters inside a small potted unit mounted inside the set chassis. The coax line goes to this potted unit, and then leads go from it to the various sections of the receiver controlled. Here," he said as he tossed a yellow-covered instruction book across to the boy. "Take that home with you tonight and see if you can figure how it is done by looking at the diagram."

"Can you hook that outfit on to any receiver?" Barney wanted to know.

"Just about any. It comes in two models: one for sets with an i.f. around 21 megacycles and another for sets with an i.f. near 41 megacycles. A set with an odd i.f. too far removed from these standard frequencies could not use the remote tuner. Neither could the remote control be applied to an old set using manual gain control without a.g.c. But outside of such rare cases, the device will work on any set. It functions equally well with split i.f. and intercarrier systems. When you want to use it for u.h.f. reception, you simply install u.h.f. strips in the remote control tuner. If you want to employ a booster in conjunction with the remote control tuner, there is an a.c. outlet on the rear of the cabinet into which the booster can be plugged."

"How about using the unit in a weak-signal area? Can you get as good reception with the remote unit as you do with the set's own tuner?"

"If you hook it on to a set employing a less-efficient type of tuner, you will actually get better reception when the modern cascode circuit of the remote unit is in use. In general, you should be able to use this remote control unit in any area in which the set alone will receive a watchable picture."

"Whose set is this you are using?"

"The wife and I were visiting friends at Big City over the weekend. They have a little boy with rheumatic fever who must spend the next few months in bed. Television is the best thing they have found to keep him entertained; but, like most kids, he likes to do a lot of channel hopping. That means his mother has to dash in from the kitchen, laundry, or upstairs dozens of times a day to adjust the set. I was telling them about this remote control gadget, and they insisted I bring their set home and install the unit. We are going to take it back to them tonight."

"That will certainly be a fine thing for him and his mother, and I can see where it could be used to great advantage in a public place where the set must be up high so everyone can see it but yet you want to control it from a convenient location. Also, I can understand how elderly people will like not having to jump up and down every time they want to change programs, touch up the tuning, or adjust the volume; but I wonder if many other people—young and able-bodied people, I mean—will buy them."

"I am sure they will," Mac said emphatically. "I remember that when automatic gear shifts were first introduced a lot of people thought that they would only be used by women and 'other' inept drivers. As soon as drivers in general found out how convenient they were, though, everybody wanted them.

"Remote control of TV sets is not a brand-new idea, for we have had some novel electrical-mechanical systems

(*Continued on page* 148)


www.americanradiohistory.com

FINEST **PERFORMANCE**


GREATEST **PROFIT**

BIGGEST **PROMOTION**

To Capture the Hi-Fi Market!

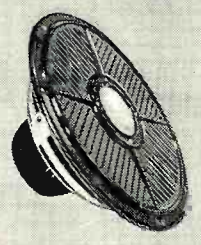


Dual Coaxial Speaker A1-400

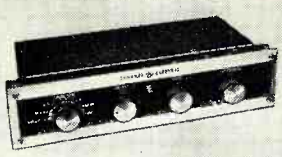

Preamplifier Control Unit A1-200



Power Amplifier A1-300

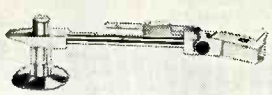

Deluxe Tone Arms:
A1-500 (12") A1-501 (16")



Speaker Enclosure (Blond, Mahogany, or Unfinished Veneers) A1-406

MAIL THIS COUPON TODAY!

MATCHED COMPONENTS

GE Custom Music Ensemble

A FEW MINUTES of your time now paves the way for the most successful *hi-fi* selling year you've ever experienced. Listen to this equipment today... examine its amazing potential... climb on the bandwagon of enthusiasm it has created at every audio show from coast to coast.

General Electric Custom Music Ensemble installations offer you these bonus features: *Low cost... multiple sales... service-free customers... and the most widely advertised and promoted line of matched components in the industry!*

Build your high-fidelity business in 1954 with G.E. Do it by calling your local General Electric headquarters today or writing us for complete information.



NATIONAL MAGAZINE ADVERTISING
in: Atlantic... Harper's... Saturday Review of Literature... New Yorker... House Beautiful ...Esquire... High Fidelity... Audio Engineering... Record Retailing.

TOP-NOTCH SALES TOOLS:
Posters... Streamers... Demonstration Records... Counter Cards... Folders ...Booklets.



General Electric Company, Section R924
Electronics Park, Syracuse, New York

Please send me literature and complete information on the G-E Custom Music Ensemble.

NAME.....


ADDRESS.....

CITY.....STATE.....

GENERAL ELECTRIC

www.americanradiohistory.com

International SHORT-WAVE

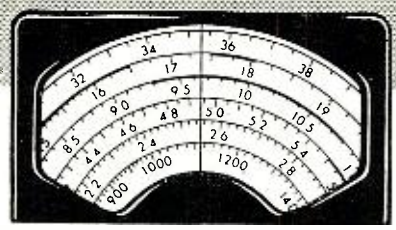

Compiled by KENNETH R. BOORD

AFGHANISTAN—*Kabul Radio,* 9.972A, noted with *English* 1050-1100, fair level in England. (Catch)

Albania—Radio Tirana, 6.570, 7.850A, has *English* 1340-1400, 1600-1630; French 1230-1300, 1630-1700. *(WHR)*

Alaska — Alaska Communications System, 5.980, Juneau, noted *testing* 0055-0110. (Kary, Va.)

Algeria—Radio Algerie, 6.160, heard closing 1658 with "La Marseillaise."

Anglo-Egyptian Sudan—Radio Omdurman, 7.085A, noted at good level ending Arabic session 2345. (Kary, Va.; Cox, Dela.) With news in *English* 1115 on *Sun.* (Pearce, England)

Angola — CR6RA, 11.862, now announces simply as *"Radio Angola;"* is heard 1330-1730. (ISWC, London) Luanda is using a *new* channel of 6.355; *Radio Clube de Benguela* signs on 1200 on 9.502. (Radio Sweden) Luanda's 11.862 channel is audible most days 1322A-1330 with interval signal of steady native drum beats preceding 1330 sign-on. (Niblack, Ind.) And closing 1730 with "A Portuguesa." (Christie, Calif.) CR6AA, Lobito, is heard in Sweden on 5.033 at 0530-0600. *(Nattuggian,* Sweden) *Etervsep,* Sweden, lists CR6RD, *Radio Clube do Huambo,* Nova Lisboa, on 11.928, heard 1120-1140.

Argentina — SIRA is using LRA, 15.345, for Latin American session 2030 - 0100. (Morgan, Balbi, Calif.) Heard occasionally in Tokyo near 0100 closedown. (Takemi) Still uses LRU, 15.29, for *English* to Western North America from 2300. (Ferguson, N. C.) Announces *English* for 1500-1600 on LRS, 11.880. (Kahan, Calif.) *Radio Splendid,* 9.310A, is good from 0145.

Azores — CSA93, 4.865, Ponta Delgada, heard 1615 in Spanish. (Dahlgren, Sweden)

Bechuanaland—Shapiro, Ireland, has heard ZNB, 8.240, Mafeking, *after* 1330 with music, in heavy CWQRM. (ISWL, England)

Belgian Congo—OTM4, *Radio Congo Belge,* Leopoldville, has *moved* from 6.295 to 6.290, closes 1600. (ISWC, London) OTM, 9.380A, noted 1515 at good level, closed 1557 with National Anthem. (Ferguson, N. C.) Heard opening 0000 in French, Flemish. (Morris, Pa.)

Bolivia — CP38, 9.444A, La Paz, is heard in Chile at very weak level, bad QRM. (Bush)

Brazil—PRL7, 9.270, Rio de Janeiro, has *English* announcements in musical session 2200 *Sat.* (Zerosh, Pa.) Has varied announcement in this session to "Radio Nacional, the Voice of Brazil." (Niblack, Ind.) ZYS8, 4.805, Manaus, noted 2036 in Portuguese; Recife, 6.085, is heard in Sweden around 1835; ZYB8, 11.765, relaying *Radio Tupi,* noted 1630. (Dahlgren) *Radio Relogio,* 4.905, noted 1900-2300, good level. (Bush, Chile)

British Guiana—ZFY, Georgetown, is currently being heard on *new* 3.255A signing off 2115. (West, Va.; URDXC)

Bulgaria—The European Service of *Radio Sofia* is now 1045-1445, 6.070, 7.670; 1500-1730, *new* 7.256, 7.670; *English* 1500-1515, 1615-1645, 1715-1730. *(WRH)*

Burma—Radio Rangoon is scheduled 2000-2130, 9.542, 955 kc.; 0030-0230, 9.542, 6.035, 955 kc.; 0700-1015, 9.542, 4.774, 955 kc.; news 2020, 0130, 1000. *(Radio Times of India)*

Canada — CFRX, 6.070, Toronto, Ont., noted 1830-1900 with news, sports. (Karrer, Pa.) CJCX, 6.010, Sydney, N. S., heard 2225-2235 with news; CBNX, 5.970, St. John's, Newfoundland, heard 0605-0615 with music, time checks. (Morris, Pa.) CHNX, 6.130, Halifax, N. S., is good level around 0740. (Hall, Que.)

Cape Verde Islands — Praia noted near 7.398 with news in Portuguese 1942, closing 1700A. (Pearce, England) Recently *listed* channels of 3.950, 400 watts, 6.350, 3 kw., scheduled 1530-1700. (Radio Sweden)

Ceylon — Radio Ceylon, 9.520, noted 1730 with music; 15.120 at 2100 with news. (Sanderson, Australia) On 11.975 at 1015-1115 or later, good level. (Kroll, N. Y., others)

Chile — Radio Yungay, 7.60086 *(measured),* noted 2013 tune-in to 2326 tune-out, fair level but with severe QRM. (Rastorfer, N. Y.)

China—Radio Peking usually comes in with news 0400 on 6.105, 6.200AV, and less often on 7.500; noted with *English* 2200 on *new* 11.96 parallel 15.06. (Morgan, Balbi, Calif.) Fair level on occasion on 9.040A at 0810. (Kary, Va.) Heard on *measured* 15.084 at 1827; on *measured* 15.060 at 1900, still on at 2316. (Ferguson, N. C.)

Colombia—HJKH, 5.070, noted signing on weekdays 1830 with soft organ music and chimes; HJDE, 6.145, Medellin, is good quality lately; HJKD, 6.000, Bogota, noted 2030-2100 with *English* feature "American Melodies," evidently by tape recording. (Niblack, Ind.) *Radio Maria,* located in what seems to be Pasto (in southwestern part of country) is noted with call of HJHO


(Note: Unless otherwise indicated, all time is expressed in American EST; add 5 hours for GCT. "News" refers to newscasts in the English language. In order to avoid confusion, the 24 hour clock has been used in designating the times of broadcasts. The hours from midnight until noon are shown as 0000 to 1200 while from 1 p.m. to midnight are shown as 1300 to 2400.) The symbol "V" following a listed frequency indicates "varying." The station may operate either above or below the frequency given. "A" means frequency is approximate.

The cheery voice of Marianna Linard, English announcer for "The Voice of Denmark," Copenhagen, is well-known to SWL's around the world. This picture of Marianna was made during a visit to the United States. Shown with Marianna is Albert K. Saylor, Quantico, Va., ISW Department monitor, whom she visited en route to California for a stay with relatives. Her English broadcasts are heard to North America over 9.52 between the hours of 2100 and 2230 Eastern Standard Time.



www.americanradiohistory.com

NEW

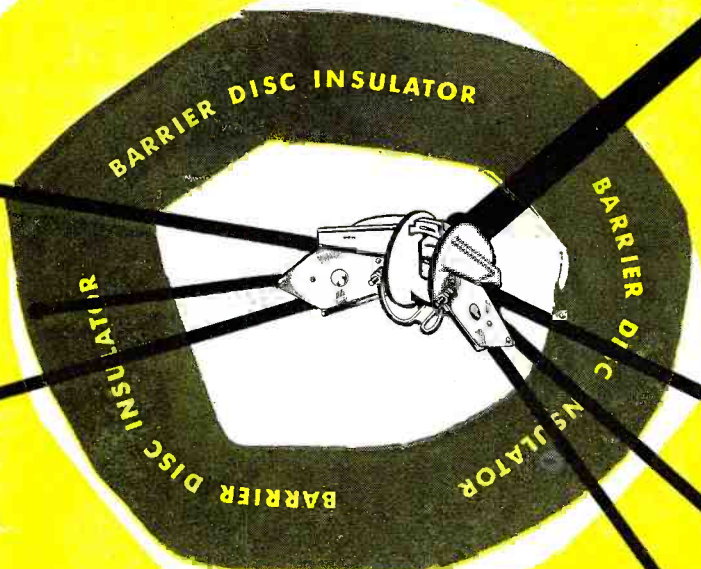

WALSCO *Imperial*

INTRODUCING the greatest advance in Conical antennas ...it's the *all-new* WALSCO *Imperial*. Featuring a new "barrier disc" insulator with 2 inches of air space between the terminals to prevent *shorts*. Soot deposits, dirt, moisture, salt, etc., *cannot* affect this insulator. The WALSCO *Imperial* will therefore maintain *lasting* high gain performance *anywhere*, regardless of weather conditions. Contact surfaces and terminals will *never* rust or oxidize. Front end hardware is *stainless steel* to prevent corrosion losses *permanently*. Front end elements are pre-assembled to holding plates which are fastened to the insulator with one wing nut. Less than 2 minutes to assemble.

MOST REVOLUTIONARY CONICAL ANTENNA IN 4 YEARS

3 year unconditional guarantee!



WALSCO

Guaranteed lasting high gain on all VHF channels

ELECTRONICS CORPORATION

3602 Crenshaw Blvd., Los Angeles 16, Calif.

www.americanradiohistory.com

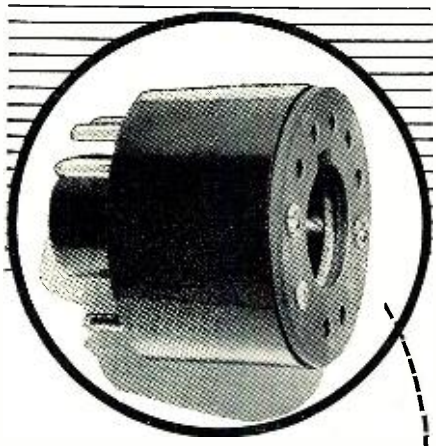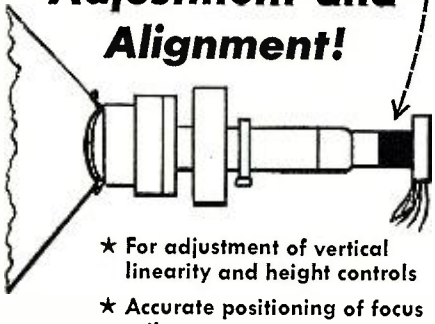HBG*
is here!

for Quick TV Set Adjustment and Alignment!

★ For adjustment of vertical linearity and height controls
★ Accurate positioning of focus coil or magnet
★ Precise setting of yoke
★ Complete with instructions
Perma-Power
HBG
*HORIZONTAL BAR GENERATOR
Dealer Net $19.95
See Your Jobber Today!
manufactured by
Perma-Power COMPANY
Chicago 25, Ill.
Manufacturers of Electronic Equipment Since 1928

on 4.825 to *past* 2230. The one on 4.747 to 2100A sign-off is probably *Radiodifusora Militar de Colombia.* (Stark, Texas) HJCH, 4.895, Bogota, noted 1700 in Spanish. (Dahlgren, Sweden) HJBE, *Radio Libertad,* 5.979A, noted with music 1800-1900. (Sutton, Ohio)

Cuba — Radio Reporta del Hora, 6.314A, noted 2335-0015, frequent time checks. (Roberts, Conn.)

Czechoslovakia — Prague, 9.504, noted with *English* 0715-0740; announced further *English* for 1400 on this channel and 1700 on *only* 233 meters, medium-wave. (Pearce, England) Heard on 9.550 at 2300 with *English* to North America. (Barnard, Calif.) And 1930-2000 on 7.255. (Morris, Pa., others)

Denmark—Copenhagen, 9.520, noted at good level opening to North America 2030. (Barnard, Calif.) And again 2200.

Dominican Republic—*"La Voz Dominicana,"* lists HI2T, 9.735, 7.5 kw.; HI4T, 5.970, 7.5 kw. Latter noted 2315-2330 with music, good level in Iowa. (Shear) *Radio Caribe,* 4.996, Santiago de Los Caballeros, is noted to 2100. (Stark, Texas)

Ecuador — Radio Mundo, Guayaquil, is noted on 4.743, up from 4.675A, goes *past* 2030. (Stark, Texas) *"La Voz de Democracia,"* 6.060A, is good level around 1000-2200. (Sawyer, Ont.)

Egypt—Cairo uses 17.725 to Indonesia, India, Pakistan 0700-1000; news 0830. (ISWC, London; *WRH;* Ferguson, N. C.) Is strong daily on 11.965 with Arabic 1000-1100. (Morgan, Balbi, Calif.) Still noted on 9.475, 11.815 to 1700 closedown. (Rastorfer, N. Y., others) The Home Service in Arabic is radiated on 6.085, 11.965, 2345-0205,

(*Continued on page* 101)

PHILCO'S "SURFACE-BARRIER" TRANSISTOR

RADICALLY new production techniques have been employed by the Philco Corporation in the development of a new type of transistor which is said to outperform all transistors currently in use. The new unit is called a "surface-barrier" transistor because advantage is taken of a "surface-barrier" effect discovered by Philco engineers. It is basically a "p-n-p" junction type.

Major operating characteristics include a gain-bandwidth product of over 50 mc., reliable operation at 70 mc. and above, and a noise figure of 4 to 8 db at 10 mc. Power gain is on the order of 1000. These characteristics are achieved by depositing a suitable material, such as indium, on each side of a very thin section of germanium. The thickness of the germanium can be accurately controlled to within 10 millionths of an inch, and actual thickness is about 2 ten-thousandths of an inch.

In manufacturing this device, the germanium is first purified to 1 part in 10 billion. A suitable impurity is then introduced in the proportion of 1 part in 10 million, forming "n" type germanium. Small wafers are cut for additional processing. These wafers are about .050 x .100 inch and are lapped to a thickness of .006 inch. Chemical etching further reduces the thickness to .003 inch.

A process called "jet electrolytic etching" was developed to produce the desired final thickness. Two small jets of a salt solution are directed against the sides of the germanium wafer and current is passed through the solution, resulting in the etching of the germanium. When the desired thickness (thinness!) is reached, the current is reversed and the process becomes one of electroplating rather than etching. The electroplating is continued until electrodes of suitable thickness are plated on the germanium. Leads are then soldered to these electrodes and the complete unit is hermetically sealed.

Fig. 1 is a cross-sectional view of the transistor. The collector electrode is made slightly larger than the emitter by using a slightly larger jet during the etching process. Although indium was used as the electrode material in experimental units, many other materials are satisfactory.

A major advantage of this manufacturing process is the uniformity that can be obtained. When mass production equipment is in use, it is expected that the uniformity will be better than that of vacuum tubes.

Pilot plant operation is being set up for the manufacture of this unit but it is expected that the military will absorb all production for some time to come. Because of its high efficiency and the low operating voltage required, the "surface-barrier" transistor is ideally suited for battery-operated or airborne military electronic equipment. An experimental military receiver has been built, using "surface-barrier" transistors, which requires only 5 to 10 milliwatts of battery power. A reduction in power requirements of 1000 to 10,000 times is anticipated in airborne equipment. —30—


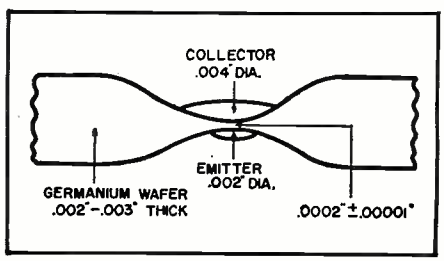



Fig. 1. Cross-sectional view of the new Philco "surface-barrier" transistor.

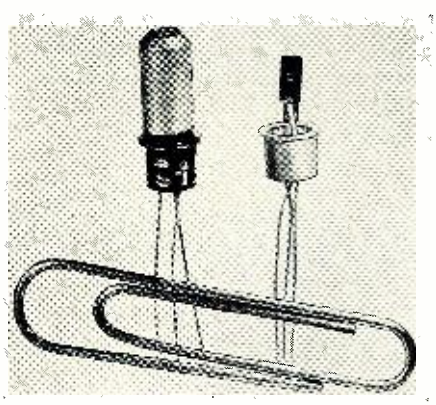Philco's "surface-barrier" transistor compared with a standard paper clip. The new units are capable of operating at higher frequencies and lower power consumption than currently-available transistors. The transistor at left is enclosed in a hermetically-sealed metal case while the one at right is complete except for case.



www.americanradiohistory.com

THE "TELCO TEN"

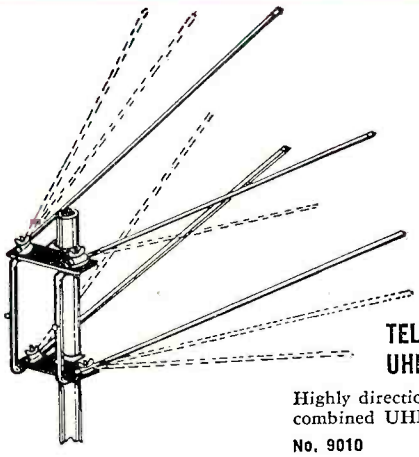

NEW!

TELCO "DOUBLE V" UHF-VHF ANTENNA

Highly directional... adjustable for combined UHF-VHF 50°-70°-90°.

No. 9010 List $6.95

... the "T" formation line—T for Top Quality and T for Ten Antenna Styles. Insist on TELCO ... the best TV antennas for the greatest "show" on earth.

TELCO

G·C




WISHBONE

... exclusive with TELCO, is a free air insulator that prevents shorting out under any condition ... found only on TELCO UHF Antennas.


FREE CATALOG—illustrates all TELCO products. Available at your jobber or write direct today!



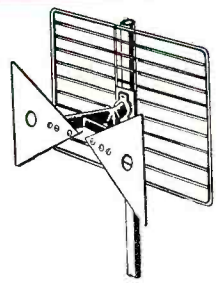
TELEVISION HARDWARE MFG. CO.
DIVISION OF GENERAL CEMENT MFG. CO.
904 Taylor Street Rockford, Illinois



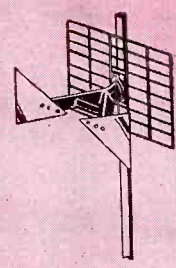
TELCO UHF "GOLDEN GRID" SUPER DELUXE BUTTERFLY ANTENNA
No. 8965 List $5.95



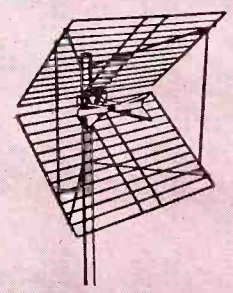
TELCO UHF "GOLDEN GRID" STANDARD BUTTERFLY ANTENNA
No. 9001 List $3.95



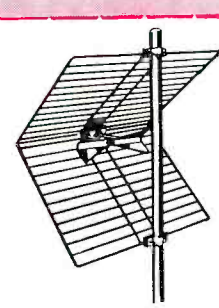
TELCO UHF "GOLDEN GRID" DELUXE CORNER REFLECTOR ANTENNA
No. 8984 List $11.25



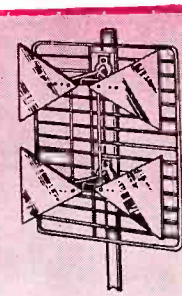
TELCO UHF "GOLDEN GRID" STANDARD CORNER REFLECTOR ANTENNA
No. 9002 List $11.25



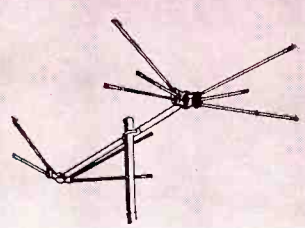
TELCO UHF "GOLDEN GRID" 2-STACK DOUBLE TIE ANTENNA
No. 9004 List $7.50 less mast



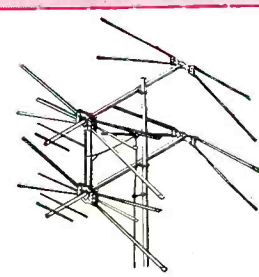
TELCO VHF CONICAL ANTENNA
No. 8700 List $9.25



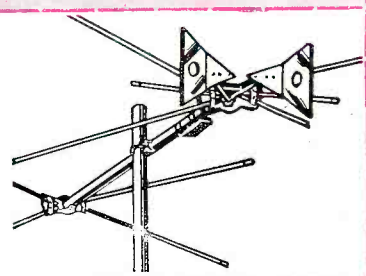TELCO VHF SUPER CONICAL ANTENNA
No. 8902 List $19.85



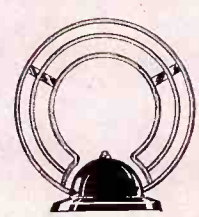TELCO UHF-VHF UNIVERSAL CONICAL ANTENNA
No. 8981 List $16.25



TELCO UHF-VHF "GOLDEN HALO" INDOOR ANTENNA
No. 9000 List $4.95


www.americanradiohistory.com

Heathkit IMPEDANCE BRIDGE KIT

MODEL IB-2

$59.50

SHIPPING WT. 15 LBS.

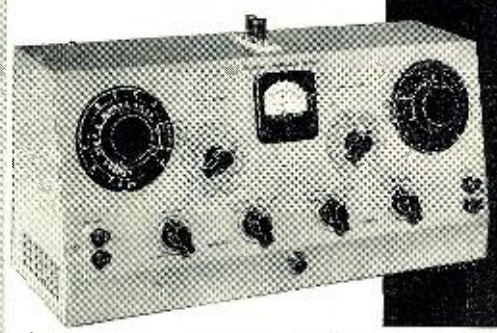

Features

- Simpson 100-0-100 microampere meter.
- Completely AC operated.
- Built-in phase shift generator and amplifier.
- Battery type tubes, no warm-up required.
- Newly designed two section CRL dial.
- Single knob D, Q, and DQ functions.
- Special impedance matching transformer.
- New modern cabinet styling.
- ½% precision resistors and silver mica condensers.

Another new, outstanding instrument design so typically characteristic of Heathkit operation in producing high quality instrument kits at the lowest possible price. A new, improved model Impedance Bridge kit featuring modern cabinet styling, with slanted panel for convenience of operation and interpretation of scales at a $10.00 price reduction over the preceding model. Built-in adjustable phase shift oscillator and amplifier with all tubes of the battery operated type completely eliminates warm-up time. The instrument is entirely AC line operated. No bothersome battery replacements.

The Heathkit IB-2 Impedance Bridge Kit actually represents four instruments in one compact unit. The Wheatstone Bridge for resistance measurements, the Capacity Comparison Bridge for capacity measurements, Maxwell Bridge for low Q, and Hay Bridge for high Q inductance measurements. Read Q, D, DQ all on one dial thereby eliminating possible confusion due to the incorrect dial reference or adjustment. Only one set of instrument terminals necessary for any measurement function. Panel provisions provided for external generator use.

A newly designed two section CRL dial provides ten separate "units" switch settings with an accuracy of .5%. Fractions of units are read on a continuously variable calibrated wire-wound control. A special minimum capacity, shielded, balanced impedance matching transformer between the generator and the bridge. The correct impedance match is automatically switch selected to provide constant load operation of the generator circuit. The instrument uses ½% precision resistors and condensers in all measurement circuits.


The new Heathkit IB-2 provides outstanding design features not found in any other kit instrument. The single low price includes the power supply, generator, and amplifier stages. No need to purchase separate instrument accessories in order to obtain the type of operation desired.

Heathkit AUDIO WATTMETER KIT

MODEL AW-1

$29.50

SHIPPING WT. 6 LBS.

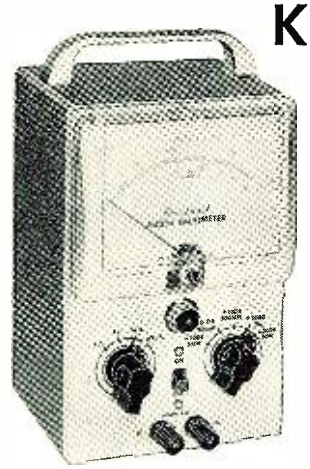

A new Heathkit design for the audio engineer, serious hi fi enthusiast, recording studio, or broadcast station; the Heathkit Audio Wattmeter Kit. This specialized instrument instantly indicates the output level of the equipment under test without requiring the use of external load resistors. All readings are taken directly from the calibrated scales of a 4½" 200 microampere Simpson meter.

The Heathkit Audio Wattmeter features five full scale power measurement ranges from 5 milliwatts up to 50 watts with db ranges of −15 db to +48 db. The instrument has a power measurement rating of 25 watts continuous and 50 watts maximum for intermittent operation. Non-inductive resistance load impedances of 4, 8, 16, and 600 ohms are provided through a panel impedance selector switch. Frequency effect is negligible from 10 cycles to 250 kc. A conventional VTVM circuit utilizes a 12AU7 twin triode tube. The meter bridge circuit uses four germanium diodes for good linearity.

With the Heathkit AW-1 desired information can be obtained instantly and conveniently without bothering with the irksome setups and calculations usually required. Useful for power curve measurements, frequency response checks, monitoring indicator, etc. Convenient calibration directly from 110 volt AC line source. This new instrument will help to supply the answers to your audio operating or power output problems.

Heathkit LABORATORY GENERATOR KIT

MODEL LG-1

$39.50

SHIP. WT. 16 LBS.



Another welcome new addition to the popular line of Heathkit instruments, the Heathkit Laboratory Generator. Specifically designed for flexibility of operation, accuracy and versatility beyond the performance level provided by the conventional service type generator. Frequency coverage of the Colpitts oscillator is 150kc to 30mc in five convenient ranges with provisions for internal or external modulation up to 50%, and .1 volt RF output throughout the frequency range. Panel mounted 200 microampere Simpson meter for RF "set reference level" to provide relative indication of RF output. Individually shielded oscillator and shielded variable and step attenuator provide flexible control of RF output.

The circuit features a 6AF4 high frequency oscillator, a 6AV5 amplifier with grid modulation, 12AU7 400 cycle oscillator and modulator, OB2 voltage regulator tube, and a selenium rectifier for the transformer operated power supply. The smart professional instrument appearance and over-all flexibility of operation will prove a decided asset to any industrial or educational laboratory. The Heathkit Laboratory Generator sets a new level of operation, far superior to any instrument in this price classification.

HEATH COMPANY · Benton Harbor 15, Mich.

www.americanradiohistory.com


THE MOST *Outstanding* OSCILLOSCOPE IN HEATHKIT HISTORY

NEW MODEL O-9


OSCILLOSCOPE KIT




Check THESE FEATURES

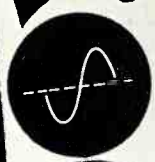

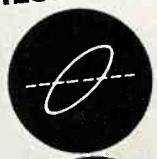
Voltage regulated for rock steady traces—complete freedom from bounce and jitter.



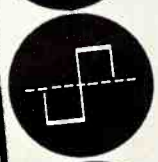
Built-in 60 cycle sweep and phasing control—a necessity for TV service work.



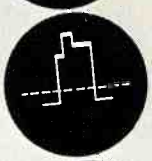
Wide band width down only 6 db at 3mc—reproduces 500 kc square wave and up to 10 mc sine wave.



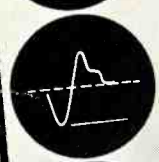
New production 5UP1 CR tube by RCA gives finest trace available for complex, hard-to-see wave forms.



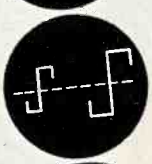
Acts as peak-to-peak vacuum tube voltmeter—measures directly on calibrated screen—built-in calibrator voltage.



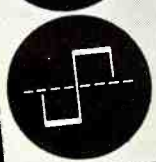Properly compensated cathode follower vertical input controls trace reproduction at any input level.



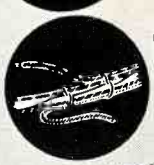Retrace blanking amplifier eliminates confusion and gives clear concise picture of viewed wave form.



New ready formed and laced wiring harness eliminates unsightly and time consuming work of assembly.

MODEL O-9

$59.50

SHIPPING WT. 28 LBS.

Announcing the newest addition to a brilliant series of Heathkit Oscilloscopes, the outstanding new model O-9 instrument. This Oscilloscope features a brand new 5UP1 cathode ray tube for really fine hairline focusing, good intensity and freedom from halation.

NEW FEATURES

Efficient voltage regulation system maintains rock steady trace stabilization. New retrace blanking amplifier circuit—amplifier band width further extended through efficient circuitry. Calibrated 1 volt peak-to-peak reference — wiring simplified by ready laced and formed wiring harness—new phasing control.

GOOD DESIGN

Terminal board for quick access to deflection plates—provisions for Z axis input—astigmatism control—balanced push-pull deflection amplifiers—internal sync on either positive or negative peaks.

VERTICAL AMPLIFIER

High impedance input with 6AB4 cathode follower, twin triode 12AT7 Cascade amplifier, 6C4 phase splitter and 12AT7 push-pull high gain deflection amplifier. Sensitivity .025 volts per inch.

HORIZONTAL AMPLIFIER

Five position input switch for choice of external input—line sweep—line sync—internal sync and external sync. Uses 12AU7 input stage, half as triode phase splitter driving 12AT7 push-pull high gain deflection amplifier. The remaining half of the 12AU7 used as retrace blanking amplifier.

POWER SUPPLY

New heavy duty internally shielded 100 milliampere power transformer. Efficient high voltage filtering system—voltage regulation completely eliminates trace bounce or jitter.

The Heathkit O-9 is the ideal general purpose oscilloscope for educational and industrial use. Radio and TV servicing and any other application requiring the instantaneous reproduction and observation of actual wave forms.

Heathkit LOW CAPACITY PROBE KIT



No. 342

$3.50

SHIP. WT. 1 LB.

Oscilloscope investigation of high frequency, high impedance or broad band width circuits requires the use of a low capacity probe. The Heathkit Low Capacity Probe features a variable capacitor to provide the necessary degree of instrument impedance matching.

Heathkit SCOPE DEMODULATOR PROBE KIT




No. 337-B

$3.50

SHIP. WT. 1 LB.

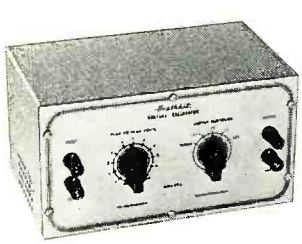In applications such as trouble shooting TV, RF, IF and video stages, the frequency ranges encountered require the demodulation of signals before oscilloscope presentation. The Heathkit Demodulator Probe will fulfill this function and readily prove its value as a service accessory.



Heathkit VOLTAGE CALIBRATOR KIT

MODEL VC-2


$11.50

SHIP. WT. 4 LBS.

The Heathkit Voltage Calibrator provides a convenient method of making peak-to-peak voltage measurements with an oscilloscope. Peak-to-peak voltages are read directly on the calibrated panel scales in the range of .01 to 100 volts peak-to-peak. A convenient "signal" position on the panel switch can be used to by-pass the calibrator and apply the signal directly to the scope input.

Heathkit ELECTRONIC SWITCH KIT

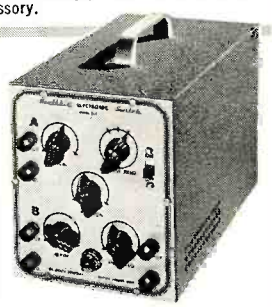The basic function of the Heathkit S-2 Electronic Switch kit is to permit simultaneous oscilloscope observation of two separate traces which can be either separated or super-imposed for individual study. Continuously variable switching rates in three ranges from less than 10 cps to over 2000 cps. Individual gain controls for each input channel and a positioning control.




MODEL S-2

$23.50

SHIP. WT. 11 LBS.

www.americanradiohistory.com

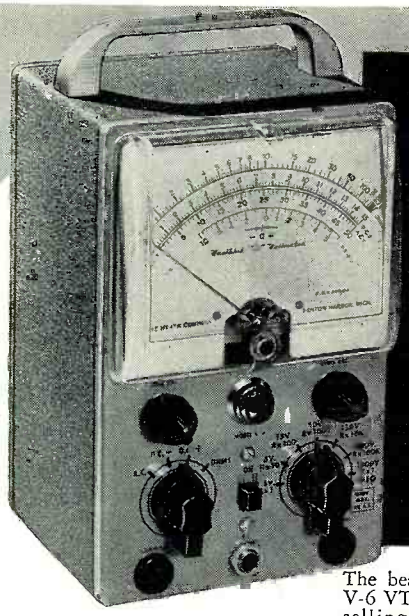

Heathkit VACUUM TUBE VOLTMETER KIT

MODEL V-6

$24.50

SHIPPING WT. 6 LBS.

Features

- New 1½ volt full scale low range
- 1,500 volt upper limit DC range
- Increased accuracy through 50% greater scale coverage
- High impedance 11 megohm input
- Center scale zero adjust
- Polarity reversal switch
- 1% precision resistors
- Clearly marked db scales

The beautiful Heathkit Model V-6 VTVM, the world's largest selling kit instrument, now offers many outstanding new features in addition to retaining all of the refinements developed and proven in the production of over 100,000 VTVM's. This is the basic measuring instrument for every branch of electronics. Easily meets all requirements for accuracy, stability, sensitivity, convenience of ranges, meter readability, and modern styling. It will accurately measure DC voltages, AC voltages, offers tremendous ohmmeter range coverage, and a complete db scale for a total of 35 meter ranges.

New 1½ volt full scale low range provides well over 2¼" of scale length per volt. Upper DC scale limit 1,500 volts. DC ranges 0-1.5, 5, 15, 50, 150, 500, 1,500 volts full scale. AC ranges 0-1.5, 5, 15, 50, 150, 500, 1,500 (1,000 volts maximum). Seven ohmmeter ranges from .1 ohm to 1,000 megohms. For added convenience a DC polarity reversing switch and a center scale zero adjustment for FM alignment.

The smartly styled, compact, sturdy, formed aluminum cabinet is finished in an attractive gray crackle exterior. The beautiful two-color, durable, infra-red, baked enamel panel further adds to the over-all professional appearance.

Top quality components used throughout. 1% precision resistors — silver contact range and selector switches — selenium rectifier — transformer operated power supply. Individual calibration on both AC and DC for maximum accuracy. DB scale printed in red for easy identification, all other scales a sharp, crisp black for easy reading. A variety of accessory probes shown on this page still add further to over-all instrument usefulness.

Heathkit 30,000 VOLT DC PROBE KIT

For TV service work or any similar application where the measurement of high DC voltage is required, the Heathkit Model 336 High Voltage Probe Kit will prove invaluable. A precision multiplier resistor mounted inside the two-color, sleek, plastic probe body provides a multiplication factor of 100 on the DC ranges of the Heathkit 11 megohm VTVM. The entire kit includes precision resistor, two-color plastic probe, tip connector spring, test lead, phone plug panel connector, and complete assembly instructions.



No. 336

$4.50


SHIP. WT. 2 LBS.

Heathkit AC VACUUM TUBE VOLTMETER KIT

MODEL AV-2

$29.50

SHIPPING WT. 5 LBS.

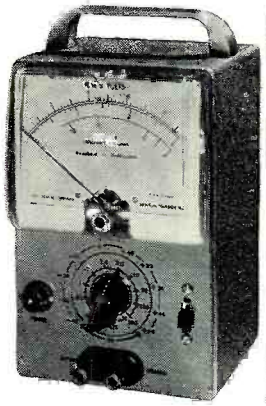

The new Heathkit AC VTVM that makes possible those sensitive AC measurements required by laboratories, audio enthusiasts, and experimenters. Especially useful for hum investigation, sensitive null detection, phono pick-up output measurements, making frequency response runs, gain measurements, ripple voltage checks, etc. Low level measurements are easy to make because of the complete voltage coverage of the instrument and the one knob operation.

The large 200 microampere Simpson meter has clearly marked and easy to read meter scales. Ten voltage ranges covering from .01 rms full scale to 300 volts rms full scale, with frequency response ± 1 db from 20 cycles to 50,000 cycles. Instrument input impedance 1 megohm, ten db ranges from −52 db to +52 db. For stability and good linearity characteristics the meter bridge circuit features 4 germanium diodes. Attractive instrument styling, a companion piece for the popular Heathkit VTVM and the new AW-1 Audio Wattmeter.

No. 338-B



Heathkit PEAK-TO-PEAK PROBE KIT

$5.50

SHIP. WT. 2 LBS.

Now read peak-to-peak voltages on the DC scales of the Heathkit 11 megohm VTVM. Readings can be directly made from the VTVM scale without involved calculations. Measurements over the frequency range of 5 kc to 5 mc. Use this probe to extend the usefulness of your VTVM in radio and TV service work. The Peak-to-Peak Probe Kit features the new polished aluminum housing with two-color polystyrene probe ends. Detailed assembly sheet including instructions for probe operation.

Heathkit RF PROBE KIT

The Heathkit RF Probe used in conjunction with any 11 megohm VTVM will permit RF measurements up to 250 mc, ± 10%. A useful, convenient accessory for those occasions when RF measurements are desired. The RF probe body is housed in the new, smartly-styled polished aluminum probe body featuring two-color polystyrene probe ends and a low capacity flexible shielded test lead. The kit is complete with all necessary material and a detailed assembly sheet as well as instructions for probe operation.



No. 309-B

$3.50

SHIP. WT. 2 LBS.

HEATH COMPANY • Benton Harbor 15, Mich.

www.americanradiohistory.com

CHECK THESE *Features*

- 20,000 ohms per volt DC sensitivity, 5,000 ohms per volt on AC
- Polarity reversal switch
- 1% precision multiplier resistors
- 50 microampere 4½" Simpson meter
- Meter ranges for service convenience
- New resistor ring-switch assembly
- Total of 35 meter ranges
- New Modern cabinet styling

NEW *Heathkit*

MULTIMETER KIT

MODEL MM-1

$26.50

SHIPPING WT. 6 LBS.



The most important Heathkit announcement of the year, the new 20,000 ohms per volt Heathkit Multimeter, Model MM-1. The universal service measuring instrument, accurate, sensitive, portable, and completely independent of AC line supply. Particularly designed for service use incorporating many desirable features for the convenience of the service man. Full 20,000 ohms per volt sensitivity on DC ranges — 5,000 ohms per volt sensitivity on AC —polarity reversal switch, no bothersome transferring of test leads — 1% precision multiplier resistors — large 4½" recessed non-glare 50 microampre Simpson meter — conveniently slanted control panel — recessed safety type banana jacks — standard universally available batteries — rugged practical sized cabinet with plastic carrying handle, and a total of 35 calibrated meter ranges.

RANGES

Voltage ranges selected entirely for service convenience. For example 1½ volt full scale low range for measuring portable radio filament voltages, bias voltages, etc., 150 volt full scale range for AC-DC service work, 500 volt full scale range for conventional transformer operated power supply systems. Complete voltage ranges AC and DC, 0-1.5—5—50—150—500—1,500—5,000 volts. DC current ranges, 0-150 microamperes—15 milliamperes—150 milliamperes—500 milliamperes—15 amperes. Resistance measurements from .2 ohms to 20 megohms x 1 x 1,000 x 10,000. DB coverage from —10 db to +65 db.

CONSTRUCTION

Entirely new design permits assembly, mounting and wiring of precision resistors on a ring-switch assembly unit. The major portion of instrument wiring is completed before mounting the ring-switch assembly to the panel. No calibration procedure is required, all precision resistors readily accessible in event of replacement.

CABINET

Strikingly modern cabinet styling featuring two piece construction, durable black Bakelite cabinet, with easy to read panel designations. Cabinet size 5½" wide x 4" deep x 7½" high. Good cabinet physical stability when operated in vertical position.

The Heathkit MM-1 represents a terrific instrument value for a high quality 20,000 ohms per volt unit using all 1% deposited carbon type precision resistors. Here is quality, performance, functional design, and attractive appearance, all combined in one low priced package.

Heathkit

BATTERY TESTER KIT



MODEL BT-1

$8.50

SHIP. WT. 2 LBS.

The Heathkit Battery Tester measures all types of dry batteries between 1½ volts and 150 volts under actual load conditions. Readings are made directly on a three color Good-Weak-Replace scale. Operation is extremely simple and merely requires that the test leads be connected to the battery under test. Only one control to adjust in addition to a panel switch for "A" or "B" battery types. The Heathkit Battery Tester features compact assembly, accurate meter movement, and a three deck wire-wound control, all mounted in a portable rugged plastic cabinet. Checks portable radio batteries, hearing aid batteries, lantern batteries, etc.

Heathkit

HANDITESTER KIT



MODEL M-1

$14.50

SHIPPING WT. 3 LBS.


The Heathkit Model M-1 Handitester readily fulfills major requirements for a compact, portable volt ohm milliammeter. Despite its compact size, the Handitester is packed with every desirable feature required in an instrument of this type. AC or DC voltage ranges full scale, 0-10—30—300—1,000—5,000 volts. Two ohmmeter ranges, 0-3,000 and 0-300,000. Two DC current measurement ranges, 0-10 milliamperes and 0-100 milliamperes. The instrument uses a Simpson 400 microampere meter movement, which is shunted with resistors to provide a uniform 1 milliampere load on both AC and DC ranges. Special type, easily accessible, battery mounting bracket — 1% deposited carbon type precision resistors — hearing aid type ohms adjust control. The Handitester is easily assembled from complete instructions and pictorial diagrams. Necessary test leads are included in the price of this popular kit.

HEATH COMPANY · Benton Harbor 15, Mich.

www.americanradiohistory.com

New *Heathkit* 12 Volt

BATTERY ELIMINATOR KIT

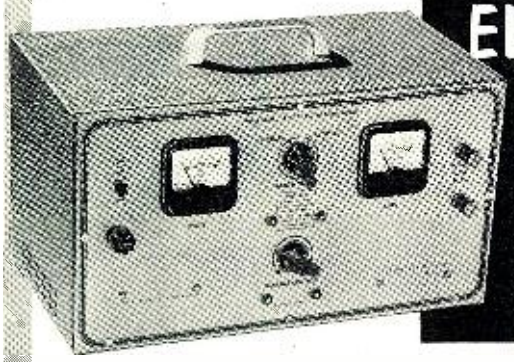

MODEL BE-4

$31.50

SHIPPING WT. 18 LBS.

CHECK THESE *Features*


- Either 6 or 12 volt operation
- Continuously variable voltage output
- Constant ammeter and voltmeter monitoring
- Automatic overload relay — self-resetting
- Two 10,000 mf condensers
- New 18 disc split type heavy duty rectifier unit
- Fuse protection

Here is the new Heathkit Battery Eliminator necessary for modern, up-to-date operation of your service shop. The Heathkit Model BE-4 furnishes either 6 volts or 12 volts output which can be selected at the flick of a panel switch. Use the BE-4 to service the new 12 volt car radios in addition to the conventional 6 volt radios.

This new Battery Eliminator provides two continuously variable output ranges, 0-8 volts DC at 10 amperes continuously, or 15 amperes maximum intermittent; 0-16 volts DC at 5 amperes continuously or 7.5 amperes maximum intermittent. The output voltage is clean and well filtered as the circuit uses two 10,000 mf condensers. The continuously variable voltage output feature is a definite aid in determining the starting point of vibrators, the voltage operating range of oscillator circuits, etc. Panel mounted meters constantly monitor voltage and current output and will quickly indicate the presence of a major circuit fault in the equipment under test. The power transformer primary winding is fuse protected and for additional safety an automatic relay of the self-resetting type is incorporated in the DC output circuit. The heavy duty rectifier is a split type 18 plate magnesium copper sulfide unit used either as a full wave rectifier or voltage doubler according to the position of the panel range switch.

Here is the ideal battery eliminator for all of your service problems and as an additional feature, it can also be used as a battery charger. Another new application for the Heathkit Battery Eliminator is a variable source of DC filament supply in audio development and research. More than adequate variable voltage and current range for normal applications.

Heathkit VIBRATOR TESTER KIT

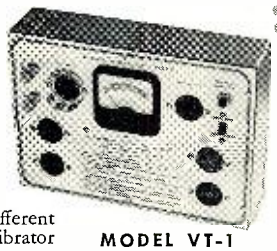

Your repair time is valuable, and service use of the Heathkit Vibrator Tester will save you many hours of work. This tester will instantly tell you the condition of the vibrator being checked. Checks vibrators for proper starting and the easy to read meter indicates quality of output on a large Bad-?-Good scale. The Heathkit VT-1 checks both interrupter and self rectifier types of vibrators. Five different sockets for checking hundreds of vibrator types.

The Heathkit Vibrator Tester operates from any battery eliminator capable of delivering continuously variable voltage from 4 to 6 volts DC at 4 amperes. The new Heathkit Model BE-4 Battery Eliminator would be an ideal source of supply.

MODEL VT-1

$14.50

SHIPPING WT. 6 LBS.

NEW *Heathkit* VARIABLE VOLTAGE ISOLATION TRANSFORMER KIT




The new Heathkit Isolation Transformer Kit provides line isolation for AC-DC radios (not an auto transformer), thereby eliminating shock hazard, hum problems, alignment difficulties, etc. The output voltage is variable from 90 to 130 volts AC and is constantly monitored by a panel mounted AC volt meter. Use it to increase AC supply voltage in order to induce breakdown of faulty components in circuits thereby saving service time. Use it also to simulate varying line voltage conditions and to determine the line voltage level at which oscillator circuits cease functioning, particularly in three-way portable radios. Rated at 100 watts continuous operation and up to 200 watts maximum intermittent operation. A useful radio and TV service tool.

MODEL IT-1

$16.50

SHIP. WT. 9 LBS.

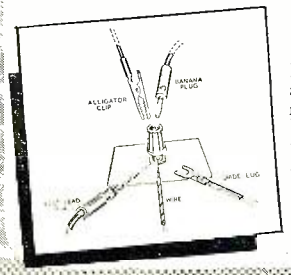

Heathkit BINDING POST

Binding post kit now available so that standardization of all instrument connectors is possible. This new, five-way binding post will accommodate an alligator clip, banana plug, test lead pin, spade lug, or hook-up wire. Sold in units of 20 binding post assemblies. Each assembly includes binding post, flat and shoulder fiber washers, solder lug, and nut. 120 pieces in all. Kit 362, $4.00.



Heathkit TECHNICAL APPLICATION BULLETINS

An exclusive Heathkit service. Technical application bulletins prepared by recognized instrument authorities outlining various combinations of instrument applications. Available now with 40 four-page illustrated bulletins and an attractive flexible loose-leaf binder. Only $2.00. (No c.o.d. on this item, please.)

HEATH COMPANY • Benton Harbor 15, Mich.

www.americanradiohistory.com

CHECK THESE *Features*

- INCREDUCTOR controllable inductor sweep
- TV and IF sweep deviation 12-30 mc
- 4 mc- 220 mc continuous frequency coverage
- Oscillator operation entirely on fundamentals
- Output in excess of 100,000 microvolts
- Automatic amplitude circuit
- Voltage regulation
- Simplified operation

NEW *Heathkit*

TV ALIGNMENT GENERATOR KIT

MODEL TS-3

$44.50

SHIPPING WEIGHT 18 POUNDS



Proudly announcing an entirely new, advanced model TV and FM Sweep Generator, the Heathkit Model TS-3. This new design provides features and combinations of functions not found in any other service type instrument. Every design consideration has been given to the requirements of the TV service man to provide a flexible, variable sweep source with more than adequate RF output and complete frequency coverage throughout the TV and FM spectrum.

The frequency range of the TS-3 is from 4 mc to 220 mc in four switch selected ranges. All frequency ranges are overlapping for complete coverage. A particularly important feature of the instrument is that the oscillator operates entirely on fundamentals, thereby providing complete freedom from spurious oscillation and parasitics normally encountered in beat frequency type oscillators. This circuitry assures a much higher total RF output level and simplifies attenuation problems.

The new TS-3 features an entirely new principle of sweep operation. Sweep action is entirely electronic with no moving parts or electro-mechanical devices so commonly used. The heart of the sweep system is a newly-developed INCREDUCTOR controllable inductor. With this system, the value of inductance of each oscillator coil is electrically varied with an AC control current, and the inductance variation is achieved by a change in the magnetic state of the core on which the oscillator coils are wound. This system provides a sweep deviation of not less than 12 mc on all TV frequencies, and up to a maximum of 30 mc on TV IF frequencies. The high RF output level throughout the instrument frequency range overcomes the most common complaint of the older type sweep generators. A new, automatic amplitude control circuit maintains the output level flat to ± 2 db throughout the instrument range. For convenience of operation a low impedance 50 ohm output is used.

Operation of the instrument has been simplified through the reduction of panel controls and separate panel terminals provide for external synchronization if desired. The circuit uses a voltage regulator tube to maintain stable instrument operation. A built-in variable oscillator marker further adds to flexibility of instrument operation. Provisions are also made for the use of an external marker, such as your service type signal generator, if desired. Use the Heathkit TS-3 for rapid, accurate TV alignment work, and let it help you solve those time consuming, irksome problems so frequently encountered.

NEW *Heathkit*

SIGNAL GENERATOR KIT



MODEL SG-8

$19.50

SHIPPING WEIGHT 8 POUNDS

Announcing the new Heathkit Model SG-8 service type Signal Generator, incorporating many design features not usually found in an instrument in this price range. The RF output is from 160 kc to 100 mc in five ranges, all on fundamentals, with useful harmonics up to 200 mc. The RF output level is in excess of 100,000 microvolts throughout the frequency range.

The oscillator circuit consists of a 12AT7 twin triode tube. One half is used as a Colpitts oscillator, and the other half as a cathode follower output which acts as a buffer between the oscillator and external load. This circuitry eliminates oscillator frequency shift usually caused by external circuit loading.

All coils are factory wound and adjusted, thereby completely eliminating the need for calibration and the use of additional calibrating equipment. The stable low impedance output features a step and variable attenuator for complete control of RF level. A 6C4 triode acts as a 400 cycle sine wave oscillator and a panel switching system permits a choice of either external or internal modulation.

The transformer operated circuit is easy to assemble, requires no calibration, and meets every service requirement for an adjustable level variable frequency signal source, either modulated or un-modulated.

NEW *Heathkit*

BAR GENERATOR KIT



MODEL BG-1

$14.50

SHIPPING WEIGHT 6 POUNDS

The Heathkit BG-1 Bar Generator represents another welcome addition to the fast growing line of popular Heathkits. The station transmitted test pattern is rapidly disappearing, and the bar generator is the logical answer to the TV service man's problem in obtaining quick, accurate adjustment information without waiting for test patterns.

The Heathkit BG-1 produces a series of horizontal or vertical bars on a TV screen. Since these bars are equally spaced, they will quickly indicate picture linearity of the receiver under test. Panel switch provides "stand-by position" — "horizontal position" — "vertical position." The oscillator unit utilizes a 12AT7 twin triode for the RF oscillator and video carrier frequencies. A neon relaxation oscillator provides low frequency for vertical linearity tests. The instrument will not only produce bar patterns but will also provide an indication of horizontal and vertical sync circuit stability, as well as overall picture size.

Instrument operation is extremely simple, and merely requires connection to the TV receiver antenna terminal. The unit is transformer operated for safety when used in conjunction with universal or transformerless type TV circuits.

HEATH COMPANY • Benton Harbor 15, Mich.

www.americanradiohistory.com


NEW *Heathkit*

TUBE CHECKER KIT

MODEL TC-2

$29.50

SHIP. WT. 12 LBS.

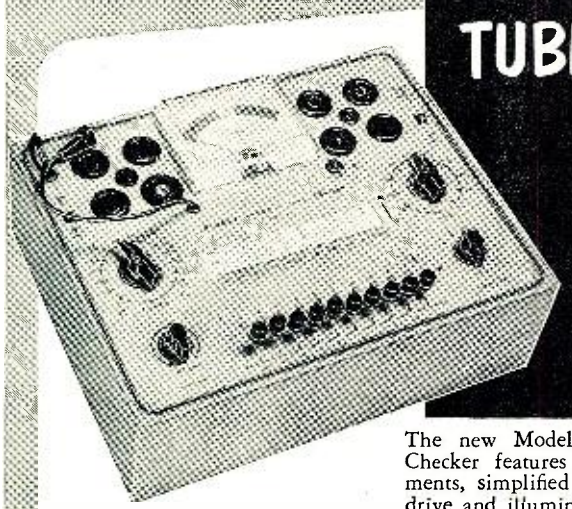

CHECK THESE NEW *Features*

- Simplified harness wiring
- Improved, smooth, anti-backlash roll chart action
- Optional roll chart illumination
- Individual element switches
- Portable or counter style cabinet
- Spare blank socket
- Contact type pilot light test socket
- Simplified test set-up procedure
- Line adjust control
- 4½" three-color meter

The new Model TC-2 Heathkit Tube Checker features many circuit improvements, simplified wiring, new roll chart drive and illumination of roll chart. The instrument is primarily designed for the convenience of the radio and TV service man and will check the operating quality of tubes commonly encountered in this type of work. Test set-up procedure is simplified, rapid, and flexible. Panel sockets accommodate 4, 5, 6, and 7 pin tubes, octal and loctal, 7 and 9 pin miniatures, 5 pin Hytron and a blank socket for new tubes. Built-in neon short indicator, individual three-position lever switch for each tube element, spring return test switch, 14 filament voltage ranges, and line set control to compensate for supply voltage variations, all represent important design features of the TC-2. Results of tube tests are read directly from a large 4½" Simpson three-color meter, calibrated in terms of Bad-?-Good. Information that your customer can readily understand. Checks emission, shorted elements, open elements, and continuity.

The use of closer tolerance resistors in critical circuits assures correct test information and eliminates the possibility of inaccurate test interpretation. Improvement has been made in the mechanical roll chart drive system, completely eliminating diagonal running, erratic operation, and backlash. The thumb wheel gear driven action is smooth, positive, and free running. As an additional feature, the roll chart is illuminated for easier reading, particularly when the tube checker is used on radio or TV home service calls.

Wiring procedure has been simplified through the extended use of multicable, color coded wires, providing a harness type installation between tube sockets and lever switches. This procedure insures standard assembly and imparts that "factory built" appearance to instrument construction. Completely detailed information is furnished in the new step-by-step construction manual, regarding the set-up procedure for testing of new or unlisted tube types. No delay necessary for release of factory data.

The new Heathkit Tube Checker will prove its value in building service prestige through usefulness — simplified operation — attractive professional appearance. Don't overlook the fact that the kit price represents a savings of $40.00 to $50.00 over the price of a comparable commercially built instrument. At this low price, no service man need be without the advantages offered by the Heathkit Tube Checker.

New

HEATHKIT

PORTABLE TUBE CHECKER KIT

MODEL TC-2P

$34.50

SHIP. WT. 14 LBS.



The portable model is supplied with a strikingly attractive two-tone cabinet finished in rich maroon, proxylin impregnated, fabric covering with a contrasting gray on the inside cover. Detachable cover, brass-plated hardware, sturdy plastic handle help to impart a truly professional appearance to the instrument.

PORTABLE TUBE CHECKER CABINET as described above will fit all earlier Heathkit TC-1 Tube Checkers. Shipping weight 7 lbs. Cabinet only, 91-8, $7.50.




Heathkit TV PICTURE TUBE

TEST ADAPTER

No. 355
Ship. Wt. 1 Lb.
$4.50

The Heathkit TV Picture Tube Test Adapter used with the Heathkit Tube Checker will quickly check for emission, shorts, etc., and determine picture tube quality. Consists of standard 12 pin TV tube socket, four feet of cable, octal socket connector, and data sheet.

Heathkit POWER SUPPLY KIT

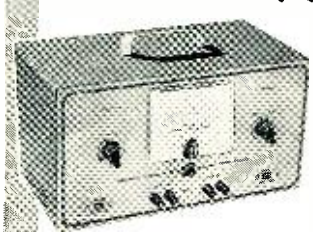

MODEL PS-2

$33.50

SHIPPING WT. 17 LBS.

The Heathkit Laboratory Power Supply features continuously variable, regulated voltage output with good stability under wide load variations. A 4½" Simpson plastic enclosed panel mounted meter provides accurate meter output information of voltage or current. All panel terminals completely isolated from the cabinet. Separate 6.3 volt AC supply at 4 amperes for filament requirements. Ripple component exceptionally low, stand-by switch provided to eliminate warm-up time of the five tube circuit.



LABORATORY AND SERVICE SHOP BOOKLETS

"Planning Your Service Business" by John T. Frye, and "Establishing the Industrial Electronics Laboratory" by Louis B. Garner, Jr., are booklets available to Heathkit customers at no charge. These booklets, written by nationally recognized authorities, outline the various requirements and considerations for establishing your own service business or for setting up an industrial electronics laboratory. Full attention is given to various details that are frequently overlooked when projects of this nature are undertaken. Just write in to the Heath Company requesting your free copy, or attach a memo to your next order.

HEATH COMPANY · Benton Harbor 15, Mich.

www.americanradiohistory.com

CHECK THESE *Features*

- Visual and aural signal tracing
- Two channel input
- High RF sensitivity
- Unique noise locater circuit
- Calibrated wattmeter
- Substitution test speaker
- Utility amplifier
- RF, audio probes and test leads included

Heathkit VISUAL-AURAL SIGNAL TRACER KIT

MODEL T-3

$23.50

SHIPPING WEIGHT 10 POUNDS



An entirely new type of signal tracer incorporating a combination of features not found in any other instrument. Designed expressly for the radio and TV service man, particularly for the servicing of AM, FM, and TV circuits. Here in a five tube, transformer operated instrument are all of the useful functions so necessary for speedy, accurate isolation of service difficulty.

This new signal tracer features a special high gain RF input channel, used in conjunction with a newly-designed wide frequency range demodulator probe. High RF sensitivity permits signal tracing at the receiver antenna input. A separate low gain channel and probe available for audio circuit exploration. Both input channels are constantly monitored by an electron ray beam indicator, so that visual as well as aural signal indications may be observed. The instrument can also be used for comparative estimation of gain per stage.

A decidedly unusual feature is a noise localizer circuit in conjunction with the audio probe. With this system, a DC potential is applied to a suspected circuit component and the action of the voltage in the component can be seen as well as heard. Invaluable for ferreting out noisy or intermittent condensers, noisy resistors, controls, coils, IF and power transformers, etc. A built-in calibrated wattmeter circuit is very useful for a quick preliminary check of the total wattage consumption of the equipment under test. Separate panel terminals provide external use of the speaker or output transformer for substitution purposes. Saves valuable service time by eliminating the necessity for speaker removal on every service job. The terminals also permit the utilization of other shop equipment, such as your oscilloscope or VTVM. The T-3 Signal Tracer can be used as a high gain amplifier for checking tuners, record changers, microphones, phono crystals, etc.

Don't overlook the interesting service possibilities provided through the use of this new instrument and let it work for you by saving time and money. The kit is supplied complete with all tubes, circuit components, demodulator probe, audio probe, and additional test leads.

Heathkit DECADE RESISTANCE KIT



MODEL DR-1

$19.50

SHIP. WT. 4 LBS.

The Decade Resistance Kit provides individual switch selection of resistance values using twenty 1% resistors providing a choice of 1 to 99,999 ohms in 1 ohm steps. Ceramic wafer switches, silver-plated contacts, smooth, positive detent action, baked enamel panel, and handsome, polished birch cabinet.

Heathkit DECADE CONDENSER KIT



MODEL DC-1

$16.50

SHIP WT 4 LBS.

The Heathkit Decade Condenser Kit features silver mica, precision condensers with a rated accuracy of ± 1%. Capacity values are arranged in three decades from 100 mmf to .111 mf in steps of 100 mmf. Ceramic wafer switches with silver-plated contacts and smooth detent action. Useful in laboratory work, for circuit development.

Heathkit RESISTANCE SUBSTITUTION BOX KIT




MODEL RS-1

$5.50

SHIP. WT. 2 LBS.

The Heathkit Resistance Substitution Box provides individual switch selection of any one of 36 RTMA 1 watt 10% standard value resistors, ranging from 15 ohms to 10 meghoms. Many applications in circuit development work, and also in radio and TV service work. Ideal for experimentally determining resistance values and for quickly altering circuit operating characteristics. Entire unit housed in attractive Bakelite cabinet, featuring the new universal type Heathkit binding posts to simplify circuit connections.

Heathkit CONDENSER CHECKER KIT

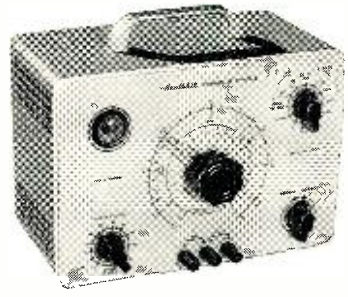

MODEL C-3

$19.50

SHIPPING WT. 8 POUNDS

Use the Heathkit C-3 Condenser Checker to quickly and accurately measure those unknown condenser and resistor values. All readings are taken directly from the calibrated panel scales without requiring any involved calculation. Capacity measurements in four ranges from .00001 mf to 1,000 mf. Checks paper, mica, ceramic, and electrolytic condensers. A power factor control is available for accurate indication of electrolytic condenser measurements. A leakage test switch with switch selection of five polarizing voltages, 25 volts to 450 volts DC, will indicate condenser operating quality under actual load condition. The spring return leakage test switch automatically discharges the condenser under test and eliminates shock hazard to the operator.

Resistance measurements can be made in the range from 100 ohms to 5 megohms. Here again all values are read directly on the calibrated scale. Increased circuit sensitivity coupled with an electron beam null indicator increases overall instrument usefulness.

For safety of operation the circuit is entirely transformer operated and the instrument is housed in the attractive, newly-styled Heathkit cabinet, featuring rounded corners, and drawn aluminum panel. The outstanding low kit price for this surprisingly accurate instrument includes necessary test leads. Good service shop operation requires the use of this specialized instrument, designed for the express purpose of determining unknown condenser values and operating characteristics.

HEATH COMPANY · Benton Harbor 15, Mich.

www.americanradiohistory.com

Heathkit AMATEUR TRANSMITTER KIT



MODEL AT-1

$29.50

SHIPPING WEIGHT 16 POUNDS

CHECK THESE NEW *Features*


- Single knob band switching
- Pre-wound coils
- Metered operation
- 52 ohm coaxial output
- Crystal or VFO excitation
- Built-in power supply
- Rugged, clean construction

Here is the latest Heathkit addition to the ham radio field, the AT-1 Transmitter Kit, incorporating many desirable design features at the lowest possible dollar-per-watts price. Panel mounted crystal socket, stand-by switch, key click filter, AC line filtering, good shielding, etc. VFO or crystal excitation — up to 35 watts input. Built-in power supply provides 425 volts at 100 ma.

This kit features pre-wound coils, single knob band switching, 52 ohm coaxial output, plug in chassis provisions for VFO or modulator and rugged clean construction. Frequency range 80, 40, 20, 15, 11, and 10 meters. Tube line-up 6AG7 oscillator-multiplier, 6L6 amplifier-doubler, 5U4G rectifier. Physical dimensions 8⅛" high x 13⅛" wide x 7" deep.

This amazingly low kit price includes all circuit components, tubes, cabinet, punched chassis, and detailed construction manual. The ideal kit for the novice just breaking into ham radio. It can be used later on as a stand-by rig or an all band exciter for higher powered transmitter.

NEW *Heathkit* ANTENNA COUPLER KIT

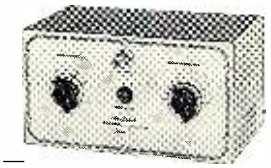

New Heathkit Antenna Coupler, specially designed for the Heathkit AT-1 Transmitter. The Antenna Coupler can be used with any 52 ohm coaxial input — up to 75 watts power. Low pass filter with cut-off frequency of approximately 36 mc — L section tuning network — neon tuning indicator — rugged, compact construction — transmitter type variable condenser, and high Q coil are all outstanding features. The AC-1 has both inductance and capacity tuning for maximum operating versatility. Dimensions 8⅛" wide x 4⅜" high x 4⅞" deep.

MODEL AC-1

$14.50 SHIP. WT. 3 LBS.

Heathkit ANTENNA IMPEDANCE METER



Use the Heathkit Antenna Impedance Meter for measuring antenna impedance for line matching purposes — adjustment of beam antennas — phone monitor, etc. It will determine antenna resistance at resonance, match transmission line for minimum SWR, determine receiver input impedance, and provide a rough indication of SWR. Precision resistors, germanium diode, 100 microampere Simpson meter. Dial calibrated from 0-500 ohms. Shielded aluminum cabinet. 7" long x 2½" wide x 3¼" deep.

$14.50 SHIP. WT. 3 LBS.

MODEL AM-1

Heathkit COMMUNICATIONS RECEIVER KIT



MODEL AR-2

$25.50 SHIP. WT. 12 LBS.

Here is the new receiver kit you have repeatedly asked for, the Heathkit Communications Receiver. The perfect companion piece for the AT-1 Transmitter kit. Many outstandingly desirable features have been incorporated in the design of the AR-2; such as, electrical bandspread for logging and tuning convenience — high gain miniature tubes — IF transformers for high sensitivity and good signal to noise ratio — separate RF gain control with optional automatic volume control or manual volume control, in addition to the conventional audio gain control. Noise limiter — stand-by switch — stable BFO oscillator circuit — headphone jack — transformer operation, etc., all contribute to a high performance standard.

Frequency coverage is continuous from 535 kc to 35 mc in four ranges. For added convenience, various ham bands have been separately identified in respect to their relative placement on the slide rule tuning scale. A chassis mounted, 5½" PM speaker is included with this kit. Tube line up 12BE6 mixer oscillator, 12BA6 IF amplifier, 12AV6 detector AVC audio, 12BA6 BFO oscillator, 12A6 beam power output, 5Y3GT rectifier.

RECEIVER CABINET

Proxylin impregnated, fabric covered, plywood cabinet with aluminum panel designed expressly for the AR-2 Receiver. Part 91-10, shipping weight 5 lbs., $4.50.


IMPROVED *Heathkit* GRID DIP METER KIT



$19.50 SHIP. WT. 4 LBS.

MODEL GD-1B

The invaluable instrument for service men, hams, and experimenters. Useful in TV service work for alignment of traps, filters, IF stages, peaking compensation networks, etc. Locates spurious oscillation, provides a relative indication of power in transmitter stages. use it for neutralization, locating parasitics, correcting TVI, measuring C, L, and Q of components, and determining RF circuit resonant frequencies. With oscillator energized, useful for finding resonant frequency of tuned circuits. With the oscillator not energized, the instrument acts as an absorption wave meter. Variable meter sensitivity control, head phone jack, 500 microampere Simpson meter. Continuous frequency coverage from 2 mc. to 250 mc. Pre-wound coil kit and rack, new three prong coil mounting, 6AF4 high frequency triode.

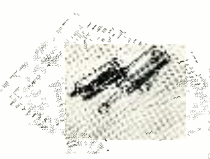

Two additional plug-in coils are available and provide continuous extension of low frequency coverage down to 355 kc. Dial correlation curves included. Shipping weight 1 lb., kit 341, $3.00.


HEATH COMPANY · Benton Harbor 15, Mich.

www.americanradiohistory.com

CHECK THESE *Features*

- First popular priced Q Meter
- Reads Q directly on calibrated scale
- Oscillator supplies RF frequencies of 150 kc to 18 mc
- Calibrate capacitor with range of 40 mmf to 450 mmf with vernier of ± 3 mmf
- Measures Q of condensers, RF resistance, and distributed capacity of coils
- Many applications in design and development work
- Useful in TV service work for checking deflection yokes, coils, chokes, etc.

Heathkit "Q" METER KIT

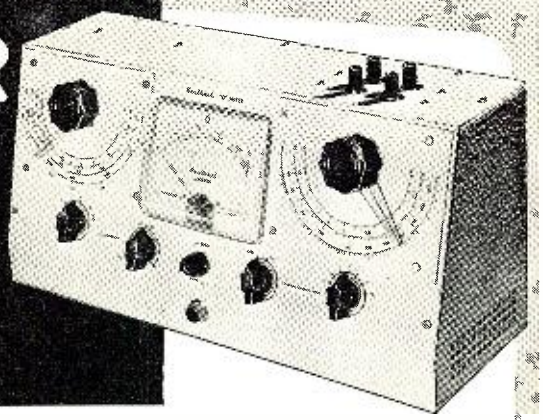

MODEL QM-1

$44.50

SHIPPING WT. 14 POUNDS

Another outstanding example of successful Heathkit engineering effort in producing a Q Meter Kit within the price range of TV service men, schools, laboratories, and experimenters. This Q Meter meets RF design requirements for rapid, accurate measurement of capacity, inductance, and Q at the operating frequency and all indications of value can be read directly on the meter calibrated scales. Oscillator section supplies RF frequencies of 150 kc to 18 mc. Calibrate capacitor with range of 40 mmf to 450 mmf, with vernier of ± 3 mmf.

Particularly useful in TV service work for checking peaking coils, wave traps, chokes, deflection coils, width and linearity coils, etc. At this low kit price research laboratory facilities are within the range of service shops, schools, and experimenters.

Heathkit INTERMODULATION ANALYZER KIT



MODEL IM-1

$39.50

SHIPPING WT. 17 POUNDS

The Heathkit IM-1 is an extremely versatile instrument specifically designed for measuring the degree of inter-action between two signals in any portion of an audio chain. It is primarily intended for making tests of audio amplifiers, but may be used in other applications, such as checking microphones, records, recording equipment, phonograph pick-ups, and loud-speakers. High and low test frequency source, intermodulation unit, power supply, and AC vacuum tube volt meter all in one complete instrument. Per cent intermodulation is directly read on the calibrated scales, 30%, 10%, and 3% full scale. Both 4:1 and 1:1 ratios of low to high frequency easily set up. With this instrument the performance level of present equipment, or newly developed equipment can be easily and accurately checked. At this low price, you can now enjoy the benefits of intermodulation analysis for accurate audio interpretation.

Heathkit AUDIO GENERATOR KIT

A Heathkit Audio Generator with frequency coverage from 20 cycles to 1 mc. Response flat ± 1 db from 20 cycles to 400 kc, down 3 db at 600 kc, and down only 8 db at 1 mc. Calibrated, continuously variable, and step attenuator output controls provide convenient reference output level. Distortion is less than .4% from 100 cps through the audible range. The ideal controllable extended frequency sine wave source for audio circuit investigation and development.

MODEL AG-8




$29.50

SHIP. WT. 11 LBS.

Heathkit AUDIO OSCILLATOR KIT

Sine or square wave coverage from 20 to 20,000 cycles in three ranges at a controllable output level up to 10 volts. Low distortion, 1% precision resistors in multiplier circuits, high level output across entire frequency range, etc., readily qualify this instrument for audio experimentation and development work. Special circuit design consideration features thermistor operation for good control of linearity.

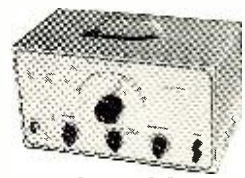

MODEL AO-1

$24.50

SHIP. WT. 11 LBS.

Heathkit AUDIO FREQUENCY METER KIT




MODEL AF-1

$34.50

SHIP. WT. 12 LBS.

The Heathkit Audio Frequency Meter provides a simple and convenient means of checking unknown audio frequencies from 10 cycles to 100 kc at any voltage level between 3 and 300 volts rms with any non-critical wave shape. Instrument operation is entirely electronic. Just set the range switch, feed an unknown frequency into the instrument, and read the frequency directly on the calibrated scale of the Simpson 4½" meter.

Heathkit SQUARE WAVE GENERATOR KIT

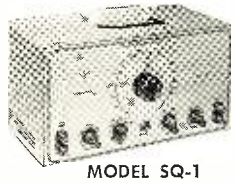

MODEL SQ-1

$29.50

SHIP. WT. 12 LBS.

The Heathkit Square Wave Generator provides an excellent square wave frequency source with completely variable coverage from 10 cycles to 100 kc. This generator features low output impedance of 600 ohms and the output voltage is continuously variable between 0 and 20 volts, thereby providing the necessary degree of operating flexibility. An invaluable instrument for those specialized circuit investigations requiring a good, stable, variable square wave source.

HEATH COMPANY · Benton Harbor 15, Mich.

www.americanradiohistory.com

Heathkit
WILLIAMSON TYPE
AMPLIFIER KIT
MODEL W-2



Particularly designed for custom installations, featuring separate cable connected units for simplicity of installation. Sheet metal work finished in attractive gray hammertone for smart appearance. All control shafts of the adjustable length break-off type.

$69.50

When selecting an amplifier for the heart of your high fidelity audio system, investigate the outstanding advantages offered by the Heathkit Williamson Type Amplifier. Meets every high fidelity audio requirement and makes listening to recorded music a thrilling new experience.

This outstanding amplifier is offered with optional output transformer operation, providing either the conventional triode output circuit or the new extended power circuitry in which the screen supply voltage is obtained from separate transformer primary taps. Frequency response within ± 1 db from 10 cycles to 100 kc. Tube complement — 6SN7 cascade amplifier and phase splitter, 6SN7 push pull driver, two 5881 push pull power amplifiers, one 5V4G cathode type rectifier.

Matching preamplifier available providing three switch selected inputs, correct compensation, and individual bass and treble tone controls. Uses 12AY7 (or 12AX7) preamplifier — 12AU7 tone control amplifier.

Particularly designed for the novice kit builder and requires no specialized knowledge or equipment for successful assembly and operation.

PRICES OF COMBINATIONS

W-2 Amplifier Kit including main amplifier, power supply, and WA-P1 Preamplifier Kit. Shipping Weight 37 lbs. Shipped Express only. **$69.50**

W-2M Amplifier Kit includes main amplifier and power supply. Shipping Weight 29 lbs. Shipped Express only. **$49.75**

WA-P1 Preamplifier Kit only. Shipping Weight 6 lbs. Shipped Express or Parcel Post. **$19.75**

NEW *Heathkit* 20 WATT
High Fidelity AMPLIFIER KIT

MODEL A-9A




$35.50

SHIP. WT. 18 LBS.

A new 20 watt high fidelity amplifier, designed especially for custom audio installations demanding clean reproduction, adequate power, and flexibility to meet individual requirements. Separate treble and bass tone controls provide up to 15 db boost or cut. Four switch selected inputs, each with the necessary compensation for the service desired. Output transformer impedances of 4, 8, and 16 ohms.

Preamplifier, tone control, and phase splitter circuits utilize 9 pin twin triode miniature tubes for low hum and noise level. Two 6L6 push pull power output tubes provide full 20 watts power. Frequency response ± 1 db, 20-20,000 cycles. Total harmonic distortion 1% (at 3 db below rated output). Tube line-up: 12AX7 preamplifier, 12AU7 voltage amplifier and tone control, 12AU7 voltage amplifier and phase splitter, two 6L6 push pull pentode power output, 5U4G rectifier. Truly outstanding amplifier performance coupled with low cost.

Heathkit ECONOMY 6 WATT
AMPLIFIER KIT

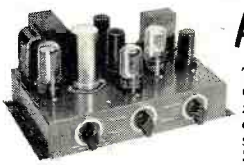

MODEL A-7B

$15.50

SHIP. WT. 10 LBS.

The new Heathkit Model A-7B Amplifier offers many unusually fine features not normally expected in this low price range. Either of the two input circuits may be individually switch selected for phono or tuner operation. Separate bass and treble tone controls. Output impedances of 4, 8, and 15 ohms. Push pull beam power output stage for balanced reproduction. Excellent voltage gain characteristics, good frequency response, and full 6 watts power output. 12J5 amplifier, 12SL7 second amplifier and phase splitter, two 12A6 beam power output, one 5Y5 GT rectifier.

A-7C incorporates preamplifier stage with special compensated network to provide necessary gain for operation with variable reluctance or low output level phono cartridge. Circuit is properly compensated for microphone operation. $17.50.

NEW *Heathkit*
BROADCAST BAND
RECEIVER KIT



MODEL BR-2


$17.50 SHIP. WT. 11 LBS.

Another new Heathkit for the student, beginner, or hobbyist. If you have ever had the urge to build your own radio receiver, this kit warrants your attention.

New high gain miniature tubes and IF transformers provide excellent sensitivity and good signal to noise ratio. A built-in ferrite core rod type antenna has been provided. A chassis mounted 5½" PM speaker provides excellent tone and volume. Convenient phono input. Can be operated either as a receiver or tuner. Simplified construction manual outlines circuit theory. Ideal for students. Tube line-up: 12BE6 mixer oscillator, 12BA6 IF amplifier, 12AV6 detector-AVC-first audio, 12A6 beam power output, 5Y3GT rectifier.

CABINET — Proxylin impregnated fabric covered plywood cabinet. Shipping weight 5 lbs. Part number 91-9, $4.50.

Heathkit
FM TUNER KIT

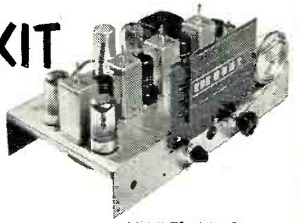

MODEL FM-2

$22.50

SHIP. WT. 9 LBS.

The Heathkit FM-2 Tuner was specifically designed for simplified kit construction. Can be operated through the "phono" portion of your radio or with a separate amplifier. The kit features a pre-assembled and adjusted tuning unit, three double tuned IF transformers, and a discriminator transformer in an 8 tube AC operated circuit. Frequency coverage 88 to 108 mc. Experience the thrill of building your own FM tuner and at the same time enjoy all of the advantages of true FM reception.

Free CATALOG

Write for free catalog containing latest price information, schematics, specifications, and descriptions of all Heathkits.

HEATH COMPANY • Benton Harbor 15, Mich.


www.americanradiohistory.com

NEW HEATHKIT *Dual* RECORD PLAYER KIT

DUAL 6" SPEAKERS for diffused room-filling sound

New MODEL RP-2 $69.50

SHIPPING WT. 33 LBS.

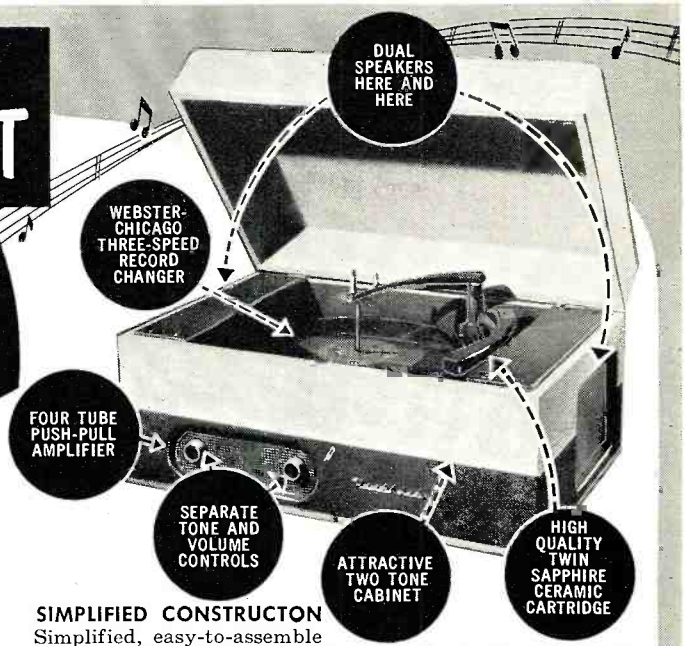

DUAL MATCHED SPEAKERS
A new economical introduction to high quality record reproduction. A simple-to-operate, compact, table-top model with two matched speakers in an acoustically correct enclosure reproduce all of the music on the record.

DIFFUSED SOUND
Because of the diffused non-directional properties of the dual speakers, listening to fine recorded music is a thrilling new experience through naturally clear, life-like reproduction of sound at all tonal levels.

HIGH QUALITY PERFORMANCE
The performance level of the Dual is vastly superior to that of the ordinary phonograph or console. Automatic changer plays all three sizes at all three speeds with automatic shutoff after last record is played.

TWIN SAPPHIRE STYLUS
A wide tonal range ceramic cartridge features an ingenious "turn-under" twin sapphire stylus for LP or 78 records providing quick selection of the correct stylus without turning the cartridge.


SIMPLIFIED CONSTRUCTON
Simplified, easy-to-assemble four tube amplifier features compensated volume control and separate tone control. Proxylin impregnated beige and saddle tan fabric covered cabinet supplied completely assembled. You build only the amplifier.

EASY TO BUILD
No specialized tools or knowledge required as the construction manual has been simplified to the point where even the complete novice can successfully construct the Heathkit Dual. The price includes cabinet, record changer, two 6" PM speakers, tubes and all circuit components required for assembly.

Send for free audio booklet "High Fidelity Especially for You."

HEATH COMPANY • Benton Harbor 15, Mich.

ORDER BLANK

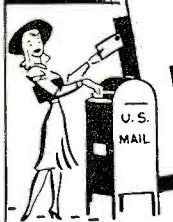

MAIL YOUR ORDER TODAY TO THE HEATH COMPANY BENTON HARBOR 15, MICHIGAN

OR PHONE BENTON HARBOR 5-1175

From _____

_____

_____

PLEASE PRINT

SHIP VIA
- ☐ Parcel Post
- ☐ Express
- ☐ Freight
- ☐ Best Way

QUANTITY	MODEL NO.	DESCRIPTION	WEIGHT	PRICE

REMARKS

TOTAL WEIGHT AND AMOUNT . . .

Enclosed find ( ) check ( ) money order for
Please ship C.O.D. ( ) postage enclosed for ____ pounds.

On Express orders do not include transportation charges — they will be collected by the express agency at time of delivery.

www.americanradiohistory.com


WHAT'S New in Radio

The products described in this column are for your convenience in keeping up-to-date on the new equipment being offered by manufacturers. For more complete information on any of these products, write direct to the company involved.

PALM-SIZE RADIO

Precision Electronics Laboratory, Placerville, California is now marketing a palm-sized radio receiver, powered by hearing aid batteries, which covers the standard broadcast band.

One 1½ volt battery is used for the

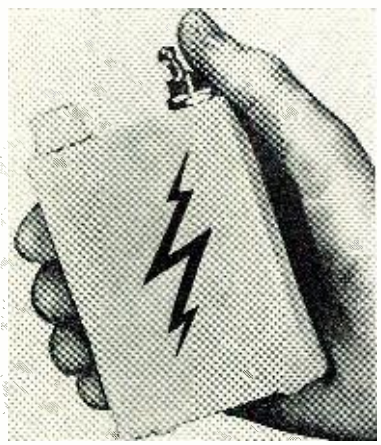

filament of a 3V4 tube while a 22½ volt battery is used for the plate circuit. Tuning is accomplished by means of a ferrite-tuned antenna coil. The circuit is self-regenerative.

An extensive antenna system is not required as a clip is provided that can be attached to a finger stop of a dial telephone, a bedspring, screen door, or a 30 foot length of wire. Any earphone of 1500 ohms impedance or more can be used. Volume on local stations is slightly greater than telephone reception.

The radio is available in both wired and kit form. The kit requires about 1 hour's time for assembling. A wiring diagram accompanies each unit.

TRANSISTOR TRANSFORMERS

Microtran Company, division of *Crest Laboratories, Inc.,* Rockaway Beach, N.Y. is now offering a line of extremely small transformers which have been designated "Veri-Miniature" transformers.

Designed for use in transistorized circuitry, such as hearing aids, etc., they are available for input, interstage, output, and choke applications. The transformers measure 7/16" x ½" x 7/16". Frequency response is flat from 300 to 10,000 cycles.

Special units are also available on a custom basis. Full details are available from the company.

TEST LEADS

A new pair of *Lucite* handled test leads, for use with standard voltmeters, multimeters, v.t.v.m.'s, and similar instruments, has been introduced by *Insuline Corporation of America,* 3602 35th Avenue, Long Island City 1, N.Y.

Virtually indestructible, the heavy handles are five inches long and ⅜ inch in diameter and furnish reliable protection against the high a.c. and d.c. voltages encountered in electronic equipment. The ends are fitted with small threaded chucks which take phonograph-needle test tips. The needles can be inserted with either the blunt or sharp points outward.


The handles are colored red and black, one of each, and carry 45-inch long kinkless, flexible leads with molded right-angle phone tip plugs.

SUBMINIATURE TRANSFORMERS

D & R, Ltd., Santa Barbara, California, manufacturer of radio and electronic equipment, has introduced a subminiaturized supply transformer which features high performance characteristics considering its size and weight.

Produced on special order to meet individual requirements and specifications, these compact transformers are capable of withstanding severe shock, temperature variations, and vibration.

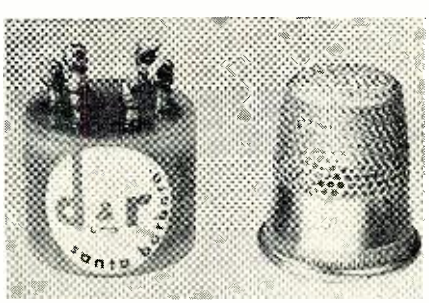The company's Model DR-T 107, for example, has been developed primarily for printed circuit applications. It delivers up to 5 watts at 400 cps and is



designed to feed a pair of synchro control transformers. It weighs ⅔ ounce and measures ⅝" high and ¾" in diameter.

MULTIPLIER PHOTOTUBE

The Tube Department of *Radio Corporation of America,* Harrison, N.J. is now offering a new multiplier phototube for headlight-control service, the *RCA*-6328.


This short multiplier phototube of the 9-stage type has instantaneous response, meeting the critical timing requirements of headlight-control service. It is capable of providing stable performance over long periods of time. Its high luminous sensitivity allows use of an amplifier with relatively low-impedance input and fewer stages than required by less-sensitive tubes.

The low electrode dark current of the 6328 makes feasible the use of high-resistance voltage-divider networks to minimize power requirements and to improve not only operating stability but tube life. A technical bulletin on this tube is available on request.

AUDIO OSCILLATOR

The *Clough-Brengle Co.,* Dept. RE, 6014 Broadway, Chicago 40, Ill. is now offering an extended-range audio oscillator, the Model 411.

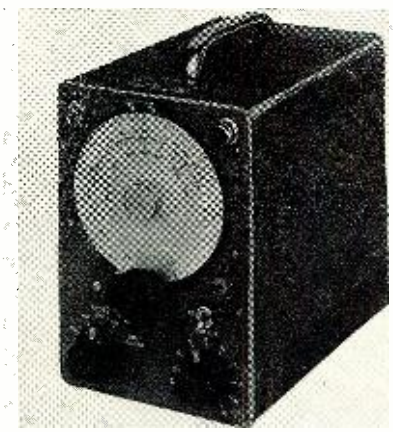This instrument is suitable for making measurements requiring a sine-wave signal over the range from 20 cycles to 1 megacycle. A resistance-capacity tuned type oscillator and a cathode follower in the output system



are employed to provide uniform response. Frequency accuracy is maintained by the use of deposited carbon resistors in the frequency-determining network.

Low-level measurements are facilitated by a panel switch which reduces output voltage, distortion, and hum output. Other features include good case ventilation, a well spread dial calibration for easy reading, and compact size.

NEW CRYSTAL

The James Knights Company, Sandwich, Illinois has introduced a new crystal in its G-9 series, available with flexure mode crystals from 4 to 80 kc.

The new crystal provides rugged, precise frequency control at temperatures in the −40 to +70 degree C. range. The crystals have a high ratio of capacities (C_0/C) resulting in a high degree of isolation from associated circuitry.

This new unit provides a practical means of close frequency control in a range not covered by any other single type of crystal. The crystals are hermetically-sealed in an evacuated glass holder for maximum protection and freedom from contamination.


ANTENNA COILS

Master Mobile Mounts, Inc., 1306 Bond Street, Los Angeles 36, California is now offering a new line of *"Hy-Q"* antenna coils which are precision-engineered to deliver the highest possible *"Q"* consistent with good design.


These antenna coils, which are

www.americanradiohistory.com


now!

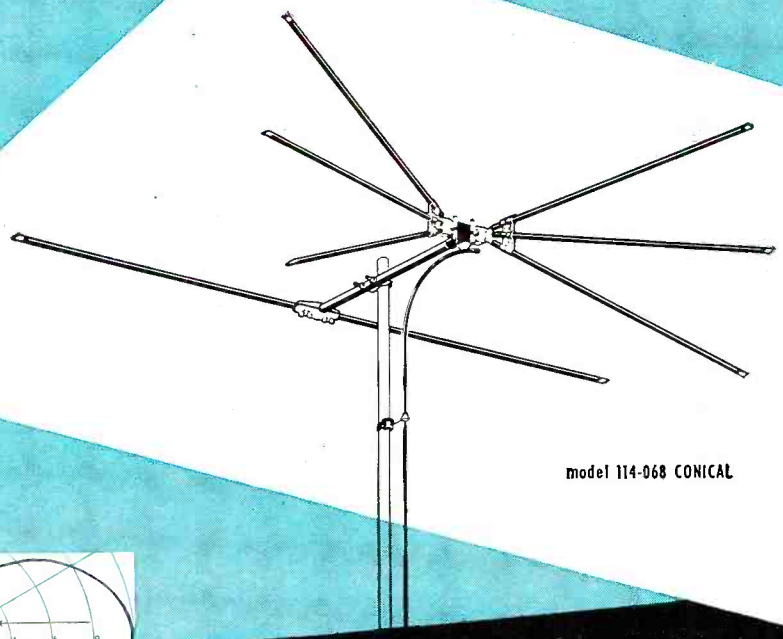

model 114-068 CONICAL

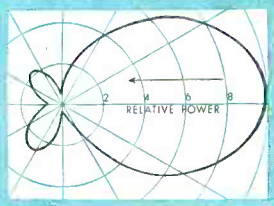

69 mc—channel 4

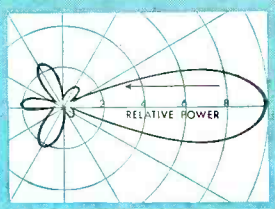

195 mc—channel 10

Directivity patterns of the CONICAL are exceptionally clean. The strong major lobe indicates fine directivity.


a VHF CONICAL antenna built to the Quality Standards of AMPHENOL


Now ready to join the fastest-growing and fastest-selling antenna line in the United States is a new AMPHENOL VHF antenna. Designed to supplement the fabulous INLINE* for VHF reception, the new CONICAL antenna will give true-picture reception in *every VHF signal area*: major, fringe and long-distance. Gain and directivity have been engineered to the high AMPHENOL standards that have set the quality goal for the entire industry; craftsmanship attention to the small but important details make the CONICAL another example of AMPHENOL's fine antenna work.

AMPHENOL CONICALs are available in single, two and four bay models. The stacked models use unique phasing harnesses for extra gain. The CONICAL may be obtained in packaging that contains all the necessary stacking equipment or else the individual antenna may be purchased one or two to a carton. In addition, the single bay CONICAL is available in a complete antenna installation kit.

All elements of the CONICAL are constructed of sturdy, long-lasting seamless aluminum tubing — assuring rust-free years of top performance.

*Reissue U. S. Patent 23,273

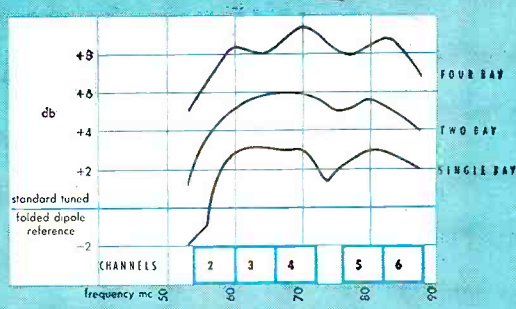

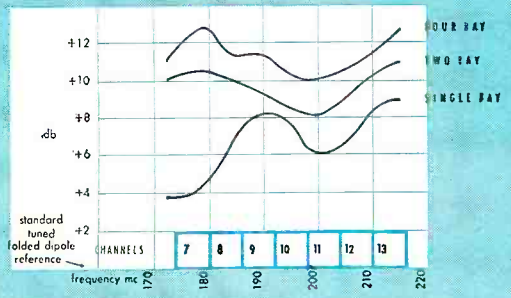

High gain of the CONICAL is illustrated in the gain charts for single, two bay and four bay models. Measured in accordance with proposed RETMA standards, the charts also show the desirable flatness of the gain.

AMPHENOL

AMERICAN PHENOLIC CORPORATION • *chicago 50, illinois*

www.americanradiohistory.com

CONCORD PROUDLY FEATURES


precise

KIT AND WIRED

INSTRUMENTS

NOW IN STOCK

EXCLUSIVE... precise

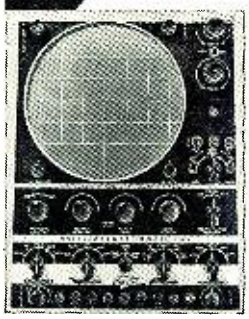

MODEL #308

8½" SCOPE

KIT $129.50

#308W $229.50

No other oscilloscope, at any price, can meet all the specifications of this electronic masterpiece.

- VERTICAL FREQ. RESPONSE—Flat ± 1½ db DC thru 5 MC.
- SENSITIVITY — Greater than 10 millivolts push-pull (3.9 Millivolts/CM)
- BLANKING—60 cycle or 120 cycle Blanking through Blanking amplifier circuit.
- SWEEP RATE—Linear sweeps from 1 cycle to 80 KC in 5 ranges. (1-10 uses Ext. C.) DRIVEN and RECURRENT sweeps.
- MAGNIFIER—Expands and magnifies signal up to 10 times.
- PUSH-PULL—Output in both amplifiers.
- CRT — The latest type 8½" NEW tube a PRECISE EXCLUSIVE.
- VOLTAGE REGULATED.
- ANODE INTENSIFIER—a PRECISE FIRST.
- INTERNAL CALIBRATOR

NEW 7" OSCILLOSCOPE

MODEL #300K.....$94.95

MODEL #300W.....$199.50

LOWEST PRICED IN ITS FIELD

NEW MODEL #909

VACUUM TUBE VOLTMETER

FACTORY WIRED $37.50



Model 909 Vacuum Tube Voltmeter. 1% Ceramic precision Resistors; Coax DC connector; FM zero alignment scale; burn-out proof circuit; DC input 25 Meg. Rugged oversize 4½" meter.

MODEL #909 KIT... $25.98



FREE! A complete, comprehensive listing of all your electronic requirements. Bursting with those SPECIAL VALUES FROM CONCORD

☐ Send me at once your new 1954 catalog. Send complete information and technical data on NEW PRECISE Models

☐ #308 ☐ #300 ☐ #909

☐ Please send PRECISE Model .....

Enclosed find $..... 20% deposit with C.O.D. required. Pre-paid if remittance in full.

Name .....


Street .....

City.....STATE.....

Concord Radio

53 Vesey Street. New York 7, N. Y.

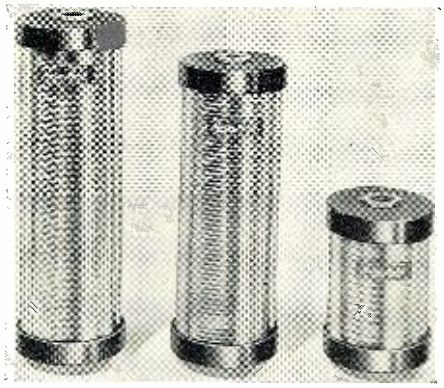available for 20, 40, and 75 meter operation, incorporate several unusual features. They are compactly designed,



rugged, and lightweight. They have a special coated air-spaced coil winding to insure improved transmission and reception quality.

The 20-meter coil measures 3½" x 2⅜" in diameter and weighs 7½ ounces, the 40-meter unit measures 6½" x 2⅜" in diameter and weighs 11 ounces, while the 75-meter coil measures 7½" x 2⅜" in diameter and weighs 12 ounces.

SMALL TRANSISTORS

Texas Instruments Incorporated has announced a size reduction in its junction transistor cases for even greater usefulness in miniature equipment.

The over-all length of the case has been reduced from .500 to .300 inch. Connections are made to the transistor case through three leads, supplied already tinned and 1½ inches long, suitable for soldering into the circuit or clipping to desired length and plugging into a subminiature socket.

Three types of these "n-p-n" tran-

(*Continued on page* 166)

NEW TV STATIONS ON THE AIR

(As of January 25, 1954)


The following new stations bring the list published in the January, 1954 issue up to date.

STATE, CITY	STATION	CHANNEL	FREQUENCY RANGE (IN MC.)	VIDEO WAVELENGTH (IN FT.)	VIDEO POWER* (IN KW.)
Arkansas					
Pine Bluff	KATV	7	174-180	5.61	24.5
California					
Stockton	KTVU	36	602-608	1.63	525
Colorado					
Denver	KOA-TV	4	66-72	14.61	100
Florida					
Fort Lauderdale	WITV	17	488-494	2.01	43
Idaho					
Idaho Falls	KID-TV	3	60-66	16.06	100
Illinois					
Bloomington	WBLN	15	476-482	2.06	16
Danville	WDAN-TV	24	530-536	1.85	1
Indiana					
Princeton	WRAY-TV	52	698-704	1.41	95
Iowa					
Waterloo	KWWL-TV	7	174-180	5.61	30
Kansas					
Pittsburgh	KOAM-TV	7	174-180	5.61	98
Louisiana					
Shreveport	KSLA	12	204-210	4.79	13
Maine					
Lewiston	WLAM-TV	17	488-494	2.01	1
Portland	WCSH-TV	6	82-88	11.8	100
Massachusetts					
Adams-Pittsfield	WMGT	74	830-836	1.18	300
Mississippi					
Jackson	WJDT	3	60-66	16.06	15.9
Missouri					
Columbia	KOMU-TV	8	180-186	5.43	60
Festus-St. Louis	KACY	14	470-476	2.09	500
Nebraska					
Kearney-Holdrege	KHOL-TV	13	210-216	4.65	56.2
New Jersey					
Asbury Park	WRTV	58	734-740	1.34	100
North Dakota					
Bismarck	KFYR-TV	5	76-82	12.74	100
Oklahoma					
Oklahoma City	KWTV	9	186-192	5.25	55
Pennsylvania					
Scranton	WARM-TV	16	482-488	2.04	252
South Carolina					
Greenville	WFBC-TV	4	66-72	14.61	100
Texas					
Midland	KMID-TV	2	54-60	17.8	26.3
Weslaco	KRGV-TV	5	76-82	12.74	28.8
Washington					
Seattle	KOMO-TV	4	66-72	14.61	100
West Virginia					
Fairmont	WJPB-TV	35	596-602	1.65	20
Wisconsin					
Eau Claire	WEAU-TV	13	210-216	4.65	52
Neenah	WNAM-TV	42	638-644	1.54	15.5

*From Station CP application. The frequency of the video carrier = 1.25 + channel lower freq. limit. Total number of television stations now on the air: 351 (123 of which are u.h.f.)

www.americanradiohistory.com


Burton browne advertising

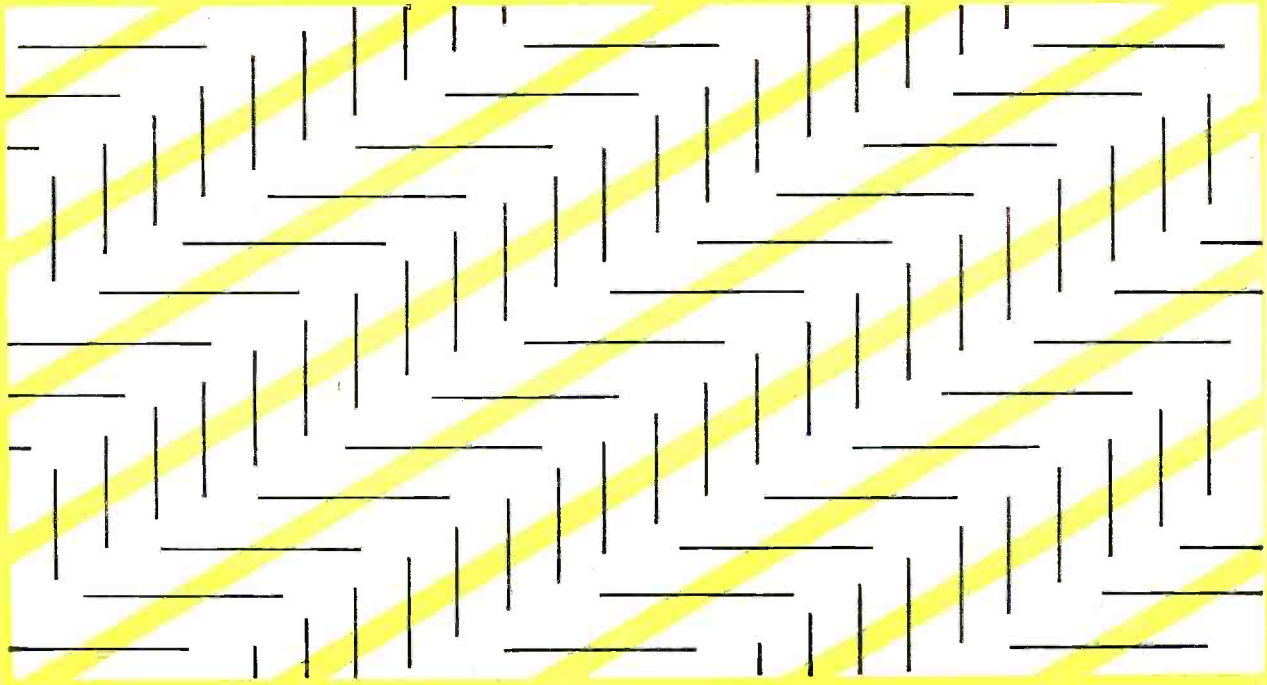


THINGS ARE NOT AS THEY SEEM...

The long lines are strictly parallel—
that they appear otherwise is an optical illusion.

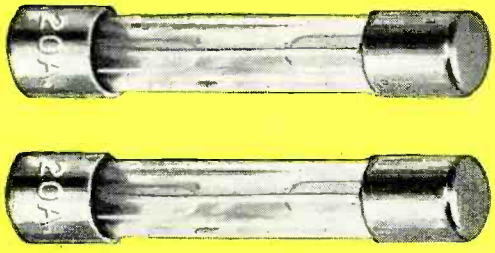This fuse merely has the metal caps cemented to the glass.



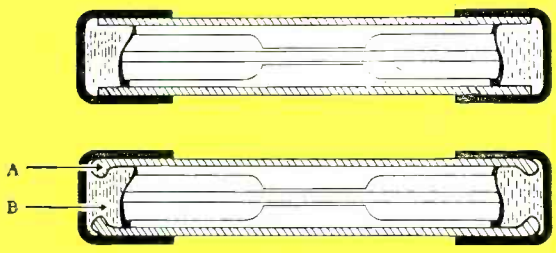The difference between these two fuses is no illusion . . .



This Littelfuse has the caps locked to glass like this.

The ends of the glass are formed[A]. The solder which is bonded in a separate operation to the cap reflows through the small aperture and spreads out to form a permanent collar-button lock[B] between cap and glass—impervious to moisture and vibration. The exclusive Littelfuse feature eliminates fuse failure due to loose caps.

Littelfuse leads all other fuse manufacturers in design patents on fuses. ***Lock-cap assembly patent no. 1922642***

L TTELFUSE

DES PLAINES. ILLINOIS


www.americanradiohistory.com

KAY-TOWNES Announces

the new Super "KATYS"

(PATENTS PENDING)

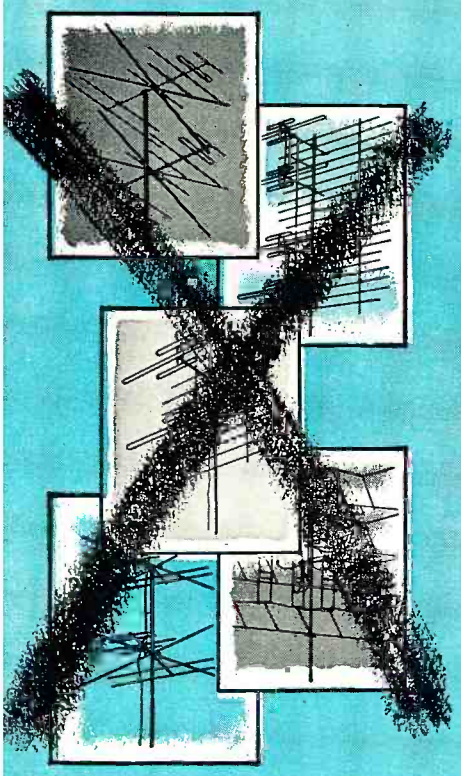Highest Gain ALL-CHANNEL VHF ANTENNAS EVER DESIGNED!



GUARANTEED

TO *OUT-PERFORM* ANY OTHER ALL-CHANNEL VHF ANTENNA ON THE MARKET

Practically every TV Antenna maker in America has made just such statements as these . . . *but, there is a big difference in making these broad claims and then being able to back them up!*

WE CAN! We are prepared to run a PERFORMANCE TEST with *anyone . . . anywhere . . . anytime* . . . to prove the vast superiority of the new SUPER "KATYS" *over all other all-channel VHF antennas* . . . regardless of manufacture, design, type or number of bays!

IN FACT, WE WILL POSITIVELY AND ABSOLUTELY GUARANTEE THAT OUR SINGLE-BAY SUPER KATY WILL OUTPERFORM ANY VHF 4-BAY ANTENNA MADE TODAY!

Our 2-Bay SUPER KATY is designed for *extremely difficult* reception areas. It has been tested in many practically impossible locations . . . *AND HAS NEVER FAILED TO BRING IN A PICTURE RATED EITHER "VERY GOOD" OR "EXCELLENT"!*



4½ Years IN DEVELOPMENT...


THE AMAZING SUPER KATY DESIGN MAKES OTHER VHF ALL-CHANNEL ANTENNA DESIGNS AS OBSOLETE AS THE HORSE AND BUGGY! WE CHALLENGE YOU TO TEST IT . . . *ANYWHERE!*

Copyright 1953

www.americanradiohistory.com

Super KATY-2

2-BAY

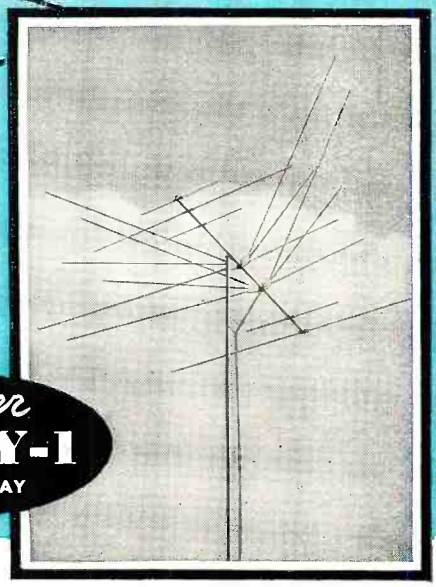

Super KATY-1

SINGLE-BAY

Now THE WORLD'S FINEST ALL-CHANNEL VHF RECEPTION!

The SUPER KATY all-channel VHF antennas feature a twin-driven aray with a combination of special cut elements for a close 300 OHM impedance across the entire VHF Band. This feature in conjunction with the long, accumulative fan dipoles, with directors and reflectors properly cut and spaced, results in performance never before obtained by any antenna design . . . *including our own "BIG JACK", whose design has been so widely "hijacked".*

Actual tests show that the Single-Bay KATY-1 will outperform any 10-element Yagi on every channel, 7 through 13 . . . and will perform as well as any 10-element Yagi on every channel, 2 through 6.

	List Price
SUPER KATY-1 Single-Bay	$25.00
SUPER KATY-2 2-Bay	$50.00

K-T Antennas are sold through selected distributors only . . . write for name of your nearest jobber.

KAY-TOWNES

ANTENNA COMPANY

ROME, GEORGIA

Recognized leaders in the field of fringe area antenna design


www.americanradiohistory.com

the **630**

IS STILL THE FINEST TV CHASSIS EVER DESIGNED

...and there is no finer 630 chassis than the **GOLD MEDAL**

by **TECH-MASTER**

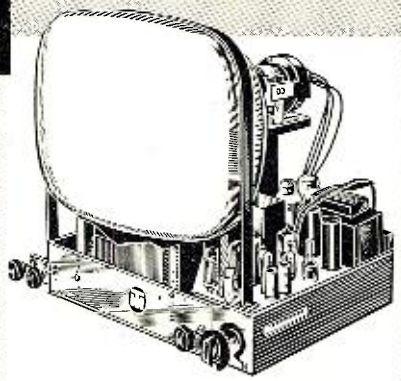

There is a Tech-Master Custom-Designed, custom-built TV Chassis for every requirement where quality and reliability are the predominant factors.

MODEL 2430: For picture tubes up to 24". Audio connection for optional use of external amplifier
Net Price.....(Less Kine).....$189.50

MODEL 2431P: Same as 2430, but with true fidelity Push-Pull audio amplifier.
Net Price.....(Less Kine).....$199.50


MODEL 2439: For new 90° kinescopes. (24" rectangular, 27" and 30")
Net Price.....(Less Kine).....$262.50

Write for Detailed Data

TECH-MASTER PRODUCTS CO.
445 BROADWAY, NEW YORK 13, N. Y.

TECH-MASTER TV Chassis
TECH-MASTER TV Kits
TECH-MASTER Audio Equipment

South River
★★NEWS★★

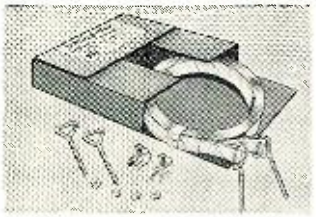

NOW! Banding Kits NEW! for EXTRA LARGE CHIMNEYS

KIT XL "ST": (Consists of)
2—18' x 3/4" STAINLESS STEEL STRAPS with eyebolts attached
2—Eyebolts Unattached
4—Nuts to Fit Eyebolts
2—KWIK KLIP Strapping Fasteners

Also available, KIT XL "G", same as above with 18' GALVANIZED STRAPS.

Universal—may be used with any chimney antenna mount.

In Can.: A. T. R. Armstrong Co., Toronto

SOUTH RIVER METAL PRODUCTS CO., INC.
SOUTH RIVER, N. J.

PIONEER AND OUTSTANDING PRODUCER OF FINEST LINE OF ANTENNA MOUNTS

Editors and Engineers
OUTSTANDING RADIO and ELECTRONIC BOOKS

RADIOTELEPHONE LICENSE MANUAL



Now, in one convenient volume, complete study-guide questions with clear, concise answers for preparation for all U.S.A. commercial radiotelephone operator's license examinations.

Book No. E&E-RL1 **$3.75***

WORLD'S EQUIVALENT TUBES (Equivalents Vade Mecum) NEW 10TH EDITION. A guide reference for the possible exchanges or substitutions of radio tubes, indicating direct or near equivalents for both simple and complex cases, with specialized information as to differences, and covering military tubes as well as conventional types.
Book No. E&E-VM10.....$5.00*

WORLD'S RADIO TUBES (Brans' Vade Mecum) 9TH EDITION. Lists over 15,000 tubes from every tube making country. Printed in 16 languages.
Book No. E&E-VM9.....$5.00*

ANTENNA MANUAL. A practical, comprehensive book on antennas, for everyone interested in transmission and reception. Over 300 pages.
Book No. E&E-AM1.....$3.50*

SURPLUS RADIO CONVERSION MANUAL. VOL. 1. Practical conversions. Write for list of contents. *Book No.* E&E-SM1.....$2.50*

SURPLUS RADIO CONVERSION MANUAL. VOL. 2. Companion to Volume 1.
Book No. E&E-SM2.....$2.50*

*Plus any tax.

Send three cent stamp for circular with detailed contents of books listed.

BUY FROM YOUR DISTRIBUTOR
ADD 10% ON DIRECT MAIL ORDERS TO
EDITORS and ENGINEERS, Ltd.
BOX 689A SANTA BARBARA, CALIF.

Tape Editor's Notebook

(*Continued from page* 51)

only the length of about one and a half 78-rpm sides on one EP side. Thus a cut must be made somewhere in the middle of the second 78-rpm side in order to stay within the EP time limit. If there is a pause or long rest in the music at the right time, the cutting is simple. But when this fortunate coincidence doesn't occur, then it is necessary to cut into continuous music and the echo chamber must be brought into play. The tape is cut at a point which is most feasible musically as well as technically, and several seconds of blank tape is spliced between the ends. The ending is then re-recorded and reverberation faded in as before.

The characteristics of tape have made the medium itself very adaptable to methods of simulating reverberation. A commercially-available unit, designed by Lewis Goodfriend, comprises a continuous loop of tape moving past a record and several reproduce heads, whose outputs can be adjusted to give the effect of various degrees of multiple reflections. Such a unit is illustrated in Fig. 1. An approximation of this effect is possible with any tape recorder having separate record and playback heads. If a small portion of the recorder output is fed back into the input, it will be recorded again, a fraction of a second behind the original, and then the combination will be recorded again, the entire process being repeated continuously until the system losses cause the sound to decay to inaudibility. As in the case of the reverberation chamber, it is advisable to insert a variable equalizer in the feedback loop, so that the quality of reverberation may be controlled. The delay time will be dependent upon the rate of speed at which the tape travels and the distance between the playback and record heads. On most commercial machines, 15 inches-per-second seems to be the best speed for usual applications, but the other speeds are often useful for special effects.

Thus we have seen a few of the tremendous advances in technique which have been made in the recording art in the few short years since the introduction of tape. At the present rate, who can possibly foresee what wonders the future holds? —30—



"Rex, here Rex. Junior's on the TV quiz program!"

www.americanradiohistory.com



J. E. SMITH
President
National Radio
Institute
Washington, D.C.
40 years of success
training men at
home in spare time.

I Will Train You at Home
for Good Pay Jobs, Success in
RADIO-TELEVISION






Practice Broadcasting with Equipment I Send



As part of my Communications Course I send you kits of parts to build the low-power Broadcasting Transmitter shown at the left. You use it to get practical experience putting a station "on the air," performing procedures demanded of Broadcasting Station Operators. An FCC Commercial Operator's License can be your ticket to a better job and a bright future; my Communications Course gives you the training you need to get your license. Mail card below and see in my book other valuable equipment you build.

Practice Servicing with Equipment I Send

Nothing takes the place of PRACTICAL EXPERIENCE. That's why NRI training is based on LEARNING BY DOING. You use parts I furnish to build many circuits common to Radio and Television. With my Servicing Course you build a modern Radio (shown at right). You build a Multitester which you use to help fix sets while training. Many students make $10, $15 a week extra fixing sets in spare time starting a few months after enrolling. All equipment is yours to keep. Card below will bring book showing other equipment you build.

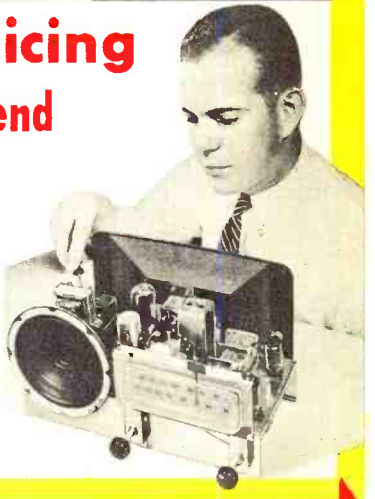



Television is Growing Fast
Making New Jobs, Prosperity

More than 25 million homes now have Television sets and thousands more are being sold every week. Well trained men are needed to make, install, service TV sets. About 200 television stations on the air with hundreds more being built. Think of the good job opportunities here for qualified technicians, operators, etc. If you're looking for opportunity get started now learning Radio-Television at home in spare time. Cut out and mail postage free card. J. E. Smith, President, National Radio Institute, Washington, D. C. OUR 40TH YEAR.

AVAILABLE TO VETERANS UNDER G.I. BILL

Good Jobs, Good Pay, Success in Radio-TV! *SEE OTHER SIDE*

CUT OUT AND MAIL THIS CARD NOW

Sample Lesson & 64-Page Book
Both FREE

This card entitles you to Actual Lesson on Servicing, shows how you learn Radio-Television at home. You'll also receive my 64-Page Book, "How to Be a Success in Radio-Television." Mail card now!

NO STAMP NEEDED! WE PAY POSTAGE

Mr. J. E. SMITH, President,
National Radio Institute, Washington 9, D.C.


Mail me Lesson and Book, "How to Be a Success in Radio-Television." (No Salesman will call. Please write plainly.)

NAME.....AGE.....

ADDRESS.....

CITY.....ZONE....STATE.....

VETS write in date of discharge.....
B C

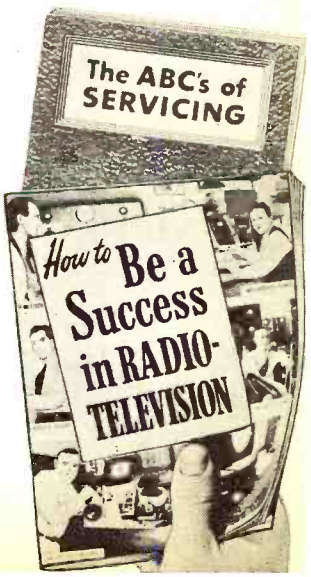

www.americanradiohistory.com

Train at Home to Jump Your Pay as a RADIO-TV Technician

Get a Better Job—Be Ready for a Brighter Future in America's Fast Growing Industry

Training PLUS opportunity is the PERFECT COMBINATION for job security, good pay, advancement. When times are good, the trained man makes the BETTER PAY, GETS PROMOTED. When jobs are scarce, the trained man enjoys GREATER SECURITY. NRI training can help assure you and your family more of the better things of life.

Radio-Television is today's opportunity field. Even without Television, Radio is bigger than ever before. Over 3,000 Radio Broadcasting Stations on the air; more than 115 million home and Automobile Radios are in use. Then add Television. Television Broadcast Stations extend from coast to coast now with over 25 million Television sets already in use. There are channels for 1,800 more Television Stations. Use of Aviation and Police Radio, Micro-Wave Relay, Two-way Radio communication for buses, taxis, trucks, etc. is expanding. New uses for Radio-Television principles coming in Industry, Government, Communications and Homes.

N I Training Leads to Jobs Like These

BROADCASTING
Chief Technician
Chief Operator
Power Monitor
Recording Operator
Remote Control Operator

SERVICING
Home and Auto Radios
P. A. Systems
Television Receivers
Electronic Controls
FM Radios

IN RADIO PLANTS
Design Assistant
Transmitter Design Technician
Service Manager
Tester
Serviceman
Research Assistant

SHIP AND HARBOR RADIO
Chief Operator
Assistant Operator
Radiotelephone Operator

GOVERNMENT RADIO
Operator in Army, Navy, Marine Corps, Coast Guard
Forestry Service Dispatcher
Airways Radio Operator

AVIATION RADIO
Plane Radio Operator
Transmitter Technician
Receiver Technician
Airport Transmitter Operator

TELEVISION
Pick-up Operator
Voice Transmitter Operator
Television Technician
Remote Control Operator
Service and Maintenance Technician

POLICE RADIO
Transmitter Operator
Receiver Serviceman

My Training is Up-to-Date You Learn by Practicing

Get the benefit of my 40 years experience training men. My well-illustrated lessons give you the basic principles you must have to assure continued success. Skillfully developed kits of parts I furnish "bring to life" the principles you learn from my lessons. Read more about equipment you get on other side of this page.

Naturally, my training includes Television. I have, over the years, added more and more Television information to my courses. The equipment I furnish students gives experience on circuits common to BOTH Radio and Television.

Find Out About the Tested Way to Better Pay

Read at the right how just a few of my students made out who acted to get the better things of life. Read how NRI students earn $10, $15 a week extra fixing Radios in spare time starting soon after enrolling. Read how my graduates start their own businesses. Then take the next step—mail card below.

You take absolutely no risk. I even pay postage. I want to put an Actual Lesson in your hands to prove NRI home training is practical, thorough. I want you to see my 64-page book, "How to Be a Success in Radio-Television" because it tells you about my 40 years of training men and important facts about present and future Radio-Television job opportunities. You can take NRI training for as little as $5 a month. Many graduates make more than the total cost of my training in two weeks. Mailing postage free card can be an important step in making your future successful. J. E. Smith, President, National Radio Institute, Washington 9, D. C. OUR 40TH YEAR.



J. E. Smith, *President*
National Radio Institute

The men whose messages are published below were not born successful. Not so long ago they were doing exactly as you are now . . . reading my ad! They decided they should KNOW MORE . . . so they could EARN MORE . . . so they acted! Mail card below now.

I TRAINED THESE MEN



Handicapped but Successful
"I am now Chief Engineer at WHAW. My left hand is off at the wrist. A man can do . . . if he wants to." R. J. Bailey, Weston, W. Va.



$10 a Week In Spare Time
"Before finishing, I earned as much as $10 a week in Radio servicing, in my spare time. I recommend NRI". S. J. Petruff, Miami, Fla.



Control Operator, Station WEAN
"I received my license and worked on ships. Now with WEAN as control operator. NRI course is complete." R. Arnold, Rumford, R. I.



Has Own Radio-Television Shop
"Doing Radio and Television servicing full time. Have my own shop. I owe my success to NRI." Curtis Stath, Fort Madison, Iowa.




Has Growing Business
"Am becoming expert Teletrician as well as Radiotrician. Without your course this would be impossible." P. Brogan, Louisville, Ky.



Got First Job Thru NRI
"My first job was with KDLR. Now Chief Engr. of Radio Equipment for Police and Fire Dept." T. Norton, Hamilton, Ohio.

Find Out What RADIO-TV Offers You

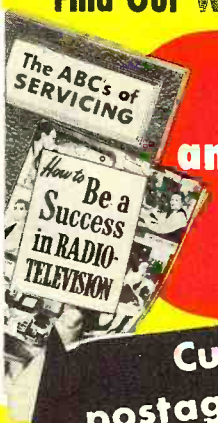

SAMPLE LESSON and 64-PAGE BOOK Both FREE

Cut out and mail postage-free card today!

FIRST CLASS
Permit No. 20-R
(Sec. 34.9, P.L. & R.)
Washington, D.C.

BUSINESS REPLY CARD
No Postage Stamp Necessary If Mailed In The United States

POSTAGE WILL BE PAID BY
NATIONAL RADIO INSTITUTE
16th and U Sts., N.W.
Washington 9, D. C.

Start Soon to Make $10, $15 a Week Extra Fixing Sets



Keep your job while training. Many NRI students make $10, $15 and more a week extra fixing neighbors' Radios in spare time starting a few months after enrolling. I start sending you special booklets that show you how to fix sets the day you enroll. The multitester you build with parts I furnish helps discover and correct troubles.

Do You Want Your Own Business?



Many NRI trained men start their own successful Radio-Television sales and service business with capital earned fixing Radios in spare time. My book tells how you can be your own boss. Joe Travers, a graduate of mine, in Asbury Park, N.J., writes: "I've come a long way in Radio and Television since graduating. Have my own business on Main Street."

www.americanradiohistory.com

International Short-Wave

(*Continued from page 78*)

0700 - 0800, 1200 - 1700; Middle East Service 0800 - 0830, 1000 - 1200, same channels. (Bluman, Israel, via Radio Sweden)

El Salvador—Radio Nacional 9.55A, is noted in Spanish to 2300 closedown. (Bush, Chile; Zerosh, Pa.)

Fiji Islands — Suva's Post Office transmitter is now on 4.880. (Fox, N. Z., via Radio Australia) Station officials inform Scheiner, N. J., that it looks like they will settle down on ZJV3, 3.980, and ZJV, 930 kc., with ZJV3 serving outlying islands with 500 watts while ZJV will serve the main island of Viti Levu with 2 kw.; hours of transmission are 1400-1600, 1900-2100, 0030-0530, mostly in *English* although some vernacular programs are given in Fijian and Hindi.

Finland—Helsinki, 15.19, noted signing on 0640; has *English* 0700 weekdays *only*. (Pearce, England) News for North America is heard 1430-1445, good level in N. Y. (Steinberg)

France — Paris, 7.105, noted 1400-1500 in Czech, Slovak; bad QRM. (Zerosh, Pa.) Heard on 9.765 in Portuguese 1410 tune-in. (Bellington, N. Y.) Noted opening 0230 with "La Marseillaise" in beam to New Caledonia in French. (Takemi, Japan) Is good level on 11.70, 9.685 at 1800-1815; strong on 15.35 to Canada 1030-1045. (Sawyer, Ont.)

French Equatorial Africa — Radio Brazzaville noted on 15.595 at 1400, good level in French; left air *abruptly* 1409. (Ferguson, N. C.) Heard with news 1745 on 9.44. (McGrath, Iowa, Parson, Va.) And on 11.970. (Kroll, N. Y.; Granrose, Fla.; Frazier, Texas) With *English* 1550 on 11.97. (Hall, Que.)


French Guiana — Radio Cayenne, 6.210A, seems to be on the air *irregularly,* around 1745 - 1830 closedown. (Kary, Va.)

French Morocco—Rabat, 6.006, noted 1745 with Arabic vocal music; closed with "La Marseillaise" 1759. (Pearce, England)

French West Africa — Radio Dakar, 9.560, noted with French identification 1500. (Ferguson, N. C.) Good level 0300 with news in French. (Sawyer, Ont.)

Germany—American Committee for Liberation from Bolshevism, Inc., Munich, sent letter verification for reports on 7.130, 6.175 outlets; asked for further reports "regarding jamming noises," and said presently uses 6.055, 6.175, 7.130, 9.585, 11.720, 11.785. Heard on 6.055 at 0155 at good level in Russian dialects; 6.175 noted parallel 0200. (Pearce, England) *Sudwestfunk,* 6.320, noted from 1845-2000 closedown on *Sat.,* may close earlier other days; mostly music. (Huttemeyer, N. J.) RIAS, 6.005, Berlin, heard with dance music 2035. (Cox, Dela.)

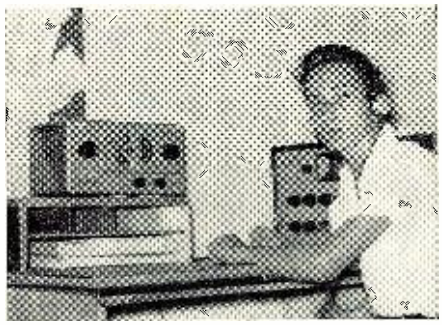Gold Coast—Accra, 4.915, noted 1240 with recordings; 1245 call in *English,* then news, weather forecast; closed



John Jerry Bartko, Masaryktown (Brooksville), Florida, 15-year-old sophomore at Hernando High School, won the top Class A prize in the first radio listening contest sponsored by "Boys' Life," national Boy Scout journal, and a Hallicrafters HT-20 transmitter. During the contest months of January-February 1953, young Bartko spent 400 hours at the controls and logged 4000 stations. He totaled 7145 points. All continents, all states, and all call areas, plus 105 countries, were logged.

1300; weak with CWQRM. (Pearce, England)

Greece — Armed Forces Station, 7.420A, is heard to 1700A sign-off, also from around 0030 *past* 0200; on *Sun.* has Orthodox religious service 0100 to *past* 0200. (Kary, Va.)

Greenland — Radio Angmagssalik sent letter verification; said operates on 7.570 as a part of the local Greenlandic News Service on 5.700 and 1500 kc., primarily for Danish and Greenlandic listeners in Greenland; listed power as 2 kw., using a dipole antenna directed SW-NE, 42 meters high, transmitter is suppressor-grid modulated; maintenance of the station—staffed by 16 Danes, 13 Greenlanders—is partly to collect weather observations from all Greenlandic stations, and to relay these to Denmark and to others who might be interested, and partly for local telegraph service *via Lynfby Radio,* Copenhagen, as well as serving as a common coast station for civil navigation; 1 kw. telegraphy-telephony transmitters are used on 500 kc., 2500; schedule for 7.570 and 1500 kc. is weekdays 0900-0950. (Pearce, England)

Guatemala — TGWA, 9.760, noted back on air around 1330. (Zerosh, Pa.) Heard 2130 tune-in. (Bellington, N. Y.) TGNB, 9.668, noted daily 2200-2345 closedown in *English,* fair to good level. (Brown, Wyo.)

Haiti—Radio Commerce noted *moved* to 6.090 from 6.140, good level to 2300 closedown. (Morgan, Balbi, Calif.) 4VEH, 9.69, heard in *English* 0830-0900. (Grace, Conn.) 4VC is good on 9.485 at 0800 in French. (Morrison, R. I.) *Radio Tropices* (formerly *Radio Fides*), 6.405, Port-au-Prince, is usually good level in French 1900, although at times has bad CWQRM. (Niblack, Ind.) 4VRW, 10.074A, noted 1400, an unusual time to hear this one in N. Z. (Collett)

Honduras—HRTL, *Radio Tela,* sent airmail letter verification for 6.035; relays 980 kc., 0900-2300 daily *except* Sun., has American music and songs daily 2120-2200. (Pearce, England; Bellington, N. Y.)

Hong-Kong—ZBW3, 9.525, Victoria,



www.americanradiohistory.com

KESTER



Since the most important single step in Radio-Television Servicing is soldering . . . it's just plain good sense to use the best —KESTER SOLDER . . . Key Name in Solder for More Than 50 Years.

KESTER SOLDER COMPANY
4235 Wrightwood Avenue • Chicago 39, Illinois
Newark 5, New Jersey • Brantford, Canada

SOLDER

GET INTO ONE OF THESE GREATER OPPORTUNITY FIELDS

Electricity or Radio-Television

TRAIN IN THE GREAT SHOPS OF

COYNE OLDEST, BEST EQUIPPED SCHOOL OF ITS KIND IN U. S.

Prepare for your future NOW. Get practical training in TELEVISION — RADIO — ELECTRICITY—ELECTRONICS—all vital in Industry. Prepare now for a better job that *also offers a real future* in the years ahead. Learn on real equipment at Coyne—no advanced education or previous experience needed.

***Approved for Veterans*—finance plan**—enroll now, pay most of tuition later. Part time employment service while training if needed.

FREE BOOK Clip coupon for Big Free Illustrated Book. No salesman will call. Act NOW.

B. W. COOKE President COYNE ELECTRICAL SCHOOL FOUNDED 1899

A TECHNICAL TRADE INSTITUTE CHARTERED NOT FOR PROFIT

500 S. Paulina St., Chicago, Dept. 24-85H

ELECTRICITY • TELEVISION • RADIO • REFRIGERATION • ELECTRONICS

B. W. COOKE, Pres.
COYNE ELECTRICAL School
500 S. Paulina St., Chicago 12, Ill. Dept. 24-85H
Send FREE BOOK and details on:
☐ RADIO-TELEVISION ☐ ELECTRICITY

NAME.....

ADDRESS.....

CITY.....STATE.....



THE *Case* WITH A 1,000 APPLICATIONS

This all-purpose case is ideal for housing meters, controls and switches of all types. Made of heavy molded black plastic. Available with matching phenolic panel. Easy to drill and saw. Available in two sizes; 5-1/4" x 6-7/8" x 2-5/16" 3-3/4" x 6-1/4" x 2"

Ask your Distributor for Waldom's Plastic Case.

WALDOM ELECTRONICS INC.
911 Larrabee St., Chicago 10, Ill.

noted 0615 at good level with music, news. (Sanderson, Australia) Has news daily 0900. (United 49'ers Radio Society)

Hungary — Budapest, 6.248A, noted with *English* from 2300. (Saylor, Va.) And 1930-2000. (Zerosh, Pa.) Announces *English* for North America as 1930-2000, 2300-2330, over 9.833, 7.220, 6.248. (Parrish, Ga.)

India—AIR, Delhi, noted opening to Southeast Asia and Far East 0830 on 9.565, 11.790; at 0945 close said next *English* for Southeast Asia would be 1930 on 9.755, 7.170; heard signing on *English* for Europe 0230 on 17.740, 15.380, closed 0330. (Pearce, Catch, England) Heard on 15.350 at 0245 with classical music; on 11.950A at 1945 with Home Service; on 21.510 at 0235 with news and music in Home Service; on 7.210 at 0715 with weather reports, local and general news; VUM, 7.260, Madras, noted 0600 with musical program and news. (Sanderson, Australia) Heard on 7.155 opening 0700 in Asiatic languages. Closes on 9.750 at 0815 after a program in Kouyu. (Kary, Va.) Opens in French on 3.950 at 1445, also on 7.170; news noted 1030-1045 on 4.760A. (Pearce)

Indo-China (Vietnam) — *Radio France-Asie,* Saigon, noted using 9.750A to Europe again 1035-1130A when closes with "La Marseillaise;" uses French and *English,* with news around 1100A. (Pearce, England; Balbi, Calif., others) Noted on 6.225A with identification in French 1800. (Stark, Texas) Heard on 11.925A with French news, then *English* program 2100; on 6.235A at 0525 with strong signal in French session; on 15.420 at 0405 with *English* program of news, music; on 9.745A at 2330 good level in French news, music. (Sanderson, Australia) Noted with French news 0300 on 6.116A. (Saylor, Va.) *"Voice of Vietnam,"* 9.62, Saigon, is fairly good in Tokyo 0500-0600. (Ishikawa) And with world news in *English* 0940. (Navarro, Philippines)

Israel — Tel Aviv some weeks ago was noted *testing* on 9.745 at 1500 parallel 9.010A and asking for comparison reports on the *experimental* 9.745 channel. (Pearce, England) Noted on 9.010A with news 1515-1530. (Zerosh, Pa.) And with "Voice of Zion" session in *English* 1615-1700 closedown. (Chapman, Pa,; Morrison, R. I.) Was heard earlier *testing* on 7.190 (Pearce)


Italy—Rome, *measured* 6.214, noted opening to Brazil in Portuguese 1915; Spanish 1935; Italian 2000. (Ferguson, N. C.) Heard with news 0400 for Australia on 15.300, 11.800A; asked for reports. (Pearce, England) Noted with news to North America 1920 on 7.29, 9.57. (Crowell, Zerosh, Pa.)

Jamaica — Radio Jamaica, 3.360, is fair level 0600-0715. (Parsons, Va.)

Japan — Sanderson, Australia, reports Far East Network on 3.975A at 0515 with variety program; JOB6, 11.725, at 0400 with news and music, good level; JOB3, 9.695, at 0410 with news.

(*Continued on page* 156)

www.americanradiohistory.com

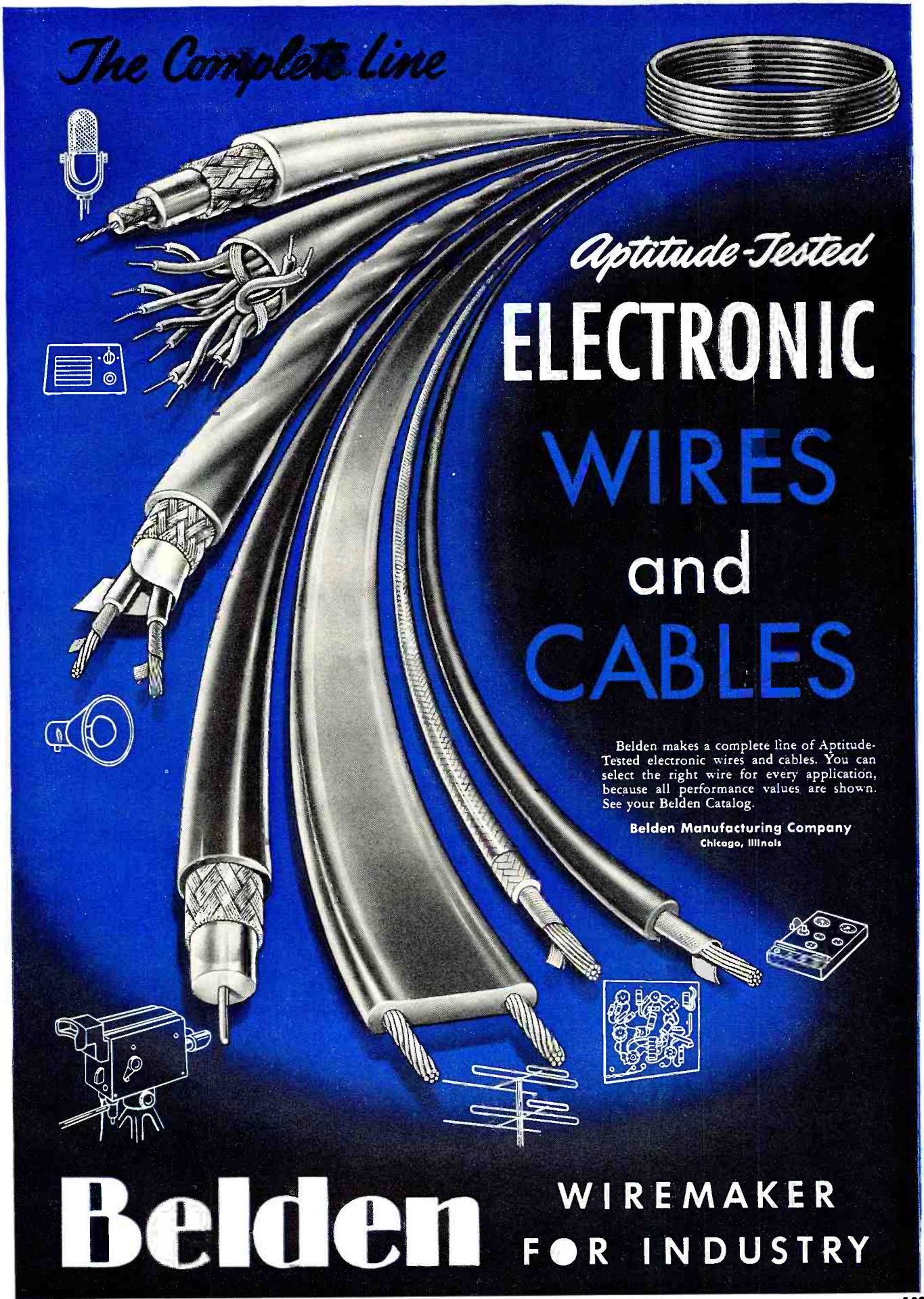

www.americanradiohistory.com



NEW VOLS. 3 & 4

HOWARD W. SAMS'

"DIAL CORD STRINGING GUIDES"

Shows you the ONE right way to string any dial cord in just seconds...

There is only ONE RIGHT WAY to string a radio receiver dial cord, and these are the *only* books that show you how. They cover thousands of receivers, clearly illustrating each dial cord system in a legible diagram that shows you how to solve the knottiest stringing problem in seconds. You'll say goodbye to trouble when you own these invaluable guides—they pay for themselves in the time you save!

VOL. 4. Latest volume includes dial cord stringing diagrams for hundreds of radio and TV-radio receivers produced from mid-1951 through 1953. Includes cumulative index to all 4 volumes. 96 pages. 5½" x 8½".
ORDER DC-4. Only.....$1.00

VOL. 3. Includes dial cord stringing diagrams for radio receivers produced from 1950 through mid-1951, as well as TV-radio receivers produced from 1946 through mid-1951. 96 pages. 5½" x 8½".
ORDER DC-3. Only.....$1.00

VOL. 2. Covers dial cords used in receivers produced from 1947 through 1949. Indexed for quick reference. 96 pages. 5½" x 8½".
ORDER DC-2. Only.....$1.00

VOL. 1. Complete dial cord stringing data for hundreds of receivers produced from 1938 through 1946. 112 pages. 5½" x 8½".
ORDER DC-1. Only.....$1.00

OWN ALL 4—LICK ANY DIAL CORD STRINGING PROBLEM IN SECONDS

HOWARD W. SAMS & CO., INC.

Order from your Parts Jobber today, or write to Howard W. Sams & Co., Inc., 2203 East 46th St., Indianapolis 5, Ind.

My (check) (money order) for $..... enclosed. Send the following books:

☐ DC-4 ($1.00) ☐ DC-2 ($1.00)
☐ DC-3 ($1.00) ☐ DC-1 ($1.00)

Name.....

Address.....

City.....Zone....State.....
(Outside U.S.A. priced slightly higher)

THE TRI-POLE ANTENNA

By

DR. YUEN T. LO

Development Engr., Channel Master Corp.

Explaining the operation of a new TV antenna covering the low and high v.h.f. bands.

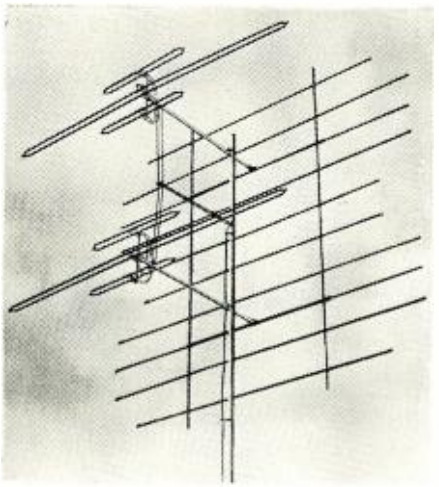


Fig. 1. Two-bay array of the twelve-channel v.h.f. antenna described here.

AMONG antenna manufacturers, there has been a steady trend toward the production of twelve-channel v.h.f. antennas to accommodate the many new TV stations on the air. This article will describe the development of a new type of antenna—the "Tri-pole"—used for TV reception of the entire v.h.f. band. (See Fig. 1.) The design of this antenna is based upon a study of the half-wave dipole antenna.

The current distribution along a half-wave dipole is shown in Fig. 2A. Since the size of the dipole varies inversely with frequency, and since the voltage that a dipole picks up is proportional to its length, a high-band dipole will pick up only about one-third the energy of a low-band dipole. (The frequency ratio of the middle of the high band to the middle of the low band is approximately 3:1.) If we attempt to use a low-band dipole for high-band reception, the current distribution is as shown in Fig. 2C. The dipole is then said to be working on its third harmonic. This current distribution results in the horizontal polar pattern shown in Fig. 2B. The low-band dipole can be considered to be three half-wave, high-band dipoles tied together. The lobe-splitting shown in Fig. 2B is due to the fact that the center dipole is 180° out-of-phase with the two outside dipoles which are in-phase.

The desirable goal would be to have the three dipoles in-phase. A half-wave dipole, having the current distribution shown in Fig. 2A has, by definition, a gain of 0 db. Theoretically, the gain of three half-wave dipoles, side-by-side in-phase, is about 3.2 db. It must always be borne in mind that the same three half-wave, high-band dipoles must also function as one half-wave, low-band dipole.

One of the early attempts to achieve an all-v.h.f. dipole was the so-called "bat wing." Fig. 3 shows the current distribution for both high-band and low-band operation. The dipole structure acts as a half-wave dipole on the low band, but on the high band the "bat wings" form electrical discontinuities in the dipole and effectively isolate the outer third of the dipole on each side. This means that from apex-to-apex of the "bat wings" on the dipole, there is one half-wave on the high band. However, the full length of the antenna is not utilized on the high band.

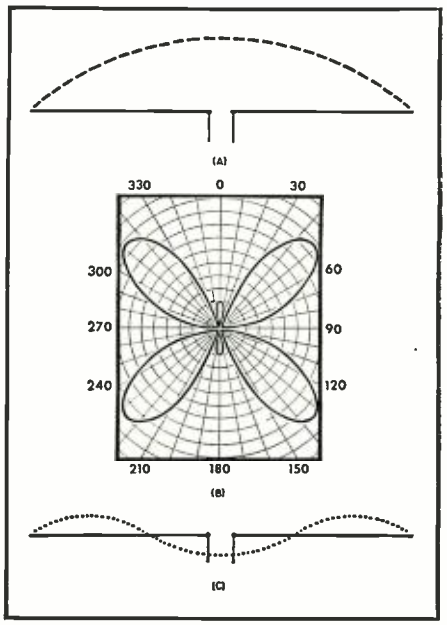


Fig. 2. Current distribution along: (A) a half-wave dipole, and (C) a dipole three half-wavelengths long. (B) Horizontal polar diagram for dipole shown in (C).

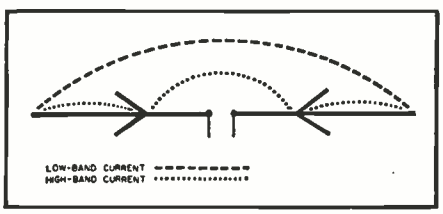


Fig. 3. Low-band and high-band current distribution along a "bat wing" antenna.


Probably the most familiar types of broadband antennas are the conical or fan types. The total length of the elements equals one half-wave on the low band, and three half-waves on the high band. (See Fig. 4.) The current


www.americanradiohistory.com

WARD TELE-VANES

styled for **NEW BEAUTY on the housetops**

INCREASED SALES of TV antennas

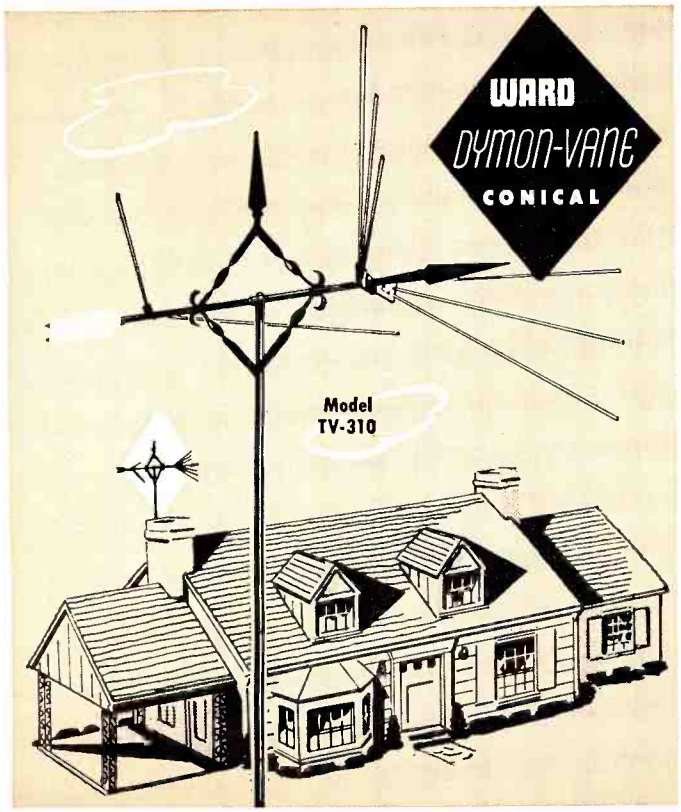

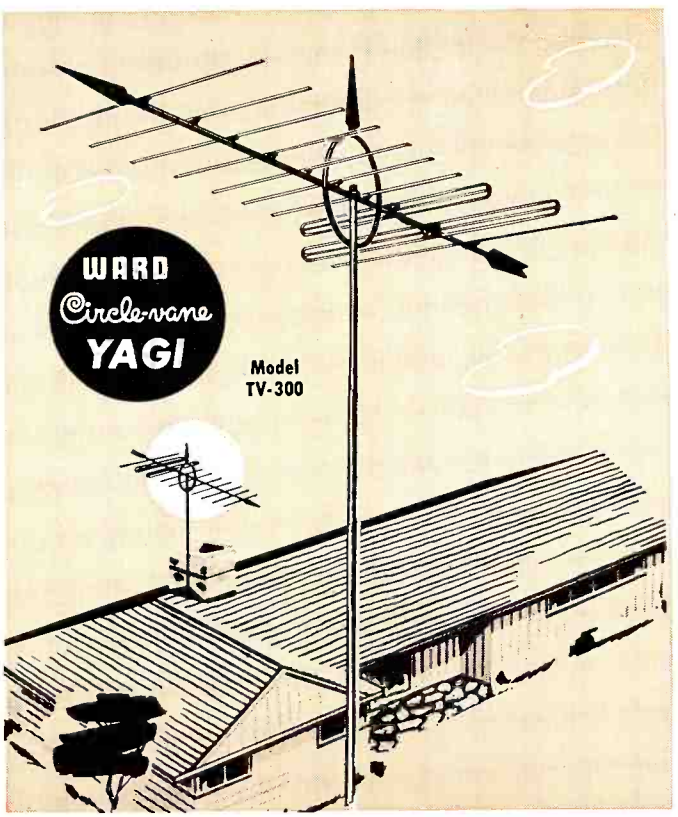

Sell the antennas that are "selling" for you. Ward is promoting their new line of Tele-vane Antennas right to the consumer with national advertisements in:

- The American Home
- Architectural Forum
- Better Homes and Gardens
- Business Week
- House Beautiful
- Popular Mechanics Magazine
- Popular Science Monthly
- Time
- House and Garden Book of Building
- Newsweek

Write today for the giant Tele-vane Sales Kit that gives you the complete schedule plus many, many more selling aids. Tie-in with this gigantic selling campaign for the newest, most revolutionary idea in TV antennas yet.

THE WARD PRODUCTS CORP.

DIVISION OF THE GABRIEL COMPANY


1148 Euclid Avenue, Cleveland 15, Ohio

A GABRIEL PRODUCT

In Canada: Atlas Radio Co., Ltd., Toronto, Ont.

www.americanradiohistory.com

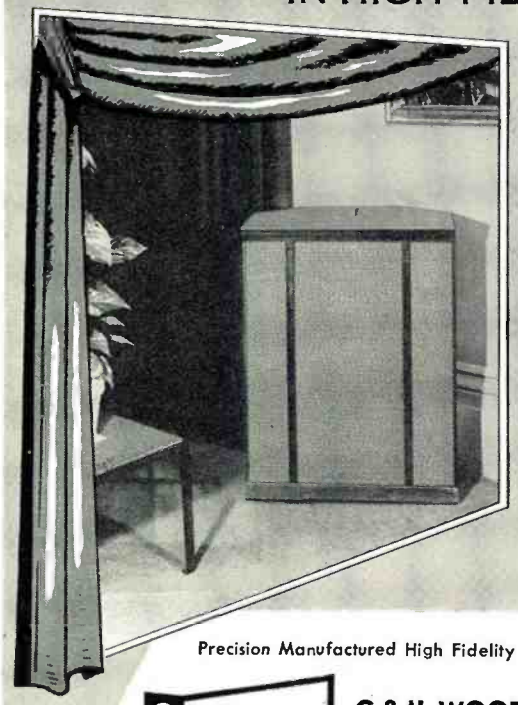FOR THOSE WHO SEEK THE **ULTIMATE** IN HIGH FIDELITY CABINETS



Klipsch REBEL IV by Cabinart

A Klipsch Corner Horn Enclosure designed especially for manufacture by Cabinart.

- Two-way system performance. So flexible in design so as to provide you wide latitude in determining your listening requirements. Removable panel allows for a variety of speaker combinations. For example, in the 12" Klipsch you can install a single 12", two 12" speakers or a tweeter-woofer combination.
- Attractively styled to blend with any interior decor, the Klipsch Rebel IV by Cabinart comes in Limed Oak, Honey Walnut, French Mahogany and Black Lacquer.

"Popularly Priced"

*$69.00 Net for 12" model

*$87.00 Net for 15" model

*Net prices, slightly higher West and South.

Precision Manufactured High Fidelity Cabinets of Character

by Cabinart

G & H WOOD PRODUCTS CO.

75 NORTH 11th STREET, BROOKLYN 11, N.Y.

Pioneers in radio furniture for high fidelity equipment

EARN MORE MONEY— BE A PROFESSIONAL

TELEVISION SERVICE TECHNICIAN



STEP INTO THE TOP PAY $5,000—$10,000 A YEAR CLASS. 7 MONTHS' SHOP TRAINING QUALIFIES YOU.

If you want to reach your goal as a Successful Service Technician you will need plenty of "KNOW HOW" to qualify for the better servicing jobs or profitable shop ownership.

SEND FOR FREE BOOK TODAY!

WESTERN TV offers real experience on live equipment in our BIG SHOPS AND LABORATORIES in the shortest practical time under expert instructors. Graduates are in big demand because they have the "field experience" necessary for immediate "bench" or supervisory positions. You learn every phase of Radio and TV servicing (AM, FM, VHF, UHF). WTI men win fast promotion . . . can demand better pay . . . develop highly profitable businesses of their own with the latest and most PRACTICAL PERSONALIZED TRAINING BEHIND THEM. You concentrate all your time on being a PROFESSIONAL TV SERVICE TECHNICIAN — non-essential math and engineering theory omitted. YOU CAN EARN WHILE YOU LEARN. Special Finance Plan.

APPROVED FOR VETERANS. Find out how you can get into the TOP PAY GROUP — Send for this fact-packed book NOW!

WESTERN TELEVISION INSTITUTE

America's Leading Television Servicing School

Western Television Institute Dept. R-24
341 W. 18th St., Los Angeles 15, Calif.
Without obligation, please send FREE fully illustrated booklet. (No salesman will call.)

NAME_____ AGE_____

ADDRESS_____

CITY_____ ZONE____ STATE_____

STOP

VOLUME CONTROL NOISE!

"NO NOISE"

New 6 oz. Spray Can

Net to Servicemen **$2.25**



CONTAINS AMAZING NEW

PERMA-FILM

★ CLEANS! . . . dirt and oxidation immediately on contact.
★ LUBRICATES! . . . one drop eliminates scratch, hum and noise.
★ PROTECTS! . . . assures continued top performance.

Perfect Contact Restorer—cleans & restores volume controls, band switches, push button assemblies, electrical contacts. NO NOISE is not a carbon tet solution.



"NO NOISE"

2 oz. bottle. Net to Servicemen **$1.00**

Available in 8 oz. bottles and quart cans. Nearest distributor—or write

ELECTRONIC CHEMICAL CORP.

813 Communipaw Ave., Jersey City 4, N. J.

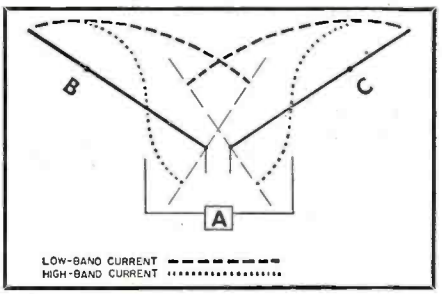



Fig. 4. Current distribution along a conical antenna cut for the low v.h.f. band.

distribution on the high band is the same as for an ordinary low-band dipole, with the outer two sections being out-of-phase with the center section. The normal split-lobe pattern is overcome by tilting the dipole forward from the apex. In this case, points "B" and "C," which are the electrical centers of the outer dipoles, are moved forward in space with respect to point "A," the electrical center of the inner dipole. Therefore, an overlapping of lobes occurs and, in this manner, a significant amount of the cancellation from the center dipole is overcome. However, this pattern still produces side lobes on the high band.

The problem in essence, therefore, is how to get the low-band dipole to act normally on its own band, and as three effective dipoles in-phase on the high band. The approach used in the "Tri-pole" is to reverse the phase of the center dipole during high-band operation. This is shown simplified in Fig. 5A. This configuration effectively produces another high-band, half-wave dipole immediately adjacent to the out-of-phase section in the low-band dipole, when operating on the third harmonic.

It is seen from Fig. 5A that, since dipoles "A" and "D" occupy almost the same point in space with relation to a received signal, they cancel one another, so that high-band operation is achieved through the use of dipoles "B" and "C." However, this approach produces only two half-wave dipoles on the high band. Low-band operation remains unimpaired. The next step,

Fig. 5. Progressive stages in the development of the "Tri-pole" TV antenna.

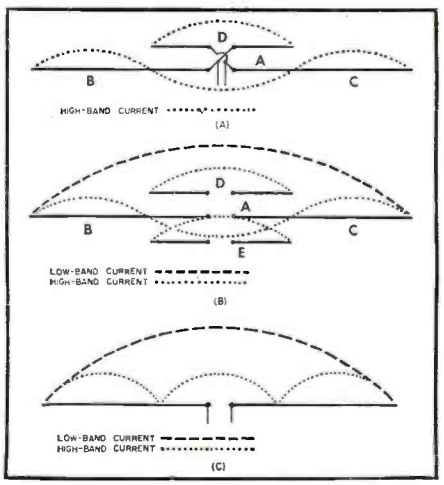

www.americanradiohistory.com

NO ROTORMOTOR YET

ALL DIRECTION UHF-VHF RECEPTION

53 CLAIMS GRANTED IN 5 U. S. PATENTS

#2,585,670
#2,609,503
#2,625,655
#2,644,091
#2,661,423
OTHERS PENDING


MONEY BACK GUARANTEED TO RECEIVE *All* CHANNELS 2-83 FROM *All* DIRECTIONS AND POSITIVELY OUTPERFORM *All* OTHER ANTENNAS WITH OR WITHOUT A ROTORMOTOR

UP TO **10 TIMES MORE POWERFUL THAN ALL OTHER ANTENNAS**

Solves Your Problem in Your Area

Yes, we said YOUR area. With the FCC allocating over 2,000 new TV Stations covering 12 VHF and 70 UHF channels, your area is due to change and you will require an antenna able to receive both UHF and VHF channels from all directions. All Channel Antenna Corp. has just the antenna to fill your needs and money back guaranteed to positively bring you at your location, clearer, sharper, pictures than any combination of present day antennas using expensive rotor motors, boosters, etc. With a flick of the 9 position electronic beam selector switch, any station in any area is instantly brought in on any TV set clearer and sharper.

Guaranteed 60 mi UHF 60 mi VHF

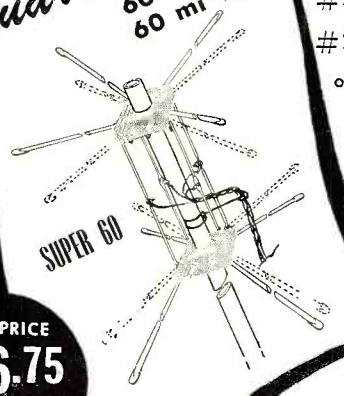

LIST PRICE **$36.75** SEE YOUR JOBBER

The Super 60 is the general purpose model for conditions prevailing in most communities today. Within a short time 15 to 20 UHF-VHF stations will be on the air within a 60 mile radius of every fair sized community. With the installation of the Super 60, you are improving your present reception in all directions and you are ready for the future.


Guaranteed 40 mi UHF 40 mi VHF



LIST PRICE **$24.50** SEE YOUR JOBBER

The Suburban 40 has been developed for suburban areas where the stations are closer and trouble with distance is less of a problem — but the advantage of all direction all channel reception is necessary. A low priced high quality antenna for the present and the future.


Guaranteed 100 mi VHF 30 mi UHF

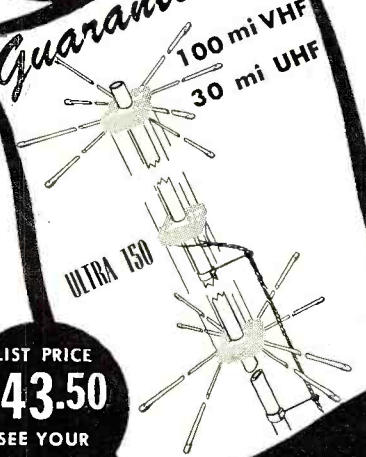

LIST PRICE **$43.50** SEE YOUR JOBBER

Here is the real go-getter of the All Channel family. The Ultra 150 reaches out at long distances on VHF and gives you a bright, clear picture 150 miles and more. This antenna has solved the problem for thousands throughout the country where long range reception was otherwise impossible.

9 POSITION ELECTRONIC ORIENTATION SWITCH

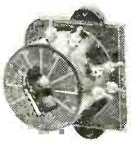


PRICE INCLUDES

Antenna arrays - necessary stacking bars - 9 position switch - switch-to-set coupler - necessary hook-up harness - 7½" stand-offs Individually boxed in mailable carton.

NEW POLYMICALENE

4 CONDUCTOR TRANSMISSION LINE

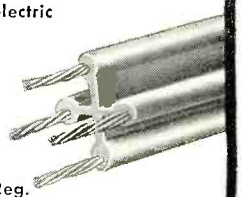- Low Loss External Air Dielectric
- Matched Impedance
- Eliminates End Sealing
- Eliminates Condensation
- Up to 50% Less Loss Than Tubular When Wet
- Easily Spiraled
- No Breaking or Shorting
- Patents Pending - T. M. Reg.



While antenna reception is guaranteed as specified, perfect pictures have been consistantly received from 2 to 3 times these distances.

ALL CHANNEL ANTENNA CORP.

70-07 Queens Blvd., Woodside 77, N. Y. Hickory 6-2304

www.americanradiohistory.com



The new, full line of ERIE rotary selector and lever switches includes twenty-five item numbers. They are made in four styles, in single or multiple sections, shorting and non-shorting types. ERIE switches meet existing R.E.T.M.A. requirements. For protection against the corrosion of heavy silver plated contacts, each switch is sealed in a durable plastic bag and then boxed for convenient stocking.

Descriptive literature is available at your distributors, or write Dept. B for your copy.

ERIE components are stocked by leading electronic distributors everywhere.

ERIE RESISTOR CORP.

ELECTRONICS DISTRIBUTOR DIVISION


ERIE RESISTOR CORPORATION

Main Offices: ERIE, PA.

Factories: ERIE, PA. • LONDON, ENGLAND • TORONTO, CANADA

SUPERIORS
New Model 770-A

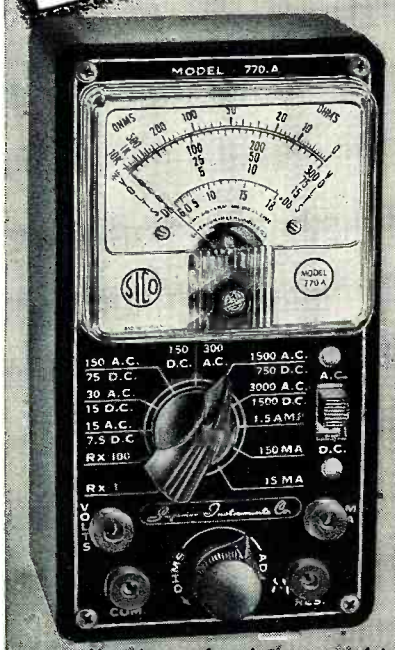The first Pocket-Sized
volt-ohm
milliammeter
using the new
"full-view" meter



71% More Scale Area!

Yes, although our new FULL-VIEW D'Arsonval type meter occupies exactly the same space used by the older standard 2½" Meters, it provides 71% more scale area. As a result, *all* calibrations are printed in large easy-to-read type and for the first time it is now possible to obtain *measurements instead of approximations* on a popular priced pocket-sized V.O.M.

Specifications

6 A.C. VOLTAGE RANGES:
0-15/30/150/300/1500/3000 Volts

6 D.C. VOLTAGE RANGES:
0-7.5/15/75/150/750/1500 Volts

2 RESISTANCE RANGES:
0-10,000 Ohms 0-1 Megohm

3 D.C. CURRENT RANGES:
0-15/150 Ma. 0-1.5 Amps.

3 DECIBEL RANGES:
-6 db to + 18 db +34 db to +58 db
+14 db to +38 db

The Model 770-A comes complete with self-contained batteries, test leads and all operating instructions $15.85

Write Dept. RN-2 for catalog of complete line.

Manufactured and Guaranteed by

SUPERIOR INSTRUMENTS CO.
2435 White Plains Road New York 67, N. Y.

AT YOUR RADIO PARTS JOBBER

then, is to tie another high-band, half-wave dipole to these same feed points. (See Fig. 5B.) Fig. 5C shows the resulting current distribution of this system. As in the previous case, dipoles "A" and "D" can be considered to cancel each other out; but now dipole "E" fills the gap since this new dipole is in the same phase relationship as dipoles "B" and "C."

Adding all the currents together, dipoles "A" and "D" cancel each other out, and dipoles "B," "C," and "E" are in-phase. This system achieves in-phase operation of the three sections on the high band, and also functions as a half-wave dipole on the low band. However, due to low-impedance characteristics, it has limited bandwidth.

To obtain higher impedance for the configuration shown in Fig. 5B, folded dipoles are used. In addition, special quarter-wave transformer lines produce a total impedance of 300 ohms for the three dipoles in parallel. The screen-type reflector used with this antenna gives an optimum gain of about 7 db and is nonresonant. This means that the reflector itself is not frequency-sensitive. This was chosen in preference to a straight-bar reflector whose maximum potential gain is somewhat over 3 db which is achieved only at one frequency. —30—

ALUMINUM CHASSIS

By ARTHUR TRAUFFER

MANUFACTURERS of aluminum kitchenware are now putting out a complete line of small seamless aluminum utensils for little girls who want to learn how to bake and cook.


The photograph shows two of the little pans, selling for about 15 cents each, that are of interest to radio and electronic experimenters and gadgeteers.

Made of seamless aluminum, the loaf pan measures 5" long, 2½" wide, and 1½" deep, while the square pan measures 5" x 5" x 1⅛".

The photograph shows a fixed frequency r.f. amplifier built into the loaf pan while the square pan is propped behind it.

It's fun to work with these little pans; the aluminum is so soft and thin you can punch it and cut it with the small blade of a pocket knife. However, the metal is plenty stiff enough for radio construction projects. —30—

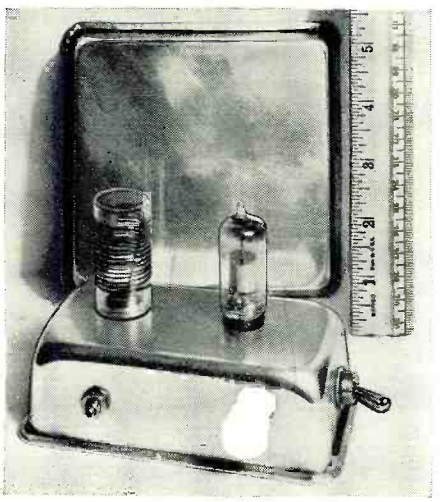How toy aluminum pots and pans can be used as inexpensive, easily-worked radio chassis.




www.americanradiohistory.com

You can't do without...

SYLVANIA'S SEE-WELL TOOL KIT

A NEW, TIME-SAVING TOOL-SENSATIO !

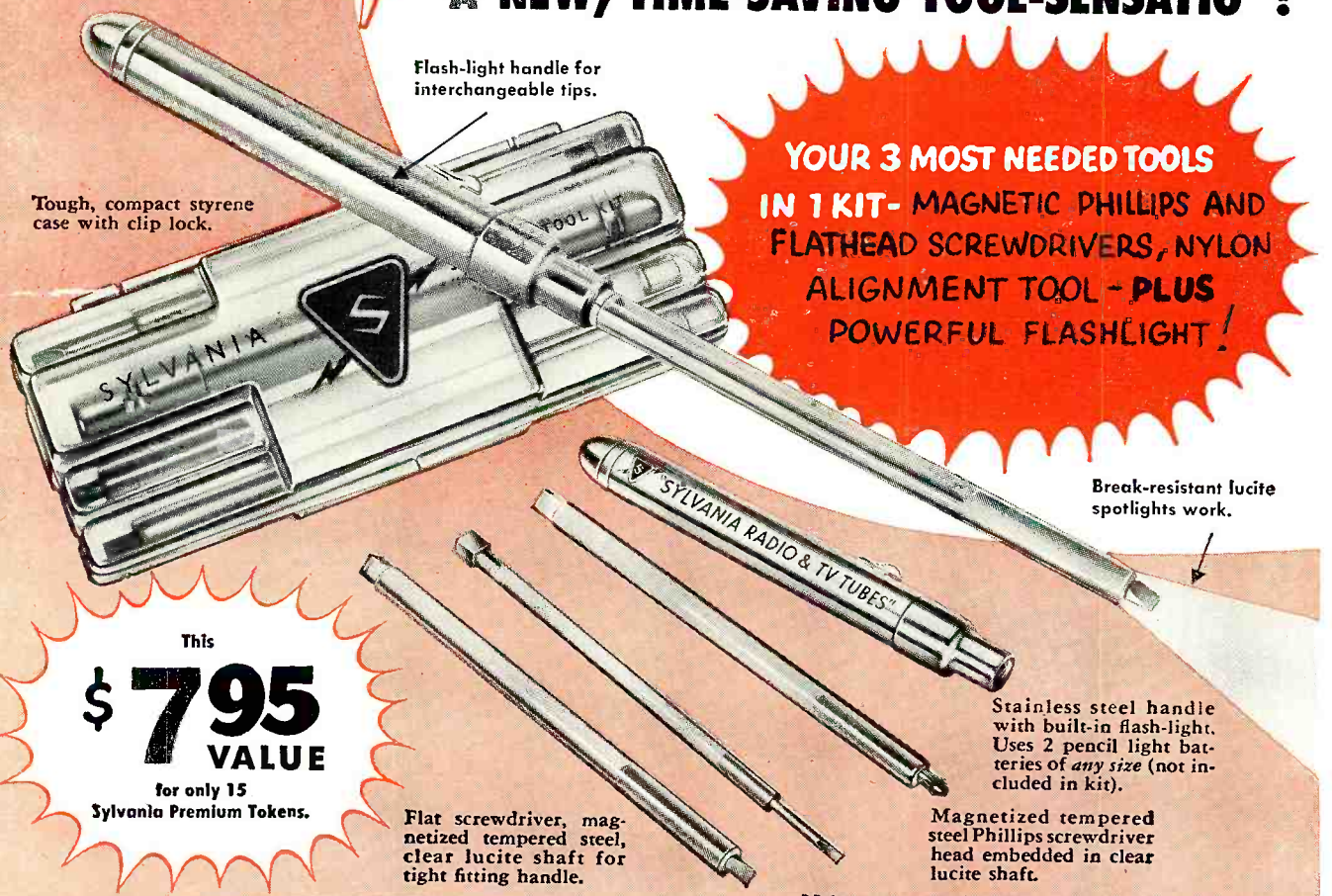

YOUR 3 MOST NEEDED TOOLS IN 1 KIT- MAGNETIC PHILLIPS AND FLATHEAD SCREWDRIVERS, NYLON ALIGNMENT TOOL - **PLUS** POWERFUL FLASHLIGHT!

This **$7.95** VALUE for only 15 Sylvania Premium Tokens.

NO MORE FUMBLING inside dark radio and TV cabinets. At the flick of a switch, a bright light automatically focuses right at the spot you're seeking. Saves your time . . . improves your work.

3 Handy Tools in 1. Magnetized Phillips and Flathead screwdrivers, nylon alignment tool—all 3 built into break-resistant lucite shafts perfectly fitted to flashlight handle.

Without doubt, this SEE-WELL Tool Kit is one of the slickest, quickest service tools ever built!

See your Sylvania Distributor Today! He has this remarkable tool kit for you now—you need only 15 Sylvania Premium Tokens. The time to get this valuable Sylvania See-Well Tool Kit is NOW—so don't delay, order high quality Sylvania tubes TODAY.

Remember, you get 1 token with every 25 Sylvania Receiving Tubes or every Sylvania TV Picture Tube you buy.



SYLVANIA

Sylvania Electric Products Inc. Dept. 4R-3502, 1740 Broadway, New York 19, N. Y.

In Canada: Sylvania Electric (Canada) Ltd.
University Tower Bldg., St. Catherine Street, Montreal, P. Q.

LIGHTING • RADIO • ELECTRONICS • TELEVISION

www.americanradiohistory.com

FIX ANY TV or



SAVE $1.25!

Make your service library complete! Have the needed data at your fingertips WHEN YOU NEED IT!

If broken into "lessons" and sent to you as a "course," you'd regard this new Ghirardi training as a bargain at $100 OR MORE! Instead you buy BOTH big books at the bargain price of only $12.00 (you save $1.25!)



A. A. Ghirardi
More servicemen have trained from Ghirardi books than any other books or courses of their kind!

Handle any job on any set easier and better! This complete Ghirardi training shows you exactly what to . . . every step of the way.

Let these two up-to-the-minute Ghirardi books make it easy for you to handle ALL types of AM, FM and Television receiver service by the very best and latest methods! Learn to handle jobs faster, better . . . and with less testing! Whether you're a service beginner or an experienced technician you'll find the speedy, *professional* methods that are so clearly explained can give BOTH your service efficiency and your earnings a big boost!

A "GOLD MINE" OF HOW-TO-DO-IT SERVICE DATA!

Almost 1500 pages and over 800 big, clear pictures and diagrams explain EVERY troubleshooting and repair operation so simply it's next to impossible to go wrong. Each book contains up-to-date data on the latest methods and equipment.

Books are sold separately at prices indicated. Better yet, you can save $1.25 by buying both together! Send no money. Practice from these great books for 10 full days FREE.

Mail coupon today to Rinehart Books, Technical Div., Dept. RE-14, 232 Madison Ave., New York 16, N. Y.

Radio & Television Receiver

1 Circuitry & Operation

by Ghirardi & Johnson
669 pages, 417 clear illustrations, $6.50

It's lots easier to repair ANY radio or television set when you know all about its circuits and just why and how each one works! You locate troubles in much less time and with less testing. You repair them faster, better —*more profitably!*

That's why *Radio & Television Receiver CIRCUITRY AND OPERATION* is invaluable to servicemen who want to be well equipped to handle today's complicated receivers! First it gives a complete understanding of basic circuits and their variations. It teaches you to recognize each one quickly. Then it shows how to eliminate useless testing and guesswork in making repairs.

Throughout, this book gives you the kind of above-average training that takes the "headaches" out of servicing —the kind that fits you for the better-paid jobs. Covers all basic circuits used in modern TV and radio receivers as well as phono pick-ups and record players.

Sold separately for $6.50—or see big MONEY-SAVING COMBINATION OFFER IN COUPON.

Radio & Television Receiver

2 Troubleshooting & Repair

by Ghirardi & Johnson
822 pages, 417 clear illustrations, $6.75

Backed by the how-to-do-it methods and procedures so clearly explained in this big book, you can breeze through all types of television and radio service jobs easier and faster than you may have thought possible!

Throughout its 822 pages, *Radio & Television TROUBLE-SHOOTING AND REPAIR* is an amazingly complete, how-to-do-it guide to *professional* service methods . . . the kind that help you handle jobs lots faster and make more money doing it!

For beginners, this big book is an easily understood course in locating troubles fast and repairing them r-i-g-h-t. For experienced servicemen, it is a quick way to "brush up" on specific jobs; to develop better methods and shortcuts; or to find fast answers to tough service problems.

Modern troubleshooting is clearly explained—from quick "static" tests to dynamic signal tracing and all the rest. Special hard-to-fix troubles are fully covered. Step-by-step charts demonstrate exactly what to do on different operations. *A big television section includes everything you need to know for fast, accurate work on any TV receiver model or make.*

Sold separately for $6.75. Save money by ordering the SPECIAL COMBINATION offer. Send coupon today. Practice 10 full days FREE!

DON'T THROW OLD RADIOS AWAY



RADIO TROUBLE-SHOOTER'S HANDBOOK
by Ghirardi
744 manual-size pages
Price $6.50

This big Handbook contains just the data you need to fix them in a jiffy!

It's a cinch to repair old radios when you have Ghirardi's famous RADIO TROUBLESHOOTER'S HANDBOOK at your side! Many users say this big book has made it easy for them to fix sets that dealers said could no longer be repaired and should be junked.

Just look up the make and model you want to repair. The Handbook shows just what the trouble is likely to be . . . then explains step by step exactly how to fix it.

No guesswork! No useless testing! No wasted time!


Handbook covers common trouble symptoms of over 4,800 old models of home and auto radios and automatic record changers *by 202 manufacturers* . . . from Atwater Kent to Zenith. Even beginners can follow its clear, easy instructions.

CUTS SERVICE TIME IN HALF ON 4 OLD SETS OUT OF 5!

Gives how-to-do-it data on specific jobs—not just a lot of general theory. In addition, a big section is chock full of tube and other component data, graphs, diagrams, service short cuts and money-making ideas. Cuts time in half on hundreds of jobs. Enables you to fix old sets cheaply for customers . . . and at a real profit to yourself!

Order Radio Troubleshooter's Handbook in coupon today for 10-day FREE examination.

BE AN EXPERT ON MAGNETIC RECORDING!

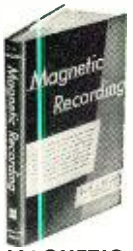

MAGNETIC RECORDING
by S. J. Begun
242 pages, 146 illustrations
Price $5.00

This how-to-do-it book makes it easy to specialize in one of the fastest-growing electronic fields

There's a real future for men who specialize in the fast-growing field of magnetic recording in all of its many branches!

From high fidelity sound to broadcasting, to sound movies, industrial communications, secret communications (speech scrambling), amateur radio, industrial sound and noise measurements and many others, magnetic recording is now an important factor. This book, *Magnetic Recording*, by one of the nation's acknowledged experts, clearly explains all details of the art.

A COMPLETE GUIDE TO RECORDING METHODS AND EQUIPMENT

First you get a clear understanding of every phase of wire and tape recording . . . from basic acoustic and magnetic theories to components, equipment and circuits in present day use. Subjects include Acoustic Factors; Magnetism; Magnetic Recording Theory and Practice; System Components; Magnetic Recording Equipment; Magnetic Recording Applications; Instrumentation and Recording Measurements; The Magnetic Phonograph, and many more.

Read it 10 full days at our risk. Order Magnetic Recording in coupon.

CASH IN ON TELEVISION SERVICE PROFITS!



PRACTICAL TELEVISION
by Johnson & Newitt
375 pages,
230 illustrations
Price $4.00

Learn Right from this easily understood book

Good training in television service doesn't need to cost you a lot of money! This great book at only $4.00 tells you step by step what to do, what mistakes to avoid, what tools, parts and equipment to use . . . in short, how to handle all kinds of TV receiver servicing fast, easy and r-i-g-h-t!

Besides explaining just how television work differs from radio, this book tells you exactly how to perform all operations in troubleshooting, diagnosing and making repairs.

DOZENS OF HELPFUL CASE HISTORIES AND SERVICE HINTS

Dozens of actual television servicing case histories and service shortcuts make the book ideal for beginners and experienced servicemen alike.

Subjects include: TV System Fundamentals; R-F, I-F and Detector Sections; Video Amplifiers; Cathode Ray Tubes; Synchronizing and Sweep Circuits; Power Supplies; Antennas and Wave Propagation; TV Receiver Installation; Test Equipment and Alignment; Wiring and Repair Techniques; Color TV; Receiver Layout Diagrams and dozens more.

Practice from it 10 days FREE. Order Practical Television Servicing in coupon.

USE COUPON FOR *10-day Free Trial!*

www.americanradiohistory.com

RADIO EVER MADE

FAST! EASY! R-I-G-H-T!

Here's How to Make HIGH FIDELITY Mean What it Says!



JUST OUT!

HIGH FIDELITY TECHNIQUES

by John H. Newitt
Staff, Mass. Inst. of Technology
494 pages, 203 illustrations, Price $7.50

A COMPLETE GUIDE TO AMERICA'S FASTEST GROWING HOBBY


Get better results from "Hi-Fi" by having all the facts and latest ideas at your fingertips!

This big, brand new book by one of the nation's experts, brings you the complete "low down" on modern sound reproduction methods and equipment. It shows how to get better results at lower cost; how to build your own; how to service hi-fi equipment; discusses all details of components; compares different methods—AND IS CRAMMED FULL OF HOW-TO-DO-IT TIPS AND IDEAS.

ANSWERS YOUR HI-FI QUESTIONS . . . Chock full of how-to-do-it ideas

Here are just a few of the many subjects: How to get the right hi-fi equipment for your needs; Hi-fi versus P.A. type speakers; Loud-speaker construction and performance; Adjusting bass-reflex cabinets; Controlling distortion; Getting rid of "hangover"; The best reproducer enclosure; Selecting a woofer-tweeter; Sound-proofing materials; All about output transformers; Special hi-fi circuits; Ways to suppress noise; Negative feedback and how to use it; Amplifier construction hints; Minimizing tuner distortion; Avoiding chatter; Limiter-discriminator vs. ratio detector FM circuits; All about records and record players; Avoiding record wear; Tips for custom builders; Bass-reflex calculations and design charts; Acoustical horn design data . . . and literally dozens of other subjects.

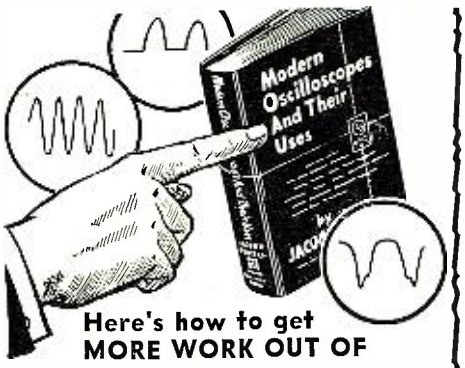Order **High Fidelity Techniques** *in coupon today for 10-day FREE trial!*



Here's how to get MORE WORK OUT OF YOUR OSCILLOSCOPE!

MODERN OSCILLOSCOPES AND THEIR USES

By J. H. Ruiter, Jr., of Allen B. Du Mont Laboratories, Inc.
326 pages, 370 illus.
Price $6.00

Oscilloscopes are "gold mines" for servicemen who learn to use them fully—*and here is a book that REALLY SHOWS YOU HOW.*

In clear, easily understood terms, *Modern Oscilloscopes and Their Uses* explains when, where and how to use the oscilloscope . . . how to interpret patterns . . . how to use your 'scope to handle all sorts of jobs easier, faster and better.

No complicated theory! This book gets right down to "brass tacks" in showing how oscilloscopes operate. Then you see exactly how to use them in lab work and on all types of AM, FM and television service.

A complete guide to the HANDIEST INSTRUMENT OF THEM ALL!

Each operation is made as simple as A-B-C. You learn where and how to use the 'scope on specific jobs; how to make connections; how to adjust circuit components, how to set the controls . . . and HOW TO ANALYZE PATTERNS. 370 illustrations including dozens of pattern photos make things doubly clear.



Practice from it 10 days FREE. Order **Modern Oscilloscopes** *in coupon.*

'SCOPE EXPERTS get better jobs . . . bigger pay!


Here's How to SAVE MONEY ON INSTRUMENTS!



. . . for servicemen
. . . amateurs
. . . experimenters

BASIC ELECTRONIC TEST INSTRUMENTS

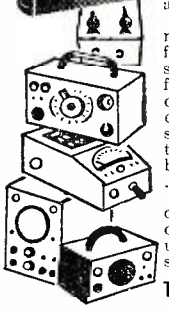by Rufus P. Turner
254 pages, 171 illus. Price $4.00



Here, at last, is an instrument book especially for servicemen, amateurs and experimenters!

Basic Electronic Test Instruments helps you work better and faster with fewer instruments; shows how to increase the usefulness of old instruments; how to choose the right instrument for each job; how to understand instrument readings and put them to practical use; how to avoid buying unnecessary instruments . . . and lots more.

Over 60 instruments from the old standbys to the very latest ones are fully described. Their uses are clearly explained. Work-saving shortcuts are outlined.

TEST BETTER—FASTER—RIGHT!

Included are complete details on simple meters for current and voltage; ohmmeters and V-O-M's, V-T voltmeters; power meters; impedance meters; capacitor checkers; inductance checkers; special-purpose bridges; oscilloscopes; R-F test oscillators; signal generators; audio test oscillators; R-F and A-F measuring devices; signal tracers; tube testers and many others.


Among other things this handy book is a complete training course in the latest instruments including grid-dip oscillators, TV sweep and marker generators; TV linearity pattern generators, square wave generators, distortion meters, etc.

Dozens of time-saving "tricks" help you put old instruments to new uses.

Check Basic **Electronic Test Instruments** *in coupon for 10-day FREE trial.*

Send No Money! TRY ANY BOOK TO FULL DAYS FREE!

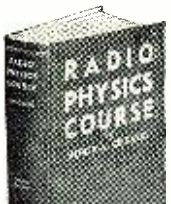Here's How to BREAK INTO RADIO-ELECTRONICS!



RADIO PHYSICS COURSE

by Ghirardi
972 pages, 508 illus.
856 self-test questions
Price only $6.50

More people now in Radio-Television-Electronics got their basic training from this book than any other of its type!

The most complete training course in radio fundamentals ever offered! . . . that's what the experts say about Ghirardi's world-famous RADIO PHYSICS COURSE book. More widely used in World War II military training and for home study than any other basic text.

RADIO PHYSICS COURSE is the oldest text of its kind on the market—and still a "best seller" *because it is so complete, clear and easy to understand, even without any previous radio training.* You can buy newer and far more costly training—but you can't buy better training at anywhere near the price. Ask the men who know!

Starts right at the beginning with Basic Electricity. Then it takes you step by step through the entire field from circuits showing basic functions to the final applications of these circuits in radio-electronic equipment.

Study from it for 10-full days. Specify **RADIO PHYSICS COURSE** *in coupon.*

Dept. RN-24, Rinehart Books, Inc., Technical Division, 232 Madison Ave., New York 16, N. Y.

☐ **Check here for MONEY-SAVING COMBINATION OFFER . . .**

. . . on Ghirardi's Radio & TV Receiver CIRCUITRY AND OPERATION, and Radio & TV Receiver TROUBLESHOOTING AND REPAIR. Price only $12.00 for the two books plus postage. (Regular price $13.25 . . . *you save $1.25*). Payable at rate of $3 after 10 days if you decide to keep books and $3 a month for three months until $12 has been paid. If not satisfactory, return books in 10 days and owe nothing.

Check here to order INDIVIDUAL BOOKS

- ☐ Radio & TV Receiver CIRCUITRY & OPERATION.....$6.50
- ☐ Radio & TV Receiver TROUBLESHOOTING & REPAIR.....$6.75
- ☐ RADIO TROUBLESHOOTER'S HANDBOOK.....$6.50
- ☐ MAGNETIC RECORDING.....$5.00
- ☐ PRACTICAL TELEVISION SERVICING.$4.00
- ☐ HIGH FIDELITY TECHNIQUES.....$7.50
- ☐ MODERN OSCILLOSCOPES AND THEIR USES.....$6.00
- ☐ BASIC ELECTRONIC TEST INSTRUMENTS $4.00
- ☐ RADIO PHYSICS COURSE.....$6.50

If cash is sent with order, we pay postage on books—same 10 day return privilege. Otherwise, postage is extra.


To order OUTSIDE U.S.A.—Special combination offer, $13.00 for both books. For all other books, add 50c each to above prices for handling through customs, etc. Sold for cash only. Any book may be returned in 10 days and money will be refunded.

Name .....

Address .....


City, Zone, State .....

www.americanradiohistory.com

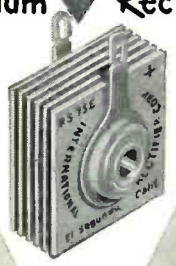INTERNATIONAL RECTIFIER CORPORATION
EL SEGUNDO CALIFORNIA
DIRECT REPLACEMENT
RADIO & TV
Selenium Rectifiers

UNIVERSAL MOUNTING
WIDER RANGE
NOW AVAILABLE AT YOUR FAVORITE JOBBER
Write for Bulletin JRP-1
INTERNATIONAL RECTIFIER CORPORATION
1521 E. Grand Ave., El Segundo, Calif · Phone: ORegon 8-6281
CHICAGO: 205 W. Wacker Drive · Phone: Franklin 2-3889
NEW YORK: 501 Madison Avenue · Phone: Plaza 5-8665

WORLD'S MOST POWERFUL RADIO TRANSMITTER

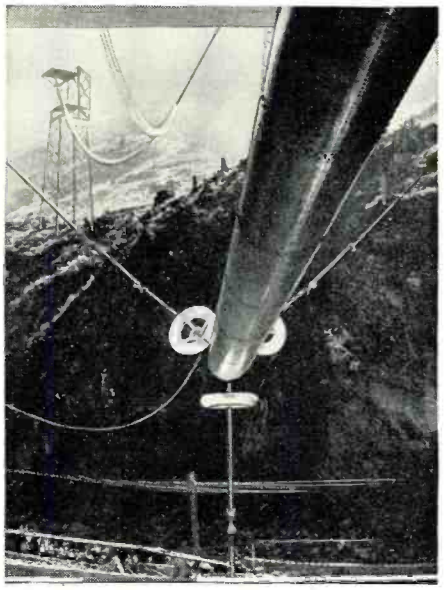Signals are so strong they may be received even by submerged subs.



View from transmitter building along the antenna lead-in trunk, shows 145 foot bus tower halfway up mountain, one of thirteen which support transmission line. The "doughnuts" are corona shields guarding the trunk from damage by corona discharge.

THE world's most powerful radio transmitter has been put into operation by the U.S. Navy at Jim Creek Valley, Washington, in the heart of the Cascade mountains.

The new 1,200,000-watt radio-telegraph transmitter can send messages to Navy forces operating in any of the seven seas and its signals will penetrate to submarines cruising below the surface as well as to arctic outposts despite frequent magnetic storms and ionospheric disturbances.

The megawatt transmitter has been designed around the special *RCA* Type 5831, 500 kw. high-vacuum triode. Each of the two power amplifiers employs three 5831's, two in the push-pull circuit with the third available as a spare.

The transmitter also features microsecond fault protection developed especially for this equipment. This electronic device relieves overload faults in the super-power amplifier tubes in seven-millionths of a second and prevents the build-up of currents that could damage the tubes.


Tuning adjustments have been confined to remote push-button control of the antenna and power amplifier tuning. This is accomplished by special broadband amplifiers developed by *RCA* and used in its standard b.c. transmitters.

The antenna is a highly-efficient catenary-type with ten catenary spans, representing the largest antenna ever erected.

The transmitter itself is contained in an enclosure 80 feet wide by 50 feet deep. The transmitter is arranged in "U" shape with the supervisory control console and the operator's desk located between the wings of the "U."

The windowless transmitter station is several stories high and is shielded against the intense electromagnetic field. The structure also includes a machine, electrical, sheet metal, and other servicing shops as well as storage space. —30—

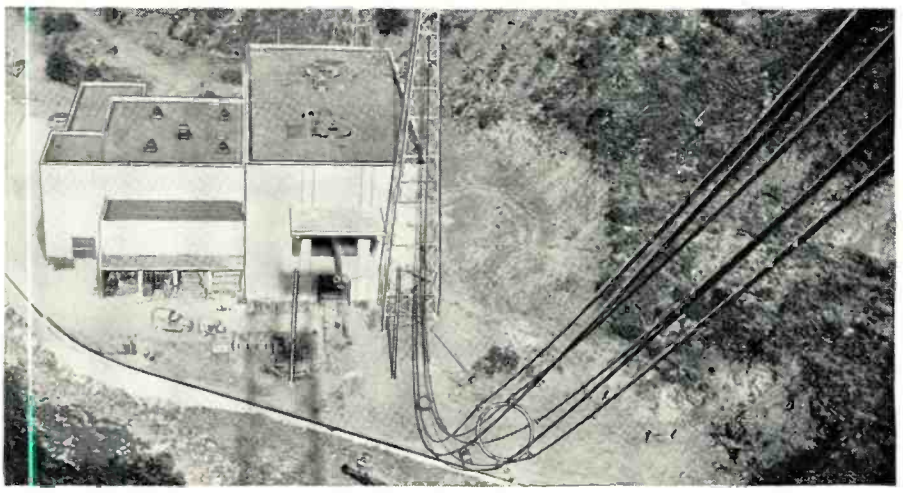Bird's-eye view through steel framework of 200-foot summit ridge tower shows transmitter building nestling in valley between 3000-foot mountains.



www.americanradiohistory.com

Send for Your **FREE** Copy of the NEW 1954 MIDWEST TELEVISION and RADIO Catalog

MIDWEST *Presents*

For 1954 a Completely NEW LINE of 21" and 27" TELEVISION

CONSOLES
TABLE MODELS
and
COMPLETE CHASSIS
at
LOW FACTORY PRICES





YOUR CHOICE OF EITHER 12 CHANNEL VHF or All-Channel VHF-UHF Models

Buy your Television or Radio Direct from the Midwest Factory . . . on 30 DAYS TRIAL . . . Easy Terms . . . and at LOW FACTORY PRICES. For 34 years Midwest, the world's largest and oldest exclusive Factory-To-You radio and television manufacturer, has served hundreds of thousands of satisfied customers all over the world.

EASY TERMS
30 DAYS TRIAL







FACTORY-TO-YOU

All models available in your choice of mahogany, walnut finish or blond limed oak.

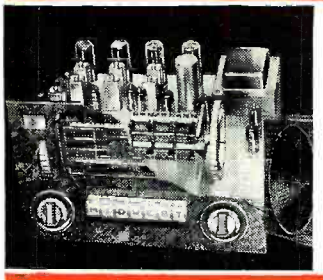Also—Powerful New 1954 World-Ranging
MIDWEST Series 16 RADIOS
In Beautiful Consoles and Complete Chassis



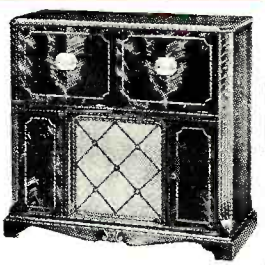Once again Midwest offers its famous series 16 five band AM-FM radio chassis and the magnificent new Symphony Grand Radio-Phonograph with 3-Speed Automatic Intermix Record Player. Also, a complete line of clock radios, table radios, and portables.



MIDWEST RADIO & TELEVISION CORP.
DEPT. H-37, 909 BROADWAY, CINCINNATI 2, OHIO

WRITE IN NAME AND ADDRESS (PLEASE PRINT) ON COUPON OR 2c POSTCARD

MIDWEST RADIO & TELEVISION CORP.
Dept. H-37, 909 BROADWAY • CINCINNATI 2, OHIO
Please send me your new FREE 1954 Catalog.


NAME _____

ADDRESS _____

CITY _____ ZONE ____ STATE _____

www.americanradiohistory.com

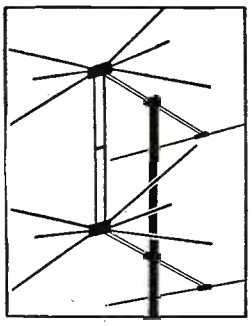Dealers—Servicemen
ATTENTION!
Tremendous Bargains in Conicals




2-BAY 16-ELEMENT CONICAL ARRAY With Hi-Band Adapters

Sturdy ⅜" Element

$4.99 Each
In Lots of Three
Single Lots $5.30

Never before has National Electronics had a BARGAIN like this. We made a special purchase in order to get these sensational prices. And this array has everything. This conical 2-bay 16-element array provides ultra-fine fringe reception. Includes sixteen ⅜ inch airplane type aluminum elements, including hi-band adapters for greater gain on the high channels and is complete with one pair of stacking bars to each array. These are packed in cartons of three 16-element arrays per carton. With tie rods at $14.95 per carton.

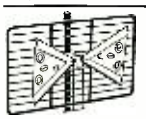When purchased in single 16-element arrays, separately boxed—your cost is.....$5.30 Each
3 Two-Bay Arrays per carton without Tie Rods.....$13.50 Carton
4 Bay Ultra-Fringe Stacking Assembly for above—Model 4B.....$1.95 Each



HI-GAIN BOW-TIE REFLECTOR For UHF.....$1.95 Each


High gain at low cost. Completely pre-assembled. Easily stacked for fringe use.
2 bay with tie rods.....$4.40
4 bays with stack harness.... 9.95
Lots of 6—Individually cartoned 9.95

Save With Rocket 35 Foot Mast Kits

Economy mast kit contains 3 self-coupling 10′ seamless TRI-COATED 1¼″ O.D. masts, one 5′ mast, 300 feet of 6/20 galvanized steel guy wire, and everything else needed including guy rings, insulators, cable clamps, guy hooks, and swivel mounting base.
35 foot Mast Kit $15.95 25 foot Mast Kit $11.95

ALL PRICES F.O.B. CLEVELAND, OHIO
Do not remit more than complete purchase price. Pay shipping charges on receipt of goods. 25% deposit on all C.O.D. orders, please. Money-back guarantee.
Prices Subject to Change Without Notice

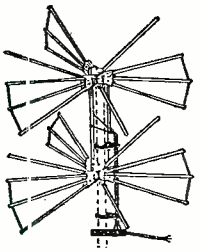NEW SUPER FRINGE MOTORLESS DIRECTRONIC VHF-UHF
CHANNELS 2-83



- Reception From All Directions
- No Motors Needed

New Super Directronic is Electronically beamed in all directions by directronic selector switch at receiver. Hi-gain 24-element array eliminates need for motors. Kit complete with 75′ tubular Tri-X cable. Directronic Switch, Matched Stacking Bars and Universal U-Clamp.

ONLY $23.50
YOU SAVE 50% ON AVERAGE INSTALLATION

ROCKET BROAD BAND YAGIS

- SENSATIONAL GAIN
- SENSATIONAL PICTURES IN FRINGE AND ULTRA FRINGE AREAS



Switch to Yagi Broad Band Hi-Gain Antennas! These new Yagis give you Yagi reception on the 5 low-band and 7 hi-band channels—no restriction to one single channel. A two-bay array will out-perform even a 10 or 12-element single channel Yagi. Price is sensationally low. Complete serviceman's array includes 1 double reflector, 2 folded dipoles, 3 directors, Universal mast clamp. Easy-to-assemble quick rig construction.

Model RB 26—Ch. 2 thru 6—7-element.....$10.95 ea.
Model RB 713—Ch. 7 thru 13—9-element... 5.95 ea.
Matched Stacking Bars..... 1.25 ea.


SAVE ON ANTENNA ACCESSORIES

UHF tubular low-loss twin lead 100′ coil....$4.95
Rocket twin lead—7/28 stranded..... .02 ft.
UHF—VHF Antenna Coupler, permits use of 1 lead for both UHF & VHF Antennas..... 2.75
Lightning Arrestor—for tubular or flat lead... .69
UHF Mast Stand-off Insulators—7″ ..... .12
UHF Screw Standoff—7″ ..... .06

NEW SPRING CATALOG AVAILABLE
Includes Sensational Profit Sharing Point Plan

National Electronics
OF CLEVELAND
THE HOUSE OF TV VALUES
102 Delco Building Cleveland 3, Ohio

The Magneloop

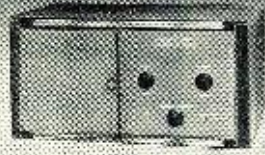

Automatic Station Break Announcer

This new endless magnetic tape loop recorder is designed to record and playback any message, music or sound effect up to twenty minutes in length or a multiplicity of messages, etc., totaling twenty minutes. Designed for extreme simplicity of operation and permanent trouble-free performance. Ruggedly constructed to minimize maintenance and insure continuous unattended performance. Equipped with low-noise level pre-amplifier and 60 kc supersonic bias and erase oscillator. Also provided with high-impedance low-level microphone input and ungrounded bridging input which is automatically disconnected when microphone plug is inserted. Meets NARTB standards.

Ideal for These Varied Applications:

- ★ Repetitive Commercials
- ★ Industrial Exhibits
- ★ Audio Advertising
- ★ Voice Training
- ★ Weather Announcements
- ★ Service Stations
- ★ Super-Markets
- ★ Elevator Announcements

Write for complete technical literature and direct factory prices to Dept. RT

AMPLIFIER CORP. of AMERICA
398 Broadway, N. Y. 13, N. Y.

(Advertisement)



"Thank Heaven . . . we can leave now. Here comes the JENSEN NEEDLE."

Amateur's Superhet

(*Continued from page 45*)

3500 kc. with the mixer tuning condenser, C_3, set at nearly maximum capacity. Likewise, the range 7000 to 7300 kc. should peak up with a low capacity setting of C_3. If it is not possible to peak up both bands, it will be necessary to prune the coil L_1. With the cathode tap at three turns from the ground end of L_1, as specified in the coil data, no difficulty should be encountered in getting the mixer to regenerate. If the mixer will not regenerate after connecting an antenna, it probably indicates too close a coupling in condenser C_1. The antenna trimmer condenser, C_1, should be increased in capacity for a short antenna and decreased for a long antenna.

For those not possessing a calibrated signal generator, an alternative method of alignment will be suggested. This method requires the use of a grid dip meter and a calibrated communications receiver, both of which are more generally available than the required test gear.

Under this method the two local oscillators are first set to their proper operating frequencies. This may be done by getting an approximate setting with the grid dip meter and then an exact setting by listening to the signal of the given oscillator in the communications receiver. With the proper setting of the second oscillator, a 1500 kc. signal applied to the grid of V_2 is converted to 175 kc. in the output. Using an unmodulated 1500 kc. signal from the grid dip meter in this manner, it is necessary to adjust the regeneration circuit along with transformer T_3 in order to obtain an audible signal in the headphones. After this is accomplished, the remainder of the alignment may be performed using the signal from the dip meter in much the same manner as the signal generator was used.

After completion of alignment, an antenna may be connected and the set is ready for many pleasant hours of operation. Almost any single-wire antenna may be used from a three-foot whip to a half-wave on eighty. The longer antenna, in addition to providing greater signal pickup, has the advantage of causing the mixer tuning to be quite broad. This means that it is not necessary to readjust the mixer tuning every few kilocycles as is necessary when using a short antenna. The adjustment of the antenna trimmer condenser, C_1, is not critical but, in general, it is desirable to have the maximum coupling that will allow the mixer to regenerate at all settings of its tuning control.

In operation the second detector may be operated in an oscillating or non-oscillating condition depending on whether c.w. or phone is to be received. The second detector regeneration control is operated in the same manner as the control in a simple re-

www.americanradiohistory.com

A Leader First

No Drift, No Coast




Only Superotor®

HAS

Double Lock Stop



At last! — an antenna rotator that really **stays "on target."** With **Superotor** there's no jumping up to make adjustments, because it locks in place **two** ways, instead of one. First, a motor brake eliminates "coasting"; second, a worm gear lock prevents "drifting." This exclusive double lock also permits rotation in increments of **less than ½-degree,** enabling razor-sharp tuning for top UHF reception!

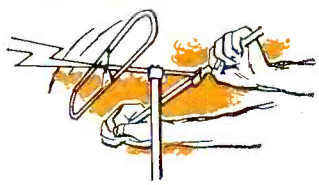

Compare All The Features, And You'll Join The Big Switch To Superotor




Patent Applied for Copyright



• **Quick Detachable Drive Unit**

A Leader First

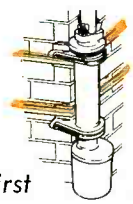

• **Built-in Chimney Mount**

A Leader First



• **Steel-Reinforced Construction**

A Leader First



• **VP* Tuning Accurate—Precise Simple**

A Leader First

Leader ELECTRONICS INC.

2925 EAST 55TH STREET


CLEVELAND 27, OHIO

LEADING THE WAY TO BETTER PRODUCTS

www.americanradiohistory.com



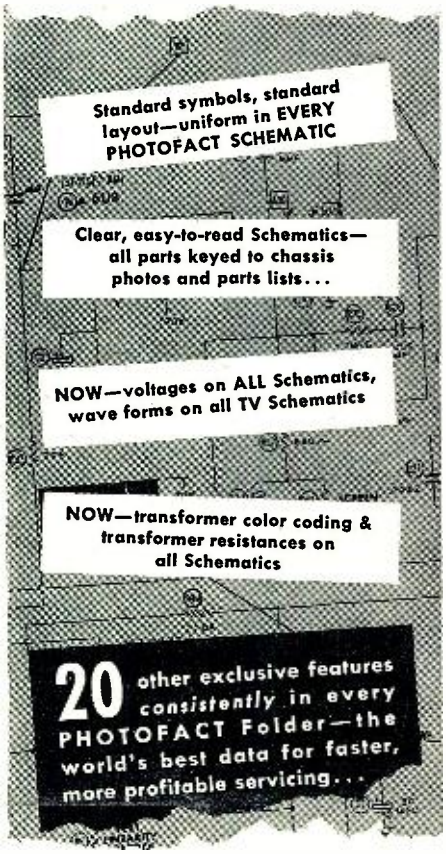you're on easy street with PHOTOFACT SCHEMATICS



NOW! GET THE PROOF FOR YOURSELF!

FREE We'll send you a Free Photofact TV Folder—just ask us for it!

Learn for yourself how PHOTOFACT pays for itself by earning bigger profits for you! We'll send you the proof—a FREE specimen PHOTOFACT TV Folder that shows all the features found *consistently* and *exclusively* ONLY in PHOTOFACT. Send for your FREE specimen TV Folder now. Examine it. Compare it. You'll see why PHOTOFACT belongs in your shop! And you'll want to ask your parts distributor about the pay-as-you-earn-plan. Only $25 down brings you the entire PHOTOFACT Library. Write for FREE specimen TV Folder—learn now how to earn more!

HOWARD W. SAMS & CO., INC.
2203 E. 46th St., Indianapolis 5, Ind.

HOWARD W. SAMS & CO., INC.

generative receiver. There is, however, no detuning effect from operation of the main tuning control. Those who have operated a simple regenerative receiver will find the regeneration control on this set very smooth indeed.

The mixer regeneration control is always adjusted so that the mixer will be non-oscillating. Allowing the mixer to oscillate will cause spurious signals to be heard due to autodyne action. Maximum gain and selectivity are realized with the regeneration set just below the point of oscillation. This may have to be readjusted slightly from time to time in tuning across the band or upon changing bands.

With the mixer tuning control peaked up at its low frequency end, the main dial should cover the range 3500 to 4300 kc. and with a high frequency setting of the mixer the range should be 6500 to 7300 kc. In practice, operation of the receiver may be done with one hand and only an occasional trimming of the mixer.

From the foregoing description the operation may sound a bit formidable. Actually that is not so. If the set has been well constructed, using good quality components, the result will be a first class communications receiver with excellent stability, selectivity, and sensitivity, but with coverage of limited bands. —30—

Positive Grid Circuits

(*Continued from page* 63)

fier. This direct connection places cathode 8 at about the same d.c. potential as plate 1 and necessitates that grid 7 receive an offsetting positive voltage. This is supplied by the voltage divider R_1 and R_2 and from this network grid 7 is given the proper operating voltage to provide the correct bias for the second r.f. amplifier.

It is interesting to note that both tube sections are in series with each other so that the same current flows through both sections. Also, a.g.c. bias is applied only to the first triode but its effect is felt by both stages because of the series connection.

This trend toward placing tubes in series is being adopted by a number of television manufacturers and is not confined only to the cascode amplifiers mentioned. A popular practice is to string one or more tubes in series-parallel arrangement across the power supply, as shown in Fig. 6. Here, between the power supply terminals of 360 volts and ground, we find the audio output amplifier, a 6V6GT, in series with a number of stages, all of which are in the front end or video sections of the receiver. Of the applied 360 volts, 230 volts are dropped across the audio amplifier tube, leaving 130 volts at the cathode. This 130 volts then serves as the plate "B+" for all of the stages to which it is connected.

The reason for using such an arrangement stems primarily from its economy. To obtain 130 volts from the power supply would require a voltage divider with appropriate bleeder resistors to step down the voltage from 360 volts to whatever level is desired. High-wattage bleeder resistors, however, are quite costly. However, by arranging the stages as shown in Fig. 6, the correct voltage distribution can be obtained without bleeder resistors. The audio amplifier tube carries all of the series current while the remaining tubes in the bottom half of this string use as much of this current as they need.

Note that the cathode of the 6V6GT audio amplifier is positive and hence the grid must be given a similar positive voltage in order to establish the proper bias. The bias value in this set is 122.5 volts for the grid, leaving this element negative with respect to the cathode by 7.5 volts.

When tubes are connected as shown in Fig. 6, many defect indications appear which differ from those obtained in a more conventionally designed receiver. Thus, failure of the audio amplifier tube to conduct will remove both sound and picture and raster from the set. Raster removal occurs because one of the accelerating elements of the picture tube is tied into the +130-volt line. Thus, the importance of the audio output tube rises sharply in such an arrangement.

Perhaps the prime lesson to learn from all this is that:

1. Tubes operate by the relative potentials between their several elements and not by the potential between an element and some arbitrary reference level, such as the chassis.

2. Positive grid voltages are perfectly feasible for certain applications.

Learn this and you have taken a long stride toward better television servicing. —30—

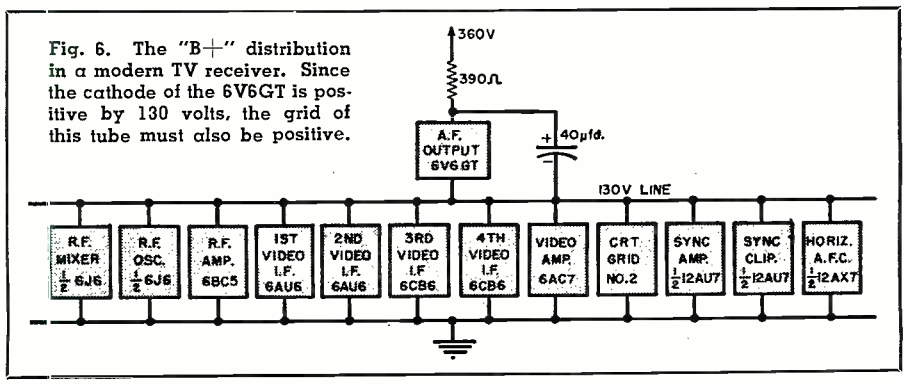


Fig. 6. The "B+" distribution in a modern TV receiver. Since the cathode of the 6V6GT is positive by 130 volts, the grid of this tube must also be positive.

www.americanradiohistory.com



It pays to ask for

"RECTIFIER RED"

the new product-line color for

Federal

MINIATURE SELENIUM RECTIFIERS

FEDERAL—the *original* miniature—has said goodbye to *gray*. The new bloom is "*Rectifier Red*"... a striking color that instantly tells servicemen they're getting the rectifier efficiency and long life that created tens of millions of profit opportunities for radio-TV servicing . . . tells them they're getting the *quality* that keeps Federal miniatures the best-seller in America's vast and growing rectifier replacement market!



Look for "*Rectifier Red*"... get the performance that *clicks* . . . the replacement profit that *sticks*! See your Federal Distributor for Federal miniatures in handy 8-unit kits . . . in quantity lots . . . or in individual packages sold through Federal's self-service rectifier dispenser . . . on hundreds of counters! See *your* "FTR" Distributor now, or write to Dept. F-759-A

"America's first and largest manufacturer of selenium rectifiers"


Federal

Telephone and Radio Company

100 KINGSLAND ROAD, CLIFTON, N. J.


In Canada: Federal Electric Manufacturing Company, Ltd., Montreal, P. Q.
Export Distributors: International Standard Electric Corp., 67 Broad St., N. Y.

www.americanradiohistory.com

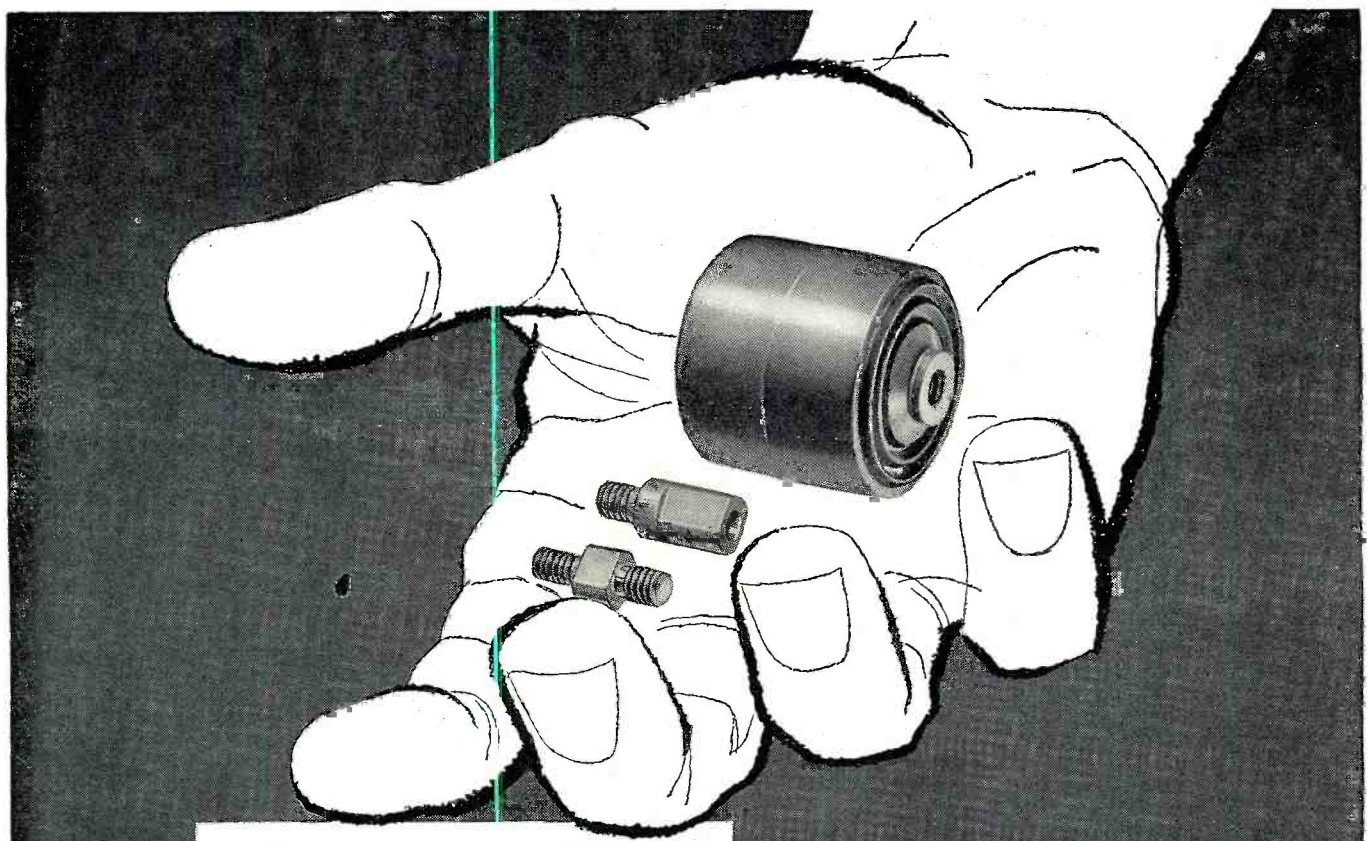

Centralab announces

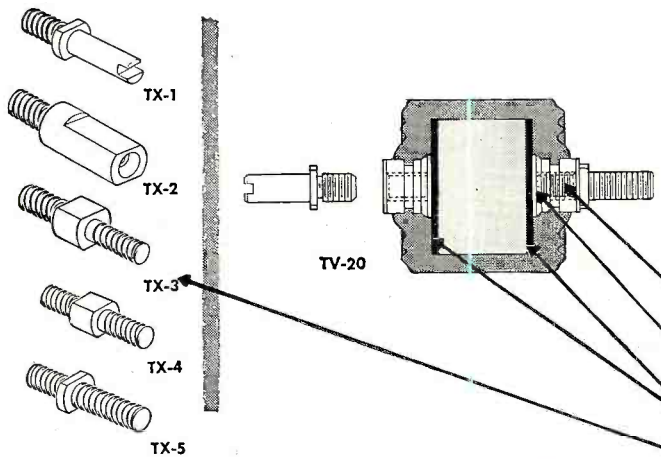Precision Attachable Terminal HI-VO-KAPS®



Again, Centralab research pays off for you. For, now, you get CRL high-voltage capacitors with *precision* attachable terminals that give you positive connections *every time.*

These CRL *Precision* Attachable Terminal Hi-Vo-Kaps withstand continuous overload up to 40,000 v.d.c. They are 100% factory-tested at twice rated working voltage — for maximum safety factor.

The diagrams at the left show other reasons why both you and your customers are money ahead, when you use CRL *Precision* Attachable Terminal Hi-Vo-Kaps:

1. Terminals and taps have heavy 8-32 thread and cannot strip or break off, when terminals are tightened. They lock in place — thus can't loosen and cause voltage breakdown.
2. Terminals seat flat at bottom of tap. There are no gaps between terminals and capacitor body to cause internal corona and "blow-up" of capacitor.
3. Positive mechanical bond between stub terminals and internal electrodes prevents loosening when terminals are attached.
4. Terminals and capacitor body are packaged separately. You don't have to buy five different terminals to get the one you need. You pay only for what you use—save money for yourself and your customers.

Keep a stock of CRL *Precision* Attachable Terminal Hi-Vo-Kaps on hand. See your Centralab distributor. Send coupon for his name and further information on this new CRL development.

CENTRALAB, A Division of Globe-Union Inc.
9108 E. Keefe Avenue, Milwaukee 1, Wisconsin

☐ Send me further information on Centralab's new precision attachable terminal Hi-Vo-Kaps.
☐ Send me name of nearest Centralab distributor.

Name.....

Company.....

Address.....

City.....*Zone*.....*State*.....

Centralab
CRL ®

A DIVISION OF GLOBE-UNION INC.
Milwaukee 1, Wisconsin
804 Mt. Pleasant Rd., Toronto 12, Ontario

www.americanradiohistory.com

Tracing Aid

(*Continued from page 65*)

forms in a system (amplifier, filter, etc.) under test. A tracing of the input waveform is first made, and the pad left in place. The scope is then connected to the output, and the output waveform appears superimposed on the input previously traced on the paper. Direct comparisons are then easily made. Small variations in gain may be observed. Distortion that might otherwise be ignored becomes apparent.

Since the Tracing Aid is basically an aid to copying, its use is not confined to tracing scope patterns. It may be used equally well to make copies of drawings or diagrams, to sketch equipment, etc. It cannot be used to copy written matter, however, due to the inverted image.

To use for copying, simply hang the material in front of the aid, so that it is in about the same position as the scope screen would be. The material should be adequately illuminated.

To use for sketching, place the object to be sketched in front of the aid, on a box or stand. Then sketch the image that appears superimposed on the same pad in the manner that the scope image is traced. -30-

TV SERVICE BENCH REPORTS

By MILTON A. KENNEDY, JR.

MOTOROLA TS-74

A hum, very much like sync buzz, was found in this model. Removing the 6J5GT vertical oscillator tube cleared up the hum. However, replacement of the 6J5GT by another glass-type tube did not help at all. When this tube was replaced with a metal one, the set worked fine.

TRAV-LER 219-8A

After this set warmed up, it began to squeal and the raster left the screen. This trouble was traced to an open filter off the high side of the horizontal tank coil. This filter condenser is approximately 15 μfd.

TELE-TONE TV-333

Attempting to set the brightness control to its fullest range caused very bad tearing in this set. This was remedied by lowering the screen voltage on the horizontal output tube.


HOFFMAN 21" SET

Arcing in the high-voltage cage was the problem on this receiver. This fault can usually be corrected by removing the complete 1B3 socket assembly, and cleaning the socket and porcelain standoff with some solvent. However, in this case, this was not good enough.

Normally, the filament winding of the 1B3 consists of only one loop around the core of the high-voltage transformer. On these sets, however, two loops are used. Removing one of the loops eliminated the arcing and did not appreciably affect the brilliance of the raster.

WESTINGHOUSE H-619T12

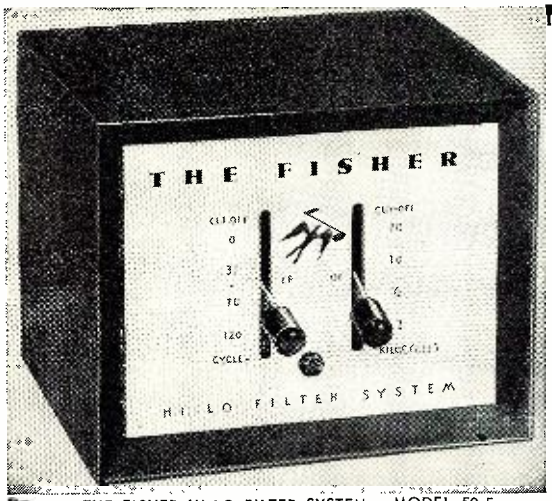This set had an intermittent squeal during which time the raster vanished. A circuit check revealed that the plate (pin 6) voltage of the 12AU7 horizontal oscillator tube was a few volts too low. The defective part was the 220,000-ohm plate load resistor. -30-



THE FISHER HI-LO FILTER SYSTEM • MODEL 50-F

A 'Must' FOR EVERY RECORD COLLECTOR

FISHER

Hi-Lo Filter System


■ Here it is at last—America's first electronic *sharp cut-off* Filter System. Suppresses turn-table rumble, record scratch and distortion, etc., with the *absolute minimum* loss of frequency response. *Separate* low and high frequency cut-offs. Can be used with *any* tuner, preamplifier, amplifier, etc. No insertion loss. Uniform response 20-20,000 cycles, ± 0.5 db. Self-powered. All-triode. Beautiful plastic cabinet. *Only* **$29.95**

FISHER

Preamplifier-Equalizer

■ Now, professional record equalization facilities are within the reach of *every* record collector. THE FISHER Model 50-PR, like its big brother (Model 50-C) is beautifully designed and built. *Only* **$19.95**

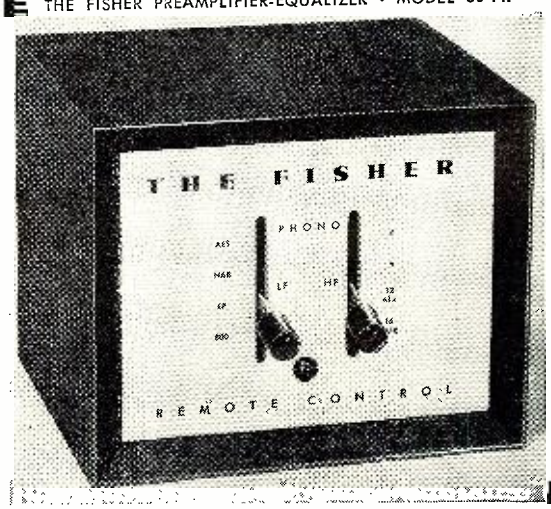THE FISHER PREAMPLIFIER-EQUALIZER • MODEL 50-PR



OUTSTANDING FEATURES

• Independent switches for low-frequency turnover and high frequency roll-off. • 16 combinations. • Handles *any* low level magnetic pickup. • Hum level 60 db below 10 mv input. • Uniform response 20-20,000 cycles, ± 1 db. • Two triode stages. • Full low frequency equalization. • Output lead any length up to 50 feet. • Beautiful plastic cabinet, etched brass control panel. • Completely shielded chassis. • Built-in AC switch. Jewel indicator light.

Write for full details

FISHER RADIO CORP.

39 EAST 47th STREET • N. Y.

www.americanradiohistory.com

LEARN MORE! EARN MORE!
WITH H. G. CISIN'S
SERVICE BOOKS

NEW! 1954 TV CONSULTANT
TV Serviceman's Silent Partner •



New, easy-to-use way to solve toughest TV troubles. UHF sect. includes conversions, installations and servicing. Modern alignment methods shown by pictures, diagrams and simple directions, tell exactly what to do and how to do it. Practical pointers on use of all TV Test Instruments. Over 300 pix, raster and sound symptoms. Detailed directions tell where and how to find faulty parts. Over 135 **RAPID CHECKS**, many using pix tube as trouble locator. 125 illustr. of scope wave forms, diagrams, station patterns, show various defects—take mystery out of TV servicing. **NO THEORY—NO MATH—NO FORMULAS**—just practical service info. covering all types of TV sets.
Only....$2

NEW! 1954 TV TUBE LOCATOR
ALL PIX TUBES LISTED!



Money-making Time Saver tells which tubes to replace to cure every type of tube trouble. Over 135 such TV troubles listed with clear charts for quickly locating the faulty tubes. Copyrighted **TROUBLE INDICATING TUBE LOCATION GUIDES** for over 3000 most popular models from Admiral to Zenith plus **PIX TUBES** used in each model! 1947 to 1953 models. A storehouse of valuable TV servicing info. priced very low for large volume sales. **Only....$1**

NEW! Trouble Shooting PIX GUIDE
incl. TV TERMS Explained

Sect. 1 is a fully illustrated **GUIDE** to oft-recurring pix faults. Causes and cures explained. Copyrighted Trouble Indicating illustrated chart tells where troubles start in typical TV set — illustrations show resulting faulty TV pictures. Sect. 2 explains hundreds of TV terms in non-technical language. **SPEEDS UP TV SERVICING — HELPS YOU DO A BETTER JOB FASTER!** **Only....$1**



NEW! TV TROUBLE TRACER

VOL'S 1 & 2 NOW READY!
70 Common TV troubles traced to source and cured. Copyrighted trouble indicating tube location guides covering over 1200 most popular TV models. Many models different from those shown in TV TUBE LOCATOR.
Each contains over 70 illustrations and tube location guides. Forty most common picture troubles illustrated, with symptoms described, causes given and remedies prescribed.



Vol. 1 ....only 50c **Vol. 2 ....only 50c**

H. G. CISIN, PUBLISHER

Order from your Jobber today, or if not stocked, write to
Harry G. Cisin, Dept. R-2
Amagansett, New York

Enclosed find $..... Send
☐ TV Consultant ☐ TV Locator
☐ TV Pix Guide ☐ TV Tracer, Vol. 1
☐ TV Tracer, Vol. 2

Name .....


Address .....

City .....Zone....State.....

TV ON MT. FUJI

By **KOICHI KASAHARA**
Exec. Dir., Japan Amateur TV Club

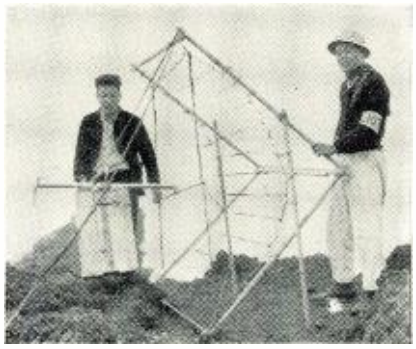Japanese amateurs check signal strengths during unique series of tests held atop Mt. Fujiyama



A parabolic reflector on Mt. Fuji, made by joining several alpenstocks.

LAST summer an interesting TV reception test was made by the Japan Amateur Television Club on top of Mt. Fuji. The test was carried out by fourteen TV amateurs during a three day period from August 2 through 4 in cooperation with the Japan Broadcast Corp. and the Electronics Laboratory of Shizuoka University which handled the transmissions.

Three TV stations of the Japan Broadcast Corp. in Tokyo, Nagoya, and Osaka, and an experimental TV station of the Electronics Laboratory at Hamamatsu took part in the test with special programs transmitted on the same carrier frequency and with the same standards. Such programs were transmitted successively, alternately, and simultaneously from each of the TV stations in order to permit the TV amateurs on Mt. Fuji to study the various forms of interference as well as to enjoy DX television reception at an altitude of 3775 meters (12,-20) feet).

The television stations taking part in the test were JOAK-TV (Tokyo) with an output power of 5 kw.; JOBK-TVX (Osaka) 5 kw.; JOCK-TVX (Nagoya) 500 watts; and JJ3A-TVX (Hamamatsu) 15 watts.


The distances from the stations to Mt. Fuji and the antenna input intensity of the television signals measured on Mt. Fuji are as follows: Tokyo (105 km. or 65 miles) 75 db; Osaka (315 km. or 195 miles) 58 db; Nagoya (108 km. or 67 miles) 21 db; and Hamamatsu (90 km. or 52 miles) 32 db.

Television signals from Tokyo and Osaka were received at practically local level. Nagoya was not received successfully, due, no doubt, to the mountains near the city. Hamamatsu was received much clearer than any of us had anticipated. Station JJ3A-TVX used a two-element doublet beamed directly at Mt. Fuji.

Many interesting results were obtained from the experiments involving interference and further studies are currently being made based on photographic evidence obtained on Mt. Fuji.

During reception lightning was seen in the cloud layers below Mt. Fuji but, surprisingly, noise images, as generally seen at home, were not observed on the *Braun* tubes being used in the tests on Fuji.

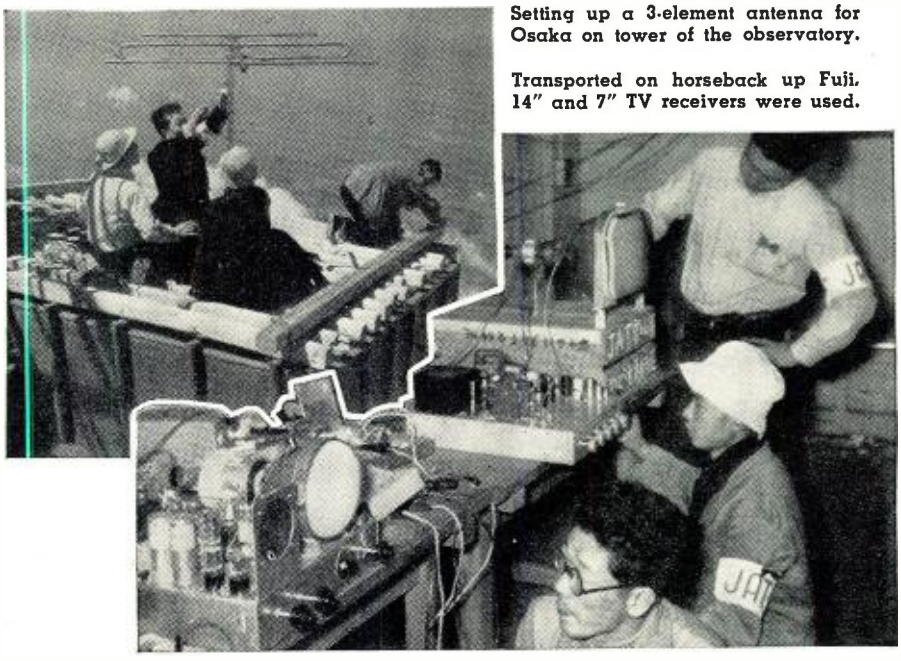Few ghost images due to clouds were observed but a peculiar triple ghost image was observed at night. It was photographed in order to permit further study. —30—



Setting up a 3-element antenna for Osaka on tower of the observatory.

Transported on horseback up Fuji. 14" and 7" TV receivers were used.

www.americanradiohistory.com

Here's your Opportunity



to prepare for a good job or a business of your own in TV SERVICING

ARE YOU SATISFIED with the position you now hold? Do you feel you're worth more money? Are you pleased with yourself, your work, your associates . . and your future? What does the next year hold for you . . . and the year after that?

Are you content merely to plod along through the best years of your life . . . or do you want to get into more pleasant work . . . hold a well-paid job . . . perhaps establish your own business?

If you are looking for a REAL opportunity . If you want to GROW with a GROWING INDUSTRY . . . If you want to grasp the success that should be yours, *then we say to you, study TV Servicing.*

Everyone knows that Television is the fastest growing industry today. Opportunities are going begging for men who have the training and ability to grasp them. *Now is the time to start on the road to success in TV Servicing.*

Study at Home in your spare time

The RCA Institutes Home Study Course in TV Servicing is easy to learn. You progress rapidly, step by step, as you learn the procedure of servicing and trouble-shooting TV receivers and installing TV antennas. Hundreds of pictures and diagrams help you understand the how-it-works information and the how-to-do-it techniques.

A Service of Radio Corporation of America

The RCA Institutes TV Servicing course was written and planned by instructors with years of specialized experience in training men. You get up-to-the-minute information, too, because you study right at the source of the latest developments in Television. Your lessons are carefully examined and accurately graded by competent teachers who are interested in helping YOU to succeed.

RCA Institutes is licensed by the University of the State of New York . . . an affiliate member of the American Society for Engineering Education . . . approved by leading Radio-Television Service Organizations.

It costs so little to gain so much

RCA Institutes makes it easy for you to take advantage of the big opportunities in TV Servicing. The cost of the TV Servicing Home Study Course has been cut to a minimum. You pay for the course on a pay-as-you-learn unit lesson basis. *No other home study course in TV Servicing offers so much for so little cost to you.*

RCA Institutes conducts a resident school in New York City offering day and evening courses in Radio and TV Servicing, Radio Code and Radio Operating, Radio Broadcasting, Advanced Technology. *Write for free catalog on resident courses.*

SEND FOR FREE BOOKLET—Mail the coupon—today. Get complete information on the RCA INSTITUTES Home Study Course in Television Servicing. Booklet gives you a general outline of the course by units. See how this practical home study course trains you quickly, easily. Mail coupon in envelope or paste on postal card.



MAIL COUPON NOW!

RCA INSTITUTES, INC., Home Study Dept. RN254
350 West Fourth Street, New York 14, N. Y.

Without obligation on my part, please send me copy of booklet "RCA INSTITUTES Home Study Course in TELEVISION SERVICING." (No salesman will call.)

Name_____
(please print)

Address_____

City_____ Zone_____ State_____

RCA INSTITUTES, INC.
A SERVICE OF RADIO CORPORATION of AMERICA
350 WEST FOURTH STREET, NEW YORK 14, N.Y.

www.americanradiohistory.com

BARGAINS • BARGAINS • BARGAINS


BARGAINS • BARGAINS • BARGAINS

STANDARD BRANDS **TUBES** *All Brand New Individually Boxed* FAR BELOW WHOLESALE COST!

0Z4	.66	6AC7	1.29	6BG6	1.99	65L7	.96	12AV7	1.14	35Z5	.53
1A7	.87	6AG5	.89	6BH6	.89	65N7	.86	12AX7	1.06	50B5	.84
1B3	.99	6AG7	1.24	6BK7	1.26	6SQ7	.63	12AZ7	1.59	50C5	.84
1H5	.73	6AH6	1.39	6BL7	1.14	6T8	1.09	12BA6	.72	50L6	.71
1N5	.82	6AK5	1.44	6BQ6	1.35	6U8	1.14	12BE6	.78	50Y6	.79
1R5	.79	6AK6	.93	6BQ7	1.49	6V6GT	.71	12BH7	.98	70L7	1.59
1S5	.79	6AL5	.71	6BN6	1.14	6W4	.73	12SA7	.83	80	.59
1T4	.77	6AQ5	.79	6BZ7	1.59	6WH	.91	12SK7	.79	117N7	1.59
1U4	.79	6AQ6	.89	6C4	.66	6X4	.62	12SL7	.99	117P7	1.59
1U5	.78	6AR5	.73	6CB6	.87	6X5	.63	12SN7	.91	117Z3	.64
1V2	.99	6AS5	.83	6CD6	2.59	6X8	1.09	12SQ7	.69	117Z6	.96
1X2A	1.02	6AT6	.71	6H6	.71	7Q7	.71	19T8	1.29		
3Q4	.89	6AU5	1.04	6J5	.63	7F7	.89	25BQ6	1.35		
3Q5	.99	6AU6	.71	6J6	.99	7N7	.87	25L6	.73		
3S4	.77	6AV5	1.09	6K6	.71	7Y4	.69	25W4	.78		
3V4	.82	6AV6	.63	6L6GA	1.39	12AH7	1.18	25Z6	.67		
5U4	.65	6BA6	.82	6SA7	.73	12AL5	.71	35B5	.79		
5V4	.99	6BA7	.99	6SC7	.84	12AT6	.62	35C5	.79		
5Y3	.49	6BC5	.86	6SH7	.86	12AT7	1.07	35L6	.73		
6AB4	.79	6BC7	1.04	6SJ7	.66	12AU6	.77	35W4	.53		
6AB7	.99	6BE6	.74	6SK7	.72	12AU7	.94	35Y4	.74		

SPECIAL DISCOUNTS: 50 Asst } 5% ; 100 Asst } 10%

Wen SANDER-POLISHER

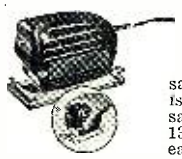

Here is the unit you have been waiting for. Does everything from sanding your car to polishing your shoes. Large sanding area a full 13¾" sq. Lightweight, easy to use. Complete with on-off switch, 6 sheets of sandpaper and polishing cloth. Powerful high speed cool operating motor. Choice of 3 colors: Black, Fire-Engine Red, and Marbled Green. 110-120 Volts, 60 cycles AC only.

List Price.....$13.95
Net Price..... $10.46

$16.99 LOTS OF 3 $17.95 each

Factory aligned ready to use. Complete with tubes and instructions.

CASCODE TUNER

SUPREME TESTERS



Model 600 — Tube & Set Tester ... $64.95

Model 616 — Tube & Battery Tester ... $49.95

MINIMUM ORDER $5.00

SEND FOR OUR LATEST CATALOG

Order by Phone: COrtlandt 7-0086

Order by Mail: Dept. N-2, 61 Reade St., New York 7, N.Y.

WEN ELECTRONIC SOLDERING GUN

250 Watts.

Choice of red, green, black



Lots of 3 $8.64 $9.71 each

STEVE-EL ELECTRONICS CORP.

Dept. N-2 61 Reade St., New York 7, N. Y. COrtland 7-0086

Crystal Clear Pictures like MAJIC with amazing CLEAR-PIX FILTERS





HIGH REJECTION EFFICIENCY

- **Scientifically designed with proven HI-Q circuits**
- **Low cost**
- **Easy to install**

Most of the 26 million TV sets now in use suffer from some type of interference. What a tremendous market to exploit! Save your customer discomfort and eyestrain . . . boost your reputation as a technician . . . boost your profits! Recommend and install GRAYBURNE CLEAR-PIX filters. There's one for each type of major interference.

Model #	Interference
CPF	FM
CPD	Diathermy
CPI	Ignition
CPH	Amateur (21 mc.)

BE PREPARED: Carry several of each model in your service kit at all times to cash in on handsome profits.

1.98 LIST **ORDER TODAY** from your local dealer.

successor to Grayburne Corp.

ELECTRONICS CORP. **Superex**

23 Atherton St., Yonkers, N. Y.

FASTER EASIER more PROFITABLE operation

GET INTO THE MASTER HABIT!

RADIO'S MASTER NEW! 1954 EDITION

- 1370 pages
- Over 85,000 items
- Over 8,000 illus.
- Completely indexed

$1.95 at your parts distributor. Publisher's price $6.50

Have complete access to the many thousands of products vital to your daily sales and service operations. In the customer's home, across the counter or on the bench, you'll value the Master's thoroughly complete descriptions, specs, illustrations and prices . . . all systematically organized in 18 big sections for instant reference. Increase your sales . . . sell directly from the Master. Facilitate your stock problem . . . use the Master for jiffy comparison of all electronic products. The Master is the only Official Buying Guide for the TV-Radio-Electronics industry. It contains unabridged catalog data direct from the manufacturers. For buying and selling — the Master gives you all the needed facts in a single volume.

Over 100,000 in active daily use. Get into the Master habit. Order your copy today!

Just a few of the products included: Tubes — Test Equipment — Tools — Transformers — Capacitors — Resistors — Relays — Coils — Attennas — Recording & PA Systems — Hardware — Transmitters — Receivers — Kits — Wire — Cable . . . and thousands of allied products!



Eliminate Incomplete Small Catalogs and Loose Literature

UNITED CATALOG PUB., INC.

110 LAFAYETTE ST., NEW YORK 13, N. Y.

The Scott 99-A

(*Continued from page 67*)

those recording curves in widest use. A very widely used equalization curve for LP records is the original one introduced by *Columbia*. This curve uses more bass and treble pre-emphasis in recording than most and therefore requires less bass and treble compensation in playback. This curve was included in the 99 equalization.

On any professional instrument, such as the 99, it is necessary to make provision for older and foreign records, so the curve marked "EUR" in Fig. 3 was added to the equalization. This curve has a turnover of approximately 250 cycles and a flat high-frequency response.

The AES and new NARTB curves are also widely used. These curves are very similar except in extremely low frequency response. Since each curve is specified to an accuracy of ± 2 db, each curve falls within the tolerance limits of the other. It is therefore possible to draw a single curve falling within these tolerances over practically the entire range of equalization. This combined curve was provided in the equalization, and it is entirely adequate for playing recordings made for either the AES or NARTB curve. (The *RCA* "New Orthophonic" curve is the same as the new NARTB). Since both turnover and roll-off equalizer controls have three positions, a total of nine record compensation curves is possible. For example, a combination of the *Columbia* turnover with the AES roll-off provides an almost exact match for *London* records. Similarly, the "EUR" low-frequency equalization used with the LP high-frequency response provides a perfect match for old 78 rpm *Columbia* shellac records. Table 1 gives a chart of equalization settings for many records. Further compensation for conditions such as pickup response, speaker response, speaker enclosure characteristics, room acoustics, and personal preferences may be obtained easily with the wide-range treble and bass tone controls.

These tone controls are continuously variable throughout their range and each provides either wide-range boost or attenuation of the response. The maximum treble boost or cut is ± 20 db, while the maximum bass range of the control is ± 15 db. These specifications are in addition to the progressive boost provided by the automatic loudness control.

Complete and continuous adjustability of the loudness compensation itself is an interesting feature. The automatic loudness control, of course, compensates for the human ear's insensitivity to extremes of treble and bass at low listening levels. This is done by progressively boosting the treble and bass response as the volume control is turned down. To maintain satisfactory tonal balance, treble loudness compensation is necessary

www.americanradiohistory.com

SCOOP of the Month!~

BC1267 Transmitter and Receiver

154 to 186 Mcs., 1KW pulse oscillator, superhet circuit, 2 RF stages, and 5 stagger tuned IF's, includes 21 tubes; 2C26(2), 3E29/829B(1), 6AG5(7), 6C4(1), 6E5(1), 6H6(1), 6AK5(3), 6J5(2), 6SN7(1), 6V6(1), 9006(1); can be easily converted to 2 meter converter and outboard amplifier, ship. wt. 75 lbs., complete with conversion instructions (NOTE: 3E29/829B is worth $10.00 alone).

excellent condition $14.95 (less tubes) **with 21 tubes $24.95**



BROADCAST BAND and AERO

Ideal for Use in Boats, etc.

MN-26-C Remote Controlled Navigational Direction finder and communications receiver. Manual DF in any one of three freq. bands, 150 to 1500 KC. 24 V. Self contained dynamotor supply. Complete installation, including receiver, control box, loop, azimuth control. Left-Right Indicator, plugs, loop transmission line and flex. shafts.

ALL UNITS BRAND NEW EXCEPT CONTROL BOX $69.50
MN-26-Y 150 to 325 KC, 325 to 695 KC, 3.4 to 7 megacycles, comp. installation 49.50
MN-26-C alone, like new 24.95
MN-26-Y as is less tubes 4.95
MN-20-E Loop. Brand New 6.95
MN-52 Crank drive, New 2.50
MN-26LB Receiver exc. freq. 150-1250 KC. 2.9-6mc 59.50

Low Freq. Crystals—FT 241 A for SSB, lattice filter, ½" spc. 54th harm channels listed by fund. Fractions omitted.

370	388	407	425	444	462	481	501
372	390	409	427	446	464	483	503
374	392	411	429	448	466	485	505
375	394	412	431	450	468	487	507
377	396	414	433	451	470	488	509
379	398	416	435	453	472	490	511
381	400	418	437	455	474	492	512
383	401	420	438	457	475	494	514
385	403	422	440	459	477	496	516
387	405	424	442	461	479	498	

49c each 10 for $3.00

BC-906 ABSORPTION-TYPE FREQ. METER

Freq. range 150-225 Mc. Uses 0-500 DC Microammeter for indicator. In black crackle carrying case with handle. 12½x8¾x6½". Net 18 lbs. With tubes and calibration chart. New **$9.95**

POWER YOUR RIG FROM AC

RA-34 RECTIFIER. Makes a ground xmtr of BC-191, the 12V version of BC-375-E. Convert BC-375-E to 12V by changing heater link switches and relay connections, power it with RA-34. Input 105-125 or 210-250V, 60 cy. Outputs: For plates, 1000V filtered dc at 350 ma; for relay and mike, 12V filtered dc at 2.4 A; for heaters, 12V ac at 14.25 A. Used condition. F.O.B. **$159.75**

BC-433 RADIO COMPASS RECEIVER

200 to 1700 KC, used, excellent condition less tubes $19.95
used, as is, less tubes and cover, excellent for parts only $6.95

VHF TRANSCEIVER

Ideal substitute for SCR-522, freq. range 140-144 mc, crystal controlled, 10 watts. The receiver section has two individual RF sections, feeding a common 3 stage 10mc IF amplifier. Both RF sections may be operated simultaneously, or either one individually. The receiver unit has 13 tubes. The transmitter is of straight forward design. Transmitter unit has 7 tubes, one #832 as final modulated by a pair of 6L6 and push-pull. Complete unit in case less tubes, and diagram less dynamotor.
EXCELLENT CONDITION **$9.95**
WITH TUBES $19.95

A SWEET OSCILLOSCOPE DEAL

ASB-7 Radar Indicator Unit: For conversion to test scope or for use as modulation monitor. Has standard test-scope CR tube. H Cent, V Cent, Bril, Foc, Gain, and range selection switch. External power source was used. Tubes: 4-6AC7, 3-6H6, 1-5BP1. Condition good. NEW **$9.95**

Hundreds of items in stock. WRITE FOR NEW BULLETIN AND PRICES. Shipments F.O.B. warehouse. 20% Deposit on orders. Minimum order $5.00. Illinois residents, add regular sales tax remittance. Prices subject to change without notice.

BC-620 TRANSMITTER-RECEIVER UNIT

FM transmitter-receiver, crystal controlled, two channels, freq. range 20-27.9 mc. 13 tubes, dual meter for testing filament and plate circuits. **$39.25**

BC-929-A

Contains power supply 110 V. 400 cycles, has 7 tubes such as 3CP1, brand new, complete with tubes. Each **$19.95**

BC-746 TUNING UNIT

Plug-in transmitter tuning unit from Army Walkie-Talkie. Contains antenna and tank coils, tuning condenser, transmitting and receiving crystals. Ideal transmitter foundation ..... ONLY **$1.29**

ID6/APN4

Made to operate in conjunction with Radio Receiver R-9( )/APN-4. Unit includes 19 tubes, one 5" scope tube, crystal controlled standard oscillator, sweep circuits, marker pulses. Excellent cond. **$42.50**

MIKES and HEADSETS

T-26 Telephone chest unit with F-1 Western Electric Transmitter $2.39
HS-33 Low Impedance Headset ..... exc. $2.95 new $5.45
HS-23 Headset used 1.89 new 4.50
CD-307 Ext. cord for HS-23-33 ..... like new .79 new 1.29
Throat Mike—T-30 ..... new .98
Lip Mike—Navy Type ..... new .98
CW-49505 High Impedance headset complete with headband ..... Used **98c**
T-45 Lip Mike. New $1.75
HS-30, miniature headset. Used $1.49, new 2.49



WOBULATOR

BUILD TV-FM-AM SWEEP GENERATOR

You can build "Versatile Sweep Frequency Generator with APN-1 magnetic units ... $ 5.95
BC-1206 Beacon Receiver . . . 200-400KC. 9.95
TS-184/AP Test Set 39.50
IE 19A-SCR522 Test Unit 295.00
I-222-Signal Generator ..... Used, exc. 95.00

R. F. MODULATOR

Complete tunable 205 mc Test Set. With 110 V., 60 cps, power supply, 3-stage audio amplifier, terrific chassis for experimentation, good condition **$8.95**

TU 8, 9 or 10—Tuning Unit for BC 375—used, good cond. **$1.95**

11 TUBE UHF TUNABLE RECEIVER 234-258 mc, less tubes **$7.95**

RA-52 RECTIFIER

Transtat controlled to produce high voltage DC from 110 VAC 60 cycle source. Up to 11,500 VDC @ 50 W. Metered high voltage (0-15 KV) and current (0-20 MA). Exc. $69.95

	As Is Less Tubes	With Tubes	New
BC-454 3 to 6 mc	—	$11.95	—
BC-455 Receiver, 6 to 9 mc	—	9.95	—
BC-456 Modulator	$2.95	4.95	$7.95
BC-458 Transmitter, 5.3 to 7 mc	2.95	—	—
BC-459 Transmitter, 7 to 9 mc	7.95	—	—

Control Boxes, racks, receivers for above in stock—write.

MG-149F excellent condition ..... $ 89.50
MG-149H excellent condition 129.50
MG-153 Inverter (3 phase) ..... Used 89.50

P-206, inverter, like new $11.95
PE-218, inverter, excellent condition 24.95

BC-640 ..... $695.00
BC-639 with RA 42 rectifier 225.00

NATIONALLY ADVERTISED TUBES

5BP1 ..... $3.95 5AP1 ..... $3.95
All Brand New in Original Cartons
304TL ..... $5.95 720DY $29.50
808 ..... $1.95

QUANTITY PRICES AVAILABLE!
1625, 1626, 33, 34, 954, CK1005, 6Z7G, 9002, 9006, 1619, 955, 9004, 12A6, 1F4, 1F5, 211, 6F5, 1A6, 1629, 19, 50.

10 for $3.00

RT7/APN-1 TRANSCEIVER UNIT—Used as an altimeter, it may be converted for signaling control circuits, etc. Used, less tubes, as is **$4.95**

RT/34 APS 13 TRANSCEIVER—Used as a tail warning radar on 415 MC. Containing a 30MC IF Strip and various other parts, these units have been stripped of RF sections and all tubes, but are an excellent buy if only for parts and IF Strip. Used **$4.95**

BC 906 FREQUENCY METER—Range 150-225 MC with modification possible for lower frequencies of TV, etc. Contains 0-500 DC microammeter and uses Battery pack of 1.5 V and 45 VDC **$4.95**

R-1/ARR-1—220 MC converted with minor alterations becomes a high gain converter with two stages of RF amplification—(complete with diagram). New **$4.95**

ALL FOUR ABOVE ITEMS FOR $10.00

BEAM ANTENNA SELSYN TRANSMITTER and indicator, per set **$12.00**
BC-684 FM Transmitter, 27-38 mc, used, ec. **$14.95**
BC-604 FM Transmitter, 20-27 mc, used. exc. **$11.95**

LOOK WHAT YOU GET FOR $14.95

- 350 feet of continuous length of 50 ohm coaxial cable
- 100 feet of same coaxial cable
- Cavity type attenuator
- 6 Short lengths of RG8U with connectors and sockets
- In wooden case—shipping weight 30 lbs.—all for $14.95

BC 347 Interphone Amplifier $2.95
I-70 Tuning Meter ..... .89
APS 13 UHF Antenna, Pair ..... .98
I-97 Bias Meter $3.95 4.95
RL 42 Antenna Gearbox Motor and Reel 1.95
BC 1066 B—150 to 225 MC Portable Receiver adaptable to many amateur uses. Used $5.95
One Tube Interphone Amplifier—Small compact aluminum case fully enclosed. 2¼"x3¾"x5¾". Less Tube 79c
BC 709 Battery operated lightweight interphone amplifier. Complete with tube and shock mount, but less battery ..... New $3.95

DYNAMOTORS

DYNAMOTORS: The best dynamotor for conversion to 6v. Multiple windings! After conversion you get choice of 190 or 350 v. at 50 MA or 250 v. at 100 MA. Complete dope sheet furnished. BRAND NEW (See "CQ" Aug. issue) **$4.65**

DM-28—Dynamotor for BC-348—28V DC at 1.25 amps in 220 V at 70 MA output Good $4.95
DM-32A—Dynamotor for Command Receiver 28V at 1.1 input 250V at 60 MA output ..... Used 2.95 New 7.50
DM-33—Dynamotor for Command Transmitters—Used $2.95
D-101 Imp. 27V 1.75 Amp. output 285 VC .075 amp ..... each $1.95
3 for $5.00
PE-94 ..... each $1.95
PE103—6V Dynamotor ..... Used $22.95
BC-1033 62-80 mc recvr. Like new, less tubes ea. $5.95
BC-1023 brand new with tubes 9.95

SCR-625—FAMOUS ARMY MINE-DETECTOR

For Prospectors, Miners, Oil Companies, Plumbers, etc. This unit is being offered now at a considerable reduction in price. Recently advertised at $79.50 it is now available in the same brand new wrappings in suitcase style carrying case (less batteries). New **$59.50**
SCR-522—Transceiver, complete in case with top bracket, less tubes **$29.95**
RU-19—Receiver. Complete control box and coils—brand new ..... ea. **$17.95**

BUY NOW! R W ELECTRONICS Dept. N, 2430 S. Michigan Ave., Chicago 16, Ill. PHONE: Calumet 5-1281-2-3 **BUY NOW!**

www.americanradiohistory.com

Did you hear?



Centralab
has
Something New
in high-voltage
ceramic
capacitors



See the
announcement by
Centralab
®
on page 118
in this issue

as well as compensation for bass tones, if a "boomy" effect is to be avoided at low listening levels.

It should be pointed out that the loudness compensation provided in the 99 is based on extended listening tests by juries of listeners rather than upon blind application of the *Fletcher-Munson* curves. Using a variety of program material, the listeners were allowed to adjust calibrated variable condensers until the music sounded best to each listener. These adjustments were made at many different volume levels. The tests, over a period of months, were statistically correlated so that subsequent analysis provided loudness compensation curves with contours and degrees of compensation most pleasing to the human ear. This was particularly important because the attempts, in some loudness controls, to provide extreme *Fletcher-Munson* compensation had almost caused loudness compensation to fall into disrepute through the invalid application of the *Fletcher-Munson* effect.

For broadcast and recording applications, of course, little or no loudness compensation may be required or desired. The loudness compensation may be continuously adjusted or entirely removed by proper settings of an input level control in conjunction with the loudness control. This input level control also permits compensation for the different outputs of various commercial pickups. For example, to remove loudness compensation entirely, the loudness control may be turned to a high value thereby removing compensation from a circuit. Volume is adjusted by the level control which functions as a simple volume control.

An input selector switch is also provided. This allows ready selection of "Tuner," "Phono," "TV," "Tape," or other channels. Separate input jacks are provided on each input circuit. In addition to the usual constant-velocity "Phono" input for magnetic pickup cartridges, a constant-amplitude input is provided for FM pickups. The constant-amplitude input is obtained with a differentiating network which matches the constant-amplitude pickup to the normal constant-velocity response of the preamplifier circuits.

On the underside of the chassis, input jacks are provided for connection of an accessory "Dynaural" noise suppressor, such as the Type 111-B. The "Dynaural" noise suppressor virtually eliminates high-frequency record scratch and low frequency turntable rumble, without eliminating music components which are audible to the human ear. The patented "Dynaural" noise suppressor should not be confused with fixed filters, since these latter eliminate audible musical frequencies under all conditions where undesirable noise and rumble are eliminated. The dynamic rumble suppression feature is particularly important with wide-range systems which include extended bass response speakers. All but the very best professional turntables are susceptible to some rumble, and sometimes rumble is actually recorded on records. Under such conditions, dynamic rumble suppression can increase listening pleasure without loss of any low bass musical tones. The inputs for the noise suppressor may also be used for dubbing records on tape while continuing to monitor through the normal sound system.

Speaker output terminals of 4, 8, 16, and 500 ohms are provided, allowing use of virtually any speaker or professional line-impedance conditions. A separate a.c. power outlet is provided on the rear of the chassis for powering accessory components such as turntable, tuner, etc. The power supply operates on 105 to 125 volts, 50-60 cycles. A "Slo-Blo" fuse provides circuit protection but prevents fuse burnout as a result of normal a.c. line transients.

It is believed that this new amplifier will be a significant contribution to professional music reproduction since the 99 exceeds all FCC requirements for FM broadcasting station performance. While its circuits are similar to those of previous *H. H. Scott* amplifiers, the over-all electronic and mechanical design is completely new and of rather remarkable simplicity. In design, construction, appearance, and performance, the 99 meets, in every respect, the amplifier standards established by its manufacturer. —30—

SNAP-ON GROUND CLAMP


By ARTHUR TRAUFFER

THOSE Gibson "gripper clips," which sell for 10c each at many hardware stores, make handy radio ground clamps for experimenters, or for use with portable radios, etc. You simply snap the clip onto a cold water faucet, or onto an unpainted water or gas pipe, and then pull the clip off again when you are through.

As shown in the photograph, fasten a binding post in the mounting hole on the flat side of the clip, and then connect your ground wire to the binding post. The binding post also serves as a handle for snapping the clip onto the pipe and for pulling it off again.

These clips are made in two sizes, and with chrome finish or black finish. The chrome finished clips are best for use as ground clamps. —30—

A simple and inexpensive ground clamp.

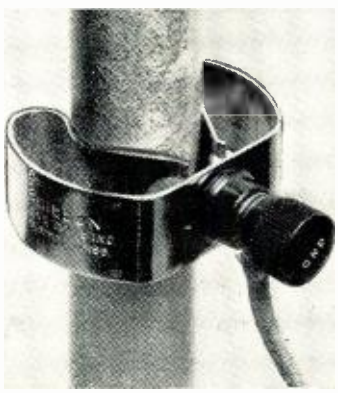

www.americanradiohistory.com

ference from other stations is fairly high. It is common, in such cases, to be able to hear interfering modulation in the background. However, it was said, the continuity of the program will usually enable the listener to follow the correct station unless the interference is drastic. Such coverage will be found to be usually considerably less than that of any signal station; and this is a high limitation.

In rural areas, coverage may or may not be intelligible, depending on the particular situation. This coverage aspect, it was noted, is of greatest importance in metropolitan areas, where the population density makes it imperative that every means possible be used to avoid mass panic and provide instructions for the movements of large numbers of people. Civil defense organizations will use the Conelrad system to give evacuation instructions in case of an attack.

When the Conelrad rules were originally issued, the Commission said that all FM and TV stations would have to go off the air, when the alert is sounded. Now, it has been reported that the FCC has not permanently shut the door on FM or TV sign-off. If someone can prove to the Commission's satisfaction that the operation of the high-frequency stations will be safe during *C* operation, it will revise the rule. To date, there has been no safe method devised to permit such operation, as with standard stations.

TV SATELLITES OR BOOSTERS, or both, may soon appear on the broadcast scene, in communities where it has been found economically unsound to install even small stations and where reception from any neighboring station has been found to be impossible. A manufacturer and a broadcaster have petitioned the Commission for permission to operate such stations on a regular basis. It was noted that the booster permits transmission of programs from the master station on the same channel, while satellites retransmit programs on different channels.

In support of its request, the broadcaster who wants the booster grant, said that there are hundreds of additional markets with channel assignments not adequate for even the smallest station. It was pointed out that during the latter part of the year, the table of assignments showed that there were 1283 cities; no applications were pending or grants made to around 900, or about 70 per-cent. Of that number, it was said, over 500 were in areas of less than 10,000 population, over 200 in zones with cities of between ten- to twenty-thousand, and about 100 in areas with populations over 20,000. The petitioner then said that, according to TV market reports, there are only 112 markets in the country with populations of at least 35,000 or more

Here's how
RCA INTERMATCHED COMPONENTS
take the mystery out of High Fidelity



RCA Intermatched High-Fidelity cabinet and enclosures house any selection of components you may choose.

If you're interested in high fidelity . . . interested in the beauty of music, beautifully reproduced, but confused about how to select the system you want . . . here's how you can have everything you want in high fidelity *plus the assurance of the RCA name on every component in your system.*

Here is professional-grade equipment—bearing the best known name in professional sound—designed to bring the concert hall and the recording studio into your home. Here is RCA's broad background in acoustics and professional sound reproduction in equipment selected to meet your needs, your taste in high fidelity, and your budget.

• • •

In RCA's broad line you can find an almost limitless number of combinations—and the *one* combination you want. Because these units are all *intermatched*, you can develop your own system without a technical background—without fear of mismatch at any stage. It's the easy way to choose . . . it's the sure way to get what you want in high fidelity.

Work out any system you want—Select from these typical combinations—or plan your own

HEAR THEM AT YOUR RCA ELECTRONICS DISTRIBUTOR'S

			TUNERS		AMPLIFIERS			SPEAKERS		
	Record Changer (SRC-51)	Pre-Amplifier (SV-1)	ST-1	SVT-1	SVP-10 (10-watt)	SP-10 (DeLuxe 10-watt)	SP-20 (DeLuxe 20-watt)	SL-8	SL-12	LC-1A
Quality record reproduction at low cost	X				X			X		
Quality record and radio reproduction at low cost	X		X		X			X		
Extended range record reproduction, medium price	X	X				X			X	
Extended range record and radio reproduction, medium price	X			X		X			X	
DeLuxe quality record reproduction	X	X					X			X
DeLuxe quality record and radio reproduction	X			X			X			X

"Professional-Grade" High Fidelity from RCA—
LEADER IN SOUND

RCA®

RCA Engineering Products
Dept. B222, Building 15-1, Camden, N. J.

☐ Please send me your new, free booklet on RCA Intermatched high-fidelity equipment.

☐ Please send me information on the new complete RCA high-fidelity "Victrola"® phonographs.

Name_____

Address_____

City_____ Zone____ State____

RADIO CORPORATION of AMERICA

www.americanradiohistory.com

What can you believe in Antenna Claims?


Every claim for all-channel antenna performance should be supported by facts—not "sales talk." Facts are what you get from DAVIS ...proof furnished by Microwave Engineering Company, of Los Angeles, who are recognized experts on antenna research and testing.

Write for this data. It's actually certified... data you can count on.

Remember, it's the picture that pays off in customer satisfaction. A DAVIS picture must please you—it's guaranteed to please or your money is refunded by the factory.

Send the coupon for facts on the DAVIS antenna.

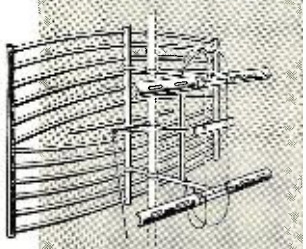"22 DB GAIN"
"OUTPERFORMS ALL OTHERS"
"Guaranteed reception"
"...most sensitive all-channel antenna"




DAVIS SUPER-VISION
COPYRIGHT 1958
DAVIS ELECTRONICS
P. O. BOX 1247 • BURBANK • CALIF.
Factories in BURBANK, CALIF., CHICAGO, ILL., SILVER SPRINGS, MD.

MAIL THIS COUPON TODAY:
DAVIS ELECTRONICS, Box 1247, Burbank, Calif.
Gentlemen ... send me the following:
☐ *Technical data and complete information on the new SUPER-VISION ANTENNA*
☐ *Name and address of NEAREST JOBBER*
COMPANY NAME
MY NAME
ADDRESS
CITY STATE

ATLAS RADIALS

FOR CHURCHES
FOR FACTORIES

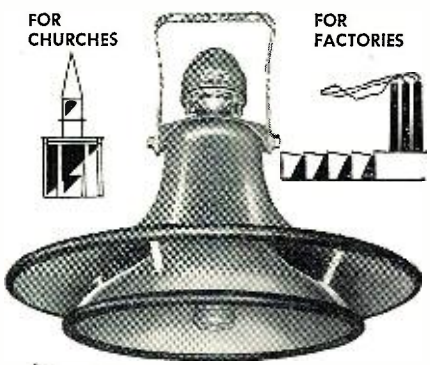

FOR TERMINALS
FOR CARNIVALS

With uniform 360° coverage, non-resonant construction, and 100% storm-proofing, ATLAS Radial Driver Unit Projectors often solve the most difficult sound problems—are excellent for reproduction of speech, chimes and music. For complete details on Radials and the famous ATLAS line of Public Address and Microphone Stand Equipment ...

WRITE NOW for FREE Catalog 553

ATLAS SOUND CORP.
1446 39th St., Brooklyn 18, N. Y.
In Canada: Atlas Radio Corp., Ltd., Toronto, Ont.

SPECIAL VALUES

783 Output Power Meter General Radio. Like New	$225.00
3200-3370 mc. Like New	400.00
LR-1 Signal Generator 160-30,000 KC. 115VAC-60 cy. with xtal calibration. Exc.	1,000.00
Model 228X Hickok Universal crystal controlled Signal Generator. Like New	125.00
Model 200C Hewlett Packard Audio Generator. Exc.	100.00
Du Mont 208B Oscilloscope. Exc.	125.00
Model 230 Clough Brengle AC Cap. & Res. Turns Ratio Bridge. Exc.	45.00
Type 726A General Radio Vacuum Tube Voltmeter. Exc.	125.00
804C Federal or General Radio Signal Gen. 8-330 mc. Exc.	300.00
BC-221 or LM Freq. Meter. Exc.	99.50
BC-221AK with modulation. Exc.	150.00
General Electric Dual Regulated Power Supply Type ST9A. New	300.00
Type 724A Precision Wavemeter General Radio, 16 KC. to 50 mc. Exc.	175.00

A LARGE STOCK OF ARC-1, AIC-3, ART-13, APN4A, APN4B, APR4, ARB, BC-312, BC-342, BC-348, BC433G, BC-611, BC-1306, CRT-3, 1j6A, I222, IE-19A, IE-35A, IE-36A, SCR-284, SCR-522, SCR-578, SCR-625, TCS, T19/APQ5, TS-34/AP, TS-100/AP, TS-184/AP, 14C, Plugs and Selsyns. PUR*

Kay Electric Mega-Sweep. Exc.	250.00
Kay Electric Mega-Pipper. Exc.	100.00
Boonton Q Meter 160A 50KC. to 75MC. Exc.	400.00

* PUR—Price upon request.

WANTED

All types of radio and electronic surplus. We especially need: APA10. APN9. APR4. ARN4. ARC1. ARC3. ART13. ATC. BC221. BC342. BC348. BC611. BC721. DY12. DY17. I100. LM10 to LM18. MG149F. MG149H. PU14. R5/ARN7. R5A/ARN7. SCR718C. TCS. TN16. TN17. TN19. TN54. TS3. TS12/AP. TS33. TS35. TS45. TS75. TS76. TS102. TS147/UP. TS148/UP. TS173. TS174. TS175. TS250. TS251. TS323. 1CT. 1F. 1G. 5CT. 5DG. 5F. 5G. 6DG. 6G. 115V. 60 c.n.s. Selsyns), and all types of Hewlett Packard. General Radio Co.. Measurements Corp.. Boonton Radio. Ferris. Leeds & Northrup. and other test equipment.
Please state accurate description, condition, and your lowest price. Explain modification, if any. We pay freight charges.

NEW CATALOG NOW AVAILABLE

PHOTOCON SALES

417 N. Foothill Blvd. SYcamore 2-4131
Pasadena 8, Calif. RYan 1-6751
CABLE: Photocon, Pasadena.

in a 50-mile radius. which are useful to national advertisers. Since a minimum investment of $100.000 must be made for the smallest station, the broadcaster added, an operator will find it impossible to amortize this expense and survive in the remote areas without national advertising support.

The broadcaster asked the Commission to approve operation of subsidiary stations, with power output of 10 watts at 300-foot average antenna elevation for low ultra-high stations; 31.6 watts for high v.h.f. stations; and 100 watts for upper ultra-highs; all for unattended systems using vertical polarization. The boosters would be required to have automatic power shut-off facilities and provide identification only at sign-on and sign-off.

The satellite proponent declared that his system offered more freedom of program selection. This argument has won the support of Rep. Bush who declared that such flexibility was important. In addition, he said, the use of specially-approved channels for the satellites on low power, would remove the problem of interference that could obtain on mother-station operation using the same channel.

The Congressman also went on record not only urging the approval of satellites but their use in place of community systems, which he called unreliable. For over a year the Commission has been probing the exact place of the community system in the broadcasting picture, and as reported in earlier columns even Congress has taken a lively interest in the matter.

Either the boosters or satellites could be built for between ten and twenty-thousand dollars, applicants declared, and the maintenance costs would be very low.

Both the broadcaster (WSM, Nashville) and manufacturer (KG2XDU-KG2XEL owned by *Sylvania*—channel 82) are operating their systems experimentally and with substantial success, it was said.

INDUSTRIAL MOBILE radio makers and potential users are making a bid for a portion of the FM band in an effort to expand two-way service facilities. The request, to be filed with the Commission, is being prepared by a committee on manufacturer's radio use of the National Association of Manufacturers.

According to a spokesman of the NAM, the re-allocation of the FM band is now simply a question of when, and not whether. This drive has been prompted by the apparent declining use of the FM bands for broadcasting; members of the Commission had warned broadcasters that unless they took a more active interest in FM, others would seek slices of the band. Only a few weeks ago, Commissioner Webster reviewed the seriousness of this situation.


Commenting on NAM's concern for more bands, the association spokesman added: "The Commission now has outstanding proposals in the mobile field

www.americanradiohistory.com

I'll Train YOU at Home in Your Spare Hours for Big Pay Job • Your Own Business • Exceptional Opportunity in

RADIO-TELEVISION

ON *New* NO-OBLIGATION PLAN!

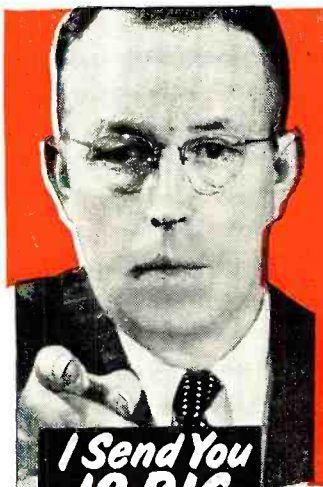

I Send You 18 BIG KITS OF RADIO-TELEVISION EQUIPMENT



Approved for Veterans Under the G. I. Bill

You Have NO MONTHLY PAYMENT CONTRACT

to sign . . . you pay for your training as you learn and earn . . . ENROLL NOW!

Be Ready in Little as 10 MONTHS!

Now you can get into Radio-Television, today's fastest growing big money opportunity field, in months instead of years! My completely new "package unit" training plan prepares you to qualify as a Radio-Television Technician in as short a time as 10 months, or even less! I offer you my training with no monthly payment contract to sign—thus NO RISK and NO OBLIGATION for you! This is America's finest, most modern and really practical training. Includes FM . . . UHF Television and all the most recent developments. My training gets you ready to handle any practical job in the booming Radio-Television industry. Start your own profitable Radio-Television Service Shop . . . or accept a fine paying job. I have trained hundreds of successful Radio-Television technicians—and I can train you regardless of lack of previous experience. Mail coupon and get all the facts—FREE!

VALUABLE EQUIPMENT INCLUDED WITH TRAINING

Much of your Sprayberry Training is actual construction, demonstration and experimentation. You get priceless practical experience this way. You build the 6 tube Sprayberry Short Wave and Broadcast Training Radio Receiver, the Sprayberry Television set, multi-range test meter, signal generator, signal tracer, cathode ray oscilloscope and many other projects. All this equipment is yours to keep. You have practically everything you need to set up your own profitable Radio-Television shop. All lessons and books I send you remain your own property.

OUR 21st YEAR TRAINING MEN FOR RADIO-TELEVISION

Earn Extra Money While You Learn

All your Sprayberry Training is given IN YOUR OWN HOME during your free time. Keep on with your present job and income while learning Radio-Television. With each Sprayberry "Package Training Unit" I include money-making plans and special "Business Builders" for spare time Radio-Television service jobs. New Television stations opening everywhere open big money opportunity for men to install UHF antennas—I tell you how! If you expect to be in the Armed Forces later, there is no better preparation than Radio-Television. Mail coupon below . . . get facts FREE. *No salesman will call.*

FREE TO YOU 3 BIG RADIO-TELEVISION BOOKS

I invite you to get all the facts—

I want you to have ALL the facts—without cost! Rush coupon for my three big Radio-Television books! "How to Make Money in Radio-Television" PLUS my new illustrated Television Bulletin PLUS an actual sample Sprayberry Lesson—ALL FREE. No obligation and no salesman will call. Mail coupon NOW!

SPRAYBERRY ACADEMY OF RADIO
111 NORTH CANAL STREET, DEPT. 25-F
CHICAGO 6, ILLINOIS

IF YOU ARE EXPERIENCED IN RADIO

Men already in Radio who seek a short intensive 100% TELEVISION Training with FULL EQUIPMENT INCLUDED are invited to check and mail the coupon at the right.

Mail Coupon Today!

NO OBLIGATION
No Salesman Will Call

SPRAYBERRY ACADEMY OF RADIO, Dept. 25-F
111 North Canal St., Chicago 6, Illinois

Please rush to me all information on your 10-MONTH Radio-Television Training Plan. I understand this does not obligate me and that no salesman will call upon me. Be sure to include 3 books FREE.

Name . . . . . Age . . . . .

Address . . . . . .

City . . . . . Zone . . . . State . . . . .

☐ Are you Experienced? ☐ No Experience

www.americanradiohistory.com

The C-800 is here to bring you new record performance!




the new craftsmen 800
FM-AM TUNER
with built-in phono preamplifier and record equalizer

Now—Craftsmen brings you a tuner that matches *all* your finest records . . . is setting new records for versatility, too. The C-800 is further evidence that Craftsmen leadership in high fidelity is something you can put your finger on, something you can hear.

- *Front-panel-selected equalization* for AES, LP or EURopean recording characteristics. Inverse feedback compensated dual-triode phono preamp for correct turnover and roll-off characteristics.
- *Improved AM reception.* Wider bandwidth for better fidelity, and sharper IF bandpass "skirts" for greater selectivity.
- *Double-shadow tuning eye* and AFC (no drift) on FM simplifies tuning. Front-panel AFC cut-out for tuning weak stations.
- *Efficient new layout.* Bottom plate, completely shielded chassis minimize oscillator radiation, assure tuner isolation.
- *Cathode follower audio output* for remote installations; 2 volts at less than ½% dist. Detector output also has cathode follower for recording applications.
- *Bass and treble controls* continuously variable from attenuation to boost—flat position clearly marked. Selector positions: FM, FM with AFC, AM, TV, LP, AES, EUR, and SPare.
- Mahogany-finish wood cabinet available.

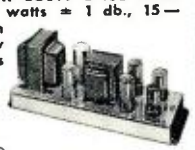HIGH FIDELITY—LOW COST! C-400 audio amplifier offers 10 watts ± 1 db., 15—20,000 cps., less than 1% distortion. New streamlined chassis design.



Write today for information

THE RADIO craftsmen INC.
Dept. R-2, 4401 N. Ravenswood Ave.
Chicago 40, Ill.

that will cut back many types of radio use formerly found to be in the public interest. How are those proposals, for example, to be squared with a substantial non-use of the FM broadcast band? . . . Of course, it is no answer for the existing FM broadcast licensees to suggest that they will meet the demands for mobile radio service by multiplexing their present facilities and supplying such service, presumably on a charge basis . . . There are existing communications common carriers in a most every community of any size who will vigorously resist any such effort, and there is a curious inconsistency in the reasoning of those, who in one breath, voice their resistance to any re-allocation of the FM band for non-broadcast purposes, and in the next, announce their plans for supplying such service there."

Currently, channels in the 150-mc. band are being used for two-way, and these must be shared with other services.

DROPOUTS AND MERGERS. resulting in rows of transfer grants, kept hearing examiners on the run during the last weeks of the old year.

Millions of dollars worth of radio and TV properties were traded during the year-end rush. Station sales and transfers approved included facilities in Des Moines, Ia.; Washington (D.C.); Orlando, Fla.; Atlantic, Ia.; Augusta, Ga.; Roswell, N. M.; Cleveland, Tex.; DeKalb, Ill.; Newport, R. I.; Asheville, N. C.; and Talladega, Ala.

In Maine, WGAN received channel 13 after another applicant dropped its bid for that channel and filed instead for channel 2 in Bangor. And in Atlanta, Ga., channel 36 was awarded to WQXI, when the University of Georgia, who operates WGST decided to drop its request for that channel.

New grants issued to very-high and ultra-high bidders appear below.

THE RECENTLY-FORMED U.H.F.-TV Association has begun an industry-wide campaign for the development and distribution of all-channel receivers that are really *efficient,* and the installation of transmitters operating on high power.

Thus far, the group said, many of the receivers have not been too sensitive. Coupled with the low powers of most of the u.h.f. transmitters, reception has been poor and interest on the higher bands has drooped, they added.

To combat this problem the association plans a public-relations program designed to accent the superiority of higher-band reception. Group also proposes to effect legal action within the Commission which will restore the balance between the u.h.f. and v.h.f. facilities and prevent new allocations or regulatory actions harmful to the public or to the ultra-high industry.

Members of this new group were severely critical of the FCC, declaring that some Commissioners are surrendering to pressure from Congress and political lobbys to . . . "accelerate grants to v.h.f. operators even in cities which already have grants for the higher bands."

ONE OF THE WORLD'S foremost physicists, Dr. Herbert E. Ives, who not only pioneered in the development of black and white, but color TV, too, and as far back as the '20's, died recently.

In '27, Dr. Ives supervised the first demonstration of TV, when the telephone company arranged for a video talk from Washington by Herbert Hoover, then Secretary of Commerce, that was seen and heard at the *Bell Labs* in New York. Shortly after, a TV color test, featuring Ives' developments, was put on and with striking success.

During 1930, he demonstrated a two-way TV system, and in '37, Dr. Ives arranged for the first practical transmission of motion pictures over coax cable, showing that it was entirely possible to network television programs.

The world will truly miss the wisdom and the talents of this brilliant scientist . . . . . L.W.

NEW TV GRANTS SINCE FREEZE LIFT

Continuing the listing of construction permits granted by FCC since lifting of freeze. Additional stations will be carried next month.

STATE	CITY	CALL	CHANNEL	FREQUENCY (mc)	POWER* (Video)
Florida	West Palm Beach	. . . . .	5	76-82	60.3
Georgia	Atlanta	WQXI-TV	36	602-608	240
Kansas	Topeka	. . . . .	42	638-644	88
Louisiana	Lake Charles	KPLC-TV	7	174-180	51.3
Maryland	Cumberland	WTBO-TV	17	488-494	19.1
Massachusetts	Pittsfield	WBEC-TV	64	770-776	17.4
Michigan	Detroit	. . . . .	62	758-764	200
"	Saginaw	WSGW†	51	692-698	26
"	Traverse City	WTCM†	7	174-180	51.3
South Carolina	Florence	. . . . .	8	180-186	316
"	Spartanburg	WORD†	7	174-180	316
Wisconsin	Marinette	WMAM†	11	198-204	102

*ERP = (effective radiated power, kw.). . . = Call letters to be announced † = Temporary call letters.


www.americanradiohistory.com

NO INTEREST!!

Buy on our radically new

Time Payment Plan

NO CARRYING CHARGES!!

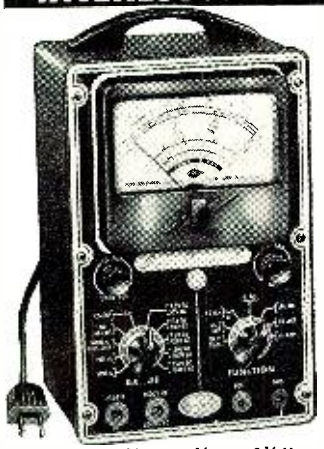

Measures 6¼" x 9½" x 4½"

Superior's new Model 670-A SUPER METER

A COMBINATION VOLT-OHM MILLIAMMETER PLUS CAPACITY REACTANCE INDUCTANCE AND DECIBEL MEASUREMENTS

SPECIFICATIONS:

D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500/7,500 Volts
A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
OUTPUT VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes
RESISTANCE: 0 to 1,000/100,000 Ohms 0 to 10 Megohms
CAPACITY: .001 to 1 Mfd. 1 to 50 Mfd. (Quality test for electrolytics)
REACTANCE: 50 to 2,500 Ohms, 2,500 Ohms to 2.5 Megohms
INDUCTANCE: .15 to 7 Henries 7 to 7,000 Henries
DECIBELS: —6 to +18 +14 to +38 +34 to +58

ADDED FEATURE:

The Model 670-A includes a special GOOD-BAD scale for checking the quality of electrolytic condensers at a test potential of 150 Volts.

The Model 670-A comes housed in a rugged, crackle-finished steel cabinet complete with test leads and operating instructions.

$28.40 NET



Superior's new Model TV-11 TUBE TESTER

SPECIFICATIONS:

★ Tests all tubes including 4, 5, 6, 7, Octal, Lock-in, Peanut, Bantam, Hearing Aid, Thyratron, Miniatures, Sub-Miniatures, Novals, Sub-minars, Proximity fuse types, etc.
★ Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin-number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TV-11 as any of the pins may be placed in the neutral position when necessary.
★ The Model TV-11 does not use any combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket.
★ Free-moving built-in roll chart provides complete data for all tubes.
★ Newly designed Line Voltage Control compensates for variation of any Line Voltage between 105 Volts and 130 Volts.
★ NOISE TEST: Phono-jack on front panel for plugging in either phones or external amplifier will detect microphonic tubes or noise due to faulty elements and loose internal connections.

EXTRA SERVICE—The Model TV-11 may be used as an extremely sensitive Condenser Leakage Checker. A relaxation type oscillator incorporated in this model will detect leakages even when the frequency is one per minute.

The model TV-11 operates on 105-130 Volt 60 Cycles A.C. Comes housed in a beautiful hand-rubbed oak cabinet complete with portable cover. .....

$47.50 NET



Superior's New Model 660-A AN AC OPERATED SIGNAL GENERATOR

PROVIDES COMPLETE COVERAGE for AM-FM & TV Alignment

SPECIFICATIONS:

• Generates Radio Frequencies from 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 220 Megacycles on powerful harmonics. • Accuracy and Stability are assured by the use of permeability trimmed Hi-Q coils. • R.F. available separately or modulated by the internal audio oscillator. — Built in 400 cycle sine wave audio oscillator used to modulate the R.F. signal also available separately for audio testing of receivers, amplifiers, hard of hearing aids, etc. • R.F. Oscillator Circuit: A high transconductance heptode is used as an R.F. oscillator, mixer and amplifier. Modulation is effected by electron coupling in the mixer section thus isolating the oscillator from load changes and affording high stability. • A.F. Oscillator Circuit: A high transconductance heptode connected as a high-mu triode is used as an audio oscillator in a High-C Colpitts Circuit. The output (over 1 Volt) is nearly pure sine wave. • Attenuator: A 5 step ladder type of attenuator is used.

TUBES USED:

1—6BE6 as R.F. Oscillator, mixer and amplifier
1—6BE6 as Audio Oscillator
1—6H6 as Power Rectifier

THE MODEL 660-A COMES COMPLETE WITH COAXIAL CABLE, TEST LEAD AND INSTRUCTIONS.

$42.95 NET

MOSS ELECTRONIC DISTRIBUTING CO., INC.
Dept. B-92, 3849 Tenth Ave., New York 34, N. Y.

Please send me the units checked. I am enclosing the down payment with order and agree to pay the monthly balance as shown. It is understood there will be no carrying, interest or any other charges provided I send my monthly payments when due. It is further understood that should I fail to make payment when due, the full unpaid balance shall become immediately due and payable.

Name.....
Address.....
City.....Zone.....State.....

☐ MODEL 670-A.....Total Price $28.40 $7.40 down payment. Balance $3.50 monthly for 6 months.
☐ MODEL TV-11.....Total Price $47.50 $11.50 down payment. Balance $6.00 monthly for 6 months.
☐ MODEL 660-A.....Total Price $42.95 $12.95 down payment. Balance $5.00 monthly for 6 months.
☐ I enclose $.....as down payment.
☐ Ship C.O.D. for the down payment.

www.americanradiohistory.com

NEW PROBES!

FOR VTVM'S & SCOPES

- FULLY SHIELDED
- SHOCK-MOUNTED TERMINAL BOARD
- SWIVEL ACTION
- ALL PARTS ACCESSIBLE
- COLOR CODED

Only EICO Probes Have All These Features!



SENSATIONAL HIGH VOLTAGE PROBE
MODEL HVP-2

ONLY . . . $4.95
FOR VTVM'S & VOM'S

See these amazing probe values at your jobber today. Write now for free catalog PR-2 Turn to our full-page ad on page 34 this magazine.

EICO® "All above probes Pat. App. for."

ELECTRONIC INSTRUMENT CO., Inc.
84 WITHERS STREET, BROOKLYN, NEW YORK

ested in best receiver sensitivity, it will pay to try the circuit with and without a ground on the antenna coil. The proper connection will depend on the antenna layout at your location.

There are a number of different door openers on the market. As a result, it is not practical to show exactly how the receiver may be used to actuate all of the various models. By exercising a little ingenuity, however, the home constructor should have no difficulty in adapting the receiver to work with the particular door opener at hand.

RL_1 acts as an s.p.s.t. switch that closes only while a signal is being received from the car transmitter. When the door is down, the closing of RL_1 should cause the door to go up, and when the door is up, the closing of RL_1 should cause the door to go down. Since RL_1 is unable to differentiate between a command to raise the door and a command to lower it, some intermediate relay between the receiver and the opener must be used to tell the opener motor which direction it is supposed to run. This relay is usually of the locking, or ratchet type. It locks in one position when its coil is energized and remains in that position, even when power is removed from its coil. It shifts to the opposite position only after the coil is re-energized.

The circuit of a typical door opener is shown in Fig. 6A. Operation of this unit may be easily understood if you will assume that a momentary signal has just been received from the car transmitter. RL_1 closed, energized the locking relay, and then opened. Power from the a.c. line is now flowing through the locking relay and the limit switch to the motor and garage light. The door is going up. When the door has opened completely, the limit switch will flip to the down

Fig. 10. Transmitter control switch and pilot bulb mounted on small bracket for easy installation beneath car dash. Since only momentary transmitter operation is required to actuate door opener, a push-button may be substituted for the toggle switch shown.



STAN-BURN S-P-A-R-K-S

CATHODE RAY TUBE SPECIALS

One Year Guarantee

G. E.		STAN-BURN	
5TP4	$44.95	10BP4	$11.00
7JP4	17.10	12LP4A	14.20
10BP4A	19.25	14CP4	17.00
10FP4A	24.00	15DP4	19.50
12KP4A	27.10	16AP4	21.60
12LP4A	21.70	16FP4	19.60
12UP4B	28.25	16GP4	21.60
14CP4	24.50	16EP4A	22.60
16AP4A	30.95	16DP/HP4	19.60
16DP4A (N.U.)	28.20	16DP/HP4A	20.60
16GP4	31.25	16KP4	18.50
16KP4/16RP4	28.20	16LP4	20.60
17BP4A	23.90	16LP4A	21.60
17CP4	23.90	17BP4	18.50
19AP4A	39.45	17CP4	21.60
20CP4	32.50	19AP4	23.90
20LP4	37.50	19AP4A	25.90
21EP4A	37.35	20CP4	29.50
24AP4A	78.50	21EP4	32.50

ANTENNAE SPECIALS

		1-5	6 or more
RED DOUBLE "V" Antenna		$2.19	$1.98
10 ELEMENT CONICAL DOWELED INSERTS		2.98	2.79
Folded Hi Straight Low Quick Rig ½" elements		4.25	3.25
WINDOW CONICALS		4.95	3.75
MASTS	5 FOOT SWEDGED	.79	.69
	10 FOOT PLAIN	1.39	1.29
	NEPCO MASTS	1.69	1.49
TV WIRE	42 Mil.	$ 9.95 M Ft.	
	55 Mil. 300 OHM	11.95 M Ft.	
	72 OHM COAXIAL	35.00 M Ft.	

12" Heavy Slug Speaker . . . . . Special $3.98

CHASSIS 630 TECH-MASTER Model C-30 with Cascode Tuner $149.50

OPEN FACE CABINET 42.00

WIRE RECORDERS IN STOCK

PENTRON — Model 9T3C — 2-speed Tape Recorder . . . . . Write for Price

RADIO CRAFTSMAN
Model C400—Hi-Fi Amplifier . . . . . Net 42.90
Model C10—AM-FM Tuner . . . . . Net 131.50
Model CS00—Williamson Amplifier . . . . . Net 99.50

We also carry MASCO—BOGEN—PILOT, etc., Amplifiers, Pre-Amps, FM Tuners and WEBSTER Tape Recorders.

6x9 PM Speaker	$ 3.98	630 Vert. Blocking OSC. XForm	.89
7" PM Speaker	3.98	Cascode Tuners	19.95
7711 G.E. Flyback	1.98	Standard Tuners	17.95
70° Yoke	1.98	Dumont 21.25 mc.	14.95
630 Vert., output upright	1.98	Famous Inputuner	10.00
630 Vert., output Potted	1.29	TV Permanent Magnet Focus Assembly	1.98

CONVERSION SPECIAL
21EP4 American Standard Tube
21" Beveled Mask
Ram Conversion Kit
(Mention Set to be converted.)
ALL FOR ONLY $43.50

AUTHORIZED DISTRIBUTORS for General Electric, Kenrad, Tung-Sol, National Union, De Wald, Regal, Automatic and General Motors.

Automatic Custom-Built Radios for Plymouth, Ford, Chevrolet and many others, always in stock.

We carry a Complete line of HI-FIDELITY and sound equipment. Send us your requests.

We also carry a complete line of popular makes of Radio Tubes at 50/10 discount. Also many other special purpose and transmitting types, and all electronic parts and equipment at lowest prices. Send us a list of your requirements for prompt quotations.

Terms: 20% with order. Balance C.O.D. All prices F.O.B., NEW YORK Warehouse. Minimum order $5.00. Write for our latest price list and Hi-Fi catalog to Dept. RN-2.

STAN-BURN RADIO and ELECTRONICS CO.
(C.B.S. THEATRE BLDG.)
1697 BROADWAY • NEW YORK 19, N.Y.

Read Radio & Television News
EVERY MONTH

THE NEW TV DYNATRACER

ONLY $4.95 Ppd. or C.O.D. + Chgs.



- TRACES TV SIGNALS AND VOLTAGES
- LOCATES DEFECTIVE COMPONENTS
- REQUIRES NO ADDITIONAL EQUIPMENT

This sensationally new piece of test equipment is ideal for trouble-shooting television sets in the home or in the shop. The "DYNATRACER" will out-perform more expensive testers and should pay for itself on the very first repair.

A Must for Every TV Technician

SPECIFICATIONS: The "DYNATRACER" is a self-powered quality test instrument designed to trace TV signals through any Video, Sound, Sync, AFC, Horizontal or Vertical Sweep Circuit—will isolate trouble to a stage or component.

ADDED FEATURE: The "DYNATRACER" will also trace voltages (50/500 V. AC/DC) and instantly locate open, shorted, intermittent or leaky (up to 20 MEGOHMS) condensers, resistors, coils, XFormers, etc.

Instruction and Trouble-Shooting Book Enclosed
10 DAY MONEY-BACK GUARANTEE

Cut out advertisement . . . attach name and address with $5.00 bill, check or money order and mail to

Century ELECTRONICS CO.
8509-21st Ave., Dept. 210, Brooklyn 14, N. Y.

www.americanradiohistory.com

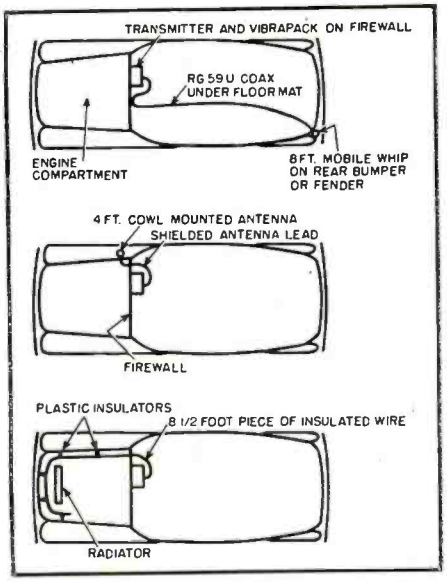



Fig. 11. Three methods for connecting the transmitting antenna. See text for details.

position, the motor will stop and the light will go out. The door will remain open until another momentary signal is received from the car transmitter. This time, the latching relay will jump to the opposite position and current will flow through it and the limit switch to the reverse winding of the motor. The door will go down, until it reaches the end of its travel, at which time the limit switch will flip to the "up" position and the motor will stop.

Some openers contain built-in locking relays and, for this reason, require very little external wiring. A unit of this type, illustrated in Fig. 13, is produced by *Ebbert Engineering Co.*, Birmingham, Michigan. A glance at Fig. 6B will show how easily the receiver may be connected to the *Ebbert* mechanism.

After the car has been put away and the door closed behind it, the problem of getting back into the garage presents itself. The most convenient way to solve this particular difficulty is to install, in the house, a push-button wired across the points of RL_1. As a safety precaution, the push-button should be located where you can look through a window to check on the door's operation. It will be noted that push-buttons are in-

Fig. 12. Typical receiving antenna layout.

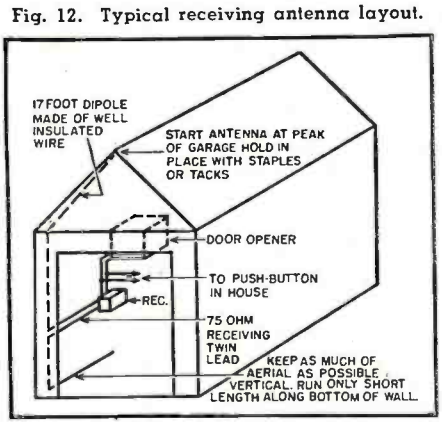

Quality Features OF TUNG-SOL PICTURE TUBES



Gun made of best grade non-magnetic steel.

Glass bead type assembly is stronger both mechanically and electrically — gives greater protection against electrical leakage.

Rolled edges in gun minimize corona.

Custom built stem with greater spacing between leads assures minimum leakage.

Low resistance of outside conductive coating minimizes radiation of horizontal oscillator sweep frequency.

Double cathode tab provides double protection against cathode circuit failure.

Selected screen composition resists burning (X pattern).

Rigid control of internal conductive coating provides utmost service reliability.

Designed for use with single or double field ion trap designs.

One-piece construction of parts assures better alignment.

Maximum dispersion of screen coating assures uniform screen distribution.

Tung-Sol makes All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers, Picture Tubes, Radio, TV and Special Purpose Electron Tubes and Semiconductor Products.

TUNG-SOL®
RADIO AND TV TUBES

TUNG-SOL ELECTRIC INC., Newark 4, N. J.
Sales Offices: Atlanta, Chicago, Columbus, Culver City (Los Angeles), Dallas, Denver, Detroit, Newark, Seattle.

YOU CAN BUILD A REPUTATION ON TUNG-SOL QUALITY

www.americanradiohistory.com

Check. these N.J.R.T. TUBE prices 70% to 90% off list . . .

Type	Price	Type	Price	Type	Price
1A7GT	.45	6AT6	.37	6SQ7GT	.37
1B3GT	.67	6AU4GT	.70	6T8	.57
1H5GT	.38	6AU6	.40	6U8	.59
1L4	.50	6AV6	.37	6V6GT	.38
1N5GT	.62	6AX4GT	.55	6W4GT	.42
1R5	.48	6BA6	.40	6W6GT	.45
1S5	.40	6BA7	.57	6X4	.35
1T4	.48	6BC5	.49	6X5GT	.35
1U4	.48	6BD6	.45	7E6	.35
1U4	.48	6BE6	.37	7F8	.63
1U5	.40	6BG6G	1.20	12AL5	.40
1X2	.65	6BH6	.45	12AT6	.35
3A4	.43	6BJ6	.41	12AT7	.65
3LF4	.49	6BK7	.89	12AU6	.38
3Q4	.48	6BL7GT	.65	12AU7	.55
3Q5GT	.48	6BQ6GT	.70	12AV6	.50
3S4	.48	6BQ7A	.92	12AV7	.60
3V4	.50	6BZ7	.95	12AX4GT	.55
5AZ4	.50	6C4	.39	12AX7	.55
5U4G	.45	6CB6	.45	12BA6	.40
5Y3GT	.39	6CD6G	1.15	12BA7	.57
5Z3	.45	6F6	.45	12BE6	.41
5Y4G	.39	6J5	.40	12BH7	.65
6A3	.57	6J6	.50	12BY7	.65
6A6	.49	6K6GT	.37	12BZ7	.65
6AB4	.42	6L6	.62	12SA7	.58
6AF4	.92	6R7	.49	12SK7	.58
6AF6	.75	6S4	.38	12SL7GT	.49
6AG5	.47	6S8GT	.51	12SN7GT	.50
6AJ5	.73	6SA7GT	.41	12SQ7	.55
6AK5	.75	6SD7GT	.39	12SR7met	.55
6AL5	.37	6SK7GT	.39	12V6GT	.50
6AQ5	.37	6SL7GT	.49	19BG6G	1.15
6AQ6	.36	6SN7GT	.50	19T8	.75

Type	Price
25BQ6GT	.75
25L6GT	.40
25W4GT	.45
25Z6	.37
35A5	.49
35B5	.38
35C5	.38
35L6GT	.45
35W4	.37
35Z3	.43
35Z5GT	.45
42	.40
43	.53
45	.53
50B5	.41
50C5	.41
50L6GT	.59
70L7GT	1.07
76	.42
117Z3	.39
117L7GT	1.19
807	1.25

Guarantee
ALL NJRT TUBES ARE BRAND NEW AND FULLY GUARANTEED FOR 1 YEAR

T.V. PIX TUBE BRIGHTENER. $1.39
For T.V. sets where voltage supply is low AC LINE BOOSTER with safety fuse and switch $5.95

Free Five 1L4 tubes individually cartoned list $11.25 with every order of $25.00 or more. Many 7 volt types not listed. All tubes individually boxed. For orders under $10 add $1 handling charge. Tubes offered subject to prior sale. Prices subject to change. All orders shipped F.O.B. 2% discount if full remittance accompanies order. 25% deposit on c.o.d. shipments. SEND FOR FREE TUBE LISTING.

NJRT TUBE CO.
NEW JERSEY TELEVISION SUPPLY CO.
Sole Distributor of NJRT Tubes
906B WESTFIELD AVE., ELIZABETH, N. J. EL. 3-6166

WALDOM
TV Conversion Kit
Mask and Escutcheon Assemblies

For a professional conversion or custom installation
1 Metol Mosk toilored for perfect fit. Green Sproyed Finish.
2 ¼" Tempered Sofety Glass.
3 Beoutiful Gold Finished Metol Escutcheon.
All popular sizes: 14", 16", 17", 20" ond 21". Rectangulor Tubes only. Eosy to install instructions included.
See your distributor

Send for COMPLETE CATALOG
Waldom carries a complete line of Electronic Components and Cronome Products.
WALDOM ELECTRONICS, INC.
911 Larrabee St. Chicago 10, Illinois

QUARTZ CRYSTALS
FT-243-.093" PIN DIA.—.486" PIN SPC
FOR HAM AND GENERAL USE

4035	5500	5950	6706	7506	7825	1015	2605	3995	6573	7240	8173
4080	5675	5973	6725	7525	7840	1110	2738	6000	6575	7273	8175
4110	5677	5975	6740	7540	7850	1150	2785	6025	6600	7275	8200
4165	5700	6225	6750	7550	7873	1525	2895	6050	6606	7300	8340
4190	5706	6240	6773	7573	7875	1915	2940	6073	6625	7306	8350
4255	5725	6250	6775	7575	7900	1930	3005	6075	6640	7325	8375
4280	5740	6255	6800	7600	7906	1940	3010	6100	6650	7340	8380
4300	5750	6273	6806	7606	7925	1950	3202	6106	7000	7350	8400
4397	5760	6275	6825	7610	7940	2065	3215	6125	7006	7375	8425
4150	5773	6300	6840	7625	7950	2105	3237	6140	7025	7400	8430
4190	5775	6306	6850	7640	7973	2118	3245	6150	7040	7425	8450
4195	5800	6325	6875	7641	7975	2125	3250	6173	7050	7440	8460
4780	5806	6335	6900	7650	8206	2140	3460	6175	7073	8000	8475
4845	5825	6340	6906	7673	8225	2145	3500	6200	7075	8006	8483
4930	5840	6350	6925	7675	8240	2305	3540	6440	7100	8025	8500
5030	5850	6373	6940	7700	8250	2320	3590	6450	7106	8050	8525
5205	5852	6375	6950	7706	8273	2390	3640	6473	7125	8073	8550
5235	5873	6400	6973	7720	8275	2415	3680	6475	7140	8075	8575
5250	5875	6406	6975	7725	8300	2430	3720	6500	7150	8100	8583
5300	5880	6425	7450	7740	8306	2442	3735	6506	7173	8106	8600
5305	5900	6673	7473	7750	8325	2460	3760	6525	7175	8125	8625
5333	5906	6675	7475	7773		2532	3800	6540	7200	8140	8650
5385	5925	6700	7500	7775		2545	3840	6550	7206	8150	8700
5485	5940			7800		2557	3885		7225		8733

49c each—10 for $4.00 | 99c each—10 for $8.00

Low Frequency—FT-241A for SSB, Lattice Filter etc., .093" Pins, .486" SPC., marked in Channel Nos. 0 to 79, 54th Harmonic and 270 to 389, 72nd Harmonic. Listed below by Fundamental Frequencies, fractions omitted.

370	393	414	436	498	520	400	459	5910	2030	2220	2390	3120	3520
372	394	415	437	501	522	440	461	6370	2045	2258	2415	3150	3550
374	395	416	438	502	523	441	462	6450	2052	2260	2435	3155	3570
375	396	418	481	503	525	442	463	6470	2065	2280	2442	3202	3580
376	397	419	483	504	526	444	464	6497	2082	2282	2532	3215	2945
377	398	420	484	505	527	445	465	6522	2105	2290	2545	3232	3955
379	401	422	485	506	529	446	466	6547	2125	2300	2557	3237	3970
380	402	423	486	507	530	447	468	6610	2131	2305	2660	3250	3995
381	403	424	487	508	531	448	469	7350	2145	2320	2940	3322	
383	404	425	488	509	533	450	470	7380	2155	2360	3035	3510	
384	405	426	490	511	534	451	472	7390					
385	406	427	491	512	536	452	473	7480					
386	407	429	492	513	537	453	474	7580					
387	408	430	493	514	538	454	475	7810					
388	409	431	494	515		455	476	7930					
390	411	433	495	516		456	477						
391	412	434	496	518		457	479						
392	413	435	497	519		458	480						

CR-1A SCR 522 ½" P ½" S
FT-171B BC-610 2 Banana Plugs ¾" SPC

Special—200 KCor 500 KC in FT241A Holder, $1.95 each

add 20c postage for every 10 crystals (orless)

49c each—10 for $4.00 | 99c each — 10 for $8.00

BC 746 TUNING UNITS — foundation coils and condenser for 80 meter VFO or exciter—less xtals 98c

Sun
PARTS DISTRIBUTORS, LTD.
520 TENTH ST. N. W.—WASH. D. C., DEPT. N

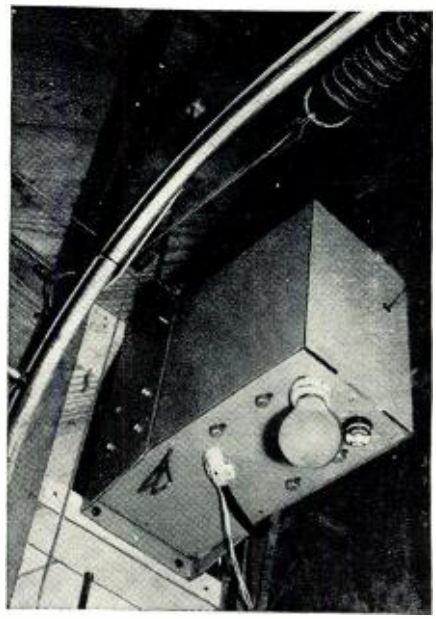


Fig. 13. "Ebbert" motor-driven door opener, a commercially-built unit suitable for use with equipment described in the text.

cluded in both Figures 6A and 6B.

Like other Citizens Band equipment, the transmitter must be registered. Obtain a copy of FCC form 505, fill it out carefully, and mail it to the nearest Commission field office. In a short time you will receive a class C Citizens Radio License covering this particular piece of gear. Upon receipt of the license, you, or anyone else with your permission, may use the transmitter to control your garage door. As long as you make no adjustments on the transmitter, outside of turning it on and off, no operator's license will be necessary.

Further information regarding Citizens Radio is contained in FCC's "Rules and Regulations Governing the Citizens Radio Service" obtainable from the Superintendent of Documents, Government Printing Office, Washington 25, D. C. The price of this pamphlet is 10c in coin. —30—

GUILD ELECTS

THE Long Island Television and Radio Technicians Guild has named Henry Wawryck president for this coming year with Arthur Cyr serving as vice-president.

John Wheaton is the new treasurer, Murray Barlowe was named secretary while Al Weil is recording secretary and Earl Horton is the sergeant at arms. Four members were added to the executive board, Jack Buck for a three-year term, Dick Bishop for two years, and Bill Allen and Ralph Milne for one year terms.

—30—

RADIO-TV CONFERENCE

THE ninth annual Michigan State Radio and Television Conference of commercial and educational broadcasters will be held Friday, March 5, 1954 at Michigan State College in East Lansing, Michigan.

The topic for the conference this year is the role of radio and television as mass media.

Robert P. Crawford of Michigan State College is conference chairman. —30—

www.americanradiohistory.com

Come Again


Radio-Electronic Men!

Just as you have been coming since 1945 to the IRE National Convention and Radio Engineering Show — coming by the thousands, 35,642 in '53 — so come again to see and hear all that is new in the engineering advances of your industry.

▲ Fifty-four in '54! — 243 scientific and engineering papers will be presented, skillfully grouped by related interests into 54 technical sessions. More than half these sessions are organized by IRE Professional Groups, thus making the IRE National a federation of 21 conferences in one. The whole provides a practical summary of radio-electronic progress.

▲ 600 Exhibitors "spotlight the new!" — A mile and a half of exhibits line the avenues of this show, intriguingly named for the elements of radio — such as "Instruments," "Components," "Airborne," "Radar," "Transistor," "Audio," "Microwave," etc., filling the four acres of the great Kingsbridge Armory to capacity. An expanding radio industry shows why it is growing by proving how engineering research pays out in new products. The exhibits themselves are an education, condensed to one place — reviewed in four days.

▲ Kingsbridge is the solution! Only the combined facilities of the Waldorf-Astoria Hotel, plus the three great halls in the Kingsbridge Armory, seating 906, 720, and 500 respectively, are able to keep pace with the increased technical papers program of the IRE Convention. The show had to move because the U. S. Treasury took over Grand Central Palace. The immense Kingsbridge Armory, connected to the very satisfactory Lexington Avenue Hotel area by direct express subway, serves well to expand the already outgrown exhibit facilities of the Palace and provide space for 200 new firms to exhibit, as well as seat greater audiences at the high-interest sessions. In addition to the subways, free busses leave the Waldorf every ten minutes in which you may travel in the congenial company of fellow engineers, direct to Kingsbridge.

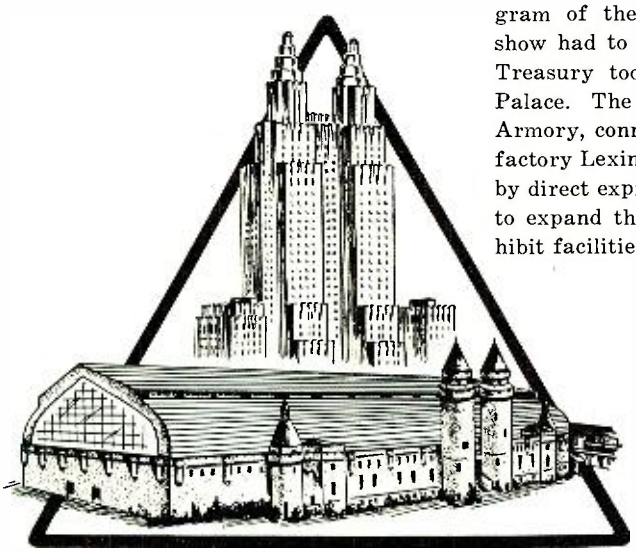

Waldorf-Astoria and Kingsbridge Armory

▲ Admission by registration only! Registration serves for the four day period. It is $1. for IRE members, $3. for non-members, covering sessions and exhibits. Social events priced separately.

March 22-25, 1954


The IRE National Convention and Radio Engineering Show

THE INSTITUTE OF RADIO ENGINEERS

1 East 79th Street, New York City

www.americanradiohistory.com

NOW IT'S
Plug-In
SELENIUM
RECTIFIERS

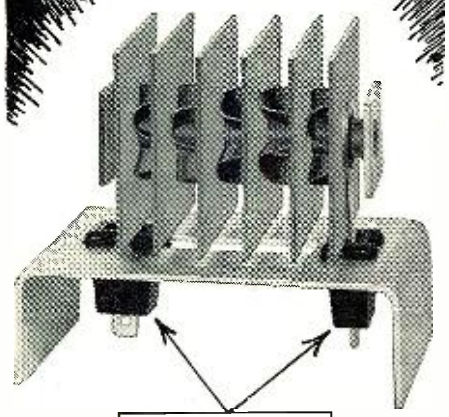

Plugged In
for Easy Replacement

Polarized
for Correct Positioning

Still Can Be
Soldered In The Set

Available In All Sizes.
Write for Further Information.

When buying selenium rectifiers be sure to specify "PLUG-INS" . . . they cost no more.

Send for your Free copy of "Selenium Rectifiers for Color Television".

Sarkes Tarzian INC

RECTIFIER DIVISION

Dept R-1, 415 N. College Ave., Bloomington, Ind.
In Canada–50 St Clair Ave. N W., Toronto

NEW TV PRODUCTS on the Market

FLYBACK TESTER

Kirby Products Corp., 20 E. Herman St., Philadelphia, Pa. has developed a



new television service instrument which has been designated as the Model 98 flyback transformer tester.

The instrument is designed to indicate shorted turns within the flyback transformer, while the transformer is in the set, by the power absorption method. It will supply an indication on as low as one shorted turn anywhere in the transformer. In addition, the instrument will test for continuity on yokes, transformers, switches, etc.

The instrument is portable, compact, and moderately priced. It is being handled through franchised electronic parts distributors. Free literature is available on request.

ANTENNA ROTATOR

Leader Electronics, Inc., 2925 East 55th Street, Cleveland 27, Ohio is now offering a new antenna rotator which is said to provide easier installation and servicing in addition to finer tuning.

Known as the "Superotor," the new



unit features a quick detachable drive unit for easy one-man removal without dismounting the antenna, a double lock stop to eliminate both drift and coast, a built-in chimney mount design thus eliminating stub mast assemblies, steel reinforced construction, and vernier precision adjustment.

The rotator is 16¼" x 7" x 4½" overall. It is rated at 60-75 watts input, 117 volts, 60 cycle a.c.

TV ALIGNMENT TOOL

General Cement Mfg. Co. of Rockford, Ill. has added a plastic television set alignment tool, the X-57, to its line of service accessories.


Designed in response to a demand for an extra-long, extra-slim, high-dielectric TV alignment tool, the new X-57 meets these requirements. It is only ⅛" in diameter and is available in three blade lengths, 7", 12", and 16".

Complete descriptive literature on this accessory is available from the company.

U.H.F. CONVERSION KIT

The Allen D. Cardwell Mfg. Corp., 97 Whiting St., Plainville, Conn. is currently marketing a new u.h.f. conversion kit for installation inside existing TV sets, irrespective of make, to provide all-channel u.h.f. tuning.

The Model ES-2 is completely fac-

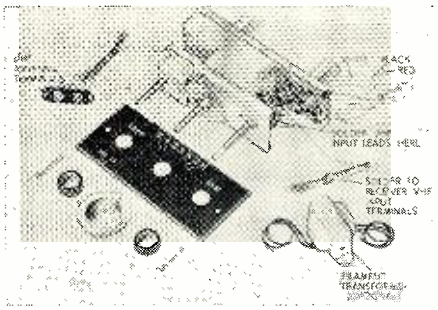

tory-aligned and assembled and comes complete with escutcheon plate, knobs, and pointer. Installation requires only soldering connections and the drilling operation using a template.

The tuner will cover channels 14 to 83 with one knob and an easy-to-read dial. A printed circuit is said to give stable tuning with no drift. Either channel 5 or 6 is used as the i.f.

MARKER GENERATOR

The Tube Department of *Radio Corporation of America*, Harrison, N.J. has announced a new crystal-calibrated marker generator, the WR-89A.

Featuring continuously tunable operation for the alignment and trouble-shooting of a wide range of communications equipment as well as TV sets, the new instrument combines the functions of a marker generator, a vertical or horizontal bar-pattern generator, a rebroadcast transmitter, and a heterodyne frequency meter.

The instrument provides an r.f. out-

www.americanradiohistory.com



IT'S FREE! **SEND FOR IT TODAY!**

THIS BIG 156 PAGE 1954 **B-A** CATALOG IS **BULGING** WITH **GIANT VALUES** LIKE THESE...

BURSTEIN-APPLEBEE CO. Dept. M,
1012-14 McGee St., Kansas City 6, Mo.

☐ Send Free B-A Catalog No. 541
☐ My order attached for items in this ad.

$..... enclosed.


Name.....

Address.....

City.....State.....

SAVE $$$ ON THESE USEFUL ASSORTMENTS

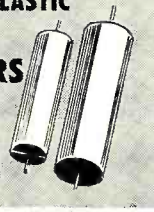36 MOLDED PLASTIC TUBULAR CONDENSERS
$11.70 List Value
$3.88



Compact, yet with the rugged construction needed to withstand the high temperature in TV. Auto and AC-DC sets. Top quality. Fully guaranteed by the maker as well as B-A. Kit of 36 all 600 volt: 4 each .001, .002, .005 and 6 each .01, .02, .05, .1.
18A263. Per Kit..... $3.88
Kit of 36 Paper Tubulars all 600 volt assorted as above. $10.50 List Value.
15A389 Per Kit..... $2.39

100 TOP QUALITY INSULATED RESISTORS
$1.49



Do not confuse with non-insulated, foreign makes etc. offered by others. 50 assorted top quality ½ watt insulated resistors in most popular capacities.
17A871. 50 Asst..... 99c

ASSORTMENT OF 100
Consists of 75-½ watt and 25-1 watt insulated top quality resistors of various resistance values.
19B796 100 Asst..... $1.49

10 ASSORTED ROTARY SWITCHES
99c




Assortment of Ten — any one of which is worth more than the price of the lot. Anyone experimenting or building will find good use for all.
18A436. 10 Asst..... 99c

SWITCH ASSORTMENT
10 Assorted—toggle, push button and slide type switches for a multitude of uses. The use of only several will pay for the lot.
18A935. 10 Asst..... $1.19

41-FT. TELESCOPING STEEL MAST FOR TELEVISION, ETC.

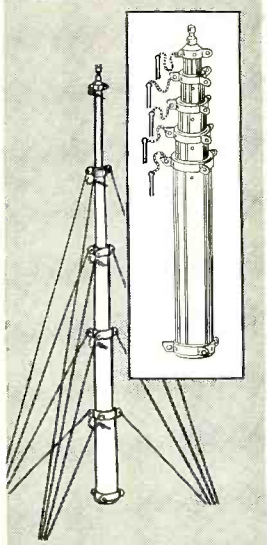FORMER SELL-OUT AGAIN AVAILABLE NOW ONLY **$13.69**




Thousands were previously grabbed up as an outstanding buy at $24.88 . Now, another huge special purchase from Gov't. surplus makes passible this Terrific Bargain. (Original Gov't. cost said to be $60.00 each.)
Built to rigid Army Specs. (AN--S-2) for portable field lighting . . . ideally suited for a truly superior TV mast as well as for amateur beams, lighting, flagpoles, etc.
Compare these specifications with ordinary TV Masts . . . 5 sections extend to 41 ft., telescope to 9½ ft. Super-strong chrome alloy seamless steel tubing, baked brown weather-proof enamel inside and out. Two machined close-fitting bushings and 3-hole guy ring at each joint. Sections extend easily, are held in position by heavy cross pins . . . **May even be raised horizontally fully extended, with no buckling!** Can be dis-jointed for shortening or dividing. Top section diameter ¾" yet stronger than usual TV masts and of ample size to accommodate antenna mast clamp hardware. Mid-sections 1⅜", 1¾" and 2⅛". Base section 2½" diameter.
Makes possible at low cost ground mounted antenna systems commonly preferred to roof-top installations because of less hazard for the installer and the home—plus better choice of antenna location. Order Now While Available at this Low Price! Every Mast **Brand New.**
No. 6A85. Shpg. wt. 40 lbs.
SPECIAL EACH..... $13.69
4 Masts in Original Wood Crate Shpg. wt. 200 lbs.
Lots of 4 for..... $49.97

A VALUE THAT DEFIES COMPARISON

FAMOUS "APPROVED" MODEL A200

SIGNAL GENERATOR

$49.50 VALUE NOW ONLY **$19.75**

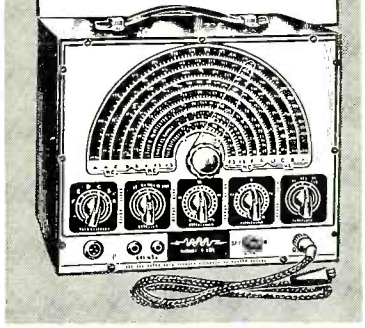

BRAND NEW! FACTORY PACKED! FULLY GUARANTEED!

Hundreds sold at ½ the Regular $49.50 Net Price. Now a final B-A lucky purchase makes available an additional quantity at a greater saving to you. Buy Now While They Last.

Extremely stable, built for long, dependable service. 8 BANDS, 100 kc to 75 mc—with 455 kc position indicated in red for quick reference. Large open-face frequency dial has multi-colored scales for 6 over-lapping fundamental ranges from 100 kc to 25 mc, with Band F2, 18-50 mc and Band F3, 27-75 mc on harmonics. Phase shift audio oscillator and internal modulator for 440 cps., internal or external—and continuously variable from front panel from 0-100%; external modulation possible, 40-30,000 cps. Extremely low leakage on all bands; completely isolated from power line, Ceramic insulated, low drift, wide spaced variable condenser of "invar" metal used as frequency selector. 3-step RF attenuator and continuously variable RF-AF attenuator control—ultra stable 2-terminal RF oscillator, 6SH7 tube as cathode follower output to a coax lead assuring frequency stability regardless of attenuator control setting. Lucite dial pointer with hair-line indicator. Pilot light line indicator. With 4 tubes, cable, instructions. Steel cabinet is 8x10x12", for operation on 105/120 volt, 60 cycle AC. Weight 20 lbs.
No. 34B173. $49.50 Value **Now While They Last..... $19.75**

"BUILD-YOUR-OWN" WITH MODEL A200K PARTS KIT

Identical to factory-wired Model A-200 described above EXCEPT in KIT form! Complete with 4 tubes, cables, cabinet, operating instructions and circuit and pictorial diagrams for easy assembly.
No. 34B175. $32.50 Value **Now While They Last..... $16.75**

LATEST TEST INSTRUMENTS ON CONVENIENT PAYMENT TERMS
Includes these popular makes: Hickok, Simpson, Triplett, EMC, RCP, Precision, etc.

B-A BURSTEIN-APPLEBEE CO. 1012-14 McGEE ST. KANSAS CITY, MO.

TERMS: F.O.B. Kansas City. Remit with order, include postage for parcel post shipments.

www.americanradiohistory.com



HERE'S A WELL-KNOWN TV HANDYMAN

Just press the button and spray on a tough, quick-drying dielectric Acrylic coating.

KRYLON Acrylic coating helps prevent corona when sprayed on high voltage coil and insulation, the socket of the high voltage rectifier, and component parts of the rectifier circuit.

KRYLON Acrylic coating*, when sprayed on antenna and lead-in connections, effectively seals out air, moisture, dirt . . . prevents pitting and keeps picture at peak quality.

KRYLON CUTS DOWN SERVICE CONTRACT CALLS . . . INCREASES YOUR PROFITS . . . AND IS THE NATION'S LARGEST SELLING ACRYLIC COATING FOR TV AND RADIO.

TECHNICAL CHARACTERISTICS:

Dielectric constant—2.8 to 2.4 (1,000 cycles)
Dielectric strength—400 to 800
Electrical resistance—10^{10} ohms/cm^3
Available from TV Jobbers everywhere.

•

KRYLON, Inc., Phila. 46, Pa.

**Also available in non-conductive Bright Aluminum, Glossy Black, and appliance White.*

put signal on fundamental frequencies from 19 to 260 mc. and can be used with TV receivers and other equipment operating in this range. A built-in crystal-controlled oscillator also provides an output signal at 4.5 mc.

The WR-89A measures 10" x 13½" x 7½" and weighs 15 pounds. It is available from the company's test instrument distributors.

U.H.F. CONVERTER

The Turner Company, 909 17th Street, Cedar Rapids, Iowa is now



offering a new u.h.f. television converter that is said to be especially effective in low signal area installations.

The new converter features a two-section preselector which has two silver-plated coaxial cavity tuners; a double-shielded fundamental oscillator; and a broadband amplifier with cascode circuit. The signal power loss in the preselector has been reduced to 3 db, according to the company. The noise figure is a maximum of 17½ db and a minimum of 15½ db.

The converter itself has an illuminated slide-rule dial, continuous single-knob tuning from 470 to 890 mc. using channels 5 or 6, and measures 8" x 6" x 6". It is designed to be used with either a u.h.f. or combination antenna. The unit is self-powered.

ISOLATION TRANSFORMER

Standard Electrical Products Company, 2240 E. Third St., Dayton, Ohio has added an adjustable variable me-



tered isolation transformer, the type LR, to its line of equipment.

Suitable for applications involving the use of a variable transformer or an isolation transformer, the new unit is designed for radio and television serv-

HI-FI BUY!
NEW
STANCOR-WILLIAMSON
Amplifier

Kit $49.50 Wired $69.50
(Complete inclusive of tubes)

Finest in sound, yours for very little cost. Only takes you a few hours to put together. Over 5,000 already built and successfully performing. Frequency responses: flat from 20-20,000 cycles at both 0.5 and 8 watt levels. Intermodulation distortion measures only 3% at 8 watts output. Kit is complete with 5 tubes (2—6SN7, 1—5U4 and 2—807), 2-punched chassis, Stancor Hi-Fi Output transformer A-8054, assembly instructions and all other necessary parts for amplifier and power.

PICTURE TUBES

	WESTINGHOUSE Tung-Sol	Liberty
10BP4A	19.25	11.00
12LP4A	21.70	14.20
14CP4	24.50	16.50
16AP4A	30.95	21.60
16DP4A	28.20	20.60
16GP4	31.25	21.60
16KP4/RP4	28.20	18.00
17BP4A	23.90	18.00
17CP4	23.90	21.60
20CP4	32.50	27.00
21EP4	37.35	32.50
24AP4A	78.50	65.00

ANTENNAS

V. Antenna . . $1.95 — Window Con. . . 3.50 each
10 EL. Con. . . . 2.75 each — Indoor V. Antenna . . 1.19 each

MASTS

5 ft. swedged . . . 65c each 10 ft. seamless. . . . 1.25

WIRE

55 mil. 300 ohms. 10.95 70 mil. 300 ohms. 12.95

SPEAKERS

4" P.M. . . . . 1.29 5" P.M. 1.39
6 x 9 P.M. 3.49

CONDENSERS

50x30 150V .39 ea. 50x50 150V .49 ea.

KINE TUBE REJUVENATOR. . . . . 95c each

GRANCO UHF Converter $29.95

25% deposit must accompany all orders. Balance C.O.D. All prices F.O.B. New York City. If remittance is made with order, you can deduct 2%. $1.00 handling charge for orders under $5.00. Subject to prior sale.

ACE ELECTRONICS, INC.
2281 Nostrand Ave. BROOKLYN 34, N. Y.
CLoverdale 3-8010

Radio Products Sales Co.
1237 SIXTEENTH ST. • DENVER 2, COLORADO • CH 6591

has **hallicrafters**

- 10 Kc to 250 cycles in six steps!
- The most *stable* receiver made!
- Single Side Band Suppressed Carrier!

The Hottest Ham News in Years!

THE HALLICRAFTERS CO. • CHICAGO 24, ILL.

www.americanradiohistory.com

ice work. It has an isolated primary winding that permits servicing a.c.-d.c. sets without shock hazard. Electrostatically shielded, the LR is used to check intermittently operating radio and TV sets by dropping the line voltage to 105 volts or lower to detect a faulty oscillator. It can also be used to "cook" sets at 130-140 volts to break down intermittent parts.

For additional information write the company direct.

TRIO ANTENNA


A new single-bay, all-channel antenna has been added to its "Zig-Zag" line by *Trio Manufacturing Company* of Griggsville, Illinois.

Known as the "Twin-Six," the new antenna is ruggedly constructed, light in weight, and features single lead-in operation. The company states that it offers exceptional gain and, in addition, provides satisfactory u.h.f. reception in primary areas.

The new antenna is competitively priced and further details on it are available from the manufacturer.

CONVERTER-BOOSTER

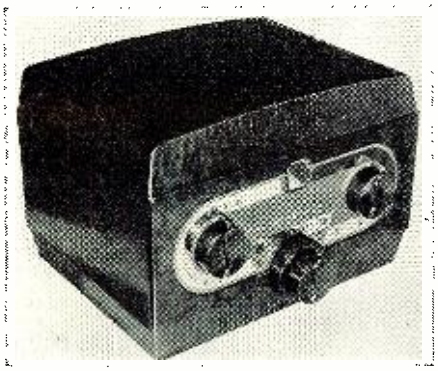Sutton Electronic Company of Lexington, Ky. is currently offering a



u.h.f. converter-v.h.f. booster combination housed in a compact cabinet.

Modern in design and the size of a small radio, the sturdy plastic cabinet is finished in marble-walnut with a gold panel. The new unit adds all u.h.f. channels to any TV set without sacrificing any v.h.f. channels.

The company will supply additional details on request.

SOLO LISTENING

Kentrol Corporation, 10 E. Coulter Street, Philadelphia 44, Pa. is now offering a compact headset unit which has been designed to permit personal TV listening.

The new unit has a 25-foot cord that can be run under a rug if desired. It can be easily attached to any set in 3 minutes and does not require wire cutting or splicing.

The company will supply additional details and price data on these units upon request.

RETRACE ERASER

Tele-matic Industries, Inc., 1 Joralemon St., Brooklyn, New York has announced a new service accessory which

NOW Soundcraft brings you Tape Perfection!

THE REVOLUTIONARY NEW

LIFETIME® magnetic recording tape



Like all Soundcraft magnetic products. LIFETIME Tape is Micro-Polished®, assuring maximum high-frequency response. It provides uniformity of ± ¼db. within a reel. and ± ½ db. reel-to-reel. It is splice-free in 600-, 1200- and 2400-foot reels.

Here is news of monumental importance to every recording perfectionist. It's the new Soundcraft LIFETIME Recording Tape. We've called this amazing high-fidelity tape "LIFETIME" because . . .

To the best of engineering knowledge, it will last forever!*

Your recording machine will never break it. Neither will careless handling. Because LIFETIME Tape is fully a third as strong as machine steel. It ends tape shrinkage and stretch when your home or studio air is dry or humid. It will never cup or curl. You can forget about storage problems.

All this means that for the first time you can preserve your important recordings, capture and keep those precious moments of music and the spoken word, for generations to come—in all their original fidelity!

LIFETIME Tape owes these new and permanent qualities to its new magnetic oxide coating, and to its base of duPont "Mylar" polyester film. For both are free of plasticizers whose gradual loss from ordinary tapes limits their useful life.

LIFETIME Tape is indeed the biggest development in tape since the tape recorder itself. Your serious recordings deserve it. Order your LIFETIME Tape today.

REEVES
SOUNDCRAFT
CORP. **Dept. U**
10 East 52nd Street
New York 22, N.Y.

***LIFETIME GUARANTEE.** Soundcraft unconditionally guarantees that Soundcraft LIFETIME Recording Tape will never break or curl, and that the magnetic oxide will never flake or crack, when the tape is used under normal conditions of recording and playback.

www.americanradiohistory.com

ALL RADIO AND TV TYPES

CLOSE OUT SET MFR'S SURPLUS TUBES

- STANDARD BRAND WARRANTY
- BRANDED
- BULK PACKED IN ORIGINAL MFR'S NESTED CARTONS OR INDIVIDUALLY BOXED
- EVERY TUBE METER AND CHASSIS TESTED FOR TOP QUALITY

OZ4	$ .49	6J5GT	$ .34	6BJ6	$ .46	6SR7	$ .49
1B3GT	.54	6J6	.51	6BL7	.76	6T8	.61
1L4	.47	6K6GT	.36	6BN6	.72	6V6GT	.41
1R5	.46	6L6GA	.99	6BQ6	.76	6W4GT	.41
1S4	.52	6SA7GT	.61	6BQ7	.76	6W6GT	.41
1S5	.38	6SC7	.81	6C4	.31	6X4	.49
1T4	.46	6SF5	.58	6C5	.41	6X5GT	.43
1U4	.46	6SH7	.65	6CB6	.42	12AT6	.31
1U5	.38	6AQ5	.38	6CD6G	1.08	12AT7	.57
1X2A	.52	6AQ6	.49	12AU7	.52	12AU6	.34
3Q4	.69	6SG7	.59	12AV7	.88	19BG6G	1.49
3Q5GT	.55	6AS5	.62	12BA6	.52	19T8	.61
3S4	.46	6AT6	.36	12BE6	.42	25AV5GT	1.05
3V4	.46	6AU6	.36	12BH7	.53	25BQ6GT	.79
5U4G	.44	6AV5GT	.79	12SA7GT	.59	25L6GT	.42
5Y3G	.36	6AV6	.36	12SG7	.61	25Z6GT	.49
6AC7	.68	6B4G	.79	12SH7	.49	35B5	.46
6AG5	.46	6BA6	.33	12SK7GT	.49	35C5	.46
6AH6	.61	6BA7	.76	12SN7GT	.46	35L6GT	.42
6AK5	.79	6BC5	.46	12SQ7GT	.49	35W4	.32
6AL5	.34	6BE6	.38	6SJ7	.54	35Z5GT	.33
6E5	.76	6BF5	.69	6SL7GT	.59	5OB5	.46
6F6GT	.54	6BG6G	1.16	6SN7GT	.46	5OC5	.46
6H6	.38	6BH6	.46	6SQ7GT	.49	5OL6GT	.42
						1I7Z3	.49

More than 400 Types in Stock—
Include all your needs when ordering.

MINIMUM ORDER: $10.00. Terms: 25% with order, balance C. O. D. Please include postage.
All prices subject to change without notice. F. O. B. New York City. Mail Order Division:

TRANSAMERICA ELECTRONICS CORP.
120 LIBERTY ST., NEW YORK 6, N. Y., COrtlandt 7-4307

AUDELS TV-RADIO SERVICE LIBRARY

HERE IS LATE INFORMATION IN A HANDY FORM FOR RADIO AND TELEVISION REPAIRMEN, SERVICEMEN AND STUDENTS



2 VOLS. $6 COMPLETE PAY ONLY $1 A MO.

AUDELS T.V.-RADIO SERVICE LIBRARY—Highly Endorsed—1001 Facts—Over 1552 Pages—625 Illustrations, Diagrams of Parts. Presents Important Subjects of Modern Radio, Television, Industrial Electronics, F.M., Public Address Systems, Auto, Marine & Aircraft Radio, Phonograph Pick-Ups, etc.

IT PAYS TO KNOW! The Basic Principles—Construction—Installation—Operation—Repairs—Trouble Shooting. Shows How to get Sharp, Clear T.V. Pictures. Install Aerials—How to Test. Explains Color Systems, Methods of Conversion, Terms, etc. Includes Ultra High Frequency (U.H.F.)—Valuable for Quick Ready Reference & Home Study. Tells How to Solve T.V. & Radio Troubles—Answers Your Questions.

Get this Information for Yourself.
7 DAY TEST—ASK TO SEE IT!

MAIL ORDER

AUDEL, Publishers, 49 W. 23 St., N.Y.10, N.Y.
Mail AUDELS T. V. RADIO SERVICE LIBRARY 2 Vols. $6 on 7 days free trial. If O. K. I will remit $1 in 7 days and $1 monthly until $6 is paid. Otherwise I will return them.

Name_____
Address_____
Occupation_____
Employed by_____ RN

NOW... enjoy luxurious hi-fi remote control!



with the beautiful Rauland LIBRETTO remote control



NOW you can have complete *remote control* of your present High Fidelity Music System with the LIBRETTO! This amazing control is completely self-powered and capable of operation several hundred feet from the amplifier. Uniquely fashioned in the form of a luxuriously bound book (only 8¾ x 11 x 2" thick). Backbone lifts for easy access to controls. Operates in either horizontal or vertical position. Controls: 1. Crossover; 2. Roll-off; 3. Volume; 4. Bass; 5. Treble. Adapter available for simple connection to your present system. Gives you the ultimate in luxurious Hi-Fi.

See the LIBRETTO at your Hi-Fi Dealer, or write for full details

RAULAND-BORG CORP.
3515 W. Addison, Dept. B, Chicago 18

Medal of Merit Int. Sight & Sound Exposition

is said to eliminate the annoying retrace lines that interfere with TV reception.

Known as the "Retrace Eraser," this plug-in electronic network permits the set owner to turn up the brightness and contrast controls and enjoy optimum reception without interference from retrace lines.

The unit is easily installed by plugging it into the back of the cathode-ray tube and connecting one lead to the yoke. Installation time is approximately 2 minutes.

U.H.F. CONVERTER

A redesigned, all-channel u.h.f. converter, the Model 88, is now available



from *P. R. Mallory & Co., Inc.*, distributor division, Indianapolis 6, Indiana.

The converter is 50 per-cent smaller than the company's previous model and incorporates all of the principles which have proven successful in that earlier model.

A single knob tunes all the u.h.f. channels in a total of 7½ turns. A second knob switches from u.h.f. to v.h.f. and also turns both the converter and TV set "on" and "off." When using the Model 88, the set may be left on either channel 5 or 6, whichever receives less external interference.

For more information write the company's distributor division.

"CASCADIAN" BOOSTER

Mark Simson Mfg. Co., Inc., 32-38 49th Street, Long Island City 3, N.Y. is



now in production on a new tunable v.h.f. TV booster which is said to increase the signal strength at least 35 db average on all channels.

The *Masco* "Cascadian" has been specifically designed to bring noise-free reception to new low-noise, high-

www.americanradiohistory.com

SYLVANIA *Presents*

The New Deluxe POLYMETER

TYPE 302

QUICK, ACCURATE MEASUREMENT OF COMPLEX WAVE FORMS



COMPOSITE VIDEO SIGNAL
Plate of video amplifier
175 volts P-P

COMPLEX WAVE FOR TRIGGERING
Grid of vertical oscillator
(180 volts P-P)

COMPLEX WAVE FOR DEFLECTION
Plate of vertical output tube
(700 volts P-P)



CUTS SERVICE TIME
READ DIRECT PEAK TO PEAK VOLTAGES

The new A.C. input circuit provides for full wave rectification to give you direct "P-P" readings of symmetrical and asymmetrical wave forms. This feature has been included in the new Polymeter to aid in measuring signals of a complex nature. A point to point search quickly localizes circuit failures and minimizes service time.

Engineered by
SYLVANIA
...world famous in electronics

Styled by
SUNDBERG AND FERAR
...leaders in industrial design

LABORATORY PRECISION ACCURACY FOR DIRECT MEASUREMENT OF...

- P-P voltages from .2v to 2800v.
- DC voltages of plus or minus polarity from .05v to 1000v.
- AC voltages from .05v to 1000v.
- RF voltages from .1v to 300v in the band of 10 kc to 300mc.
- Resistance from .5 ohms to 1000 megohms.
- Decibels from –20 db to +61.4 db

LOOK AT THESE PLUS FEATURES

- Peak to Peak Scale
- New Sylvania 7" Meter Movement
- Lighted Scale
- Sylvania Patented Linearity Circuit
- Sub-minature Vacuum Tube RF Probe
- 17 Megohm Input Impedance
- Shielded A.C. and RF Leads
- Screw-on Connectors

Available through your

SYLVANIA RADIO TUBE DISTRIBUTOR

Sylvania Electric Products Inc., Radio and Television Division
Williamsport, Pennsylvania

www.americanradiohistory.com

BECOME AN

ELECTRICAL ENGINEER





Bachelor of Science Degree in 36 months.

Major in Electronics or Power. Now, prepare for a career in these rapidly expanding fields.

This school will prepare you to become an engineer, technician or service man. Previous military, academic or practical training may be evaluated for advanced credit.

Enter Both Radio and Television

In 12 months you can attain the *Radio-Technician's* certificate. An added 6 months course qualifies you for the *Radio-TV Technician's* certificate and the Degree of "Associate in Applied Science." The Technician's course is the first third of the program leading to a Bachelor of Science Degree in Electrical Engineering with a major in Electronics.

Also offered: 12-month Radio-TV service course; 12-month Electronics or Electro Technician Courses; 6-month Electrical Service Course and 3-month refresher and general preparatory classes.

Terms Open April, July, Sept., January

Famous for its Concentric Curriculum. Faculty of specialists. 50,000 former students. Annual enrolment from 48 states and 23 overseas countries. *Non-profit. 51st year.* Courses approved for Veterans. Residence courses only.



MILWAUKEE

SCHOOL OF ENGINEERING

MILWAUKEE SCHOOL OF ENGINEERING
Dept. RN-254 1025 N. Milwaukee
Milwaukee 1, Wisconsin

Send: ☐ Free 45-page "Your Career" booklet describing Electrical Engineering Courses; ☐ Booklet on Careers in Radio-TV.

I am interested in.....
name of course

Name..... Age.....

Address.....

City..... Zone... State.....

If veteran, indicate date of discharge.....

gain television receivers as well as to older style receivers. The booster uses a special low-noise circuit employing a 6BZ7 tube.

A single control knob provides simplicity of operation. The metal cabinet, finished in two-tone brown and tan, can be used in any setting. The booster is automatically switched "on" and "off" by the TV set.

GUYLINE WINCH

Royal Television Supply Co., P.O. Box 1383, Modesto, California is now offering a new guy line winch which has been tradenamed "Royal Giline Winch."


The new product is designed to simplify and improve guy line installations. Its design for one bolt mounting makes for speedy installation. The channel and ratchets are made of 12 gauge steel with drums of heavy steel rods. The entire unit is electroplated. A cotter pin locks firmly in place against the ratchet pawl. A turn of the wrench gives proper tension on the line.

A data sheet on the new winch is available on request.

REMOTE CONTROL

The *Regency Division, I.D.E.A.*, 7900 Pendleton Pike, Indianapolis 26, Ind. is now offering a remote control unit which is operated on a single conductor cable.

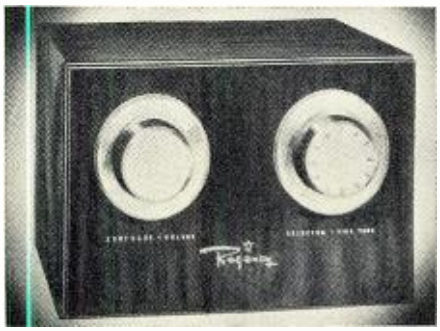Capable of being installed by an experienced technician in 15 minutes, this versatile unit selects stations, adjusts fine tuning, and controls contrast and volume at distances up to 100 feet.



The new control has been designated as the Model RT-700.

ADHESIVE FOR TV

National Adhesives, 270 Madison Ave., New York 16, N. Y. has developed a permanently tacky, solvent-type adhesive for TV production use.

The Resyn 35R2625 is painted on in all areas where there is contact between the cabinet and metal parts in order to trap chips and dust fall. The tacky film holds these minute particles, thereby keeping the inside of the set clean and reducing unnecessary service calls.

Manufacturers desiring further details on this adhesive for production applications may obtain full details from the company direct.

—30—

Admiral TV Receivers

(*Continued from page* 60)

overdriving the video amplifier, and will cause horizontal picture jitter, bending or tearing, and possibly complete blanking out of the picture, especially in strong signal areas. In using the "DX Range Finder," keep its setting as low as possible consistent with satisfactory pictures.

In early runs (1 and 2) of the 23A1 chassis, a.g.c. voltage for the r.f. amplifier (V_{101}) and the 1st and 2nd video i.f. amplifiers was obtained at test point "T," between R_{333} and R_{337} to ground. To reduce tube noise (snow in the picture) in the 23A1 chassis stamped run 3, the a.g.c. voltage for the r.f. amplifier is held at a lower negative value than the a.g.c. voltage at test point "T". The a.g.c. voltage applied to V_{101} is determined by a resistor network consisting of R_{333}, R_{337}, R_{350}, R_{351}, and R_{352} between test point "T," "B+," and ground.

Sync Separators. The sync separator (V_{403}) also receives a portion of the composite video signal from the video amplifier plate circuit. The sync separator, the sync clipper, and V_{401B}, the sync inverter, separate the sync pulses from the rest of the video signal and then direct these pulses to the vertical and horizontal sweep oscillators. The three separator stages are so designed as to effect as clean-cut a separation as possible, while at the same time minimizing the effects of noise pulses. This is achieved by the careful choice of "B+" operating voltages and the use of *RC* networks throughout these stages.

Vertical Deflection. The vertical oscillator (V_{401A}) is of the familiar blocking variety, preceded by an integrator network. An unusual aspect of the circuit is condenser C_{411}. This is incorporated to filter out any 15,750 cycle horizontal pulses picked up on the grid from the horizontal deflection circuit that would tend to trigger the vertical oscillator, causing poor interlace or vertical flutter.

In the vertical output stage, V_{402}, a 6AV5 pentode provides sufficient voltage to sweep the full height of the picture tube. Also provided by this circuit is a vertical retrace blanking pulse. Condenser C_{406} couples the negative pulse present at the vertical output transformer to the grid of the picture tube. C_{318} and R_{346} properly shape the waveform to insure cut-off of the picture tube only during the vertical retrace interval.

Horizontal Deflection. In the horizontal deflection system there is a 6AL5 sync discriminator, a 6SN7GT horizontal oscillator, and a 6CD6G output amplifier. The sync discriminator develops a d.c. voltage across R_{429} that is proportional to the phase difference between the received sync pulse frequency and the sweep voltage developed by the horizontal oscillator. This d.c. voltage is then fed to the

www.americanradiohistory.com

TUBES & PARTS

ALL TUBES are guaranteed for one year . . . individually boxed. Very BEST BRANDS available for immediate delivery!

0A46	1.04	2A6	89c	6AH6	1.89	6BH6	69c	6K5GT	.69	6SQ7	59c	7C5	.89	12AU7	.79	12SN7GT	.99	26	59c	57	79c
0Z4	59c	2A7	.89	6AK5	.89	6BJ6	1.19	6K6GT	.59	6SQ7GT		7C6	79c	12AV6	.59	12SQ7	69c	27	.99	58	1.49
0Z4G		2B3	.89	6AK6	1.08	6BK7	1.19	6K7GT	.69	6SR7GT		7C7		12AV7	.89	12SQ7GT		35A5		70L7	
1A5GT	.79	2B7	.89	6AL5	69c	6BL7	.79	6K8GT	1.19	6SS7	.99	7E5		12AW6	1.19	12SR7GT		35B5		70L7GT	
1A7	.69	2C34	.60	6AQ5		6BN6	1.19	6L5G	.95	6T7G	1.15	7E6	79c	12AX4	.69	12Z3	.95	35C5	69c	71A	.87
1A7GT	.79	2E5	.89	6AQ6	.81	6BQ6G	1.19	6L6G		6T8	.89	7E7		12AX7	.69	14A7	1.05	35L6		75	.79
1B3GT	.95	2X2/879	.74	6AQ7	1.19	6BQ6GT	1.19	6L6GA	95c	6U5		7F7	.89	12AY7	1.95	14AF7	.93	35W4	.59	77	.69
1B5	.29	3LF4	1.25	6AR5	.79	6BQ7	1.29	6L7	1.19	6U6GT	69c	7F8	1.47	12BA6	.59	14B6	89c	35Y4	99c	78/6D6	1.10
1H5GT	.59	3Q4	.69	6AT6	.59	6BZ7		6N6G	1.40	6U7G		7G7	1.19	12BA7	1.19	14B8		35Z3		80	.69
1J6GT	69c	3Q5GT	.89	6AS5	.90	6C4	.59	6N7GT	1.19	6U8	.89	7H7	1.05	12BE6	69c	14C5	1.25	35Z4	.75	83	1.45
1L4		3S4	.69	6AU5GT	1.29	6C5GT		6P5GT	.69	6V3	1.29	7K7	1.19	12BF6		14C7	1.12	35Z5	.55	84/6Z4	.72
1L6	1.29	3V4	.95	6AU6	.59	6C6	69c	6Q7GT	.59	6V6GT	.69	7L7		12BH7	.89	14F7	1.05	35/51	.79	85	.79
1LA4	1.19	5T4	1.40	6AV5GT	.89	6C8G		6R7GT	.69	6W4GT	.59	7N7	.79	12BY7	.89	14F8	1.45	36	1.06		
1LA6	1.19	5U4G	.59	6AV6	.59	6C8	1.29	6S4	.59	6W6	.69	7Q7	.79	12BZ7	1.19	14H7	1.12	37	.93	VR90	
1LC5	.69	5V4G	.87	6AX4	.69	6CD6	2.49	6S7GT	1.15	6X4	59c	7R7	1.19	12F5GT	.65	14Q7	1.05	38		VR105	$1.19
1LC6	1.19	5W4	59c	6AX5	.79	6CD6G	1.69	6S8GT	1.25	6X5GT		7S7	1.19	12H6	.89	14W7	1.19	39/44	88c	VR150	
1LD5		5W4GT		6AX6	.69	6CF6		6SA7GT	69c	6X8	1.29	7V7	.79	12J5GT	.75	14X7	1.19	41	.72	VT51	29c
1LE3	1.19	5Y3GT	.45	6AY5GT	.89	6D6/78	1.19	6SC7		6Y6G	.69	7W7	1.19	12K7GT	.69	19BG6	1.89	42	.69	VT52	
1LH4	1.19	5Y4G	.54	6B4G	1.44	6D8G	1.15	6SD7GT	.99	6Z4/84	.72	7X7	1.05	12K8	.89	19BG6G		43	72c	117L7	1.40
1LN5	1.19	5X4G	81c	6B8GT	1.15	6E5	.69	6SF5	.59	7A4	.95	7X7	79c	12Q7GT	.89	19T8	.89	45		117N7	1.95
1N5GT		5Z3		6BA6	.59	6F5GT	59c	6SF5GT	.59	7A5	1.19	7Y4		12S8	.89	20	1.40	45Z5	.69	117P7	1.95
1P5GT	79c	6A3	1.68	6BA7	.89	6F6GT		6SG7		7A6	.89	7Z4	.89	12SA7GT	.69	24A	.69	46	89c	117Z3	.59
1Q5GT		6A7	89c	6BC5	.69	6F7	1.59	6SH7	69c	7A7	79c	12A7	1.59	12SC7	1.05	25AC5GT	1.04	47		117Z6	1.19
1R5		6A8GT	69c	6BC7	1.05	6F8G	1.53	6SH7GT	.69	7A8	.89	12A8	.69	12SF5GT	.69	25BQ6	1.19	50A5	1.05	715B	7.75
1S4	.99	6AB4		6BD5GT	.89	6G6G	.95	6SJ7	.79	7B4	.89	12AH7	1.38	12SF7	.99	25BQ6GT		50B5	69c	807	1.55
1S5		6AB7	1.15	6BE6	.59	6H6GT	.89	6SJ7GT	59c	7B5	.89	12AL5	.54	12SG7	.89	25L6GT	.59	50C5		866A	1.49
1T4	69c	6AC5GT	.89	6BF5	69c	6J5GT	.59	6SK7GT		7B6	.89	12AT6	.59	12SH7GT		25W4GT	.69	50C6G	1.39	1299	
1U4		6AC7	1.45	6BF6		6J6	.79	6SL7GT	.69	7B7	89c	12AT7	.89	12SJ7GT		25Z5	.69	50L6	.69	1619	49c
1U5	.59	6AF4	1.19	6BG6	1.89	6J7G	.69	6SN7GT	.69	7B8		12AU6	.69	12SK7GT	69	25Z6GT	.69	50X6	.69	2051	1.15
1V	89c	6AG5	1.05	6BG6G		6J8G	1.15			7C4	1.30			12SL7GT		32L7GT	1.15	50Y6	.99		
1X2A		6AG7	1.49																		

SPECIAL

10% DISCOUNT

on orders of 100 tubes or more, 5% DISCOUNT on orders of 50 to 99 tubes.

FREE

$20 list value assortment of filter condensers with order of 50 or more tubes.

Write for our free BARGAIN CATALOG

Regency All channel UHF Converter Hottest news in UHF history. The Cadillac of UHF converters NOW $14.96 net

Picture tube brightener 5.95 list dealer cost $1.95

TV Arrow antenna to receive UHF, VHF, or UHF-VHF $2.95

Midget Radar Outdoor UHF antenna $4.77

Bazooka Hottest antenna in town! For UHF and VHF reception. Durable and rugged $9.95

TV 2-set antenna couplers $1.17 ea.

Flyback Transformer TV Horizontal output, universal replacement, 14,500 V. $2.49 ea

70 degree cosine yoke with 4 leads and network $2.95 ea.

Write for our free BARGAIN CATALOG

FILTER CONDENSERS

FP Type or Tubular With Leads. Fresh Stocks Always

8 mfd.	450 V.	.35	10 mfd.	50 V.	.19
8-8	450 V.	.45	20-	50 V.	.19
10-	450 V.	.39	25-	50 V.	.19
10-10	450 V.	.45	50-	50 V.	.25
20-	450 V.	.45	100-	50 V.	.29
20-20	450 V.	.49			
30	450 V.	.45	20 mfd.	150 V.	.35
30-30	450 V.	.59	20-20	150 V.	.45
40	450 V.	.49	30	150 V.	.45
40-40	450 V.	.69	30-30	150 V.	.49
60	450 V.	.69	40	150 V.	.49
60-40	450 V.	.89	40-20	150 V.	.49
80	450 V.	.69	40-40	150 V.	.49
80-40	450 V.	1.29	50-30	150 V.	.49

Teleron TV Wave Trap



For VHF Channels 2 through 13. Clears VHF picture, stops interference at once. 30 seconds to attach.

ea. net $1.75

All UHF channels $2.75

RADAR TYPE TV ANTENNA



For UHF and VHF

RECEIVES ALL CHANNELS

212 miles reception recorded. 125 miles common. This unbeatable antenna has been reinforced to withstand 150 mile winds.

Satisfaction guaranteed or your money back. Less Mast. List Price $49.95

Your Cost $19.95

5 ft. ALUMINUM MAST heavy gauge 1¼" diam. with interlocking end. Slip two sections together for a ten-footer. 5 sections = 25ft.


Each section $1.25

MOLDED BY-PASS CONDENSERS

50 Condensers assorted in package $6.95

600 VOLT			
.001	9c	.05	12c
.002	9c	.1	13c
.005	9c		
.01	12c	400 VOLT	
.02	12c	.25 mfd.	ea. 13c
		.5 mfd.	ea. 23c

TV Antennas

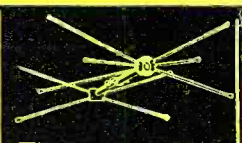


10 Element conical . . . rugged throughout. Only $3.95

Double bay array, with stacking bars .. $7.75

4 Bay array, with harness and stacking bars $14.95

6 Element Conical. Only $2.95

JFD BOW TIE REFLECTOR

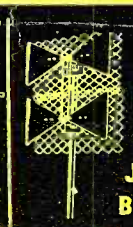

UHF Antenna

Bowtie Reflector

Ultra-high Gain

Completely assembled—ready to mount. For all UHF Channels — easy to stack for two or four-bay.

Single Bay $4.50

Two Bay, complete. $8.45



Standard Coil UHF TV tuner strips fit into your tuner in place of unused VHF strips. Set of strips consists of matched antenna & oscillator sections. For all channels 14 through 82. Specify channel wanted as well as letter indicating model of standard coil tuner such as 25K or 19Q or 31F/G etc.

1 set required per channel net each set $7.35


MISCELLANEOUS BUYS

I. F. TRANSFORMER—456 Kc. . . . 29c
PILOT LIGHTS. Type No. 47 10 for 39c; 100 for $2.95
VOLUME CONTROLS FOR SWITCH, 2" shaft. 1 meg, ½ meg, ¼ meg 34c
SINGLE ION TRAPS 19c
DOUBLE ION TRAPS ..... ea. 29c
OUTPUT TRANSFORMER—for SOL6 29c for 6V6, 39c
6-foot LINE CORD UL . . . 10 for $1.95
TV INTERLOCK CORDS ..... ea. 49c

SELENIUM RECTIFIERS

65 mil	.69
75 mil	.79
100 mil	.89
150 mil	1.29
250 mil	1.65
300 mil	1.75
350 mil	1.95
400 mil	2.45
450 mil	2.49
500 mil	2.55

THE DUAL LAZY H

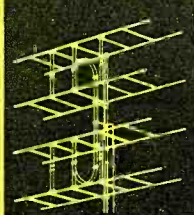


PRE-ASSEMBLED CO-LATERAL ARRAY

$29.35

The dual LAZY H. Only 6 connections instead of 40. A snap open Lazy H is the serviceman's desire for the UHF-VHF band. One lead in for high gain UHF-VHF. Strictly for the fringes.

UHF Antenna Kit

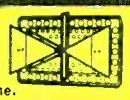

Includes everything you need.
1.) UHF bow tie antenna with reflector.
2.) 3 mast sections.
3.) Jumbo 300 ohm tubular transmission line.
4.) Sealer cap for UHF transmission line.
5.) Universal mast base.
6.) 50 ft. top quality guy wire.
7.) 3 screw eye anchors for guy wire.
8.) Guy wire ring.
9.) 3 stand off insulators for 300 ohm transmission line.
10.) 2 mast stand off insulators for 300 ohm transmission line.
11.) Illustrated instructions for quick, easy assembly.

All in one carton for only $7.65

Double bay array complete as above plus 5 mast sections and matching device for proper stacking $11.77

RESISTOR KITS

Insulated ½, 1 and 2-watt assortment of most used values, I.R.C. Ohmite, Stackpole, Speer. 100 for $2.95

TELEVISION PICTURE TUBES

Rectangular Tubes Are Supplied With Daylight Type Dark Face

SIZE	PRICE	SIZE	PRICE
7JP4	17.95	17HP4	25.10
8BP4	23.00	17TP4	
10BP4	15.95	19AP4	28.70
12JP4	18.60	19DP4	
12UP4	19.95	19FP4	
14BP4	21.20	20CP4	29.95
15AP4	23.50	21AP4	32.30
16AP4	23.95	21EP4	
16DP4	23.80	21FP4	
16EP4	26.35	21MP4	
16GP4	23.80	24AP4	77.30
16JP4		24CP4	
16KP4	23.80	24DP4	98.50
16LP4		27EP4	
16RP4	21.80	27GP4	
16WP4		27LP4	99.95
17BP4	25.10	27MP4	
17GP4		27NP4	
17CP4		27RP4	

ONE FULL YEAR WARRANTY ON ALL TYPES

SEND US YOUR ORDER AND WE WILL SHIP FROM STOCK IMMEDIATELY

P. M. SPEAKERS



32" COAXIAL PM SPEAKERS. High Fidelity with Crossover filter attached. 20 watts; 40-19,000 cps. response: 8 ohm Voice-Coil. ea. $12.95

15" COAXIAL SPEAKER. 20-17,500 cps. ea. $19.95

Very best quality — NATIONAL BRANDS. Individually Packed.

3"	ea. $1.35
4"	ea. 1.55
5"	ea. 1.55
6"	ea. 1.79
8"	ea. 1.21
10"	ea. $5.10
12"	ea. $5.95

6" SPECIAL PRICE .....

TV CONVERSION KITS



Easily Installed consisting of rectangular tube, 70 degree yoke, beautiful mask, flyback transformer and width coil.

17" Conversion Kit, as above, complete	$24.95
20" Conversion Kit, as above, complete	29.95
21" Conversion Kit, as above, complete	31.95
24" Conversion Kit, as above, complete	89.95
24" Conversion Kit, Round	69.95
27" Conversion Kit, as above, complete	129.95

27" Kit Contains 90° yoke

300 OHM TWIN LEAD



55 Mil, 100 ft.	$ 1.59
1,000 ft.	13.95
20 Ga. 80 Mil. 100 ft.	1.89
1,000 ft.	16.95
UHF TUBULAR 300 OHM LINE 1,000 ft.	$34.50
100 ft.	$4.95

TUBE KITS

BEST BRANDS AT BEST PRICES



3V4, 1T4, 1R5, 1S5 ..... $2.19

3Q4, 1T4, 1R5, 1S5. List Value $8.00. Tube Kit only. $1.98

3S4, 1T4, 1S5, 1R5, List Value $7.80. 4-Tube Kit ... $1.98

1U4, 3S4, 1S5, 1R5. List Value $7.80

All Four Tubes for $1.98

1T4Z3, 1U5, 3S4, 1R5, 1T4. AC-DC Portable Kit. All for $2.49

12AT6, 12BA6, 12BE6, 35W4, 50B5. 5 Tubes for ... $2.59

50L6GT, 35Z5GT, 12SA7G. 5 Tubes for $3.22


12SQ7GT, 12SR7GT, 12SN7GT, 12AV7, 12AT7, 12AU7, 12BA7, 12AX7, 12AY7, 12BE6, 12BA6, 12BH7, 12AV6, 12AW6, 12AX4, 12BY7, 12BZ7, 12SA7GT, 12SK7GT, 12SL7GT, 6SN7GT, 6SQ7GT, 6SR7GT, 6X5GT, 6AT6, 6AV6, 6AQ5, 6BA6, 6BE6, 6C4, 6CD6G, 6K7GT, 6SA7GT, 6SK7GT, 6V6GT, 6W4GT, 6AU6, 6AL5, 6BG6G, 6F6GT, 6K8GT, 6SC7, 6SH7GT, 6SJ7GT, 6SL7GT, 6X4, 6AX4, 6BN6, 6BQ6GT, 6CD6, 6CF6, 6D6/78, 6E5, 6F5GT, 6F8G, 6G6G, 6H6GT, 6J5GT, 6J6, 6J7G, 6J8G, 6K6GT, 6L6GA, 6SG7, 6SH7, 6SJ7, 6SK7, 6SQ7, 6T8, 6U8, 6X8, 6Y6G, 6Z4/84, 7A4, 7A5, 7A6, 7A7, 7A8, 7B4, 7B5, 7B6, 7B7, 7B8, 7C4, 7C6, 7C7, 7E5, 7E6, 7E7, 7F7, 7F8, 7G7, 7H7, 7K7, 7L7, 7N7, 7Q7, 7R7, 7S7, 7V7, 7W7, 7X7, 7Y4, 7Z4, 12A7, 12A8, 12AH7, 12AL5, 12AT6, 12AU6, 12AV6, 12AW6, 12AX4, 12AX7, 12AY7, 12BA6, 12BA7, 12BE6, 12BH7, 12BY7, 12BZ7, 12F5GT, 12H6, 12J5GT, 12K7GT, 12K8, 12Q7GT, 12S8, 12SA7GT, 12SC7, 12SF5GT, 12SF7, 12SG7, 12SH7GT, 12SJ7GT, 12SK7GT, 12SL7GT, 12SN7GT, 12SQ7, 12SQ7GT, 12SR7GT, 12Z3, 14A7, 14AF7, 14B6, 14B8, 14C5, 14C7, 14F7, 14F8, 14H7, 14Q7, 14W7, 14X7, 19BG6, 19BG6G, 19T8, 20, 24A, 25AC5GT, 25BQ6, 25BQ6GT, 25L6GT, 25W4GT, 25Z5, 25Z6GT, 32L7GT, 26, 27, 35A5, 35B5, 35C5, 35L6, 35W4, 35Y4, 35Z3, 35Z4, 35Z5, 35/51, 36, 37, 38, 39/44, 41, 42, 43, 45, 45Z5, 46, 47, 50A5, 50B5, 50C5, 50C6G, 50L6, 50X6, 50Y6, 57, 58, 70L7, 70L7GT, 71A, 75, 77, 78/6D6, 80, 83, 84/6Z4, 85, VR90, VR105, VR150, VT51, VT52, 117L7, 117N7, 117P7, 117Z3, 117Z6, 715B, 807, 866A, 1299, 1619, 2051

TERMS: 25% DEPOSIT with order, balance C.O.D. ALL shipments F.O.B. Chicago. ORDERS LESS THAN $5.00—$1.00 SERVICE CHARGE. CABLE ADDRESS: CONTULAB. These prices supersede all previously advertised prices, subject to change

PREMIER RADIO-TV SUPPLY, division of CONTINENTAL CORPORATION
3239 West North Avenue, Chicago 47, Illinois · ARmitage 6-5550

www.americanradiohistory.com

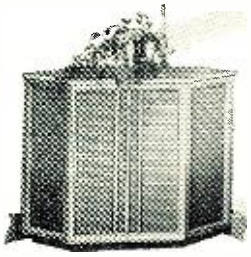2 New Ways to Cure... Home-monic distortion*



Angle Genesee's new chairside cabinet solves the space and budget conscious audiophile's equipment housing problem to perfection! A proud piece of furniture . . . for record player, tuner, pre-amp, and amplifier.

And the new A-G corner enclosure makes good speakers sound better! Adjustable baffles. Both in traditional mahogany or contemporary blonde oak! See your dealer or write us — we'll tell you where. Get the full details now on these and other A-G cabinets, *designed for any combination of hi-fi equipment.* Replaceable panels permit revision and expansion of sound system.



*Home-monic Distortion is a wife's eye-view of unsightly bare wires, glowing tubes, naked speakers.

ANGLE GENESEE CORPORATION

107 NORRIS DRIVE, ROCHESTER 10, NEW YORK

COMPLETE COLOR TV STORY

INTRODUCTION TO COLOR TV

by Kaufman & Thomas

Complete story on NTSC color system. Explains the color TV receiver circuits—how color receiver differs from black and white, how single and triple gun color tubes differ from black and white picture tubes. Answers all questions on present day color TV.

Over 100 pgs. illus. . . $2.10

JOHN F. RIDER PUBLISHER, INC. 480 Canal St., N.Y. 13 N.Y.

HEADSET SALE!

HS-33 . . . . . $4.50 each

HS-23 . . . . . $4.00 each

BRAND NEW

TALLEN CO., Inc., Dept. RN

159 Carlton Avenue, Brooklyn 5, New York

MOSLEY WALL-FEED

TV LEAD-IN ENTRANCE For Homes and Trailers

- Low Cost!
- Easy to Install!
- Attractive Appearance Wins Customer Approval!
- Weather-proof!
- For All UHF and VHF Lines!



Cat. 626
MOSLEY WALL-FEED
List Price, $1.26

available at Radio and Television Parts Distributors—coast-to-coast.

MOSLEY ELECTRONICS, INC.

8622 St. Charles Rock Road — St. Louis 14, Missouri

grid of one triode section of the horizontal multivibrator where it causes the generated frequency to change as required to keep in step with the frequency of the incoming sync pulses.

In the horizontal output amplifier, a special high voltage, high current 6CD6G tube is used to meet the necessary power requirements in this circuit. This includes the horizontal deflection coils, the high-voltage rectifier, and the damper tube. The latter tube, a recently developed 6V3, suppresses oscillation in the horizontal deflection coils and then converts the oscillatory current that flows after retrace into useful "B+" voltage which is added to the voltage delivered by the power supply. Beneficiaries of this boosted voltage include the horizontal output amplifier, the vertical oscillator, and grid number 2 (pin 10) of the picture tube.

Width control is obtained by using one winding of the width control coil, L_{402}, as a variable inductance to change the loading of the horizontal output transformer T_{404}, and at the same time, using the other winding as a variable inductance in series with the horizontal deflection coils. The inductance of the width control coil is varied by a slug moving out of one winding and into the other winding. Thus, when the inductance of the winding connected across the secondary winding of the horizontal output transformer is maximum, the inductance of the winding in series with the horizontal deflection coils is minimum. This condition results in minimum loading of the horizontal output transformer T_{404}, by the shunt winding of the width coil, and maximum transfer of energy to the horizontal deflection coils, resulting in increased width. This type width control coil provides a constant load on the horizontal output transformer and results in little or no change in the second anode voltage for the picture tube as the width control is varied.

Power Supplies. An important aspect in the servicing of any television receiver is the ability to trace your way through the d.c. distribution system. In radio receivers, the simplicity of the circuit permits all the stages to feed directly off one "B+" line. In television sets, however, not all tubes have the same voltage requirements and while it is possible to step down voltages to a desired value by means of voltage divider networks, the power wasted in this way can be considerable. A more efficient approach is employed in the 23A1 chassis in the form of two separate low-voltage power supplies. See Fig. 2. One, labeled the "H.V. Rectifier" (V_{502}), develops a voltage of 280 volts past the filter; the other, labeled the "L.V. Rectifier" (V_{501}), develops 150 volts past the filter. Both systems are relatively independent of each other, although the a.g.c. tube, V_{307} uses the +280 volts for its screen grid and the +150 volts for its cathode. The picture tube cathode ties into the +150-volt line, the control grid connects to the 280-volt line, and

www.americanradiohistory.com

XCELITE Hand Tools
PREFERRED BY THE EXPERTS


TO "LICK" THAT NEXT JOB, MAKE SURE YOU'VE GOT WHAT IT TAKES!



XCELITE PR "99"
Multi-Purpose Kit

AND! It's Now Available with Detachable Reamer!

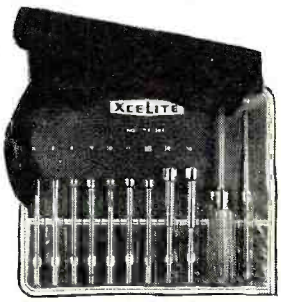Tops in shops, and "out" on gobs of jobs, the "99" has all it takes! Contains 13 quick-change nut drivers and regular and Phillips screwdrivers, all fitting that husky, man-sized Xcelite handle. (Now more useful than ever with the new Xcelite super-hard reamer!) —and a complete "tool chest" you CAN take with you—a real buy at only $11.95, less your discount.



See Your Xcelite Dealer NOW!

XCELITE, INCORPORATED
(Formerly Park Metalware Co. Inc.)
DEPARTMENT E
ORCHARD PARK
NEW YORK

For Originality LOOK TO XCELITE

GERMANIUM

Do you know Radio Receptor Company gives

Instant attention to Diode

Orders, and prompt

Deliveries on many types—

Especially JAN types 1N34A, 1N69, 1N70, 1N81.

So why not consult with us now!

AND

TRANSISTORS

Diffused PNP Junction Transistors RR14, RR20, RR21 and RR34 in production quantities for applications in low level audio circuits. Also available hermetically sealed.

Seletron & Germanium Division
RADIO RECEPTOR COMPANY, INC.
In Radio & Electronics since 1922
SALES DEPARTMENT
251 WEST 19th ST., NEW YORK 11
FACTORIES IN BROOKLYN, N. Y.

Attention!! • EXECUTIVES • SALESMEN • PUBLIC OFFICIALS • POLICEMEN • FIREMEN • OUTDOOR MEN REPORTERS • FIELD INSPECTORS • DOCTORS • LAWYERS, ETC.

DICTATE IN YOUR CAR with **ATR**



INVERTERS

for changing your battery current to **A.C.** *Household* **CURRENT** *Anywhere* .... in your own car!!

Announcing! NEW MODELS NEW PRICES

ATR INVERTERS . . . especially designed for operating standard 110 volt A.C. Tape Recorders, Wire Recorders, Dictating Machines and Electric Razors IN YOUR CAR.

EASY TO INSTALL
EASY TO OPERATE

There is an ATR INVERTER for most applications for inverting D.C. Voltages (ranging from 6 volts D.C. to 220 volts D.C.) to 110 volts A.C. . . . Specially Designed for operating A.C. Radios, Tape Recorders, Wire Recorders, Dictating Machines, Electric Razors, Record-Changers, Television Sets, Amplifiers, Address Systems, Radio Test Equipment and most small electrical and electronic devices FROM D.C. VOLTAGES IN AUTOMOBILES, BUSES, TRUCKS, SHIPS, TRAINS, PLANES AND IN D.C. DISTRICTS.

Additional information available upon request.

A VALUABLE TIME SAVER FOR:

- TRAVELLING SALESMEN—Dictate reports in your own car. Send your dictated reports in daily to your home office or sales manager.
- FIELD INSPECTORS & INVESTIGATORS—Dictate your field inspection reports in the field—on the spot. Give the complete story factually and completely. Include your clients recordings also.
- DOCTORS—Dictate and record your house calls on the completion of your call while everything is fresh in your mind. Have these records for transcription by your office girl.
- LAWYERS—Record evidence in the field at your client's premises. Obtain factual and complete witness reports, etc.
- EXECUTIVES—Dictate in your car all business matters while on trips for pleasure or business.
- PUBLIC OFFICIALS—Dictate complete field reports in your car. Obtain recorded opinions and expressions of Mr. Public in the field. Dictate your business reports while traveling.
- POLICE SQUAD CARS—Dictate accident reports right on the scene complete and factual. Include witness recordings at the same time. Have the complete story available by dictation.
- FIRE TRUCKS—Dictate your fire reports factually and complete on the scene and include witness reports. Have the complete story.
- AMBULANCES—Dictate complete reports of your ambulance run. Include witness recordings, etc.
- ADVERTISING AGENCIES—Use AC operated animated or illuminated displays in or on the car.
- FISHERMEN & HUNTERS—Use your electric razor on camping trips, operating in your car. Also small home radios and other electrical or electronic items.
- CAMPERS—Make your camping and outing trips more exciting using mix-masters, tape recorders, or wire recorders operating from your car battery.
- WAREHOUSE & MATERIAL HANDLERS—Dictate your inventory and material handling reports on the scene, in the warehouse, yard, or wherever you may be.

Announcing!

NEW **ATR** INVERTERS

New models New features New prices

WRITE FOR NEW FREE LITERATURE


See your jobber or write factory

√ NEW MODELS √ NEW DESIGNS √ NEW LITERATURE

"A" Battery Eliminators, DC-AC Inverters, Auto Radio Vibrators

ATR AMERICAN TELEVISION & RADIO CO.
Quality Products Since 1931
SAINT PAUL 1, MINNESOTA—U. S. A.

www.americanradiohistory.com

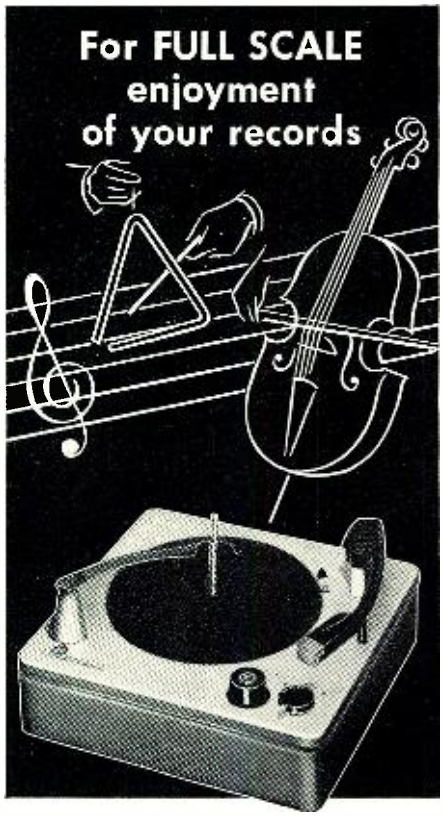

Model 936HF $69.95*

Model 935HF (without base pan) $59.95*

V-M tri-o-matic®

936HF HIGH FIDELITY RECORD CHANGER ATTACHMENT

Every note on your finest records makes its contribution to your pleasure . . . when fully and faithfully reproduced by the unmatched V-M 936HF high fidelity record changer attachment. Here, for your enjoyment, is the first automatic, 3-speed changer specifically designed, feature by exclusive feature, to satisfy the rigid standards of high fidelity enthusiasts. The beautiful gold and burgundy 936HF plugs into the amplifying system as easily as plugging in a lamp, needs only a horizontal surface on which to rest.

WORLD'S LARGEST MANUFACTURER OF PHONOGRAPHS AND RECORD CHANGERS EXCLUSIVELY



V-M Portable HIGH FIDELITY P-A System. Includes V-M tri-o-matic 960 changer, V-M 160 8 Watt amplifier and 10" Jensen speaker, in two matched cases.

Slightly higher in the west.

the Voice of Music

PLEASE MAIL COUPON

V-M Corporation, Benton Harbor 4, Michigan

Please send illustrated folder, "Bring Concert Halls Within Your Walls."

NAME_____

ADDRESS_____

CITY_____ STATE_____


grid number 2 receives its positive voltage from the boosted "B+". A diagram such as that shown in Fig. 3 can be of considerable assistance in tracking down defects in the receiver, especially when they concern abnormal d.c. voltages.

Table 1 contains the video and sound i.f. alignment procedure of the *Admiral* television receiver. The various slugs and test points mentioned in the chart can be readily located from Fig. 4. Also useful, not only for alignment, but service as well, is the tube location diagram, Fig. 5. Unless a man deals exclusively with one type of set, and very few technicians do, such a chart is one of the most useful service aids available.


U.H.F. Reception

Reception of u.h.f. signals on *Admiral* receivers is accomplished in one of two ways: either by the insertion of u.h.f. strips for unused v.h.f. strips in the turret tuner, or by the addition of a continuous tuning type of u.h.f. tuner to the standard v.h.f. turret tuner.

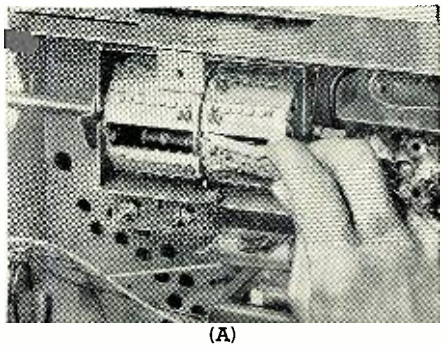The installation of the u.h.f. strips is illustrated in Figs. 6A and 6B. First, remove a pair of channel coils for an unused v.h.f. channel from the turret of the TV tuner. For convenience in tuning the set, it is suggested that the coils removed be adjacent to the coils for a v.h.f. channel in operation. Then, the u.h.f. channel strips are inserted



(A)

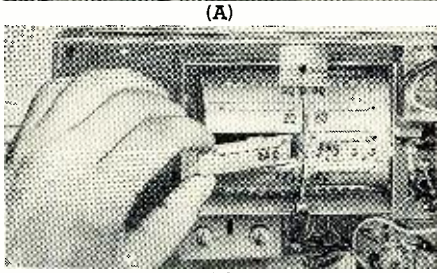


(B)

Fig. 6. Installing u.h.f. strips in a turret tuner. (A) Inserting the 5-contact antenna strip, (B) slipping in the 6-contact oscillator-converter strip.

in the usual manner, starting with the antenna (5 contact) strip first and then the oscillator-converter (6 contact) strip. The oscillator-converter strip has a connecting pin extending from one end which must be carefully fitted into the metal sleeve at the end of the antenna strip.

Fig. 5. Tube location chart for the Admiral 23A1 television chassis.

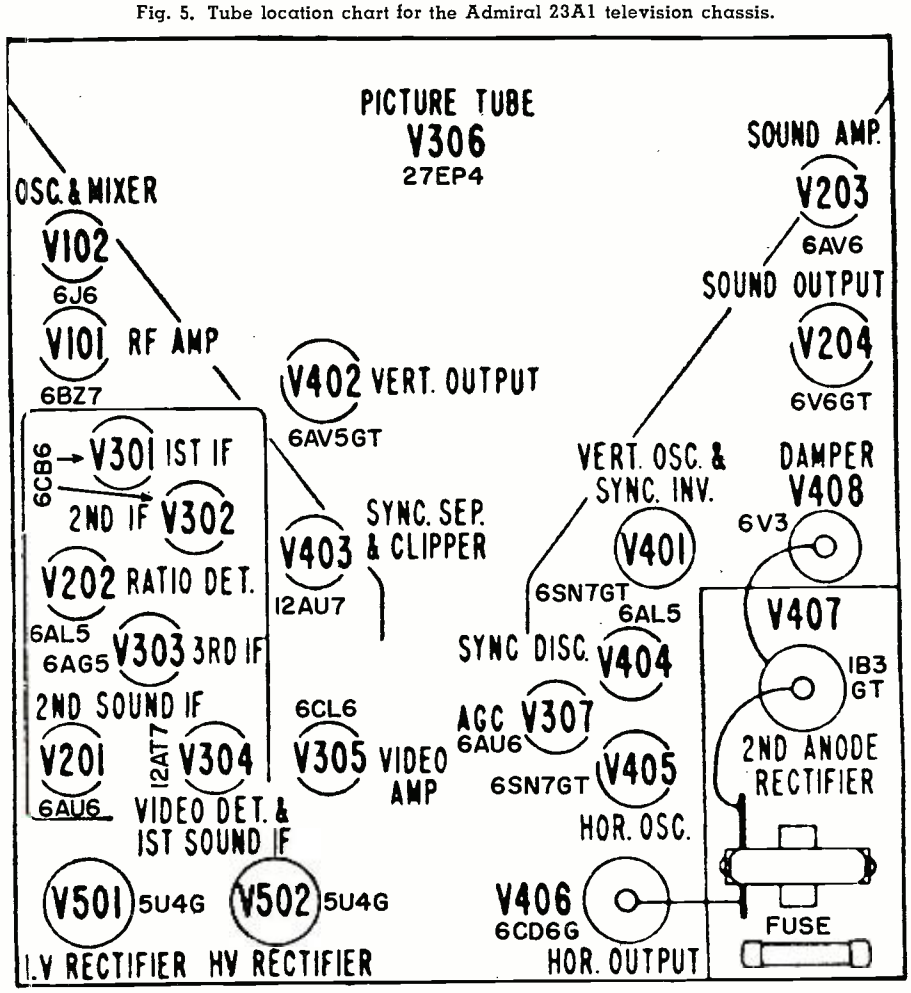


www.americanradiohistory.com



"Don't bother him, Junior. He's all tied up in a deal with Walter Ashe."

HAM GEAR

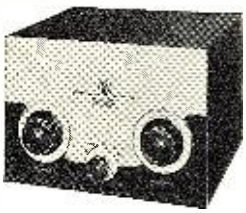JOHNSON MATCH BOX—
Bandswitching antenna coupling system. Model 250-23
Net $49.85






JOHNSON STANDING WAVE RATIO BRIDGE. Model 250-24. Net $9.75



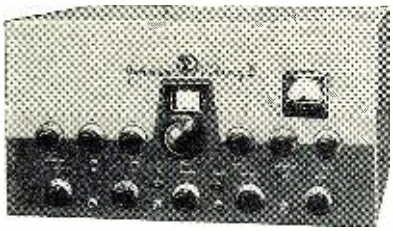JOHNSON SIGNAL SENTRY —Phone and CW monitor. Model 250-25. Net $14.70




JOHNSON VIKING II TRANSMITTER KIT
Net $279.50

JOHNSON VIKING II WIRED AND TESTED
Net $337.00


No matter how you "figure" it . . . a "Surprise" Trade-In allowance is the best, money-saving way to dispose of used (factory-built) test or communication equipment in exchange for the new instrument of your choice. Get your trade-in deal working today. Wire, write, phone or use the handy coupon below.

FIXED OR MOBILE

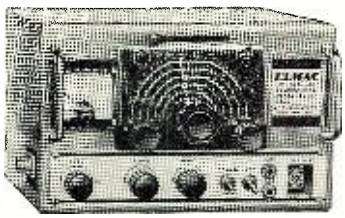

NEW ELMAC AF-67 TRANS-CITER— VFO or crystal controlled. Complete phone or CW transmitter, ideal for home installation or for under-dash mobile operation. Complete with tubes. Net $177.00

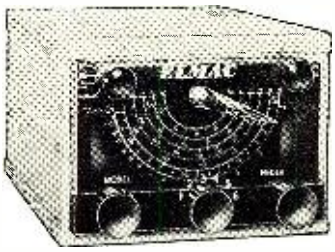ELMAC MOBILE RECEIVER. Dual conversion, 10 tubes, VFO, noise limiter, covers all amateur bands 10 through 160 meters plus BC band.



Model PMR-6A	For 6 Volts	Net $134.50
Model PMR-12A	For 12 Volts	Net $134.50

HALLICRAFTERS RECEIVERS		NATIONAL RECEIVERS	
Model S-38C	Net $ 49.95	Model SW-54	Net $ 49.95
Model S-40B	119.95	Model NC-88	119.95
Model S-76	199.95	Model NC-125	199.95
Model SX-71	249.95	Model NC-183D	383.50
Model SX-88	499.95	Model HRO-60	533.50

All prices f.o.b. St. Louis
Phone CHestnut 1125

Walter Ashe RADIO CO.
1125 PINE ST. • ST. LOUIS 1, MO.

FREE CATALOG!

RN-2-54

WALTER ASHE RADIO COMPANY
1125 Pine Street, St. Louis 1, Missouri

☐ Rush "Surprise" Trade-In Offer on my_____

for_____
(show make and model number of new equipment desired)

☐ Send new FREE 1954 Catalog.

Name_____

Address_____

City_____ Zone_____ State_____

Send for your copy today

www.americanradiohistory.com

3 Super Standard Output Transformers

±1 db 20—30,000 cycles
High Efficiency
Small Size

S-510-F, 10 watts
Pri: 10,000ΩCT-8,000ΩCT
Sec: 16-8Ω

S-526-F, 20 watts
Pri: 6,600ΩCT-5,000ΩCT
Sec: 16-8-4Ω

S-542-F, 40 watts
Pri: 5,000ΩCT-4,000ΩCT
Sec: 16-8-4Ω

	Dimensions Inches	Wt. lbs.
S-510-F	2⅞—2¾—2½	2
S-526-F	4⅜—3 1/16—2¾	3
S-542-F	4 15/16—3 9/16—3 9/16	5½



Write today for the Peerless Catalog

PEERLESS
Electrical Products
A DIVISION OF ALTEC LANSING CORPORATION
9356 Santa Monica Blvd., Beverly Hills, Calif.
161 Sixth Avenue, New York 13, New York

There are several precautions to observe when installing these u.h.f. strips.

1. If more than one set of u.h.f. channel strips is to be installed, they must not be inserted adjacent to each other.

2. The transmission line from the tuner to the antenna terminal board should be straight. If any loops exist, these should be removed.

3. Handle u.h.f. strips very carefully so lead dress and spacing between wires and components is not disturbed. The antenna strip should always be inserted first for ease in installation and protection against damage to the connecting pin.

The continuous u.h.f. tuner is physically located directly in front of the v.h.f. tuner. See Fig. 7. The channel selector and fine tuning control shafts for the v.h.f. tuner protrude through the hollow channel selector shaft of the u.h.f. tuner. Thus, the channel selector and fine tuning controls of the two tuners operate independently of each other.

Circuitwise, the u.h.f. tuner appears as shown in Fig. 8. The u.h.f. signal is coupled to the first tuned line of the preselector circuit by a coupling loop CL_1. The loop is center-tapped in order to provide a balanced 300-ohm input. The signal from Z_{1A} is transferred to the second tuned line Z_{1B} by means of coupling loop CL_2. To provide the most uniform coupling over the entire tunable range, the loop is placed as close as possible to the point of current maximum.

Coupling from the second tuned line Z_{1B} to the cathode of the 6AM4 mixer tube, V_1, is provided by coupling loop CL_3. Tuning is accomplished by means of variable condensers.

A Colpitts oscillator, employing a 6AF4 tube, is used as a local oscillator. To sustain oscillation, feedback is provided by the cathode circuit; the plate is grounded by condensers C_3 and C_4. Two condensers are used to reduce lead inductance which would restrict oscillation at the high end of the u.h.f. band. The r.f. choke, L_5, is effectively the load for the 6AF4 tube and keeps the cathode at an r.f. potential above chassis ground. The oscillator frequency is varied by tuning line Z_{1C} with condenser TC_1. Condenser TC_1 is ganged to preselector condensers TC_2 and TC_3.

For tracking purposes, a low-fre-


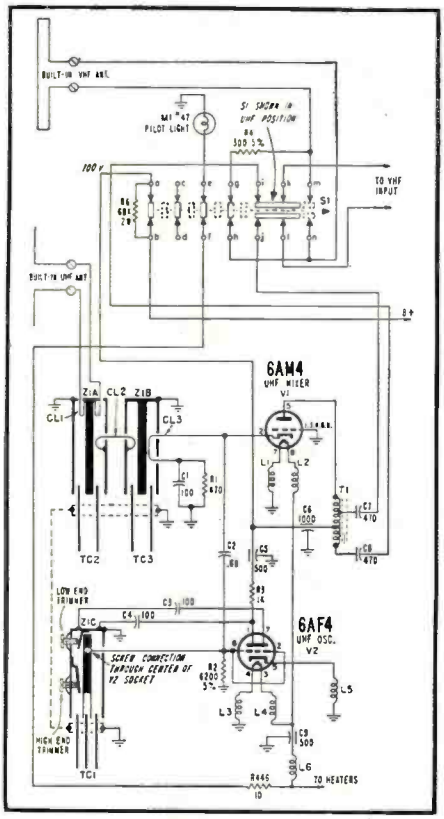


Fig. 8. Schematic diagram of the u.h.f. continuous tuner described in the text.


Fig. 7. Combination turret-type v.h.f. and continuous-type u.h.f. tuner used by Admiral; the v.h.f. tuner is in the rear, u.h.f. in the front.

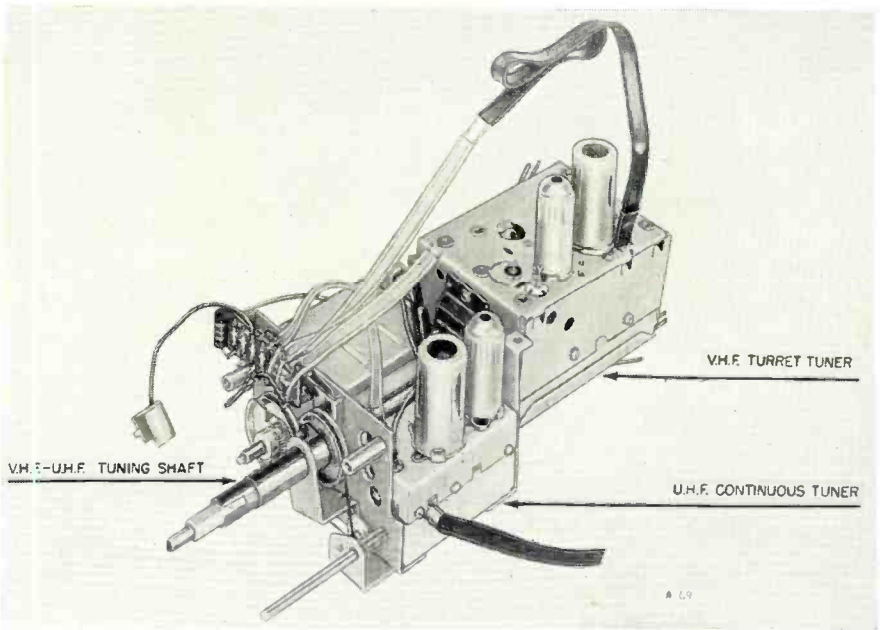

www.americanradiohistory.com

Now! RAD-TEL Tubes & Parts At Savings!

Wafer Rotary Switch Kit

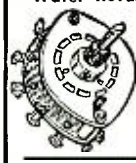

A choice combination of single, double, etc., from 2 to 8 positions. Special kit of 10

$1.39

Smashing Reductions on FP CONDENSERS



All famous makes. Save plenty on these top quality FP Condensers. Made by leading manufacturers. You can't miss—these values are hits no matter how you look at them!

CERAMICON KIT

1 kit of 50 assorted ceramic discs, biplates, tubular condensers. All condensers popular sizes, used in T.V. and F.M. sets. A MUST kit



List price $10.00

$1.99

Hi-Watt RESISTOR KIT

Consisting of 5, 10, 15 and 20 Watt vitreous type resistors by Ward, I.R.C., etc. A top-flight buy!



$1.95 Assorted Kit of 20

Filter CONDENSER KITS*



*(10 to a pkg. min.)

Kit of 10 20-20. List Price $15 . . . . $3.25

Kit of 10 40-40. List price $15 . . . . $3.25

Kit of 10 50-30. List price $15 . . . . $3.25

FILTER CONDENSER

20-20 Mfd, 450 V.



Color-coded leads. Ideal for use where impossible to use metal cans. For top performance at a give-away price. List price $2.40.

49c

BIAS CONDENSERS



Sangamo, Aerovox, Cornell-Dubilier

500 mfd 12V List Pr. $2..35c ea. Pkg. of 10 . . . . $2.95

SPECIAL . . . .

4-50 mfd 8-100 VDC Kit of 7 . . . . . $1.29

CAN ELECTROLYTICS

Mfd. by SPRAGUE AEROVOX PHILCO, Etc.

Capacity	DC Working Voltage	Price
40-40-40	450-450-25	$.99
250-1000	10-6	.49
40	450	.49
60-10-10-20	450-450-450-150	.89
80-40-10	450-450-450	.99
20-8-8-8	450-450-450-250	.59
80	500	.79
15-15-20	450-450-25	.59
40-10-100	450-450-200	.79
10-20	450-25 F.P.	.39
10-8-8-8	450-450-450-150	.49

Kit of 10 Assorted Electrolytic Condensers

Consists of singles, doubles, triples and quadruples, all of popular voltages and capacities—all standard popular brands.

$2.39

National Turret T.V. BOOSTER



Made by National, famed for quality and precision communications equipment. Turret selects each channel. Completely self-contained including tube and selenium rectifier for A.C. operation. Housed in metal cabinet. In factory-sealed cartons with complete instructions.

List price $39.95 . . . . . **$9.95**

25 Paper BY-PASS CONDENSERS



An assortment of 25 by-pass condensers, made by leading manufacturers. Top quality. Most popular sizes and voltages. Values .002 to .2 MFD 200 to 1000 VDC.

KIT OF 25 **99c**

Hi-Voltage POWER SUPPLY

4500 VOLTS 6 MA.

12AU7 oscillator, 183 rectifier



Completely wired, enclosed in shielded metal case, removable cover. Use as R.F. high voltage supply.

BRAND NEW! **$2.95**

Kit of 2 tubes for above—$1.08



FLY BACK TESTER

"A Must for every Serviceman!"

Fast, sure horizontal trouble-shooting. Responsive to as small a defect as a 1-turn shot. Tested while in receiver! Tests continuity on yokes, coils, speakers, switches, etc.

Your Price **$39.95**

VARIABLE CONDENSERS

Mfd. by Philco, Radio Condenser, etc.



2 Gang AM and FM contains 2 separate sections for AM and 2 for FM with padder condensers. Attached a stug tuned high frequency coil whose plunger is geared to condenser shaft. Pulley type drive wheel 89c

2 Gang AM Equipped with drum pulley and padders 79c

3 Gang FM

3 Gang Superhet Complete with padders and drum pulley drive 89c



Kit of Wafer Sockets

Assortment of 6, 7, 8 and 9 pin sockets. These are brand new, standard manufacture. Kit of $0.$1.49

ALL BRAND NEW PARTS!

TRIMMER KIT




Compression type mica for radio, F.M., T.V. Very few duplications. Don't let this chance pass you by!

25 FOR . . . **99c**

FILAMENT ISOLATION TRANSFORMER

6.3 V @ 1.2 A

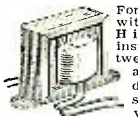

For damper use with 6W4, etc. High voltage insulation between primary and secondary to withstand high voltage surge. Can be used for general replacement. 79c

List price—$1.75

RCA Type FLYBACK TRANSFORMER Type 215T1



Lowest net price elsewhere—$4.70 At this give-away price, order in quantity while they are available. Each . . 95c

Vertical OUTPUT TRANSFORMER



Very popular, used in most T.V. sets. Well-known manufacturer. Matches vertical output tube to the deflection yoke. 10 to 1 ratio. A terrific buy on a top performer 95c

List price—$4.50

BIG SAVINGS YOU CAN'T PASS BY! 70° YOKE

Mfd. by TODD, SICKLE & other top Mfrs.



Very good value, makes conversion profitable and simple. Get 'em while they're still around! . . $1.95

List price—$7.50

55° YOKE . . . 99c

Horizontal Output TRANSFORMER



Type 204T1

A horizontal Output Transformer designed for deflection circuits employing rf-operated high-voltage supplies. Intended for 30° magnetic-deflection kinescopes. Used with RCA Deflecting Yokes 201D1, 201D2, 201D3 or 201D12 . . . . . **$2.95**

List price—$13.95

HIPO TV rectifier tube—replaces the 5U4 tube directly! Makes pictures bigger, brighter, larger and increases the gain in TV receivers. HIPO 567 . . . . . **$1.39**

RESISTORS

(Assortment of 200)

Standard RTMA Coded or Value Printed. Uninsulated. ½ Watt, 1 Watt, 2 Watt, and Some 10 Watt. RAD-TEL SUPER BUY!!! Assortment of 200 for $1.39

List price—$10.00

Kit of 50 MICA CONDENSERS



All popular sizes of mica condensers. In regular and silver construction. For FM and TV use . . . **$1.95**

List price—$12.50


American Makes Kit of 100 Insulated RESISTORS



50 - ½ and ⅓ watt, 25 - 1 Watt, 25 - 2 Watt. All new, all clean. Good value $2.65

List price—$15.00

Hi-Voltage T.V. CONDENSERS

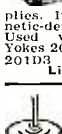

500 mmfd 10KV. $ .39 ea.
500 mmfd 15KV. .49 ea.
500 mmfd 20KV. .49 ea.
500 mmfd 30KV. 1.59 ea.

Volume Control Kit



Kit of 10 includes 3 wire-wound, 2 dual post, 5 carbon

The price of one (1) for the quantity of ten (10). Short and long shaft.

PER KIT $1.79



KNOB KIT (Choice Groups!)

Assortment of home, auto, and T.V. knobs. All colors—plastic, wood and bakelite knobs.

Bag of 50 . . . . . $1.29

Super Bag of 100 extra val. 1.95

Sells from 12c to 18c each.

..OLD FASHIONED SAVINGS!

Cathode Ray TUBE REJUVENATOR



Fits all makes of picture tubes. Completely automatic. Easy to install, no tools needed. For A.C. parallel circuits. (Available for all sets.) $1.39

YOUR OLD PICTURE TUBES ARE STILL USEFUL

List price—$5.95

Everyone is a potential user—10 for $12.90

Army - Navy HEADSETS




Individually boxed. Very sensitive. Meets both Army and Navy specifications.

Ea. per set $2.95

List price—$16.00

SPEAKERS—All Standard Brands, Dynamic

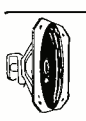

Size	Ohms	Price
3"	1000	79c
4"	1800 (tapped at 300)	79c
5"	4 (auto speaker)	79c
6"	2500	99c
10"	2500	1.49
4 x 6	1800	99c
4 x 6	2750	99c
5 x 7	1000	99c
5 x 7	1800	99c
5 x 7	2750	99c
6"	90 (with 6K6 output transformer)	1.49
8"	680 (with 6V6 output transformer)	1.95
6.5"	38	1.49

Alnico V P.M. standard brand Speakers

4" 1.47 oz. with 50L6 output transformer . $1.95

5" 1.47 oz. with 50L6 output transformer . $1.95

6" 2.15 oz. $2.19

4" .68 oz. with 50L6 output transformer . $1.89

4 x 6 . . . . . $1.95

5" 2.15 oz. $1.69

7½" 3.16 oz. Mopar $2.95

8" 2.15 oz. $2.95

10" 2.15 oz. with 6K6 output transformer . $3.95

12" Magnavox $5.95

Kit of BATTERY PLUGS

Polarized, 3, 4, 5, etc. 50 for **$1.69**

TERMS: A 25% deposit must accompany all orders—balance C.O.D. All shipments F.O.B. Irvington warehouse. Orders under $10—$1.00 Handling Charge. Subject to prior sale.

SOLDER LUG STRIPS

Kit of 48—very usable assortment of solder lug terminal strips. Brand new. Unusually fine value! Comp. Kit of 48 . . . . **89c**

List price $4.00

TERMINAL STRIPS

Assortment of 50 terminal strips (screw type). Kit contains wide selection to meet every design. Kit of 50 . . . . . **89c**

2, 3, 4 and 5 screw strips.

T.V., RADIO, and F.M. COIL KITS

Kit for television servicemen and experimenter consisting of width coil, peaking coil, 4.5 m.c. ratio detector, and 21.9 m.c. IF coil. TV. Standard kit of ten (10) 99c

TV. Super value; not duplicated. 25—$1.85

Broadcast and short-wave, midget to multi-band replacement coils.

BC. Standard kit of ten (10) 99c

BC. Super value; not duplicated. Kit of 25 . . . . . $1.85

BC kits include RF, Osc., IF, and detector coils.

Send for FREE Illustrated PARTS CATALOG

70% to 90% OFF ON TUBES!

All Tubes Individually Boxed!—1 Year Guarantee!—1 Day Service.

Type	Price	Type	Price	Type	Price
0A2	.74	6BN6	.59	12AY7	.99
0B2	.81	6BQ6	.79	12BA6	.38
0C3	.72	6BQ7	.90	12BA7	.60
0D3	.70	6BZ7	.90	12BD6	.45
0Z4	.55	6C4	.37	12BE6	.39
1A5	.30	6C5	.39	12BF6	.39
1A7	.47	6C6	.58	12BH7	.63
1AX2	.62	6CB6	.44	12BY7	.65
1B3	.68	6CD6	1.11	12BZ7	.65
1B7	.30	6E5	.48	12C8	.34
1C5	.43	6F5	.39	12J5	.42
1E7	.29	6F6	.59	12K8	.59
1G6	.24	6G6	.52	12Q7	.59
1H4	.30	6H6	.41	12S8	.62
1H5	.49	6J5	.43	12SA7	.65
1L4	.46	6J6	.52	12SF5	.50
1LA4	.59	6J7	.43	12SJ7	.67
1LE3	.59	6K5	.47	12SK7	.63
1N5	.67	6K6	.37	12SL7	.47
1P5	.57	6K7	.44	12SN7	.52
1Q5	.58	6L6	.64	12SQ7	.56
1R5	.49	6Q7	.45	12SR7	.49
1S4	.59	6S4	.38	12V6	.46
1S5	.43	6S8	.53	12X4	.38
1T4	.49	6SA7	.43	14A5	.59
1U4	.49	6SD7	.41	14AF7	.59
1U5	.43	6SF5	.46	14H7	.59
1V	.53	6SG7	.41	14J7	.30
1X2A	.63	6SH7	.49	14W7	.30
2A3	.30	6SJ7	.41	19BG6	.95
2A4G	.24	6SK7	.41	19C8	.70
2W3	.38	6SL7	.48	19T8	.69
2X2	.59	6SN7	.52	19V8	.79
3A4	.45	6SQ7	.37	24A	.39
3E5	.46	6SR7	.45	25AV5	.83
3Q4	.48	6557	.42	25BQ6	.79
3Q5	.49	6T4	.99	25L6	.39
3S4	.49	6T8	.56	25W4	.59
3V4	.51	6U4	.60	25Z5	.66
5U4	.50	6U5	.44	26	.45
5W4	.50	6U6	.59	27	.39
5Y3	.37	6U8	.61	35	.58
5Z4	.59	6V6	.39	35B5	.40
6AB4	.44	6W4	.44	35C5	.39
6AC7	.86	6W6	.44	35L6	.41
6AF4	.90	6X4	.37	35W4	.37
6AG5	.48	6X5	.37	35Z3	.59
6AH4	.57	6X8	.75	35Z4	.47
6AH6	.73	6Y6G	.48	35Z5	.47
6AJ5	.65	7A4	.47	36	.39
6AK5	.55	7A5	.59	41	.42
6AL5	.38	7A6	.69	42	.42
6AQ5	.39	7A7	.69	43	.55
6AQ6	.37	7AF7	.53	45	.55
6AR5	.37	7B4	.44	45Z3	.44
6AS5	.50	7B6	.69	45Z5	.49
6AT6	.37	7C4	.59	50B5	.43
6AU4	.68	7C5	.69	50C5	.39
6AU5	.82	7E5	.59	50L6	.61
6AU6	.38	7E6	.30	50Y7	.50
6AV5	.83	7E7	.59	53	.24
6AV6	.37	7H7	.59	57	.58
6AX4	.53	7L7	.59	58	.60
6B4	.64	7X7	.70	70L7	.97
6BA6	.39	7Y4	.69	76	.44
6BA7	.57	7Z4	.59	77	.57
6BC5	.49	12A8	.61	78	.47
6BD5	.59	12AL5	.37	80	.35
6BD6	.45	12AQ5	.52	83V	.68
6BE6	.39	12AT6	.37	85	.59
6BF5	.41	12AT7	.66	117L7	.99
6BF6	.37	12AU6	.38	117Z3	.37
6BG6	1.25	12AU7	.54	807	.99
6BH6	.46	12AV6	.39	866A	1.39
6BJ6	.43	12AV7	.63	1274	.30
6BK7	.80	12AX4	.56	2050	.89
6BL7	.83	12AX7	.56	1000FM	.59

RAD TEL TUB CO.

Ph. Essex 5-2947, Dept. RN-2, 115 Coit St., Irvington 11, N. J.

www.americanradiohistory.com

Reliance Specials



FILTER CHOKE—10 HY
400 MA. 90 OHMS
3500 VDC. Test
HERMETIC SEALED
Size: 5¼Lx4½Wx4H
$4.88



A LOT OF "SUDS" TO DO A LOT OF WORK
HIGH CURRENT Filament Transformer. Pri. 105-125 Vac 60 cy 1 Phase Sec. 5V @ 190 Amps. 97KVA. Insulated for 35 KV RMS. Just the thing to light up those 304TL's. Also ideal for welding, thawing frozen pipes, etc. Wt. 80 lbs. **$29.50**
7"x10"x12" FOB Phila.

OIL FILLED CONDENSERS

MFD	VDC	PRICE	MFD	VDC	PRICE
2	400	$0.55	3	2000	$3.75
6	400	.85	8	2000	7.95
1	600	.55	12	2000	8.95
2	600	.69	2	4000	7.95
3	600	.95	1	5000	4.88
4	600	1.65	1	6000	9.95
4-4-4	600	2.50	.02-.02	7000	1.55
5	600	1.65	.1	7500	1.75
6	600	1.85	.075-.075	8000	6.50
8	600	1.85	1	10KV	29.50
10	600	3.25	1	15KV	45.00
50	600	7.95	.075	16KV	8.95
1	1000	.69	.25	20KV	19.95
2	1000	.95	.001	50KV	24.50
4	1000	1.59	.025	50KV	42.50
.3	2000	1.30	.2	50KV	85.00
1	2000	1.95	.25	50KV	95.00

STORAGE BATTERIES—SHIPPED DRY
BB54 Willard plastic case. Built in charge indicator 2V 20 amp hrs. 4x3x5⅛ Hi. . **$1.95 EA.**
BB212/U—2V 40 amp. hrs.—6⅞x2⅛x4½ in. **EA. $2.35**
NT-6—6V 3.5 amp. hrs.—3½x1¾x2⅜ in. **EA. $1.95**

RG-8 U Brand New Govt. Surplus 100 ft. coil. **$5.95**
32 MFD 2500 VDC Fotoflash Condenser. . . . **$15.80**
IN34 Crystal 66c
2X2 TUBES RCA . . . . . 2 for 1.00
6SN7 TUBES SYL or Kenrad . . . . . 3 for 2.20
5BP1 CATHODE ray tube 5.50
1 MEG 1W 1% Prec. Resistor WW 1.50
GEAR ASST. 100 gears, bushings, etc. 6.50
HARDWARE ASST. 5 lbs. nuts, bolts, etc. 2.00
200 ASSORTED resistors ½W all insulated . . . 2.50
10 MA DC Meter 3" Rd. DeJur ±310 . . . . . 3.95
1 MA DC Meter 3" Rd. DeJur ±310 . . . . . 5.75
1 MA DC Meter Fan type 4" scale 3.95
5 AMP AC Meter 4" Rd. JBT ±432 . . . . . 4.11
500 MA DC Meter 2⅛" Rd. G.E. 2.95
30 VDC Meter 2⅛" Rd. G.E. 3.95
500 MICRO amps DC Meter 2⅛" Rd. Sun 4.30
GLYPTAL CEMENT G.E. ±1286 . . . . . Qt. can 1.15
AT-4/ARN-1 Altimeter Antenna NEW 9.75
RT-7/APN-1 Altimeter Exc. Used 25.00
WE D 171584 Mercury Relay 8.75
AT-48/UP 3 CM Horn Antenna 9.95
INVERTER 6VDC to 110VAC 60 Cy 75W 22.95
BK 78 Sensitive Relay 4000 ohm ½ Mil SPDT . ea. 1.75

AIRCRAFT GENERATORS

OUTPUT—115 VAC 19.4 AMPS 800-1400 CY 1 PH. PLUS 30 VDC 60 AMPS New **$29.50**
OUTPUT 30 VDC 15 AMPS 2500-4500 RPM 6" L x 5" DIA SPLINE SHAFT ¾ x 1½". WT. 16 lbs. NEW **15.50**
OUTPUT 28 VDC 140 AMPS 2500-4500 RPM New **38.50**



SOUND POWER PHONES
Sound Powered Handset TS-10 TYPE
Uses no batteries or external power source. Ideal for TV installation work, farms, construction projects, connecting outbuildings, extensions, etc., includes 5 ft. cord. Each **$9.48**

SOUND POWERED HEAD & CHEST SET
Navy type M head and chest set. Brand new. For work requiring free use of hands. Heavy duty—consists of headset with 2 phones and chest mike. Includes 20 ft. rubber cord. Each **$14.88**
Same as above except used exc. cond. Each **$5.95**

COAXIAL CABLE CONNECTORS

Full line of JAN approved coaxial connectors in stock.



83-1AC	$0.42	PL-274	$1.10	UG-88/U	$0.90
83-1AP	.30	PL-275	2.10	UG-89/U	1.10
83-1BC	.35	SO-239	.40	UG-102/U	.80
83-1F	1.10	UG-13/U	1.70	UG-103/U	.68
83-1H	.12	UG-18B/U	1.05	UG-104/U	1.40
83-1HP	.22	UG-20B/U	1.60	UG-105/U	1.50
83-1J	.73	UG-21/U	.85	UG-106/U	.15
83-1R	.40	UG-21B/U	1.00	UG-107B/U	2.75
83-1RTY	.65	UG-21C/U	1.05	UG-146/U	2.00
83-1SP	.45	UG-21D/U	1.45	UG-167/U	3.75
83-1SPN	.50	UG-22/U	1.30	UG-175/U	.12
83-1T	1.30	UG-22A/U	1.60	UG-176/U	.12
83-2AP	1.95	UG-22B/U	1.20	UG-185/U	.95
83-2J	2.10	UG-23/U	1.20	UG-196/U	1.65
83-2R	.65	UG-23B/U	1.50	UG-203/U	.65
83-22AP	1.40	UG-23C/U	1.10	UG-224/U	1.15
83-22F	2.10	UG-24/U	1.30	UG-255/U	1.95
83-22J	1.40	UG-27/U	1.25	UG-260/U	.85
83-22R	.68	UG-27A/U	2.25	UG-261/U	1.10
83-22SP	.80	UG-27B/U	2.95	UG-262/U	1.10
83-22T	1.95	UG-28A/U	2.95	UG-273/U	1.45
83-168	.12	UG-29B/U	1.75	UG-274/U	2.30
83-185	.12	UG-30/U	2.30	UG-290/U	.90
CW-123A/U	.45	UG-57B/U	1.85	UG-281/U	.95
M-358	1.30	UG-58/U	.70	UG-306/U	2.65
M-359	.30	UG-58A/U	.90	UG-414/U	1.95
M-359A	.65	UG-89A/U	1.90	UG-469/U	1.25
PL-258	.75	UG-83/U	1.75	UG-625/U	1.35
PL-259	.45	UG-85/U	1.65	Quotations on All Other Types	
PL-259A	.50	UG-87/U	1.40		

NEW COAXIAL CABLES JAN APPROVED

	Price Per Ft.		Price Per Ft.
RG 8/U	12½c	RG 58/U	7½c
RG 11/U	12½c	RG 59/U	7c
RG 22/U	19c	RG 62/U	9c

Deduct 20% 500 ft. or more of a type.

TERMS—Cash with Order or 25% Deposit—Balance C.O.D. Net 10 Days to Rated Accounts. All Prices are Net F.O.B. our Warehouse.
Send for our Latest Bargain Catalog.

RELIANCE MERCHANDISING CO.
2219 ARCH ST., PHILA. 3, PA.

quency trimmer is used to set the local oscillator on channel 14 frequency. This trimmer is adjustable externally from the rear of the tuner. A high-frequency tracking fin is located near the tuning condenser plates (TC_1) and is set on channel 83 frequency. In later production tuners, the high-frequency tracking fin is replaced by a trimmer, which is adjusted at the factory externally the same as the low-frequency tracking trimmer.

The mixer uses a special u.h.f. triode connected as a grounded-grid amplifier. The 6AM4 tube is designed with low interelectrode capacitances and multiple grid pin connections to reduce lead inductance in the tube. The control grid and the multiple pin connections, spaced around the tube base, serve as a shield between plate and cathode. In addition to this, any energy fed back to the cathode is out-of-phase and oscillation will not occur.

Coupling loop CL_3 and condenser C_2 feed the u.h.f. signal and oscillator injection voltages to the cathode of the mixer stage. C_1 and R_1 provide cathode bias. The two voltages mix within the 6AM4 tube and the resultant frequency appearing in the plate circuit is that of channel 5 or channel 6 (v.h.f., 76 mc. to 88 mc.). Transformer T_1 and the mixer tube plate-to-ground capacity resonate at this first conversion frequency to form the mixer plate load impedance. A balanced 300-ohm output impedance is also provided by tapped transformer T_1. The d.c. blocking is accomplished by coupling condensers C_7 and C_8. Proper matching to the v.h.f. antenna is furnished for approximately 12 mc., so that either channel 5 or 6 can be used to receive the output of the u.h.f. tuner.

There are three series of chassis in the *Admiral* 1954 line. One of these, the 23 series, was described in this article. The second, the 22 series, differs principally from the 23 series in the design of the horizontal deflection system. Furthermore, because of this difference, the 22 series chassis requires only one low-voltage rectifier whereas the 23 series uses two. The third series of chassis is the 19 series and this is quite different from either of the other two. For one thing, it possesses 19 vacuum tubes against 22 for the 22 series and 23 for the 23 series. Other differences include a somewhat narrower video i.f. bandpass, use of the synchroguide a.f.c. system, a modified a.g.c. system, and a simpler sound system. All series, however, are available with the u.h.f. tuner, if desired.

All *Admiral* combination u.h.f.-v.h.f. receivers come equipped with two built-in antennas; one for u.h.f. and one for v.h.f. The v.h.f. built-in antenna is connected to the two lower antenna terminals at the top rear of the high-voltage cage, and the u.h.f. antenna is connected to the two upper terminals. If the set is positioned properly, external antennas may not be required. —30—

Mac's Service Shop

(*Continued from page 74*)

in the past that worked pretty well. This unit here, however, is representative of several new all-electronic remote controls that are being placed on the market by various manufacturers at this time; and these new units have several things to recommend them. In the first place, they can be installed easily and quickly and do not interfere with the normal operation of the receiver. It is a well-known fact that you can do a better job of adjusting a picture from the viewing position. That is proved by the wide use of that earliest form of remote control: a wife in her easy chair instructing her husband at the set exactly how to set the volume and contrast controls. Unless you are a contortionist, it is practically impossible to set the controls on the set without blocking the view of some of the watchers. Finally, a remote control unit fits in beautifully with the radio-phonograph-TV custom installations that are becoming so popular these days.

"I have been thinking these control units would be a good item for small shops such as ours to stock and sell," Mac said musingly. "They are small and take up very little room. Every owner of a set we repair is a potential customer. We have the jump on an ordinary store because only a service technician is in a position to install them.

"A technician friend of mine reports a kind of sneaky but effective way he has of selling them. When he has to remove a tuner and send it in for repair, he temporarily installs one of these units so the set can be used while the tuner is away. He says not a single set owner so far has let him remove the remote control when the repaired tuner is returned."

"Say, I think I know another use for that remote control unit," Barney exclaimed. "Suppose I run the output of that coax line through a blocking condenser into the antenna connections on my communications receiver tuned to twenty-one megacycles. Then a short piece of twin-lead, run through a high-pass filter to the tuner's antenna terminals ought to make a dandy probe for detecting TVI-causing harmonics leaking out of any transmitter. The receiver's S-meter would show instantly any change in the strength of those harmonics."

"It would probably work," Mac said with a grin; "but you remind me of a guy who can't watch a steam shovel at work without thinking about how he could use it to dig his garden potatoes."

Barney wandered across to the bench and picked up a large red-backed book lying by Mac's elbow. "What's this?" he asked.

"Handle that with care," Mac warned. "I had a heck of a time borrowing that copy. It contains the in-

www.americanradiohistory.com

for ENGINEERS, RESEARCHERS, DESIGNERS, EXECUTIVES only!

3 magazines in 1

The RADIO-ELECTRONIC ENGINEERING Edition of RADIO & TELEVISION NEWS is now three magazines in one!

RADIO-ELECTRONIC *Engineering*

A special engineering edition of RADIO & TELEVISION NEWS

1. RADIO & TELEVISION NEWS—for broad coverage: servicing AM—FM—TV, new products and developments in audio, radio, TV, broadcasting, amateur radio . . .
2. RADIO-ELECTRONIC ENGINEERING—for selected and exclusive engineering articles of lasting practical value. TV—Radio—Radar—Theory—Communications—Microwaves—Design . . .
3. TV & RADIO ENGINEERING—newly merged with RADIO-ELECTRONIC ENGINEERING for added engineering features on TV and Radio.

RADIO-ELECTRONIC ENGINEERING presents each month in addition to all RADIO & TELEVISION NEWS contents at least 6 important engineering articles. And now, incorporating the very best features of TV & RADIO ENGINEERING magazine, RADIO-ELECTRONIC ENGINEERING gives you the most extensive electronics coverage anywhere obtainable.



SUBSCRIBE TODAY

for SERVICE TECHNICIANS, AUDIOPHILES, AMATEURS, DEALERS, INSTRUCTORS, STUDENTS.

Save time, save money every month with the authoritative guidance of the world's most widely read electronics journal.

RADIO & TELEVISION NEWS

. . . brings you new and vital information on all phases of the fast-moving electronics field. Get the facts quickly, concisely, dependably in RADIO & TELEVISION NEWS.



SUBSCRIBE TODAY

www.americanradiohistory.com

formation *RCA* presented to the FCC when they were seeking approval of their color television system."

"What kind of information?"

"Just about any sort you can think of, from detailed engineering description of the apparatus used in transmitters and receivers to purely personal opinions of the observers."

"I've read a lot about color television," Barney remarked, "but I have never seen anything about how color receivers are going to compare with black and white sets in fringe areas. How will color reception be affected by things like adjacent channel interference and noise?"

Mac took the book from Barney and flipped the pages to a section near the center. "Ah, here we are," he said. "Color and monochrome sets are about equally susceptible to co-channel interference and to lower adjacent channel interference. Color sets, though, are a little more disturbed by upper adjacent channel interference. Color reception, too, is a little more susceptible than monochrome to random noise. However when the noise is of the impulse type, such as is produced by an electric razor, one type of reception is not bothered any more than the other. And for good measure, I might add that observers decided multi-path reception—'ghosts' to you—interfered a trifle more with the enjoyment of color reception. The important thing is, however, that in every comparison of the effect of interference on color and black and white receivers, the difference was slight."

"That must be a pretty complete report," Barney conceded, "but let's give it one more acid test. See if it can answer the same disturbing question everyone pops at me when I try to talk about color television: What color is the snow?"

A slow grin spread across Mac's wrinkled face. "I know the answer," he said, "but I must confess I did not find it in the book. I thought I knew what color it would be, but I was not sure; so when everyone out here in the fringe area kept asking the same question, I wrote to *RCA* and asked them. They came right back with a telegram, which made me feel that I was getting serious consideration of a rather silly question; but now we have an authoritative answer right from the horse's mouth.

"As we might have suspected, snow on color television can be, and is, any color through the whole spectrum. Since it is a manifestation of random noise, it affects the color circuits as well as the others; and this results in the snow's appearing as multi-hued sparkles of light."

Barney heaved a big sigh of relief. "It may be a silly question, but I'm surely glad they answered it. You can't imagine the awful thing it was doing to my ego to have to say, 'I don't know,' every time someone asked about the color of the snow. Now I'll just snap, 'It's technicolored, of course!'"

—30—



HAROLD J. SCHULMAN
director of service for
DUMONT
and chairman, service committee,
RETMA
says:


"...a product as complex as a television receiver cannot possibly be maintained satisfactorily without timely, understandable and helpful service information.

"...it is only through the efforts of the experts in the field, like yourself, that servicemen can expect a *steady flow of all-inclusive* service information.

"We have found your publications to be consistently *high in quality* and *integrity*. We particularly single out your current Parts Replacement Information program as a service to the industry."

Rider *TEK-FILE—NOW, only $1.50 per pack! (at your jobbers)

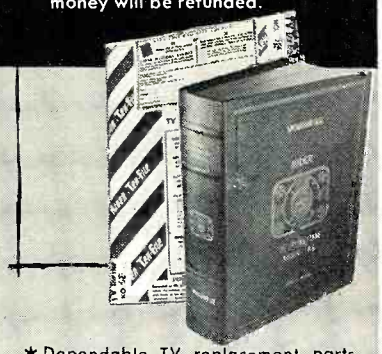Try a pack. If you're not satisfied, return the pack within 7 days and your money will be refunded.



* Dependable TV replacement parts listings starting with pack 57 and TV 10

JUST OUT! TV 12

Announcing!

RIDER RADIO MANUAL 23!

Out in February, Up-to-the-minute information on all home AM, FM radios built during 1952 and 1953.

JOHN F. RIDER PUBLISHER, INC. 480 Canal Street, New York 13, N. Y.

CRYSTALS

LARGEST STOCK IN THE WORLD



In FT 241-A Holders—½ in. Pin SPC. These are designated 54th or 72nd Harmonic MC freq. Listed by fundamental freq. with fractions omitted.

NOTE! HUGE PRICE REDUCTIONS! FREE GIFT OFFER BELOW.

COMPLETE SET—80 CRYSTALS
Ranging from 370-516 Kc., 54th Harmonic, INCLUDING 500 Kc. & 455 Kc. crystals. Only....Per set $6.95

COMPLETE SET—120 CRYSTALS
Ranging from 370-540 Kc., 72nd Harmonic, PLUS 500 Kc. & 455 Kc. crystals. Only.....Per set $9.95

200 KC. CRYSTAL.....Ea. $1.75
500 KC. CRYSTAL.....Ea. .75
1,000 KC. CRYSTAL.....Ea. 2.75

FREE WRIST COMPASS—On request with every $15.00 order for crystals.

MISCELLANEOUS BEST BUYS

ULTRA-VIOLET COCKPIT LAMP. Used..$1.95
PILLOW SPEAKER. Used..... 1.95
SOUND POWERED 2-WAY COMMUNICATION SET. With 50 ft. of wire. Palm type. Excel. cond. $3.35
24V. TRANSFORMER. Pri. 110 V. @ 2 amps. New $1.95

SPECIAL! 12 V. 35 AMP GENERATOR Ideal for mobile rig. Used. ONLY..$3.95

SILVER CIRCLE TUNER. Used. Ea. .....$1.25 3 for.....$2.95
GUY LINE: Ideal for TV and radio tower. Heavy duty, with turnbuckle on one end. New. Approx. 40 ft. length.....$1.25
10 Lengths (40 ft. ea.)..... 9.95
APS-13 TRANSCEIVER: Complete with tubes and dynamotor. Easily converted to 420 MC. Excellent cond. $14.95
PE-73 DYNAMOTOR. Used. As is.....$3.49
BARBEQUE MOTOR. AC. New..... 9.45

SPECIAL COMBINATION!
WILLARD 6 V. plastic storage battery for model control equipment. Uses standard electrolyte. NEW. (Orig. sold for $2.49.) PLUS REVERSIBLE MIDGET MOTOR. Operates on 1½-6 V. at top speed of 10,000 RPM. (Orig. price $1.95). NEW, BOTH units now only $2.79

All merchandise sold as is. Prices net F.O.B. Los Angeles. All items subject to prior sale.

J.J. GLASS ELECTRONICS CO.
1615 S. MAIN STREET
LOS ANGELES 15, CALIF.

NORMANDIE & RADIO ELECTRIC
532 CANAL STREET
NEW ORLEANS, LA.

has hallicrafters

- 10 Kc to 250 cycles in six steps!
- The most *stable* receiver made!
- Single Side Band Suppressed Carrier!

The Hottest Ham News in Years!

THE HALLICRAFTERS CO. • CHICAGO 24, ILL.

TELEVISION

PREPARE FOR A GOOD JOB!
BROADCAST ENGINEER
COMMERCIAL OPERATOR (CODE)
RADIO SERVICING

Television Servicing

(Approved for Veterans)
SEND FOR FREE LITERATURE
BALTIMORE TECHNICAL INSTITUTE
1425 EUTAW PLACE, BALT. 17, MD.

www.americanradiohistory.com

Color Alignment

(*Continued from page 54*)

transmitted, the white portion serves to allow color brightness adjustment. On the color test pattern the relative intensity of each primary color, not the hue, is dependent on the color contrast control setting. As a check on this adjustment observe the yellow portion of the test pattern to find any unbalance in the color contrast control setting. To sum up, the brightness controls are balanced out to obtain white, and the contrast controls are set for relatively equal color intensity and the correct shade of yellow.


Tri-color Tube Adjustments

Single gun color picture tubes are not much more difficult to adjust than ordinary picture tubes, therefore, this discussion is limited to the tri-color tube and its equivalents.

On any color tube the conventional adjustments for vertical linearity, height, width, and horizontal linearity are the first steps towards obtaining a picture. All these adjustments can be made by electrical controls on the chassis, without affecting the positioning of any of the components on the picture tube. In color TV the linearity, height, and width must be much better than in monochrome receivers and these adjustments should be made carefully and precisely. In addition to the conventional adjustments, a number of special color controls and settings are required at the tri-color tube. One type of adjustment is the physical placement and setting of the various components around the neck of the tube; the second series of adjustments are electrical controls for the operation of the tube.

In Fig. 7 are shown the various components mounted on the *RCA* tri-color tube. The purity coil assembly is placed next to the tube socket. This assembly consists of three parts: the outer shield, which is a magnetic shield and is usually grounded; the purity coil itself (shaded portion); and three threaded magnets. These three magnets are spaced 120 degrees apart and should be located directly over each of the three electron guns. Before starting the adjustment procedure, set all three brightness controls for zero brightness, set the convergence and

Fig. 7. Tri-color picture tube setup.

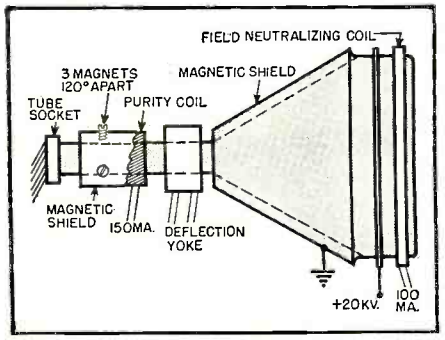



"Of the very best!"
—HIGH FIDELITY MAGAZINE

FISHER

SERIES "50"

It is only natural that more than one manufacturer will claim *his* product is the best. For that reason it remains for *you* to be the judge. We say—*demand the specs.* Then check workmanship, performance and beauty of appearance. If you do all these things, the answer will inevitably be . . . THE FISHER SERIES "50." There is no finer made.

THE FISHER **Master Audio Control** SERIES 50-C

■ "One of the finest units yet offered to the enthusiast or audio engineer." —*Radio and TV News.* Can be used with *any* amplifier. IM distortion virtually non-measurable. Complete, professional equalization settings and tone controls; genuine F-M loudness control; five inputs, five independent input level controls, two cathode follower outputs. Self-powered.
Chassis, **$89.50** • *With blonde or dark cabinet,* **$97.50**

THE FISHER **FM-AM Tuner** MODEL 50-R MODEL 50-RT

■ Features *extreme sensitivity* (1.5 mv for 20 db of quieting); *low distortion* (less than 0.04% for 1 volt output); *low hum* (more than 100 db below 2 volts output.) Armstrong system, *adjustable* AFC with switch, *adjustable* AM selectivity, separate FM and AM front ends (shock-mounted), cathode follower output, fully shielded, aluminum chassis, self-powered. **$164.50**

Model 70-RT, same as Model 50-R, but including tone controls, phonograph preamplifier-equalizer, and loudness balance control. **$184.50**

THE FISHER **50-Watt Amplifier** MODEL 50-A

■ Truly the world's finest all-triode amplifier, yet moderately priced. 100-watt peaks! Less than 1% distortion at 50 watts (.08% at 10 watts.) IM distortion below 2% at 50 watts. Uniform response within .1 db from 20 to 20,000 cycles; 1 db, 5 to 100,000 cycles. Hum and noise more than 96 db below full output. Quality components throughout. **$159.50**

Prices slightly higher west of the Rockies


WRITE TODAY FOR COMPLETE SPECIFICATIONS

FISHER RADIO CORPORATION · 39 EAST 47th STREET · N. Y.

www.americanradiohistory.com

384,000 MOBILE-RADIO RIGS NEED MAINTENANCE!

Make frequency and FM deviation checks on unlimited numbers of channels with just these 2 meters!

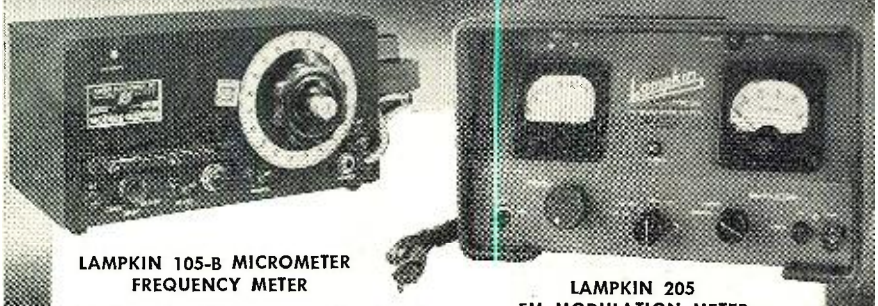

LAMPKIN 105-B MICROMETER FREQUENCY METER

Uses one crystal to measure all transmitters from 0.1 to 175 mc. Gives readings of percent error from assigned frequencies. Acts as precision CW signal generator for receiver final alignment.

PORTABLE — Width less than 13" . . . weight less than 14 lbs., each.

MEET FCC REQUIREMENTS—for mobile-service checks.

For low prices...and technical data... mail coupon today!

LAMPKIN 205 FM MODULATION METER

Direct indication of peak voice deviation, 0-25 kc positive or negative. Tunable 25-200 mc. in one band. Doubles as relative field-strength meter. Built-in speaker. Jack for oscilloscope.

LAMPKIN LABORATORIES, INC.
Bradenton, Florida

LAMPKIN LABORATORIES, INC.
MFM DIVISION
BRADENTON, FLORIDA
Without obligation, please send me data on Lampkin meters.

Name_____

Street_____


City_____ State_____

For Values You Know Check These from

$$ HARJO $$

APS 13 COMPLETE 420 MC RADIOPHONE

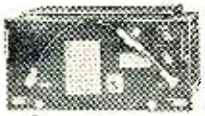when converted with our easy-to-follow schematics and instructions. Range in most cases equal to 2 meters. Fine for short-distance communication, ranches, farms, etc. **$4.95**



$14.95 value
Complete with RF sections, conversion booklet, and 30 MC I.F strip, less tubes, dynamotor.

Power Supply Kit
Supplies 24 V. AC for filaments and 250-300 V. DC for plate supply **$9.95**

CERAMIC CONDENSERS
Kit of 100 asstd. (25 mmf to .001 mfd). Brand new. Standard brands. $10 value. **$1** postpaid

SPECIAL VALUE
954 ACORN TUBES & SOCKETS All new. 4 sets **$1**

Brand New POWER TRANSFORMERS
110 V. 60 cy. primary
150 V. 30 MA secondary
6.3—1 Amp. Fil
FB for grid dip kits, test equip., etc. **79¢**

SPLINED TUNING KNOB—only 59c ea.
Really hard-to-find, but we have it. Fits BC-453, BC-454, and other 274N receivers.

PROP-PITCH MOTORS (See Feb. '53 issue Radio-TV News, p. 66) **$17.95**

MICRO SWITCHES. new ..... 4 for **$1.00**

SCOPE TRANSFORMERS—$2.95
Prim. 110 V., 60 cyc.
Secondary 3500 V., 25 ma., 10 KV ins.
Shipping wt. 15 lbs.

MORE CASH for your equipment! No haggling. Get what you want. Write today!

Write for FREE Surplus Catalog

All shipments F.O.B. warehouse.

HARJO SALES CO. Dept. RA

4109 Burbank Blvd., Burbank, Calif.
P. O. Box 1187, Magnolia Park Sta.
Cable: Harjo Phone: ROckwell 9-2411

New 1954 Edition Covers All Latest Developments, Including UHF and Color TV!



TELEVISION SERVICING

by Walter H. Buchsbaum

All New! 2nd Revised Edition
TRANSISTORS
COLOR
UHF and LATEST TV CIRCUITS

Get this brand-new, complete handbook for sure-fire working knowledge of TV installation, maintenance and trouble-shooting. Tells you step-by-step procedures for audio IF alignment, video IF alignment, aligning RF amplifiers, mixers, oscillators, etc. All possible defects classified for ready reference, thoroughly analyzed to show what is wrong and why . . . and what to do to correct the defect. No mathematical knowledge needed!

Part I—Principles of TV receivers, including all new 82 channels. Latest data and illustrations on UHF tuners, converters and antennae. Separate chapter covers the new, all electronic color TV system, explains for the first time all the standards, circuits and color picture tubes. Transistors, theater TV, industrial TV, etc.

Part II—covers latest installation and alignment techniques for all receivers. Both UHF and VHF alignment data for the newest TV models are given. Antenna installation, fringe area reception and apartment house installations are described.

Part III—the trouble-shooting section. Defects are classified according to symptoms and a detailed step-by-step procedure is given for locating and repairing all possible trouble.

USE IT 10 DAYS FREE

Coupon below brings you "Television Servicing" on FREE trial for 10 days, without obligation. Mail it NOW.

PRENTICE-HALL, INC., Dept. R-RTN-254
70 Fifth Ave., New York 11, N.Y.

Send me, for 10 DAYS' FREE TRIAL, "Television Servicing." I will return it in ten days and pay nothing—or keep it and send $5.95 (plus few pennies postage) in full payment.

NAME .....

ADDRESS .....

CITY..... STATE.....

SAVE! Send $5.95 with this coupon, and we'll pay postage and packing.

focus controls at their center positions, and set the purity coil and field neutralizing coil controls for zero current. Unscrew the three magnets on the purity coil assembly to provide minimum field. With high voltage on, adjust each of the brightness controls to obtain a raster. Next, connect a signal, monochrome or color, and adjust the focus controls to get focus over the entire screen. Check height, width, linearity, etc. as in monochrome receivers without regard to color.

To adjust for color purity cut the blue and green guns off, remove the test signal, and rotate the purity coil while adjusting the current through it until the center of the screen shows a uniform red pattern. The position of the deflection yoke along the neck of the tube will have a great effect on the purity of the red field along the edges. Another adjustment to be made for edge purity is the amplitude and direction of current through the large field neutralizing coil. When the optimum red field is obtained, check the green and blue fields next. It may be necessary to touch up some of the previous adjustments for best results on all the three colors. Recentering of the raster may also be necessary after the purity adjustments. To adjust the three beam positioning magnets, a dot pattern generator is helpful. The position of each magnet is set so as to produce a small equilateral triangle made up of three adjoining color dots. Each magnet also affects the positioning of the other two beams so that a number of touch-up adjustments may be necessary. The d.c. convergence voltage is set so that three color dots near the center of the screen are clearly visible. After they have been brought to an equilateral triangle, the convergence control can be reset to produce a white spot at the center.

The d.c. convergence and focus control should be set for best convergence and focus at the center, while the dynamic convergence and focus controls are adjusted for best over-all focus and convergence. Each setting of the convergence control may require a touch-up of its corresponding focus control and *vice versa*. When it is possible to obtain optimum convergence and focus all over the screen by merely setting the d.c. controls, the dynamic controls have been properly adjusted.

When all the adjustments have been satisfactorily made, examine the picture critically, with a signal, without a signal, and with each single gun operating alone. It may well happen that after other adjustments are made, the color purity is off and each of the purity adjustments must be reset. Centering, width, or height may also be off, requiring further adjustment.

Setting up a tri-color tube for correct color reproduction is not a simple, five minute job, but requires time, patience, and know-how. A complete, detailed article could be written about purity adjustments alone or about the operation of the dynamic convergence circuits. This article only furnishes

www.americanradiohistory.com

CREI prepares you quickly for success in

- BROADCASTING
- TELEVISION
- MANUFACTURING
- COMMUNICATIONS
- SERVICING
- AERONAUTICAL ELECTRONICS

The future is in your hands!

The signs are plain as to the future of the trained men in the electronics industry. It is a tremendous industry, and—at the *present time* there are more jobs than there are trained men to fill them. But—when there's a choice between a trained and untrained applicant, the trained man will get the job. Your biggest problem is to decide on—and begin the best possible training program.

CREI Home Study . . . The Quick Way to Get There.



Since 1927, CREI has given thousands of ambitious young men the technical knowledge that leads to more money and security. The time-tested CREI procedure can help *you*, too—if you really want to be helped. CREI lessons are prepared by experts in easy-to-understand form. There is a course of instruction geared to the field in which you want to specialize. You study at *your* convenience, at *your* rate of speed. Your CREI instructors guide you carefully through the material, and grade your written work personally (not by machine).


Industry Recognizes CREI Training.

CREI courses are prepared, and taught with an eye to the needs and demands of industry, so your CREI diploma can open many doors for you. Countless CREI graduates now enjoy important, good-paying positions with America's most important companies. Many famous organizations have arranged CREI group training for their radio-electronics-television personnel. To name a few: All America Cables and Radio, Inc.; Canadian Aviation Electronics, Ltd.; Canadian Broadcasting Co rporation; Columbia Broadcasting System; Canadian Marconi Company; Hoffman Radio Corporation; Machlett Laboratories; Glenn L. Martin Company; Magnavox Company; Pan American Airways, Atlantic Division; Radio Corporation of America, RCA Victor Division; Technical Appliance Corporation; Trans-Canada Air Lines; United Air Lines. Their choice for training of their own personnel is a good cue for *your* choice of a school.

Benefits Felt Right Away.



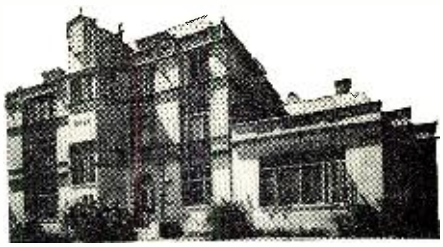Almost immediately, you feel the benefits of CREI training. Your employer, when informed of your step toward advancement (only at your request), is certain to take new interest in you and in your future. What you learn in CREI Home Study can start helping you do a better job immediately.



CREI also offers Resident Instruction

at the same high technical level—day or night, in Washington, D. C. New classes start once a month. If this instruction meets your requirements, check the coupon for Residence School catalog.

INFORMATION FOR VETERANS

If you were discharged after June 27, 1950—let the new G. I. Bill of Rights help you obtain resident instruction. Check the coupon for full information.

Get this fact-packed booklet today. It's free.

Called "Your Future in the New World of Electronics," this free illustrated booklet gives you the latest picture of the growth and future of the gigantic electronics world. It includes a complete outline of the courses CREI offers (except Television and FM Servicing) together with all the facts you need to judge and compare. Take 2 minutes to send for this booklet right now. We'll promptly send your copy. The rest—your future—is up to you.



MAIL COUPON TODAY

CAPITOL RADIO ENGINEERING INSTITUTE

Dept. 112-A, 3224 16th St., N.W., Washington 10, D. C.

Send booklet "Your Future in the New World of Electronics" and course outline.

CHECK FIELD OF GREATEST INTEREST
- ☐ TV, FM & Advanced AM Servicing
- ☐ Practical Radio Engineering
- ☐ Broadcast Radio Engineering (AM, FM, TV)
- ☐ Practical Television Engineering
- ☐ Aeronautical Radio Engineering

Name.....

Street.....

City.....Zone.....State.....

Check—☐ Residence School ☐ Veteran

CAPITOL RADIO ENGINEERING INSTITUTE

An Accredited Technical Institute • Founded in 1927

3224 16th Street, N.W. Washington 10, D. C.

www.americanradiohistory.com

HARVEY

for Civilian Defense
COMMUNICATION EQUIPMENT

26th ANNIVERSARY YEAR

GONSET
"COMMUNICATOR"




A complete two-way station for 2 meter band operation. Suitable for mobile or fixed location use. Receiver is a sensitive superheteradyne with built-in noise clipper circuit and 6BQ7 Cascode rf stage. Transmitter uses 2E26 in final 15 watts input. Employs 8 mc. crystals for stability, and has a range of over 100 miles. Operates on either 110 volts AC or 6 volts DC. Weight approx. 16 pounds.

Complete with Tubes (less crystal and microphone) $209.50

Deluxe Model. All features as above, plus: earphone jack, built-in adjustable squelch, and new ventilated cabinet $229.50

Deluxe Transmitter Kit
JOHNSON VIKING II

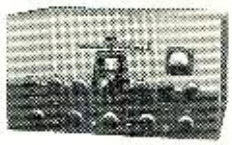

100 WATTS ON PHONE
130 WATTS ON CW

Every desirable feature has been included in this outstanding transmitter: BAND-SWITCHING to all amateur bands, from 160 through 10 meters . . . TVI suppression . . . 100% AM modulation . . . PARALLEL OUTPUT 6146 tubes . . . PUSH-PULL 807 MODULATORS. Supplied complete with pre-punched chassis, copper-plated steel cabinet, tubes, hardware, assembly instructions, and all necessary parts and components $279.50

Viking II complete with tubes, wired and air tested	334.50
Viking VFO Kit	42.75
VFO Kit—wired and tested (with tubes)	62.75
Viking Mobile Kit, up to 60 Watts input	99.50
Viking Low Pass Filter, 4 section, 75 DB Att., handles a KW	16.50
Viking TVI Kit, everything to TVI suppress the Viking I	24.75

The NEW NATIONAL NC-88 Receiver



Covers 540 kcs to 40 mcs, with illuminated calibrated band-spread scales for 80, 40, 20, and 10 meter bands. Has tuned RF stage, two IF stages, and two high fidelity audio stages, with phono input and tone control provided with built-in speaker, antenna trimmer, separate high frequency oscillator, gain control, noise limiter, AVC, headphone jack, and send-receiver switch.

Complete with tubes $119.95

Generous Trade-in Allowances Made for All Equipment

Visit the Harvey AUDIOtorium
See, hear, and compare sound equipment from the largest selection available anywhere.

NOTE: Prices Net, F.O.B., N.Y.C. Subject to change without notice.

hrc **Harvey**
RADIO COMPANY, INC.
103 W. 43rd St., N.Y. 36, N.Y. • JU 2-1500

the basic data which will permit the service technician to undertake a color installation. Obviously a great deal more information will be required.

At the present stage of color television receiver development, the initial adjustment of many of the color circuits will be time consuming and extremely subjective. The adjustment of the voltages to the set of first anodes, for example, which is necessary to effect a proper gray scale for the monochrome image, is time consuming because the settings must be made for various beam currents so that the black-and-white picture will not be color tinted. Also, the color hues that the service technician adjusts for may not be the ones the customer thinks are natural.

A great deal more experience in color adjustments, receiver alignment, and installation procedure is required before a hard and fast method of setting up a color receiver can be evolved. However, many simplifications in adjustments, automatic control circuits, and new service aids eventually make the color TV receiver much easier to install. —30—

CITIZENS BAND TRANSCEIVER AVAILABLE

THE TV, radio, and electronics division of Stewart-Warner Corporation, Chicago has been granted an FCC class B radio telephone-type approval on its new "Portafone" transceiver.

Operating in the Citizens band at a fixed frequency of 465 mc., the new transceiver may be operated as a portable station when used with a battery pack, or as a fixed central station by connecting it to a special power pack designed to plug into any 115-volt, 60-cycle a.c. outlet. It may also be used in a car by plugging a special adapter into the cigarette lighter socket of the car's instrument panel.

The "Portafone" requires an FCC station license, but not an operator's license. It is sold in pairs. Each instrument weighs 28 ounces. The case measures 10½" long with a 6½" antenna.

The elements of the two-tube superregenerative receiver are reconnected by the "press-to-talk" switch so that the unit operates as a two-tube transmitter. Transmission is set at 465 mc. Stability of the unit is such that there is a drift of less than ± .5% over the temperature range of 0 to 125 degrees F and from 0 to 100% humidity with the "B" battery voltage change from 130 to 90 volts and the filament voltage change from 7 to 5.2 volts. This includes 500 kc. of a frequency-modulated component which is inherent in the unit when it is modulated at maximum. Stability of the receiver is the same as that of the transmitter.


All components used in the unit are operated at 50 per-cent of their maximum ratings or less with most being operated at about 20-per-cent of maximum. All of the parts which normally require replacement are standard and are available through jobbers. Transmitter adjustments, however, must be made by an FCC licensed operator of the proper rating.


The unit normally delivers a power of 500 milliwatts. Audio output is about 15 milliwatts as measured into a 600-ohm earphone. Sensitivity of the receiver is about 12 microvolts (absolute) for a readable signal.

Under a condition of 10 per-cent transmit time and 90 per-cent receive time, the battery pack gives a life of about 10 hours with a recovery of an additional life of some 5 hours after the battery rests 24 hours. The unit includes an indicator light which shows whether the voltage of the pack is sufficient to provide "on frequency" transmission.

The new Model 73 will be distributed through major parts jobbers which have special industrial electronics departments. —30—


(Left) The central station power pack, shown with the Stewart-Warner "Portafone," permits operation of the unit from a fixed location. The power pack, plugged into a 115-volt, 60-cycle a.c. outlet, permits use of the unit without a battery pack. (Right) Internal view of the "Portafone." The use of printed circuits makes possible the required compactness and light weight. A glow lamp in the antenna base indicates the battery reserve. The battery pack can be worn strapped to the waist.

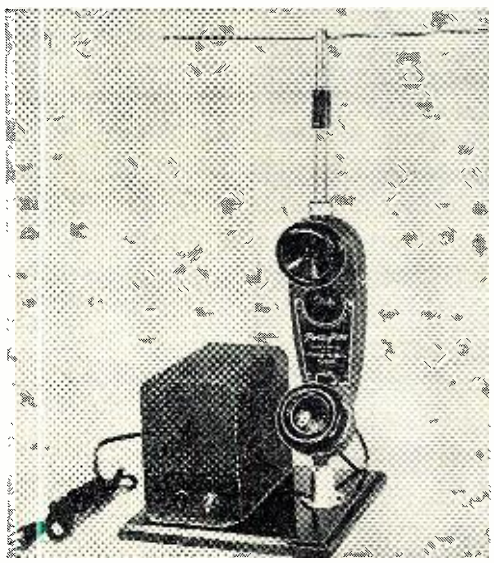

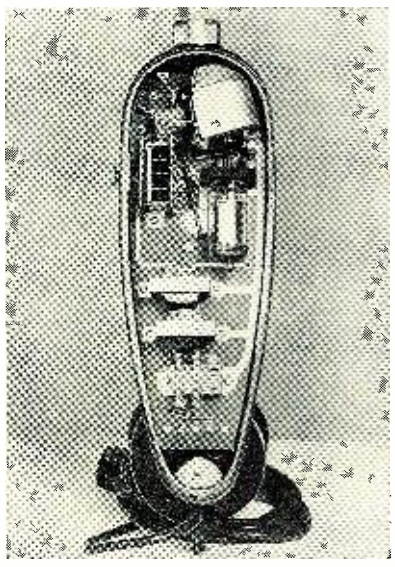

www.americanradiohistory.com

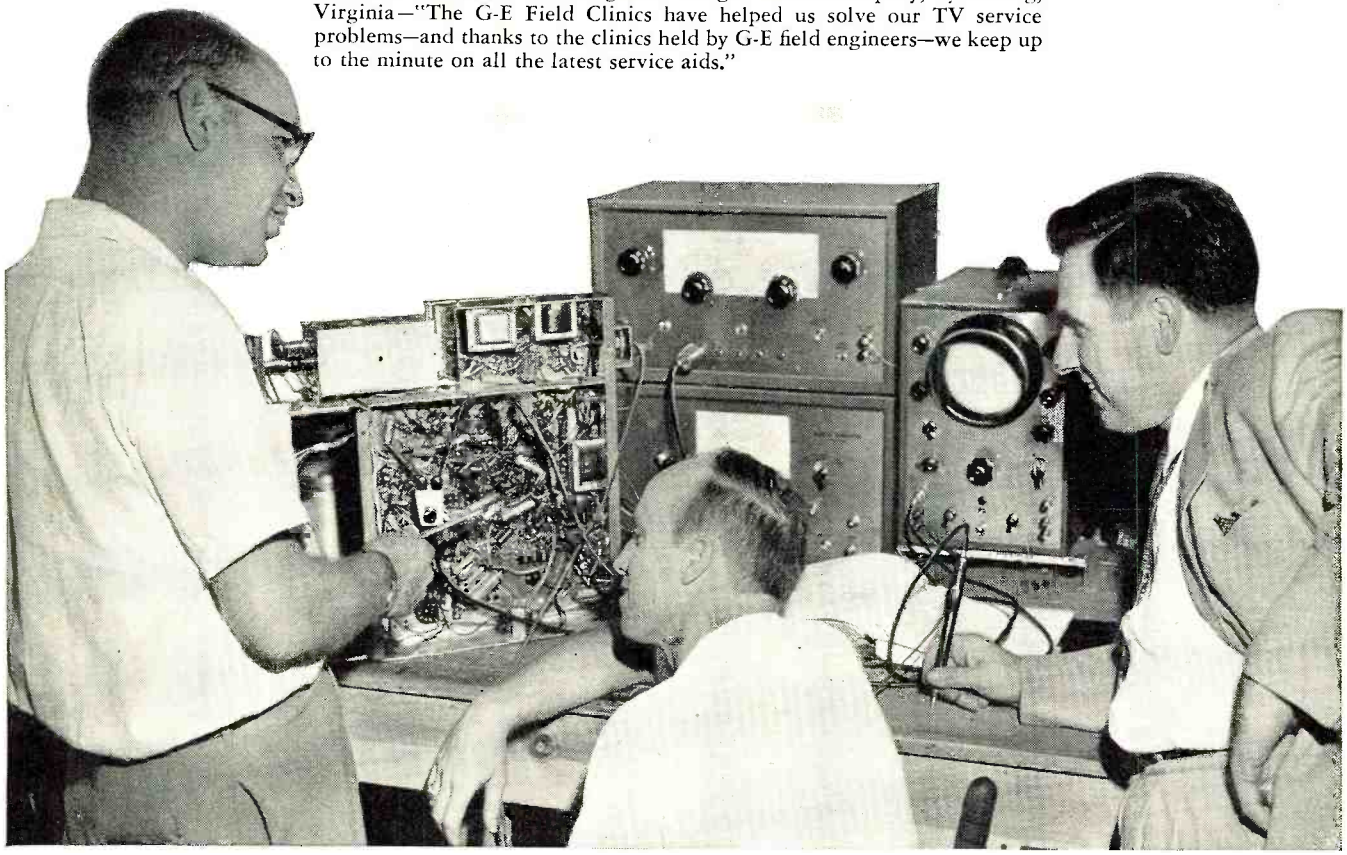● According to William Vaughn of Vaughn Motor Company, Lynchburg, Virginia—"The G-E Field Clinics have helped us solve our TV service problems—and thanks to the clinics held by G-E field engineers—we keep up to the minute on all the latest service aids."



Left to right – C. R. Lewis, Alex A. Driskill and William Vaughn discuss TV service.

G-E FIELD CLINICS


demonstrate up-to-the-minute service methods

General Electric Field Clinics are Open to All TV Servicemen—Without Charge

● Efficient TV service operation is becoming more and more important. Successful dealers coast to coast are enthusiastic about the value of the G-E Field Clinics. They show you new ways to increase the efficiency of your Service Department. They demonstrate the latest and easiest ways to diagnose and correct TV troubles—with special emphasis on UHF. They answer your questions on all phases of TV service.

Get in touch with the Service Manager at your G-E TV distributor's. Sign up for the next G-E Field Clinic in your area.

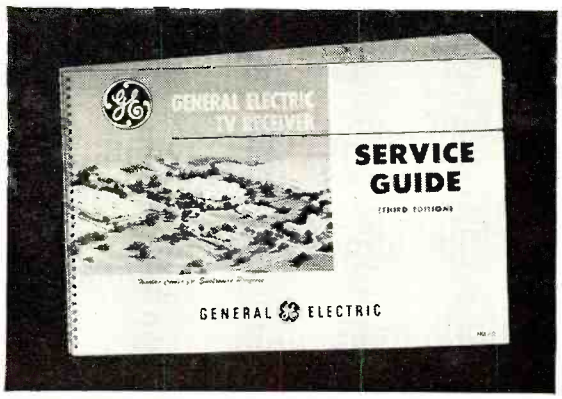General Electric Company, Radio & TV Department, Syracuse, N. Y.



● The latest edition of the G-E Service Guide is a vital reference manual. Order your copies today at $1.25 each through your General Electric TV Distributor.

You can put your confidence in—

GENERAL ELECTRIC

www.americanradiohistory.com


SPECIAL!
20 LBS. of ASSORTED RADIO PARTS
A terrific buy at only
$1.99




SPECIAL THIS MONTH ONLY!!
40 LBS. ASSORTED RADIO PARTS..... **$3.49**

TUBES BRAND NEW! JAN! BOXED! **TUBES**

1B22	.69c	114B	.29c	841	.29c
1B23	$3.75	215A	.09c	843	.17c
2B22	.49c	221A	.29c	864	.19c
2C26	.09c	316A	.29c	1626	.19c
2C26A	.09c	388A	.59c	7193	.19c
3B22	$1.19	471A	$1.19	9002	.69c
3D6	.39c	532A	$1.19	E1148	.49c
7C4	.39c	722A	.99c	RK34	.99c
12KSY	.39c	801A	.19c	VR92	.14c
15R	.39c	826	.39c	VT127	.15c
39/44	.29c				

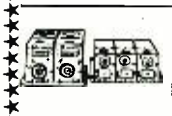

SCR-274N COMMAND and ARC-5 EQUIPMENT

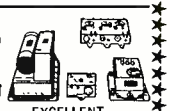

	USED	EXCELLENT USED	NEW
RECEIVERS			
BC-453—190 to 550 KC	$29.95		$49.95
BC-454—3 to 6 MC			24.95
BC-455—6 to 9 MC	5.95 (as is)	$13.95	19.95
1.5 to 3			34.95
TRANSMITTERS			
A-958—2.1 to 3 MC			29.95
BC-457—4 to 5.3 MC		14.95	
BC-458—5.3 to 7 MC	9.95	14.95	29.95
BC-459—7 to 9.1 MC			24.95
T-15 ARC 5—500 to 800 KC			29.95
ADDITIONAL EQUIPMENT			
BC-456 Modulator			7.29
BC-450 Control Box (3 Receiver)	1.49	1.95	
BC-451 Control Box (Transmitter)	1.29	1.79	
BC-442 Relay Unit (ANT)			5.69
Plugs: PL-147, 148, 151, 152, 153, 154, 156—EACH		1.25	
Flexible Shafting with gear to fit receivers			2.69
3 Receiver Rack	1.79	2.29	2.98
2 Transmitter Rack	1.69	2.39	3.97
Single Transmitter Rack			3.97
DM-33 Dynamotor for Command Set		2.95	3.95
Mounts for Above Racks		1.95	

BC-221 Frequency Meter
Real Value! QUANTITY IS LIMITED—so first come, first served. They are just like new, with original calibration charts. Range 125-20,000 KC with crystal check points in all ranges. Complete with crystal and tubes..... **$139.50**
MODULATED TYPE..... $169.50
MODULATED TYPE with AC Power Supply..... 189.50
These Frequency Meters factory treated, checked for frequency alignment and GUARANTEED.






T9/APQ-2 RADAR TRANSMITTER
80/115 V 400-260-26 VDC. Designed primarily for aircraft operation.
NEW! **$19.95**
AS-65/APQ-2 ANTENNA ASSY. FOR APQ-2. COMPLETE—BRAND NEW.....$6.95

HEADSETS



HS-23 high impedance. BRAND NEW with ear pads.....$4.65
HS-33 low impedance. BRAND NEW with ear pads, cord and PL54 plug..... 5.65
CD-307A Cords. 6 ft. NEW.....$1.49
H-16/U high impedance. Includes two receiving units..... 3.95
HS-16 high impedance—used..... .98

TELEGRAPH KEYS

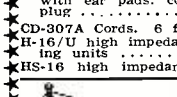

J37 .....$1.50
J38 ..... 1.50
J41 ..... .98
J45 ..... 3.95

Field Telephones
Army surplus, completely reconditioned and electrically tested, using 2 flashlight cells and a pair of interconnecting wires. GUARANTEED. New $28.95
Like new
$21.95





SPECIAL!
45 Henry 60 ma 625 ohm. LIMITED QUANTITY OF THESE CHOKES
$1.95

MINIMUM ORDER $2.00
Immediate Delivery—Send 25% deposit on C.O.D. orders. All shipments F.O.B., N.Y.C. (N.Y.C. residents add sales tax to your remittance.)

PLATT ELECTRONICS CORP.
Dept. A, 489 Broome St., N. Y. 13, N. Y.
PHONES: WO 4-0827 and WO 4-0828

International Short-Wave

(*Continued from page* 102)

Noted to North America 0000-0100 over JOB2, 7.18, and JOA3, 9.695. (Stein, Morgan, Calif.) JKI2, 9.655, is in the clear, after 0200 sign-off of *Radio Moscow*, with Japanese Home Service; JKL, 4.86, AFRS, Tokyo, is noted at weak level around 0700. (Morgan, Calif.) Tokyo noted on 9.535 at 0100-0200 with music and phone talk, *irregularly;* formerly was on 9.555; fair level. JOB, 7.18, and JOA3, 9.695, noted at good level at 0925 beamed to China. (Balbi, Calif.) JOB2, 7.180, heard to Europe 1400-1500; announces 9.695 as parallel. (Pearce, England)

Kuwait — Radio Kuwait officials say the station is scheduled on 5.000 in Arabic 1200-1500 with 1 kw.; will install a *new* station of 25 to 50 kw. soon, but didn't say if would be s.w. or not. (Scheiner, N. J.)

Liberia — ELBC, 6.024A, Monrovia, noted 1752 with popular music, weak level. (Cox, Dela.) Closedown is 1845.

Libya—Forces Broadcasting Service, Benghazi, sent QSL card for broadcasts on 4.782, 4.965; said has two *test* transmitters, of 500 and 700 watts, using; transmitter Type BC690's, antenna half-wave dipole; further reports welcomed. Heard on 4.785A to 1600 closedown, when said would open again 2330; signature tune had bugles, is *not* National Anthem. (Pearce, England)

Malaya — BFEBS, Singapore, noted on 11.82 at 0515 with news, music. (Sanderson, Australia). And in Calif. 0730; 9.69 is fair at that time. (Balbi) With news on 11.82 at 0415, when *announced* use of 15.435, 11.820, 7.120, 6.110. (Ballou, Calif.) Kuala Lumpur, 6.025, heard with organ recital at 0430; at times a station on 3.330A seems parallel. (Saylor, Va.)

Mexico—XEBR, 11.820, Hermosillo, has sports news in Spanish 1600. (Kahan, Calif.)

Mozambique — Lourenco Marques noted signing on in *English* 2300 on 3.48A and 4.916A; 3.48A fades out rapidly *after* 2315, and 4.916A *after* 2330; is heard sometimes on 11.764A *after* 0030. (Morgan, Balbi, Calif.) The 4.916A channel noted around 1450. CR7BV, near 4.780, heard 1242 in Portuguese, call after chimes 1300. (Pearce, England)

New Zealand—ZL19 is call of *Radio New Zealand's new* channel on 11.830, fair around 2300, with ZL4, 15.280, parallel. (Niblack, Ind.) Used from 1800. (Collett, N. Z.) Noted on 9.52, 9.62 around 0200-0545A. (Sawyer, Ont.)

Northern Rhodesia—Central African Broadcasting Station, 4.826, Lusaka, tuned 1245 with music and announcements in native African dialect; usually relays BBC news 1300. (Pearce, England)

Pakistan — Radio Pakistan, 17.710, noted with news 0330; with news at slow speed 1310-1330 on 6.235, 7.010; heard on 7.010 with news 1545. (Pearce, England) Closing on 7.010 at 1615. (Campbell, Pa.) News noted 0200 on 17.770. (Sanderson, Australia) Heard in native on 9.484 around 0900, with *English* news 1015-1030. (Saylor, Va.) Noted on 6.235 at 1510 with news commentary. (Bellington, N. Y.)

Panama—HOLA, 9.505, Colon, noted 1648 tune-in with *English;* started another *English* session 1700; good level; announced *Radio Atlantico.* (Bellington, N. Y.) HOF7, 9.685, *Ondas Popular.* noted at weak to fair level in Spanish 2010. (Cox, Dela.) And around 0800. *Radio Miramir,* 6.031, opens 0555. (Stark, Texas)

Peru—OAX4R, 15.150A, *Radio Nacional,* Lima, has news in *English* daily 1315-1330; and now announces this as in "Overseas Services." (Niblack, Ind.)

Philippines — The *new* VOA relay channel 11.700 is fair to 1500 sign-off. (Balbi, Morgan, Calif.) DYH4, 6.055, Silliman University, Dumaguete City, is scheduled 0500-0830, soon will *test* on 3.277. (Radio Australia) DZH7, 9.73, and DZH2, 9.64, are strong around 0500. (Ishikawa, Japan) DZH9, 11.855, Manila, heard announcing for FEBC in *English* 2015; DZH7, 9.730, noted in *English* 1945, Japanese 2000. (NNRC)

Portuguese India—Radio Goa, 9.610, noted 1100 with "Catholic Hour" in *English.* (Pearce, England)

Roumania — Bucharest has been heard on *new* 5.990 opening 2200 with *English* to North America; still on the air 2331. (Bellington, N. Y.) Heard in Sweden 1200-1730 on this channel. (Radio Sweden)

Saudi-Arabia — Djeddah noted on 7.095A at 2335 with news in Arabic, fair level in Dela. (Cox) On 11.95A in Japan from 2300-0205. (Japanese Short Wave Club)

South Africa—Springbok Radio, Johannesburg, is heard in Ireland on 3.356A around 1330 when amateur and CWQRM permit. (*Radio Amateur,* London) Cape Town, 4.892A, noted from 2345 sign-on; news in Afrikaans 2400. (Cox, Dela.)

South Korea—Radio Pusan, 2.510, is heard in Korean 0430; *Radio Seoul,* 9.555, is noted from 0400. (Hardwick, N. Z., *via Malmo-DX-aren,* Sweden) The Pusan 7.935A channel has *English* 0430-0500, announces *"Voice of Free Korea."* (Cushen, N. Z.)

Spain — Madrid, 9.363A, noted with *English* for Europe 1515-1545, news, music. (Zerosh, Pa.) Heard on 15.626 at 1110 tune-in when had program for Spanish seamen to 1818; re-opened 1126 to Canary Islands, closed 1150 with march; good level in N. C. (Ferguson) Malaga, 6.180, noted 1800. (Pearce, England) *Radio Falange de Valladolid,* 6.997A, noted 1445 with classical music; *Radio S.E.U.,* 7.140A, is fair to good around 1535; *Radio Murcia,* 7.104A, noted 1541 with overture, fair level. (Cox, Dela.) FET5, Leon, has been heard on 6.840A to 1800 sign-off. (Radio Sweden)

Surinam — Paramaribo, 5.758, noted closing in Dutch 2100. (Roberts, Conn.)

Sweden—Radio Sweden, 6.065, noted with *English* for Canada 1930-2000. (E. Gates, Conn.) Heard to Eastern North

www.americanradiohistory.com

America now on 9.62 at 0700 in *English*. (Grace, Conn., others)

Switzerland — HER7, 17.784, Berne, noted 1000 and onwards. (Zerosh, Pa.) Home Service noted over HER22, 3.985, at 1045, music. (Pearce, England) Is good level on 7.165, 7.210, 9.535 to North America from 2030. (Todosiev, Ont.; Rivers, Mass.)

Taiwan — BED6, 11.735, heard 2315 with news, music; BED24, 9.820V, noted 0645 with Western music, Chinese news; BED36, 7.344, heard 0700 with Western music, Chinese news; BED3, 15.235, noted 0045 with news, then music; BED26, 10.080V, heard 0500 at good strength in Chinese news, Western music. (Sanderson, Australia) BED7, 7.130A, Taipeh, is one of the most consistently heard Asiatics at present, peaks around 1015, dropping off until sign-off 1200; in native dialects. (Morgan, Calif.)

Thailand — HSK8, 6.240, Bangkok, noted 0600 with news in Thai and music in Home Service. (Sanderson, Australia) Strong during hour before sign-off which varies 1020-1045; closes with announcements in *English*, Thai, followed by National Anthem; 7.100A parallels but is much weaker. (Morgan, Calif.) HSK9, noted on *measured* 11.670, in native session 0800; should run to 0920A. (Ferguson, N. C.) Heard in England signing on 0500 with news. (Pearce) Final announcements in *English* are given before leaves the air 0700-0715V. (Catch)

Trieste—FBS sent letter verification, said still is *experimental,* using channel formerly occupied by FBS, Malta; schedule was given 1100-1800 although this is *not rigidly adhered to during testing period.* (Pearce, England) Frequency is presumed 15.125.

Trinidad — Radio Trinidad, 3.275, noted opening 0500. (Hardwick, N. Z., via *Malmo-DX-aren,* Sweden) Heard on 6.085 at 0715 tune-in. (Stark, Texas)

USI (Indonesia) — YDF6, 9.710, Djakarta, has been weaker lately in the 0930-1030 *English* transmission; has CWQRM. (Morgan, Calif.) Noted closing 1100. (Brown, Wyo.) YDB2, 4.910, 300 watts, and YDF6, 9.710, 50 kw., are used 0600 - 1100, *English* 0600 - 0700, 0930 - 1030. (Navarro, Philippines) YDF7, 11.770, noted in Indonesian language 1150. (Dahlgren, Sweden) YDF, 6.045, noted signing off 1030 with chimes. (Balbi, Calif.)

USSR—Home Service has powerful signal on 7.150 from around 0500 to 1000 sign-off; noted on 7.190 at slightly lower level. (Morgan, Balbi, Calif.) Moscow is good signal on 6.07 to North America 1900 with news, commentaries, classical music. (Calos, Calif.) Tiflis, 5.040, Georgian S.S.R., appears to be the Russian on this channel, logged 1405 with call of "Govori Tbilisi;" Baku, Azerbaidjan S.S.R., 4.958, is heard in Britain around 1330 with speech which sounds like a mixture of Russian and Arabic. (Fairs, *via* URDXC)

Vatican — HVJ is noted with news 1000 on 9.646; weaker in parallel on

B-T LABS Ultraverter

THE ALL CHANNEL UHF CONVERTER THAT OFFERS YOU Everything



PRICE
PERFORMANCE
SALES APPEAL
EXCLUSIVE FEATURES
and GREATER PROFIT MARGIN

Make Your Own Point By Point Comparison:

- LIST PRICE IS ONLY $39.95
- High Gain with Lowest Noise Factor
- Makes ANY TV Set a Modern 82 Channel Receiver
- Rapid Dual-Speed Tuning Controls
- Has No Power-Switch—'On-Off' Automatically Controlled by TV Set
- Rugged Construction, Attractive Styling, and Rubber Protective Feet
- Exclusively Designed 3-Section B-T Ultratuner
- Better Discounts for Greater Profits.



Supported By Hard Hitting Sales Promotion

- National Advertising in Consumer, Dealer, and Service Publications.
- Cooperative Newspaper Advertising
- FREE Attention-Getting SalesDisplays for Dealers
- Catalog Sheets, Service Data, other Sales Aids

It's *Ultra* POWERFUL . . . It's *Ultra* DEPENDABLE

For complete details, write to Dept OB-4

B-T LABS BLONDER-TONGUE LABORATORIES
WESTFIELD, N. J.


Manufacturers of TELEVISION AMPLIFIERS, UHF CONVERTERS, MIXERS, DISTRIBUTION UNITS and TV ACCESSORIES

www.americanradiohistory.com

Federated Purchaser

PRESENTS

Exclusive EICO

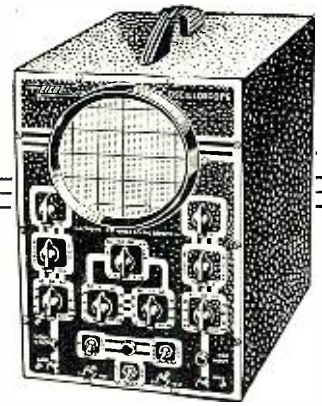

5 INCH PUSH-PULL EICO SCOPE 425K

KIT $44.95 Factory Wired $79.95

COMPARE THESE SPECIFICATIONS WITH SCOPES SELLING AT MANY TIMES THE EICO ECONOMY PRICE!

- Visually align TV, FM and AM sets
- Visually signal trace and trouble-shoot every stage of any electronic device
- Visually analyze complex waveforms —All without disturbing circuits
- Push-pull Vert. & Hor. amplifiers
- Full-screen V & H centering controls
- Intensity (Z-axis) mod.
- 6.3 volt AC, 60 cps test signal output
- Direct connections to deflection plates
- V & H Freq. Resp: 5 cps—500 kc; usable to 2.5 mc.
- V Sens: .05 to .1 volts rms/inch
- V & H input imp: 1 megohm
- Multivibrator Sweep Generator Range: 15 cps—75 kc
- Tubes: 2-5Y3, 2-6J5, 3-6SN7, 1-5" CRT.

EICO VTVM

221K VTVM KIT $25.95. WIRED $49.95.

- AC & DC volts: 0-5, 10, 100, 500, 1000 V (30 KV with HVP-1 probe).
- 5 ohm ranges from .2 ohm to 1000 megs.
- DC input Z 25 megs.
- 4½" meter movement in can't-burn-out circuit.
- 1% mult. resistors.



CABLE: FEDERPURCH

Federated Purchaser

INCORPORATED

• 66 DEY ST., NEW YORK 7, N. Y. •

DIgby 9-3050

- Newark, N. J., 114 Hudson St.
- Allentown, Pa., 1115 Hamilton St.
- Easton, Pa., 925 Northampton St.
- Los Angeles 15, Cal., 911 So. Grand Ave.

11 685; Polish session 1015 is *jammed.* (Morgan, Balbi, Calif.; Catch, England) Heard on 15.120 with news in French 0930-0945. (Kary, Va.) Heard in Sweden with *English* 1315-1330 on 9.646. (Olsson)

Yugoslavia—Radio Yugoslavia, 6.100, Belgrade, noted with news 1645. (Zerosh, Pa.) And 0115 on 9.505. (Cox, Dela.)

* * *

Press Time Flashes

The Universal Radio DX Club, 21446 Birch St., Hayward, Calif., recently observed its 20th anniversary; its prexy is Charles Norton.


A station heard on 5.990 with news 0730 just after opening is probably *Radio Pakistan.* (Stark, Texas) *"Radio Free Japan,"* clandestine Communist station believed located at Peking or Tientsin, China, now seems to be on a regular schedule on 1230 kc., 10.180, 11.896 at 1630-1700, 2230-2300, 0530-0600, 0630-0700, 0745-0815, 0900-1000. (Wada, Japan) The clandestine *Yugoslav Emigrant Station* is noted on 6.890A around 1625 to *after* 1700. (Hill, Mass.) Cushen, N. Z., reports HLKA, South Korea, on 3.895, 1 kw., signing on 0400.

A Spanish station, believed *Radio Mediterraneo,* Valencia, Spain, is sometimes audible through strong CWQRM on 7.000A from about 1615 *past* 1800. (Kary, Va.) *Radio Athens* more recently has been on 9.607 for the 1245 news session; AFN, 5.470, Germany, heard 1040 with popular music, AFN news 1100.

Radio Commerce, Box 1143, Port-au-Prince, Haiti, lists schedule of 0630-2300 (0600-1900 *Sun.)* on 4VA, 1080 kc., 1 kw., m.w.; 4VB, 6.091, 7.5 kw., and 4VC, 9.485, 7.5 kw.; at present uses *only French. Radiodiffusion Nationale Kemere Cambodia,* Phnom Penh, Cambodia, Indo-China, uses 6.090 with 1 kw. (over an American-made transmitter) and 1433 kc., 500 watts, 1800-1900, 2300-0100, 0500-0815. Complete schedule received from *"Voice of Free China,"* Taipeh, Taiwan, is to America 2300-0200, BED6, 11.736, BED3, 15.235, with news 2305-2320, 0035-0050; for Europe and Near East 1400-1600, BED4, 11.920, with news 1420-1430; for mainland China, Japan, Korea, South Sea Islands, Southeast Asia 0530-0800, and for mainland China, South Sea Islands, and Japan 0800-1200, BED7, 7.130, BED4, 11.736. (Scheiner, N. J.)

The 1954 *"World Radio Handbook,"* a "must" for the SWL, is now available for $1.50, postpaid, direct from Ben E. Wilbur, 47 Mounthaven Drive, Livingston, N. J. Contains many new features, up-to-date information on both radio and television stations throughout the world.

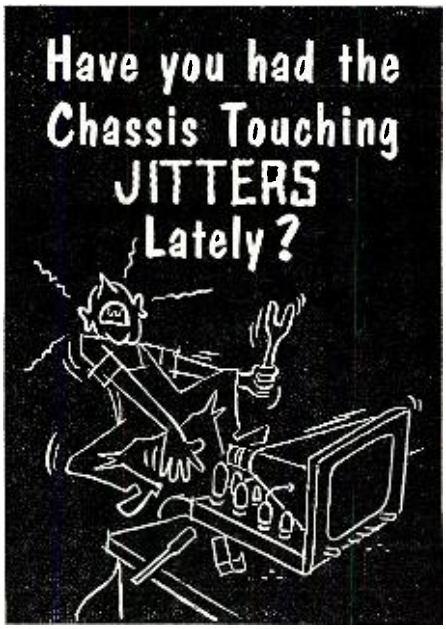YDR, Ambon, 4.865, Moluccas, Indonesia, now closes 0950; relays news in Indonesian from Djakarta 0930. (Cushen, N.Z.) *Radio Parkistan* schedules for the Home Service include APL2, Lahore, 1 kw., 6.138, 4.785, 3.915, 2125-2330; 7.284, 6.138, 0200-0400; 7.284, 4.785, 3.335, 0730-1300; APD2, Dacca, 7.5 kw., 7.150, 6.112, 4.807, 2000-2230;



Adjust-A-Volt

LR-5 VARIABLE TRANSFORMER

with *isolated primary winding* lets you service any TV or radio set made without a chance of a "bite" . no more chassis touching jitters.



$29.50

Delivery from stock of your favorite jobber.

This husky ½ KVA electro-statically shielded unit is "Must" test equipment for thousands of service men. Intermittent operating TV or radio sets are checked by dropping line voltage to 105 V or lower to detect a faulty oscillator. Also used to cook a set at 130-140 V to break down intermittent part. On any application where either isolation or a variable transformer is needed Adjust-A-Volt will do the job. Black wrinkle finish, jeweled pilot light and convenient fuse. Write for new 18-page catalog listing all types and sizes.

STANDARD ELECTRICAL PRODUCTS CO.

2238 E. THIRD ST. • DAYTON, OHIO

www.americanradiohistory.com

9.614, 7.150, 6.120, 0030-0230; 6.120, 4.807, 3.955, 0600-1130. (Scheiner, N.J.) *Bayerischer Rundfunk,* Munich, Germany, lists schedules on 6.160 as weekdays 2330-0420, 0515-1900; *Sun.* 0000-1900. (Catch, England) This one noted with setting-up exercises in German just prior to 0100, then with news in German. (Sawyer, Ont.) Zurich sunspot predictions include Feb. 10; March 9; April 8. (Ferguson, N.C.)

Acknowledgment

Thanks for all the fine reports. Keep them coming to Kenneth R. Boord, 948 Stewartstown Road, Morgantown, West Virginia, USA. Good DX-ing, fellows! . . . . . K. R. B.

VERSATILE ANTENNA COUPLER

By R. H. MITCHELL, W6TZB


A FEW years ago, Frank C. Jones described an antenna coupling unit ("The Engineering Forum," Amateur Radio Defense, February 1941) which permitted the use of either series or parallel tuning with a single-wire antenna. The writer has made a couple of changes in the tuner to permit the use of coaxial feedlines or random length single-wire antennas.

The circuit of the tuner is shown in Fig. 1A. The numbered points indicate banana jacks. Short jumpers, terminating in banana plugs, are used to make the various connections. Switches could be used in place of the jumpers but this would increase the complexity of the tuner. Figs. 1B, 1C, and 1D show the proper connections for the tuner when used with voltage-fed, current-fed, and coaxial-fed antennas, respectively.

L_3 may be omitted if the antenna to be used is resonant in the ham bands. However, its use will be necessary with random-length, voltage-fed antennas. With this coil, the tuner can be used to load a transmitter into anything from the bedsprings to a mile or so of barbed-wire fence, from 10 through 160 meters.

—30—

Fig. 1. (A) Circuit of antenna tuner. (B) Connections for tuner when used with voltage-fed antenna. (C) current-fed, and (D) coaxial-fed antennas. See text for details.

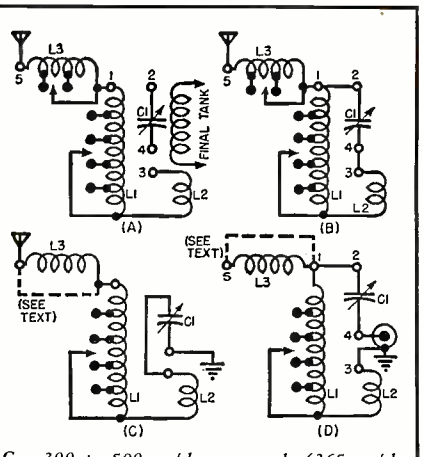

C_1—300 to 500 μμfd. var. cond. (365 μμfd. receiver-type var. is satisfactory for powers up to 150 watts)
L_1—20 t. #14 en. tapped at 2nd, 5th, 10th and 15th turns. Space dia. of wire, 2½" dia.
L_2—Regular pick-up coil from final tank
L_3—15 t. #14 en. tapped every 3rd turn. Space dia. of wire, 2½" dia.

Win a McIntosh Amplifier and Compensator and $500 cash*!





Mac needs your help! He needs a name for the famous McIntosh output transformer circuit. Just by naming it you can win one of six big prizes. Names may be either technical, for example, "Bicoupled", or non-technical like "Perfectone". Your McIntosh dealer can supply you with a folder that tells all about the McIntosh circuit. Get one, it will make it easy for you to win. Your entry blank is in the booklet.


Six Big Prizes!

1st prize, a McIntosh 50W2 50 watt Amplifier, a McIntosh C-108 Audio Compensator and $500 cash*; **2nd prize,** McIntosh 50W2 50 watt Amplifier and C-108 Audio Compensator; **3rd prize,** McIntosh A-116, 30 watt Amplifier and C-108 Audio Compensator; **4th prize,** McIntosh A-116, 30 watt Amplifier; **5th prize,** McIntosh C-108 Audio Compensator and D-101 Power Supply; **6th prize,** McIntosh C-104 Audio Compensator and D-101 Power Supply.

*If you are the first prize winner, McIntosh's Chief Engineer will install your equipment and assist you in the selection of other components.

The McIntosh Circuit

At right is a drawing of the patented McIntosh output transformer circuit which is not available on any other amplifier. See your Hi-Fi dealer and find out why McIntosh amplifiers guarantee substantially less than ½% distortion at all frequencies 20-20,000 cycles even at full power output. Hear the difference — the difference can be your suggested name. All you have to do then is name it, and you can have it . . . IF you're one of the lucky winners!

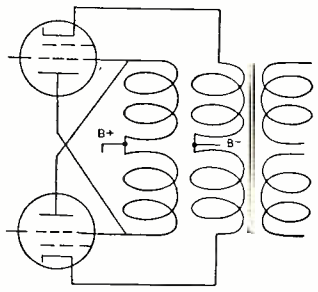

"Name the McIntosh Circuit" Contest Rules

1. Send in as many entries as you wish. There is nothing to buy, but each entry must be mailed separately, and should be accompanied by an explanation of 25 words or less as to why you think this name fits the circuit or its performance. Entries may be on a postcard, plain sheet of paper, or better still, the entry blank in the booklet available at your hi-fi dealer. If you win, there is a prize for your dealer, so be sure to include his name with your entry.

2. All entries are to be mailed to: McIntosh Laboratory, Inc., Post Office Box No. 5822, Cleveland, Ohio, by midnight March 31, 1954.

3. Entries will be judged on the basis of aptness and originality. The decision of the Contest Judges will be final. In the event of a tie, the award will go to the entry bearing the earliest postmark. All entries become the property of McIntosh Laboratory, Inc. and will not be returned.

4. The contest is open to all residents of the U.S. and Canada only, and is valid only where permitted by Federal, State and Provincial laws. Your entry must be postmarked not later than midnight, March 31, 1954.

5. Employees of McIntosh Laboratory, Inc., their representatives, advertising agency or families are not eligible.

6. Winners will be announced in HIGH FIDELITY Magazine as soon as possible after May 1, 1954. A complete list of winners will be sent to you about May 15, 1954, if a self-addressed, stamped envelope is enclosed with your entry.


McIntosh LABORATORY, INC.
BINGHAMTON, N. Y.

Makers of the World's Finest Amplifiers and Compensators

Manufactured under patent numbers 2,646,467; 2,545,788; 2,654,058; 2,477,074

www.americanradiohistory.com

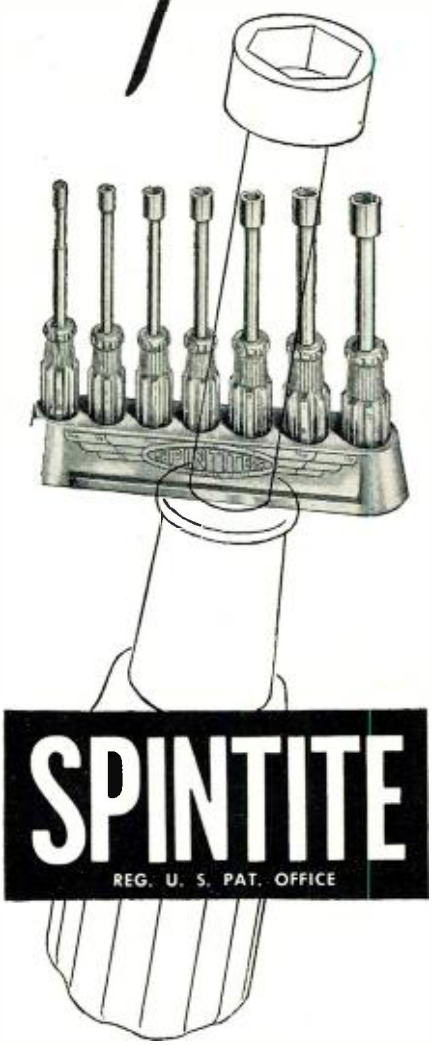THE *Original* WRENCH WITH THE SCREWDRIVER ACTION!



SPINTITE
REG. U. S. PAT. OFFICE

120 STYLES and SIZES
for

- ASSEMBLY WORK
- REPAIR WORK
- RADIO
- TELEVISION
- INDUSTRIAL
- AIRCRAFT

WALDEN WRENCHES WORCESTER

STEVENS WALDEN, Inc.
WORCESTER 4, MASS.

RADIO-TV Service Industry News

AS REPORTED BY THE TELEVISION TECHNICIANS LECTURE BUREAU

THE response from readers to the various discussions that have been carried out in this department during the past several months about the up-grading of service practices by stabilizing the methods of charging for service labor, has been truly phenomenal. It has been most interesting to observe the unanimity of opinion among the better service business operators about service labor pricing policies. This has been clearly reflected in the letters that have come from every section of the country.

Comments carried in the letters indicate that many service operators have been very much confused about how to charge for their labor. The idiosyncrasies of complex electronic circuits are such that some circuit failures take hours to locate and minutes to fix once they have been isolated. Many service operators badly underrate their own capabilities; they feel if they were more advanced in their technical knowledge they would be able to service the tough ones in less time. Yet these same technicians will usually locate and correct circuit failures that would stump the engineers who designed the circuits.

This lack of confidence in his own capabilities and know-how often results in a technician making a smaller charge for a service job than the job actually was worth. The existing charts of standard labor charges for television service and repair provide good yardsticks for measuring the adequacy of the service charges in any shop. However, many other factors must be taken into consideration in the determination of the net income a service business will have when using these basic labor charges charts.

Determining Service Income

To provide an intelligent analysis of the factors involved in labor costs in a service business, we will take a specific case that represents a typical situation—paralleled in service businesses in every section of the country. The situation in this service business is accurately described in the following excerpts from a letter from the owner:

"Our firm now employs two outside technicians on house calls. These men are much better qualified technicians than the average 'tube changer' but they are not fully qualified bench men. These men work on a strictly commission basis figured at 50% of all labor charges and 20% of all tubes and parts they install. However, the company is going in the red on this basis. We are currently doing about three thousand dollars a month gross business.

"Here are my questions: (1) What are some of the averages, percentagewise, technicians of this caliber are now getting? (2) We work a six-day week and on that basis what would these men be getting if they were on salary? They average about twenty-two calls per week for each man."

While there is no such thing as a national wage average for various classes of field service technicians, the recently adopted union scale for journeymen technicians may serve as a convenient guide. This union scale provides for the payment of $2.35 per hour for journeymen technicians—technicians fully qualified to handle electronic service in the home. On the basis of this new union scale, technicians working 8 hours per day, 6 days per week will be paid $112.80 per week. In addition to these weekly wages they would receive a mileage allowance for operating and using their own cars or would be furnished company-owned service cars or trucks.

It is a generally accepted fact among successful service operators that labor costs must not exceed 40% of the service labor income if the business is to show a profit from its service activities. To provide the income needed to warrant the payment of $112.80 per week for their work, each of the technicians in the company in question must manage to make enough completed home service calls to bring in $282.00 per week in labor charges for their work. On the basis of a $5.00 minimum charge per call it would be necessary for each of these technicians to average 9.6 calls per day.

It is unrealistic to even assume that field service technicians can average nine and one-half completed calls per day. The most efficient service companies in the business with expertly handled field service control systems

www.americanradiohistory.com

BARGAINS FROM "WHOLESALE RADIO"

TV-RADIO-PHONO PARTS

Pix tube brightener for parallel circuits. Part No. A-4 ..... $ 1.49
SPECIAL! Brush Model BA-116 crystal microphone 5.95
4" Sq. Alnico V PM Speaker 1.19
5" Sq. Alnico V PM Speaker 1.29
12" Round Alnico V PM Speaker 4.95
12" Round 350 Ohm Dynamic Speaker 3.95
110 V AC Motor 3⅛"x2"x1¾" 2800 rpm at full load 1.69
TV Cheater Cord. Stand. type. 6 ft. U/L approved ..... .29
TV Cheater Cord, Philco, Zenith type. 6 ft. U/L approved ..... .39
HV anode connector with 18" lead for TV Pix tube 20-20 mfd.—150 V. Gudeman tub. elect. cond. ..... .29
16 mfd.—450 volt, Gudeman tubular electrolytic, condenser ..... .29
PHONE PLUG, standard type ..... .29
Carbonfilm 2 meg. 2 watt, +/−1% tolerance resistor for TV ..... .49
100 assorted ½-1-2 watt carbon resistors 1.95
50 assorted 5 mfd. to .001 mfd., mica condensers 1.95
100 assorted (18 values) ½ watt resistors in partitioned plastic box 4.95
Phono pickup arm with crystal cartridge (78 rpm) 2.49
Willard type N-T-6 midget 6 volt storage battery (less acid) 2.49
Volume controls, with switch (2" shaft). Choice ¼, ½, or 1 meg. Each ..... .49
100 ma. selenium rectifier 1 13/64" sq. plates ..... .85
250 ma. selenium rectifier 1 17/32" sq. plates 1.35
350 ma. selenium rectifier 1 ¾" sq. plates 1.75
400 ma. selenium rectifier, 2" sq. plates 1.95
Audio amplifier—5 watt, 3 tube AC amp. Model 305MP 14.95
Army surplus headphones Type HS-16A. 125 ohm DC resistance 1.95
Signal Corps Hand Key Type J-38 ..... 1.49
Mechanical reproducer head (plastic) ..... .90
2 volt storage battery (surplus) Willard 20-2. (Less acid) 2.95
2 volt vibrator, round can, 7 prong. Surplus Type VB-8 ..... 1.95
18" extension for auto antenna lead-ins. Type LLA ..... .49
Crystal phono cartridge (78 rpm) 3 volt output 1.95
Vertical Output Transformer. Turns ratio 10:1, mtg. centers 2 13/16". Part =43T011. Replaces Stancor A-8112 and Merit A-3036 ..... 1.79
Vert. Block Osc. Transf. (shielded). Turns ratio 1:4.2, mtg. centers 1 15/16". Part =16TV11. Replaces Stancor A-8121 and RCA 208T2 ..... 1.49
4 ft. Ground Rods ..... .75
DPDT Knife Switch ..... .45
Clothespin type TV Antenna Connector ..... .30
Rytel "AIM" Automatic Impedance Match 1.77
Swivel Mt. Base (for 1¼" OD mast) Lots of 10 or more 35¢ ea. ..... Singly .39

FREE! Write For Big New FY! Bulletin #127

TV ANTENNA ACCESSORIES

Strap type 3½" Stand-off Ins. for 300 ohm twin; takes masts up to 2½" OD—$7.50 per 100. Singly ..... $ .09
Snap-on type 3½" Stand-off Ins. for 300 ohm twin; clips on to 1¼" mast—$5.50 per 100. Singly ..... .06
Guy Rings for 1¼" OD masts—$6.00 per 100.
5 ft., 1¼" OD Mast (one-end crimped) 1.19

WALL MOUNTS

6" PAM-1 for masts 1" to 1½" Dia. 1.15
12" PAM-4 for masts 1" to 1¾" Dia. 1.89

ROOF MOUNTS

BMA-136 for sloping or flat roofs and side walls; takes masts ¾" to 1½" Dia. 1.79
PRA-148 for peaked or flat roofs and side walls; takes masts ¾" to 1½" Dia. 2.69

TWO SET COUPLERS (for 300 ohm line)
Operate 2 TV Sets Off One Antenna

Snyder AC-800 ..... $1.50
RMS AC-2 ..... 2.40
Penn TC-374 ..... 2.95
JFD TT2-300 ..... 3.57
Telematic AM-200 ..... 4.77

FOUR SET COUPLERS

JFD TC4L-300 Couples 4—300 ohm sets to one 300 ohm antenna 7.77
JFD TC4L-72 Couples 4—72 ohm sets to one 300 ohm antenna 7.77

PENN ANTENNA SWITCH
To Couple More Than One Antenna To A Set


TS-551 2—Antenna Switch $1.55
TS-587 3—Antenna Switch 2.10

LEAD-IN WIRE & CABLE
Antenna Rotator Wire

4 Cond. flat Rotor Wire, 3c per ft., $2.70 per 100 ft., $25.00 per 1000 ft.
8 Cond. round Rotor Wire, 6¢ per ft., $5.50 per 100 ft.
Tubular 300 Ohm Twin-Lead
Amphenol =14-271 ..... 5c per ft., $4.77 per 100 ft.
Federal =TV-1185 ..... 5c per ft., $4.77 per 100 ft.
AWG 20 strand copper. 55 mil. web poly $1.95—100 ft., $14.50—1000 ft.
STEEL MASTS, 10 ft. 1¼" di. 99c
95c each in lots of six
UNIVERSAL STAND-OFF INSULATORS, each 3c
3½" wood screw-in type, for tubular and flat 300 ohm twin lead or RG59U coax. ..... $2.50 per 100
GUY WIRE, 6 strand =20, 50 ft. coil 39c
1200 ft., consisting of 24 interconnected 50 ft. coils $6.00
CHIMNEY MOUNTS, in lots of six, per set $1.49
Complete with straps, hardware, instructions. Holds masts ¾" to 1½" ..... $1.59 per set
RMS LIGHTNING ARRESTOR, Model LA-3 ..... 59¢
U/L approved ..... 10 for $5.50
NEW UHF-VHF ARRESTORS, Model LA-UH3 ..... 79¢
U/L approved. Universal for all tubular and twin lead and 375 and 450 ohm open line. ..... 10 for $7.50

SNYDER'S SENSATIONAL NEW CONICAL TV AERIAL

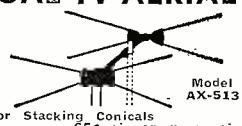8 hi-tensil ⅜" aluminum elements. Included Universal U clamp. Easy multi-stacking. $2.49 each. $2.39 in lots of 6




Model AX-513

Tie Rods For Stacking Conicals 75¢ a pair ..... 65¢ six or more pair


Equal to $50 Aerial Systems
All Directional TV AERIAL
360° DIRECTRONIC SYSTEM

Exclusive Snyder Engineering and designs cut cost to $18.95 FOR FRINGE AREA

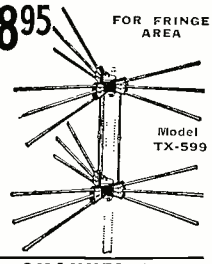COMPLETE with three 3½ ft. masts. 75 ft. 3 cond. cable. Beam selector sw., guy rings and mtg. base. Electronically beams complete 360° rotation to give clear pic on all channels. You choose direction with directronic selector sw. mounted on or near TV set. Complete double stacked array with 18 hi-tensil double alloy aluminum elements. AX-599 same as TX-599 less masts, guy rings & mtg. base $16.95



Model TX-599

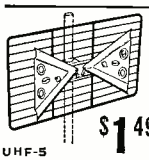

UHF-5 $1.49

ALL CHANNEL UHF BOW TIE & REFLECTOR

Channels 14-83


All pre-assembled. Just unfold, tighten and erect. Hi-tensil aluminum bow. All-welded steel screen, all-weather zinc-plated. U clamp included. Model UHF-5.

UHF-6 BOW TIE with Corner Reflector ... $3.49

SNYDER BROAD BAND YAGIS

- Higher Gain Than Conventional Yagis
- For Fringe and Ultra Fringe


High signal level for sharp, bright pictures. Hi-tensil ⅜" aluminum elements: 7 on low band; 9 on high band. Complete with universal U clamps.

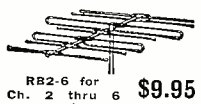

RB2-6 for Ch. 2 thru 6 $9.95
RB7-13 for Ch. 7 thru 13 $4.95

WHOLESALE RADIO PARTS CO., Inc.
311 W. BALTIMORE ST., BALTIMORE 1, MD.

Just Out

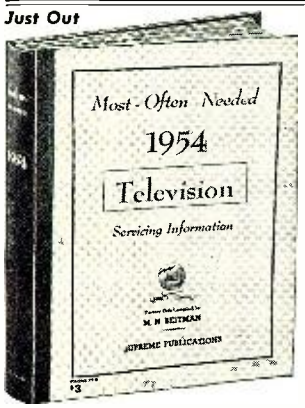

New SUPREME 1954 TV *Manual*

FULL YEAR'S TV MATERIAL IN A GIANT VOLUME — $3

This newest giant volume of the *Supreme* **TV** manuals covers **1954** factory data on all popular television sets of all makes. There are explanations of new circuits, 192 pages of alignment procedure, test patterns, response curves, pages of waveforms, voltage charts, service hints, production changes, and dozens of double-spread circuit diagrams. Manual-style binding (opens flat). Special price, only..... **$3**

COVERS ALL POPULAR SETS

This new *Supreme* **1954 TV** manual has all the required service material on every popular television set of every important manufacturer. Here is helpful, practical, factory-prepared data that will really make TV servicing and adjustment easy for you. More pages, more diagrams, more service data per dollar of cost. This new giant TV manual and previous volumes for other years have complete circuits, alignment facts, test patterns, response curves, service hints, recommended changes, voltage charts, waveforms, and many double-page diagram blueprints. Here is your TV service material to help you do more expert work quicker; and priced at only $3 and $2 per manual covering a whole year of material. See coupon below for complete list of all eight TV volumes, from 1947 to 1954, and the 1953 UHF Converters manual. Order for a 10-day trial.

AMAZING BARGAIN OFFER

The new **1954 TV** manual is the most remarkable value offered by **Supreme Publications** in their 20 years of business. This mammoth television servicing manual at only $3, or the TV manuals for previous years for only $3 and $2 each, are amazing bargains and defy competition. There is nothing else like them. Each manual is a virtual treatise on practical television repairs. By normal standards, each such large manual packed as it is with practical facts, hundreds of illustrations, diagrams, charts, photographs, and expensive extra-large blueprints, should sell for $10—but as SUPREME special values they are priced at $3 and $2 each. Only a publisher who sold over one million TV and radio manuals can offer such bargains based on tremendous volume-sales. Be ready to repair any TV set by having in your shop all eight **Television Manuals** listed in coupon. Or try the new **1954 TV** manual to see what an amazing bargain you get for only $3. Send trial coupon or ask your jobber.



The repair of any television set is really simple with **Supreme TV** service manuals. Every set is covered in a practical manner that will simplify trouble-shooting and repair. This is the help you need to find toughest faults in a jiffy. Each $3 volume covers a whole year of material. Be wise, buy **Supreme Manuals** only once each *year* instead of spending dollars every *week* for *not* needed data.

Newest



RADIO DIAGRAMS

Here is your complete source of all needed RADIO diagrams and service data. Covers everything from most recent radios to pre-war old-timers; home radios, auto sets, combinations, changers, and portables. Sensational values. Still sold at pre-Korean prices. Only $2 for most volumes. Every Radio manual contains large schematics, all needed alignment facts, parts lists, voltage values, trimmers, dial stringing, and helpful service hints. All volumes are large in size, 8½x11 inches, about 192 pages. See coupon at right for a complete list of these low-priced manuals.

Supreme Publications
Available from Leading Parts Jobbers

NO-RISK TRIAL ORDER COUPON

SUPREME PUBLICATIONS, 1760 Balsam Rd., Highland Park, ILL.

Radio Diagram Manuals

☐ *New* 1953 Manual, $2.50
☐ 1952 Radio
☐ 1951 Diagrams
☐ 1950 Manual
☐ 1949 Radio
} EACH $2.50

☐ 1948
☐ 1947
☐ 1946
☐ 1942
☐ 1941
☐ 1940
☐ 1939
} RADIO MANUALS PRICED AT ONLY $2 EACH

☐ 1926-1938 Manual, $2.50
☐ Master INDEX only 25¢

Send **TV** manuals checked ☒ below and **Radio** manuals at left. Satisfaction guaranteed or your money back.

☐ *New* **1954 Television Servicing** Manual, only . . . **$3.**
☐ **1953 TV** Manual, **$3.** ☐ **1953 UHF Units, $1.50**
☐ **1952 Television** Manual, **$3.** ☐ **1951 TV, $3.**
☐ **1950 Television** Manual, **$3.** ☐ **1949 TV, $3.**
☐ **1948 TV, $3.** ☐ **1947 TV & FM,** only **$2.**

☐ I am enclosing $..... Send postpaid.
☐ Send C.O.D. I am enclosing $.....deposit.

Name: .....

Address: .....

www.americanradiohistory.com

SPECIAL OF THE MONTH

OIL CONDENSERS, BRAND NEW

4 MFD—600 VDC $0.65
10 MFD—600 VDC 1.05
6 MFD—1500 VDC 2.75

WESTON METERS

Model 301, RECTIFIER TYPE

0-150 Volts AC, 1000 ohms per volt AC, Round bakelite case ..... $9.95 Ea.
NEW! BOXED ..... 10 for $89.95

OTHER WESTON MODEL 301—

0-200 Microamps DC $9.95
0-10 Volts DC (1000 ohms/v) 7.95
0-1Ma (KV Scale) 7.95
0-50 Ma DC 7.95
0-1.5 Mills DC 7.95

MODEL 731

0-200 Microamps (Spec. Scale) 9.95
0-1 Ma (0-100 Scale) 8.95

MODEL 506

0-200 Microamps 7.95
0-1 KV with Mult. 7.95

WESTERN ELECTRIC METERS

3½ inch round

100-0-100 Microamps DC 8.95
0-1.5 Ma DC 5.95

WESTINGHOUSE METERS—Model NX35

0-500 Microamps (0-100 Scale) 6.95

GENERAL ELECTRIC

0-150 Volt AC—Model AO 22 ..... 7.95
0-3 Amp RF w/thermo—Model DO44 ..... 7.95
0-5 Amp RF w/thermo—Model DO44 ..... 7.95
Running Time, 99,999 Hours, 115 V., 60 cy. 10.95

G. E. RELAY CONTROL

(Ideal for Model Controls, Etc.)

Contains a sigma midget 8,000 ohm, relay (trips at less than 2 MA), high impedance choke, bi-metal strip, neon pilot and many useful parts. The sensitive relay alone is worth much more than the total low price of.... $1.25 Each 10 for $9.90

Panel Meters

NEW GOV'T SURPLUS
STANDARD BRANDS

2" METERS

DB meter—10 to +20 ..... $3.49
0-500 ma DC 3.49

3" METERS

0-200 Microamps .. $6.95
0-400 Microamps .. 5.95
0-500 Microamps .. 5.95
0-200 Milliamp ... 4.50
0-1000 Milliamp .. 4.50
0-1.5 Volts AC.... 4.95
0-3 Volts AC..... 4.95

4" METERS

0-200 Microamps... $8.95

OIL CONDENSERS

2 MFD—1000 VDC .95
2 MFD—2000 VDC 2.50
4 MFD—2000 VDC 5.50
2 MFD—2500 VDC 3.95
3 MFD—4000 VDC 5.95
1 MFD—5000 VDC 3.95
2 MFD—5000 VDC 5.95
50 MFD—330 VAC 6.95
.1 mfd 7500VDC .. 1.75
1 MFD 20 KVDC.49.95
15 MFD 5 KVDC.49.95
5 mfd 660 VAC.... 2.95

NON-INDUCTIVE RESISTORS
Ohmite, 250 Ohm, 100 Watt. 59¢
Special, 5 for $2.50

ACME PLATE TRANSFORMER

Pri. 220V, 50/60 Cy. 3 Phase, Delta Connected. Secondary 3 phase, Y connected, 2622 Volts @ 7.5 KVA ..... Ea. $99.50

RAYTHEON PLATE TRANSFORMER

Pri. 220V single phase, tapped, 60 cycle. Secondary. 6000 Volts to 8000 Volts @ 1 Amp in 400 Volt steps ..... Ea. $99.50

SOLA CONSTANT VOLT TRANSFORMERS

Input 95-125 V 60 Cy Output Regulated 115V

250 VA $33.65
500 VA 48.65
1 KVA 79.95

CARTER SUPER DYNAMOTOR

12V Input, 400V Output @ 200 MA $24.95
CONTINENTAL DYNAMOTOR
11V Input, 475V @ 210 MA Output $19.95

WIRE WOUND RESISTOR KITS

25 assorted 10 Watt $1.95
25 assorted 20 Watt 2.50
50 assorted 5, 10, 20, and 50 Watt..... 4.95

WIRE WOUND RESISTORS

Stock too long to list. We can supply most sizes, so order what you need.

10 Watts. From 1 Ohm to 70K Ohms.. Ea. $ .15
20 Watts. From 4 Ohms to 50K Ohms.. Ea. .20
25 Watts. From 1 Ohm to 100K Ohms.. Ea. .30
50 Watts. From 5 Ohms to 100K Ohms.. Ea. .40
100 Watts. From 50 Ohms to 100K Ohms.. Ea. .50

ADJUSTABLE SLIDER, WIRE WOUND

10 Watts from 1 Ohm to 10K ..... $ .25
25 Watts from 20 Ohms to 2.5K ..... .35

EIMAC VACUUM CONDENSERS

6 MMF 32 KVDC (VC 6-32) ..... $ 9.95
12 MMF 32 KVDC (VC 12-32) 10.95
50 MMF 32 KVDC (VC 50-32) 12.95
100 MMF 5 KVDC G.E. 4.95

Min. Order $3.00—25% with Order

PEAK ELECTRONICS CO.

66 West Broadway, New York 7, N. Y.
Phone WOrth 2-5439

are able to average only seven calls per day per man. For a six day week, an average of 7 completed service calls per day would total forty-two for the week. To develop a service labor income of $282.00 from 42 calls it would be necessary to raise the charges for home service calls to $6.70 per call.

It is quite obvious from these figures that the company whose letter was quoted at the beginning of this discussion cannot even hope to break even on 50% of the revenue from only 22 completed calls per man in a six-day week. If these men were to receive the union scale of wages and the company got even the marginal "break" of 50% of the income from their labor, it would be necessary to charge $12.82 per call.

It is also quite obvious from this analysis that it would be impossible and inadvisable to set labor charges that would be applicable in service businesses of all sizes and operating at varying degrees of management and technical efficiency.

A series of tables is now being prepared that will show the various relationships between service charges and costs of doing business for organizations of varying sizes and with different levels of technical and management efficiency.

Delving into the rising costs of doing business and the continuing high mortality rate among small service businesses invariably leads to one undeniable conclusion: Every man engaged in any phase of the electronic service business must raise his sights about the value of competent technical skill and the public must be educated to pay adequate labor charges for service on home electronic instruments.

Service business operators who are seriously interested in building stable, reliable, long-range businesses in electronic servicing realize that the activity is now *basically a business.* When service is considered in the light of being a business, the owner or manager realizes that it must earn an income commensurate with the investment involved and the managerial know-how to run it. He knows that to gain recognition as a businessman in his community he must act and live like a businessman and operate his service shop as a business.

Lots of service operators have been afraid to raise their charges for service because they think their customers would not stand for it. They have feared, too, that if they raised their rates and their competitors did not, the latter would gobble up all of the service business in the community. These facts have been revealed in dozens of letters received by the editors of this department.

However, sheer economic necessity has made it necessary for small service shop operators to either raise their labor charges or load their service jobs with a lot of unnecessary tubes and parts. Many men have a natural revulsion against sticking a customer for tubes and parts not actually needed in repairing the set. To them this

RCA MI-2475 SOUND POWERED PHONES

NEW EXPORT PACKED
Shipping weight 5 lbs.



complete with 22' rubber covered cable press to talk switch are light weight, the mic is on a swivel boom that can be moved to any position in front of face. Cost $62 ea.

Price $13.95 Ea.

AC-METER 0-150VAC Weston or West. 2" R. $3.25

MOTOR 4 pole shaded pole induction 1700 RPM G.I. 1/70 HP running torque 12 oz. inches list $12.00 F/tape wire or disc recording $3.50
HEADSET TELEX monoset Mod. 2570 reg. 14.00 4.95
MICROPHONE SHURE 707A & S24B desk stand. 4.95
RECTIFIERS Fed. Sel. 403D27S7 150 Mil 130V .75
CIRCUIT BREAKERS Heinemann Cat. 0711 5 amp 115VAC curve D 1.00
833A tubes RCA fully guaranteed ..... each 16.00
SCOPE TUBES 5CP1 $4.95, 5BP4 $4.00, 5FP7 $1.00, 3AP1 $3.95, RCA 902P1 ..... 3.95
TV PICTURE TUBES 14CP4 $16.00. 16RP4 16KP4 16TP4 Raytheon Syl. & Sheldon brand new Guar. 18.95
WIRE HOOKUP #18 solid grey W.E. 1200 ft. roll 3.50
TA-12B trans. osc. section 4 channel new spec. 4.95
L&S Navy Waterproof speakers brand new each. 9.95
RM-29A REMOTE TEL. new W/canvas case & ringer 6.95
TEST SET I-236 for AC DC and Ohms with prods 3.95
MN-26C DF RECEIVER 150 to 1500 KC with 12 tubes dyn. and tuning motor in like new condition spec. 23.50
CURRENT RELAY West. .2 to 1 amp DC type M with glass cover Reg. $28.00 brand new a spec. 4.95
Famous Brand 2X2MFD 600VDC oil filled round ea. .75
Famous Brand D4430 2MFD 750VDC oil filled ea. .85
CD PC1599 2MFD 660 VAC 1250 VDC oil filled 1.25
CD TJ6010 1 MFD 600 VDC oil filled ..... .75
CD TYPE 86 MICA .01 3500 VDC 1.75
Famous Brand A 1 MFD 5000 VDC special 2.95
XTALS 500 KC standards CR-2B/U special 1.00

Include postage with order. Min. order $3.00

McCONNELL'S

New Address: BARTO, PA.
Phone: BALLY 5-3621

NOW Start fixing TV and Radio sets right away!



Even if you never fixed a lamp or door bell before . . .

It's easy with these plain, simple directions written for the man with no technical training. You deal only with the things that go wrong in sets—the parts—start doing actual repair work even before you finish the book. Just think—**No Math! No Theory! No Lab work!**

Just Published!

Television and Radio Repairing

by John Markus • *556 pp., 225 illus., $7.95*

For every television and radio part, no matter what make the set is, Markus shows you how to recognize symptoms of trouble . . . how to test to make sure . . . how to order the new part . . . and how to install it. Here's your chance to share the big money going to servicemen today—without investing a good deal of cash—and by starting right in your own home or working for a service outfit. **First repair job pays for the book.**

Shows you how to:
—Test tubes without a tester
—Eliminate noise in receiver . . . improve dim TV picture
—Repair, replace, adjust all parts
—Solder connections
—Install antennas
—Run your own service shop profitably
—and many others.

SEE THIS BOOK 10 DAYS FREE

McGraw-Hill Book Co., Inc., 327 W. 41 St., NYC 36
Send me Markus' Television and Radio Repairing for 10 days' examination on approval. In 10 days I will remit $7.95, plus few cents for delivery, or return book postpaid. (We pay for delivery, if you remit with this coupon; same return privilege.)
PRINT

Name .....
Address .....
City ..... Zone... State.....
Company .....
Position RTN-2

This offer applies in U.S. only.

www.americanradiohistory.com

practice is a form of petty thievery—akin to stealing something of value from a customer's home to make up for inadequate service charges which it is *assumed* the customer would not pay.

So what has been happening?

During a period of less than three weeks twenty-seven service operators wrote your editors to say they had raised their charges to conform with those listed on the standard TV labor charges schedules and they were not getting any more complaints about charges than they had when their charges were on a low, inadequate scale. Fifteen of these companies said they were observing *an increase* in their volume of service business in a few weeks after adopting the higher scale! Most of them attributed this increase to the fact that they were able to give better service after they started to get adequate pay for it and the whole *tone* of their businesses was better.

A number of organizations are using the Standard TV Labor Charges Charts available through this column rather extensively in their areas. The Television Service Association of Michigan reproduced it in their monthly house organ, the "TSA News." The Utah Association of Radio & TV Servicemen is distributing a reprint of the contents of this department from a recent issue of RADIO & TELEVISION NEWS, along with copies of the Standard TV Labor Charges Charts in the hopes of encouraging service shop operators throughout the State of Utah to base their service charges realistically on sound pricing practices. The GMP Qualified Service Dealers of northern California are using the charts in an aggressive program to indoctrinate set owners in what they must expect to pay for competent, reliable TV service.

Wall charts (size 11 x 14 inches on heavy bristol board) of the schedules of standard TV labor charges are still available to readers of this department. You may obtain copies of these charts by sending $1.00 to the TTLB, P. O. Box 1321, Indianapolis 6, Indiana. In writing to the Bureau for charts, bulletins, or other information please be sure to *write your name and complete address* on your letter. A number of letters have been received asking for charts or bulletins without any other identification than the sender's name.

Your editors would also like to suggest that more service businesses should get the fine stationery that is offered to them by the tube companies. These letterheads, imprinted with the name of the service business, are very impressive. Here's a specific instance that clearly indicates the effectiveness of these imprinted letterheads that are made available to you through your parts distributors by the tube companies:

A new employee on the Bureau staff was assigned the job of filling requests for bulletins, Notebooks, and Standard TV Labor Charges charts. While casually watching her do her work, your

EXCLUSIVE AT RADIO SHACK!
$85 APPROVED FM-AM TUNER AT A SACRIFICE LOW PRICE!
12 TUBES! TUNED RF! ARMSTRONG-TYPE FM!



12 MINIATURE TUBES*
*Plus germanium diode AM detector!


ORDER NO. 36-206RN
7 LBS

$41.95

DUAL CASCADE LIMITERS!
NOT ratio detector but true HIGH-FIDELITY Armstrong-type FM, plus sensitive AVC AM. Twelve — not 8 — miniature tubes. 30-15,000 cps *cathode follower* output! Dual FM-AM band indicating lamps. Ultra compact to fit anywhere: 8¼ W x 5⅜ H x 8" deep.

TUNED RF STAGE FM, AM!
Yes! Tuned RF stage and separate RF and IF stages on both FM and AM. Rugged 6-GANG condenser! Hundreds now in use by appreciative music lovers from coast to coast. Attach to any amplifier, radio, TV set or sound system. Immediate delivery!

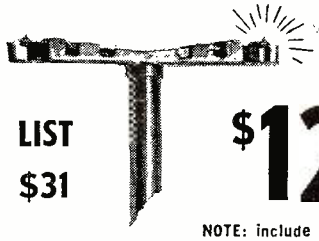SIMPLIFIED POWER SUPPLY
The model V-12 tuner comes less power supply, requires 6.3V AC @ 4 amps, 190V DC @ 35 ma. Available from us, 100% wired, for just $12.95. Order No. 36-207RN. 7 lbs.



DIAMOND-SAPPHIRE for G-E RPX-050

LIST $31

$12.95

NOTE: include est. postage

Big savings on a limited quantity of the EXACT RPX-050 replacement stylus with diamond tip for LP and sapphire tip for 78's. Here's a bargain every hi-fi fan will recognize, for America's most popular magnetic pickup, the G-E triple play! Guaranteed first quality; and the LP diamond is a genuine South African whole stone, not a fragile chip or splint. *Immediate delivery* on mail orders, while they last! Order No R-6008-N.


ORDER BY MAIL, PHONE, WIRE! FREE 224-PAGE CATALOG!

RADIO SHACK CORPORATION
167 Washington St., Boston 8, Mass. (Dept. RN)

www.americanradiohistory.com



SCR-274N COMMAND and ARC-5 EQUIPMENT

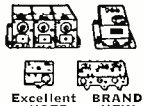

Type	USED	Excellent USED	BRAND NEW
BC-453 Rcvr. 190-550 Kc.	$21.50	$28.50	$44.50
BC-454 Rcvr. 3-6 Mc.	10.50	12.50	24.95
BC-455 Rcvr. 6-9 Mc.	10.95	12.95	17.95
BC-456 Modulator	——	2.75	5.75
BC-457 Xmtr. 4-5.3 Mc.	13.50	18.50	29.50
BC-458 Xmtr. 5.3-7 Mc.	8.50	9.75	29.50
BC-459 Xmtr. 7-9.1 Mc.	14.95	16.50	24.50
BC-450 3 Rcvr. control box	——	1.49	1.95
BC-451 Xmtr. control box.	——	1.25	1.49
3 Receiver rack	——	1.79	2.95
2 Transmitter rack	——	1.59	3.25
Single Transmitter rack	——	1.59	3.25

ARC-5/T-23 Transmtr, with tubes. Brand New $49.50

Terrific Transmitter-Receiver Buy!

FAMOUS BC-645 450 Mc.—15 Tubes



BRAND NEW $39.50 each

BRAND NEW, in original carton! Easy to convert for phone or CW 2-way communication, covering these bands: 420-450 Mc Ham Band, 450-460 Mc fixed or Mobile, 460-470 Citizens Band, 470-500 Mc TV experimental. Contains 15 tubes: 4-7F7, 4-7H7, 2-7E6, 2-6F6, 2-955, 1-WE-316A. Size 10½x13½x4¾". Wt. 25 lbs.

CONVERSION DIAGRAM INCLUDED!

PE-101C DYNAMOTOR for above BC-645 ..... $4.85

UHF ANTENNA ASSY, for above BC-645 ..... $2.45

HEADSETS

	Excellent USED	BRAND NEW
HS-23 high impedance	$2.95	$4.75
HS-33 low impedance	2.45	5.75
HS-30 low imp (featherwt)	1.49	2.45
H-16/U high imp (2 units)	——	4.95
CD-307A cords, with PL55 plug and JK26 jack, 8' long	——	1.19

Sensational Buy!

BC-221 FREQUENCY METER



JUST LIKE NEW! Limited quantity, first come, first served! Range 125 to 20,000 Kc, with crystal check points in all ranges. Complete with tubes, crystal, calibration charts.

YOUR COST $129.50

Modulated BC-221-AK BRAND NEW Complete $210.00

These Frequency Meters are factory treated, checked for frequency alignment and GUARANTEED.



BEACON RECEIVER BC-1206-C

Complete with 5 tubes. Tunes 195 KC to 420 KC. IF Frequency —135 KC. Receiver Sensitivity—3 Microvolts for 10 Milliwatts output. Output Impedance—300 Ohms and 4000 Ohms. Volume Control—RF Gain Control. Power Supply—24-28 Volts Aeroplane Battery, Current—.75 Amperes.

BRAND NEW $12.95

Used, as is, special $6.95

DYNAMOTORS

Type	Input		Output		Exc. Used	Brand New
DM-32A	28V	1.1A.	250V	.05A.	$4.90	$7.50
DM-33A	28V	5 A.	575V	.16A.	2.25	3.95
	28V	7 A.	540V	.25A.		
DM-40	14V	3.4A.	172V	.138A.	7.40	9.50
DM-28	28V		224V	.07A.	3.95	6.95
DM-21	14V		235V	.09A.	6.85	16.50
PE-73	28V	20A.	1000V	.350A.	9.50	12.50
PE-86	28V	1.25A.	250V	.060A.	2.95	5.50
PE-94A	28V	10 A.	300V	.200A.	7.50	11.50
			150V	.101A.		
PE-94B	28V	10A.	300V	.200A.	8.50	11.75
			150V	.101A.		
PE-94C	28V	10A.	300V	.200A.	10.00	12.75
			150V	.101A.		



WILLARD 6-VOLT MIDGET STORAGE BATTERY

3-amp hr. BRAND NEW. 3⅝"x 1-13/16"x2⅜". Uses standard electrolyte $2.65

WILLARD 2-VOLT STORAGE BATTERY

20 AMP. HR. BRAND NEW $2.69

Please include 25% Deposit with order—Balance C.O.D. MINIMUM ORDER $3.00. All Shipments F.O.B. Our Warehouse N.Y.C.

Dept. N-2

G&G Radio Supply Co.

51 Vesey St., New York 7, N. Y., CO 7-4605

Branch: 16 W. Kinzie St., Chicago, Ill.

editor noticed that she carefully separated the letters into two stacks—one stack consisted of letters on printed letterheads; the cards and other letters were put in the other stack. Then she filled the requests called for on the printed letterheads first and took special pains in supplying what they wanted.

In answer to a query about why she followed this routine she said, "Isn't it better to take care of the important companies first?"

The moral to that is: If you want to be rated as an "important company" in the eyes of office workers who may handle your correspondence, get yourself some printed letterheads.

Customer Relations

Perhaps the most important factor in the operation of a TV service business is that of maintaining good relations with its customers. The money factor involved in the servicing of sets isn't nearly so important in the mind of the customer when the simple rudiments of good customer relations practices are used in contacts with him.

A few years ago the *Central Television Service Company* of Chicago, perhaps the largest independent servicing organization in the industry, realized that good customer relations were essential to maintain the volume of business necessary to keep its 200 employees busy. They prepared a manual for their own staff and called it the "TV Technicians Handbook on Customer Relations." This manual tells you what to do if the customer invites you to have a drink with her, or if you do some damage to the customer's furniture, or if the customer insists on keeping the old CRT which you replaced. It also gives suggested answers to the oft asked questions: "Did I buy a lemon?" "What kind of set do you have in your home?" "Why is my neighbor's set better than mine, when I paid more for my set?" and many others.

Because of the large number of requests that the Bureau has received from the readers of this department for information on problems that come under the heading of customer relations, arrangements have been made with the *Central Television Service Company* for the Bureau to distribute copies of their handbook to readers who would like one. Send one dollar to TTLB Special Services Dept., P. O. Box 1321, Indianapolis 6, Indiana, and ask for the "*Central* CR Manual."

MODERN MICROPHONE DESK STAND


By ARTHUR TRAUFFER

EXCEPT for the plastic saucer, which was borrowed from the pantry, the writer built the microphone desk stand shown in the photograph from materials found in his "junk box." Even if you have to buy all the parts, this stand can be assembled for about 50 cents.

Bore a ⅜" diameter hole in the center of the bottom of a 5½" diameter plastic saucer. Obtain a 5" length of ⅛" pipe (⅜" o.d.) which is threaded on one end. Using a flat file, the other end of the pipe is reduced just enough for a drive fit into the end of an Amphenol 75-MC1M cable connector, as shown in the diagram. Tighten the setscrew in the connector.

Next fasten the pipe to the inverted saucer by means of two washers and two hexagon nuts, as shown. The pipe can be enameled to match the color of the saucer. The threads on the end of the cable connector are standard microphone threads and will fit sockets on all U.S.-made microphones except for RCA units which use a special thread. —30—

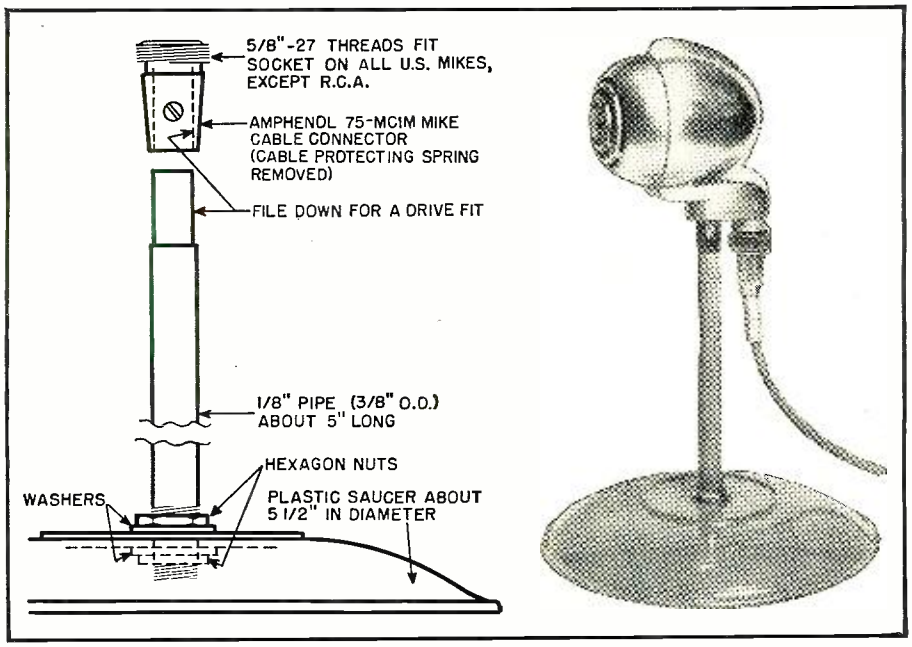Mechanical details for constructing the desk stand and photo of finished product.



www.americanradiohistory.com

Leonard Smith, president of the Texas Electronics Association, sent in a suggested solution to a ticklish problem facing service operators. In Fort Worth, Texas, they were up against the growing problem of customers who had made no credit arrangements before a service job was completed, telling technicians to "Charge it," when presented with the bill. When the technician used the stock answer, "Sorry, we don't do a credit business," the customer usually blew a fuse.

To whip this problem, Stan Taber of *Acme Radio & TV* of Fort Worth, bought some credit applications from the Fort Worth Retail Merchants Association with the Credit Bureau seal on them. He gave each of his field service technicians a supply of these forms to carry in his car. When a customer says "Charge it," the technician asks him if he has a charge account with the company. If the answer is "No," the technician hands him a credit application and says, "Sir, since you don't have an account with us, this job must be cash. However, if you will fill out this application and mail it to us we will be able to handle any future work on a charge basis after the application has been approved."

Mr. Taber reports that nine out of ten customers do not fill out and send in the applications and the way is paved for all future relations with him to be on a cash basis without having the customer blow a gasket. —30—

COMPUTER CONFERENCE

THE second annual Western Computer Conference and Exhibit, sponsored jointly by the AIEE, IRE, and Association for Computing Machines, will be held at the Ambassador Hotel in Los Angeles on February 11 and 12.

The conference is composed of two parallel sessions, one on control systems and one on data processing systems.

The exhibit portion of the meet will feature the latest electronic computing machines which are capable of solving the most complex problems.

For further information write H. G. Weightman, publicity chairman, at Weightman & Associates, 1405 W. Magnolia Blvd., Burbank, California. —30—

RADIO COURSES

NEW YORK University has announced several courses of interest to persons in the radio, television, audio, and electronic fields in addition to the basic courses on fundamentals the school offers.

The courses, which will run from February 3 to May 19, include elements of radio tubes and circuits; radio tubes and circuits (2); transistor applications in modern electronics; television circuits; television transmitter and u.h.f. circuits; operation and maintenance of TV equipment; measurements and testing in radio, audio, and TV; high-fidelity reproduction of sound; and radio operator license tutorials.

For full details write to the Program of Technical Studies, New York University, Division of General Education, 3 Washington Square, North, New York 3, N. Y. —30—

BUY DIRECT AND SAVE

'PRE-FAB' COLLINS TUNERS and RECEIVERS


OUTSTANDING for HIGH FIDELITY!

AUDIO PRODUCTS CO.

Two ALL NEW Complete Kits for Every High-Fidelity Need


Collins Audio Products Co. is in no way affiliated with Collins Radio Co.

Each Collins Tuner Kit is complete with punched chassis, tubes, power transformer, power supply components, hardware, dial assembly, tuning eye, knobs, wire, etc., as well as the completed sub-assemblies: FM tuning units, AM tuning units, IF amplifiers, etc., where applicable. All sub-assemblies wired, tested and aligned at the factory make Collins Pre-Fab Kits easy to assemble even without technical knowledge. The end result is a fine, high quality, high fidelity instrument at often less than half the cost—because you helped make it and bought it direct from the factory.

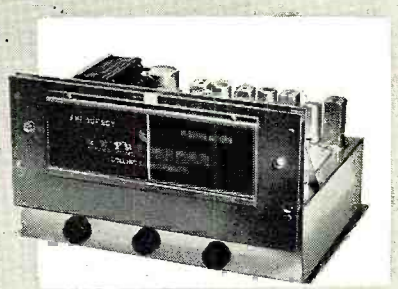


FM Tuner Kit $55

The FM-11 tuner is available in kit form with the IF Amplifier mounted in the chassis, wired and tested by us. You mount the completed RF Tuning Unit and power supply, then after some simple wiring, it's all set to operate. 11 tubes: 6J6 RF amp, 6AG5 converter, 6C4 oscillator, 6BA6 1st IF, (2) 6AU6 2nd and 3rd IF, (2) 6AU6 limiters; 6AL5 discriminator, 6AL7-GT double tuning eye, 5Y3-GT rectifier. Sensitivity 6 to 10 microvolts, less than ½ of 1% distortion, 20 to 20,000 cycle response with 2DB variation. Chassis dimensions: 12½" wide, 8" deep, 7" high. Illustrated manual supplied. Shipping weight 14 lbs.

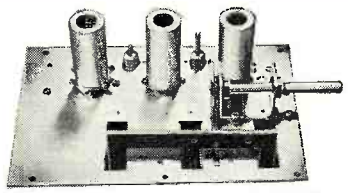


FMF-3 Tuning Unit $15.25

The best for FM. The most sensitive and most selective type of "front end" on the market. 6 to 10 microvolts sensitivity. Image ratio 500 to 1. 6J6 tuned RF stage, 6AG5 converter, 6C4 oscillator. Permeability tuned, stable and drift-free. Chassis plate measures 6½"x4½". In combination with the IF-6 amplifier, the highest order of sensitivity on FM can be attained. Tubes included as well as schematic and instructions. Draws 30 ma. Shipping weight FMF-3: 2½ lbs. Dial available @ $3.85.

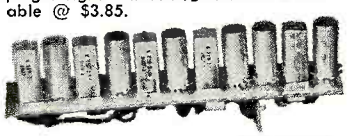

IF-6 Amplifier $19.75

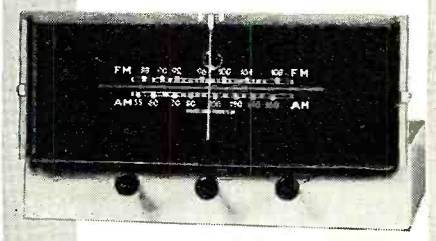A remarkable value! 6 tubes are used in the IF amplifier: 6BA6 1st IF, (2) 6AU6 2nd and 3rd IF's, (2) 6AU6 limiters and 6AL5 discriminator. High gain, wide-band response (200 KC) for highest fidelity. 20 to 20,000 cycles. Distortion less than ½ of 1%. Draws 40 ma @ 220 volts. Chassis plate dimensions: 11 5/16" x 2½". Shipping weight: 3 lbs.



FM/AM Tuner Kit $77.50

The original 15 tube deluxe FM/AM pre-fab kit redesigned on a smaller chassis. The tuner now measures 14" wide by 12" deep by 7½" high. This attractive new front and dial assembly opens up new applications where space is at a premium. Kit includes everything necessary to put it into operation—punched chassis, tubes, wired and aligned components, power supply, hardware, etc. Kit comprises FMF-3 tuning unit, IF-6 amplifier, AM-4 AM tuning unit, magic eye assembly and complete instructions. All tubes included. Shipping weight 19 lbs.



AM-4 Tuning Unit $24.50

Tops in AM superhet performance! A 3-gang tuning condenser gives 3 tuned stages with high sensitivity and selectivity. Assembly is completely wired, tested and aligned ready for immediate use. Frequency coverage 540 KC to 1650 KC at a sensitivity of 5 microvolts. Tubes 6BA6 RF amplifier; 6BE6 converter; 6BA6 IF amplifier and 6AT6 detector. Draws 30 ma @ 220 volts. Mounts on a chassis plate measuring 4"x7⅜". Shipping weight 2½ lbs. Dial available at $3.85.

MAIL COUPON TODAY

To: Collins Audio Products Co. Inc.
P.O. Box 368, Westfield, N. J. RN-2
Tel. WEstfield 2-4390

☐ FM Tuner Kit ☐ FM/AM Tuner Kit ☐ Slide Rule Dial Assembly
☐ FMF-3 Tuning Unit ☐ IF-6 Amplifier ☐ AM-4 Tuning Unit

NAME .....

ADDRESS .....


CITY ..... STATE .....

Amount for Kit $..... See weights, add shipping cost $.....

Total amount enclosed $ Check ☐ Money Order ☐

WHEN YOU THINK OF TUNERS, THINK OF COLLINS AUDIO PRODUCTS

www.americanradiohistory.com

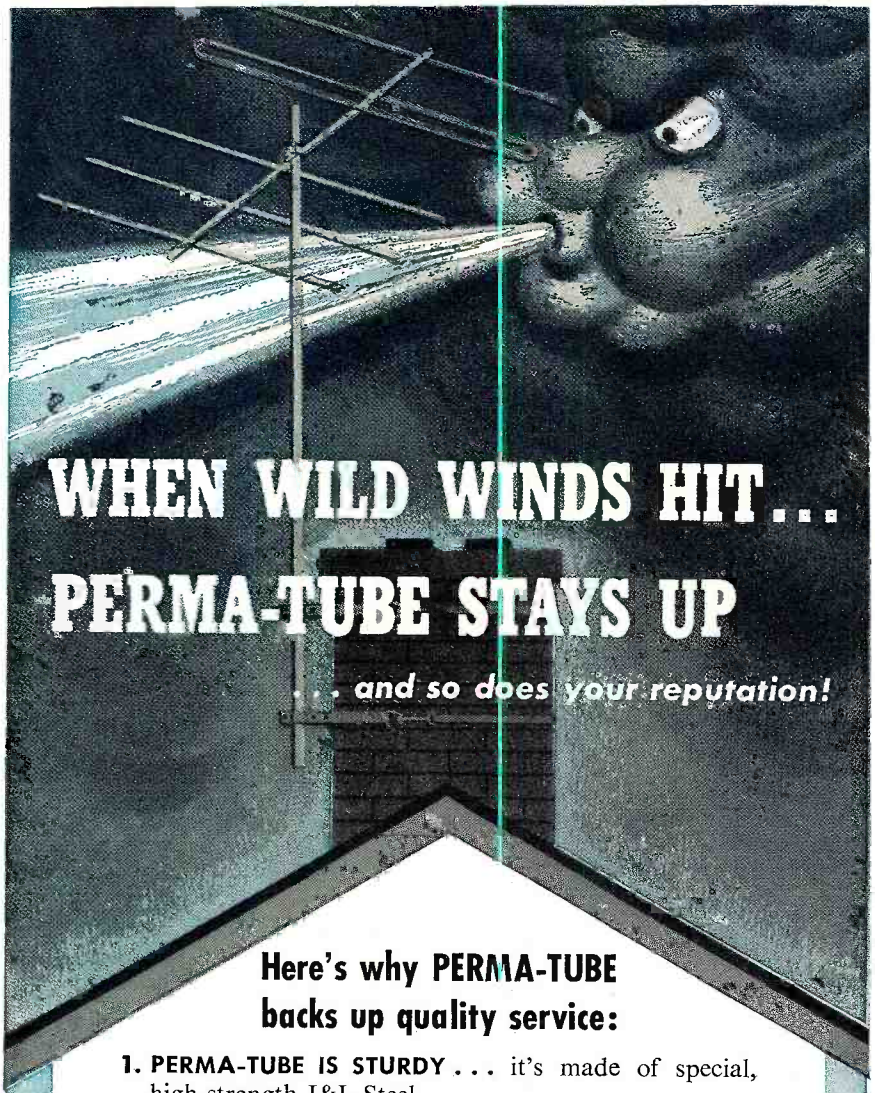

WHEN WILD WINDS HIT... PERMA-TUBE STAYS UP

. . . and so does your reputation!

Here's why PERMA-TUBE backs up quality service:

1. **PERMA-TUBE IS STURDY . . .** it's made of special, high-strength J&L Steel.
2. **PERMA-TUBE IS CORROSION-PROOF . . .** it's treated with vinsynite—then *coated inside and outside* with a metallic vinyl resin base.
3. **PERMA-TUBE IS EASILY INSTALLED . . .** it's the only mast with *both ends* of the joint machine fitted.

Here's proof of Perma-Tube's superior strength.

Ordinary masts and Perma-Tube were subjected to regular deflection and permanent set tests with the following results:

TV Mast Tested	*Size and B W Gauge*	*Bending Force To Produce 2½ lbs Set*
Mast A	1¼" OD x 20 Ga.	1870 inch pounds
Mast B	1¼" OD x 18 Ga.	2740 inch pounds
Mast C	1.65" OD x 17 Ga.	2780 inch pounds
Perma-Tube	1¼" OD x 18 Ga.	2930 inch pounds
Mast D	1¼" OD x 15 Ga.	4370 inch pounds
Mast E	1¼" OD x 16 Ga.	4560 inch pounds
Perma-Tube	1¼" OD x 16 Ga.	5950 inch pounds

CHECK THE 500 HOUR MINIMUM SALT SPRAY TEST RATING OF YOUR TELEVISION MASTS (Am. Soc. of Testing Materials—Spec. 5117-49T). Remember Perma-Tube passes this test . . . remains corrosion-proof.

J&L STEEL

Jones & Laughlin STEEL CORPORATION — *Pittsburgh*

What's New in Radio

(*Continued from page 94*)


sistors are currently available with guaranteed alpha minimums of .90 for the Type 200, .95 for the Type 201, and .98 for the Type 202.

For further information write the company at 6000 Lemmon Avenue, Dallas 9, Texas.

NEW PM MOTOR

Pioneer Electric & Research Corporation, Forest Park, Ill. is now in production on a new miniature permanent magnet motor which is smaller than a standard cigarette pack.

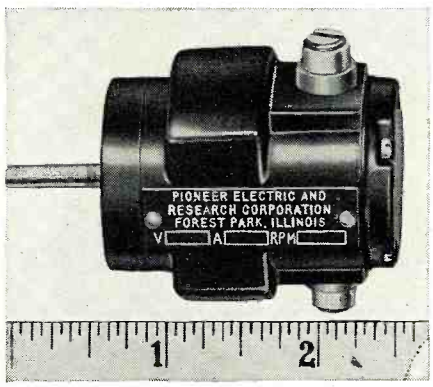The new unit offers horsepower ratings from .004 to .0165 and speeds from 2000 to 20,000 rpm with total weights from 3.5 to 9 ounces. It is made with its magnetic structure cast into an aluminum housing. In its basic



construction the new motor conforms to JAN specifications although optional features (watertight and explosion-proof housing, fungicided armature, noise filter, speed governor, and gear reducer) are available.

WIRE STRIPPER

Holub Industries, Inc. of Sycamore, Illinois is currently in production on a completely automatic wire stripper that eliminates triggers, cocking, or other holding devices.

Known as the "Hi-Speed" wire stripper, the new unit is designed to strip all kinds of building and fixture wire with a single squeeze of the handles. After the wire is stripped, a concealed cam holds the jaws open until the wire is removed.

The stripper is made in seven sizes for stripping Nos. 8 to 30 solid and stranded wire, also POSJ for parallel wire and 300-ohm flat twin-lead. An adjustable stop is furnished with each tool.

MINIATURE CONNECTORS

Viking Electric, 1061 Ingraham St., Los Angeles 17 is now offering an improved series of miniature rectangular connectors with 7, 8, 14, 18, 20, 21, 34, or 41 contacts.

Except for the 8-contact unit, all connectors are interchangeable with similar equipment. The company will forward a complete catalogue on these units on request. —30—

www.americanradiohistory.com

The publisher of a fascinating new magazine explains its purposes and offers you the first copy with his compliments...



MUSIC at HOME is a completely new kind of magazine, planned to help everyone find more entertainment in hi-fi records, tape and FM radio. The wealth of intriguing articles, dramatically illustrated, covering both music and equipment, express the concept that music is for everyone, and the more realistic the reproduction, the more enjoyable the music — whether the original was a symphony orchestra, a hot trombone, or a crooner giving out with the blues!

With the perfection of LP records, tape recorders, FM radio, and hi-fi equipment, people are coming to realize that music can make a more important contribution to the home than any other form of entertainment.

It has a special appeal to each member of the family, from the little tot who, with uncertain steps, responds to the rhythm of tunes for children, to the grandparents for whom music recreates happy events of days gone by. And for those ages in between, there is music for dancing, for relaxation, and for the pure joy of listening. This assumes, of course, that what is heard from the loudspeaker is an accurate recreation of the original music, which we have come to call hi-fi reproduction.

The purpose of MUSIC at HOME is to help you:

1. Select the best recordings of the kind of music you enjoy the most,

2. Learn more about the many exciting uses of tape recorders,

3. Find the FM stations that are providing top-quality programs,

4. Select the kind of hi-fi equipment suited to your particular needs, within the limits of your budget,

5. Install the equipment so that it will be both decorative in appearance and fine in performance,

6. Use the equipment correctly, so that you will have all the thrilling enjoyment from your music that hi-fi reproduction can provide.

In short, MUSIC at HOME is a how-to-do-it magazine, filled with articles and special features planned for the thousands of people who are interested in learning more about this wonderful form of home entertainment.

The special offer below is extended so that you can have the first issue with my compliments, and see for yourself how interestingly the subjects of music and hi-fi equipment are presented in MUSIC at HOME.

Milton B. Sleeper.

Music AT HOME

HI-FI REPRODUCTION FROM RECORDS, TAPE, AND FM RADIO

The following offer is made so that you can judge the value of MUSIC at HOME to you and your family, without risking even the very modest cost of a subscription:

Send in your order, using the coupon below. The first issue will be sent you with our Publisher's compliments. If you are not so delighted with this first issue that you will want to receive those following, write us within 30 days after you receive the first copy, and the full amount of your remittance will be refunded promptly, without question. MUSIC at HOME is a large-size magazine, handsomely designed, elaborately illustrated with photographs and drawings, and beautifully printed on fine paper. You'll enjoy it from cover to cover, and you'll be proud to show it to your friends. **Mail your order today, so you can be sure of getting it from the very first issue.**

Milton B. Sleeper, Publisher
207 East 37th Street
New York 16, N. Y.

Please send me the first issue of MUSIC at HOME without charge, and enter my subscription to start with the second issue. My remittance is enclosed for

☐ $6.00 for 3 years (18 issues)
☐ $3.00 for 1 year (6 issues)

If I am not completely satisfied with the first copy, I will notify you within 30 days, and you will return my remittance in full.

Name.....

Address.....

City & Zone.....State.....

www.americanradiohistory.com

SOLVE your hi-fidelity problems with
University
CONE SPEAKERS
-HIGHEST QUALITY!
-LOWEST COST!



MODEL 6201 — COAXIAL SPEAKER SYSTEM. Now generally acknowledged to be industry's finest value in a high quality 12" speaker. TRUE coaxial dual range system comprising clean sounding woofer with heavy exclusive Alnico 5W magnet, DRIVER TYPE tweeter with "Reciprocating flares" wide angle horn, and BUILT-IN crossover network complete with "Balance" control.

DIFFUSICONE-12 — WIDE RANGE WIDE ANGLE 12" SPEAKER. Exclusive "diffusicone" design utilizes the benefits of dual-horn loading, radial projection and diffraction principles to achieve unsurpassed quality and sound distribution from a single unit speaker. Enjoy full fidelity ANYWHERE in the room . . . at a surprisingly reasonable cost.





DIFFUSICONE-8 — WIDE ANGLE 8" SPEAKER. Same as the Diffuscione-12 except in 8" size. Remarkable fidelity and exceptional sensitivity and power handling capacity make this a truly outstanding eight. Ideal for use where space is limited, and is also a perfect selection for a mid-range speaker in 3-way systems.

MODEL 6200—EXTENDED RANGE 12" SPEAKER. Designed for general applications, capable of highly efficient FULL-BODIED response throughout the operating spectrum. May be used with equal facility to improve commercial radio, TV, phono sets, high quality sound re-inforcement in night clubs, churches, schools, etc., or as a woofer. The 6200 must be heard to be appreciated.





MODEL C-15W—DUAL IMPEDANCE RANGE 15" WOOFER. Brand new low frequency reproducer embodying many exclusive advance features. Its superior response and acoustic output is due, in part, to a newly University-developed cone and voice coil suspension system permitting the greatest axial movement ever achieved. The incredibly low distortion results from a new magnet assembly.

There is a UNIVERSITY Tweeter for every application and pocketbook. Write for descriptive illustrated literature. Address Desk RT-2.

University
LOUDSPEAKERS INC
80 SO. KENSICO AVE., WHITE PLAINS, N. Y.

Certified Record Revue

(*Continued from page 56*)

orchestra wound up, he made a terrifying experience of this evil fable. The Borodin and Glinka pieces, while of less stature on this disc, nevertheless are recorded with equal effectiveness. Control setting was flat for the *ffrr* curve. Surface in my copy a little "ticky."

SCRIABIN
THE POEM OF ECSTASY and THE POEM OF FIRE
New York Philharmonic conducted by Dimitri Mitropoulos. Columbia ML 4731, NARTB curve. Price $5.95.

Back in the days when I was more of a romantic than I am now I greatly admired the old Monteaux version of "The Poem of Ecstasy." I thought that was really great shakes as an example of "mood" music. When one becomes more musically mature, one realizes that there is a good deal that is trite and banal in this score. I suppose what really fascinated me was not so much the music as the composer. Now this boy Scriabin was a real squirrel! I haven't got the space to go into all of it here, but he was a character from the word go. He was "high priest" of a sort of "back to nature" cult and as years passed he became ever more of a mystic. He believed that art forms are at their best when co-mingled and he was wont to give and sponsor recitals in which music and voice were merely parts of his whole philosophy as they were combined with color and even odor! For all of his eccentricities he was a clever rascal. He invented a color "organ" an instrument that would produce myriad color variations projected on a screen, by keying certain prisms and mirrors, etc. Yes Sir! Some character! This recording is as good an exposition of this music as you're likely to get in some time. It is far superior to the recent version on *Capitol*, at least as far as sound is concerned. The *Capitol* disc was noteworthy for a good performance. Mr. Mitropoulos has a particular affinity for music like this and his reading accents the broad line rather than highlight detail which, while important, obscures the composers intent. Sound or this disc is typical of some of the late *Columbia* efforts, which is to say, splendid. The strings are well delineated without being edgy, woodwind playing is reproduced with particularly fine overtone and vibrato. "The Poem of Fire" is equally well recorded and performed. Since this is the second of Scriabin's tone poems, its roots in his ever increasing mysticism are clearly evident. Some wonderful sounds on this side and a bow to Leonid Hambro for some brief but very effective solo piano. Conformed perfectly to NARTB curve and required no treble or bass, cut or boost. Surfaces were quiet.

DVORAK
SYMPHONY #2 IN D MINOR
Hamburg Radio Symphony Orchestra

ID-WINTER SALE
PRICES SLASHED

T.V. TUBES—ROCK BOTTOM PRICES
In lots of 6 each No. only

6BG6	.89c	6BQ6	.57c	1L4	.45c
19BG6	.89c	6AQ5	.38c	1T4	.45c
12AX7	.47c	6CD6	$1.05	6X4	.36c
6CB6	.39c	6S4	.37c	6V6GT	.38c
6AK5	.63c	6T8	.55c	6AX4	.52c

6X5 .35c
6SA7 .42c
6AT6 .36c
6BA6 .38c
6BE6 .38c

Tube Special—Broken Keys—Electrically Perfect
12A6..29c; 4 for $1.00 12K8..49c; 7 for $3.00
Tube Sale—#2A7-55-27-85-31-56. No Mixed Ass't. 6 of Any Type $1.75
RCA UV876 Tubes.....50c
Heavy Duty Shielded P.P. Input Trans.....$1.00
H.D. Silver Contact Trans. Keys..... 1.00
Isolantite Octal Panel Clamp Sockets.....3c ea.
100 Assorted Resistors.....$1.95
1 Mfd., 1,000V Oil Filled Cond.....75c
2 Gang Var. Cond. 456 K.C. with Osc. Section, 2¾ in. Pulley on ⅜" Shaft.....49c
Westinghouse Kuprox Rectifier 0.64 Amp. 28 Volts. Reg. $11.00 ea. Special.....$1.95
BRAND NEW 10" PHONO RECORDS—Ass't. Jazz—Popular, Rhythm—Blues. Please specify. 12 for $1.79 or 24 for $3.00 or 50 for $5.75
Single Pole—10 Pos. 2-Gang Switch.....29c
Grind your own Crystals. Pure Brazilian Quartz. Various sizes and thicknesses. ¼ lb. pkg.....$1.00
4-Tube Drilled Chassis. 4½"x6½"x1¾".29c each
Signal Corps Phones—2 M. Ohms (8 M. Ohms Imp.) Brand new.....$1.75
2 Ft. Ext. Cord (and Plug).....40c
2¾"x4" Bake. Panel Mounting—5 Res.; 6 Mica Cond.; 2 Choke Coils.....49c
2½ M.H. R.F. Choke Coil.....27c ea.; 4 for $1.00
7 Ft. Und. App. AC Line Cord.....20c
Miniature 9 pr. Sockets.....7c Ea.; 60c Doz.
RCA 4"x6" Oval P.M. Speakers.....$1.25
5x7" Oval 1700 Ohm Dyn. Speaker.....$1.69

TUBULAR ELECTROLYTICS
20-20 MFD. 150 V..49c 30-30 MFD. 150 V..57c
40-40 MFD. 150 V..59c 80-50 MFD. 150 V..75c

Low-Loss Short Wave Lock Type Air Trimmer Variable Condensers
5 Pl.—20 Mmfd.....16c
7 Pl.—25-30 Mmfd..18c
8 Pl.—30-35 Mmfd..20c
14 Pl.—56 Mmfd....28c
D.P.D.T. SLIDE TOGGLE SWITCH 15c

1,000 OHM WIRE WOUND POTENTIOMETER....15c
30 HY-FILTER CHOKE SHIELDED.....3 for $1.25
PIEZO CRYSTAL HOLDERS.24 for $1.25; $3.50 per C
RCA Band Switches—
3 gang, 3 pos. 3 band.30c 6 gang, 4 pos. 4-5 band.40c
Trimmer-Padder Asst.—all isolantite—singles, dual: triples—100 asst.....$2.25
ATTENTION: Prospectors, Explorers for Hidden Treasures! Construct a U.S. Army Type of Metallic Mine Detector Amplifier. Amplifier unit only (less tubes and batteries) with cables, headphone cord, and jack. Army wiring diagram. Type AN/PRS-1.....$1.95
Philco push button Rotary Switch Double Pole...35c
8 Gang Push Button Switch.....49c
DRILLED CHASSIS FOR 5-6 tubes 5"x10"x1¾"..25c
PHONE JACKS—OPEN & CLOSED AUTO.....18c
SALE—PHONO RECORD ALBUMS—12"—3 comp.—15c; 10"—3 comp.—15c; 4 comp.—20c; 12 comp.—69c
VULCAN HEAVY DUTY 100 WATT SOLDERING IRON. Built for U.S.N.—Brand New—Equiv. sells for $8.50.....OUR PRICE $3.25

MINIMUM ORDER $3.00—NO C.O.D.
SHIPMENTS—PLEASE INCLUDE POSTAGE
NEWARK SURPLUS MATERIALS CO.
324 Plane Street, Dept. FE, NEWARK 1, N. J.

VARIETY ELECTRIC CO., INC.
468-470 BROAD ST.
NEWARK 2, N. J.

has hallicrafters
• 10 Kc to 250 cycles in six steps!
• The most *stable* receiver made!
• Single Side Band Suppressed Carrier!
The Hottest Ham News in Years!
THE HALLICRAFTERS CO. • CHICAGO 24, ILL.

RADIO and TELEVISION ELECTRONICS
RCA
in all Technical Phases
New Classes (Day and Evening) Start 1st of Dec., Mar., June, Sept.
Free Placement Service for Graduates
For Free Catalog write Dept. RN-54
RCA INSTITUTES, INC.
A Service of Radio Corporation of America
350 WEST 4TH ST., NEW YORK 14, N. Y.

FREE • BARGAIN LIST • FREE
1N34 Crystal diode cartridges.....5 for $1.00
6AL5 tubes.....5 for 1.50
6J6 tubes.....3 for 2.49
Stancor, boxed choke C-1410, 4HY 174 MA... 2.60
Sensitive plug in relay, SPDT, 2K ohm, 2MA.. 3.95
Telephone relays (11) in metal box, new..... 9.90
Hring Aid test panel, with 2" GE O-1 MA meter 9.95
Send for Free Bargain List
POLY-TECH
253 E. 32nd St. New York 16, N. Y.

www.americanradiohistory.com


conducted by Hans Schmidt-Isserstedt, London LL778, ffrr curve. Price $5.95.

Those of you who know this work and have been waiting for a really top notch recording, will be gratified to know that your wait is over. At least that is the way I feel about this present version. As one of Dvorak's most interesting and beautiful works, I could not understand the neglect which seemed to be its lot. After all, the LP companies have been turning out hundreds of items far less "standard" than this work. Yes, there has been a previous version on LP, issued by *Urania*. But what worthiness this record had as a performance was marred by its uneven and undistinguished sound. This *London* recording has the advantage of splendid engineering. Blessed with a very live, spacious type of sound, it's not too far off mike to destroy important inner detail. String tone is generally good, some may want to roll off the treble ever so slightly. Percussion is solid, authoritative. Schmidt-Isserstedt is obviously an old hand at conducting this lovely score and he lavishes attention on it to achieve a gracious and compelling reading. He senses the need to maintain a broad melodic line as a framework for Dvorak's colorful orchestration. The disc reproduced well with the *ffrr* curve with perhaps the little extra treble roll-off, I mentioned before. Surfaces were quiet.

AMERICANA
Eastman Rochester Symphony Orchestra conducted by Howard Hanson. Mercury MG 40003, AES curve. Price $5.45.

This is a most unusual disc which will appeal to a greatly diversified group of people. A collection of works by American composers such as Aaron Copland, Wayne Barlow, and Dr. Hanson, the emphasis here is on solo winds such as flute, oboe, and clarinet, accompanied by string orchestra. There is some really beautiful music represented here and some particularly expert performances. The works vary widely, ranging from Copland's "Quiet City," a rather contemplative and moody piece with fine trumpet solo by Sidney Mear, to Dr. Hanson's lovely "Serenade for Flute, Strings, and Harp." This latter work is an inexpressibly beautiful outpouring of sound with some wonderful flute playing by Joseph Mariano. Believe me, if your wife doesn't like this work, you may as well give up this hi-fi business. This is passionate, beguiling music, with a universal appeal. The other pieces are equally interesting and well performed, and the woodwind sound throughout this disc is so clean and articulate, that the disc is sure to find favor among students of the instruments involved. It is interesting to note that while this disc is composed of solo works, *Mercury* did not resort to the use of an extra pickup mike for the solo instruments using their single *Telefunken* as usual. The result is a splendidly balanced recording with the soloists in their proper concert hall perspective.

TG-34A KEYER

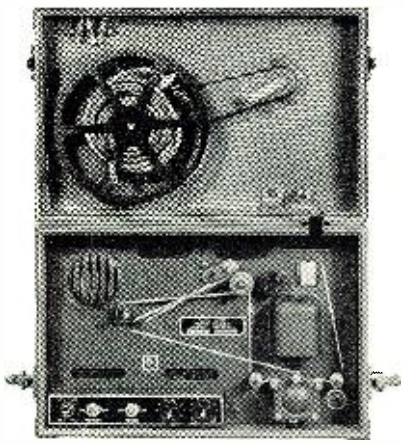

PORTABLE

• 115 or 230 V. @ 50 to 60 cycle—KEYER TG-34A is an automatic unit for reproducing audible code practice signals previously recorded in ink on paper tape. By use of the self contained speaker, the unit will provide code practice signals to one or more persons or provide a keying oscillator for use with a hand key. The unit is compact, in portable carrying case, complete with tubes, photo cell, and operating manual. Size: 10 9/16" x 10 1/2" x 15 13/16". Shipping weight: 45 lbs. BRAND NEW—in Original Box—While They Last Only: $24.95

NEW—LOW—LOW PRICES

ARC-5 COMMAND EQUIPMENT:

R-25/ARC-5 Rec. 1.5 to 3 MC. No Tubes.	Used:	$14.95
R-26/ARC-5 Rec. 3 to 6 MC. No Tubes.	Used:	7.95
R-27/ARC-5 Rec. 6 to 9 MC. No Tubes.	Used:	6.95
R-28/ARC-5 Rec. 100 to 156 MC. No Tubes.	Used:	12.95
T-20/ARC-5 Trans. 4 to 5.3 MC.	New:	16.95
T-22/ARC-5 Trans. 7 to 9 MC.	Used:	14.95

274-N COMMAND EQUIPMENT:

BC-454 Rec. 1.5 to 3 MC.	Used:	$10.95
BC-455 Rec. 6 to 9 MC.	Used:	9.95
BC-458 Trans. 5.3 to 7 MC.	Used:	9.95
BC-459 Trans. 7 to 9 MC.	Used:	14.95
BC-456 Modulator	Used:	2.95
FT-225 Mtg. F/BC-456	Used: 50c... New:	.95
FT-220 3 Rec. Rack	Used: $1.50... New:	2.50
FT-221 3 Rec. Shock	Used: .50c... New:	.95
BC-450 3 Rec. Cont. Box	Used: $1.50... New:	2.00
BC-451 Trans. Cont. Box	Used: $1.00... New:	1.50
PLUG—Male for rear of Rec. or Trans.		.55
DM-32 Dynamtr F/Rec. 24V.	Used: $2.95.. New:	6.95
DM-33 Dynamtr F/Modulator & Trans.	Used:	2.95

BLOWERS—115 VAC 60 CYCLE



SINGLE TYPE: (Illustrated at left) 100 CFM. 2¼" intake: 2" outlet. Complete size: 5" x 6". Order No. 1C939 ..... $8.95

DUAL TYPE: 100 CFM. 4" intake; 2" Dis. Each Side. Complete Size: 8" x 6". Order No. 1C880 ..... $13.95

COMPACT TYPE: 108 CFM. Motor built inside squirrel cage, 4½" intake; 3⅜" x 3" Dis. Complete size: 4¼" W x 8⅜" H x 8⅛" D. Order No. 2C067 ..... $14.50

FLANGE TYPE: 140 CFM. 3½" intake; 2½" Dis. Complete size: 7½" W x 7¼" H x 6¾" D. Order No. 1C807 ..... $13.95

FLANGE TWIN: 275 CFM. 4½" intake; 3¼" x 3" Dis. Complete size: 11¾" W x 8⅜" H x 8-1/16" D. Order No. 2C069 ..... $21.95

AERIAL WIRE—Phosphorus Bronze #16 Stranded, 200 lb. test, Weatherproof, 150 Feet on Reel. RL-3 with Clips $1.50

SOUND POWERED HEAD AND CHEST SET



Navy Type—No Batteries Required—Ideal for TV Antenna Installations and many other uses. 20 Ft. Cord. Used - Tested: ..... $5.95 EA.

TELEPHONE WIRE FOR THE ABOVE

COMBAT TYPE—2 Cond. Twisted, Rubber Covered, Medium Weight, W-130 ..... @ .01c per Ft.

FIELD WIRE—2 Cond. Twisted, Weatherproof, Heavy Duty, W-110—525 Ft. Roll.. $4.75

COPPER WELD WIRE — Weatherproofed, 2 Cond. Solid. 1200 Ft. Roll, $10.00. Per Ft. @ .01c per Ft.

FREE CATALOG

LISTING HUNDREDS OF TRULY EXCEPTIONAL "BUYS"!—WRITE FOR YOUR FREE COPY NOW!

DYNAMOTORS


HEAVY DUTY MOBILE DYNAMOTOR:

14 V. INPUT—Output: 1030 VDC 260 MA. Tapped 515 V. 215 MA. use @
6 V DC INPUT—500 V. 175 MA. While they last—
DM-42: ..... Excel. Cond.: $14.95 ..... New: $29.95

INPUT VOLTS:	OUTPUT: VOLTS:	MA.	STOCK No.	PRICES: USED:	NEW:
14 VDC	230	90	DM-21	$9.95	
14	330	150	BD-87	6.95	$8.95
14	250	50	DM-25	6.95	8.95
14	1000	350	BD-77	22.50	39.95
28	230	100	DA-1A	3.95	5.95
24	250	60	DM-32	2.95	6.95
24	575	160	DM-33	2.95	
28	210	125	DY-22	7.95	
24	220	80	DM-53	3.95	
28	1000	350	PE-73	8.95	
14	172	138	DM-40	6.95	8.95
28	250	60	PE-86	2.75	8.95
12 or 24	500	50	USA/0515		4.95
12 or 24	275	110	USA/0516		4.95
12	150	100	DM-310X	4.95	7.95
6 or 12	500	160	PE-103	29.95	39.95
12	230	90	PE-133	6.95	8.95
18	450	60	SP-175	3.00	4.95

PE-101 DYNAMOTOR—6 or 12 Volt. (Reprints of original CQ conversion articles—Oct. & Dec., '52 issues—furnished.) This is the Dynamotor the Hams have been talking about! Easily adapted to supply 625 V. @ 150 MA. and 325 V. 125 MA. @ 12 Volts—or 300 V. 90 MA. and 160 V. 110 MA. @ 6 Volts ..... NEW: $4.95

ANTENNA EQUIPMENT

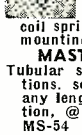

MAST BASES—INSULATED:

MP-132 BASE—Illustrated at left—1" heavy coil spring, 2" insulator. Overall length: 11½." Weight: 2¾ lbs. Price $3.95

MP-S-33 BASE—Insulated type with heavy coil spring and 5" dia. insulator. Requires 2" hole for mounting. Weight: 9 lbs. $5.95

MP-48 BASE—Insulated type base with heavy coil spring. Requires 1⅜" mounting hole. Weight: 11 lbs. $6.95

MP-37 BASE—Insulated type with heavy coil spring: 7" dia. insulator; requires 1⅜" hole for mounting. Weight: approx. 10 lbs. $8.95

MAST SECTIONS FOR ABOVE BASES:

Tubular steel, copper coated, painted in 3 ft. sections, screw-in type. MS-53 can be used to make any length with MS-52-51-50-49 for taper. Any section, @ 50c each. Larger Diameter Section:
MS-54 ..... $1.25

COAXIAL CABLES:

RG-8/U (SPECIAL) 51.5 ohms. Same size as RG-8/U. Prices: 1 to 100 ft. @ 8c per ft.—100 to 500 ft. @ 7½c per ft.—500 to 1000 ft. @ 7c per ft.—1000 ft. Rolls @ 6½c per ft.
RG-34/U—71 ohms, 145 ft. length $15.00

TRANSFORMERS—110 V. 60 CYCLE PRI.:

5 Volt CT-25A—10,000 V. Ins. OPEN FRAME—6" x 5" x 4½" $7.95

6.3 V. 1 Amp.	1.25	24 V. 1 Amp.	1.95
24 V. ½ Amp.	1.50	24 V. 6.5 Amp.	5.95
6—24—or 30 Volt 8 Amp.			5.95

BATTERY SWITCHING UNIT and METER

Used to switch load from one battery to another—or 6 to 12 Volts. Contains 2" Meter—0-15 Volt DC Scale for reading battery voltage. 20 Amp DPDT Switch and Indicator. Case size: 4" x 6¼" x 2¾" ..... NEW: $2.95

Address Dept. RN • Minimum Order $5.00 • Prices F.O.B., Lima, Ohio • 25% Deposit on C.O.D. Orders

FAIR RADIO SALES 132 SOUTH MAIN ST. LIMA, OHIO

www.americanradiohistory.com

New 2nd Edition



THEORY AND DESIGN OF ELECTRON BEAMS

By John R. Pierce
Bell Telephone Laboratories, Inc.

Here is a truly basic presentation of the theory of electron flow. It is particularly useful in the analysis and design of microwave amplifier and oscillator tubes, cathode ray tubes, and other devices in which a high beam current is important. It also includes much fundamental material on general electron optical problems, with emphasis on such important topics as space charge, thermal velocities and periodic focusing. New material that has not yet been published has been integrated with fundamental relations from many sources to provide in one systematic treatment the minimum amount of theoretical material necessary for a thorough understanding of electron flow and focusing in these various present-day devices. From the first page to the last this book is organized most effectively to give a thorough understanding of the basic principles governing electron beams in their application to many important design problems.

Brief Outline of Contents

Properties of Electric and Magnetic Fields • Forces and Equations of Motion • Simple Electron Motions • Some General Relations • Some Typical Special Problems • The Paraxial Ray Equation • Magnetic and Electric Lenses: Analytical and Numerical Solutions • The Effect of Thermal Velocities • Space Charge in Electron Beams • Electron Guns • Periodic Focusing Fields • About Designing Electron Beam Devices.

240 pages, illustrated $4.50

New 4th Edition

TELEVISION SIMPLIFIED



By Milton S. Kiver
Associate Instructor in Radio,
U. S. Army Air Force

Here, in a concise, up-to-the-minute handbook is the complete, practical information you need for success in present-day television. Beginning with a clear, over-all picture of the entire field, it breaks down the television receiver into its component parts and circuits, and analyzes them, step by step, showing how they are formed, the roles they play, and their operating characteristics. Hundreds of vivid illustrations bring every fact right before your eyes. You will be amazed at how simple television can become with this authoritative handbook.

618 pages, illustrated, $6.75

....FREE EXAMINATION COUPON.....

RTN 2-54

D. Van Nostrand Company, Inc.
250 Fourth Avenue, New York 3, N.Y.

Please send me an examination copy of the books or book I have checked below. After 10 days I will send you the full purchase price, plus postage, or I will return the books or book and owe nothing.

☐ THEORY and DESIGN of ELECTRON BEAMS, $4.50
☐ TELEVISION SIMPLIFIED, $6.75

Name.....

Address.....

City.....Zone.....State.....

SAVE! If you enclose full purchase price with this coupon, we will pay the postage. Same return privilege if not entirely satisfied.

The disc reproduced perfectly from the AES curve without further compensation. Surfaces were quiet. An off beat item that is highly recommended.

ADAM
GISELLE
L'Orchestre du Theatre National de L'Opera Paris conducted by Richard Blareau. London LL869, ffrr curve. Price $5.95.

For those who have been dissatisfied with the fragmentary recordings of this ballet, here is the complete score at last. Balletomanes will probably pounce on this as "Giselle" is one of the most popular works in the ballet repertory. Beautifully recorded and performed with a great deal of finesse and admirable restraint. Some of the performances I've heard of this work the orchestra sounded like they were going to a fire. I am not familiar with Mr. Blareau or his background, and the shuck is quite mute on his attainments. No matter, for he does a yeoman job in keeping things going at just the right tempi. He handles his forces very well and elicits some warm and effective playing from a better-than-average orchestra. No sensational sound on this disc, but everything is clean and in proper balance. A little touch up on the bass control was necessary with the *ffrr* curve. Surfaces were slightly noisy.

BRAHMS
SYMPHONY #3 IN F MAJOR
Vienna Philharmonic Orchestra conducted by Karl Bohm. London LL857, ffrr curve. Price $5.95.

I suppose the advent of this disc should give vent to more howls about "needless" duplication. Friends, I've just about given up on this duplication of repertoire business. As I explained in a previous column, it's just too much to expect record companies to risk capital on recordings of questionable commercial value. Don't misunderstand me. The companies would be glad to venture further into the musical unknown if they had an idea they would at least cover the cost of recording. In fact, we should be profoundly grateful for the plentitude of works which have already been recorded outside the standard repertoire. But sales figures are notoriously cold-hearted and care not a whit about musical esthetics. So the recording companies take the next best step and endeavour to so polish and refine a previously recorded work that it will find new commercial acceptance. The Brahms "3rd" here is a good case of this thinking. *London* already has this work in their catalogue by George Szell and the Concertgebouw. It is an altogether admirable recording and probably sells very well. However they felt that Szell's interpretation was basically different from that of Mr. Bohm, and reasoned that many people would want the warmer, more Viennese reading to be expected from Bohm. There is also the question of advances in recording technique, to further enhance the salability of the work. I can say that their reasoning is sound, for this *is* a better recording from the audio viewpoint and the reading *is* newly interesting, and as far as I am concerned to be preferred to the Szell. Bohm has conducted here with great intensity of feeling, a reading that is all heart and human. He never becomes maudlin or too introspective, but manages to project sincerity into the score. The sound leaves little to be desired with richly sonorous strings and much cleanliness and weight to the brass. Splendid acoustics add further to the merits of this version. All in all, I am inclined to say this is the most satisfying Brahms "3rd" now available, and a version that is going to be hard to surpass. The disc conformed perfectly to its curve and no touch up of bass or treble was necessary. Quiet surfaces.

TSCHAIKOVSKY
NUTCRACKER SUITE and SLEEPING BEAUTY BALLET
Philadelphia Orchestra conducted by Eugene Ormandy. Columbia ML 4729, NARTB curve. Price $5.95.

Speaking of duplication in the previous review we have here the same situation. Both of these works have been recorded *ad infinitum*. Can these new versions hope to compete in this tough market? The answer is a somewhat qualified yes. I say qualified because of one thing. Performance. Mr. Ormandy does a very expert job with these two charming pieces, but he (and no one else for that matter) can equal the matchless job of conducting done by Stokowski. I don't know what particular facet of Stokowski's talent is responsible for this complete mastery of these scores, but he has it and to spare. His readings are unalloyed magic. Soundwise, the Stokowski versions are good recordings, but it is here where the Ormandy disc really shines. The disc here has been given some fabulous recording, with sharp, precise percussion, clean incisive strings, and some really fine acoustical treatment. Fine tonal balance is maintained throughout. The "Sleeping Beauty" has some terrific effects in it, far beyond any previous version. A tough deal here all right. It's six of one and half dozen of another in matter of choice. It really depends on what qualities weigh most heavily with you, sound or performance, which will determine your ultimate choice.

DEBUSSY
SUITE BERGAMASQUE
RAVEL
GASPARD DE LA NUIT
Friedrich Gulda, pianist. London LL-754, ffrr curve. Price $5.95.

Here is some of the best piano sound you're likely to hear in a long time. Absolutely on pitch, with no evidence of flutter. Warm toned when needed, properly percussive on demand. The music is interesting and beautifully played. In the "Suite Bergamasque" is to be found one of the most famous of all pieces for piano, "Clair de Lune". As for the rest of the work, it can best be described as an attempt to convey a new musical idiom within the frame-

www.americanradiohistory.com

work of 18th century stylism. The Ravel piece is typical of that fabulous talent. This is piano music as brilliantly conceived as his work in other forms. The color, the subtleness, the flashing rhythm are all here. The last section of "Gaspard de la Nuit" called "Scarbo", is supposed to be one of the most technically difficult pieces ever composed for piano. You can well believe it, as Gulda exhibits his amazing dexterity. Here is a young man destined for greater things in music. He possesses an absolutely fabulous technique, comparing in this respect to the great Horowitz. Happily he is not all technique and dazzle, but can play with heart and feeling as he so clearly shows in this disc. The only quibble I have with this whole disc is the somewhat dry acoustical environment the piano was recorded in. No matter, it is still one of the best around, ranking for piano quality with the best *Westminster*. A slight roll-off in the treble was necessary with the *ffrr* curve. Good surfaces.

MASTERPIECES OF MUSIC BEFORE 1750
Danish soloists and ensembles. Haydn Society HSL 2071, NARTB curve. Price $5.95.


This is an monumental undertaking, being the first record of three to be issued in this little known area of music. Actually these recordings can be likened to "talking books" since it follows the complete text of a book of the same title published by *W. W. Norton and Co.* That is, at least the musical pieces contained in the book. Let it be understood that this is certainly not hi-fi demonstration music. The recording *is* high fidelity, the soloists and choruses and the various instruments come through with startling clarity, quite wide range and distortion free. But the musical material does not lend itself to flashy effects if that's what you are after. This is music for the serious student, one who would trace the ancestry of much of our present works. The compilation of this material represents a fantastic amount of work and much credit should be given the researchers and to the Haydn Society for venturing into this unknown and formidable (sales-wise) era of music. It would be interesting indeed to sit down with the book and follow with this disc when the text called for the music. A new departure in learning to say the least! There is much of this music that any music lover will appreciate. If you can overcome a common tendency to consider this type of music "dry", there is much interesting listening here.

—30—

Visit Us
At The West Coast
AUDIO FAIR
February 4-5-6
in Los Angeles, Calif.



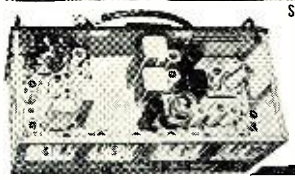FOLLOW ARROW FOR BIGGEST STOCK AT LOWEST PRICES
• RADAR—TRANSMITTERS
• RECEIVERS — TUBES — PARTS



Sensational buy!
UHF TRANSMITTER-RECEIVER
Frequency range 415-420 MC. Receiver uses 13 tubes. 5 Stages of 30 MC. IF amplifier. With schematic. Less dynamotor and tubes. Excellent condition. Never before offered at this money-saving price! $5.95



C.A.P. SPECIAL BC-625 VHF TRANSMITTER
Freq. range 100-156 MC. With modulation section and speech amplifier. Less tubes & crystals, with conversion dope. **$9.95**
Used, good condition. See Nov. 53 C. Q.



UHF Transmitter
450-710 MC. Tunable Transmitter. 10 W. output. Two 368-type tubes as push-pull oscillators. Wide band video amplifier. Less tubes. with schematic. Excellent condition... **$8.95**




INTERPHONE AMPLIFIER BC-709-B
A 2-position single stage audio amplifier. Uses 1 tube and operates from self-contained batteries. With Instruction Manual and Schematic. NEW (less batteries)..... **$3.95**

R-28/ARC-5 RECEIVER
100-156 MC. With tubes. Excel. cond.....$45.00

MOTOROLA MODEL TR 20-18 MOBILE 2-WAY RADIO. Used condition.....$150.00

RADAR TEST EQUIPMENT
TS-3, TS-12, TS-13, TS-15, TS-33, TS-34, TS-35, TS-36, TS-45APM3.

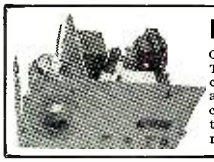SCR-283 TRANSMITTER-RECEIVER. Complete with dynamotor and tubes. 40, 80 meter. F.B. for mobile. NEW with service manual.....$24.50



R.F. Modulator
Complete Tunable 205 MC. Test Set. With 110 V. 60 cps. power supply. 3-stage audio amplifier. Terrific chassis for experimentation. With schematic. like new. **$9.95**

Monthly Specials!

ID6/APN4



Made to operate in conjunction with Radio Receiver R-9( )/APN-4. Unit includes 19 tubes, one 5" scope tube, crystal controlled standard oscillator, sweep circuits, marker pulses. Excellent cond. **$42.50**
Also available: 1D6A. 1D6B. Write for quotations.

BC-604 30 W. FM TRANSMITTER. For 20-27 MC. band. Ideal for 10-11 meters. Complete with tubes, temperature controlled crystal oven and technical manual with all instructions for BC-603 and BC-604. Less dynamotor and crystals. Excel. cond. **$12.95**

DYNAMOTOR SPECIAL: 9 V. input. Output 450 V. 75 mils. With extended shaft and drive gear on one end. New. $7.95
TA-12 TRANSMITTER. 50 W. Excellent cond..$29.95
MP-28 POWER SUPPLY. Excellent cond.....$14.95

COMMAND EQUIPMENT (SCR-274N)

		Used	New
BC-442	ANTENNA RELAY. Less cond.	$1.95	
BC-451	TRANSMITTER CONTROL BOX		$1.50
BC-450	3-RECEIVER REMOTE CONTROL BOX		2.95
MC-215	MECHANICAL DRIVE SHAFT. Per length		2.95
BC-496	2-POSITION RECEIVER CONTROL BOX		2.95
BC-454	RECEIVER. 3-6 MC. With tubes	12.95	
BC-455	6-9 MC RECEIVER. With tubes	9.95	14.95
BC-457	TRANSMITTER. 4-5.3 MC. With tubes	9.95	
BC-458	TRANSMITTER. 5.3-7 MC. With tubes	$9.95	
MC-211	90° ANGLE COUPLING UNIT.		$0.95
FT-234	MOUNTING RACK for single transmitter	2.95	3.50
FT-226	MOUNTING RACK for 2 Command Xmtrs.		3.95
FT-221	MOUNTING PLATE for FT-220		1.50
FT-220	MOUNTING RACK for 3 receivers	2.25	3.95
FT-225	MOUNTING PLATE for BC-456		2.25
BC-456	MODULATOR. For SCR-274.. Complete set of 4 tubes for transmitter	5.75	1.25

Miscellaneous Specials!

HAVE YOU ANY NEW OR USED RADIO GEAR TO SELL? FOLLOW ARROW FOR TOP PRICES!

H-16U HEADSET. 8,000 ohms.....$3.95
HS-18 HEADSET. New 2.45
HS-23 HEADSET. High imp. New..... 4.95
HS-30 HEADSET. Featherweight type. Low imp. NEW.....$2.49 USED..... 1.49
HS-33 HEADSET. Low imp. New..... 5.50
HS-38 HEADSET. USED, excel. cond 1.49
NEW 3.50
T-48 DESK STAND MIKE. New..... 4.95
LIP MIKE. Navy type. New..... .98
MP-22 MOBILE ANTENNA. MOUNTING RACK. Comp. with hardware. Per Pair $4.95. Ea. 2.95
TU-17 TUNING UNIT. (2-3 MC.) For BC-223 Xmtr. Used 2.95
TU-25 TUNING UNIT. (3.5-5.2 MC.) For BC-223 Xmtr. Used 2.95
I-70 "S" TUNING METER. NEW..... 1.49
WOBULATOR. See p. 43 Dec. '51 RADIO NEWS 5.95
BC-1023 75 MC. MARKER BEACON RECEIVER. Complete with tubes, mtg. rack, NEW..... 10.95

PE-125 POWER SUPPLY: Operates on 12 or 24 v. battery. NEW $17.95
CD-307 EXTENSION CORD. For HS-23-33. NEW .95
RS-38 MIKE. Excellent cond..... 3.95
SCR-625 MINE DETECTOR. New.....59.50
T-9 MODULATION TRANSFORMER. For BC-610 transmitter. New 34.50
TELEPHONE REPEATER AMPLIFIERS:
EE-99. New, with tubes 17.95
EE-89. New 12.95
FL-8 RANGE FILTER..... 1.95
PL-68 MIKE PLUG. New..... .79
IN-4A L/R TUNING METER. Used..... 3.95
FL-5 RANGE FILTER..... .95
TS-10 SOUND POWERED HAND SET—Used, excel. cond. Per Pair..... 14.50
PE-55 DYNAMOTOR 12 V input. 500 VDC @ 200 mils output. New..... 24.50
FIELD TELEPHONE. EE-8. Complete BRAND NEW. SPECIAL ONLY..... 27.50
DC OVERLOAD RELAY. West. 0.2-1.0 amps.... 6.50
234-258 MC RECEIVER..... 17.95

CCT-52232 NAVY COMMAND TRANSMITTER
2.1-3 MC. New, with tubes.....$14.95
250 TL TUBE.....Ea. $9.95 Per Pair $17.00

INDUSTRIAL CORPORATIONS
We carry one of the most complete stocks in U. S. of Military Electronic Equipment, Test Equipment, and Aircraft Electronics. Call or write for NEW catalogue.

$5.00 MINIMUM ORDER ACCEPTED. All items subject to prior sale. All shipments F.O.B. warehouse. Calif. residents add tax with remittance. 20% deposit required. Please specify shipping instructions with order.
EQUIPMENT WANTED! Highest prices paid for all types of Electronic Gear!


ARROW SALES, INC.
Cable Address: ARROWSALES POplar 5-1810
Mailing Address: P. O. Box 3878-R, N. Hollywood, Calif.
Office-Warehouse: 7460 Varna Ave., N. Hollywood, Calif.

www.americanradiohistory.com

REAL SAVINGS!
AT PART-MART

WILLIAMSON CIRCUIT

AMPLIFIER KIT

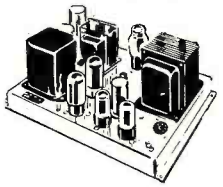


Uses famous Williamson Circuit with unique modifications for true HI-FI reproduction at increased power output. Only top-quality products are used . . . specially wound, famous-make HI-FI audio output transformer . . . ruggedly constructed power transformer. Power output 15 Watts undistorted. Output imp.—4-8-16 ohms. Hi-imp. input for xtal pickup, preamp, tuner. Freq. response at 5 Watts ± 1 db.—8-80,000 cps. Furnished complete with punched chassis, transformers, tubes and all other components. Full, detailed wiring and assembly instructions. DIM.: 9"x12"x6½". SHIPPING WT.: 28 lbs. STOCK NO. L114. **$48.95 EA.**

4-CHANNEL PREAMP KIT

Designed for above amplifier but can be used with any HI-FI equipment. Selector switch for FM-AM or TV tuner, xtal or reluctance type pickup, tape or wire recorder, or other signal source. 3-pos. equalizer switch in high gain input circuit permits selection of turnover and roll-off characteristics to match most types of recordings. 2 independent, continuous controls provide full Base and Treble boost and attenuation. Power obtained from main amplifier. AC outlet on chassis permits main amplifier and associated equipment control by master switch. Complete with punched chassis (with pictorial diagram), all components, tubes, cabinet, detailed instructions. DIM.: 10¾"x4"x4". SHIPPING WT.: 5 lbs. STOCK NO. L115. **$19.55 EA.**

STANDARD COIL

CASCODE TUNER

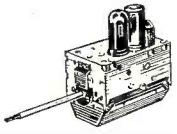


New low price on the most popular front end tuner in the Industry. Uses Cascode R. F. amplifier and dual-triode mixer-oscillator. 25.75 PIX IF and 21.25 mc. sound. Use with either "split-sound" or intercarrier as desired. Covers all channels from 2-13. Uses easily interchangeable coils on strips which may be later used for UHF work. Each channel has individual oscillator adjustment screw for front end alignment of picture brilliance, definition and sound. Balanced 300-ohm input. 3½" concentric control shafts for channel selection and fine tuning. Cascode model supplied with 6BK7/6BQ7 and 6J6 tubes. DIM: 4⅝"x3¼"x6¼". SHIPPING WT.: 5 lbs. STOCK NO. L117. **$17.88 EA.**

STANDARD COIL PENTODE TUNER


Front End as above but with Pentode RF amplifier, complete with 6CB6/6BC5 and 6J6 tubes. SHIPPING WT.: 5 lbs. NO. L118. **$18.88 EA.**

PHONO AMPLIFIER

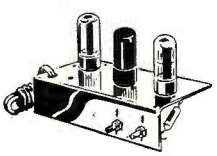

Low priced, high quality, complete kit for 2 Watt phonograph amplifier equipped with variable tone control, separate volume control. Has connections for phonomotor. Uses 50L6, 12SQ7 and 35Z5 rectifier tubes. For 110V AC-DC operation. Kit includes punched chassis, line cord and plug, all parts but less tubes. SHIPPING WT.: 3 lbs. STOCK NO. L119. LESS TUBES **$3.19 EA.**

MALLORY INDUCTUNER

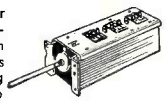

Way below wholesale cost for this popular 3-gang tuning device! For replacement or in own designs for TV and FM receivers and boosters. Continuous tuning from 52-120 mc and 175-216 mc with 4 turns of shaft. Size, 4 1/16"x 2⅛". Shaft length, 3". SHIPPING WT.: 3 lbs. STOCK NO. L108. **$2.49 EACH** LOTS OF 3 **$2.19 EACH**

12" P.M. SPEAKER



A quality speaker mode by R.C.A. for use in the finest sets. Alnico V centerless ground magnet. Seamless cone. Extended Frequency Range. Voice coil 3.2 Ohms. Maximum power output 10 Watts. Fresh stock. SHIPPING WT. 4 lbs. STOCK NO. L106. **$3.49 EACH** LOTS OF 3 **$3.19 EA.**

Write for Additional Listings

INCLUDE POSTAGE—EXCESS PROMPTLY RETURNED

TERMS: F.O.B., N.Y.C.—MIN. ORDER $3.00—25% Deposit on C.O.D. Orders. SAVE C.O.D. CHARGES—REMIT IN FULL PLUS POSTAGE. Excess Promptly Returned. SUBJECT PRIOR SALE.

PART-MART
ROCKVILLE CENTER L. I., N. Y.

Music Probe

(*Continued from page 61*)

the volume control. (This provides a "ground" for the crystal detector and keeps hum under control. If the TV set is an a.c-d.c. type, there should be an isolation transformer in the power lead to prevent accidental short—or you should test to make certain that the chassis is on the ground side of the line, of course.)

Touching the end of the probe to the "high" end of the volume control should yield a good signal—with the somewhat strange situation of the TV set playing the sound from an AM station while going merrily on with the picture from the TV station.

You can probably tell at once if the audio end is OK—even if there is nothing on but a soap opera. However, once the AM station plays a little music, you will be able to tell for certain. If the sound is still bad, you know that the trouble is in the TV audio circuits and won't waste time chasing rainbows in the front end of the video set.

Likewise, moving the grid to the final output tube will indicate (by fall-off in volume) if the first audio stage is amplifying.

In an AM set, the testing technique is similar, of course. You can start with the volume control, and work your way to the grid of the output stage.

Signal tracking through the video amplifier stages is just as fast as audio checking on a TV set. Applying the probe to the grid of the first video amplifier tube will place a strong, and highly unusual, pattern on the picture tube. This pattern is difficult to describe—but *quite* different from anything ordinarily encountered in television servicing, so once you have seen it you will remember it. And when you *don't* see it, anywhere along the video tube circuit right down to the picture tube, chances are you have the trouble cornered.

So much for *using* the probe—building it takes a little longer, but not much. The photographs are just about self-explanatory. The parts are assembled, and soldered together. Then the unit is "tuned" to the nearest AM (standard broadcast) set in the area—the station which can be depended upon to develop a good signal. The tuning is accomplished by sliding the core of the coil in and out, and cementing it in place at the proper point. (In the preliminary tune-up, the test lead can be connected to an antenna and the clip on the probe to a ground. Then a pair of headphones connected between the prod and ground will provide the signal.)

C_1, parallel with the coil, is needed to tune the coil if the broadcast station is at the low end of the dial—in fact, a larger condenser, up to 250 $\mu\mu$fd. may be needed. For a station at the high end, above 1200 kc. or so, it may be possible to omit the condenser.

Once everything is in working order, the "works" is stuffed into a plastic case from a small penlite flashlight. You may have to modify the physical layout somewhat to fit the particular flashlight you buy.—30—

Headphone Radio

(*Continued from page 42*)

order to compensate for the loading effect of the grid on the resonant circuit. It should not be supposed, however, that the same results can be obtained with an ordinary coil and regeneration. In the latter case, a much longer antenna, together with panel controllable regeneration, still gives inferior performance. The ferrite core of L_1 is adjusted in order to establish the optimum amount of feedback. It should be possible to make the receiver oscillate by means of this adjustment. Oscillation is indicated by whistles as C_2 is rotated through its range. Each whistle is a heterodyne, or beat frequency, between a radio station and the receiver oscillation frequency. This mode of operation should be obtained when the brass adjusting screw has its greatest length protruding from the coil because the core will then be in a position resulting in the highest mutual induction between the feedback coil and the resonant circuit. The screw should be turned slowly clockwise until there is no longer evidence of oscillation for any setting of the tuning condenser, C_2. It is possible to obtain peppy performance with the feedback adjusted a comfortable margin below the point of oscillation. The foregoing adjustment must be made with a four foot vertical antenna. If oscillation cannot be obtained, the connections to L_1 should be reversed.

For very weak or distant stations, the antenna can be made a little longer; conversely, if one is close to powerful stations, it can be shortened. In general, the length will be between three and five feet. There is no advantage in lengthening the antenna much beyond five feet because the "*Q*" of the resonant circuit will be degraded and the advantages of the ferrite core coil will be lost. —30—

460 MC. LICENSE

THE Carey Division of Swan Rubber Company has received the first license granted by the FCC permitting operation of a point-to-point two-way radio system in the 460 mc. band.

The frequency assigned is 460.7 mc. in the u.h.f. portion of the Citizens Radio Service band.

Two Motorola 20-watt, local control desk-top consoles are used at each of the company's two plants. A directional 24-element yagi antenna at one plant beams the signal to its counterpart at the other plant.

The system is said to speed communications between the two plants and to eliminate telephone tie-ups. —30—

www.americanradiohistory.com

Hi-Fi Speakers

(*Continued from page 73*)

In the case of the high-frequency unit of a "Duo Cone" loudspeaker, the nonlinear distortion due to the suspension system was minimized by making the stiffness of the space behind the cone the controlling acoustical impedance. For example, the resonance of the high-frequency unit without the back enclosure occurs at 750 cycles. With the back enclosure as used in the "Duo Cone" speaker, the resonant frequency is 1500 cycles. Thus, the cavity behind the cone becomes the controlling acoustical impedance involving acoustical capacitance elements. The acoustical capacitance of the cavity is linear and, therefore, does not introduce distortion.

Employing these expedients, the nonlinear distortion in the Type LC-1A is very low, as shown by the characteristics of Fig. 18.

Transient Response[6]*:* Since all speech and music is in a continuous state of change, it is, of course, of a transient character. Therefore, a high-fidelity sound reproducing system must be capable of reproducing these rapid changes without any appreciable deviation.

One of the common methods for testing the transient response of a loudspeaker is observing the response to a tone burst. A tone burst is a single frequency, sine wave signal of short duration, having a rectangular envelope. The duration of the signal may vary from 50 to 500 milliseconds, depending upon the frequency. The rectangular envelope characteristic means that a tone burst consists of a signal of practically instantaneous rise and decay periods. A deviation from the rectangular envelope depicts the transient response of the loudspeaker. The maintenance of a rectangular envelope, that is, the almost instantaneous rise and decay of the tone burst, is a very severe test. Therefore, any loudspeaker passing this test will handle any transients encountered in speech and music without distortion. From the shape of the envelope of the tone burst emitted by the loudspeaker, it is possible to correlate the shape with the response frequency characteristic. For example, if there is a peak in the response frequency characteristic, some time will be required for the output to build up to the steady-state value after the electrical input has been applied, and some time will be required for the output to decay after the electrical input has been stopped. If there is a dip in the response frequency characteristic, there will be a rapid build up in the output after the electrical input has been applied; then this is followed by a very low, steady-state value and then another rapid rise in the output when the electrical input has been stopped. From the foregoing it will be seen that the growth and

You can **SEE** *the difference...*
HEAR *the difference*
in the ***NEW***
BRILLANTE



BRILLANTE—Genuine mahogany—Model HF 100 M—Complete—Enclosure and Speaker —$164.50. Blonde Korina Model HF 100 B Complete—$174.50

A NEW HIGH IN HIGH FIDELITY BY **utah**

SEE *the difference.....* **STYLING**—A cabinet designed by Maurice—with simple, modern-classical lines that will smartly blend in and grace any decor. The new Brillante will be admired by everyone.

BEAUTY—Glowing with the splendor and lustre of fine woods—hand rubbed to a rich patina of fine furniture—the new Brillante—in either genuine honduras mahogany or blonde korina—is truly a masterpiece of woodworking art.

HEAR *the difference.....* **PERFORMANCE**—An enclosure and high fidelity speaker system designed as a unit that reproduces smooth, fundamental bass and bright, clean highs—every nuance of tone—from the softest pianissimo to thunderous fortissimo.

QUALITY—The new Brillante marks an epoch in design and engineering. Produced by Utah—a pioneer and leader for over 30 years in the field of sound engineering—the name Utah assures the finest quality in design, engineering, production and performance. Quality is built right in. It is right—because it is built right by Utah.

Write today for complete details

utah RADIO PRODUCTS CO., INC.
1350 MONROE ST., HUNTINGTON, IND.

HELP WANTED!

This established radio & television manufacturing firm in Western New York has openings for:

Test Engineers	Trouble Shooters
Technicians	Aligners


Applications should contain details of past experience. Write to

Personnel Manager, H. E. Dudley

STROMBERG-CARLSON COMPANY, Rochester 3, New York

www.americanradiohistory.com

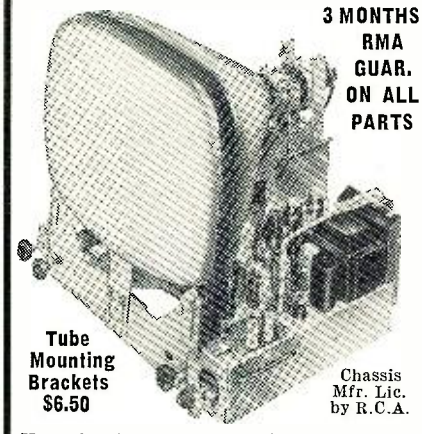AIREX'S 1954 Co-Channel 630 FA-2A with Genuine FM Armstrong Sound System



3 MONTHS RMA GUAR. ON ALL PARTS

Tube Mounting Brackets $6.50

Chassis Mfr. Lic. by R.C.A.

Here is the most powerful fringe area chassis on the market today . . . the one TV engineers and servicemen are buying for themselves. Clear, sharp, exceptional reception up to 200 miles.

CHECK THESE EXCLUSIVE FEATURES

• 10 WATT push-pull audio output. Frequency range from 40 to 12,000 cycles • 3 position fringe area switch • Delayed gated AGC system • Standard Coil Cascode Tuner prevents radiation • Retrace Blanking Circuit allows you to raise the brightness without the annoying vertical retrace lines • Heavy duty front focus control • Automatic gain control potentiometer allows you to adjust the threshold sensitivity as low as 4 microvolts & still keep the full 4 MC band width • Improved sync amplifier • Improved automatic brightness control • Set aligned for 21.9 MC. New Ham band will not interfere • Improved fused high voltage power supply gives full 14.5 KV under load. Will handle all picture tubes up to 24 inch with full sweep • Improved video amplifier has a gain of 40 • All moulded plastic condensers give long life & trouble-free operation • Easily adapted to new UHF stations in 2 minutes by just changing a strip in the tuner • Extra heavy duty power transformer with large safety factor • 6CB6 tubes in Video IF to give full gain • Extra filtering in power supply for hum & ripple-free operation • Phono Connection & switch on chassis allows you to play your phonograph or tuner through the built-in 10 watt hi-fidelity amplifier • Extra heavy duty focus coil, which runs cool • Full focus cosine yoke.

THE ONLY CHASSIS WITH 10 WATT PUSH-PULL AUDIO OUTPUT AT

Fed. Tax Included **$169.95** Less C.R. Tube and Brackets

Complete with 12" ROLA Hi-Fi Speaker
With UHF 83 Channel Converter—$199.95
Detailed Service Manual & Schematic—$1

TV PICTURE TUBE SALE

Standard Brands. Factory New. Guar. 1 year.

- 17" Tube.....$27.95
- 20" Tube.....$34.95
- 21" Tube.....$39.95
- 24" Tube (Guar. 6 Mos.)..$79.95
- 27" Tube.....$79.95
- Ring and Sleeve for 24".....$ 7.50

630 CHASSIS FOR 24" & 27" RECT. OPERATION PRICE $189.95
Not push pull audio

TV GOLD PLASTIC MASKS

16" and 17".....$ 4.95
20" and 21".....$ 7.95
24" $14.95

UHF SLUGS—$7.95

BARGAIN CABINET BUY

Beautiful mahogany consolette cabinet cut for 630 FA-2A Chassis. Complete with mask, glass & tube mounting brackets.. **$49.95**
In Blond.....$59.95

Send for complete cabinet brochure

Send post card to be put on FREE Monthly Special Mailing List

All merchandise brand new, factory fresh, guaranteed. Mail & phone orders filled upon receipt of certified check or money order for $25 as deposit on TV chassis. 20% on other items. Balance C.O.D., F.O.B. N. Y. Prices & specifications subject to change without notice. NO FED. TAXES TO PAY.

AIREX RADIO CORP.

SHOWROOM: 171 Washington St., N. Y. 7 Gramercy 7-9245
MAIL ORDER: 400 Lafayette St., N. Y. 3


decay characteristics of speech and music will not be reproduced unless the system exhibits good response to transients. In addition, faithful transient response frequency characteristics of the loudspeakers described herein are smooth. The tone burst tests of these loudspeakers have shown that the shape of the tone burst is faithfully reproduced throughout the frequency range of the loudspeakers. Therefore, these loudspeakers will reproduce the growth and decay characteristics of speech and music.

Sensitivity: During the past decade, considerable emphasis has been placed upon high sensitivity, with little regard for directivity and distortion. The reason for this state of affairs is that high sensitivity is easily demonstrated and is more dramatic in a quick test than the degradation of quality due to distortion and sharp directivity. As a consequence, smooth response, broad directivity, and low distortion have been sacrificed for sensitivity. For example, a loudspeaker with a high order of distortion and a narrow directivity pattern will sound louder than one with low distortion and a broad directivity pattern. Furthermore, the impression is often conveyed that the loudspeaker with the highest sensitivity is the superior one. This is erroneous because a careful consideration will show that a more uniform directivity coupled with lower distortion at the sacrifice of sensitivity will produce a superior loudspeaker. It is after very careful tests are made, that the more important characteristics of low distortion and uniform and broad directivity are realized.

In a direct radiator dynamic loudspeaker, with the following factors fixed, namely; the cone diameter, the amount of magnet material, and the frequency, the only remaining parameter that involves the efficiency in a maximized design is the mass of the voice coil and the cone. In typical loudspeakers, a reduction in mass of the cone of two to one will result in a gain in efficiency of three decibels. The heavier cone in this case will have a stiffness of eight times, a yield point of more than two times. Therefore, it will handle at least four times as much input power as the lighter cone for the same distortion. For the same distortion, the heavier cone will deliver at least two times as much sound power output and the distortion will be much less than from the lighter cone. Thus it will be seen that there is nothing magic about obtaining increased efficiency in a loudspeaker at the expense of nonlinear distortion.

When comparing loudspeakers by listening tests, the observation point is always on or near the axis. However, in the home, the listening position in the room may be almost anywhere. Under these conditions it is important that the loudspeaker cover almost 180 degrees in order that there be no frequency discrimination due to

COMPACT • INEXPENSIVE

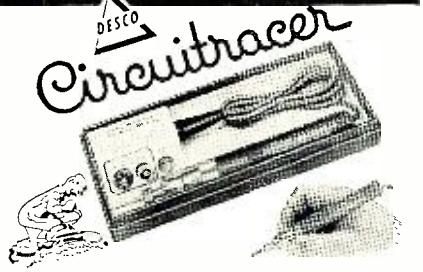

Tracks 'em down dead or alive!

Amazing, new, indispensable electrical tester takes guess-work out of electrical troubleshooting. Signal light in tip at point of contact assures fast, accurate results. Popular, practical Desco Circuitracer . . . DEVELOPED FOR THE SERVICE MAN! Can be used to quickly locate grounds, opens and shorts in both dead and live circuits, ac or dc. Check these added features: ✔ Tests tube filament; plates, screens; vibrators and output voltages, relays, switches, fuses, controls. ✔ Tests condition of wiring and devices in all types of electrical systems, with power on or off.

Rugged, yet conveniently small. Weighs only 2½ oz. ONLY $3.95. Money-back guarantee. Order yours TODAY. (Jobber inquiries invited.)

DESCO MFG. CO.
605 E. WALNUT, PASADENA 1, CALIF.

EASY TO LEARN CODE



It is easy to learn or increase speed with an Instructograph Code Teacher. Affords the quickest and most practical method yet developed. For beginners or advanced students. Available tapes from beginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready—no QRM.

ENDORSED BY THOUSANDS!

The Instructograph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the Instructograph System. Write today for convenient rental and purchase plans.

INSTRUCTOGRAPH COMPANY
4711 SHERIDAN ROAD, CHICAGO 40, ILLINOIS

CONTACT SPRINGS FOR ORGAN KEY BOARDS

$.05 EACH WITH HARDWARE

Send 3c Stamp for Sample and Flyer on Other Electro Mechanical Equipment.

SOUNDTRONICS LAB
632 Arch Street Philadelphia, Pa.

HI-FI AUDIO RESISTORS

Low-noise. Deposited. 1% guaranteed tolerance, Brand new, Beautiful appearance, gold markings. Enough resistors for Williamson, or several Preamps. Kit: 2-50K 2W, 2-20K 1W, 1-47K 1W, 2-470K ½W, 2-100K ½W. Entire kit only $4.39 P.P. Money back guarantee.

SOUTHERN ENGINEERING
Dayton Pike Rt. 5 Chattanooga 5, Tennessee

FOR SALE
30,000 5BP1
5" Cathode Ray Tubes.
Other large quantities of various tubes available
LIBERTY ELECTRONICS, INC.
135 Liberty Street, New York 7, N. Y.
Phone: WOrth 4-8262

www.americanradiohistory.com

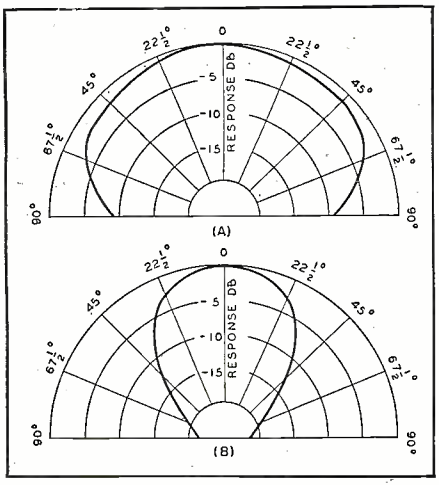


Fig. 19. (A) Broad directivity pattern, and (B) a narrow directivity pattern.

the directivity pattern. Therefore, listening tests on the axis alone are unrealistic. To show how the directivity affects the sensitivity on the axis, a comparison will be made of two loudspeakers with the same efficiency but with different directivity patterns, as shown in Fig. 19. The sensitivity on the axis of the loudspeaker with the narrow directivity pattern will be approximately six decibels above the one with the broad directivity pattern. The loudspeaker with the broad directivity pattern will cover the entire room, if it is placed in the normal location along a wall. However, in the case of the loudspeaker with the narrow directivity pattern, only a fraction of the room can be covered without frequency discrimination.


For home and other small room sound reproduction, high sensitivity is not a requirement because the power available from the amplifier is more than adequate to obtain satisfactory sound levels.[2] For example the loudspeakers described in this article will deliver a sound level of 80 db in the average living room for an input of .05 watt. Most amplifiers used in high-fidelity radio receivers and phonographs have an output of at least 5 watts. A 5 watt input to these loudspeakers will produce a level of 100 decibels. This is the peak level[8] of a full symphony orchestra, in the best seat in an orchestral hall. Furthermore, the loudspeaker with the heavier cone and lower sensitivity, used with conventional amplifiers, will actually deliver more sound power before it overloads than a loudspeaker with a lightweight cone. This is due to a loudspeaker with a light cone overloading at a fraction of the input of one with a heavy cone. Therefore, smooth response, low distortion, and a broad directivity pattern are more desirable than high sensitivity, because high sensitivity is of no practical value if it is obtained at the expense of low distortion and a broad directivity pattern.

REFERENCES

1. *Olson, H. F. & Preston, John: RCA Review, Vol. 7, No. 2, 1946, page 155.*

THE TEST OF TIME

Has proven ROHN TOWERS *Superior!*

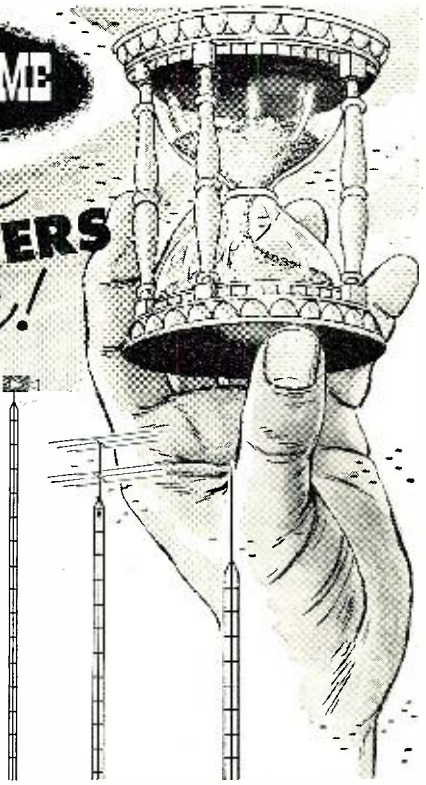

IN CONSTRUCTION

Rohn Towers are built of heavy duty tubular steel electrically welded throughout by skilled workmen exactly to specifications. Proof of Rohn construction lies in the fact that thousands of towers have been sold in the past several years and have successfully withstood the rigors of *time* in all *climates* and under the *severest of conditions!*


IN PERFORMANCE

Rohn Towers assure you of trouble-free performance and once installed give unquestioned satisfaction year in and year out! You are free of complaints because over the years Rohn Towers have *proved* themselves from the serviceman, dealer and customer point of view!

IN SALES

Sales acceptance has been phenomenal — thousands have been sold coast-to-coast — and the design has been one which has withstood every test known! Why "experiment" with an unproved tower design when you can *sell* Rohn?

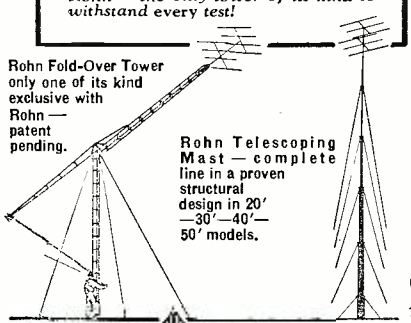So we ask you, "Why take chances with an untried tower? Be sure — sell Rohn — the only tower of its kind to withstand every test!



3 Self Supporting Rohn Towers To Fit Your Every Need

The No. 5 — The self-supporting tower for use up to 40', or guyed to 80'. An economical, yet sturdy, permanent tower!

The No. 10 — The standard 12' design that is self-supporting to 50' and can be installed to 120' when guyed!

The No. 20 — The heavy duty Rohn Tower, ideal for communication and where great height is required — self-supporting to 60', or guyed to 150'!

All Rohn Towers are in 10' sections — easily erected, transported and stored!

A COMPLETE LINE OF TOWER ACCESSORIES AND HARDWARE

A full line of Superior Design Tower accessories is available including guying brackets, house brackets, wall mounts for towers and masts, special tower bases such as peak and flat roof mounts, etc.

Contact your Rohn authorized representative or your distributor for FREE CATALOG or write . . .

ROHN **MANUFACTURING CO.**
DEPT. RTN 116 LIMESTONE BELLEVUE
PEORIA, ILL.

TUBES — ***RCA, G. E., SYLVANIA ONLY AT TREMENDOUS SAVINGS OVER REGULAR WHOLESALE***

OTHER TUBES AVAILABLE AT SAME LOW, LOW PRICES

Latest Code Dates • Boxed • Fully RTMA Guaranteed

0Z4	.62	6AL5	.63	6CB6	.76	12AV7	1.13
1B3	.95	6AQ5	.76	6CD6	1.98	12BA6	.73
1X2	1.06	6AU6	.67	6J6	.92	12BE6	.78
5U4	.63	6AV6	.60	6K6	.65	12BH7	1.07
5Y3	.48	6BA6	.71	6SN7	.85	12SA7	.80
6AB4	.80	6BG6	1.98	6S4	.73	12SK7	.77
6AC7	1.25	6BK7	1.28	6V6GT	.75	12SQ7	.67
6AG5	.83	6BQ6	1.42	6W4	.70	35W4	.49
6AH6	1.40	6BQ7	1.42	12AT7	1.05	35Z5	.51
6AK5	1.30	6BZ7	1.52	12AU7	.85	50L6	.75

Brand New Pix Tubes Full One Year Guarantee

	With Old Tube		With Old Tube
10BP4	10.50	10.00	16RP4 18.50	16.00
12LP4	12.50	12.00	17BP4 19.50	17.00
12LP4A	13.50	12.00	17CP4 20.00	17.00
16AP4	18.00	16.00	19AP4 24.00	19.00
16AP4A	23.00	16.00	19AP4A 23.00	19.00
16DP4/A	17.50	16.00	20CP4 25.00	20.00
16GP4	19.50	16.00	21EP4 27.00	21.00

STUART ELECTRONIC DISTRIBUTORS 149-09 Union Turnpike Flushing 67, N. Y.
Dept.—R12 **Minimum Order $10.00** **OLympia 8-3553, 4352**
TERMS: 25% Check or Money Order, Balance C.O.D., F.O.B. New York. Satisfaction Guaranteed.

www.americanradiohistory.com

BUILD 15 RADIOS AT HOME

With the New Improved 1954 Progressive Radio "EDU-KIT"

ONLY $19.95

NOW INCLUDES

SIGNAL TRACER and CODE OSCILLATOR



- FREE TOOLS WITH KIT
- ABSOLUTELY NO KNOWLEDGE OF RADIO NECESSARY
- NO ADDITIONAL PARTS NEEDED
- EXCELLENT BACKGROUND FOR TELEVISION
- 10-DAY MONEY-BACK GUARANTEE

WHAT THE PROGRESSIVE RADIO "EDU-KIT" OFFERS YOU

The "Edu-Kit" offers you a Home Radio Technician Course at a rock-bottom price. You will learn how to identify Radio Symbols and Diagrams; how to build radios, using regular radio schematics; how to wire and solder in a professional manner. You will learn how to operate Receivers, Transmitters, and Audio Amplifiers. You will learn how to service and trouble-shoot radios. You will learn code. You will receive training for F.C.C. license. In brief, you will receive a basic education in Radio exactly like the kind you would expect to receive in a Radio Course costing several hundred dollars.

THE KIT FOR EVERYONE

It is not necessary that you have even the slightest background in science or radio. The "Edu-Kit" is used by young and old; by radio schools and clubs; by Armed Forces personnel and veterans for training and rehabilitation. No instructor is required. Instructions are complete, simple and clear. You cannot make a mistake.

PROGRESSIVE TEACHING METHOD

The "Edu-Kit" uses the principle of "Learn by Doing." Therefore you will build radios, perform jobs, and conduct experiments to illustrate the principles which you learn. You begin by learning the function and theory of each of the radio parts. Then you build a simple radio. Gradually in a progressive manner, you will find yourself constructing more advanced multi-tube radio sets, and doing work like a professional Radio Technician. The "Edu-Kit" Instruction Books are exceedingly clear in their explanations, photographs and diagrams. These sets operate on 105-125 V. AC-DC.

The Progressive Radio "EDU-KIT" Is Complete

You will receive every part necessary to build fifteen different radio sets. Our kits contain tubes, tube sockets, chassis, variable condensers, electrolytic condensers, mica condensers, paper condensers, resistors, line cords, selenium rectifiers, tie strips, coils, hardware, tubing, etc. Tools are included, as well as an Electrical and Radio Tester. Complete, easy-to-follow instructions are provided. In addition, the "Edu-Kit" now contains lessons for servicing with the Progressive Signal Tracer, F.C.C. instructions, quizzes. The "Edu-Kit" is a complete radio course, down to the smallest detail.

TROUBLE-SHOOTING LESSONS

Trouble-shooting and servicing are included. You will be taught to recognize and repair troubles. You will build and learn to operate a professional Signal Tracer. You receive an Electrical and Radio Tester, and learn to use it for radio repairs. While you are learning in this practical way, you will be able to do many a repair job for your neighbors and friends and charge fees which will far exceed the cost of the "Edu-Kit." Our Consultation Service will help you with any technical problems which you may have.

FREE EXTRAS

• Electrical and Radio Tester • Electric Soldering Iron • Book on Television • Radio Trouble-Shooting Guide • Membership in Radio-Television Club • Consultation Service • Quizzes • Training for F.C.C. License.

Attractively Gift Packed.

MAIL TODAY Your Order Shipped Same Day Received

Send me the "Edu-Kit" with Money-back Guarantee—include All FREE extras.

☐ Check or M.O. enclosed—postage prepaid
☐ C.O.D. (U. S. Only)—I will pay postage
☐ Send further information

Outside U.S.A.—No C.O.D.'s; send check on U.S. bank or intern'tl M.O. for $19.95. Postage prepaid. "Edu-Kit" for 210-250 V. AC/DC $22.45.

NAME_____

ADDRESS_____

PROGRESSIVE "EDU-KITS" INC.

497 Union Ave., Dept. RN-27, Brooklyn 11, N.Y.

2. *Olson, H. F. & Morgan, A. R.: "A High-Quality Sound System for the Home," RADIO & TELEVISION NEWS, November, 1950.*
3. *Olson, H. F.: Audio Engineering, Vol. 34, No. 10, 1950, page 15.*
4. *——: "Elements of Acoustical Engineering," Second Edition. D. Van Nostrand Co., New York, 1943, page 47.*
5. *Olson & Pennie: RCA Review, Vol. 12, No. 1, 1951. page 35.*
6. *Olson, H. F.: Audio Engineering, Vol. 34, No. 10, 1950, page 5.*
7. *——: Audio Engineering, Vol. 34, No. 10, 1950, page 15.*
8. *Bell Laboratories Record, Vol. 12, No. 10, 1934, page 314.*

—30—

QRZ Mobile

(*Continued from page 47*)

control box duplicated at the transmitter, as they always are, and a headset connected across the extra "audio" line, complete two-way operation for test purposes may be obtained without "leap-frogging" around the car and the pedestrians who inevitably gather to watch.

The controls line up in three rows on the rig's front panel. See Fig. 1. Across the top row are the 1" plate current meter, antenna tuning, and a toggle switch for selecting oscillator or final amplifier plate currents for meter readings. The middle row has the crystal plug-in socket, final plate tuning, and the 3-position bandswitch (shown in the 20-meter position). The bottom row has the main "on-off" toggle switch (duplicated at the dashboard remote-control box and normally left in the "off" position), oscillator plate tuning, and the "transmit-receive" toggle switch (also duplicated at the dashboard and normally left in the "receive" position).

Should the rig have to be removed from the trunk for inspection or service, the job can be done in a jiffy because of the simple 2-bolt mounting employed. A plywood shelf is permanently mounted on the wall of the car trunk. Two 2½" x ¼" machine bolts are secured to the rig's bottom cover plate and two matching holes are drilled through the plywood shelf. When the rig is fully assembled with the top and bottom covers in place, the unit is set on the plywood shelf, the two machine bolts protruding from the bottom of the rig slipping into the two matching holes of the shelf. The rig is then secured with two wing nuts and lock washers. A braid conductor connected from the car body to the forward wing nut is included as an assurance of a good grounding condition between the rig and the car body. It may or may not affect performance in your installation but its inclusion is recommended. Tubes can be replaced, if necessary, in a jiffy, simply by removing the top panel of the rig's box. It is secured by four self-tapping machine screws usually supplied with the box. Please note, however, that the tubes should last indefinitely under the modest operating conditions of this transmitter.

Tuning Up

The transmitter operates satisfactorily with d.c. supply voltages of from 300 to 500 volts. The power output will depend to a large extent on the plate voltage used. For a supply voltage of 400 the power input to the 5516 r.f. final is approximately 25 watts and is consistent with extended tube life. The slider on the bleeder resistor, R_s, should be adjusted for 300 volts for proper oscillator and modulator operation. After the installation is completed and all cables and an antenna load (preferably a "dummy," for the sake of the other hams in QSO) are connected, insert the crystal in its socket and throw the main power toggle switch to "on." (A 40-meter crystal works very well for 20-meter output of the rig. The oscillator has excellent harmonic output and provides sufficient driving power for the grid of the 5516 tube so that it is always operated as a straight-through amplifier. An active 40-meter crystal, therefore, should drive the final as a straight-through amplifier even at the 10-meter bandswitch setting.)

With the bandswitch set for the desired output frequency and the oscillator tube already heated, set the "meter reading" toggle switch to read "oscillator" plate current. Next, throw the "transmit-receive" toggle switch to the "transmit" position and adjust the oscillator tuning for the sharp meter dip which indicates resonance. At resonance the current will be between 30 and 40 ma. (It is suggested that, for the sake of the tube's life, the 5516 be left out of its socket during this initial adjustment of the oscillator, and put back in its socket and the plate cap attached after the ability of the oscillator to be resonated is ascertained.) No difficulty should be encountered in resonating the oscillator if parts values and wiring are correct. You can then proceed to tune the final stage. Throw the meter toggle switch to the opposite direction and adjust the final plate tuning control for resonance. By adjusting the antenna tuning control and readjusting the final tuning control, the final meter reading can be brought to a point of loading which gives a resonant dip at 60 to 65 ma. With a 300-volt plate supply the final current will be about 55 ma. With a 500-volt supply the current should be limited to 60 ma. During the tune-up it is not necessary to have a microphone plugged in. However, in the interest of good operating practice, if a "live" antenna is used instead of a "dummy" for the tune-up, it is recommended that a frequency be selected that will not QRM other stations (don't underestimate the power of a 25-watter) and your own call sign be given at frequent intervals.

Come on and join in the fun. Spring and summer are the times for automobile-ing. Take one on your vacation and meet the guys on the way. There are local rag chews with the gang or exciting DX, all while cruising along the highway or while parked outside the market waiting, as is the usual case, for the XYL! —30—

www.americanradiohistory.com

Manufacturers' Literature

The bulletins reviewed in this section are for your convenience; unless otherwise indicated they are available to all our readers. For prompt attention write directly to the manufacturer for literature described.

RECTIFIER REPLACEMENTS

The Rectifier Division of *Sarkes Tarzian, Inc., Bloomington, Ind.* has issued a new "Selenium Rectifier Replacement Guide" which is currently available for 25 cents.

The publication is divided into two sections—one dealing with television receivers and the other with radios. Sets are listed by make and model number and the manufacturer's part number given. The *Sarkes Tarzian* replacement model number is also listed in the catalogue.

FEDERATED'S SOUND DATA

Federated Purchaser of 66 Dey Street, New York 7, N. Y. has issued a pocket-sized booklet which offers a series of audio components assembled in "packages" available at prices ranging from $100 to $250.

The booklet also lists miscellaneous components and suggested installation layouts. A copy of this booklet may be obtained by writing the company direct.

CENTRALAB DATA

Five new and revised catalogue sheets covering special types of ceramic condensers are now available from Dept. K-10, *Centralab,* 900 E. Keefe Ave., Milwaukee 1, Wisconsin.

Complete technical specifications are given for the following styles: broadcast disc units (Bulletin 42-4R), ceramic trimmers (Bulletin 42-101R), tubular trimmers (Bulletin 42-59R), feedthroughs (Bulletin 42-206), and high-accuracy units (Bulletin 42-123R).

Any or all of these bulletins are available on request.

CONVERTER CATALOGUE

Carter Motor Company, 2644 N. Maplewood Ave., Chicago 47, is now offering copies of its new catalogue which lists the company's entire line of d.c. to a.c. converters.

Known as Catalogue No. 553, the new publication includes 20 pages of electrical and mechanical specifications on the line as well as a "selector chart" for determining the right converter for the job.

For a free copy of this catalogue, write Dept. 7 of the company.

TEST EQUIPMENT


Heath Company, Benton Harbor, Michigan is now offering copies of its

If you want professional sound quality



Sound engineers know that the selection of a fine amplifier, pickup and speaker system is only part of the story; that unless the turntable is of equal quality, music reproduction must suffer. That is why they insist on such high standards for turntable performance.

do as the professionals do...

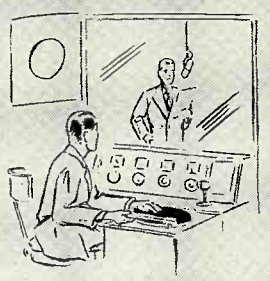

Rek-O-Kut precision turntables are made to conform to the highest standards in the professional field, and they certainly represent the finest you can use in the home. A Rek-O-Kut turntable will make all the difference in the world. The finer your present system, the more apparent the improvement will be. Whether you select the deluxe T-12H or the standard LP-743, the entire performance of your sound system will become a new and thrilling experience.

use a REK-O-KUT precision turntable



Rek-O-Kut Precision Turntables are priced from $59.50. Write for specifications and descriptive literature to Dept. J–12

The REK-O-KUT COMPANY

Manufacturers of Professional Disc Recorders and Specialized Sound Systems.

38-01 Queens Boulevard, Long Island City 1, New York

Export Division 458 Broadway, New York, U.S.A. Cables: Morhanex

In Canada: Atlas Radio Corp., Ltd., 560 King Street, W., Toronto 2B

GET INTO **ELECTRONICS**



You can enter this uncrowded, interesting field. Defense expansion, new developments demand trained specialists. Study all phases radio & electronics theory and practice: TV; FM; broadcasting; servicing; aviation, marine, police radio. 18-month course. Graduates in demand by major companies. H.S. or equivalent required. Begin Jan., March, June, Sept. Campus life. Write for catalog.


VALPARAISO TECHNICAL INSTITUTE
Dept. RD Valparaiso, Indiana

CORONA RADIO KITS

EASY TO BUILD • EDUCATIONAL
EXCELLENT RECEPTION

Broadcast Superhet Kit

$14.75

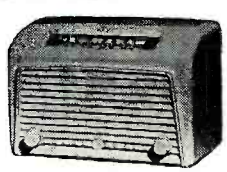

ROCKET 115K—Latest Single Band superhet circuit for ultimate in sensitive reception and tonal quality. Kit includes all necessary parts, punched chassis, attractive bakelite mahogany cabinet, built-in loop antenna, iron core IFs, big 5" Alnico V spkr.; tubes: 12SK7, 12SA7, 12SQ7, 50L6, 35Z5. Automatic vol. control, beam power output. Tunes 540 to 1700 Kc. Simple step-by-step instructions included.

Plaza 812K 2-Band AC-DC Super Kit..net $20.75
Globemaster 814K 3-Band Super Kit..net $24.75

All kits supplied less wire and solder. Please include 25% deposit with C.O.D. orders. Dept. N-2.

CORONA RADIO & TV CO.
136 LIBERTY ST., NEW YORK 6, N. Y.

www.americanradiohistory.com



12 V. DYNAMOTOR

(D. W. Thomas Engineering, Inc.) NEW! Guaranteed. Ready to use. Continuous duty ratings. Gray finish. Model 1224-2 Output 600V 200 ma. (Less base.) ... **$9.95**

Add $6.00 for base box containing starting relays & filters as shown. Shipping wt.: 11 lbs.; with base, 13 lbs.

GENERATOR ALTERNATOR SPECIAL

AC PLUS 12 OR 24 VDC

Two units in one package, each complete in itself: the removable centrifugal slip clutch and the generator-alternator. Clutch maintains armature speed of 2400 rpm for drive speeds varying between 2400 and 4200 rpm. Generator-alternator available in two models, 24 v (Navy NEA) and 12 v (Eclipse 1003-4). SPECIFY WHICH YOU WANT! Both put out 120 v, 800 cy, 1 ph, 1080 VA. DC output is 14.3 v, 30 A for 12 v model; 28.5 v, 25 A for 24 v model. Drive it from engine or electric motor. With diagram and instructions. Excellent used..... **$5.95**

(Shipping wt. 40 lbs.)

VOLTAGE REGULATOR (Carbon pile) for above. New **$2.95**

RELAYS! RELAYS! RELAYS!

Weston Sensitrol is a SPST Normally Open relay that operates directly from a photocell, thermo-couple, etc. 10 ua closes it. See Nov. ad p. 207 for further details **$12.95**

BK-7 adjustable-sensitivity SPDT, starts at ½ ma. See Nov. ad p. 207..... **$1.95**

Dual-Sensitive: Sequence switching. First contacts close at 4 ma., second at 6½ ma. See Nov. ad p. 207..... **95c**

12V Antenna Relay BK-16 DPDT, NO. 30A contacts, plus NC 5A contacts plus small NO contacts for added function **$1.75**

6V or 12V Starting Relay BK-17, SPDT, 30A intermittent. 20A continuous..... **$1.75**

115V, 60 cy SPDT 30A contacts, Normally open **$1.45**



MINIATURE 6 V. WET BATTERIES

The famous NT-6 Willard 2.4 AH, 6 volt battery. A standard for model control, etc. Plastic case, only 3⅝" long, 1 13/16" wide, 2⅜" high. Uses standard electrolyte. New. Boxed.

EA. ..**$1.49** 4 for..**$5.45**

CHARGER **$2.45**

OUNCER TRANSFORMERS, one for mike to push-pull grids, flat 30 to 15,000 CPS; other for push-pull output, tapped sec., turns 14:1. In unit for resistors, condensers, etc. BOTH FOR ONLY.....**98c**

$45.00 HI-FI HEADSET AT $7.95

Uses annular grooved plastic fibre cones with voice coils as in speakers, and padded chamois ear muffs to obtain spacing for correct acoustical load. Gives finest music reproduction, 600 ohms. Checked out with freshly laundered ear pads and long flexible fabric cord with phone tips. (Shpg. wt. 3 lbs.).**$7.95**

MODEL 27-Z TESTER

(Made in Japan)

$9.95

(Plus 25c shipping)



RANGES: AC and DC volts 0-5/25/250/500. DC MA 0-1/10/100/250. Ohms 0-10K, 100K. Black bakelite panel, metal case. Manufacturer claims extreme accuracy and our spot checks show them to be within 1%! Here is a meter to be proud of!



Pocket Model Jap. Import Multimeter

In genuine Leather carrying case

Only $11.95

(Plus 25c shipping)

RANGES: AC and DC volts 0-15/150/750, 4%, DC MA 0-150, 4%. Ohms 0-100K, 10%. In rugged black bakelite case and leather carrying case.

METER: 0-1 MA. New, 2" Rd— (Japan).....**$2.95**

13V to 9V in one volt steps: Tapped transformer, 3 amps out. Input 115 V, 60 Cy. Use for Model Railroad or heaters of surplus receiver.....**$1.89**

12-CHANNEL TV FRONT END

Famous "Silver Circle" tuner, with original factory instructions. Use for 2-meter converters, receivers, etc. The TV bargain of the year! Factory rejected for minor damage. Less tubes. **$1.95** each, 3 for **$5.00** (Shipping wt. each 3 lbs.) Tubes, shields and knobs for above.....**$1.25 set, 3 for $3.00**

ANTENNA MAST SECTIONS, MS-49, 50, 51, 52. New, original packing..... **39c**

CRYSTAL MICROPHONE GIVEAWAY!

Sensitive hearing aid capsule sealed in compact, flat container with tinned terminals. Crisp, clear, high-level output. Ideal for lapels, ties, tuck-aways. Individually tested, guaranteed.....**ONLY 98c**

G. L. ELECTRONICS, INC.

905 S. Vermont Ave., Los Angeles 6, Calif.

Minimum Order $5.00 Total, 25% Deposit Required With All Orders

All Prices F.O.B. Los Angeles, Calif. Buyers Add Sales Tax

GET ON OUR MAILING LIST

"OPEN MONDAY NITES 'TIL NINE"

SCHEMATICS—CONVERSIONS FOR SURPLUS GEAR

NEW LIST! MANY ADDITIONS!

Send stamped, self addressed envelope for List C. Add 25c for chart explaining AN nomenclature.

R. E. GOODHEART — BOX 1220 BEVERLY HILLS, CAL.

1954 *"Heathkit"* catalogue which lists the wide variety of test equipment, receivers, amateur radio gear, and amplifiers available in kit form.

This colorful new publication lists complete specifications on each item and provides full data for ordering the equipment.

"ANTENAPLEX" DATA

The Engineering Products Department, *Radio Corporation of America,* Camden, N.J., has issued a colorful 4-page brochure describing installations of its "Community Antenaplex" system.

Included are pictures and descriptions of systems installed in Pottsville, Pa., Laconia, N.H., Fayettesville, Ark., Wilkes-Barre, Pa., Graham, Texas, Carmel, Calif., and Brockway, Pa.

For a copy of this brochure, write to the Antenaplex Sales department of the company.

TV ACCESSORIES

Admiral Corporation, 3800 Cortland St., Chicago 47, Ill. is currently offering a copy of its new 20-page, two-color catalogue which lists antennas, masts and towers, tables and bases, multiple installation equipment, transmission lines, and hardware.

The new publication is being offered with distributors' imprints. For a copy of this catalogue or additional information, address your requests to the Accessories Division of the company.

ELECTROLYTIC CATALOGUE

Pyramid Electric Company, North Bergen, N. J., has recently issued a new catalogue which contains listings for almost 300 new dry electrolytics which have been added to its line.

Catalogue DE also includes listings and full information on the company's new Type TDL—a hermetically-sealed dry electrolytic in a tubular metal can which has an outer cardboard tube and 6" flexible insulated wire leads.

G-C CATALOGUE

General Cement Mfg. Co., 904 Taylor Street, Rockford, Ill., has released copies of its No. 156 catalogue which contains detailed descriptions, specifications, and prices of its complete line of radio, TV, and electronic products.

The 64-page catalogue carries a complete index for ready reference. More than 3000 items in over 150 different classifications are included.

C-D REPLACEMENTS

Cornell-Dubilier Electric Corp. of South Plainfield, N. J. has issued a comprehensive catalogue for service replacement needs covering condensers for a wide variety of applications.

The 36-page catalogue provides data on 134 replacement condensers presented in clear, concise form. The listings serve as a valuable inventory guide as well. Another feature of the new #200 D catalogue is the use of two indexes—one according to classification and the other according to type number or brand name.

A free copy of this new catalogue is available from local *C-D* distributors.

MERIT CATALOGUE

Merit Coil and Transformer Corp., 4427 North Clark St., Chicago 40, Ill. has issued a new replacement catalogue covering transformers, coils, and TV replacement components.

The 16-page catalogue gives complete specifications on the company's line including type number, list price, mounting centers, mounting types, etc. A copy of this catalogue, which replaces No. 5211, is available on request.

"MOTOROLA SERVICE NEWS"

A new monthly magazine, *"Motorola* Service News," has made its debut according to an announcement received from *Motorola Inc.,* 4545 W. Augusta Blvd., Chicago 51, Illinois.

The new house organ, published by the service department, will be sent free to service contractors and dealer and distributor technicians. The technical section features service hints, bulletins, and new circuit schematics which may be lifted out for filing.

Articles on technical subjects as well as on business news and methods, etc. are also included. The new publication is edited by Russell C. Hansen, the company's service contract manager.

TUNG-SOL MANUAL

Tung-Sol Electric Inc. of Newark 4, N. J. has announced publication of the 19th edition of its "Tube Characteristics Manual."

Over 166 pages of this manual are devoted to technical information about receiving and cathode-ray tubes. Six different colored pages are used to separate the charts, diagrams, and technical data for easy reference.

The back of the manual carries a special section which contains basic marketing information to help technicians plan local promotion programs for their own businesses.

The manual is distributed through the company's tube wholesalers.

"SOUND ADVICE"

Asco Sound Studios, 115 W. 45th Street, New York 36, N. Y. has recently released a comprehensive 148-page booklet entitled "Sound Advice," prepared by Irving Greene.

The booklet includes the latest information on high-fidelity developments, monaural systems, the binaural trend, new high-fidelity components, cabinetry, and other allied subjects.

The booklet, which measures 7" x 5½", carries on its cover a reproduction of the May 1953 cover of RADIO & TELEVISION NEWS which pictured the *Asco* "Audiomat." Although the booklet sells for 50 cents a copy, readers of this magazine may obtain a copy by sending 10 cents in coin to cover postage and handling costs.

SUN RADIO CATALOGUE

Sun Radio & Electronics Co., Inc., 650 Sixth Avenue, New York 11, New

www.americanradiohistory.com

York has recently issued an eye-catching catalogue covering audio gear of all types.

Prepared by the high-fidelity sound sales department of the company, the new catalogue features a compatibility chart of radio tuner and amplifier components, a 5000-word article on planning a high-fidelity music system, and photographs and specifications on hundreds of items of interest to audiophiles.

First distributed at the New York Audio Fair, copies of this new catalogue are now available upon request to the company.

INVENTORY CONTROL

The Tube Department of *General Electric Company,* Schenectady, N.Y. has come up with a solution to the inventory problems of users of industrial and transmitting tubes.

The answer to the problem is in the form of a new simplified record-keeping system for all required data on such tubes. The record comes in a 10" x 12" leatherette binder which includes sections for a one-year inventory, service report forms, data and prices on the tubes, a sheet describing the company's tube manuals, and an interchangeability data section.

In addition, the system includes tube life record cards for large industrial tube users, broadcasters, and telecasters. This system provides a supply of tube life record cards and a metal file cabinet for the cards.

G-E tube distributors are handling this control system.

MILLER GUIDE

J. W. Miller Company, 5917 South Main St., Los Angeles 3, California has issued a new TV replacement guide, No. 154.

This concise 20-page guide lists hundreds of video and sound i.f. transformers, ion traps, peaking coils, etc., as used in various TV sets and then lists the *Miller* equivalent part number.

In addition, the new guide carries a catalogue page on TV replacement components and another on radio replacement coils.

A copy of this publication is available without charge, on request.

HI-FI CATALOGUE

Hudson Radio & Television Corp., 48 West 48th Street, New York 36, N. Y. has released a new 56-page high-fidelity catalogue and buying guide—the most complete ever issued by the company.

Included in the catalogue are the very latest tuners, amplifiers, speakers, record changers, tape recorders, TV chassis, tubes, replacement parts and accessories, and cabinets. Specifications, photographs, and prices are given on all of these items.

The company invites readers to pick up a copy of this new publication at any one of its three salesrooms or obtain one by writing the firm direct. —30—

Only 10% Down...18 Months to Pay!

hallicrafters

I can SAVE you money... Liberal Trade-ins



Leo I. Meyerson, WØGFQ

Now it is easier than ever to buy from WRL. Pay as little as 10% down and the balance in 12 to 18 months. No red tape — we handle our own financing. GENEROUS TRADE-IN ALLOWANCE on your present equipment. We have over 600 reconditioned used items — with new factory guarantee. Send for free list. You will profit most when you deal with WRL — THE WORLD'S MOST PERSONALIZED RADIO SUPPLY HOUSE and ONE OF THE WORLD'S LARGEST DISTRIBUTORS OF AMATEUR RADIO TRANSMITTING EQUIPMENT.

S-40B RECEIVER . . . $119.95



$9.54 Per Month (12 months)

$12.00 CASH DOWN

Communication receiver with built in speaker covering 540-Kc to 44 Mc in four bands. One RF stage, 2 IF stages.

SX-88 RECEIVER . . . $599.95



$47.70 Per Month (12 months)

$60.00 CASH DOWN

$32.69 18 MONTHS

Dual Conversion Receiver 535-33.3-Kc in 6 bands. 2 RF stages, variable 6 position band width selectivity, 250 cycles to 10 Kc. 10 watt audio output. 17 tubes plus voltage regulator, ballast tube and rectifier.

HALLICRAFTERS RECEIVERS AVAILABLE FOR IMMEDIATE SHIPMENT

MODEL NUMBER	12 MONTHLY PAYMENTS	DOWN PAYMENT	CASH PRICE	MODEL NUMBER	18 MONTHLY PAYMENTS	DOWN PAYMENT	CASH PRICE
S-38C	$3.97	$ 5.00	$ 49.95	S-76	$10.90	$20.00	$199.95
S-53A	$7.95	$10.00	$ 99.95	SX-62	$19.07	$35.00	$349.95
S-72 Port	$8.74	$11.00	$109.95	SX-71	$13.62	$25.00	$249.95
S-77A	$9.54	$12.00	$119.95	HT-20XMTR	$24.50	$44.95	$449.50



FREE 1954 CATALOG

WRITE—WIRE PHONE 2-0277

Get your BIG NEW 1954 WRL CATALOG, offering the greatest selection of radio and television equipment, parts and supplies for the Novice, Experimenters, Hams and Professionals.

WORLD RADIO LABORATORIES R-2
3415-27 W. Broadway
Council Bluffs, Iowa

Please send me:

- ☐ 3' x 4' U.S. Radio Map 25c
- ☐ New Catalog
- ☐ Used Equipment List
- ☐ WRL XMTR Info
- ☐ SX-88 Info
- ☐ S-40B Info
- ☐ NEW LOG BOOK 25c

Name .....

Address .....

City ..... State.....

World Radio LABORATORIES — EVERYTHING IN RADIO — COUNCIL BLUFFS, IOWA

NEW HANDI-PACK

prevents tangling... keeps wire clean



Tuf-Guy "ten-spot"

The GUYWIRE that is spot marked every 10 feet for easy measuring.

Write Dept. RN-2 for complete FENWIRE line.

FENTON COMPANY

15 MOORE ST. • NEW YORK 4, N. Y.

FENWIRE

Sold Through Jobbers Only

www.americanradiohistory.com

FACTS YOU SHOULD KNOW ABOUT UHF CONVERTERS

Many converters on the market today are unsatisfactory in fringe and shadow areas where signal strength is low. Before you install a UHF converter in these areas you should know these facts:

Signal power loss in the preselector seriously affects picture quality. Most UHF converters use sliding-contact shorted line tuners in the preselector with a fixed power loss of 6 db. The Turner uses High Q coaxial cavity tuners with no sliding contacts. Signal power loss is cut to 3 db. The resulting low noise figure keeps picture quality high.

2 Oscillator radiation often causes interference with neighboring sets. In the Turner converter the oscillator tube socket and all associated circuits are inside the coaxial cavity, self-shielded. Removable covers provide a second shield against radiation.

3 High amplifier noise figure can further damage picture quality. The Turner converter uses a special broadband amplifier with Cascode circuit. It retains the preselector signal savings without appreciably increasing the noise figure. The Turner amplifier noise figure is only 4 db.

Whether installing converters in shadow and fringe areas, or putting one in your own home, remember . . . the Turner often means the difference between good reception and bad reception.

EXCLUSIVE TURNER FEATURES

- Higher sensitivity
- Extremely low noise figure
- Exceptional frequency stability
- Double shielding
- Hi-Q silver plated coaxial cavities
- No sliding contacts

OTHER MAJOR TURNER FEATURES

Continuous single-knob tuning. Illuminated slide-rule dial. Smaller size: 8"x6"x6". Use with UHF or combination antennas. Self powered, uses channels 5 or 6. Complete installation instructions. For 110-120 volts 50-60 cycles AC. Schematic included.

List price $49.50



In VHF fringe and shadow areas, the Turner Booster is a superior performer, too.

The TURNER Company
900 17th St., N.E., Cedar Rapids, Iowa

Gentlemen: Please send complete information on the Turner UHF Converter ☐ Turner Booster ☐

Name _____

Address _____

City _____

State _____

Export: Ad Auriema, Inc., 89 Broad St., New York 4, N. Y.
Canada: Canadian Marconi Co., Toronto, Ont. & Branches

NEW EQUIPMENT FOR THE AUDIO TECHNICIAN

MAGNETIC PORTABLE

J. C. Warren Corporation, 21 Hanse Avenue, Freeport, N.Y. has developed a compact magnetic portable recorder-playback unit, the Model 777.

The new unit weighs 22 pounds and measures 6" x 10" x 15". It takes a 5"



reel and tape speed is 1.87 inches-per-second. The motor is a d.c. reed synchronous constant speed type. Playing time is 1 full hour on each track.

The Model 777 features high impedance crystal input, a power output of 200 millwatts, frequency response from 200 to 4000 cps, flutter and wow of ½ of 1 per-cent, and distortion less than 10 per-cent. It will operate on either a.c. or self-contained batteries.

LABELING TAPE

Minnesota Mining and Manufacturing Co., 900 Fauquier St., St. Paul 6, Minn. has developed a new pressure-sensitive labeling tape which is said to make the identification of tape recordings faster and easier.

Called *"Scotch"* write-on tape No. 48, it provides a continuous roll of 40 printed labels that stick at a touch to the reels themselves. Complete with a convenient metal dispenser, the new labeling tape features a special matte



finish that can be written on with pen, pencil, ball point pen, or typewriter.

Printed on the new white tape is "Reel No.," "Date," and "Subject" together with adequate room for filling in the necessary data.

BELL AMPLIFIER

Bell Sound Systems, Inc. of Columbus, Ohio has added a moderately-priced amplifier to its line of audio components.

The Model 2199 has a 12-watt output at less than 1% distortion with a peak of 16 watts. Frequency response is rated from 20 to 20,000 cps, ± ½ db with the controls flat. There are six controls, including a seven-position selector switch with equalization for all types of records. tuner, crystal, tape, and television inputs. Outputs with impedance ratings of 4, 8, 16, and a high impedance jack for tape or disc recorders are also provided.

THREE-SPEAKER RECORDER

Webster-Chicago Corporation of Chicago, Illinois is currently marketing a new three-speaker tape recorder, the *"Webcor"* Model 2030.

The amplifier uses five tubes including a rectifier with three of the tubes being double-purpose types to provide eight-tube performance. The circuit also includes bass and treble boost during playback and bass-compensated volume control. The amplifier is



coupled to the tape speed control to provide automatic equalization for 3¾" tape speed.

The recorder incorporates two six-inch speakers and one four-inch PM type speaker. The three speakers are used to cover a wide frequency range with uniform response.

STROMBERG COMPONENTS

A new combination radio receiver and amplifier and a 15" coaxial loudspeaker have been added to the *Stromberg-Carlson Company's* "Custom 400" series of high-quality sound reproducing equipment.

The receiver-amplifier, known as the "SR-405," combines on a single chassis the company's high-quality tuner and a 10-watt amplifier. It provides radio reception on both the AM and FM bands plus amplification of the entire spectrum from 20 to 20,000 cps.

The "RF-475" fifteen-inch coaxial speaker has a 10½ pound permanent magnet, a woofer cone of special fiber, a 3" voice coil mounted on an aluminum form, and a pressure-type high-frequency tweeter which is mounted coaxially through the woofer

www.americanradiohistory.com

pole piece. A 10-element acoustic lens of non-resonant plastic transmits the highs uniformly through a 90-degree angle of coverage in all planes.

FISHER AM-FM TUNER

Fisher Radio Corporation, 45-41 Van Dam Street, Long Island City 1, N.Y. is now offering its new Model 70-RT FM-AM tuner which includes tone controls, a phonograph preamplifier,



adjustable record equalization, and a loudness control—all in a single cabinet.

The tuner uses fifteen tubes and has separate front ends for AM and FM. There is a separate d.c. supply for all audio tube filaments as well as a completely shielded and shock-mounted main and sub-chassis.

The FM section has two i.f. stages, dual limiters and a cascode r.f. stage; the AM section has two i.f. stages and one tuned r.f. stage. Audio response is uniform ± 1 db from 20 to 20,000 cps. Distortion is less than .04% for 1 volt output and .8% for 10 volts output.

The tuner has six controls on the front of the cabinet which measures 14¾" wide, 8½" high, and 9¼" deep.

AUTOMOTIVE SOUND

A complete sound amplifying system for buses, trucks, and cars is now being offered by the electronics division of *Z & W Machine Products Co.* of 5100 St. Clair Ave., Cleveland 3, Ohio.

The Model 31-A system includes a microphone, remote control head, cables, speakers or reflex trumpets, and a shock-mounted amplifier housed in welded steel. It operates on 6 or 12 volts d.c.

For full information on the Model 31-A or modifications for custom use, write direct to R. M. Wood at the company.

PORTABLE P.A. SYSTEM

The Sound Product Equipment Section of *Radio Corporation of America's Victor Division,* Camden, N.J. has announced the availability of a new portable sound system which has been designed for audiences ranging from a few people to several thousand.

The system includes four newly-designed components: a deluxe dual-speaker carrying case (Type MI-12762); either a 15-watt amplifier (Type MI-13295-A) or a 30-watt amplifier (Type MI-13296-A); and a dynamic microphone (MI-12017) with stand (MI-13240).

The case divides into two acousti-



"Boy... Have I Got the Lines!"

You, too, can have the lines—that meet your exact leadline conditions — whether you are a TV Set Dealer or Service Organization making the finest television reception installations, or a TV fan that demands sharp, "SNOW-FREE" pictures.

We specialize in the manufacture of television transmission lines — built with only one idea in mind: "THE FINEST TELEVISION RECEPTION."

For UHF and VHF

"SHEATH-LEED" — the all-weather leadline for the toughest conditions: Salt spray in coastal areas; hot, humid weather, or for frosty, icy, wintry wind-whipping conditions which impose a severe tax . . . Pure Polyethylene Tubing encasing Standard GOODLINE AIRLEAD.

"GOODLINE" AIRLEAD—standard of leadline excellence —with 80% of the loss producing web removed. Correct impedence for sharp, "snow-free" pictures. Of pure polyethylene with flexible stranded copper-clad conductors. MANY IMPORTANT FEATURES.

NEW FULL-WEB "SHEATH-LEED" — the pure polyethylene of "SHEATH-LEED" and full characteristics of GOODLINE AIRLEAD — but NO *PERFORATED WEB.* No 20 (7 strand 28) copperweld wire in pure electronic golden clear polyethylene — with a pure silver-gray polyethylene sheath overall — for *Maximum Weather Protection.*

Don Good, INC.

SOLD BY LEADING JOBBERS & DEALERS

Send coupon *NOW!*
Get samples "in your hands"
—you'll realize why
Don Good Products make
the finest television
reception possible.

DON GOOD, INC. 1-13
1014 Fair Oaks Ave., So. Pasadena, Calif.
Please rush Samples and Complete Information covering Don Good Products.

*Name*_____

*Street*_____

*City*_____ *State*_____

3000 MILES of TELEPHONE WIRE at 1947 PRICES..



7th ANNIVERSARY SALE
During our Anniversary Sale—our wire is rolled back to 1947 prices.
ALL PURPOSE—ALL WEATHER COMMUNICATION WIRE
This is genuine **W110B ARMY FIELD WIRE** on original steel reels. Insulated, 2-conductor, copper-steel strands. Excellent for all types of communication. Used extensively by phone companies, industry, engineering projects, ranches.
GR. 1—Unused. Ex. Cond., mi. reels (5,280 ft.; 160 lbs. **$16.00.** ½ mi. reels (2,640 ft.; 80 lbs., **$9.00**
GR. 11—Unused, gd. cond. Mi. rls. **$11.50,** ½ mi. **$6.50**
W-130—±22 ga. New 2-conductor, copper-steel, plastic insul. wire 10,560 ft. reels **$34.50.** 3,500 ft. reels **$16.00**
EASY TO INSTALL PHONES, RING AND TALK UP TO 20 MILES
EE-8—Army Field Phones, factory reconditioned—like new . . . . . pr. **$42.50**
EE-91—Field Phones, factory checked, per pair **$34.50**
NEW EE89A—Telephone Repeaters **$8.50**
NEW EE99A—Telephone Repeaters **$10.00**
Brand New TS9F Western Electric Handsets, ea. **$9.50**
TS-10 Sound powered Handsets . . . . . pr. **$17.95**
EE6SG Line Test Set Unit Phone, Brand New. **$27.50**
MANY LOW-COST PHONES FOR THIS SPECIAL SALE!
ORDER BY AIRMAIL TODAY—Write for Free Folder. Send check or M.O.—No C.O.D.'s. Prices F.O.B. Sacto. Calif. Buyers Add 3% Tax.

LORIS SALES
P. O. BOX 1896 M-2. SACRAMENTO, CALIF.



110V. AC POWER SUPPLY FOR ANY 274-N RECEIVER
Just plug it into the rear of your 274-N RECEIVER . . . any model. Complete kit and black metal case, with ALL parts and diagrams. Simple and easy to build in a jiffy. Delivers 24 volts plus B voltage. No wiring changes to be made. Designed especially for the 274-N receiver. **Only $8.95.**
Filament trans. for 274N receivers. Pri. 110V, 60 cy. AC. Sec. 24V @ .6A. An excellent buy at . . . . . **$1.95** ea.

SPLINED TUNING KNOB FOR 274N RECEIVERS



An exclusive Q-R item manufactured for us. Fits BC-453, BC-454 and other 274N receivers. This is a really hard-to-obtain item. Only . . **89c** ea.

OFFENBACH-REIMUS
1564 Market Street, San Francisco, Calif.

www.americanradiohistory.com

Make your Math EASY!



See the NEW

ELEMENTS of MATHEMATICS
For RADIO & TELEVISION

by Bernhard Fischer & H. V. Jacobs

If you've ever hesitated to use a time-saving equation because you were not quite sure how to set it up; or had moments of doubt about decimals or percentages; or wanted a quick check on your figuring—THIS IS THE BOOK FOR YOU. It makes crystal clear each step in the reasoning and each procedure in the arithmetic, geometry, and algebra needed by radio and TV technicians. You'll see how the simple, basic calculations are used in the more complex problems. You'll find it EASY to work out frequency resolutions, voltage drops, inductive reactances, decibels and the many other radio and TV problems in which accurate use of math is essential. Hundreds of sample problems, with answers, give you thorough practice. *Ready in February* $6.60 (probable)



● and the famous

Handbook of Problems and Solutions—

RADIO & TV MATHEMATICS

by Bernhard Fischer

"A book for the place of honor beside its natural partner the slide rule," says *Radio-Electronics*. Step-by-step solutions for 409 problems in radio, TV, and industrial electronics. Whatever YOUR problem—whether it is to correct the power factor of a motor, find the impedance and length of a matching stub between antenna and transmission line, or any of hundreds of other problems—here is the clear, exact solution. $6.75

● Special Notice

Save time and trouble; get better results. Use Mandl's TV SERVICE COURSE MANUAL in your shop training. Here are clear what-to-do and what-to-observe instructions, with report sheets, for 46 practical problems in TV servicing. Ready in February. Write for a sample copy.

SEE THEM ON APPROVAL

The Macmillan Co., 60 Fifth Ave., New York 11

Please send me copies of the books checked below. I will either remit the full price plus small delivery charge or return the books in 10 days. (Save: Send check or money order and we pay delivery charge)

N-1 ☐ Elements of Mathematics for Radio & TV $6.60 (prob.)
☐ Radio & TV Mathematics $6.75

Signed .....

Address .....

.....

This offer good only within continental limits of U.S.A.

cally designed baffles, each housing a heavy-duty 12" speaker, provided with 25 feet of cable and connectors. Overall case dimensions are 22½" high, 15¾" wide at the base, and 16¾" deep at the base.


Full details on this new system are now available from the company's sound equipment distributors.

MASCO TAPE RECORDERS

Mark Simpson Mfg. Co., 32-28 49th St., Long Island City 3, N.Y. is now offering its new series 53 tape recorders which feature improved portability and more modern styling.

Both the Models 53 and 53R (with radio) have dual-speed, 3¾ or 7½ ips, with automatic amplifier equalization for each speed; fast forward and rewind speeds; and two-motor drive. Their dual-track feature permits up to two hours of recording on a single 7" reel. Inputs are provided for microphone, radio, or phonograph; outputs for external speaker, external amplifier, or telephone lines are also provided. A press-to-record push-button prevents accidental erasure and provides foolproof recording and playback.

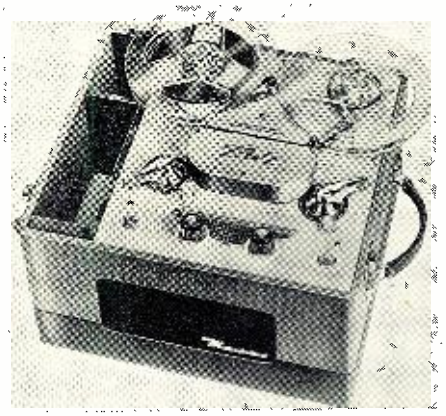Frequency response is 80 to 8500 cps ± 3 db at 7½ ips and 80 to 5000 cps



± 3 db at 3¾ ips. Additional technical specifications and literature on the series 53 recorders are available.

"IRISH" REEL TABS

Orradio Industries, Inc. of T-120 Marvyn Road, Opelika, Alabama is offering reel tabs for its *"Irish"* brand recording tape without charge to professional tape users.


The tab is designed to replace the makeshift scraps of paper and china crayon markings used for labeling purposes. The new reel tab fits snugly beneath the edges of any type of 7" plastic or metal reel, whether the reel is full, half-full, or empty. It is made of sturdy stock and has plenty of room for identification on both sides.

For tabs, write to Nat Welch at the company.

ALLIED AMPLIFIER

Allied Radio Corporation, 100 N. Western Ave., Chicago 80, Ill. is now offering a deluxe 24-watt amplifier which has been tradenamed the "Golden Knight."

BUILD your own TV Set

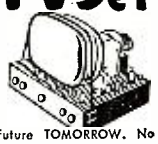


YES, actually build a valuable TV Set *right at home*. At the same time learn all about installing, repairing, servicing—and get ready for a Big-Pay Job in America's fastest-growing, most exciting industry. The CTI TV Train-at-Home Plan is preparing hundreds for bigger pay TODAY—and a brighter Future TOMORROW. No experience needed. We supply easy-to-understand instructions—made clear with hundreds of charts, diagrams, photos—*plus* TWENTY KITS of Parts, Professional Equipment and Tools. Get a *TV Set* to ENJOY. Get *set* to ENJOY a TV Future. Make money in spare time while taking Course. THOUSANDS SUCCEEDING! So can You. Send today for big FREE Book, "You Can Succeed in Television."

COMMERCIAL TRADES INSTITUTE
Dept. T19-2, 1400 Greenleaf Ave., Chicago 26, Ill.

EXPERT RADIO-TELEVISION SERVICE with EICO TEST INSTRUMENTS

Free!

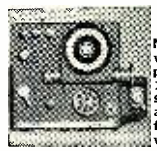Get More Service Calls with
EICO DECALS
For Store Windows & Cars.
Write EICO
Brooklyn 11, N.Y. Dept. DR-2



RU-18 RECEIVER

Navy 6-tube aircraft receiver with DF loop and antenna input; complete coverage from 190 KC to 13.9 meg.; in 8-coil sets, less tubes; brand new with any 5-coil sets; you name the freq. you desire; F.O.B. shipping wt., 25 lbs. $16.95

McCONNELL'S New Address: BARTO, PA. Phone: BALLY 5-3621

World's Only Recorder of its Kind
WALKIE-RECORDALL
8-LB SELF-POWERED BATTERY RECORDER

- AUTOMATIC UNDETECTED RECORDING up to 4 hrs.
- PICKS UP WITHIN 40 FT. RADIUS.
- VOICE ACTIVATED "SELF-START-STOP"
- NO WIRES OR PLUGS.

Records noiselessly in or out of closed briefcase, containing hidden mike while walking, riding, flying. Conferences, lectures, dictation, 2-way phone. Permanent, unalterable, indexed recording at only 3c per hr.

MILES REPRODUCER CO., INC.
812 Broadway, N. Y. 3, N. Y. Dept. RN-2

SPEAKER RECONING

Complete line Cones, Spiders, Rings and Voice Coils. Custom Built Voice Coils. Low prices. Write for Parts List and Reconing information.

WESTERN ELECTRONICS CO.
3164 West Colfax Denver 4, Colo.

ARKAY
world's finest radio kits
Write for Free Brochure
RADIO KITS, INC., 120 Cedar St., N. Y. 6

ENJOY 3 COLOR TELEVISION FILTER SCREEN NOW

Changes dull eye-straining black and white pictures into beautiful color tones. Seconds to attach. No tools used. Helps eliminate glare. Order direct. Send $1 for screen size up to 16", $1.25 size 17", $1.50 size 20", $2 size 21", $2.50 size 24", $3 size 27". (Also available are single solid color screens in blue, green, or amber.) Prices on solid color screens are 10% less. We pay postage except on C.O.D. orders. Satisfaction guaranteed. Inquiries from dealers also welcomed.

Zingo Products, Johnstown 19, New York


YOUR TESTER DAMAGED?
Let Douglas Repair It
Contractors to U. S. Government

Repairs and calibration by skilled craftsmen on all makes of Meters, Testers, Sig. Gens., etc. Prompt service. For immediate estimate send instrument by P.P. Ins. to

DOUGLAS INSTRUMENT LABORATORY
Electrical Instrument Repairers
176 Norfolk Avenue Boston 19, Mass.

www.americanradiohistory.com

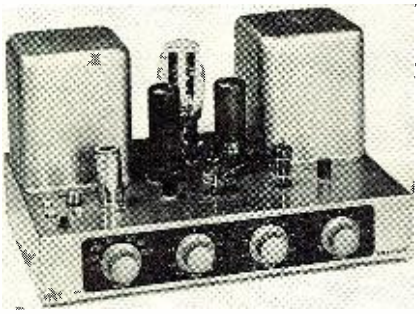This moderately priced unit uses a heavy-duty, grain-oriented output transformer which contributes to the clean response of the amplifier. Frequency response at 24 watts output is ± .75 db from 20 to 40,000 cps. Harmonic distortion is less than 1% at




the rated output with intermodulation distortion less than 2% at rated output.

The amplifier has four inputs, one for *G-E, Pickering,* or *Audak* magnetic cartridges; two inputs for radio tuner, crystal cartridge, television, or tape recorder; while the fourth input will take any high-impedance microphone. A panel switch permits selection of any input.

ENCLOSURE KIT

Karlson Associates, Inc., 1379 East 15th St., Brooklyn 30, N.Y. has announced the availability of the new "Ultra-Fidelity" cabinet kit.

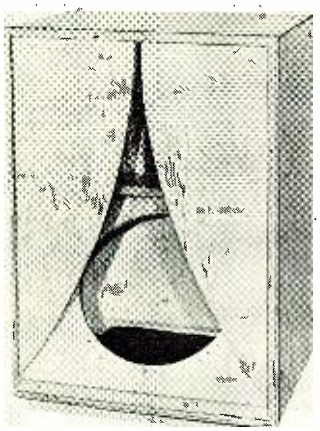The unit is exactly the same size and construction as the finished models made by the company and will provide the same standard of perform-




ance. The kit comes ready to be assembled with all 34 pieces precision-cut to size. It is constructed of rough plywood in order to furnish a good surface for the application of veneer for finishing or it may be used as is in hidden installations.

The Model 15PK is furnished with a hole cut for a 15" speaker. Adapters are available for 12" speakers on request. Construction plans for the kit are available from Dept. 1K of the company.

CRESTWOOD RECORDER

The *Crestwood Recorder Division* of *Daystrom Electric Corporation,* Poughkeepsie, N.Y. has introduced a new tape recorder to the trade, the 401.

Frequency response of this medium-

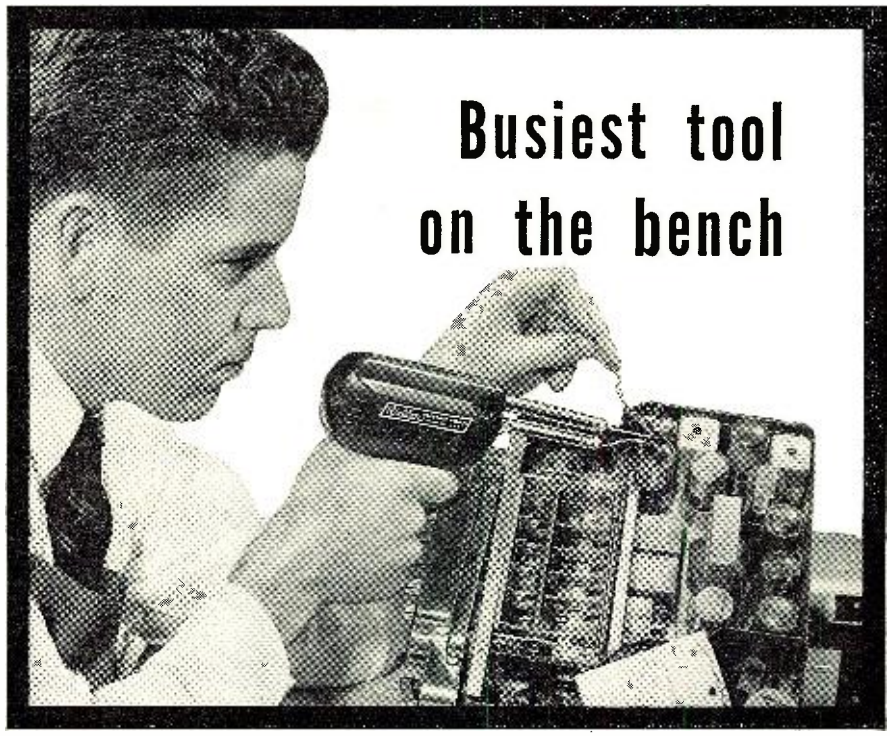

The new Weller Soldering Gun—the tool that finishes the job before ordinary soldering tools warm up!

Weller's newest models—

Go anywhere inside circuit-jammed chassis of smallest portables and table models. Slim streamlining and longer reach makes tight spots a cinch—in a fraction of the normal time.

Get hot instantly with click of trigger. Another click and—power is instantly boosted—up to *275 watts!*

Give wide selection of power for every job—100, 135, 200, 250, and now—*275 watts!* Light and heavy duty models, either single or dual heats.

You'll like the perfect balance and slim lines, too—on all latest Weller models. Ask your distributor for a demonstration, or write direct for bulletin.

Weller

Better from Grip to Tip
SOLDERING GUNS
810 Packer Street, Easton, Pa.

ALLIED RADIO
CORPORATION
100 N. WESTERN AVE. • CHICAGO 80, ILL.

has **hallicrafters**

- **10 Kc to 250 cycles in six steps!**
- **The most *stable* receiver made!**
- **Single Side Band Suppressed Carrier!**

The Hottest Ham News in Years!

THE HALLICRAFTERS CO. • CHICAGO 24, ILL.

RADIO ENGINEERING DEGREE IN 27 MONTHS

Radio engineering is a big field. There's room for you in it—if you're good. Get first-class training at Indiana Tech. Intensive, specialized course, including strong basis in mathematics and electrical engineering, advanced radio theory and design, television, electronics. Modern laboratories. Low rate. Also **B.S. DEGREE IN 27 MONTHS** in Aeronautical, Chemical, Civil, Electrical and Mechanical Engineering. G.I. Government approved. Enter March, June, September, December. You can earn part of your expenses right here in Fort Wayne while you are studying.

INDIANA TECHNICAL COLLEGE
924 E. Washington Blvd., Fort Wayne 2, Indiana

Please send me free information on B.S. Engineering Degree in 27 months as checked.

☐ Radio-Television ☐ Aeronautical
☐ Civil ☐ Mechanical ☐ Electrical

Name .....

Address .....

www.americanradiohistory.com

POWER TRANSFORMERS FOR SELENIUM RECTIFIERS OR FILAMENTS. PRIMARIES 115V 60 CYCLES.

12.6VCT/2A/2500V INS	$ 2.79
25.2VCT/1A/2500V INS	2.79
12.6V/7A or 25.2V/3.5A/2500V INS	6.17
26VCT/3A/2000V INS	4.11
104VCT/3A/2000V INS	11.76
78V TAP 26V/52V/6A/2000V INS	22.34
13V/12A/2000V INS	7.06
104VCT/6A/2000V INS	24.69
156V TAP 130V/3A/2000V INS	23.52
130V TAP 104V/12A/2000V INS	70.56
156V/6A/2000V INS	41.16
36VCT/10A/2000V INS	15.87
72VCT/10A/2000V INS	29.40

RACK PANEL CABINETS BLACK CRACKLE FINISH

Size	Panel Space	Price
#42 42-1/16 x 22 x 17¼	36¾ x 19	$27.25
#47 47-5/16 x 22 x 17¼	42 x 19	31.20
#66 66-9/16 x 22 x 17¼	61¼ x 19	40.50
#82 82-5/16 x 22 x 17¼	77 x 19	48.75
#10 10½ x 21½ x 15	8¾ x 19	9.70
#14 14 x 21½ x 15	12¼ x 19	11.88
#15 15¾ x 21½ x 15	14 x 19	13.20
#19 19¼ x 21½ x 15	17½ x 19	15.70
#28 28 x 21½ x 15	26¼ x 19	18.45
#36 36¾ x 21½ x 15	35 x 19	20.45

Grey Crackle Furnished on Request—Same Price.

RACK PANELS BLACK CRACKLE FINISH

Size	Steel	Aluminum
1¾	$ .63	$ .73
3½	.70	.99
5¼	.88	1.50
7	.99	1.80
8¾	1.25	2.15
10½	1.48	2.70
12	1.75	3.15
14	1.99	3.63
15¾	2.25	3.99
17½	2.48	4.45
19¼	2.75	4.88
21	3.05	5.25
26¼	on request	
35	on request	


Grey Crackle Furnished on Request—Same Price.

All prices F.O.B. our warehouse New York

LEEDS RADIO CO.

75 Vesey St. Dept. A New York City 7

Radio War Surplus SAVE UP TO 85%

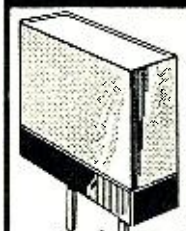

CRYSTALS

. . . in FT 241-A Holders—½" Pin SPC. Marked 54th OR 72nd Harmonic MC Freq. Listed below by fundamental frequency with fractions omitted.

500 KC Crystals ea. $1.50

1000 KC Crystals ea. $3.95

200 KC Crystals

370	407	444	476	509
372	408	445	477	511
374	409	446	479	512
375	411	447	480	513
376	412	448	481	514
377	413	450	483	515
379	414	451	484	516
380	415	452	485	518
381	416	453	486	519
383	418	454	487	520
384	419	455	488	522
385	420	456	490	523
386	422	457	491	525
387	423	458	492	526
388	424	459	493	527
390	425	461	494	529
391	426	462	495	530
392	427	463	496	531
393	428	464	497	533
394	430	465	498	534
395	431	466	501	536
396	433	468	502	537
397	434	469	503	538
398	435	470	504	540
400	436	472	505	
401	437	473	506	
402	438	474	507	
403	440	475	508	
404	441			
405	442			
406	443			

$5 Per Doz. Postpaid

PLEASE ENCLOSE FULL AMOUNT WITH ORDER
QUANTITIES AVAILABLE
WRITE FOR YOUR REQUIREMENTS

C & H SALES CO.

2176 E. Colorado St. • Pasadena 8, Calif.
BOX 356-TF EAST PASADENA STA. • PASADENA 8, CALIF.

priced unit is from 30 to 13,000 cps ± 2 db at 7½ ips tape speed. The model 401 has two speeds, 7½ and 3¾ ips. It also has a separate recording volume control in addition to the regular monitor control and magic-eye indicator which prevents recording overlap. Three separate inputs, for radio-TV, phonograph, and microphone, are controlled by a single selector switch.

PUSH-BUTTON RECORDER

Radio Corporation of America. Engineering Products Dept., Camden, N.J. has introduced a new push-button tape recorder which is characterized by ease of operation and good performance.

All of the recorder's functions are actuated by push-buttons. The unit itself has two speeds, a quick-threading feature, a tone-sensitive microphone, easy-to-carry case, and trouble-free construction.

The cabinet measures 9" x 14" x 12" and the cover holds the microphone, two reels, and the a.c. power cord. A data sheet and additional information on the Model SRT-301 are available from the company on request.

PREAMP-EQUALIZER

Fairchild Recording Equipment Corp., 154th St. and 7th Ave., Whitestone, N.Y., has designed and is producing a new preamplifier-equalizer which retails in the moderate price class.

Although it performs every function of a high-quality preamplifier-equalizer, it uses only two knobs in normal operation. An exclusive "balanced-bar" control permits exact shading of tone coloring to suit individual taste. When used in conjunction with the control knobs, this feature provides for adjustment to match the acoustics of the room in which the equipment is installed.


Frequency response is 20 to 50,000 cps ± ½ db with controls in the uniform response position. There are seven input channels and complete equalization for all records, American and foreign, standard and microgroove.

PROFESSIONAL RECORDER

Magnecord, Inc., 225 W. Ohio Street, Chicago 10, Illinois has introduced a new professional magnetic tape recorder, the M80.

The new unit is designed for 10½ inch reels and incorporates all the latest features including slot loading, safety interlocked push-button controls, unitized construction, and full-range frequency response from 30 to 15,000 cps at 7½ ips tape speed.

The recorder will operate at either

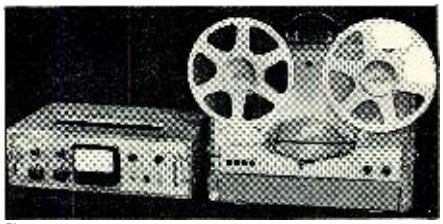

7½ or 15 ips without capstan change. Starting time is less than .1 second and stopping time is within less than 2 inches of tape when operating at 15 ips.

The unit is designed for rack, portable, or console operation. The company will supply full details on this recorder upon request.

SHADED POLE MOTOR

Electro Engineering Products Company, Inc., 609 W. Lake Street, Chicago 6, Ill. is now offering a new, powerful, and compact shaded pole motor for phonographs and tape recorders.

The new motor, the Model MS-3600, has been specially designed to withstand high temperatures and rough service yet is low priced for application to mass-produced equipment.

It is a 4-pole, shaded pole, a.c. type motor and is available in either two or four coil design. It has self-aligning, oil-impregnated sleeve bearings with a specially-designed oil retaining washer and dynamically balanced rotors. —30—



www.americanradiohistory.com

Within the Industry

(*Continued from page 26*)

11th and Cambria, in Philadelphia. It will be devoted to the assembly of the company's line of connectors.

* * *

JOHN E. MARTIN has been named director of research for *The Gabriel Company,* Needham Heights, Massachusetts.



Mr. Martin, who was born in Stafford, England, graduated from King's College, London University, after having majored in physics and mathematics. During the war he was engaged in naval radar research for the British Admiralty and later did postgraduate work at London University. Following that he became senior engineer for the *BBC,* specializing in antenna design.

* * *

WILLIAM R. HEWLETT, vice-president of *Hewlett-Packard Co.* of Palo Alto, California, has been elected president of the Institute of Radio Engineers for 1954. He succeeds Dr. James W. McRae as head of the international society of over 35,000 radio engineers and scientists.

Maurice J. H. Ponte, director of *Compagnie Generale de Telegraphie Sans Fil* of Paris, France is the new vice-president.

Elected as directors for the 1954-1956 term are Axel G. Jensen, director of television research for *Bell Telephone Laboratories, Inc.* and George Rappaport, chief engineer of the Countermeasures Branch, Aircraft Radiation Lab., Dayton, Ohio.

* * *

ARTHUR A. CURRIE, assistant general sales manager of the radio and television division of *Sylvania Electric Products Inc.,* has been named sales manager for radio and television.



Assistant sales manager since October 1952, Mr. Currie served as field sales manager from Jan. 1951 to October 1952 and as district sales manager from 1949 to the beginning of 1951.

Prior to joining *Sylvania,* he was associated with *Apex Electrical, Allied Appliance Co.* of Boston, the OPA, and *New England Power.*

* * *

W. S. ANDERSON, director of *Automatic Electric Co.,* was elected president of the New York Chapter of the Armed Forces Communications Association.

Emmett R. Shute was elected vice-president. The balance of the chapter's officers were re-elected for another term. —30—

CBS-COLUMBIA
GENERAL ELECTRIC
PHILHARMONIC
WESTINGHOUSE
MOTOROLA
SYLVANIA
HOFFMAN
EMERSON
PHILCO
ADMIRAL
MUNTZ
RCA

STANCOR HAS EXACT REPLACEMENT FLYBACKS FOR ALL THESE TV MANUFACTURERS' SETS...and others will be available soon

Designed for quick, simple installation, these Stancor flybacks save your time. There are no holes to drill, no leads to splice. Terminal board layouts duplicate the original units—even include choke coils, resistors, tube sockets and any other components that are on the original.

Stancor TV replacements are listed in Sams' Photofact Index, Counterfacts, Rider Manuals and Tek-Files

CHICAGO STANDARD TRANSFORMER CORPORATION
3584 ELSTON AVE., CHICAGO 18, ILL.

EXPORT SALES: Roburn Agencies, Inc.
39 Warren Street • New York 7, New York

MORE JOBS *than graduates*

Electronic Engineers
Excellent opportunity for pro... ssional growth and advanc... Interesting and ...

Demand for our engineering graduates exceeds supply. *Effective placement.* Study in this world-famed college established 1884. Quarters start March, June, Sept., Jan. *Approved for Korean Vets.*

Bach. Sci. degree in 27 months

Complete Radio Eng. courses . . . TV, UHF and FM. Also Mech., Civil, Elec., Chem., Aero. and Adm. Eng.; Bus. Adm., Acct. Small classes. Well-equipped labs. Modest costs. Prep. courses. *Write J. McCarthy for Catalog and Campus View Book.*

TRI-STATE COLLEGE
1624 College Avenue, Angola, Indiana

EVANS RADIO
10 HILLS AVENUE
CONCORD, NEW HAMPSHIRE

has **hallicrafters**

- 10 Kc to 250 cycles in six steps!
- The most *stable* receiver made!
- Single Side Band Suppressed Carrier!

The Hottest Ham News in Years!

THE HALLICRAFTERS CO. • CHICAGO 24, ILL.

www.americanradiohistory.com

In DETROIT it's AARON!


TG-34A KEYER
PORTABLE



• 115 or 230 V. @ 50 to 60 cycle—KEYER TG-34A is an automatic unit for reproducing audible code practice signals previously recorded in ink on paper tape. By use of the self contained speaker, the unit will provide code practice signals to one or more persons or provide a keying oscillator for use with a hand key. The unit is compact, in portable carrying case, complete with tubes, photo cell, and operating manual. Size: 10 9/16" x 10 1/2" x 15 13/16". Shipping weight: 45 lbs. BRAND NEW—in Original Box—While They Last


Only: $24.95

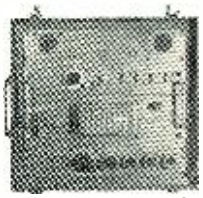TRANSCEIVER
RT-48/TPX-1
IDEAL FOR UHF EXPERIMENTERS
157 TO 187 MC



Contains vidio ampl., sweep circuits, 17 tubes, plugs and many misc. parts—in case with lid.

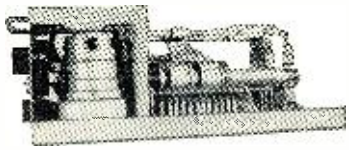Priced only at fraction of original cost. NEW $14.95



TYPE T-3074 UHF TRANSMITTER
Ideal for UHF experimenters. 180 to 200 mc. British made. Has pair of tuned lines and 2-vt-90 tubes. NEW $14.95

PHONETTE



Made by Personal Music Corp. 24v operated. Hayden Timer Motor. 5" dyn. speaker. 2 pilot lights. Coin inserts 1 to 5 pennies. Chromed metal and grill. Wt. 6 1/2 lbs. Size 4 1/4 x 7 1/2 x 6" high. Used. ONLY $1.95

25% with order—
balance including postage C.O.D.
Michigan residents please add 3% sales tax

AARON ELECTRONIC SALES
6025 MT. ELLIOTT DETROIT 11, MICH.

WIRELESS OPS OF OLD

By C. HOWARD BOWERS


ON THE West Coast they start early too, and in this issue we salute COMMANDER CLIFTON H. WATSON, USNR. and also thank him for his story, as told to his friend E. H. Marriner of La Jolla, California.

The Commander's career started in Portland, Oregon in 1905, after he had read of Marconi's achievement test from Glace Bay, N. S. to Clifden, Ireland. His first experiment was with a magnetic coherer and a spark-coil which transmitted signals the full width of a room. It was during that same year that the *USS Charleston* along with several other war ships came into Portland harbor and our young experimenter, through a personal acquaintance with Admiral Fullam, had an opportunity of looking over some real Navy wireless equipment. He soon became a bona fide amateur—the fourth one in Portland.

Cliff's first wireless job was at Grangeville, Idaho, where his father owned a mine and at 13 he was handling traffic with the *United Wireless Telegraph Co's* station "PE" Portland, Ore., "PH" San Francisco, California, and "PA" Seattle, Washington. There were no news broadcasts those days. By summer, 1906, Cliff found himself breaking in at "PE" Portland where only Morse code was used over their old *DeForest* transmitter. A three slide tuner and a carborundum detector comprised the receiving apparatus.

During 1911 young Watson took the examination for a commercial license (Certificate of Skill in Wireless Telegraphy) at Mare Island (Calif.) Navy Yard, and his first sea-going job after obtaining his certificate was aboard the *SS Chehalis*, sailing between Gray's Harbor, Wash., and San Diego, Calif., with stops at San Francisco and San Pedro, Calif. Following two years on the good ship *Chehalis*, "Sparks" Watson traveled on the steamers *Senator*, *Alameda*, and *Humbolt*—mostly between Seattle, Wash., and Nome, Alaska. Cliff looks back on this period with a nostalgic interest due to the many young school marms who were then making summer excursions to Alaska. He also had other experiences while on the *Senator*. Once the ship ran into a terrific blow off Cape Serichef in the Bering Sea and for three days no one knew if they would make it to Unimak Pass and calm water. They made it! Another time Cliff, answering an SOS from the *SS Spokane* in distress off Alaska, directed some of the rescue work and remembers receiving $25.00 as his share of the salvage money.

About 1913, the Commander-to-be decided on working "shore-side" and was employed by the *North West Electric Company* of Portland, Ore., as an operator at their power plants, using wireless for dispatching. In 1915 he installed five different wireless stations for the *Montana Power Company* and in 1917 he accepted the appointment of Radio Inspector at Seattle, Wash., relieving Bennie Wolf (well known R.I. in that area) who had been called into the Navy. Before long, however, he went to the Mare Island Navy Yard in charge of their Wireless Laboratory where he remained until 1921. Having gained considerable experience in wireless techniques by this time, he went into business for himself and with an associate, Joe Hallack, formed the *HALLACK & WATSON RADIO CORPORATION*, constructors of broadcasting stations. In 1930, disassociating himself from this business, he became identified with the Portland Bureau of Police and installed their first wireless station, "KGPP," where he remained as their radio engineer until 1941 when he went on active duty with the Navy with the rank of Commander, USNR. On being mustered out in 1946, our "restless electron" was ap-

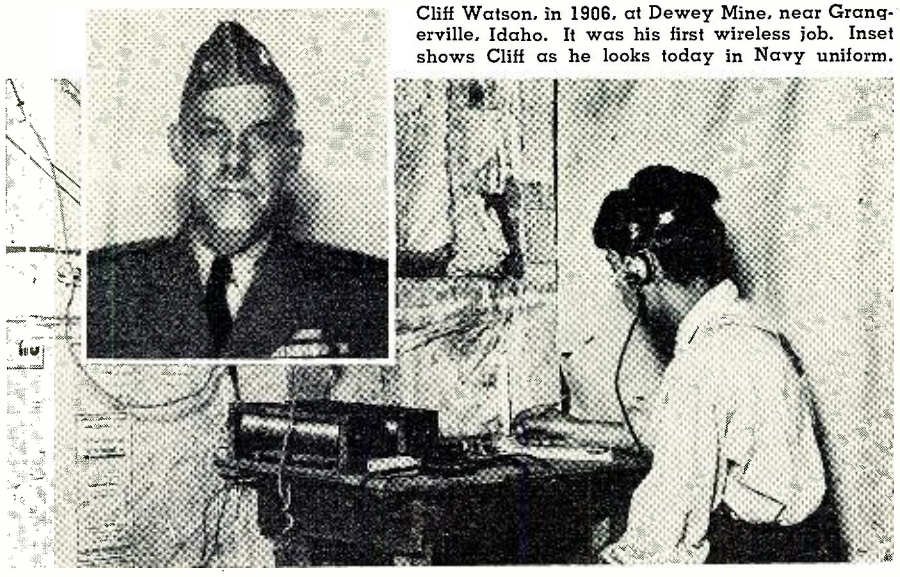

Cliff Watson, in 1906, at Dewey Mine, near Grangerville, Idaho. It was his first wireless job. Inset shows Cliff as he looks today in Navy uniform.

www.americanradiohistory.com

NOW do all 5 testing jobs with 1

RCP
"DO-ALL"
Tube and Set Tester
Model 808A



1 **A Tube Tester**—All the features of the famous 324 Dynoptimum free point tube tester—protected against obsolescence—tests all modern standard, miniature, naval base and subminiature tubes. Easily read on 4½" meter.

2 **A Cathode Ray Tube Tester**—Will check all magnetic deflection type Television Picture tubes. Locates and isolates all shorts or leaks.

3 **A Reactivator**—Revives and Reactivates many otherwise Dim or Bad Television Picture tubes. Can also be used on other tubes.

4 **A VT Voltmeter (AC-DC)**—This really outstanding 17 Range instrument is a VT Voltmeter for AC as well as DC. Balanced bridge type push-pull circuit. Draws negligible current due to high impedance of 25 megohms. Accuracy ±2% DC, ±5% AC. Discriminator alignment scale with zero center. AC & DC volts 0 to 5-25-100-250-1000; db—20 to 16, —6 to 30, 6 to 42, 14 to 50, 26 to 62.

5 **An Ohmmeter**—Reads all Resistances 0.2 ohms to 1000 megohms on 5 ranges. Use this instrument also to check condensers for leakage and shorts.

Equipped with a double rollindex and enlarged, easy to read letters and numbers, the new RCP 808A is so designed as to simplify each operation. Truly a professional instrument for the professional technician.

The RCP 808A is housed in a handsome handrubbed oak carrying case and features an attractive, highly visual panel. Compartment available to hold test leads, isolation probe, batteries, etc. Size 12½" x 12¾" x 4¾". Weight 12 lbs. Complete, ready to operate at **$99.95**

See it at your local parts distributor and ask for catalogue RN-2

RADIO CITY PRODUCTS CO., INC.
152 West 25th Street RCP New York 1, N. Y.

pointed radio engineer in the Electronic Laboratory of Navy Radio, "NPL," Pt. Loma, (San Diego) California, the very station he used to gaze at in wonder from his old ship.

Cliff Watson has had quite a career and we say, "Lots of good luck, Commander! It looks like your vocation is going to be permanent!"

George H. Mullnix

Not only has the West Coast produced men who pioneered the wireless field, but some who also added materially to the population. Take George H. Mullnix, father of five children and grandfather of four; he started experimenting with wireless in 1913, and learned the code even before that.

George had plenty of ambition in those days as in 1915 we find him presiding over the *DeForest* radiotelephone exhibition at the San Francisco World Fair. This was a forerunner to his joining the aviation section of the U.S. Army Signal Corps as a journeyman electrician.

While in the Signal Corps he attended A & M College of Texas' radio mechanics course, went through the David Rankin Institute's special electrical engineering course, also through the radio operators' course at University of Texas, with finishing touches at Ellington Field, Texas. The amount of soldiering done by our wireless wizard is the unknown quantity of course, but we do know that he was separated from the Air Service at Mitchell Field, L. I., December 13, 1918 and after a refresher course secured his commercial license in September, 1919.

After some "warm up" duty on Pacific Coast lumber schooners, George sailed as 2nd operator on the *SS Colusa* from San Francisco to Manila, and the Straits Settlements. Then followed a year on the tanker *Miskianza*. The liners *Lurline* and *President* also carried our young wireless expert before he finally decided to come ashore —object matrimony!

George Mullnix was married September 24, 1922 at Carmel, California and has made his home there since 1944. In the interim he was identified with the *Pacific Gas and Electric Co.* as a radio troubleshooter and subforeman and, as a side-line he taught electrical classes in public schools.


After slightly more than 20 years with the power company, our ambitious friend retired October, 1943 and since then has alternated between being in business for himself and being a journeyman electrician.

With this background, our old time wireless man was well qualified to revert to amateur status some time ago with the assigned call of W7WDU.

Mr. Mullnix's own conclusion is, "I am now 53 years of age and with the help of amateur radio, I hope to live to be 100!"

EDITORS NOTE: *If your experiences as a commercial wireless operator date back to 1912 or thereabouts, you are an Old Timer and you should write us giving a thumbnail sketch of your career.* —30—

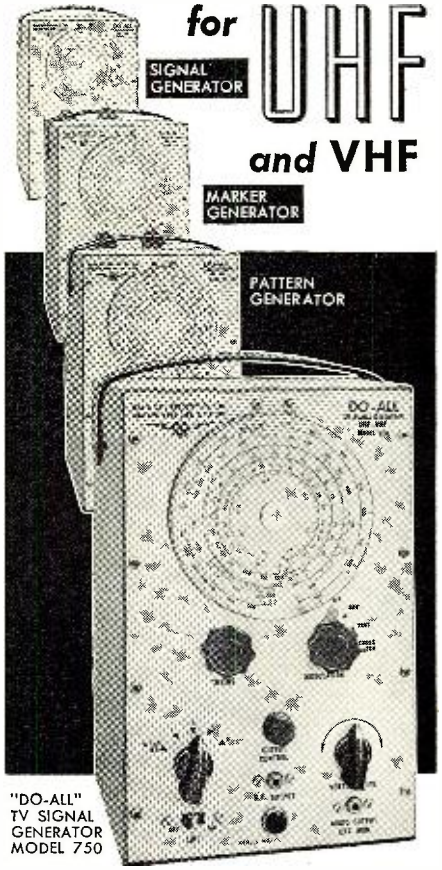You can do MORE with an RCP "DO-ALL" for UHF and VHF



"DO-ALL" TV SIGNAL GENERATOR MODEL 750

ONE
RCP "DO-ALL"
SIGNAL GENERATOR
for all THREE

- SIGNAL GENERATOR
- MARKER GENERATOR
- PATTERN GENERATOR

Designed for portable or bench use, the 750 reflects the finest in construction and appearance. It is handsomely finished in an attractive brushed aluminum panel with a steel carrying case.

- Inductuner insures accuracy of within ½ of 1% over the entire range of 9 Mc to 900 Mc.
- All VHF frequencies are on fundamentals.
- RF's and IF's are clearly calibrated on a large etched aluminum dial.
- Steady horizontal bars, vertical bars and crosshatch pattern individually produced on all channels.

PRICE $79.50

See Model 750 At Your Local Parts Distributor.

Write For Complete Catalog RN-2

RADIO CITY PRODUCTS CO., INC.
152 WEST 25th STREET RCP NEW YORK 1, N. Y.

www.americanradiohistory.com

SAVE 50%



Measurements Corp.

STANDARD SIGNAL GENERATORS
Model 78

FREQUENCY RANGE: 15 to 25 and 190 to 230 mc in two bands.
OUTPUT VOLTAGE: 1 to 100,000 micvlts
MODULATION: AM, fixed at 30%.
POWER SUPPY: 117V, 50-60 cycle.
Limited Quantity ONLY $79.50

Western Electric



Laboratory Magnets

GAUSS: 900
POLE FACE diameter 3½ inches
DISTANCE between pole faces: 4 in.
CENTER point between faces to base: 6⅜ inches.
DIMENSIONS: 15⅛" x 6" x 1⅜"
WEIGHT: 65 lbs
Complete stock of MAGNETS and MAGNETRON TUBES. Send for complete listings, prices, and technical data.

RA-34
RECTIFIERS

Originally designed as an A. C. Power Supply for BC-191 and BC-375 transmitters, this SELENIUM rectifier is both efficient and versatile.
INPUT: 105-125 or 210-250 volts, 1000 watts. Transformer is tapped to accommodate 11 different steps of voltage within these ranges.
OUTPUT: **Filament Voltage** 12V AC up to 14.25 amp. **Control and Mike Voltage** 12V DC at 2.4 amp. **Plate Supply** 1000V DC to 350 milliamp.
Dimensions: 13¾ x 12 11-16 x 16¼ in. Weight 140 lbs **Immediate Delivery** $175.00

RA-37 RA-49 RA-50 RA-62 RA-63 RA-67 Extensive stock of rectifiers and power supplies.

Certified - Guaranteed
All equipment is sold with our **certified, unconditional guarantee,** checked and tested in our own shop. We are a recognized and approved supplier for **Foreign and U. S. Govt. Agencies.** We invite your inquiries for supply or technical data.

A DIVISION OF
Arnold A. Semler, Inc.
6855 TUJUNGA AVENUE
NORTH HOLLYWOOD, CALIF.

AMERICAN ELECTRONICS

SERVICE HINTS ON ADMIRAL TV SETS

SERIES 19 CHASSIS


Audio hum.

An objectionable residual hum level may be found in the chassis of this series using a 10-inch electromagnetic speaker.

To remedy this, do the following:

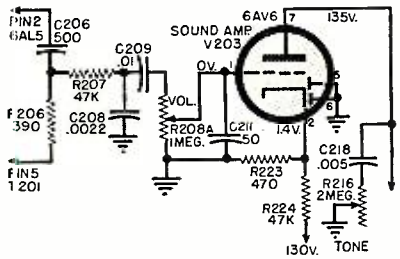1. Check the lead dress in the audio input circuits, paying particular attention to the a.c. leads of the "on-off" switch. These leads should be kept well away from the audio amplifier grid circuit (pin 1 of V_{203}, 6AV6). The audio coupling condenser, C_{209} (.01 μfd.), should be dressed away from the "on-off" switch.

In models with tone control, dress the lead between the control and the



audio amplifier plate away from the a.c. leads. (See accompanying diagram.)

2. Check all filter condensers, especially C_{101}, the 60-μfd. electrolytic in the "B+" power supply, between pin 8 of the 5U4G and ground.

3. Substitute a PM speaker with choke attached (*Admiral* Part No. 78B80-1). If this clears up the hum, then the original speaker is probably at fault.

Vertical jitter and poor interlace.

This condition may occur if the red lead to the horizontal deflection yoke is too near the grid circuit of the vertical output tube (V_{402}, 6S4). This lead should be dressed against the chassis well away from the grid circuit.


Horizontal instability.

To increase the horizontal sync level and "square up" the horizontal sync pulse, add an 8200-ohm resistor between pin 1 of V_{401B} (12AU7 sync clipper) and the number 3 lead of the vertical integrator Couplate.

Picture bending and unstable horizontal sync.

To minimize bending of the picture at high contrast control settings in strong signal areas, and improve horizontal sync in medium fringe areas, make the following changes:

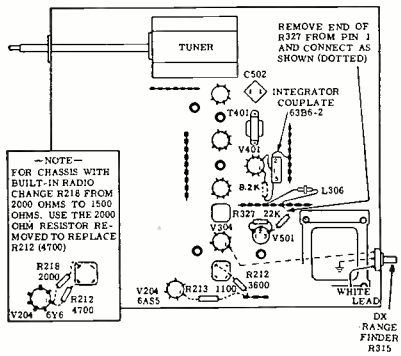1. Check the connections to the "DX range finder" control, R_{315}. Be sure that the center terminal is grounded and that the white wire goes to the control terminal nearest the bottom edge of the chassis. Connect a wire lead from pin 1 of V_{304} (6AL5)



to the remaining terminal of the range finder control. (See accompanying diagram.)

2. In chassis using a 6AS5 sound output tube (V_{204}), change resistor R_{212} from 3600 ohms to 1500 ohms, ½ watt, 5%, and change resistor R_{213} from 1100 ohms to 910 ohms, ½ watt, 5%.

In chassis using a 6Y6G sound output tube, change resistor R_{212} from 4700 ohms to 2000 ohms, ½ watt, 5%, and resistor R_{218} from 2000 ohms to 1500 ohms, ½ watt, 5%.

3. Disconnect resistor R_{327} (22,000 ohms) from the junction of resistors R_{325} and R_{326} (2700 ohms), and reconnect R_{327} to the junction of R_{325} and peaking coil L_{306}.

4. Connect an 8200-ohm resistor in series between terminal 3 of vertical integrator Couplate and pin 1 of V_{401B}.


5. Since step 1 is effective only with the "DX range finder" set at zero, use this setting unless a higher one gives better results.

CHASSIS 19E1, 19G1 & 19N1

Repeated fuse failure.

In some of these chassis, the ⅜ ampere fuse, M_{401}, may blow when the function switch is rotated from the "Radio" to the "TV" position. This may occur because the rotor contact of the switch section, S_{701C}, is wide, and during rotation of the switch there is one position where all contacts of this section may short, resulting in a surge of current that blows the fuse.

This difficulty can be corrected by

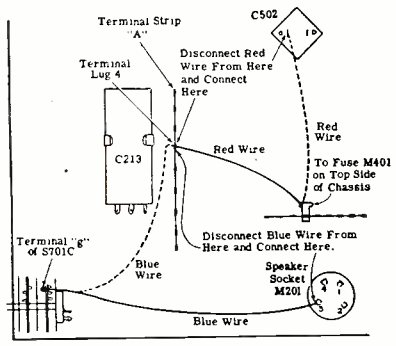

www.americanradiohistory.com

changing the circuit location of the fuse, as illustrated in the accompanying diagram and explained in the next paragraph. (The dotted lines indicate the original connections.)

1. Disconnect the blue wire from lug 4 of terminal strip "A." This is the blue wire from terminal "g" of switch section S_{701c}.

2. Connect the blue wire to pin 3 of speaker socket M_{201}.

3. Disconnect the red wire that goes to fuse M_{401} from the positive terminal of the electrolytic condenser, C_{502} (80 μfd.). Two red wires are connected to C_{502}, be sure to disconnect only the red wire connected to the fuse.

4. Connect the red wire removed from the positive terminal of C_{502} to lug 4 of terminal strip "A."

SERIES 22 CHASSIS

60-cycle hum.

A cathode-to-heater short in the 2nd sound i.f. tube, V_{201}, 6AU6, will cause a loud 60-cycle hum when there is a signal being received. To test whether this tube is at fault, disconnect the antenna, and if the hum level decreases, it is likely that V_{201} is defective.


CHASSIS 22A2, 22A2A, 22C2, 22E2, 22M1 & 22Y1

Horizontal ripple.

Horizontal ripple moving up or down in the picture is usually due to a power source frequency difference between the transmitter and the television receiver. It is caused by some of the 60-cycle power source voltage feeding into the horizontal oscillator. This a.c. voltage can come from the "B+" power supply, through the horizontal sync discriminator, and thus be applied to the control grid of the oscillator, or from flux leakage around the power transformer. The most common cause is flux leakage around the power transformer (even though it has a copper band) to the horizontal lock coil.

To shield the horizontal lock coil from the power transformer, see the accompanying diagram and do the following:

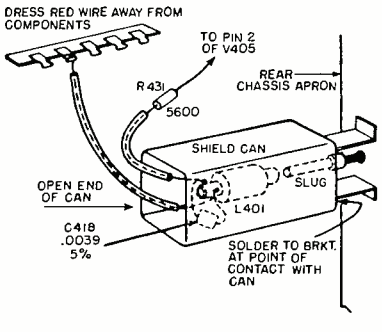1. Disconnect the red lead from the lug on the horizontal lock coil, L_{401},



and reroute it away from all chassis components. Reconnect the red lead to the lock coil lug.

2. Replace R_{431}, the 5600-ohm resistor connected between the lug of the lock coil and pin 2 of V_{405} (6SN7), with

RADIO & TV RECEIVING
Windsor TUBES

TESTED and GUARANTEED for PEAK PERFORMANCE


WHAT EVERY SERVICEMAN SHOULD KNOW . . . No tube checker reading of "Good" can positively insure that a specific tube will function perfectly in a TV set . . . only a substitution test in an actual set will do that! This is particularly true of tubes used in power and sweep circuits, deflection amplifiers, oscillators, reactance modulators, etc.

YOU PLAY IT SAFE when you buy WINDSOR tubes—because every tube we ship has been carefully pre-tested in a radio or TV set for PEAK PERFORMANCE under actual operating conditions. So we unconditionally guarantee every Windsor tube in accordance with the Standard Warranty: full replacement of any defective tube within 90 days of purchase, excepting only burnouts and breakages. Each tube is attractively packaged in individual carton.

Type	Each	Type	Each	Type	Each	Type	Each	Type	Each	Type	Each
1A7GT	$ .67	1U5	$ .51	6AU6	$ .47	6J5GT	$ .44	6Y6G	$ .64	12BA7	$ .66
1B3GT	.69	1X2A	.74	6AV5	.85	6J6	.68	7A4/XXL	.57	12BD6	.51
1C6	1.06	2A7	.74	6AV6	.41	6J7	.70	7A5	.70	12BE6	.52
1E7GT	1.09	2X2	1.43	6AX4	.72	6K6GT	.45	7A6	.57	12BH7	.69
1H5GT	.51	3LF4	.76	6B8G	.93	6K7	.70	7A7	.58	12BY7	.77
1H6	.93	3Q4	.66	6BA6	.50	6L6G	.88	7A8	.56	12J5GT	.48
1J6	.93	3Q5GT	.72	6BA7	.66	6L6GA	.88	7AD7	1.05	12SA7GT	.57
1L4	.63	3S4	.61	6BC5	.58	6Q7GT	.55	7AF7	.63	12SK7GT	.55
1L6	.66	3V4	.62	6BD5GT	.98	6S4	.51	7AG7	.65	12SL7GT	.67
1LA4	.82	5R4GY	1.00	6BD6	.54	6S8GT	.75	7AH7	.65	12SN7GT	.59
1LA6	.80	5U4G	.44	6BE6	.51	6SA7GT	.57	7AJ7	.70	12SQ7GT	.46
1LB4	.82	5V4G	.83	6BF5	.66	6SC7	.63	7B4	.54	14A7	.58
1LC5	.80	5Y3G	.37	6BF6	.43	6SD7	.55	7B5	.51	14AF7	.68
1LC6	.80	5Y3GT	.32	6BG6G	1.47	6SF5GT	.66	7B6	.52	14B6	.50
1LD5	.80	5Y4G	.43	6BH6	.63	6SH7GT	.52	7B7	.58	14C5	.85
1LE3	.80	6A8GT	.68	6BJ6	.53	6SJ7GT	.52	7C4	1.05	14C7	.70
1LG5	.80	6AB4	.51	6BK5	.76	6SK7GT	.55	7C5	.56	14E6	.70
1LH4	.80	6AC5GT	.82	6BK7	.97	6SL7GT	.68	7C6	.50	14E7	.85
1LN5	.80	6AG5	.59	6BL7GT	.94	6SN7GT	.59	7C7	.58	14F7	.69
1N5GT	.63	6AH4	.68	6BN6	.98	6SQ7GT	.46	7E5	.85	14F8	.99
1P5	.76	6AK5	1.05	6BQ6GT	.98	6T8	.85	7E6	.65	14J7	.85
1Q5	.72	6AL5	.44	6BQ7	.92	6U8	.86	7E7	.85	14N7	.75
1R4	.85	6AQ5	.51	6BZ7	1.09	6V3	1.09	7F7	.69	14Q7	.62
1R5	.62	6AQ6	.47	6C4	.41	6V6GT	.51	7F8	.97	14R7	.85
1S4	.67	6AQ7	.75	6CB6	.58	6W4GT	.50	7G7	.85	14S7	.80
1S5	.52	6AR5	.42	6CD6G	2.04	6W6GT	.63	7H7	.61	19BG6G	1.53
1T4	.62	6AS5	.55	6D6	.63	6X4	.37	7J7	.85	19T8	.87
1T5GT	.78	6AT6	.42	6E5	.72	6X5GT	.36	7K7	.85	25BQ6GT	.98
1U4	.61	6AU5GT	.85	6F5GT	.54			7L7	.85	25L6GT	.53
								7N7	.62	25W4GT	.53
								7Q7	.62	25Z6GT	.46
								7R7	.70	35A5	.55
								7S7	.90	35B5	.53
								7V7	.92	35C5	.53
								7X6	.62	35L6GT	.52
								7Y4	.45	35W4	.33
								7Z4	.50	35Z5GT	.33
								12AT6	.53	50A5	.55
								12AT7	.75	50B5	.52
								12AU6	.47	50C5	.52
								12AU7	.58	50L6GT	.52
								12AV6	.41	117Z3	.43
								12AV7	.87		
								12AX4	.72		
								12AX7	.67		
								12AY7	2.15		
								12BA6	.50		

FREE!
WINDSOR TUBE CADDY

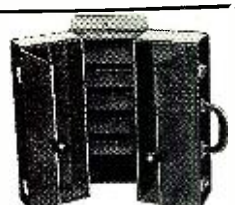The most practical Service-Aid ever designed for the radio and TV repairman. This ideal television carry-all now offered free with every purchase of $160.00 or accumulated purchases totalling $160.00 within 90 days. (You get caddy credit memo with each purchase.)



- Carries approximately 125 tubes including meters and tools.
- 16¾ inches long x 8¼ inches wide x 13¾ inches high.
- Weighs only nine pounds.
- Ruggedly constructed with heavy leatherette covering, strong plastic handle, nickel plated hardware, and reinforced with metal clamps.

Windsor Tube Caddy may also be purchased outright for $14.95.

DON'T MISS THIS SENSATIONAL OFFER!

WRITE FOR ADDITIONAL TUBE TYPES AND PRICES. We also stock Special Purpose and Transmitting Tubes at similar savings! Dept. N-2.

25% Deposit with Order. All merchandise F.O.B. NYC. For orders less than $10, add $1 handling cost. Deduct 2% if full remittance accompanies order. All merchandise subject to prior sale and price changes without notice.

Windsor ELECTRONIC TUBE CO.
1515-N SHEEPSHEAD BAY ROAD, BROOKLYN 35, N. Y.

CODE SENDING SPEED RECEIVING



Be a "key" man. Learn how to send and receive messages in code by telegraph and radio. Commerce needs thousands of men for jobs. Good pay, adventure, interesting work. Learn at home quickly through famous Candler System. Qualify for Amateur or Commercial License. Write for FREE BOOK.
CANDLER SYSTEM CO.
Dept. 2-B, Box 928, Denver 1, Colo., U.S.A.

$$$$$$$$$$$$$$$$
WE PAY CASH
for all types of MILITARY ELECTRONIC EQUIPMENT
Top Dollar for:

- BC-348 RCVRS (Bonus on Q & R Models)
- ART-13 & any accessories
- BC-788 (Bonus on C Model)
- I-152 (Bonus on C Model)
- RADAR EQUIPMENT (Specify full name plate info)
- DIRECTION FINDING EQUIP. (Specify full name plate info)
- TEST EQUIPMENT (Specify full name plate info)

Plus anything you have not listed here. Send complete description of your equipment to:


V & H RADIO & ELECTRONICS
2033 W. Venice Blvd., Los Angeles 6, Calif.
Phone: REpublic 3-1127

RECORDING TAPE (Plastic Base)
40% OFF (NEW)
WASHINGTON, D. C. WHERE ELSE WOULD THERE BE MORE RED ∧ TAPE? *Magnetic*

- 1200 ft. plastic tape with plastic reel included.
- Each reel individually boxed.
- Choice of nationally famous top quality brands such as: Webcor (2806) 3.20; Reeves (SPN-12) 3.20; Audio (1251) 3.25; Scotch (111-A) 3.25; Panacoustic (711-A) 3.25; Irish, Professional grade (211 RPA) 3.20.
- FREE! A 7.95 tape carrying case included with purchase of 12 new tapes!

★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★

USED RECORDING TAPE (PLASTIC BASE)

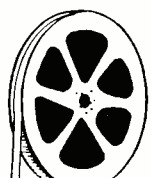

1.99 for 7"—1200 foot
.99 for 5"— 600 foot
.59 for 4"— 300 foot
.29 for 3"— 150 foot
Plastic reels included with all above sizes


New empty plastic reels in boxes for easy labeling. 3" 10¢; 4" 22¢; 5" 24¢; 7" 30¢; 7" Professional reel (21¼" hub) 45¢ ea. EMPTY BOXES: 3" 3¢; 4" 5¢; 5" 5¢; 7" 10¢ ea.

We carry new recorders, recording blanks, tape, tape recorders, etc. at large savings. PLEASE INCLUDE SUFFICIENT POSTAGE.

COMMISSIONED ELECTRONICS CO.
2S03 Champlain St. N.W., Washington 9, D. C.

www.americanradiohistory.com

BARRYMOUNTS

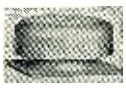

C-2045
C-2060
C-2070
C-2090

45¢ each
$35/100

UPRIGHT OIL CONDENSERS

CAP.	PRICE
220VAC/600VDC	
6.2	$1.29
15	3.49
330VAC/1000VDC	
15	$3.79
6	1.25
1000 VDC	
.5	$ .69
.5-.5	1.19
1	1.49
4-1.5	2.19
1.5	1.39
1500 WVDC	
4	$1.95
1.5	1.59
2	1.79
2000 WVDC	
1	$1.79
2500 WVDC	
.5	$2.98
4000 WVDC	
.15	$6.95
4800 WVDC	
.1-.1	$4.79
6000 WVDC	
.1	$3.69
115-.15	3.89
1.5	10.98
7000 WVDC	
.1-.1	$3.79
1	9.95
8000 WVDC	
.075-.075	$3.79
10K VDC	
.1	$8.95
15K VDC	
.0016	$7.95
16K VDC	
.015	$9.50
20K VDC	
.25	$17.50
25K VDC	
1	$85.00
.5	65.00

MOBILES! C. D. MEN! CAP!!

IDEAL DYNAMOTOR — CONVERTS EASILY TO SUPPLY UNIT DELIVERING

12 Volt Input: 610 V @ 150 MA; 325 V @ 125 MA
OR
6 Volt Input: 300 V @ 90 MA; 160 V @ 110 MA

Brand New with Conversion Data.....$3.75

DYNAMOTORS

TYPE	INPUT VOLTS	INPUT AMPS	OUTPUT VOLTS	OUTPUT AMPS	PRICE
DM 416	14	6.2	330	.170	$6.75
DM 33A	28	7	540	.250	3.95
BD AR 93	28	3.25	375	.150	7.50
23350	27	1.75	285	.075	3.95
B-19 Pack	12	9.4	275	.110	8.95
			500	.050	
DA-3A*	28	10	300	.260	6.95
			150	.010	
			14.5	5.	
S053	28	14	250	.060	3.95
PE 73 CM	28	19	1000	.350	22.50
BD 69‡	14	12.8	220	.08	12.95
D-402†	13.5	12.2	300	.200	
			8.8VAC		12.50
SP 175	18	3.2	450	.06	4.49
DM 25†	12	2.3	250	.05	6.95

‡ Less Filter
† Used, Excellent
* Replacement for PE 94.

INVERTERS

PE-218-H: Input: 25/28 vdc, 92 amp. Output: 115v. 350/500 cy 1500 volt-amperes. NEW.....$37.50

PE-206: Input: 28 vdc, 36 amps. Output: 80 v 800 cy, 500 volt-amps. Dim: 13"x5½"x10½". New $22.50

NAVY COR-211095: Input 22-30 VDC/75-60A.

OUTPUT: 115V/400 CY, 1 KVA/8.7A. RPM: 4800. With coupling provision for motor. Brand New. Original packing $150.00

SELENIUM RECTIFIERS

Current (Continuous)	18/14 Volts	36/28 Volts	54/42 Volts	130/100 Volts
1 Amp.	$1.35	$2.15	$3.70	$8.50
2 Amps.	2.25	3.60	5.40	10.50
2½ Amps.	....	....	6.00	13.00
4 Amps.	4.25	7.95	12.95	25.25
6 Amps.	4.75	9.00	13.50	33.00
10 Amps.	6.75	12.75	20.00	44.95
12 Amps.	8.50	16.25	20.50	49.00
20 Amps.	13.25	25.50	38.00	79.50
24 Amps.	16.25	32.50	45.00	90.00
30 Amps.	20.00	38.50	....	....
36 Amps.	25.00	48.50		* F. W. Bridge

INTERPHONE AMPLIFIER



Easily converted to an ideal Inter-Communications set for office, home or factory. Original. New w/conversion diagram..... $4.75

INTERPHONE TRANSFORMER SET

Rig your own interphone. Kit consists of 1-Input Transformer (Matches 4 or 6 OHM SPKR to Grid) and 1-Output Transformer (Matches 50L6, 35L6, 25L6, etc., to 4 or 6 OHM Speaker Set of 2 XMRS. ONLY..... $1.00

RECTIFIER TRANSFORMERS

Pri: 115V, 60 Cy. Sec: 28V/3.1A, 26V/8.4A 7.3V/14A $12.95

Pri: 210/215/220/225/230/235/240V, 60 Cy., 1 Phase Sec: 11/10/7.5/5VCT @ 35A.....$19.50

Pri: 115V 60 Cy: Sec: 8.1V @ 1.5A.....$1.39

Pri: 115V 60 Cy: Sec. 18.5V @ 5A.....$2.79

12-14V SUPPLY KIT

Delivers 12-14VDC at 3.5A from 115V, 60 cy., Kit contains 1—Transformer Rated 18.5V, 4A, 1—Selenium Rectifier, F. W. Bridge..... $6.35

Send M.O. or Check. Shipping Chgs. C.O.D.

COMMUNICATIONS EQUIPMENT CO.
131 Liberty St. Dept. N-2 New York City 7, N. Y.

a new 5600-ohm, ½-watt resistor, having longer leads. Cover the resistor with spaghetti. (The original 5600-ohm resistor may be used by splicing a wire to one lead in order to lengthen it.)

3. Remove the horizontal lock coil from the rear chassis apron by placing the fingers on the end of the coil form nearest the rear of the chassis, and pulling the coil toward the front. This leaves the slug and part of the assembly still attached to the chassis. Procure a metal shield can, preferably an i.f. can that is not made of aluminum, and slip this can over the slug as shown in the diagram. The hole through the top of the can should be 7/16 inches in diameter or larger.

4. Insert the lock coil through the shield can over the slug and back into its original assembly. Solder the shield can to the mounting bracket of the assembly, being sure to clean and tin thoroughly the surfaces to be soldered, to insure a good electrical connection.

5. It may be necessary to readjust the horizontal lock slug for optimum receiver operation.

CHASSIS 22C2 & 22E2

Ringing.

This effect, consisting of at least four tunable ghosts about ½ inch apart, may be caused by the 3rd i.f. transformer (T_{303}) being wired in backwards. The numbered terminals on the bottom of the transformer should be connected as follows:


Terminal #1 to the red "B—" wire going to the screen of the 3rd i.f. tube (pin 6 of V_{303}, 6AG5); terminal #2 to the cathode of the video detector tube (pin 3 of V_{3014}, 12AT7); terminal #3 to chassis ground; terminal #4 to the plate of the 3rd i.f. tube (pin 5 of V_{303}).

CHASSIS 22C2, 22E2 & 23A1

Snow in intermediate fringe areas.

To reduce snow (front-end noise) in intermediate fringe areas, reduce the tuner a.g.c. voltage to 1½ or 2 volts. To accomplish this, do the following:

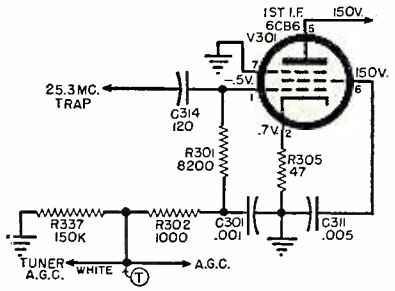1. Remove resistor R_{337} (150,000 ohms) and replace it with a 100,000-



ohm resistor and a 47,000-ohm resistor connected in series. Connect the 47,000-ohm resistor to chassis ground, and the 100,000-ohm resistor to R_{302}, 1000 ohms (test point "T"). (See accompanying diagram for original circuit.)


2. Remove the tuner a.g.c. lead (white) from test point "T," and connect it to the junction of the 100,000-ohm and 47,000-ohm resistors.

3. Bypass the tuner a.g.c. lead to chassis ground with a .005-μfd. ceramic condenser.

ALL-CHANNEL TUNERS

Poor performance.

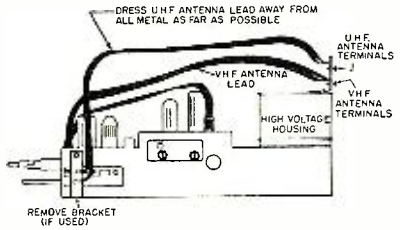This may be caused by the lead from the u.h.f. antenna terminals to the u.h.f. tuner being close to or touching the metal brackets of the rear picture-tube mount. This lead is purposely long, and acts as a quarter-wave trap at the mean frequency of the lower v.h.f. channels, and a three-quarter wave trap at the mean frequency of the higher v.h.f. channels.



Remove the back cover of the cabinet and check this lead to be sure that it is not close to any metal, and straighten it out if it is looped or doubled up.

While the back is off the cabinet, check the lead from the u.h.f. antenna terminals at the point where it is soldered to the side of the u.h.f. tuner. (See accompanying diagram.) Remove the metal bracket (if used) that covers the u.h.f. antenna connections.

—30—

SYLVANIA TV AWARDS

THE Sylvania Television Awards for 1953, established "to honor those who are advancing creative television technique," were presented recently at the Awards Announcement Dinner held at the Hotel Pierre in New York.

The 16 men and women who served on the awards committee were unanimous in their selection of Rod Steiger as the outstanding TV actor of the year for his performance in the title role of the drama "Marty." Mary Martin won an award for her individual pantomime on the Ford 50th Anniversary Show.

ABC won the network award for its presentation of the Coronation with BBC and CBC similarly honored for their cooperation in making the telecast possible.

A special award was given to the TV-Radio Workshop of the Ford Foundation for its outstanding contribution to the advancement of creative television technique.

Other award winners included "Ding Dong School," "Person to Person," "American Forum of the Air," "Dragnet," "Make Room for Daddy," and "What's My Line."

Individuals named for awards included Donald O'Connor, Leland Hayward, Clark Jones, Jerome Robbins, and Irving Gaynor Neiman.

Deems Taylor served as chairman of the awards committee and read the citations at the dinner.

This is the third year that Sylvania Electric Products Inc. has sponsored this award and hosted the presentation dinner. —30—

www.americanradiohistory.com

U.H.F. Measurements

(*Continued from page 49*)

should be shorted with a piece of copper or other good u.h.f. shorting device to produce strong line reflections. Use a marker generator to produce pips on the response curve and measure the frequency at two adjacent peaks. The frequency change between peaks is Δf.

$$\textit{Velocity of prop. constant} = \frac{L \times \Delta f}{492}$$

where L is the length of the line in feet, and Δf is the frequency difference from peak-to-peak, or valley-to-valley, in megacycles. Multiplying the velocity of propagation constant by 100 gives the velocity of propagation down the line as a per-cent of the speed in air. If the propagation constant of a certain line is 0.6, then a full wavelength on the line will be only 0.6 wavelength for the same distance in air.


A U.H.F. Sweep Generator

Fig. 9 is the block diagram of a u.h.f. sweep generator such as can be used for the measurements described in this article. The heart of the r.f. section of this generator is a modified form of the new *Philco* u.h.f. tuner. The r.f. sweep oscillator circuit utilizes the new 6AF4 u.h.f. triode. It operates in a simple capacitance-tuned circuit which provides continuous tuning over the entire u.h.f. television band. Both high- and low-frequency compensation are used to maintain more uniform oscillation over the band.

Sweep action is provided by the use of a mechanical "wobbulator" which gives the convenient 60-cycle sine-wave sweep. A silver-plated plunger is made to move inside the oscillator "hairpin loop" or coil, in a way that will give best linearity of scope deflection with a minimum of amplitude modulation (variation of sweep amplitude as indicated by the vertical deflection of the scope).

The automatic leveling circuit serves to flatten the output of the generator and thus avoid any appreciable amplitude modulation. It not

Fig. 9. Block diagram of the Philco model G-8002 u.h.f. sweep generator.

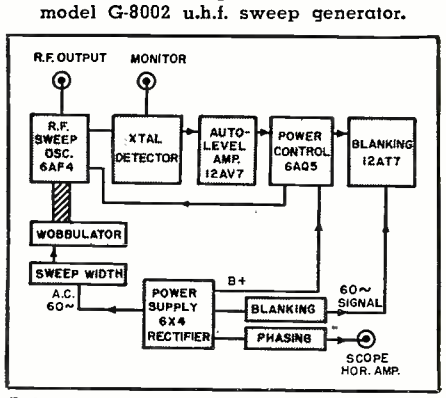

The NEW BROOK



MODEL 22A Is Creating A Sensation!

- so dramatically different, it's a new concept in amplifier design.
- so functionally compact, it simplifies any installation.
- so exceptionally attractive, it captivates at first glance.
- But, FOREMOST, so genuine in HIGH QUALITY AUDIO PERFORMANCE, despite it's unprecedented low cost.


10-watt single-chassis power and pre-amplifier combination

Dept. RT-4

SEE and HEAR the New Model 22A at your local dealer's Sound Department soon. A listening treat awaits you. Write today for free technical information.

BROOK ELECTRONICS, INC.
34 DeHART PLACE, ELIZABETH 2, N.J.
First in the High-Quality Audio Field Since 1934

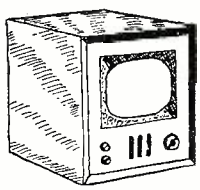WHILE THEY LAST!
10" TV REMOTE "SLAVE" SETS



HERE'S YOUR CHANCE TO GET THAT EXTRA SET FOR PLAYROOM, BEDROOM, KITCHEN, ETC.!!
These are COMPLETE, OPERATING slave units. Hook up to any standard TV receiver (only 4 soldered connections) to reproduce any tuned TV channel. COMPLETE SCHEMATIC & HOOK-UP DATA SUPPLIED. Operates on 110V.DC; AC conversion data included.
FEATURES: • 19 TUBES including 10" PICTURE TUBE—(10BP4). ALL 90 DAY GUARANTEED. • H.V. OSC. POWER SUPPLY—detachable unit. • 4" HVY. DUTY PM SPEAKER. • MAJOR STANDARD PARTS INCLUDE: Def. Yoke, Focus Coil, Horiz. & Vert. Outputs, two 10H-100ma Chokes, 150ma Sel. Rect., Electrolytics, Controls, etc. • HANDSOME WALNUT VENEER & LEATHERETTE CABINET (20½"x17"x14½"). !! PARTS ALONE WORTH SEVERAL TIMES THE PRICE!! Perfect condition—used. Shipped Railway Exp. **$23.95**

POWERFUL ALNICO "MAGNETRON" MAGNET—Approx. 2000 gauss. 8¼"x5⅝"x2¾". Poles 1⅝" O.D. Gap 1½". Shpg. wt. 18 lbs. **$24.95**
5" C.R. TUBE FRONT BEZEL—black crackle. .98
5" SCOPE VISOR—mouled vinyl ..... .98
5¼" CLEAR CONVEX GLASS LENS—39¢; 6/1.98
RADIO HARDWARE TREASURE—FULL LB. CAN of: NUTS, SCREWS, WASHERS, LUGS, EYELETS, ETC. .....89¢ lb.; 3 lbs./2.49
ATTENTION SOUND MEN!! . . . FAMOUS RACON RADIAL RE-ENTRANT HORNS (Mod. SR-35R). Weatherproof alum. deflectors project hi-fidelity sound evenly over 360°. Takes any RACON driver unit. "U" mtg. brkt. 16" L. (48" acoust. path). 17" O.D. Shpd. exp. (List $47.50). **$18.95**
BRAND NEW—ONLY .....
25 WATT RACON DRIVER UNIT for above—Powerful ALNICO V magnet. Weatherproof alum. shell. 15 ohm imped. 4" O.D. Shpg. wt. 5½ lbs. BRAND NEW $14.95

STOP!! LOOK!! SAVE!!—with the NEW "JUMBO RADIO-ELECTRONICS PARTS KIT"—CHOCK-FULL OF: COILS, CONTROLS, SOCKETS, WIRE, RESISTORS, CONDENSERS, PHOTOFACT, TV PARTS & DIAGRAMS, ETC., ETC. Shpg. wt. 20 lbs.—BETTER THAN EVER!! . . . **$3.95**

POWER TRANSFORMER (Stancor)—117V.Pri.; Sec:6V/2A, 6V/1A,5V/6½A, 220V/50ma. 6¾"x5"x4". Shpg. wt. 14 lbs. $4.50
25W-250 OHM POT.—¼" shaft. Tap at 125 ohms. Clarostat, ceramic, new. 49¢; 12/5.00
2000 LAB. POTENTIOMETER (DeJur)—5% accuracy. W.W. 3"O.D., bakelite shaft. ea. 98¢; 6/5.00

"DIRECT FACTORY SPEAKER REPAIRS SINCE 1927" Min. order $3.00. 20% deposit req. on all C.O.D.'s. Full remittance with foreign orders. Please add sufficient postage—excess refunded.

EDTONE Radio Corp. 67 Dey Street New York 7, N.Y.

New Guaranteed **TUBES** Standard Brands

0A2	$0.90	3FP7	1.75	802	2.95
0A3/VR75	1.10	3GP1	3.95	803	3.65
0A4G	1.80	3HP7	3.95	RK4	10.95
0B2	1.10	4C27	12.50	805	3.25
0C3/VR105	.95	4C28	35.00	807	1.65
0D3/VR150	.85	4C35	19.50	811A	2.90
1A3	1.00	4-125A	22.50	812	3.50
1B23	8.95	4X150A	27.50	813	10.95
1R3A	5.50	5BP1	4.50	814	2.95
1D21	12.50	5C22	37.50	827	8.95
1D21/5N4	4.50	5FP7	1.95	829B	8.95
1N21B	2.50	5R4GY	1.25	830B	2.75
1N22	1.25	5R4WGY	2.75	832A	8.95
1N23	1.25	6AK5	.89	833A	25.95
1N23B	1.25	6AL5W	1.50	836	3.50
1N34A	.75	6AS7G	3.50	837	1.45
1N38	1.50	6K4	3.50	866A	1.50
1N68A	1.25	15E	1.75	872A	2.95
1N69	2.15	15R	.79	884	1.25
1N69	.68	FG57	14.95	931A	5.50
2C39	12.50	RK60/1641	2.25	954	.33
2C40	8.50	100TH	9.50	955	.49
2C51	6.25	250TH	16.50	956	.49
2D21	1.25	304TL	7.95	957	.49
				958A	.69
				959	1.25
				992	.29
				1005	.68
				CK1006	1.15
				1616	.60
				1625	.79
				1629	.29
				2050	1.50
				2051	1.10
2E22	2.75	307A/RK75	3.95	5670	3.50
2E24	4.65	393A	6.95	5687	3.75
2E25	4.50	394A	3.95	5702	2.85
2K25	28.50	446A	1.19	5718	5.95
2K28	28.50	703A	4.50	5726	2.00
2K45	110.00	705A	1.50	5814	1.75
2K48	99.50	707B	13.95	5844	4.50
3A4	.75	715B	7.50	6012	1.95
3A5	1.25	715C	14.95	6020	1.95
3B28	3.50	717A	.98	6939	1.25
3B24/24G	1.50	723A/B	16.95	N025A	4.95
3C33	12.50	724B	2.75	8001	1.25
3D22	12.50	726A	12.00	9002	.98
3E29	11.85	801A	.49	9003	1.50

SPECIAL! Vacuum Capacitors

50-15	$ 7.50
50-32	12.50
12-32	10.00
100-20	14.50

Complete line of Receiving Tubes. Thousands of other types of Transmitting Tubes. If you don't see it, WRITE. Prices subject to change without notice. Californians add sales tax. Add postage to order.
Minimum order—$3.00.

VEEDER ROOT COUNTER

5 figure. Adds ten for each revolution of shaft in one direction; subtracts ten for each revolution in opposite direction. Size ¾"x¾"x1" dovetail mounting; lever arm removable.



ONLY **1.25** ea.
Quantity Discounts

FREE! Write for new complete Catalog just off presses.

Jsh SALES CO. ELECTRONICS Dept. R-A 7552 Melrose Ave. Los Angeles 46, California

www.americanradiohistory.com

TO THE

E. E.

OR

PHYSICS

GRADUATE

WITH EXPERIENCE IN

RADAR

OR

ELECTRONICS

HUGHES RESEARCH AND DEVELOPMENT LABORATORIES ARE ENGAGED IN A CONTINUING PROGRAM FOR DESIGN AND MANUFACTURE OF ADVANCED RADAR AND FIRE CONTROL SYSTEMS IN MILITARY ALL-WEATHER FIGHTERS AND INTERCEPTORS.

YOU WILL serve as technical advisor in the field to companies and government agencies using Hughes equipment.

TO BROADEN your field of experience in radar and electronics you will receive additional training at full pay in the Laboratories to become thoroughly familiar with Hughes radar and fire control equipment.

AFTER TRAINING you will be the Hughes representative at a company where our equipment is installed; or you will direct operation of Hughes equipment at a military base.

THE GREATEST advancements in electronics are being made in this sphere because of military emphasis. Men now under 35 years of age will find this activity can fit them for future application of highly advanced electronic equipment.

HUGHES

RESEARCH AND DEVELOPMENT LABORATORIES

SCIENTIFIC AND ENGINEERING STAFF

Culver City, Los Angeles County, Calif.

Assurance is required that relocation of the applicant will not cause disruption of an urgent military project.

only holds the r.f. output constant during sweep, but it also maintains a practically flat output over the entire u.h.f. band. The circuit works as follows:

The r.f. output of the sweep oscillator is monitored by the u.h.f. crystal detector, and the detector output voltage is amplified by a d.c. amplifier, which consists of the two sections of a 12AV7. The amplified d.c. voltage from this tube is used to control the current flowing through the 6AQ5 power control tube. The current through the 6AQ5 is also the current for the sweep oscillator. Thus, whenever the oscillator output tries to fall off, the output of the crystal starts to decrease and the amplified d.c. bias applied to the 6AQ5 grid also decreases (becomes less negative). This allows the 6AQ5 plate current to increase which, in turn, increases the r.f. sweep oscillator current and plate voltage. Thus, a tendency of the r.f. output to fall off is counteracted by a rise in oscillator plate voltage, with the result that the oscillator output level remains practically constant.

The 6AQ5 and d.c. amplifier also provide a means for manual control of the r.f. power output. The r.f. power control of this circuit serves as an electronic attenuator when low-level outputs are required. This feature can best be appreciated if one has attempted to make very low level measurements at u.h.f., only to find that the high power output of the generator produces enough signal leakage to make true readings a somewhat difficult procedure.

A third function of the 6AQ5 is to blank the r.f. sweep oscillator during the return trace on the scope. The 12AT7 blanking tube, operating on a 60-cycle signal from the power supply transformer, is connected to the 6AQ5 screen grid so that the 6AQ5 plate current flowing to the sweep oscillator will be reduced during blanking or retrace time. In this way, the 6AF4 r.f. oscillator is made to stop oscillating during the return time. This permits the vertical deflection of the scope to drop to zero and, in this way, the return trace is on the zero signal line. The effect is the formation of a base line when the blanking and phasing controls are properly adjusted. The blanking control contains an "on-off" blanking switch.

The phasing control is built into the sweep generator and operates in conjunction with the scope connector to provide the 60-cycle horizontal sweep for the oscilloscope. The phasing control permits adjustment of the scope sweep voltage to give the correct phase or timing with respect to the actual sweeping of the r.f. oscillator frequency.

A full-wave 6X4 rectifier is used in the power supply. The a.c. line cord is very carefully filtered with a low-pass u.h.f. filter network. A low-pass filter is also built into the oscilloscope sweep circuit to minimize leakage from the scope connector. —30—

Technical BOOKS

"HOW TO TROUBLESHOOT A TV RECEIVER" by J. Richard Johnson. Published by *John F. Rider Publisher, Inc.,* New York. 121 pages. Price $1.80. Paper bound.

This is a specialized book on a specialized topic and service technicians seeking specific data on troubleshooting will find a boon in this little handbook.

Written in easy-to-read, down-to-earth style, the author has presented his material in logical progression, starting with available service data and how to use it effectively through TV receiver sections, tools and equipment, preliminary observations and checks, use of test patterns and crosshatch patterns in troubleshooting, controls and their adjustment, tubes and tube checking, the dead receiver, interpreting raster on picture distortion, and sound troubles.

The text material is lavishly supplemented by line drawings, photographs, and schematic diagrams. The text itself does not deal with troubleshooting specific receivers but instead covers the techniques applicable to all troubleshooting.

Those beginning their servicing careers will find this book especially helpful while old timers at the game can use it to speed their troubleshooting tasks.

* * *

"TRANSISTORS AND THEIR APPLICATIONS" by Louis E. Garner, Jr., Published by *Coyne Electrical School,* Chicago. Distributed by *Howard W. Sams Company,* Indianapolis. 103 pages. Price $1.50. Paper bound.

The name of Garner is so familiar to readers of this magazine in connection with transistor circuitry and equipment using transistors that the mere mention of the fact that he has now written a book on the subject should suffice.

This little book is divided into ten chapters which deal with the history of the transistor, transistor action, characteristics, amplifier and oscillator circuits employing transistors, special transistor circuits, components designed to be used with transistors, the care and servicing of transistors, practical transistor circuitry, and reference data.

The author has included a representative selection of transistor circuits for various applications. Complete parts lists accompany these diagrams to permit the reader to build the equipment.

For those interested in workable "projects" in the transistor field, this book should be of considerable interest.

* * *

"PRINCIPLES OF ELECTRONICS" by L. T. Agger. Published by *St. Martin's Press,* 103 Park Ave., New York. 333 pages. Price $3.75.

This book has been written expressly for those whose primary interest is in electrical engineering but who wish to

www.americanradiohistory.com

NEW Address! Catalogue! Merchandise! Low, LOW Prices!

12 V. 35 AMP DELCO-REMY MOBILE GENERATOR
Fair, used cond. Never before sold at this sensationally low price. Stock up! **$3.95**

SCR-518 UHF ELECTRONIC ABSOLUTE ALTIMETER. Terrific for conversion to 420 MC and citizen's bands. Consists of transmitter, receiver, indicator, power supply, control boxes, cables with plugs, mounts, etc. Complete and BRAND NEW. Never before priced so low. ONLY..... **$19.95**

WARD-LEONARD RHEOSTAT. 12.5 ohms, 10 amps. 600 V. Maximum. Excel. cond. $1.29

RADAR CONTROL BOX
Consists of one 0-25 ma, 2½ in. round meter. PLUS a raft of miscellaneous parts, NEW. Has 400 cycle variac. SPECIAL SALE PRICE **$5.50**

RESISTOR ASSORTMENT. 100 for only..... 98¢
BARGAIN ASSORTMENT: Rheostats, pots, volume controls. A $5.00 value, 10 for..... 99¢

APS-13 "Tail End Charley" TRANSCEIVER 420 MC. UHF. 5 stages of 30 MC. IF amplifier. Complete R.F. section & schematic less tubes & dynamotor. Good cond. $4.95

MINIATURE 6 V. WET CELL BATTERY. With 6 V. rev. DC motor. F.B. for R/C boat. 3½x2½x1¾". Battery less motor...$1.49 With motor...$2.99

SLASH PRICE TUBE BUYS!
6BP4...$2.95 6L6G...$ .49 6AK5...$ .60
6SN7... .75 6AC7... .62 6H6.... .49

HEAD AND CHEST SETS: Many-mile coverage. Light weight. Each....$3.50 PER PAIR ONLY....$5.95

ARR-1 RECEIVER: For conversion to 220 MC. With schematic. See Jan/49 Radio News for conversion. Good condition. ONLY..... $3.99

SUPREME MODEL 600
Illuminated TUBE & SET TESTER
Tests all latest tubes. Seven in. multi-tester tests DC 0-2,500 V. in 7 ranges. AC 0-2,500 V. in 6 ranges. DC current 7 ranges: 0-1,000 microamps, 0-1,000 ma., and 0-10 amps. Ohmmeter 3 ranges: 0-20 megohms. Output meter and battery tester which tests radio batteries under load. Comes with test leads and gray metal Hammerloid case. Size: 11x15x6¾ in. Factory guarantee includes 1 year of free tube setting service. BRAND NEW IN ORIGINAL BOXES. You know this set is designed to net for $117.50. While they last, our Price—the country's lowest, only ... **$59.50**

HS-33 LOW IMPEDANCE HEADSETS. Used...$1.99
O-1 MIL METER. 2" panel type. New boxed. Ea. $3.95

SCR-183 12 V. RECEIVER & TRANSMITTER! Covers aircraft, marine and ham bands! Complete with 2 coils, control boxes, tuning head, flex cable, rack and shock mount! Plus 12 V. Dynamotor! Individual parts worth $25.35. Approx. 25w. output. EXCEL. COND., COMPLETE! Plus schematic. Never before sold at this sensationally low price. NEW DRASTIC REDUCTION **$12.95**

ARC-5 OR 274-N TRANSMITTERS
All pre-tested & guaranteed!
2.1-3 mcs. Brand new $19.95
3-4 mcs. With tubes 25.00
4-5.3 mcs. With tubes 8.95
5.3-7 mcs. With tubes 6.95
7-9.1 With tubes 14.50
7-23 ARC-5 VHF TRANSMITTER. For C.A.P. with tubes 100-156 MC. Crystal control 29.95

ARC-5 OR 274-N RECEIVERS
Equipped with Tuning Knobs
.19-.55 kc. $19.95
1.5-3 mcs. Like new 24.50
3-6 mcs. Brand new 22.50
3-6 mcs. With tubes 10.95
6-9.1 mcs. With tubes. Used 7.95
New 22.50
6-9.1 mcs. Used. Less tubes 6.95
BC-456 274-N Modulator. Less dynamotor. Excel. cond. 3.95
12 V. COMMAND RECEIVER DYNAMOTOR. New 12.95
Plus All Accessories Needed for Above. Conversion dope available on request.

Write Today—and ask for FREE CATALOGUE!

All orders F.O.B. Los Angeles. 25% deposit required. All items subject to prior sale. Note New Address. Dealer Inquiries Invited.

COLUMBIA ELECTRONIC SALES
2251-53 W. Washington Blvd., Los Angeles 18, Calif.
Come in and visit our new, larger centrally located warehouse-store!

HEATHKIT
INSTRUMENTS ASSEMBLED & TESTED

Take advantage of Heathkit's engineering skill and our construction ability, at far less than ready-made instruments of equal calibre or quality.

A-9A Hi-Fi Amplifier $49.50
TC-2 Tube Checker 44.50
GD-1B Grid Dip Meter 28.50

Please include postage. (We refund overpayments.) Any of the other Heathkit instruments at comparable prices. Workmanship fully guaranteed. Write for full details.

R. A. MOOG CO. 51-09 PARSONS BLVD. FLUSHING, NEW YORK

have more than a nodding acquaintance with electronics and common vacuum-tube circuitry.

The author has assumed that the users of this text have a basic knowledge of electricity and electrical principles and, as a result, introductory material of a general nature is completely lacking. The book opens with a discussion of electron dynamics and carries through eighteen chapters devoted to such subjects as thermionic emission, conduction through gases, diodes, rectification, triodes, voltage amplification, multi-electrode tubes, multi-stage amplifiers, tuned amplifiers, power amplification, gas-filled tubes, controlled rectification and inversion, oscillators, modulation and demodulation, cathode-ray tubes, and photoelectricity.

For the student using this as a home-study text, a series of test questions has been provided to enable him to check his grasp of the subject matter. Since the book is written by an Englishman and published in England, the terminology is, of course, British usage. American readers should experience no difficulty in making the necessary transitions. —30—

PHOTO CREDITS

Page	Credit
35	Overhead Door Company
39	Jensen Mfg. Co.
48, 49, 78	Philco Corporation
50	Audio Instrument Co.
52, 55, 69	Radio Corporation of America
57, 58, 60, 144, 146, 188	Admiral Corporation
66, 67	Hermon Hosmer Scott, Inc.
68	International Resistance Company
104	Channel Master Corporation
112	Official U.S. Navy Photo
120	Japan Amateur TV Club
154	Stewart-Warner Corporation
184	RETMA

ERRATA & ADDENDA

There are several errors in the parts list accompanying the article, "A New V.F.O.", which appeared in the November issue. L_1 should be #32 s.c.c. closewound on a 5/8" dia. form, 1½" winding length. L_2 should be 68 turns of #26 en. closewound on 1½" dia. form. C_7, C_8, C_{12}, C_{14}, C_{18} should be .002 μfd. or larger not .002 μμfd. as listed.

* * *

The Thordarson choke T14C70 listed in connection with the article "Amplifier Features Phase Shift for 3D Effect" (November 1953 issue) is no longer available. A new and improved version of this choke is available as part T20C74.

* * *

In the article "A Small-Package Modulator" appearing in the November issue the driver transformer, T_2, should have a center tap in the secondary and this center tap should be grounded.

* * *

Hans Schoeneich has sent us a tip to pass along to those building the "Jam-Jar Rectifier" described in the December issue. He suggests that in order to prevent the borax solution or electrolyte from creeping up and over the jar and to prevent evaporation that a thin layer of mineral oil should be added to the top of the solution. He also adds that distilled water is better than tap water for mixing the electrolyte because of the impurities in most tap water.

* * *

In the listing of "Television Stations on the Air" which appeared in the January issue, the listing for KFXD-TV (Nampa, Idaho) and WBES-TV (Buffalo, N. Y.) should be removed. The Nampa station has dropped plans to go on the air and the Buffalo station has returned its license to the FCC and has discontinued operation.

TRANSVISION

makes this greatest of TV offers—backed by

MONEY-BACK GUARANTEE:

$88 TV SERVICE INSTRUMENT VALUE FOR— **$39.95**

NEW **TV Component Tester** performs functions you've always wanted. Look what you get:—
FLYBACK TESTER, value..... $39.00
SELENIUM RECTIFIER TESTER, val. 29.00
CRT TESTER and REACTIVATOR, val. 20.00
Total Instrumentation, value..... 88.00
ALL 4 in 1 great instument, net..... 39.95



NEVER BEFORE SUCH GREAT VALUE. For only $39.95 you get 4 testing-and-repair instruments all in one! Compact, weighs only 3 lbs. Does things never been done before! Pays for itself quickly. Prove it yourself—

TRY IT for 10 DAYS
on Money-Back Guarantee:

10-DAY TRIAL: Try this Transvision TV COMPONENT TESTER for 10 days. Then, if you are not 100% satisfied, you may return it. Your purchase price, less 10% (our cost of handling and re-packing) will be promptly refunded.

TRANSVISION, INC. • NEW ROCHELLE, N. Y.

RUSH THIS COUPON NOW

TRANSVISION, INC.
DEPT. RN-24 NEW ROCHELLE, N. Y.
☐ Send____ TV COMPONENT TESTERS @ $39.95.
☐ Enclosed find $____ deposit. Balance C.O.D.
☐ Enclosed find $____ in full.
I accept your 10 Day Trial terms.
Name____
Address____
City____ State____
My Jobber is____

JOBBER INQUIRIES INVITED

www.americanradiohistory.com

WORLD'S LARGEST MANUFACTURER OF CUSTOM BUILT TELEVISION

MATTISON

SILVER ROCKET 630 CHASSIS

Featuring Syncromatic Tuning


NO DRIFT UHF-VHF-DX

ONLY THE MATTISON 630 ELIMINATES DRIFTING APART OF PICTURE AND SOUND ON UHF, VHF and DX RECEPTION. SELECT YOUR CHANNEL . . . SOUND IS AUTOMATIC. (Syncromatic tuning is an exclusive Mattison 630 Circuit)

Tube Complement:
29 tubes
3 rectifiers
1 CRT

SILVER ROCKET
630 Chassis with built in UHF Tuner

33

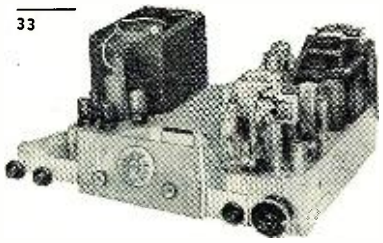

All Channel UHF Tuner


- UHF Cascode I.F. amplifier adds additional I.F. stage. Very important because UHF transmitters operate with moderate power and RECEIVER must be sensitive to give top notch UHF performance.

SILVER ROCKET 630 CHASSIS • with TUNEABLE • BUILT-IN BOOSTER for Better DX Reception

Tube Complement:
28 tubes
3 rectifiers
1 CRT

Select Your Channel . . . SOUND IS AUTOMATIC!

32

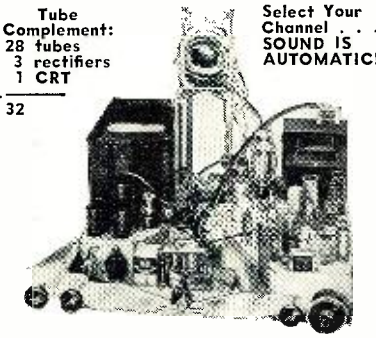

All Channel Booster

- Broad band single knob control pre-amplifier built in to eliminate long leads which may cause regeneration and attenuation of signal.
- **ONLY THE MATTISON 630 CHASSIS HAS AN ALL CHANNEL TUNEABLE BUILT-IN BOOSTER THAT INCREASES SIGNAL STRENGTH UP TO 10 TIMES.**

ALL CABINETS MADE IN MATTISON'S OWN CABINET FACTORY. AVAILABLE IN EVERY FINISH AND STYLE. WRITE FOR COMPLETE CATALOG.

DEALERS! SERVICE DEALERS! Here is your opportunity to become the "important" TV Dealer in your area for THE FINEST CUSTOM-BUILT LINE OF TV RECEIVERS. **FREE!!** Write for Mattison's merchandising portfolio explaining the "UNASSEMBLED PLAN" and "$1,000,000 FLOOR PLAN."

MATTISON

Manufactured with integrity

When you buy from Mattison you need only one source of supply! You can buy a Mattison Chassis, a Mattison Cabinet or a complete Mattison TV Set!

Mattison Television & Radio Corp.
10 West 181st St., Dept. RN, N. Y. 53, N. Y.

INDEX OF Advertisers

FEBRUARY 1954

ADVERTISER	PAGE
Aaron Electronic Sales	186
Ace Electronics	136
Airex Radio Corp.	174
All Channel Antenna Corp.	107
Allied Radio Corp.	9
Altec Lansing Corp.	146
American Phenolic Corporation	93
American Radio & Television Co.	143
Amplifier Corp. of America	114
Angle Genesse	142
Arkay Radio Kits	182
Arrow Sales Inc.	171
Asche Radio Company, Walter	109
Associated Industries	188
Atlas Sound Corp.	126
Audel Publishers	138
Baltimore Technical Institute	150
Belden	103
Bell Telephone	28
Blonder Tongue Labs.	157
Brook Electronics Inc.	191
Burstein-Applebee Co.	135
CBS Hytron	7
C & H Sales	184
Candler System Co.	189
Capitol Radio Engineering Institute	153
Centralab	24, 101, 118, 124
Central Tech.	19
Century Electronics Co.	130
Channel Master Corp.	30, 31
Cisin, H. G. Publisher	120
Cleveland Institute of Radio Electronics	21
Collins Audio Products Co., Inc.	165
Columbia Electronic Sales	193
Commercial Trade Institute	182
Commissioned Electronics Co.	189
Communication Equipment Co.	190
Concord Radio	94
Corona Radio & TV Co.	177
Coyne School	102
Davis Electronics	126
De Forest's Training, Inc.	5
Desco	174
Douglas Institute	182
Dumont Laboratories Inc., Allen B.	3rd Cover
Editors & Engineers Ltd.	98
Electronic Chemical Corp.	106
Electric Instrument Co., Inc.	34, 130, 158, 182, 191
Electro Voice	8
Erie Resistor Corporation	108
Excelite	143
Fair Radio Sales	169
Falcon Electronics Company	10, 11
Federal Telephone & Radio Company	117
Fenton & Company	179
Fisher Radio Corporation	18, 119, 151
G & G Radio Supply Co.	164
G & H Wood Products Co.	106
G. L. Electronics	178
General Cement Manufacturing	79
General Electric Co.	75, 155
Good, Inc., Don	181
Greenlee Tool Co.	195
Hallicrafters	25, 136, 150, 168, 183, 185
Hario Sales Co.	152
Harvey Radio Company	154
Heath Company	80 thru 91
Henshaw Radio Supply	194
Hughes Research & Development Laboratories	192
Indiana Technical College	183
Institute of Radio Engineers, The	133
Instructograph Company	174
International Correspondence Schools	13
International Rectifier Corporation	112
International Resistance Co.	6
Jensen Industries, Inc.	114
JFD Mfg. Company, Inc.	27
J. J. Glass Electronics Co.	150
Jones & Laughlin	166
JSH Sales Co.	191
Kay-Townes Antenna Co.	96, 97
Kester Solder Company	102
Krylon	136
Lampkin Laboratories	152
Leader	115
Leeds Co.	184
Leotone Radio	191
Liberty Electronic Co.	174
Littelfuse, Inc.	95
Loris Sales	181
MacMillen Company	182
Mallory, P. R.	4th Cover
Mattison Radio & Television Corporation	194
McConnell's	162, 182
McGraw-Hill Book Company, Inc.	162
McIntosh	159
Midwest Radio & Television Corp.	113
Miles Reproducer Co.	182
Milwaukee School of Engineering	140
Moog Co., R. A.	193
Mosley Electronics, Inc.	142
Moss Electronics Distributing Co., Inc.	129
National Electronics of Cleveland	114
National Radio Institute	99, 100
National Schools	23
Newark Surplus Materials	160
New Jersey Television Supply Co.	132
Offenbach-Reimus	181
Partmart	172
Peak Electronics, Inc.	162
Perma Power Company	70
Photocon Sales	126
Pickering & Company Incorporated	3
Platt Electronics Corp.	156
Polytech	160
Premier Radio-TV Supply	141
Prentice Hall, Inc.	152, 193
Progressive Edu-Kits, Inc.	176
Pyramid Electric Company	12
RCA Institutes, Inc.	121, 168
RW Electronics	123
Radiart Corporation	32, 33
Radio City Products Co., Inc.	187
Radio Corporation of America	125
Radio Craftsmen, Inc.	128
Rad-Tel Tube Co.	147
Radio-Television Training Association	29
Rauland	138
Radio Receptor Co., Inc.	143
Radio Shack Corporation	163
Raytheon Company	2nd Cover
Reeves Soundcraft Corp.	137
Rek-O-Kut Co., Inc.	177
Reliance Merchandising Co.	148
Rider Pub., Inc., John F.	142, 150
Rinehart Books	110, 111
Rohn Mfg. Co.	175
Sams & Co., Inc., Howard W.	104, 116
Sarkes-Tarzian, Inc.	134
Sleeper, Milton	167
Sonatone	26
Soundtronics	174
Southern Engineering	174
South River Metal Products Co., Inc.	98
Sprague Products Co.	17
Sprayberry Academy of Radio	127
Stan Burn Radio & Electronics Co.	130
Standard Electrical Products	158
Standard Transformer	185
Steve-El Electronics Corp.	122
Stevens Walden, Inc.	160
Stromberg Carlson	173
Stuart Electronic Distributors, Inc.	175
Sun Parts Distributors, Ltd.	132
Superior Instruments Co.	108
Superex Electronics	122
Supreme Publications	161
Sylvania Electric Products, Inc.	109, 139
"TAB"	196
Tallen Co., Inc.	142
Tech-Master Products Co.	98
Television Communications Institute	195
Terado Company	16
Transamerica Electronics	138
Transvision, Inc.	24
Trio Manufacturing Company	14, 15
Triplett Electrical Instrument Co.	20
Tri-State College	185
Tung-Sol Electric, Inc.	131
Turner Company	180
United Catalog Publishers, Inc.	122
University Loudspeakers, Inc.	168
Utah Radio Products Co.	173
V & H Electronic Industries, Inc.	189
V-M Corporation	144
Valparaiso Technical Institute	177
Van Nostrand, D.	170
Waldom Electronics, Inc.	102, 132
Walsco Electronics Corporation	77
Ward Products Corp.	105
Weller Electric Corp.	183
Western Electronics Co.	182
Western Television Institute	106
Westinghouse Electric	22
Wholesale Radio Parts Co., Inc.	161
Windsor Electronic Tape Co.	189
Zingo Products	182

When Answering Advertisements Say You Saw It In RADIO & TELEVISION NEWS



RADIO SERVICEMEN!
Write for SENSATIONAL CATALOG
HENSHAW RADIO SUPPLY
3619 TROOST KANSAS CITY, MO.

www.americanradiohistory.com

Classified

Rate 50c per word. Minimum 10 words

RADIO ENGINEERING

COMPLETE radio, electronics theory & practice: television; broadcasting; servicing; aviation, marine, police radio. 12 or 18 months. Catalog. Valparaiso Technical Institute, Dept. N, Valparaiso, Ind.

FOR SALE

FOUR new TAJ-19 GE Transmitters complete—$495.00. New under water ranging & sound equipment—no reasonable offer refused. 7 used 1 KW Ham Transmitters and other gear, Federal BC-325-C Transmitter—$795.00. Write for more information and list. Radio & Television Supply Co., PO Box 201, 717 Bank St., Decatur, Ala.

REVOLUTIONARY New Type television antenna solves reception problems. Guaranteed. Derr, 1018 Taylor, Vallejo, Calif.

5 LB. mix latest pigtail types, resistors, condensors, micas ceramics, electrolytics, tubulars, etc. Every piece new, usable, some short leads. $5.00 Prepaid. Cagan, Box 1152, Rochester, N. Y.

CIRCUIT Diagrams will save your precious time. Radio $1.00, Television $2.00. Give make and model. Carleton Radio, 39 Daniel, East Hartford 8, Conn.

DIAGRAMS—Radio $1.00; record changers, recorders $1.25. Television with service data $2.00. Where model unknown, give part numbers. Kramer's Radio Service, Dept. S53, 36 Columbus Ave., New York 23, N. Y.

TUBES and equipment bought, sold, and exchanged. For action and a fair deal, write B. N. Gensler, W2LNI, 136-F Liberty, New York 6, N. Y.

TAPE Recorders, Tapes, Accessories. Unusual Values. Dressner, 624-R East 20th St., N.Y.C. 9.

FREE, Bargain List, tubes bought, sold. Write Mark, Box 14, New York City 72.

ALUMINUM tubing, angle and channel, plain and perforated sheet. Willard Radcliff, Fostoria, Ohio.

AUTO radios, all models, best brands. Wholesale. Free catalog. "Radio Frank," 14456 Michigan, Dearborn, Mich.

FREE: Get our monthly electronic lists. Dick Rose, Everett, Wash.

WANTED

AN/APR-4, other "APR-," "ARR-," "TS-," "IE-," ARC-1, ARC-3, ART-13, everything surplus; Tubes, Manuals, Laboratory equipment. Describe, price in first letter. For Sale: Reconditioned Watthour Meters, four for $10.00. Engineering Associates, 434 Patterson Rd., Dayton 9, Ohio.

WILL buy all ART-13/type T-47A $200.00; ART-13/type T-47, $150.00; BC-348 unmodified $65.00, BC-348 modified $50.00; APN-9 $200.00; ARC-3 complete $600.00; R77 Receivers $300.00; ARC-1 $300.00; BC-312 $60.00; BC-342 $60.00. Ship via Express C.O.D., subject to inspection to: H. Finnegan, 49 Washington Avenue, Little Ferry, N. J.

CORRESPONDENCE COURSES

SIMPLIFIED Radio Repairing Instructions. Only $1.00. Slate's Radio Service, Corsicana, Texas.

USED Correspondence Courses and Educational Books Bought, Sold, Rented. Catalog Free. Educational Exchange, Summerville, Ga.

AMATEUR radio is fun. Fifty pages, easy to understand, code and theory for Novice Class license. $1.00. Satisfaction guaranteed. Radiographic, 3246 North Orange, Chicago, Ill.

USED correspondence Courses and Books sold and rented. Money back guarantee. Catalog free. (Courses bought.) Lee Mountain, Pisgah, Ala.

BUSINESS OPPORTUNITIES

BUY Wholesale 25,000 items, Catalog 25c. Matthews, 1472-R5 Broadway, N. Y. C. 36.

SITUATIONS WANTED

ARMY officer, release in Feb. 1954, seeking position as engineering rep., sales eng., etc. Foreign assignment preferred. 5 years military and civilian experience in electronics, including design and supervision. Box 539, Radio & TV News, 366 Madison Ave., New York, N. Y.

MISCELLANEOUS

SPEAKERS repaired, wholesale, guaranteed. Jobbers wanted. Amprite Speaker Service, 70 Vesey St., New York City 7.


FREE money saving bargain list. 10 MFD/600WV Oil Capacitor 98c; RCA 3AP1A $4.95; add postage. Mark Electronic, 1888 Randell Ave., Bronx 72, N. Y.

TAPE Recording Exchange for education, amusement. Foreign Members. World Tape Pals, Box 9211, Dallas, Texas.

THE Audiophile Bulletin, monthly confidential consumer hi-fi equipment reports. Year's subscription $2.00. Department D, 1379 East 15th, Brooklyn 30, N. Y.

Let MILTON S. KIVER Help You Prepare For U.H.F.-TV, Color And...

TELEVISION SERVICING

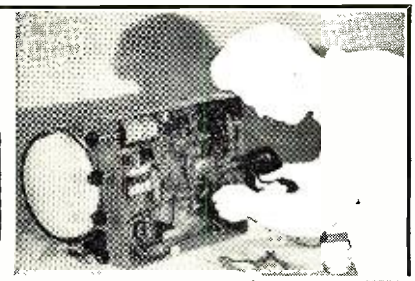

Easy to TRAIN AT HOME This Practical Way!

Men with the right training in Television Servicing are in big demand . . . pull down big pay. T.C.I. TRAINS YOU RIGHT with easy-to-follow technical training designed *by* servicemen, *for* servicemen! You learn practical, professional type Television Servicing without leaving your present job. Included are money-making extras such as set conversion, master antenna installation, U.H.F.-TV NTSC Color System and field servicing short cuts. You can start earning Television money after the first few lessons. You learn to test, trouble shoot and repair all types of TV sets the proven, *practical* way!

HERE'S HOW YOU GET EXPERIENCE!

You train on your own large screen modern television receiver, furnished as part of your course. This set is yours to keep! As an optional feature you can get two weeks of actual field experience out on service jobs and on the repair bench for Chicago's largest independent servicing organization. You learn Television Servicing by *actually doing* Television Servicing . . . you get the *practical* know-how you need to qualify for BIG MONEY in this fast-growing field! **Age is no barrier. Many TCI students are over 40!**

YOU GET and keep modern large screen Television receiver.

YOU DO actual testing, servicing, trouble shooting and repairing

BEGINNERS! LEARN ABOUT NEW BASIC TV COURSE! You don't need radio experience for practical, home-study training in Basic Television. Start earning money in TV after first few easy lessons. Check coupon for details.

VETERANS! T.C.I. is approved for G.I. training under Public Law 550. Check coupon.

ACT NOW! Mail coupon for FREE Catalog and SAMPLE LESSON. Write TODAY!

TELEVISION COMMUNICATIONS INSTITUTE

605 W. Washington Blvd., Dept. AX, Chicago 6, Ill.

MAIL NOW FOR FREE BOOKLET

MILTON S. KIVER, President
TELEVISION COMMUNICATIONS INSTITUTE
605 W. Washington Blvd., Dept. AX
Chicago 6, Ill.

Rush full facts on practical TV training. I am not obligated. Salesman will not call.

Name ..... ☐ Veterans: check here

Address .....

City ..... Zone.... State.....

☐ BEGINNERS check here for information on Basic Television Course.

New 2nd Edition Covers Transistors, Latest Data on AM-FM Receivers, and Up-to-date Material on the New Radio Tubes!

RADIO SERVICING



by ABRAHAM MARCUS
co-author of famous "Elements of Radio" which has sold over 800,000 copies!

Here is every up-to-date detail you need to know about radio repair, replacement, and readjustment. Easy-to-understand, step-by-step self-training handbook shows you how to locate and remedy defects quickly.

Covers: TRF Receivers; Superheterodyne Receivers; Short-Wave Receivers and Converters; Multiband Receivers; Portable Receivers; Automobile Receivers; Communication Receivers; F-M Receivers; Power Supplies operated from AC, DC, Batteries, Motor-Generators, etc. Tells you the HOW and WHY of: **Electron Tubes** (Diode, Triode, Pentode, Beam Power, Thyratron, Phototube, Cathode Ray, etc.); **Rectifier Circuits** (Half-wave, Full-wave, Bridge, Voltage-Doubler, etc.). **Detector Circuits** (Diode, Triode, Regenerative, Superregenerative, Infinite-Impedance, etc.); **Amplifier Circuits** (Audio, Radio, I-F, Video, D-C, etc.); **Oscillator Circuits** (Hartley, Colpitts, Crystal Transitron, Multivibrator, Sweep-circuit etc.). **Control Circuits** (Volume, AVC, DAVC, Tone, Noise-Suppression, Automatic Tuning, Automatic Frequency Control, etc.). Explains how to use **testing instruments** such as: meter, vacuum-tube voltmeters, ohmmeters, bridges, multimeters, signal generators, tube checkers, cathode-ray oscilloscopes, etc. Over 100 pages and 69 illustrations in this section alone!

All in one big volume — easy to read. 16 Big Chapters. 121 Sections. 400 "Show-How" Diagrams. 775 pages.

Get this authoritative radio repair handbook today! Coupon below brings you "Radio Servicing" on FREE trial for 10 days. Mail it NOW.

PRENTICE-HALL, Inc., Dept. M-RTN.254
70 Fifth Ave., New York 11, N. Y.

Send me, for 10 DAYS' FREE TRIAL, "Radio Servicing—2nd Edition," by Abraham Marcus. I will return it in ten days and pay nothing—or keep it and send $1.95 down (plus postage) and $2 monthly for 2 months.


Name .....

Address .....

City ..... State .....

( ) SAVE! Send $5.95 WITH COUPON—we pay postage.

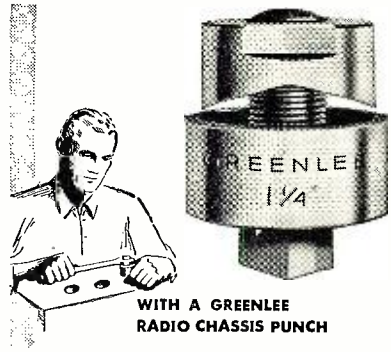CUT HOLES 1/2" to 3 1/2" IN RADIO CHASSIS



WITH A GREENLEE RADIO CHASSIS PUNCH

● Save hours of work . . . no reaming or tedious filing. Punch cuts through chassis quickly . . . makes accurate, clean holes for sockets, plugs, and other receptacles. Just turn with an ordinary wrench. There's a GREENLEE Punch in each of these sizes: ½"; ⅝"; ¾"; ⅞"; 1"; 1 1/16"; 1 1/8"; 1 3/32"; 1 3/16"; 1 1/4"; 1 3/8"; 1 1/2"; 1 5/8"; 1 3/4"; 1 7/8"; 2"; 2 1/4". Write for facts. Also get information on Knockout Punches and Cutters for conduit and meter holes up to 3½". Greenlee Tool Co., 1882 Columbia Avenue, Rockford, Illinois.

TOOLS FOR CRAFTSMEN
GREENLEE

www.americanradiohistory.com

100 WATT SEC PHOTOFLASH KIT



Includes DX Flash Lamp Rated 150 Watt Sec. Flash Lamp Holder & 8" Reflector & Cable. Power Trans & "CD" Condensers (2) 525MFD/450V 100Watt Sec. Resistors. Capacitors. Rectifiers & Sockets....$36.98

100 Watt Second Condenser Bank .72MFD/1800V per unit/85 units equals 61.2MFD/100 W.S. SPEC. ..$6.98
525MFD 450V "CD"...$8.00; 2 for $15
16MFD/600VAC 1800VDC/2800V Intermittent C'dubilier $5.95
WRITE FOR DETAILS & SPECIAL PRICES


PHOTOFLASH LAMPS

"Tab" No.	Replaces	W-Sec Max.	Each
U5W	SPRG/FA104	150	$5.98
U10	GE FT114	100	7.25
No. 1	AMGLO 5804X	100	10.98
23ST	GE FT 210	200	9.98
VA	SYL. 4330	200	9.98
22ST	FT 110	200	9.98
V4X4	X400	200	10.98
DX	SPRGFA100	150	9.00

T2FD ANTENNA RESISTOR

Described in **CQ FEB 53** Globar Non-Inductive "RF" Resistor. Rated 400 Ohm 250 Watt or 350 Ohm with mgt. clips.
"TAB" SPECIAL.....$2.25; 3 for $5.98

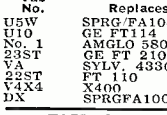NEW "LENK" 180 Watt Perfect Balance SOLDERING GUN



No other soldering gun offers all these features at any price. 115VAC 180 Watt, light weight 28 ozs., melts solder 3½ seconds. swivel 180 deg. tip. Special Alloy Korodless Tip. Heavy Duty Transformer. Beam Focus Light. Luger Pistol Feel.
"TAB" SPECIAL.....$7.45

TV & COAX CABLE

300 Ohm Twinex. 100 feet $1.39
1000 foot reel $11.95
RG59U 73 ohm TV Coax Cable MFGRD to rigid **UHF** specs.
per ft. 5c; 100 feet $4.50
SPECIAL 500 feet ...$22.00



CRYSTAL DIODES

1N21—Lots of 100...40c ea.
SMALLER QTY. 85c; 10 for $5.00
KEMTRON—W.E.—SYLVANIA

1N23B	$2.25; 5 for $10.00
1N21A	$1.55; 5 for $ 7.00
1N21B	$2.89; 4 for $10.00
1N27	$1.55; 5 for $ 7.00
1N46	69c; 5 for $ 3.25

ONE YEAR GTD PICTURE TUBES

7JP4 Hytron	$17.95
10 BP4	10.00
12" Glass	12.00
14" Rectangular	14.00
16" Glass	16.00
17" Rectangular	19.00
19" Round	19.00
20" Rectangular	20.00
21" Rectangular	21.00
24" Hytron	74.95
27" Hytron	89.95

Send your old tube prepaid only, and we will ship one year guaranteed Picture Tubes at above prices. No dud return required for 7", 24", 27" tubes. Prices based on $1.00 per inch. Metal or Electrostatic tubes add 10¢ per inch additional. Prices FOB NYC.

CONDENSER SPECIALS



2 MFD 1000 VDC 330 VAC "CD" MFGR 25c Lots of 10

Smaller Quantities, each..49c; 3 for $1.25

OIL CONDENSERS WAREHOUSE CLEARANCE SALE


RECTANGULAR CASE

.5MFD	150VDC.....95c; 2 for	$1.50
5MFD	600VDC.....1.50; 3 for	4.00
10MFD	600VDC.....1.98; 2 for	3.50
2x2MFD	330VAC 1000VDC.49c; 3 for	1.20
2x2MFD	600VDC/VIT "Q".1.25; 2 for	2.00

BATHTUB SIDE TERMINALS

1MFD	600VDC.....39c; 3 for	1.00
4MFD	50VDC.....50c; 5 for	2.00
2x.1MFD	400VDC.....49c; 5 for	2.00

OIL CONDENSER SPECIAL

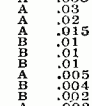

2 MFD 600 VDC

Aerovox Type PO9. Steatite insulators. Adjustable Mounting Clamp. Case 2" Dia. x 2⅜" High. Brand New. Special ...69c; 3 for $1.50

STORAGE BATTERIES

36 V Willard Mini—Brand New: 5 oz. Designed Port. Equip Models.98c; 4 for $3
/4/36V Batteries w/acid*.....$3.35
2V/20AH Willard PLUS 2V. Vibrator .98
2V/20AH w/vib & acid*.....3.59
6V/6AH Willard NT6/BB214U.....2.98
6V/6AH Battery w/acid*.....3.25
6V/40AH Battery 6.98
6V/40AH Battery w/acid*.....9.25
*We ship acid in bottles, R exp. only.

MICA CONDENSERS



Fig.	MFD	WVDC	PRICE
A	.033	600	69c; 5 for $2.50
A	.03	600	69c; 5 for 2.39
A	.02	600	69c; 5 for 2.25
A	.015	2500	1.75; 2 for 3.00
B	.01	600	56c; 3 for 1.20
B	.01	1000	49c; 3 for 1.25
B	.01	1200	69c; 3 for 1.49
A	.0005	2500	1.19; 3 for 2.95
B	.004	600	49c; 3 for 1.10
B	.002	1200	58c; 3 for 1.25
A	.002	2500	98c; 3 for 2.25
A	.001	1200	55c; 3 for 1.20
C	.0007	3000	89c; 3 for 2.39
A	.0004	2500	39c; 6 for 1.95
A	.0001	600	25c; 5 for 1.00
C	.0001	3000	89c; 3 for 2.00
C	.0001	5000	1.49; 4 for 5.00
C	.00005	3000	39c; 4 for 1.00

WRITE FOR QUANTITY PRICE

"TAB" THAT'S A BUY

INFRARED SNOOPERSCOPE

SEE-IN-DARK TUBE

Image-Converter Tube HiSensitivity simplified design 2" dia. Willemite screen—data & tube, ea. ..$7.98; 2 for $13.98
SNOOPERSCOPE PWR SUPPLY
1800VDC/35MA Using Doubler Crkt. Transformer, Rectifiers Sockets. Resistors. Capacitors and Diagram $6.98


VARIABLE VOLTAGE TRANSFORMER

POWERSTAT—GR—STACO



#10/132V/1.25A/LN	$ 7.98
#20/0-135V/3A/LN.	11.25
#116/135V/7.5A/LN	20.70
#116U/135V/7.5A/LN	16.20
#116/270V/3A/LN.	23.40
#216U/270V/3A/LN	18.00
#1126/135V/15A/LN	41.98
#1226/270V/9A/LN.	41.98
GR50A/0-135V/45A/LN	100.00
GR50B/0-270V/31A/LN	115.00
3000B/0-135V/30A/* CASED	55.00
3000BU/0-135V/30A/* UNCASED	49.00
3020BU/0-270V/15A/* UNCASED	49.00
3020B/0-270V/15A/* CASED	55.00
STACO (RLS/METERED/140V/5A	41.50
STACO/PAL-7/METERED/135V/7.5A (LN) LIKE NEW COMPLETE GTD.	40.50

LABORATORY PWR SUPPLY

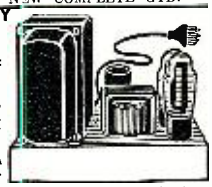

- Sola Constant Voltage Xfmr
- Mfr Dumont
- Brand New
- 400VDC/250 MA & 5V/6A 3%, Regulated
- 12.6VCT/6A or 2X6.3V/6A common tap.
- 105-129VAC

Complete with Filter Condensers, Chokes, & Rectifier Tubes. $59.00 Value.
"TAB" SPECIAL $18.98

RHEOSTAT SPECIALS

15 ohm 25W w/knob	$1.49; 2 for $2.49
20 ohm 50W Model J	1.98; 2 for 3.50
60 ohm 50W w/knob	2.25; 2 for 3.98
100 ohm 50W Model K	1.98; 2 for 3.50
250 ohm 25W	1.19; 3 for 2.98
300 ohm 225W Model P	2.98; 2 for 5.00
350, 500, 5000 ohm Slotted shaft, 25 watt	79c; 3 for 2.00

TACHOMETER GENERATOR



MARK V STUD MTG GENERAL ELECTRIC
Part #2CM5-AAK-20. Write for quantity price. Brand New Original Carton.
$3.98

DC POWER SUPPLY




0 to 12 VDC/2 Amp. Variable DC supply, completely built—inpt. 115V/60 cy. Usable LAB supply. filament D.C. plating, battery charging, model railroad, includes voltage or speed control and center off reversing sw. Prepaid to Your Door **U.S.A.** "TAB" SPECIAL ...$10.95; 2 for $20.00

FEDERAL "ITT" SELENIUM BATTERY CHARGER RECTIFIER

10-0-10V (CT) 100 Amp., fan cooled. Replace your old inefficient sulfide rectifier w/new selenium type. SPECIAL...$11.98

SELENIUM RECTIFIERS

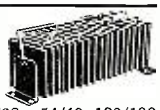

We specialize in Rectifiers and Power supplies to specifications. Immediate delivery.

Current (cont.)	18 14 Volts	36/28 Volts	54/40 Volts	130/100 Volts
1AMP	1.35	2.15	3.70	8.50
2AMP	2.20	3.60	5.40	10.50
4AMP	4.25	7.50	9.00	25.25
6AMP	4.75	9.00	13.50	33.00
10AMP	6.75	12.75	20.00	44.95
12AMP	8.50	16.25	25.50	49.00
20AMP	13.25	25.50	39.00	87.50
24AMP	15.75	32.50	45.00	95.00

Full Wave Rectifier & Transformer

All 115V/60 cy inputs

up to 14VDC at 12 amps	$19.98
up to 28VDC at 4 amps	14.98
up to 28VDC at 12 amps	29.98
up to 28VDC at 24 amps	59.95
up to 28VDC at 50 amps	127.00

RECTIFIER XFMR



PRIMARY 115V., 60 cycle.

SECONDARY 0-9-12-18-24-36V	
4 Amp	$8.75
12 Amp	16.75
24 Amp	35.75
30-32-34-36V/48Amp	59.75

RECTIFIER CHOKES

4 Amp .07	Hy .6	Ohm	$7.95
12 Amp .01	Hy .1	Ohm	14.95
24 Amp .004	Hy .025	Ohm	29.95

WAREHOUSE CLEARANCE

ANTENNA Mast Sections MS49 & MS50. 3 FT. EACH SECT .2 for 49c; 25 for $3
VEEDER ROOT Counter 3-Dig. 85c; 3 for $2
RF CHOKE 2½MH/300MA, 29c; 10 for $2
BAND PASS Filt 60, 90, 150 cy., 3 at $4
SHOCK MOUNT 45 lbs. 39c; 4 for $1.00
CHASSIS Amplifier, Punched, 9x3½x1¼"H. 5 for $1.00
RF CHOKE 20MH/200MA. 39c; 6 for $2
FILTER G.E. 100Amp 50V. $1.98; 2 at $3

NEW YORK CITY SERVICEMEN

"TAB" PAYS YOUR SUBWAY FARE.
FREE: 2 SUBWAY TOKENS WITH ANY $5.00 STORE PURCHASE.

TUBES

"TAB" TESTED & GUARANTEED
PRICES SUBJECT TO CHANGE
WRITE FOR COMPLETE LISTING

0A2	$0.88	3D22	13.97	6SQ7GT	.62	81	1.38	829	7.94
0A3/VR75	1.04	3D23	4.90	6SR7	.62	83	1.12	829B	12.48
0B2	1.37	3E29	14.95	6SS7	.88	83V	1.12	832	7.72
0B3/VR90	.96	4C35	21.49	6SU7GTY	2.69	84/6Z4	.62	832A	9.92
0C3/VR105	.92	4D21	18.99	6T8	.96	100TH	9.88	833A	39.45
0D3/VR150	.92	4E27	22.49	6U4	.74	FG105	19.48	834	5.95
1B3/8016	.80	4J22	129.51	6U8	.98	117L7/M7GT	1.98	836	5.95
1B22	1.49	4J31	99.51	6V6	1.39	117Z6GT	.96	837	1.42
1B23	8.87	4J52	199.99	6V6GT	.59	CV148	7.98	849	29.45
1B24	8.98	EL5BHD	15.99	6W4GT	.52	FG166	48.49	860	4.48
1B26	2.24	5C21/C6J	9.89	6X5GT	.54	FG172	29.00	861	22.48
1B27	11.98	5C22	38.95	6Y6G	.88	250TH	18.97	865	1.26
1B32/532A	2.48	5D21	14.98	7A8	.68	250TL	17.75	866A	1.50
1B35	9.15	5J29	11.92	7C7	.76	304TH	8.90	872A	3.29
1B37	14.87	5R4GY	1.20	7F7	.82	304TL	8.90	CK1005	.68
1B38	29.47	5R4GYW	1.75	7F8	1.24	388A	1.48	1613	.82
1B41	49.95	5U4	.55	7H7	.72	WL417A	8.48	1614	1.95
1B42	17.48	5V4G	.95	7N7	.92	417A/		1619	.36
1B46	1.98	5Y3GT	.43	7V7	1.06	5842	18.50	1625	.98
1B63	45.00	6AG5	.71	7Y4	.68	GL434A	12.59	1632	.68
1D21/SN4	3.80	6AH4	1.14	8D21	298.00	446B	3.48	1633	.98
1L4	.48	6AH6	1.22	12A6	.48	450TH	49.97	1634	1.18
1L6	1.35	6AJ5	1.40	12AH7GT	1.45	450TL	52.00	1635	1.18
1LD5	.98	6AK5	.77	12AL5	.54	460/		1636	3.08
1LN5	.71	6AK6	.92	12AT6	.89	HF200	15.95	1642	.62
1P5	.78	6AL5	.48	12AT7	.89	CK502AX	1.49	1644	.92
1P21	33.00	6AL7GT	.98	12AU6	.72	CK503AX	1.49	2050	1.48
1U4	.59	6AN5	2.90	12AU7	.69	CK505AX	1.79	2050W	2.48
1U5	.58	6AQ5	.52	12AV6	.52	CK512AX	1.45	5654	1.72
1X2A	.98	6AQ6	.81	12AV7	.98	CK531DX	1.89	5670	3.44
2A4G	1.18	6AQ7GT	1.29	12AW6	1.18	531	5.72	CK5672	1.20
2C36	27.00	6AR6	2.98	12AX7	.98	CK532DX	1.89	CK5678	1.28
2C39A	26.98	6AS7G	3.48	12AY7	1.69	CK533AX	1.29	5687	3.74
2C40	7.50	6AT6	.54	12BA6	.59	CK534AX	.99	CK5702	2.90
2C43	17.48	6AU5GT	1.10	12BA7	.94	CK536AX	.99	CK5703	1.29
2C44	1.15	6AU6	.58	12BD6	.59	CK540AX	.99	5713	120.00
2C51	3.88	6AV5GT	.98	12BE6	.59	CK541DX	1.99	5812	2.99
2D21	1.19	6AW6	.49	12BF6	.85	CK5390X	2.19	5814	2.08
2E31	1.49	6AW8	1.09	12BH7	1.29	CK541DX	1.99	5840	7.98
2E43	1.49	6B4G	1.18	12SA7GT	.68	CK543DX	.99	8012	2.98
2J31	27.00	6BA6	.54	12SC7	1.08	CK544DX	.99	8013A	3.92
2J32	29.48	6BA7	1.59	12SF7GT	.84	CK546DX	1.99	8025A	4.68
2J33	27.00	6BC5	.63	12SG7	.80	CK571AX/		9001	1.12
2J34	24.98	6BC7	1.23	12SH7	.63	5886	2.49	9002	.55
2J37	12.70	6BD6	.83	12SJ7	.54	CK573AX/		9003	1.12
2J38	69.18	6BE6	.54	12SK7	.66	6029	3.49		
2J39	6.98	6BF5	.98	12SL7GT	.62	WL676	34.98		
2J42	148.98	6BG6G	1.58	12SN7GT	.68	703A	4.72	**XTAL DIODES**	
2J48	24.45	6BH6	.63	12SQ7GT	.54	705A	1.88		
2J49	84.97	6BJ6	.98	12SR7	.66	707B	14.88	1N21A	1.55
2J50	99.9H	6BK7	1.58	FG17	3.90	707B	14.88	1N21B	1.92
2J51	238.98	6BL7GT	1.19	24G/3C24	1.32	715A	4.96	1N22	1.22
2J55	84.98	6BN7	2.69	25BQ6GT	.98	715B	7.94	1N23	1.35
2J56	149.98	6BQ6GT	1.20	25L6GT	.58	717A	17.98	1N23A	1.98
2J62	49.45	6BQ7	1.65	25Z5	.78	719A	24.48	1N23B	2.22
2K22	23.48	6C21	24.50	25Z6GT	.58	721A	3.92	1N25	4.98
2K23	11.48	6C4	.52	FG27A	8.24	723A	1.94	1N26	8.75
2K25	28.49	6C5	.68	35B5	1.94	723A/287	1.94	1N27	1.55
2K25/		6C8G	.99	35B5	.52	723A/B	16.98	1N34	.64
723AB	23.88	6CD6G	1.69	35L6	.58	724A	3.95	1N34A	.99
2K28	27.48	6D4	2.70	35T	4.88	724B	2.74	1N35	1.65
2K29	22.88	C6J/5C21	9.89	35Y4	.68	724B	14.48	1N38A	1.29
2K33	219.98	6J4	6.50	35Z5	.54	726A	14.48	1N41	8.95
2K39	134.99	6J5	.54	41	.72	726B	44.88	1N42	15.00
2K41	126.00	6J6	.58	42	.68	726C	64.88	1N43	1.73
2K48	99.48	6K4A	3.68	45Z3	.88	801A	2.62	1N45	1.45
2K50	4.42	6L6	1.98	50A5	.98	803	3.48	1N46	.69
3B22	2.48	6L6G	1.08	50A5	.76	805	3.22	1N47	4.00
3B23/RK22	4.95	6L6GA	1.08	50B5	.54	807	1.54	1N48	.55
3B24	4.70	6L6GAY	1.98	50C5	.54	808	3.62	1N51	.45
3B25	4.30	6L7GT	.68	50L6GT	.62	810	9.58	1N54	.78
3B26	3.70	6SC7	.90	RK61/		810	10.88	1N54A	1.79
3B28	7.90	6SF5	.78	XFG1	2.65	811	3.00	1N58A	1.15
3C22	85.00	6SG7	.64	FG67	14.68	812	2.70	1N60	.60
3C23	8.67	6SH7	.61	HY69	4.98	813	11.48	1N63/K63	2.49
3C31/C1B	7.45	6SJ7	.58	71A	.74	814	4.98	1N64	.69
3C33	9.51	6SK7GT	.56	75	.64	815	5.98	1N69	.98
3C45	9.98	6SL7GT	.64	78	.58	826	.95		
3D21A	8.15	6SN7GT	.68	80	.58	828	11.29		

TUBE SPECIALS

YOU PICK THEM 39c EA.

Lots of 10
Cracked Base or Broken Key
Electrically Perfect
Tested & 90 Day Guaranteed
6SN7; 5Y3GT; 5U4G; 6V6GT; 6K6GT; 6W4GT; 6BQ6; 12SA7GT; 25L6GT; 25BQ6GT; 6H6; 12SG7.
ORDER NOW. WHILE THEY LAST

PRECISION OILER OR CARBON TET DISPENSER



Indispensable for the Laboratory or Service Shop. Designed for Pin Point Oiling, or When Using Carbon Tet. For Quieting & Cleaning Controls. A Precision Made Needle Point Permits Use on the Most Delicate Lubrication Job. SUPPLIED WITH OIL.
"TAB" SPECIAL .....89c; 6 for $5.00

SPECIAL HI-FI AMPS

TAB308 PRE-AMP & PWR AMP 8 WATT. 20 to 20KC. SIMILAR "GROMMES" LJ2 LITTLE JEWEL.....$32.25
TAB310 PRE-AMP & PWR AMP 10 WATT. 20 to 20KC. SIMILAR "GROMMES" SPEC'S 50-PG-3 .....$48.50
TAB315 PRE-AMP & PWR AMP 24 WATT. 10 to 100KC. WILLIAMSON DSGN SIM "GROMMES" 215BA $87.75
TAB5AP PRE-AMP RELUCT G.E. CART $10.25
TAB-RC1 RECORD COMPENSATOR..$9.50
Write for Amplifier Catalog

AUDIO AMPLIFIERS READY TO GO



Model AMP5 Hi-Fi 5 Watt AC amplifier, plus built-in Pre Amp **GE** V.R. pick-up. 60 to 18000 cps/1DB down 40 DB 40 cys. Hum Level —55DB. Mike & Phone Volume. Continuous Bass Treble Controls. 6SJ7. 6SC7. 6V6. 6X5 Not Shown. "TAB" special to your door. Ppd..$21.39
Same unit less GE Pre Amp. Prepaid **15.98**

AUDIO COMPONENTS



GE RPX041	Cart. Gold Tone $5.25
GE RPX-052	Triplay Diamond & Sapphire....17.75
GE RPX050	Triple Play Cart 4.98
Electrovoice	Triple Play.. 1.08
GE RPJ010	Dual .001" & .003" Sap. 1.98
GE RPJ005	Single .001" Sapphire... 1.35
GE RPJ001	Single .003" Sapphire... 1.35
GE RPJ004	Single .001" Diamond...11.98
GE RPJ013	Dual Diamond & Sapphire.12.98

"ZIMPHONE" INTERCOM 2 PHONE SET




PREPAID* CLEARAS A BELL

Performs loud & clear, just like your telephone. Hear even whispers, built-in signaling buzzer, oper. up to 1 mile. Set includes: 2 phones, wall brackets, 50 ft. wire, batteries, makers 1-year gtd.
"TAB" SPECIAL. Prepaid **USA** ..$5.98
Less Signal Buzzer Prepaid **$4.39**

FILAMENT TRANS.


6.3V/2AMP	$1.08; 2 for $1.98
2.5V/2A @ 79c; 2 for	$1.49; 10 for 6.49
2.5VCT/10A	15KVins @ $6.98; 3 for $18.
2.5VCT/10A	5KVins 3.59
7.5VCT/12A	15KVins @ $10.95; 2 for $17.50
24V/1.25A	CSD @ $1.98; two for... 3.49

TRANSFORMERS

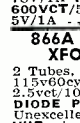

All 115 V 60 Cyc Input TV & CR Pwr Xmfr up to 20" tubes. Hi VOLTS to 20 KV (w/quadrupler ckt.) ALL Tubes. PL & FIL wndgs 300 VDC 275Ma Full-Wave: 6.4V/10.3A, 5.4V/8A, 2.5V/3A Hypersil Core. Oil Impreg.....$4.98; 2 for $9.00
1000VCT/45MA, 795VCT/80MA. 360VCT/55MA. 3X5V/3A. 6.3VCT/1A. 6.3VCT/.3A CSD HVNS CAN BE USED 2X RATING RAYTHEON HYPERSIL CORE.....$4.50
900V/35MA, 2X2.5V/2A. XCLENT 1800V DBLER TWO 2X2 FIL WNDGS.....$2.25
850VCT/148MA 5V/3A. 6.3/5A. 6.3V/3A .....$4.98; 2 for $9.00
800VCT/150MA .....$4.98; 3 for $12.00
778VCT/200MA, 5V/3A. 6.3VCT/5A Thordarson Mfgr.....$4.98; 2 for $9.00
780VCT/250MA, 5V/6A. 12.6V/5.5A $7.95
770VCT/200MA, 5V/6A. 12.6V/5.5A $6.95
700VCT/120MA, 2X6.3V/3A. 6.3V/1A Price .....$3.98; two for $7.25
680VCT/200MA, 5V/3.5A. 6.3V/4A. 78V/1A .....$4.39; 3 for $12
600VCT/50MA. 6V/3A. 6V/1.5A. 5V/1A $2.49

866A KIT and XFORMER

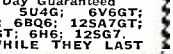

2 Tubes, Sckts. xmfr. 115v60cyc Input. output 2.5vct/10A/Hvt 5KV **DIODE PROBE TUBE** Unexcelled for No-Loss **VHF** testing. New. w/data VR92 .....25c; 5 for $1

FILTER CHOKES

Check These Reduced Low Prices

12Hy/80Ma/HVSil/3KVins	$2.25
50Hy/125ma/Csd/HVSil	2.89
20Hy/300ma or 15Hy/400ma/12KVins	8.95
13.5 HY 1 Amp./17KVins/Raytheon	39.95
Dual 2HY/300ma. USN	95c; 2 for 1.49
10HY 100 MA Freed	1.39
3HY 40ma UTC Hi "Q"	95c; 2 for 1.39

Money Back Guarantee (Cost of Mdse. Only) $5 Min. Order F.O.B. N.Y.C. Add Shpg. Charges or 25% Dep. Tubes Gtd. via R-Exp. only. Prices subject to Change. Rector 2-6245
CABLE: "TABPARTS"

"TAB" THAT'S A BUY

DEPT. 2RN — 111 LIBERTY STREET — NEW YORK 6, N. Y., U. S. A.

PRINTED IN U.S.A.

www.americanradiohistory.com

Decide on DuMont

on the basis of...



Microscopic look at the cathode surface reveals soft, even texture, necessary for efficient tube performance

Product Superiority

not too wet, not too dry—
not too light or heavy...

THE CATHODE plays an important role as source of electron energy in the picture tube. Moisture content and texture of the cathode coating must meet rigid standards to insure maximum picture tube life.

At Du Mont, exclusive processes are used for applying the cathode substance. The soft even texture achieved (see illustration) packs the effective emitting area (in circle) with extra electron power.

The resulting brighter performance over maximum tube life tells you why Du Mont is the right replacement for any set.



*Trade-mark

REPLACEMENT SALES, CATHODE-RAY TUBE DIVISION • ALLEN B. DU MONT LABORATORIES, INC., CLIFTON, N.J.

www.americanradiohistory.com

None... in a Million

A well-known TV and radio set manufacturer reports not one field reject during a 12-month period in which he used over 1,000,000 Mallory FP Capacitors. Yes, it's hard to believe but it happened. And it's

Proof Positive of Mallory Capacitor Dependability

Odds are staggering against such a record but they are all on your side . . . if you use Mallory Capacitors.

You can bet your bottom dollar that jobs *stay* done when you install Mallory Capacitors. That means no loss of time and money on call-backs!

Don't miss a sure thing. The Mallory FP Capacitor line is complete. There's a rating for every set. They are the only Fabricated Plate Capacitors on the replacement market. And they cost no more than ordinary capacitors.

And be sure to use Mallory Plascaps® for plastic tubular replacements. Permanently secured leads . . . no off-center cartridges . . . no premature shorts.

Prove to yourself what manufacturers and thousands of servicemen know — YOU CAN ALWAYS DEPEND ON MALLORY CAPACITORS.



P.R. MALLORY & CO. Inc.

MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
RECTIFIERS • POWER SUPPLIES • FILTERS • MERCURY BATTERIES

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

www.americanradiohistory.com